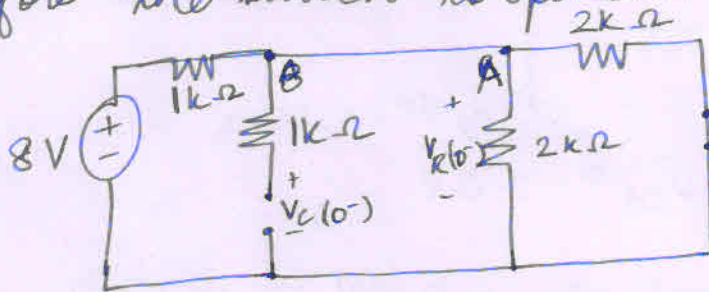


Assignment 3 SolutionsAns 1. Before the switch is opened:

applying nodal at node B,

$$\frac{V_C(0^-) - 8}{1} + \frac{V_C(0^-)}{2} + \frac{V_C(0^-)}{2} = 0$$


$$\Rightarrow V_C(0^-) = 4V = V_C(0^+) = V_R(0^-)$$

$$i_L(0^-) = \frac{4}{2} \text{ mA} = 2 \text{ mA} = i_L(0^+)$$

at  $t = 0^+$ : It is a source free circuit.

$$\therefore \tau = \frac{L}{R} = \frac{1H}{4k} = 0.25 \text{ ms}$$

$$\begin{aligned} \therefore V_R(t) \Big|_{t \geq 0} &= -i_L(t \geq 0) \cdot 2k \text{ V} \\ &= -2k \times i_L(0^+) e^{-t/\tau} \text{ V} \\ &= -2 \times 2 e^{-4t} \text{ V} \\ &= -4e^{-4t} \text{ V} \end{aligned}$$

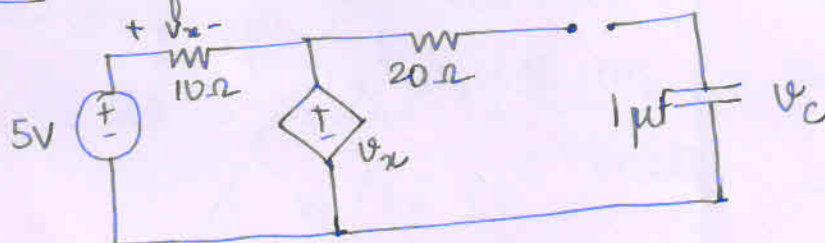
Ans 2. Before the switch is closed:

applying KVL in the first loop,

$$5 - V_x - V_C = 0$$

$$\text{or } V_x = 2.5 \text{ V}$$

after the switch is closed:

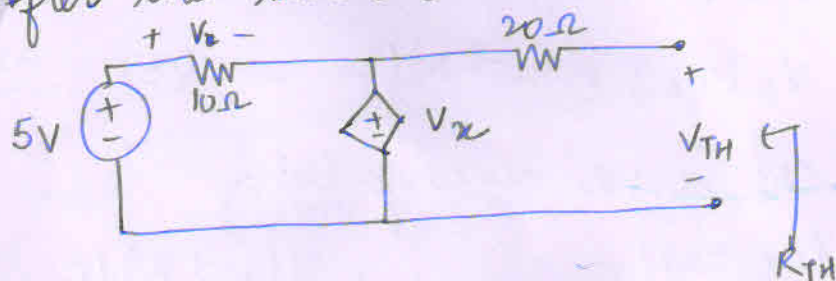

Thevenin voltage,

$$V_{TH} = 2.5V$$



Short circuit current =  $I_{sc} = \frac{2.5}{20} A = 125mA$

$$\therefore R_{TH} = \frac{2.5V}{125mA} = 20\Omega$$

$$\therefore \tau = 20 \times 10^{-6} s = 20\mu s$$

$$\begin{aligned} \therefore V_c(t) &= V_c(\infty) + [V_c(0) - V_c(\infty)] e^{-t/\tau} \\ &= 2.5 + (0 - 2.5) e^{-t/2 \times 10^{-5}} V \\ &= 2.5(1 - e^{-t/2 \times 10^{-5}}) V \end{aligned}$$

Ans 3.

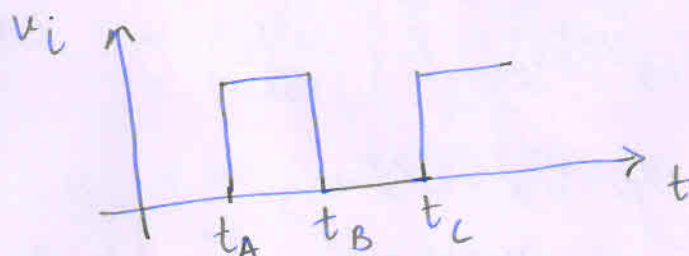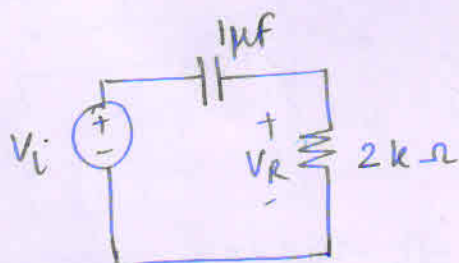

$$\tau = RC = 10^{-6} \times 2 \times 10^3 s = 2ms$$

$$V_{max} = 1V, V_{min} = 0V$$

Charging cycle:  $t_A < t < t_B$

$$\begin{aligned} V_c(t) &= V_{max} + [V_c(t_A^-) - V_{max}] e^{-\frac{1}{\tau}(t-t_A)} \\ &= 1 + [V_c(t_A^-) - 1] e^{-\frac{1}{\tau}(t-t_A)} \quad \text{--- (1)} \end{aligned}$$

Discharging cycle:  $t_B < t < t_C$

$$\begin{aligned} V_c(t) &= V_{min} + [V_c(t_B^-) - V_{min}] e^{-\frac{1}{\tau}(t-t_B)} \\ &= V_c(t_B^-) e^{-\frac{1}{\tau}(t-t_B)} \quad \text{--- (2)} \end{aligned}$$

In steady state,

$$V_c(t_A) = V_c(t_C)$$

Inserting this condition in equations (1) and (2)

$$\therefore V_C(t_B) = V_C(t_A) e^{(t_C - t_B)/\tau} \quad (3)$$

Put  $t = t_B$  in (1) and (2) and using (3),

$$1 + [V_C(t_A) - 1] e^{-(t_B - t_A)/\tau} = V_C(t_A) e^{(t_C - t_B)/\tau}$$

$$\therefore V_C(t_A) = \frac{1 - e^{-(t_B - t_A)/\tau}}{e^{(t_C - t_B)/\tau} - e^{-(t_B - t_A)/\tau}}$$

$$t_B - t_A = 2\text{ms and } t_C - t_B = 2\text{ms}$$

$$\therefore V_C(t_A) = \frac{e - 1}{e^2 - 1} = 0.269\text{V}$$

$$V_C(t_B) = 0.731\text{V}$$

$$\therefore V_R(t) = R \left( C \frac{dV_C}{dt} \right) = \tau \frac{dV_C}{dt}$$

$$V_C \quad t_A < t < t_B:$$

$$V_C(t) = 1 + [V_C(t_A) - 1] e^{-(t - t_A)/\tau}$$

$$t_B < t < t_C$$

$$V_C(t) = V_C(t_A) e^{-(t - t_C)/\tau}$$

$$\therefore t_A < t < t_B:$$

$$V_R(t) = -\frac{1}{\tau} [V_C(t_A) - 1] e^{-(t - t_A)/\tau} = -0.731 e^{-(t - t_A)/\tau}$$


$$[\tau = 2\text{ms}]$$

$$t_B < t < t_C:$$

$$V_R(t) = -\frac{1}{\tau} V_C(t_A) e^{-(t - t_B - \tau)/\tau}$$

$$= -\frac{0.731}{2} e^{-(t - t_B)/\tau}$$



$$= -e V_C(t_A) e^{-(t - t_B)/\tau}$$

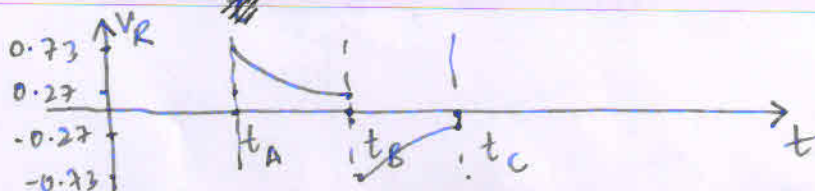

(3)




44.  $t = 0^-$

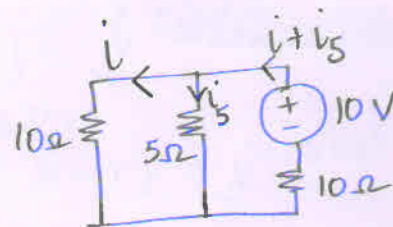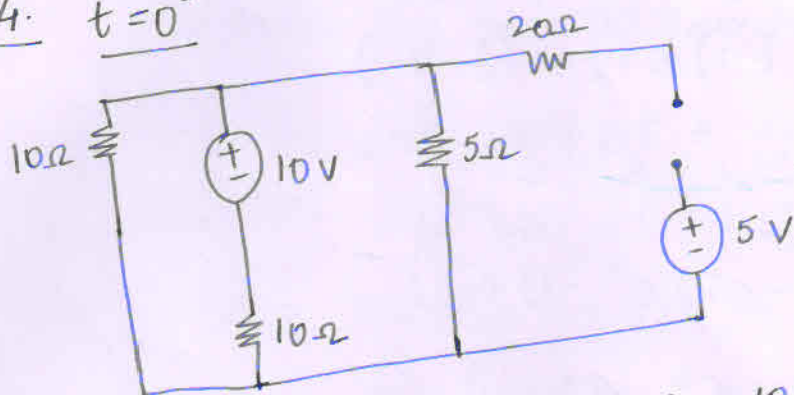


$$R_{eq} = 10 + \left( \frac{10 \times 5}{15} \right) \Omega = 10 + \frac{50}{15} \Omega = 10 + \frac{10}{3} \Omega$$

$$\therefore i_{5\Omega} = \left( \frac{10}{10 + \frac{10}{3}} \right) \times \frac{10}{15} A = 0.5 A$$
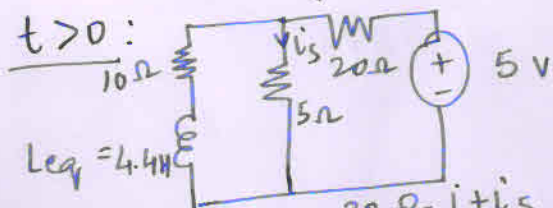
$$\begin{aligned} 10 - 10i - 10i - 10i_5 &= 0 \\ 1 - i_5 &= 2i \\ 10 - 5i_5 - 10i - 10i_5 &= 0 \\ \Rightarrow i &= \frac{1}{4} A \\ i(0^-) &= \frac{1}{4} A = i(0^+) \end{aligned}$$



$$L_{eq} = 4.4 mH$$

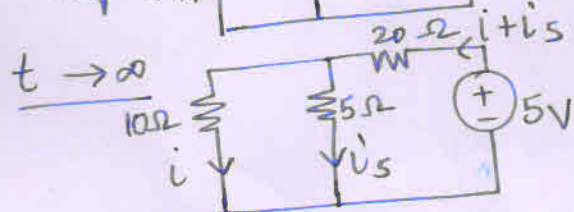

$$5 - 20i - 20i_5 - 5i_5 = 0$$

$$5 - 20i - 20i_5 - 10i = 0$$

$$\Rightarrow i = \frac{5}{70} A, i_5 = \frac{10}{70} A$$

$$R_{TH} = 20 \parallel 5 \Omega + 10 \Omega = 14 \Omega$$

$$\therefore \tau = \frac{4.4}{14} = 0.314 s$$

$$t > 0 \quad i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$$

$$\therefore i(t) = \frac{1}{14} + \left( \frac{1}{4} - \frac{1}{14} \right) e^{-3.2t} A$$

$$V_{5\Omega} = 10i + L \frac{di}{dt} = \frac{5}{7} + \left( \frac{5}{2} - \frac{5}{7} \right) e^{-3.2t} +$$

$$4.4 \left( \frac{1}{4} - \frac{1}{14} \right) e^{-3.2t} (-3.2) V$$

$$\therefore V_{5\Omega} = \frac{10}{14} (1 - e^{-3.2t}) V$$

$$\therefore i_{5\Omega} = \frac{1}{7} (1 - e^{-3.2t}) A$$

Ans 5. i)  $v(t) = -110 \cos(\omega t + 30^\circ) V$

$$\Rightarrow v(t) = -110 \cos(180^\circ + (\omega t - 150^\circ)) V$$

$$\Rightarrow v(t) = +110 \cos(\omega t - 150^\circ) V$$

ii)  $v(t) = 220 \sin(\omega t + 220^\circ) V$

$$\Rightarrow v(t) = 220 \sin(90^\circ + (\omega t + 130^\circ)) V$$

$$\Rightarrow v(t) = 220 \cos(\omega t + 130^\circ) V$$

iii)  $v(t) = 10 \sin(\omega t + 110^\circ) + 4 \cos(\omega t + 110^\circ) V$

$$\Rightarrow v(t) = \sqrt{100 + 16} \left[ \frac{10}{\sqrt{116}} \sin(\omega t + 110^\circ) + \frac{4}{\sqrt{116}} \cos(\omega t + 110^\circ) \right]$$

$$\Rightarrow v(t) = \sqrt{116} [\sin(68^\circ) \sin(\omega t + 110^\circ) + \cos(68^\circ) \cos(\omega t + 110^\circ)]$$

$$\Rightarrow v(t) = \sqrt{116} \cos(\omega t + 110^\circ - 68^\circ)$$

$$\Rightarrow v(t) = \sqrt{116} \cos(\omega t + 42^\circ)$$

$$\text{iv) } v(t) = 10 \cos(\omega t + 370^\circ) + \sin(\omega t + 10^\circ) \text{ V}$$


$$= 40 [\sin(2\omega t + 380^\circ) - \sin(360^\circ)]$$

$$= 40 [\sin(2\omega t + 380^\circ)]$$

$$= \cancel{40 \cos(\omega t + 2870)}$$

$$= 40 \cos(2\omega t + 290^\circ) \text{ V} = 40 \cos(2\omega t - 70^\circ) \text{ V}$$

Ans 6.

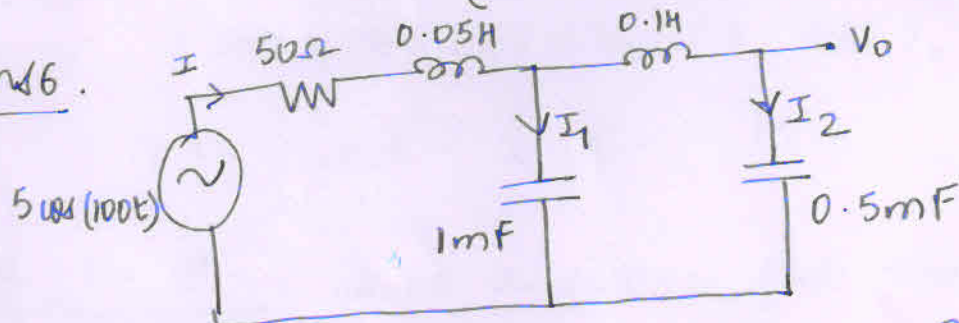

$$Z_{eq} = 50 + j5 + \left[ -j10 \parallel (j10 - j20) \right]$$

$$= 50 + j5 + (-j10 \parallel -j10)$$

$$= 50 + j5 - j5$$

$$= 50 \Omega$$

$$\therefore I = \frac{5 \cos(100t)}{50} \text{ A} = 0.1 \cos(100t) \text{ A}$$

$$\therefore I_2 = \left( \frac{-j10}{-j10 + j10 - j20} \right) I = \frac{-10}{-20} \times 0.1 \cos(100t) = 0.05 \cos(100t) \text{ A}$$

$$\therefore V_0 = I_2(-j20) = \cos(100t - 90^\circ) \text{ V}$$

$$= \sin(100t) \text{ V}$$