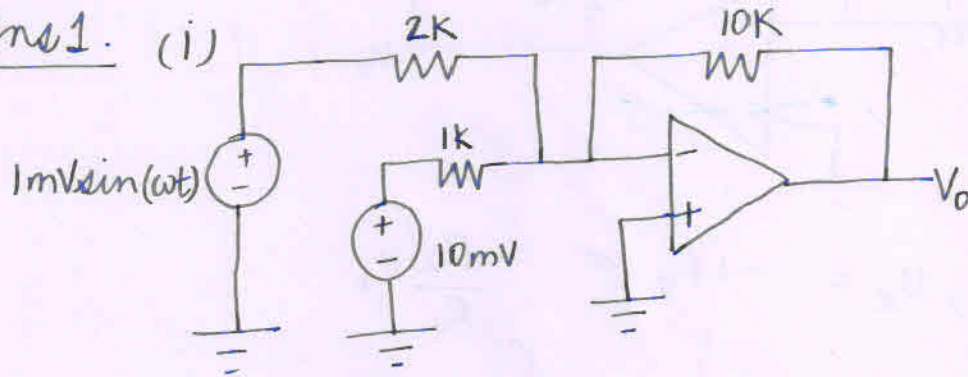


# ESC 201 Assignment 8 Solutions


Ans 1. (i)




$$V_o = - \left\{ \frac{10k}{1k} \times 10mV + \frac{10k}{2k} 1mV \sin(\omega t) \right\}$$

$$= - (0.1 + 5 \times 10^{-3} \sin(\omega t)) V$$

(ii)

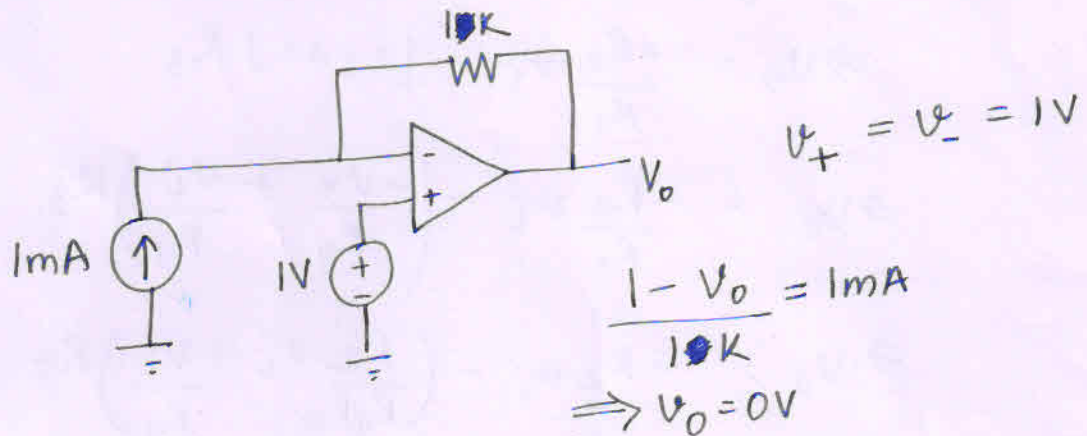

(iii)

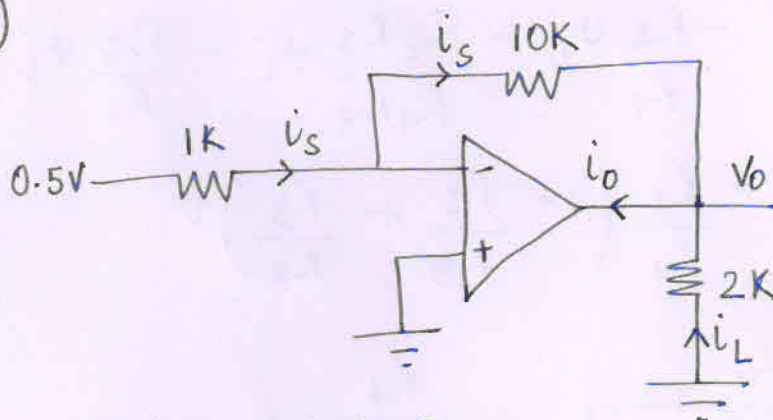


$$i_s = \frac{0.5}{1k} A = 0.5mA$$

$$V_o = -i_s \times 10k = -0.5 \times 10^{-3} \times 10 \times 10^3 V = -5V$$

$$i_L = \frac{-V_o}{2k} = \frac{5}{2k} A = 2.5mA$$

$$i_o = i_s + i_L = 0.5mA + 2.5mA = 3mA$$

(iv)

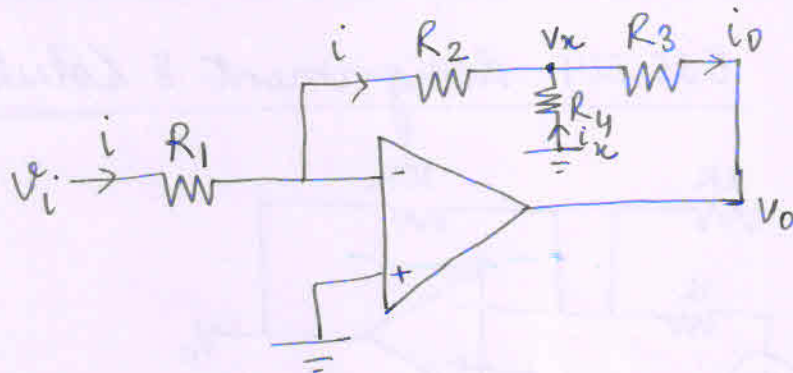

$$i = \frac{V_i}{R_1}, \quad V_x = -iR_2 = -\frac{R_2}{R_1} V_i$$

$$i_x = \frac{-V_x}{R_4}$$

$$i_o = i_x + i$$

$$V_o = V_x - i_o R_3$$


$$\Rightarrow V_o = -\frac{R_2}{R_1} V_i - (i_x + i) R_3$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} V_i - \left( \frac{-V_x}{R_4} + \frac{V_i}{R_1} \right) R_3$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} V_i - \left( \frac{R_2}{R_1 R_4} V_i + \frac{V_i}{R_1} \right) R_3$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} V_i - \frac{R_2 R_3}{R_1 R_4} V_i - \frac{R_3}{R_1} V_i$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} \left( 1 + \frac{R_3}{R_4} + \frac{R_3}{R_2} \right) V_i$$

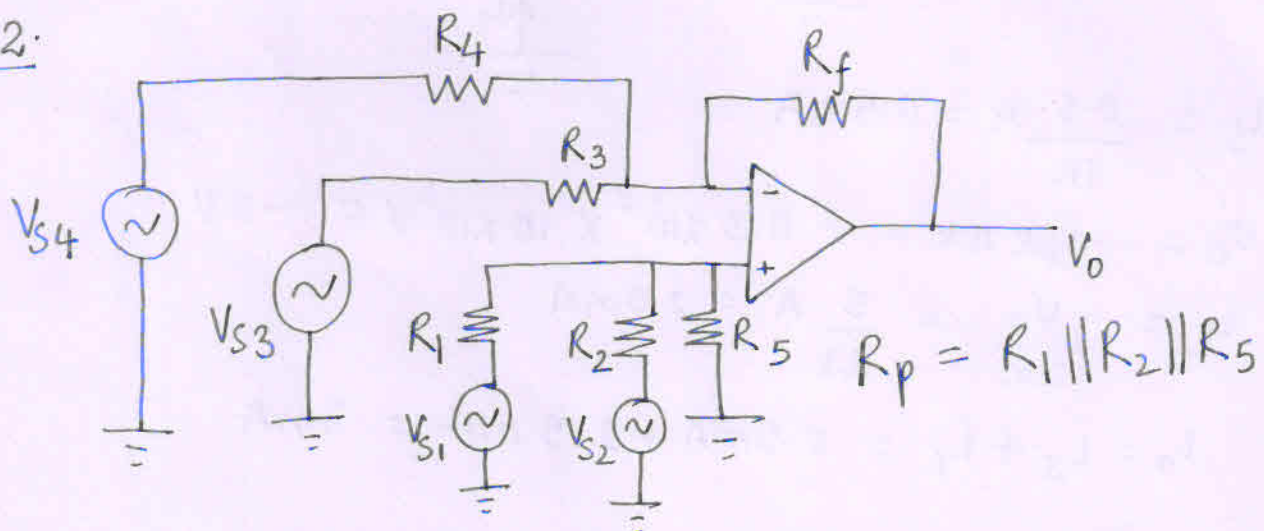Ans 2.

$$V_0 = -\left(\frac{R_f}{R_3}\right)V_{S3} - \left(\frac{R_f}{R_4}\right)V_{S4} + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_p}{R_1} V_{S1} \\ + \left(1 + \frac{R_f}{R_3 \parallel R_4}\right) \times \frac{R_p}{R_2} V_{S2}$$

$$V_0 = 2V_{S1} + 4V_{S2} - 8V_{S3} - 10V_{S4}$$

$$\text{Let } R_f = 10K$$

$$\therefore \frac{R_f}{R_3} = 8$$

$$\frac{10K}{R_3} = 8 \Rightarrow R_3 = 1.25k\Omega$$

$$\frac{R_f}{R_4} = 10$$

$$\therefore \frac{10K}{R_4} = 10 \Rightarrow R_4 = 1k\Omega$$

$$\frac{R_f}{R_3 \parallel R_4} \times \frac{R_p}{R_1} = 2 \Rightarrow \frac{10K}{(1.25k \parallel 1k)} \times \frac{R_p}{R_1} = 2$$

$$\Rightarrow \frac{R_p}{R_1} = 0.105$$


$$\frac{R_f}{R_3 \parallel R_4} \times \frac{R_p}{R_2} = 4 \Rightarrow \frac{10K}{(1.25k \parallel 1k)} \times \frac{R_p}{R_2} = 4$$

$$\Rightarrow \frac{R_p}{R_2} = 0.211$$

$$\frac{R_1}{R_p} \times \frac{R_p}{R_2} = \frac{1}{0.105} \times 0.211 \Rightarrow \frac{R_1}{R_2} = 2$$

$$\text{Let } R_2 = 1k\Omega \Rightarrow R_1 = 2k\Omega \Rightarrow R_p = 0.211k\Omega \\ \therefore R_5 = 0.308k\Omega$$

Ans 3.

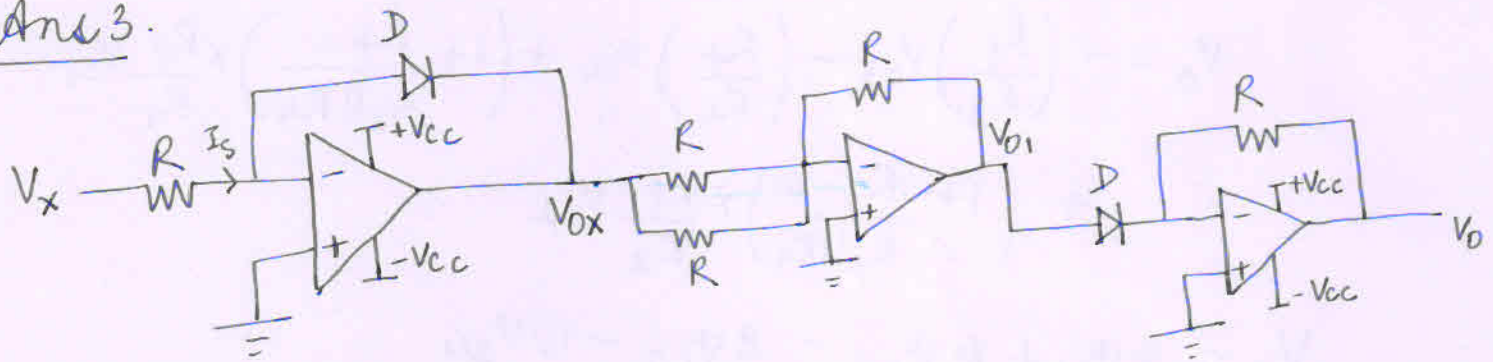

$$V_{0x} = -V_T \ln\left(\frac{V_x}{R I_S}\right)$$

$$V_{01} = V_T \times \left[ \ln\left(\frac{V_x}{R I_S}\right) + \ln\left(\frac{V_x}{R I_S}\right) \right]$$

$$\Rightarrow V_{01} = V_T \times \ln\left(\frac{V_x^2}{R^2 I_S^2}\right)$$


$$V_0 \approx -R I_S \times e^{V_{01}/V_T}$$

$$= -R I_S \times \left(\frac{V_x^2}{R^2 I_S^2}\right)$$

$$= -\frac{V_x^2}{R I_S}$$

$$[\text{Here, } K = -\frac{1}{R I_S}]$$

Ans 4.

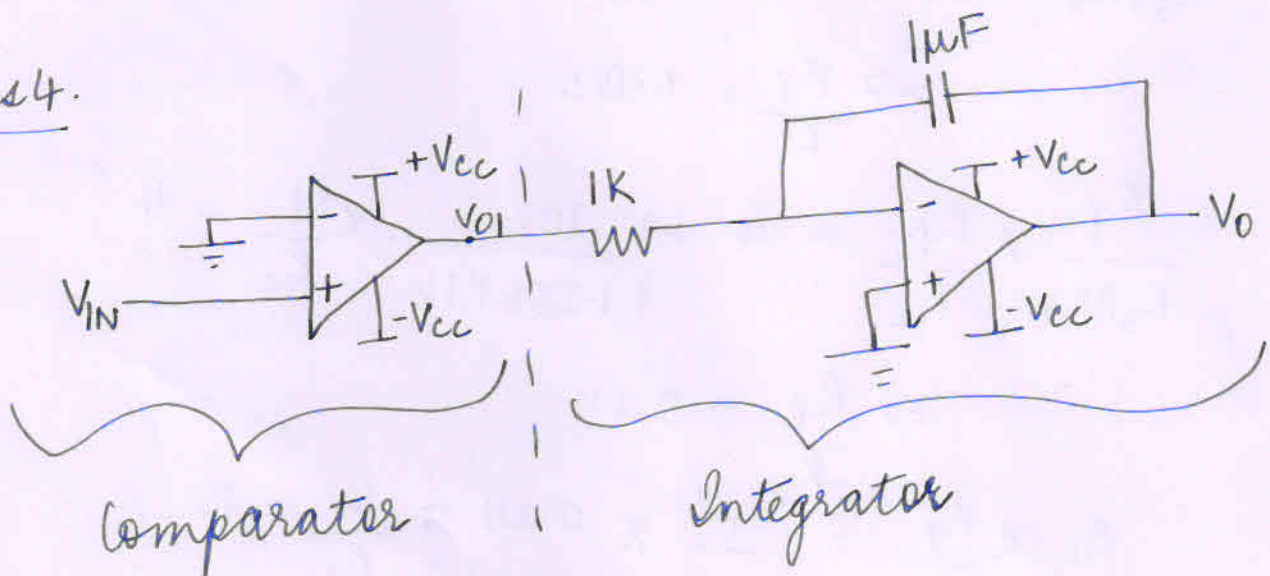

Comparator


Integrator



for the comparator,

$$V_{O1} = +5V \text{ if } V_{IN} > 0$$


$$= -5V \text{ if } V_{IN} < 0$$

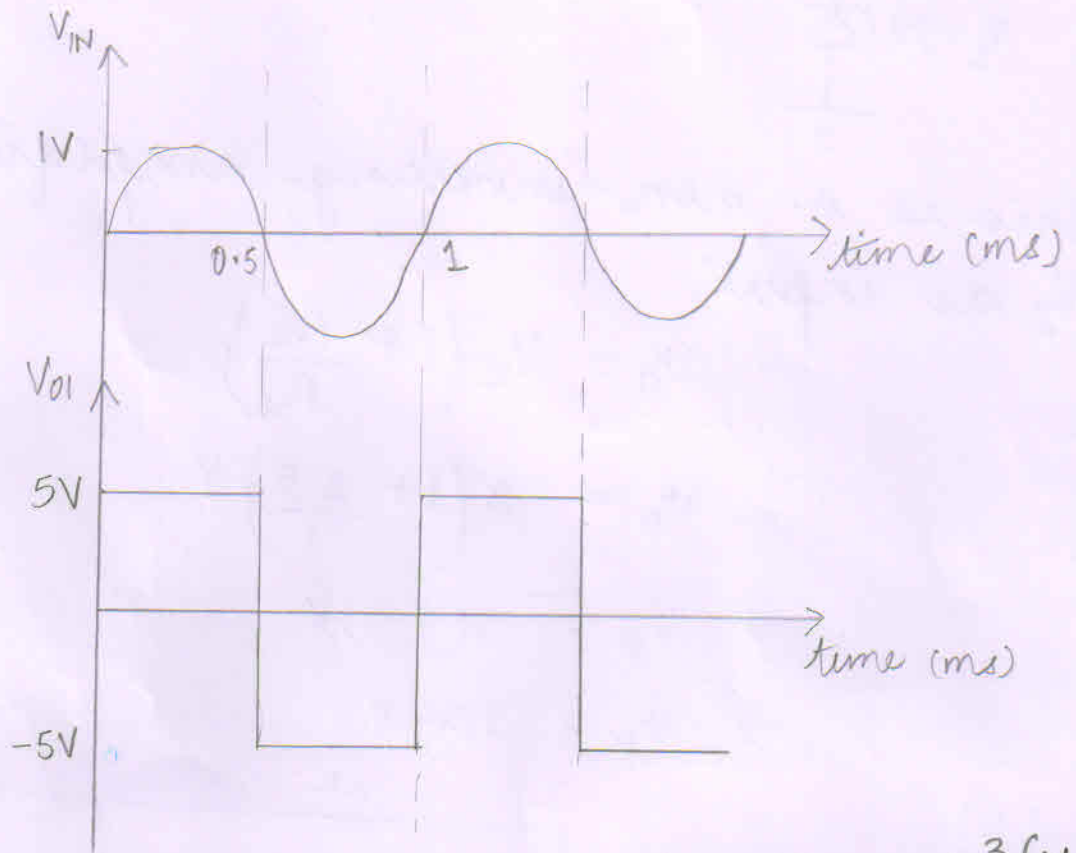


For the integrator,  $V_O(t) = -\frac{1}{RC} \int V_{O1} dt = -10^3 \int V_{O1} dt$

for  $V_{IN} > 0$ ,  $V_O = -5 \times 10^3 \times t$

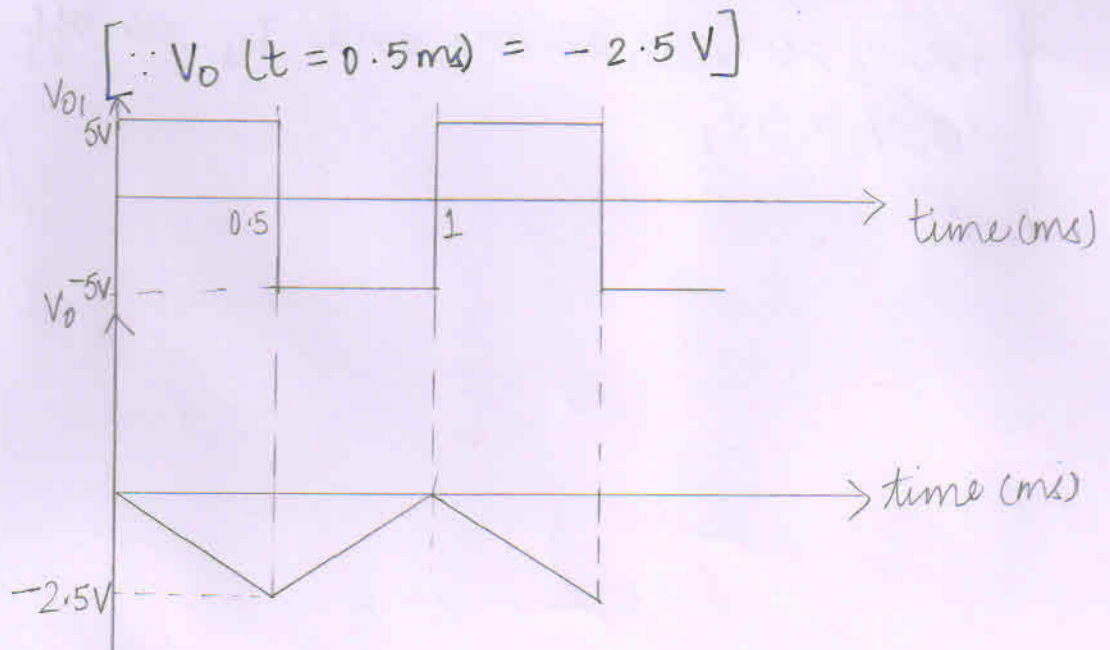for  $V_{IN} < 0$ ,  $V_O = -2.5 + 5 \times 10^3 (t - 0.5 \text{ ms})$



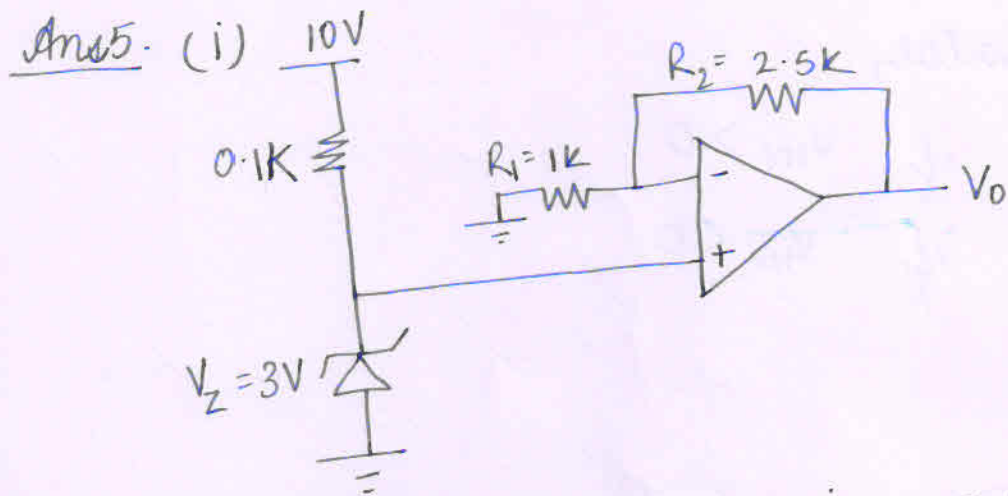

This is a non-inverting amplifier with  $V_Z$  as input.


$$V_o = V_Z \left( 1 + \frac{R_2}{R_1} \right)$$

$$\therefore V_o = 3 \left( 1 + \frac{2.5}{1} \right) V$$

$$\Rightarrow V_o = 3(3.5) V$$

$$\Rightarrow V_o = 10.5 V$$

(iii)

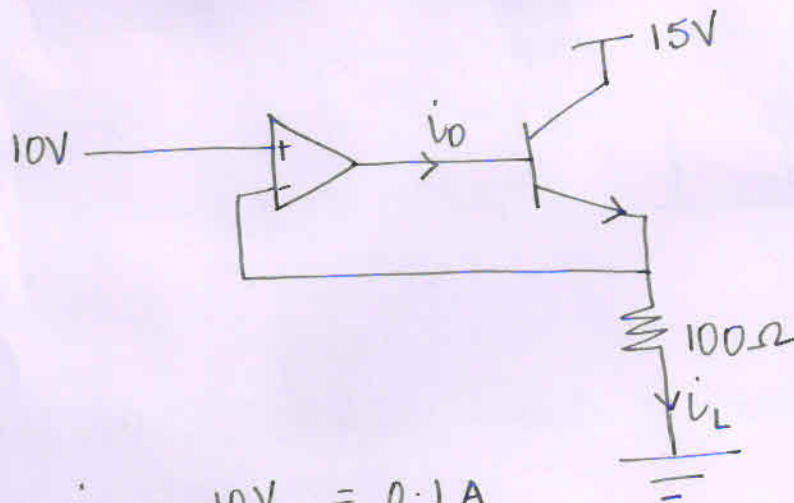

$$i_L = \frac{10V}{100\Omega} = 0.1 A$$

$$I_{B0} = I_B = \frac{I_E}{\beta + 1} = \frac{i_L}{\beta + 1} = \frac{0.1 A}{101} = 0.99 mA$$

The circuit can supply load current that is much larger than op-amp output current.