

ESc201: Introduction to Electronics

Amit Verma

Dept. of Electrical Engineering

IIT Kanpur

Recap: Techniques of Circuit Analysis

Nodal Analysis


1. Identify and number the nodes
2. Pick Ground node/Reference node wisely, if it is not already specified
3. Writing KCL Equations in Terms of the Node Voltages

Mesh Analysis


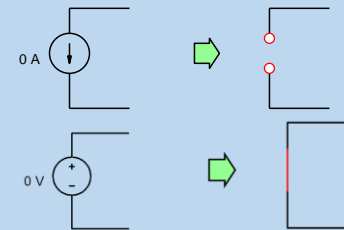
1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes.
2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting n simultaneous equations to get the mesh currents.

Superposition Method for Linear Circuits

The superposition principle states that the total response is the sum of the responses to each of the **independent sources** acting individually.





Thévenin Equivalent Circuits





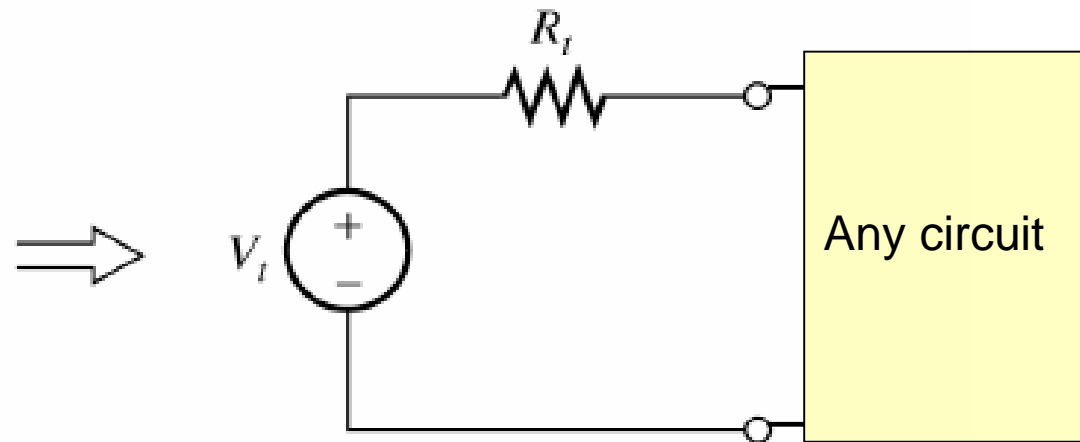
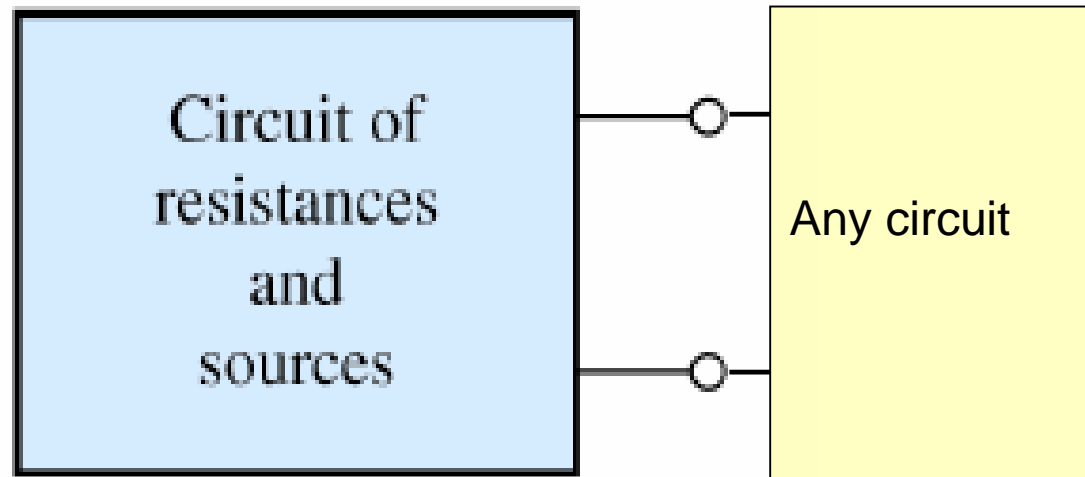


Thévenin equivalent
circuit


Thévenin Equivalent Circuits

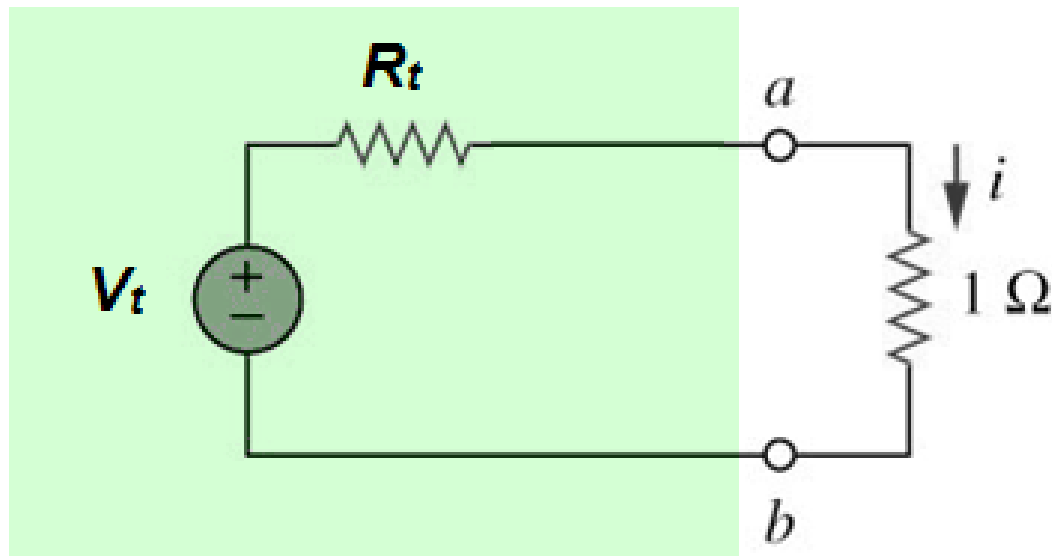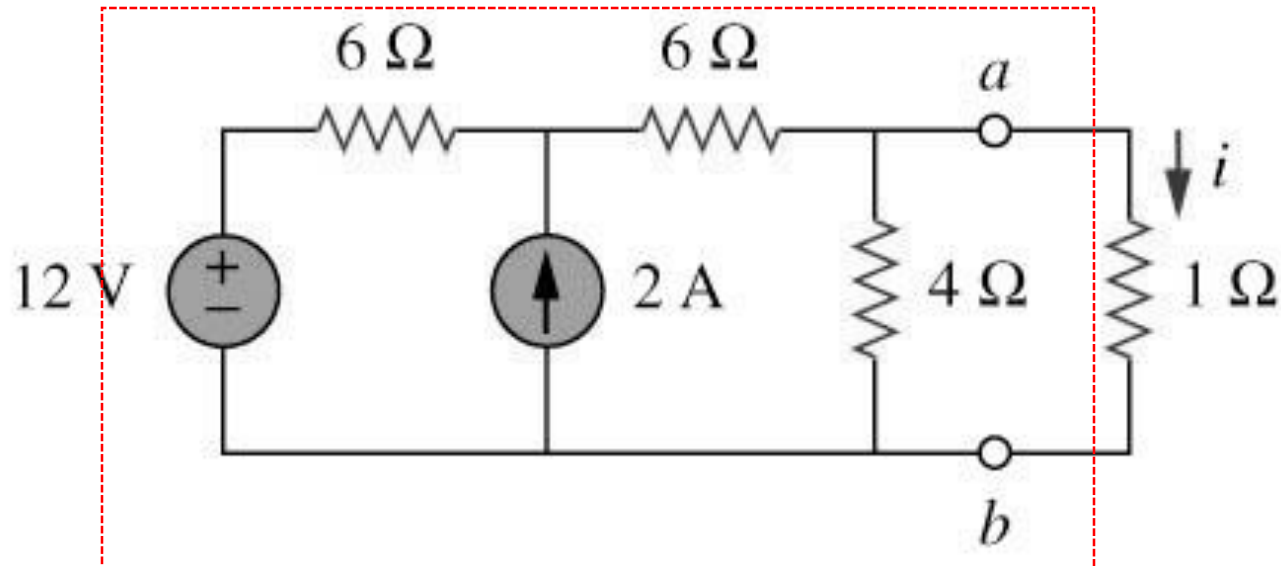

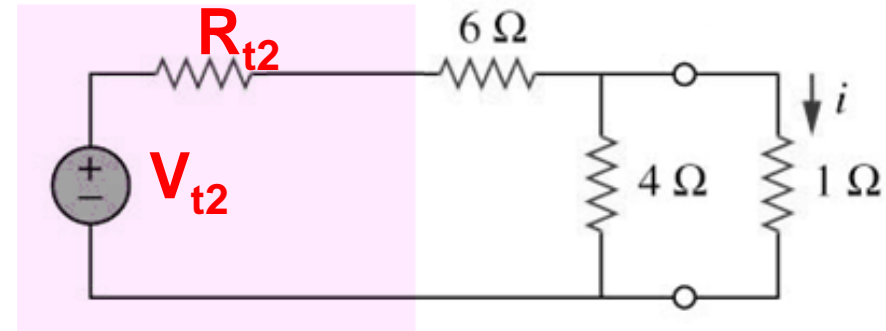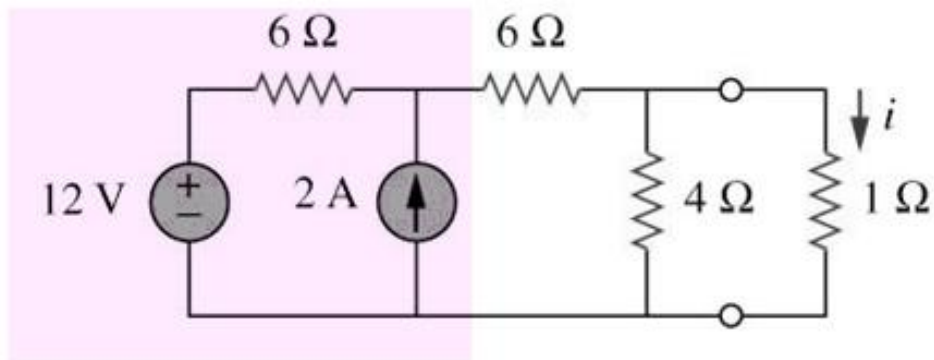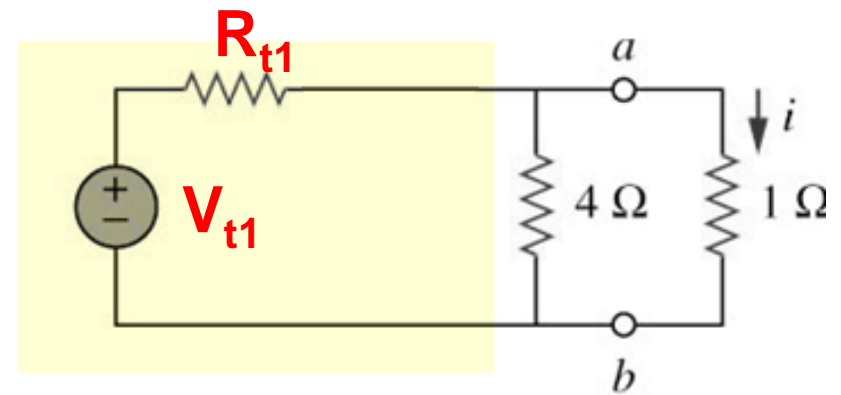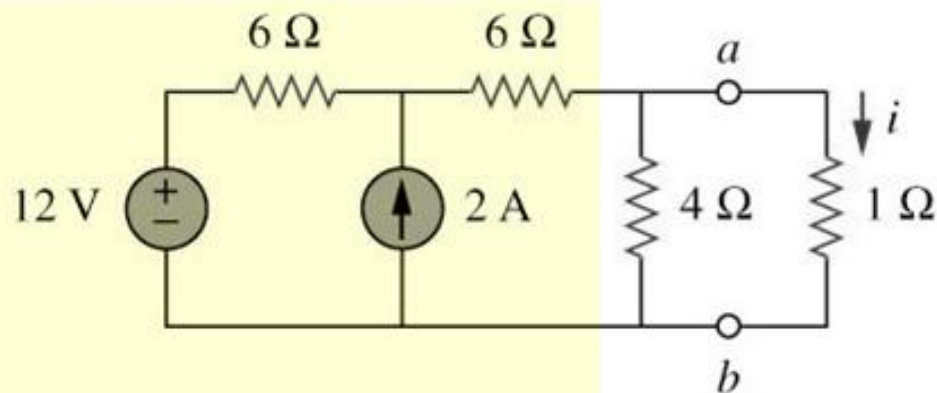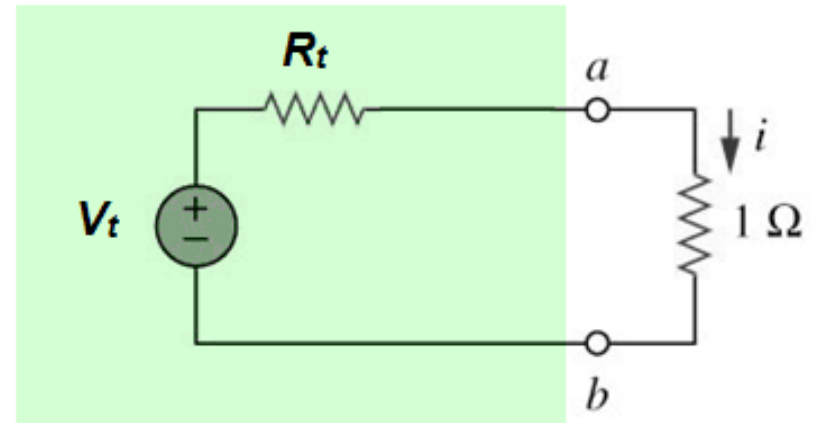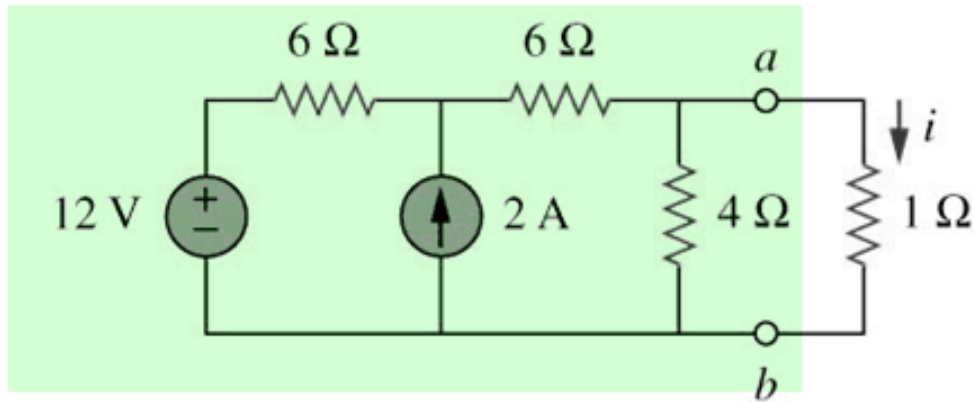
We can apply Thevenin's theorem to any part of the circuit




Thévenin Equivalent Circuits

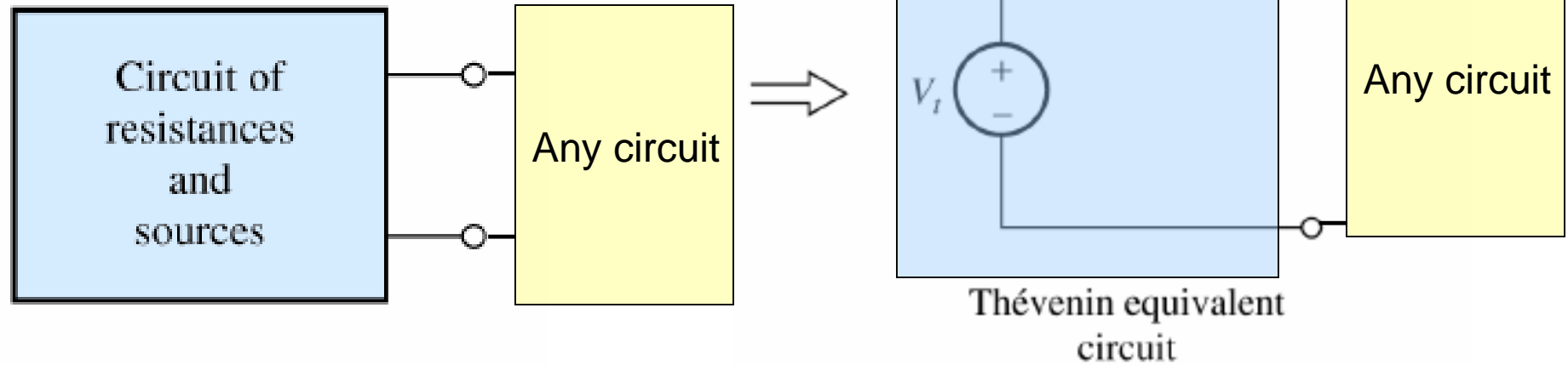


What is V_t ?

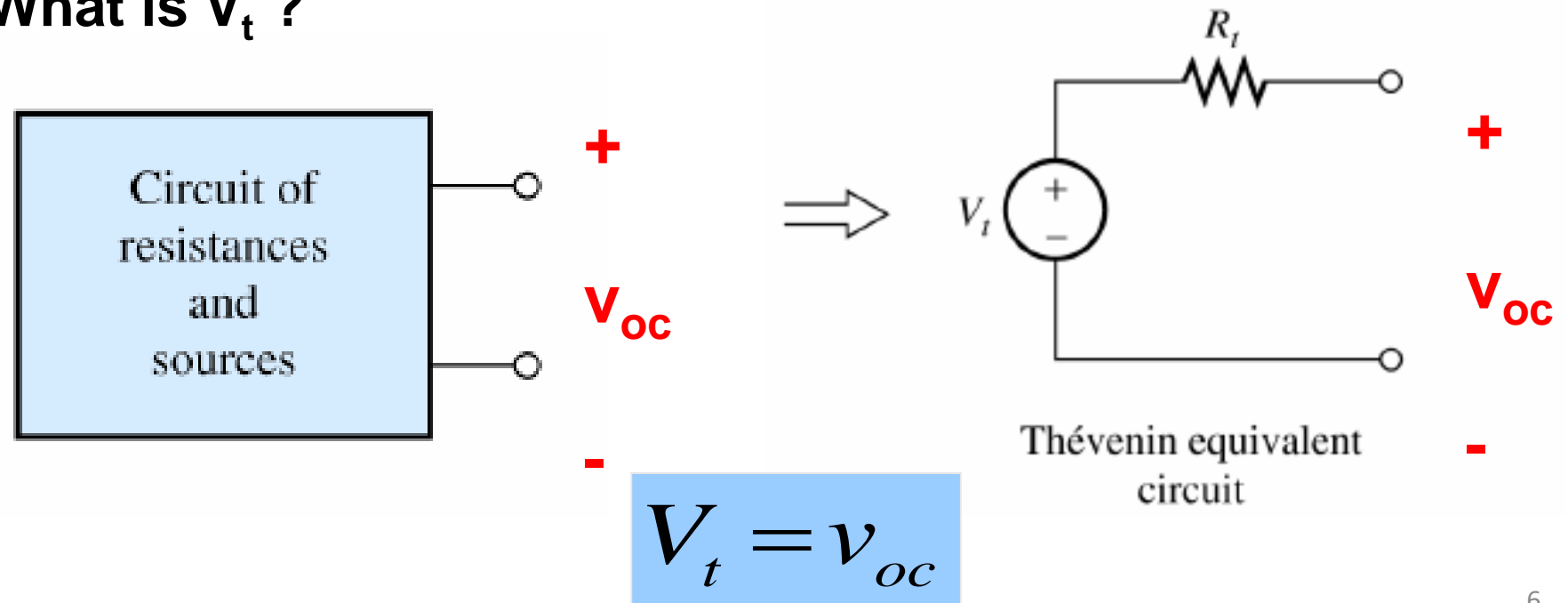


Thévenin Equivalent Circuits

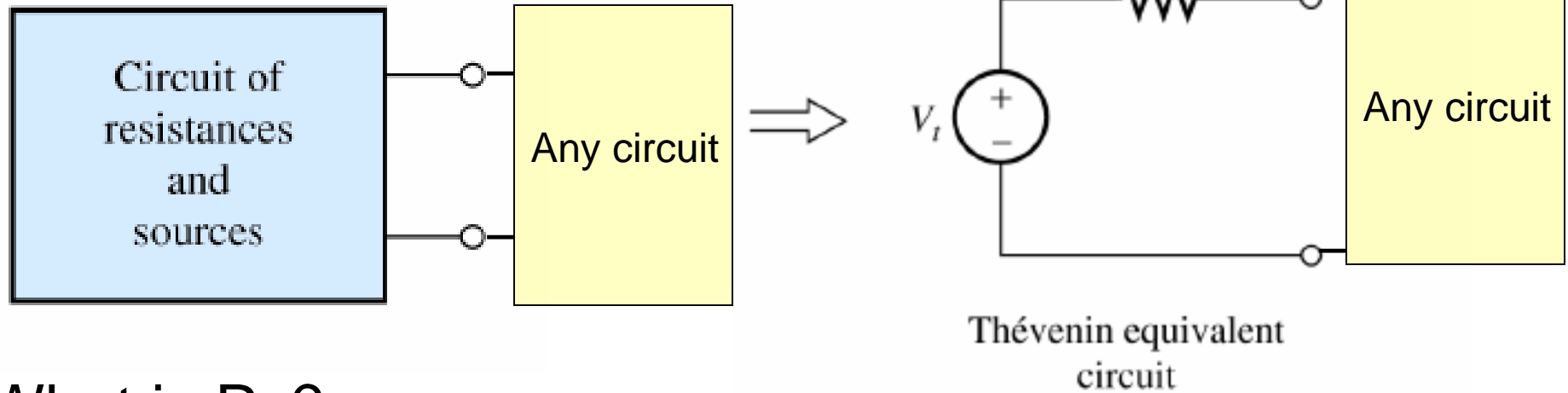

What is R_t ?

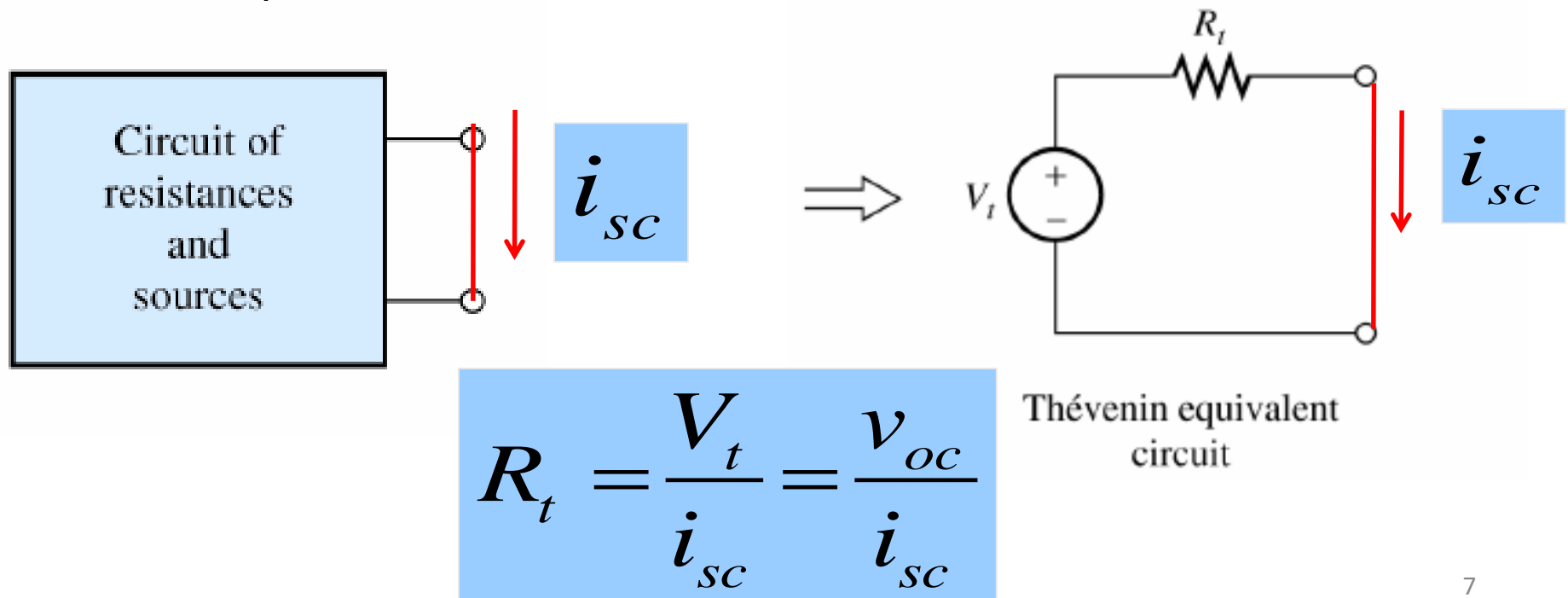


Examples

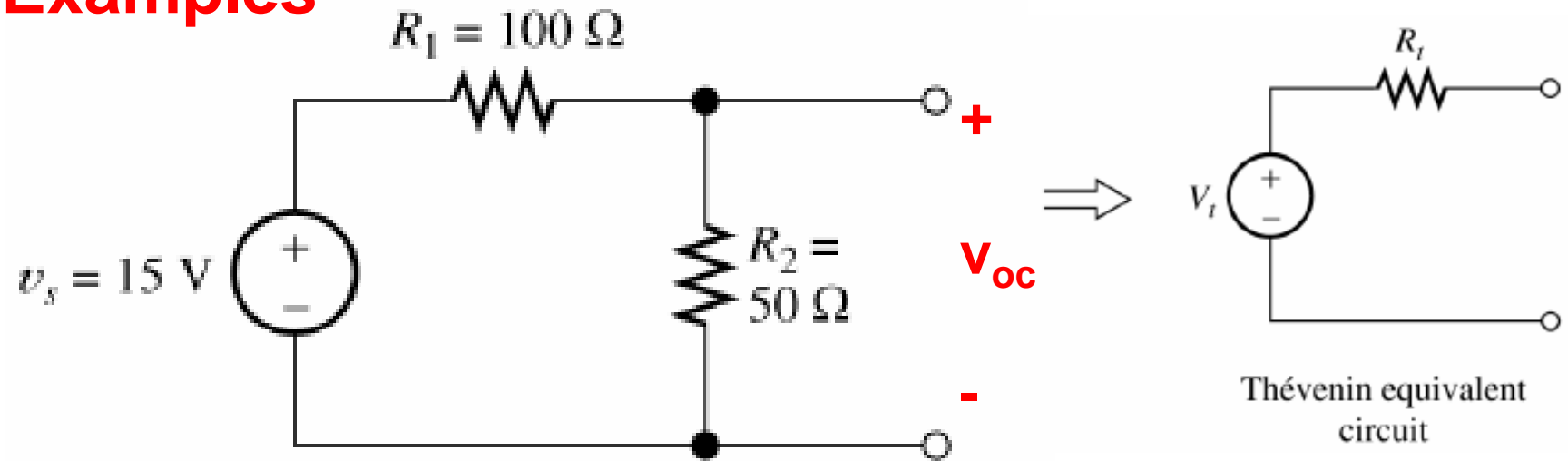


$$V_t = v_{oc}$$
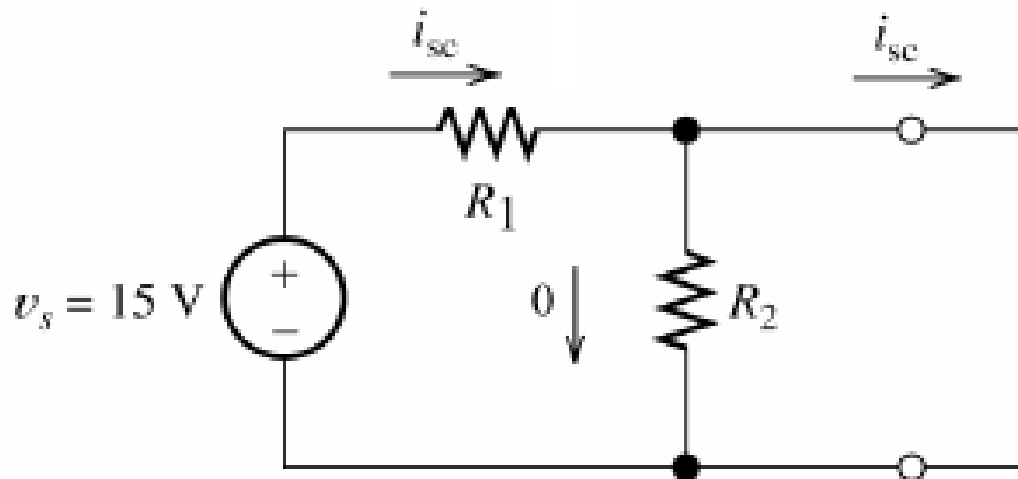
$$V_t = \frac{R_2}{R_2 + R_1} \times 15 = 5$$




$$i_{sc} = \frac{v_s}{R_1} = 0.15 \text{ A}$$
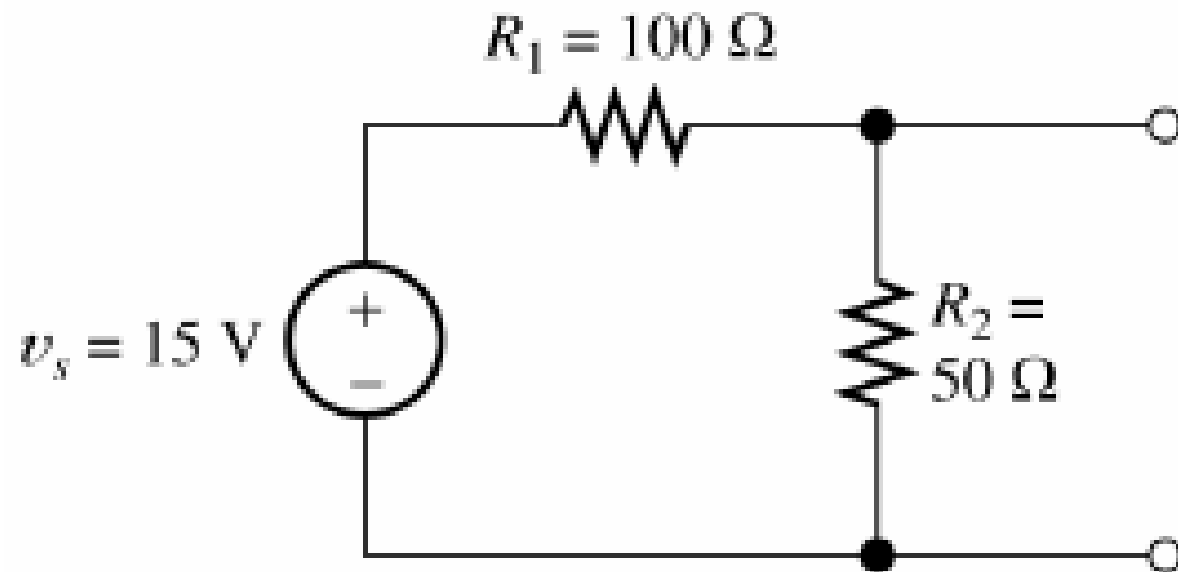
$$R_t = \frac{v_{oc}}{i_{sc}} = 33.3 \Omega$$




$$V_t = 5$$


$$R_t = 33.3\ \Omega$$

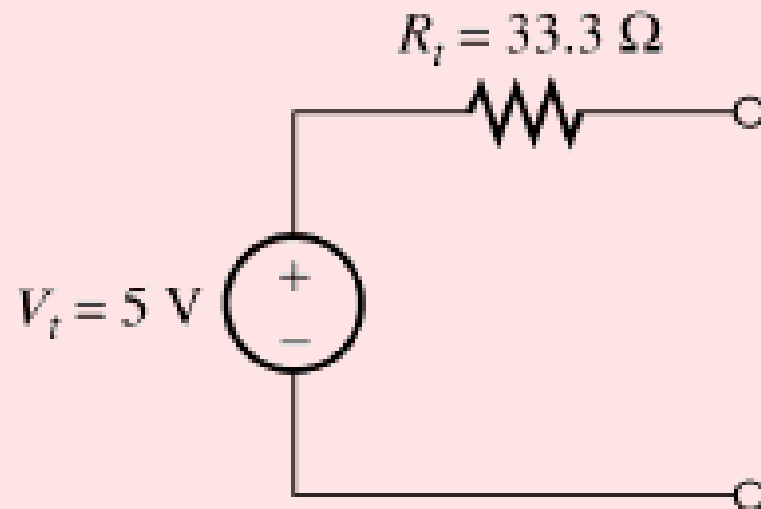


Finding the Thévenin Resistance Directly

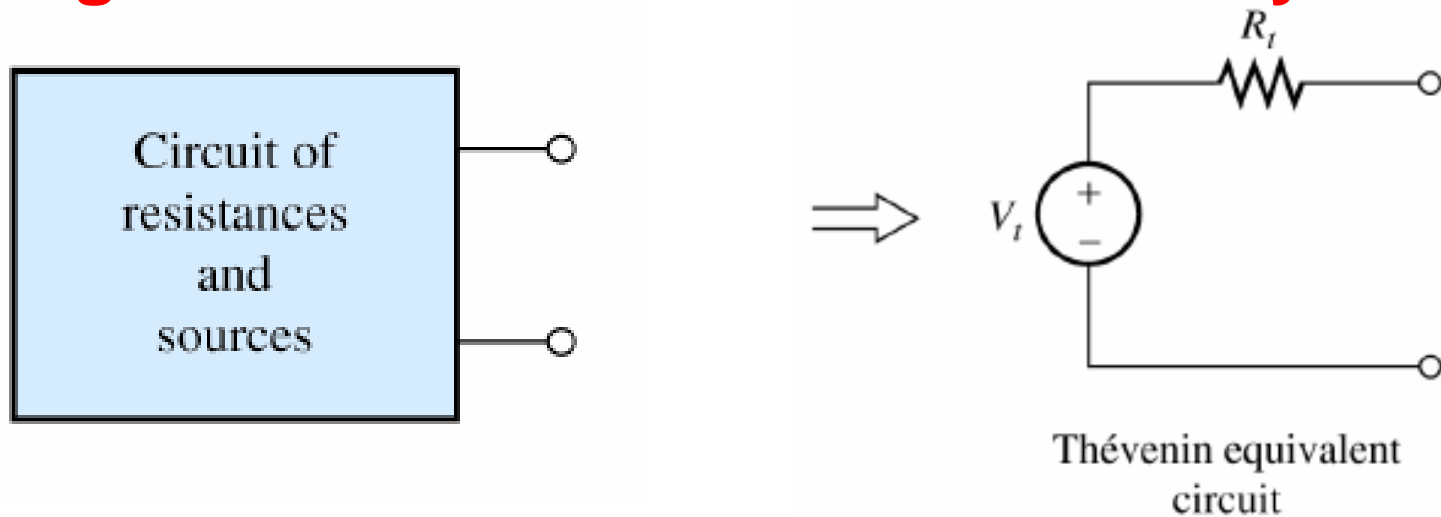

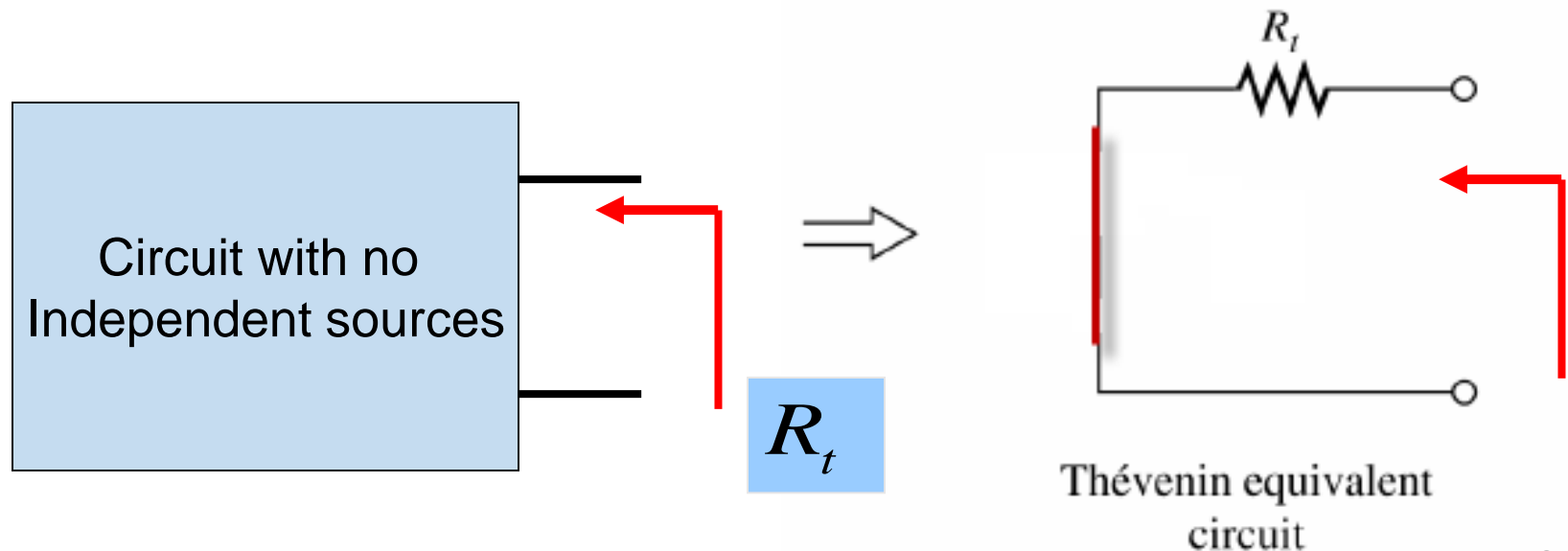Suppose we turnoff all independent sources in the circuit




Finding the Thévenin Resistance Directly

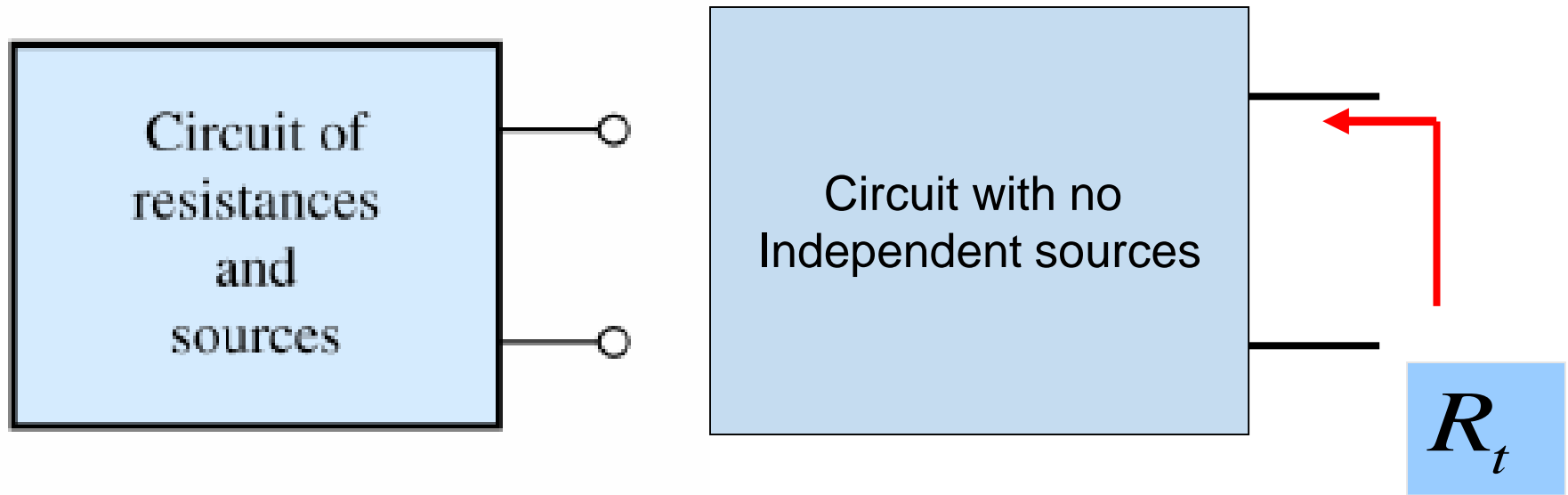


1. Turn off independent sources in the original network:

- A voltage source becomes a short circuit
- A current source becomes an open circuit

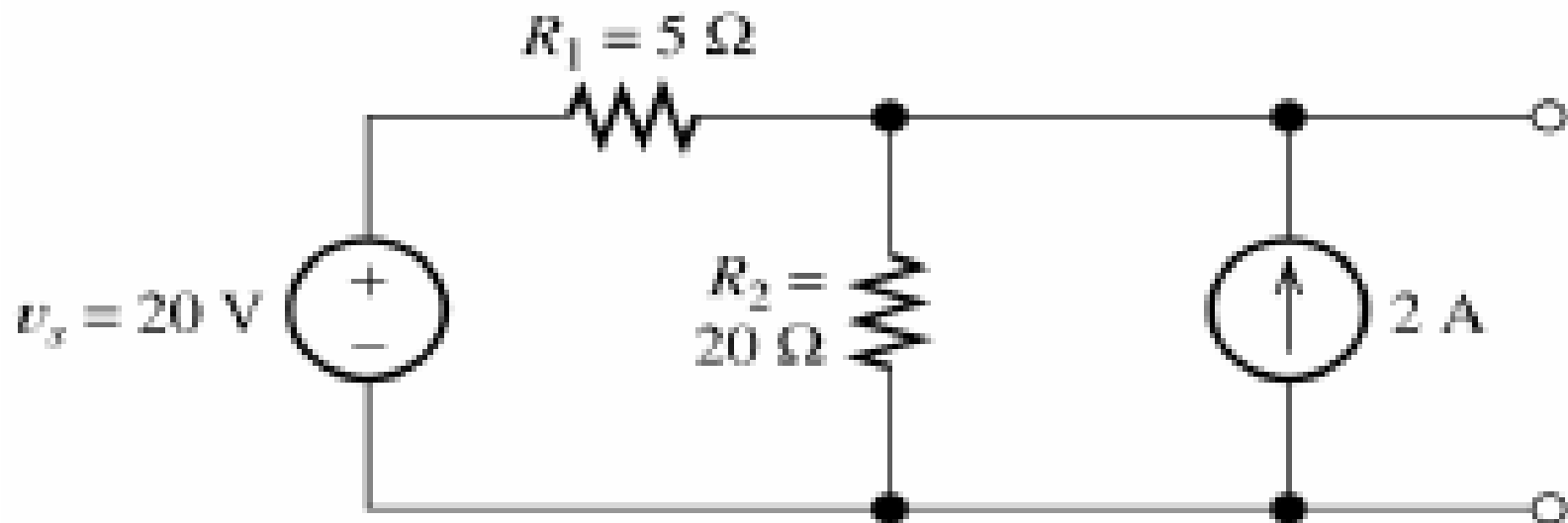2. Compute the resistance between the terminals



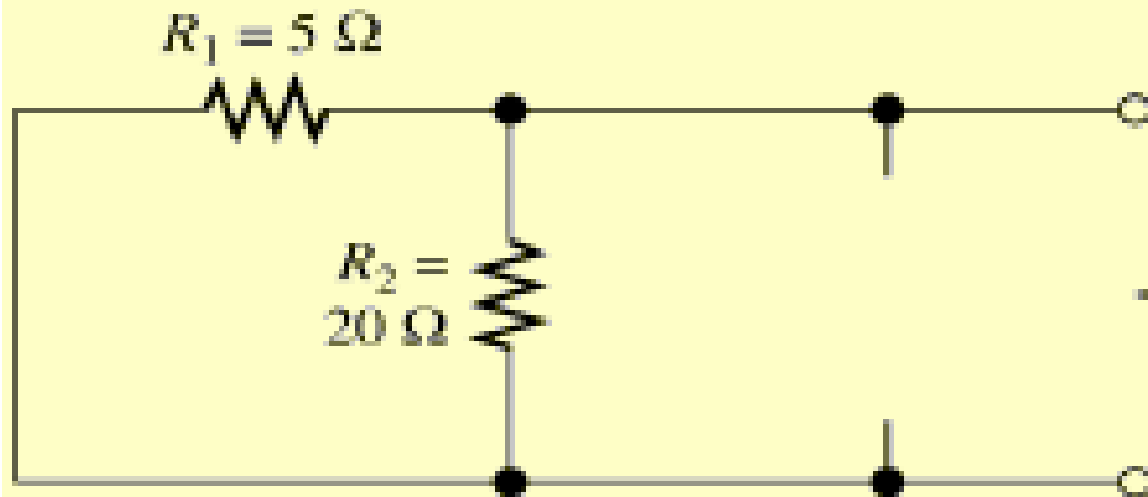
$$R_{eq} = \frac{5 \times 20}{5 + 20} = 4 \Omega$$



$$\leftarrow R_{eq} = R_i$$

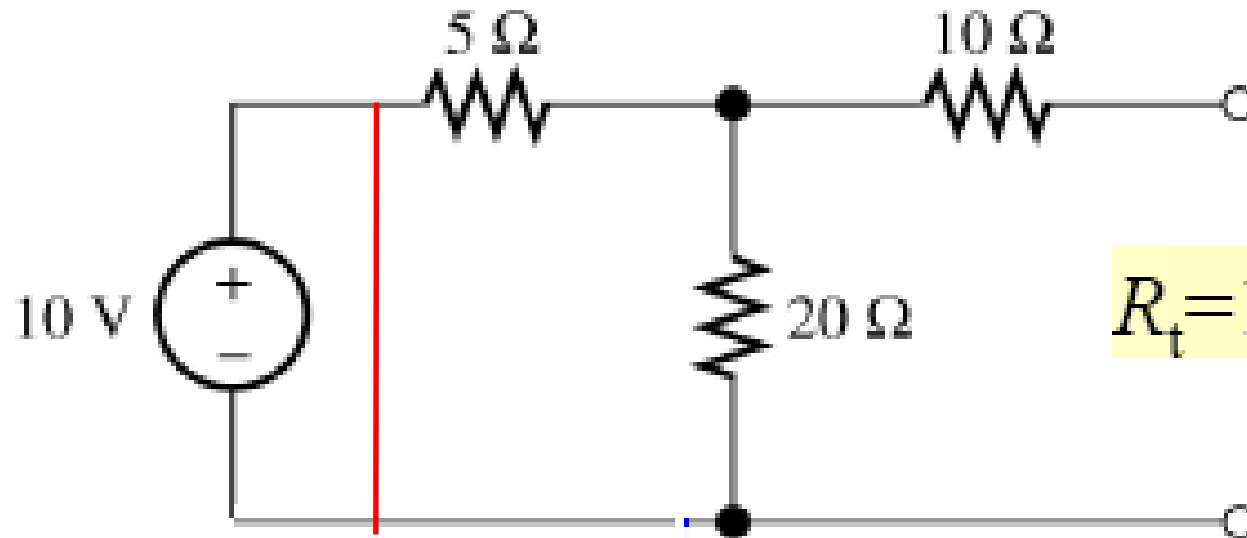
Find Thevenin resistance for each of the circuits shown below



$$R_t = 10 + (5 \parallel 20) = 14$$



$$V_{OC} = V_t = \frac{20}{20 + 5} \times 10 = 8$$
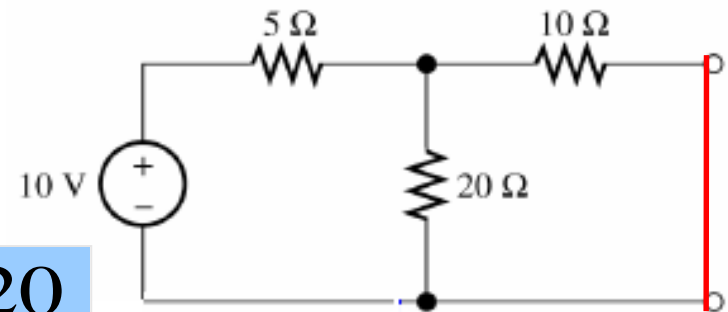
$$i_{sc} = \frac{10}{5 + (10 \parallel 20)} \cdot \frac{20}{20 + 10} = \frac{20}{35}$$




$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{8 \times 35}{20} = 14$$

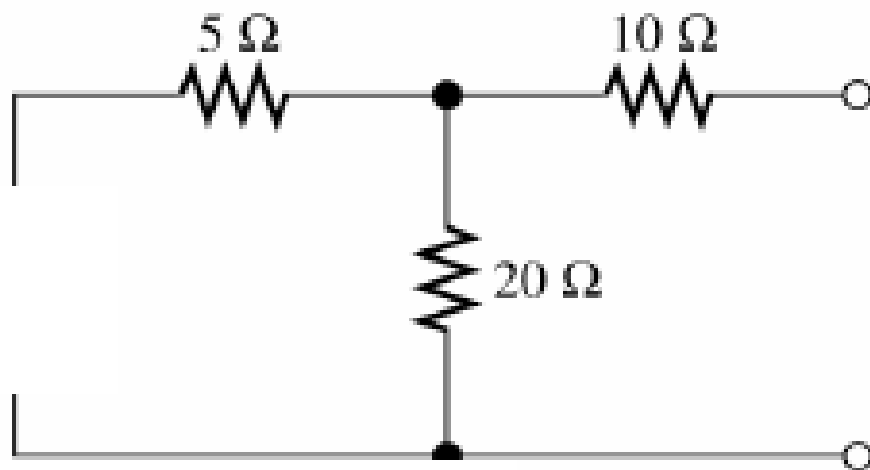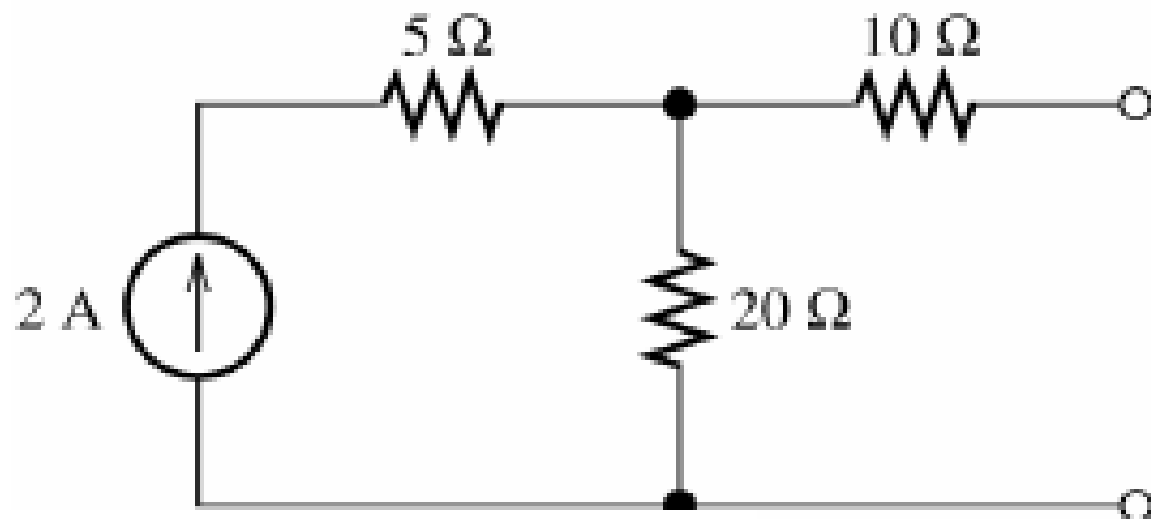Find Thevenin resistance for each of the circuits shown below





$$R_t = 10 + 20 = 30$$

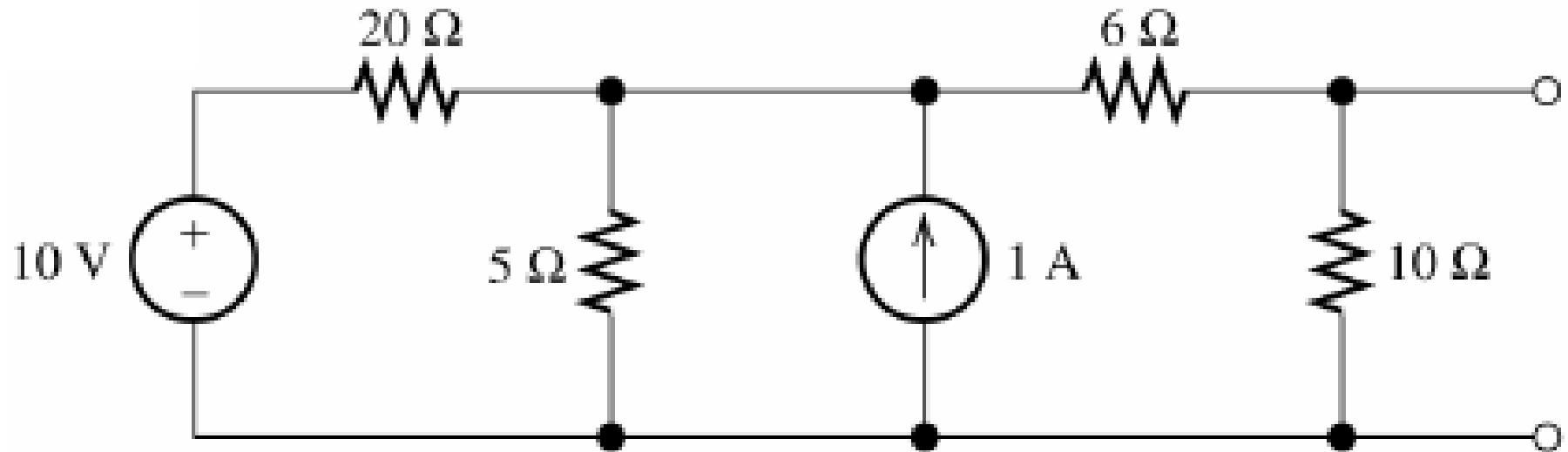Find Thevenin resistance for each of the circuits shown below




$$R_t = ((20 || 5) + 6) || 10 = 5$$

Circuit with dependent Sources

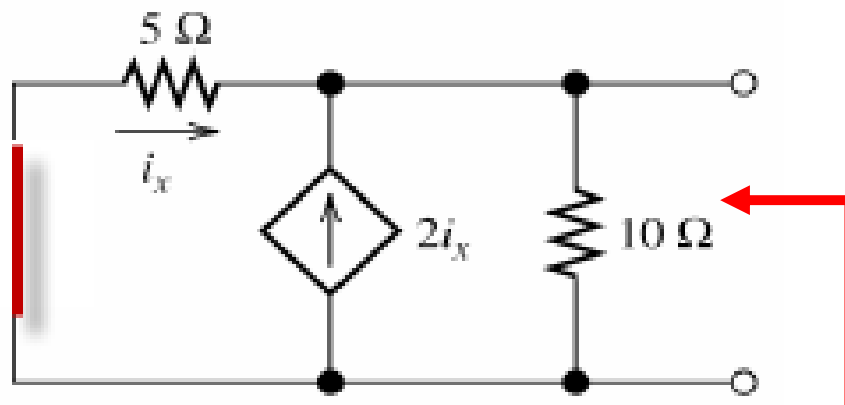
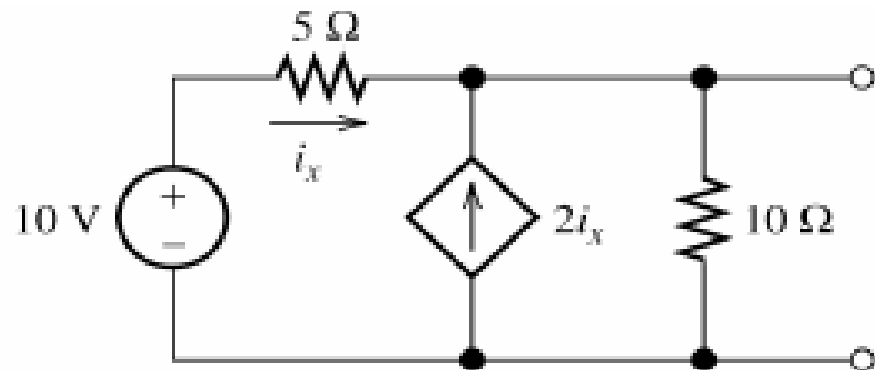


$$R_t = ?$$

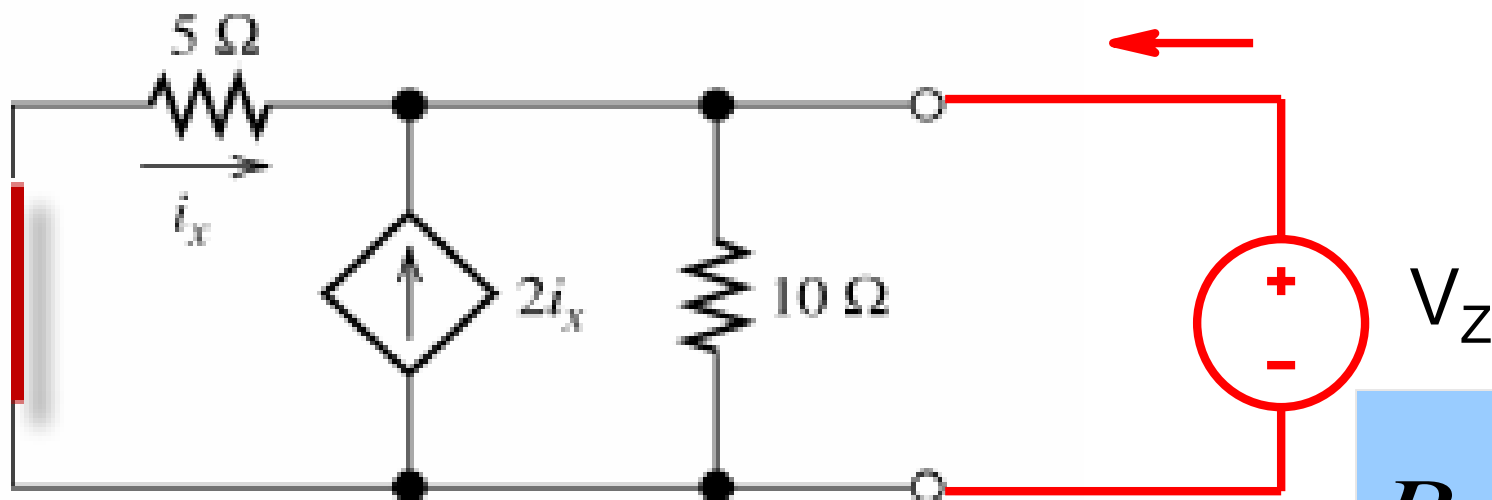


$$R_t = \frac{V_Z}{I_Z}$$


Norton's equivalent

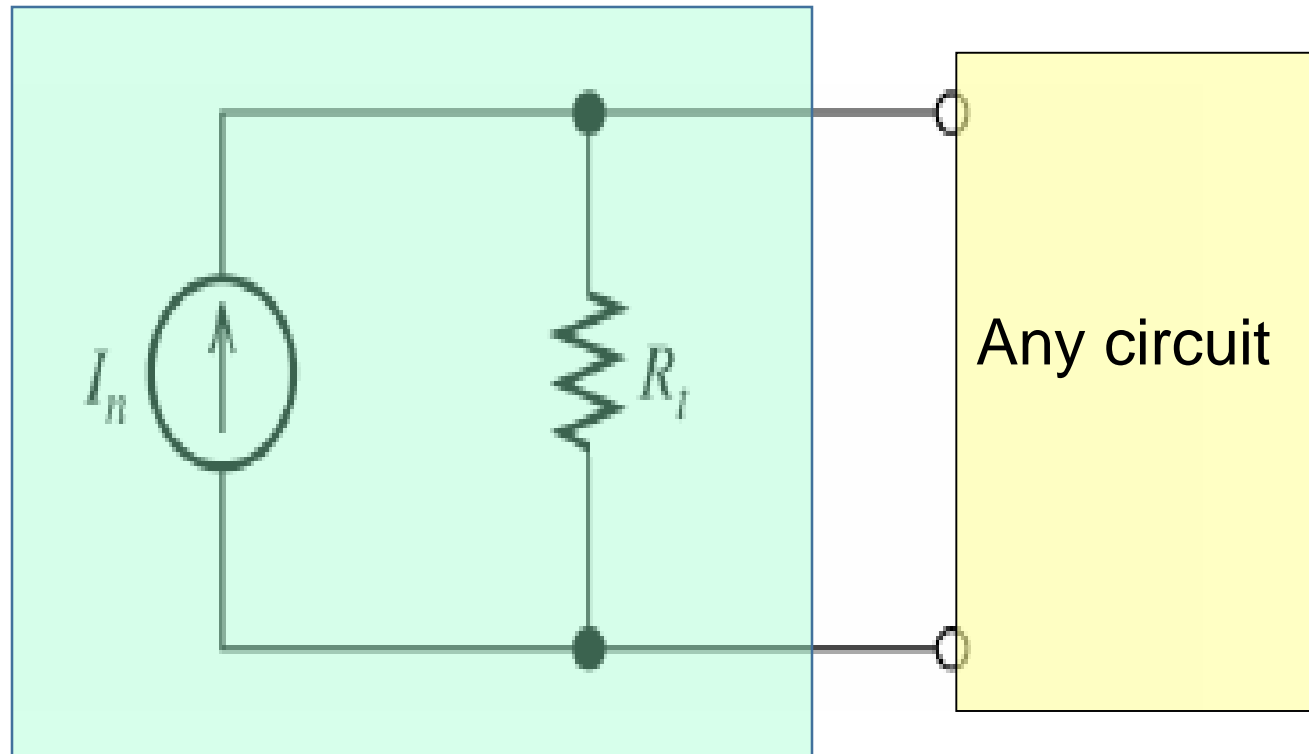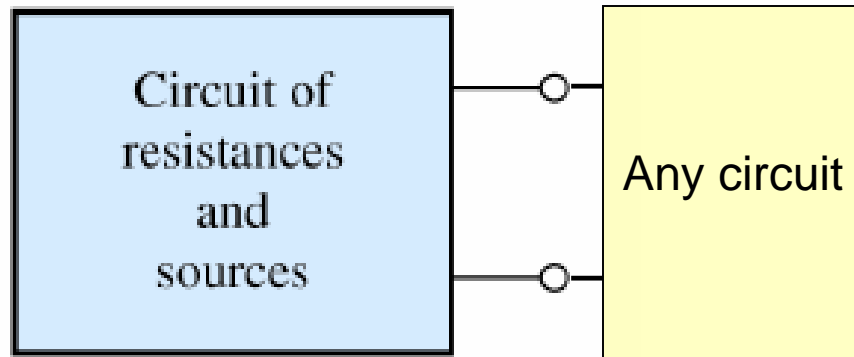


Norton's equivalent

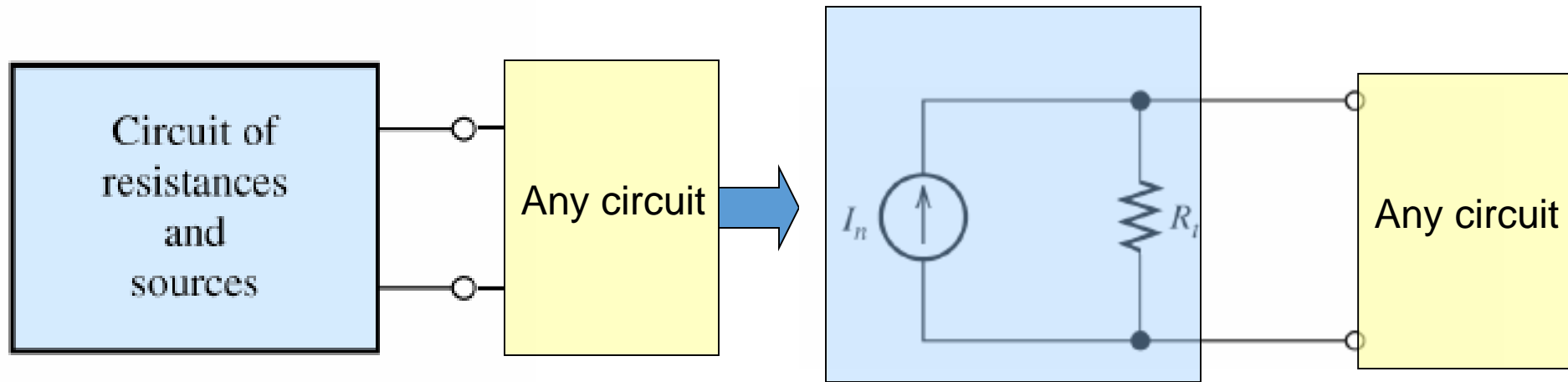


How do we find I_N ?

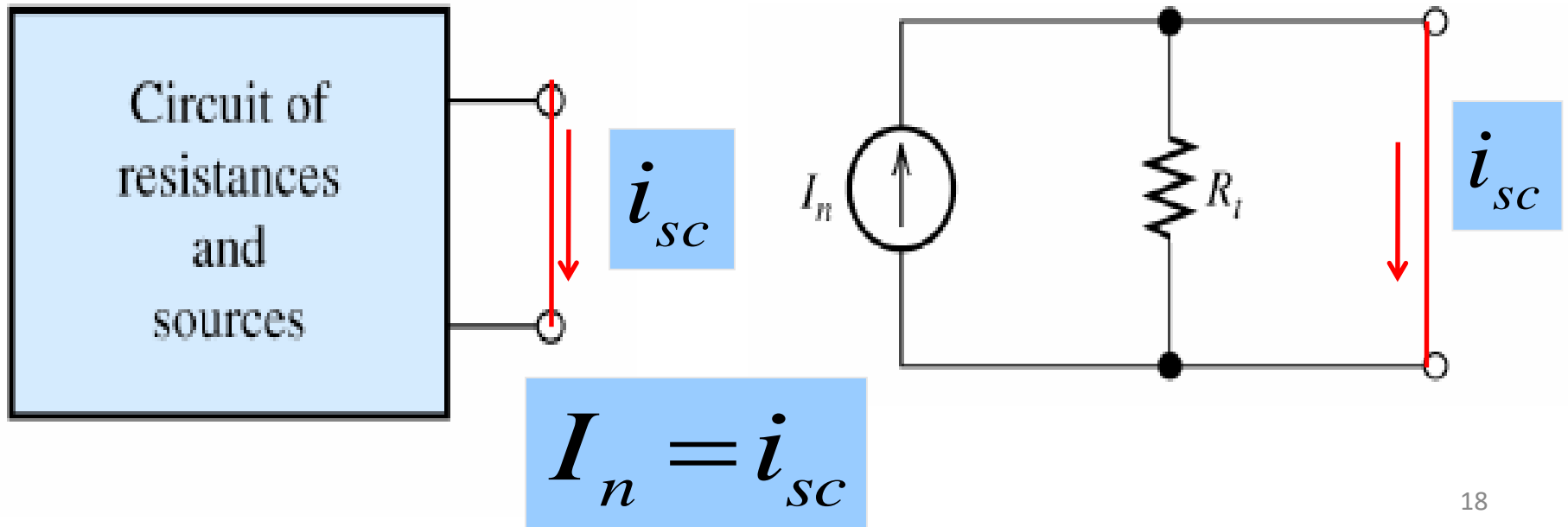

Norton's equivalent

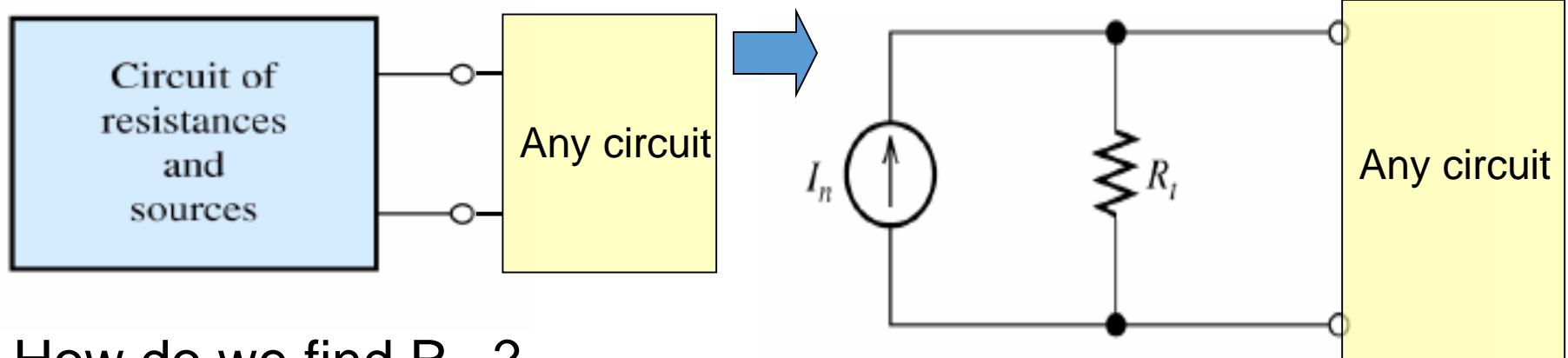


How do we find R_N ?

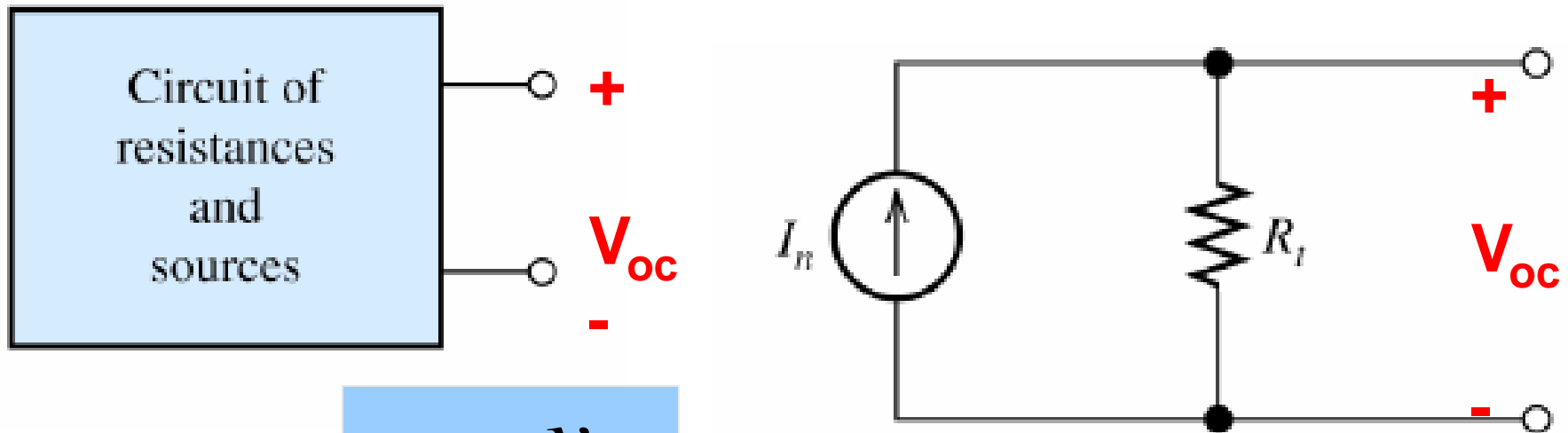


$$R_t = \frac{v_{oc}}{i_{sc}}$$

$$v_{oc} = I_n \times R_t$$

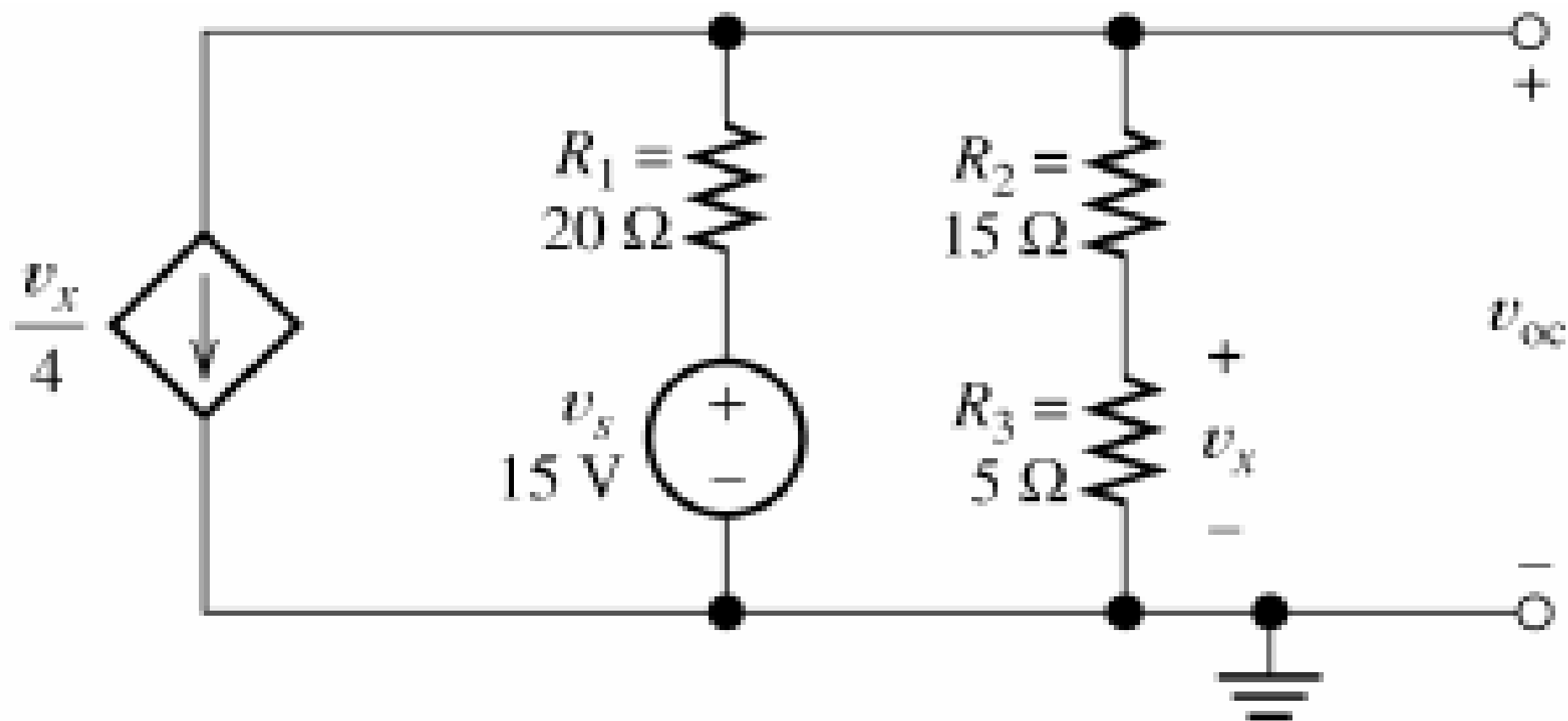Example: Find the Norton equivalent for the following circuit




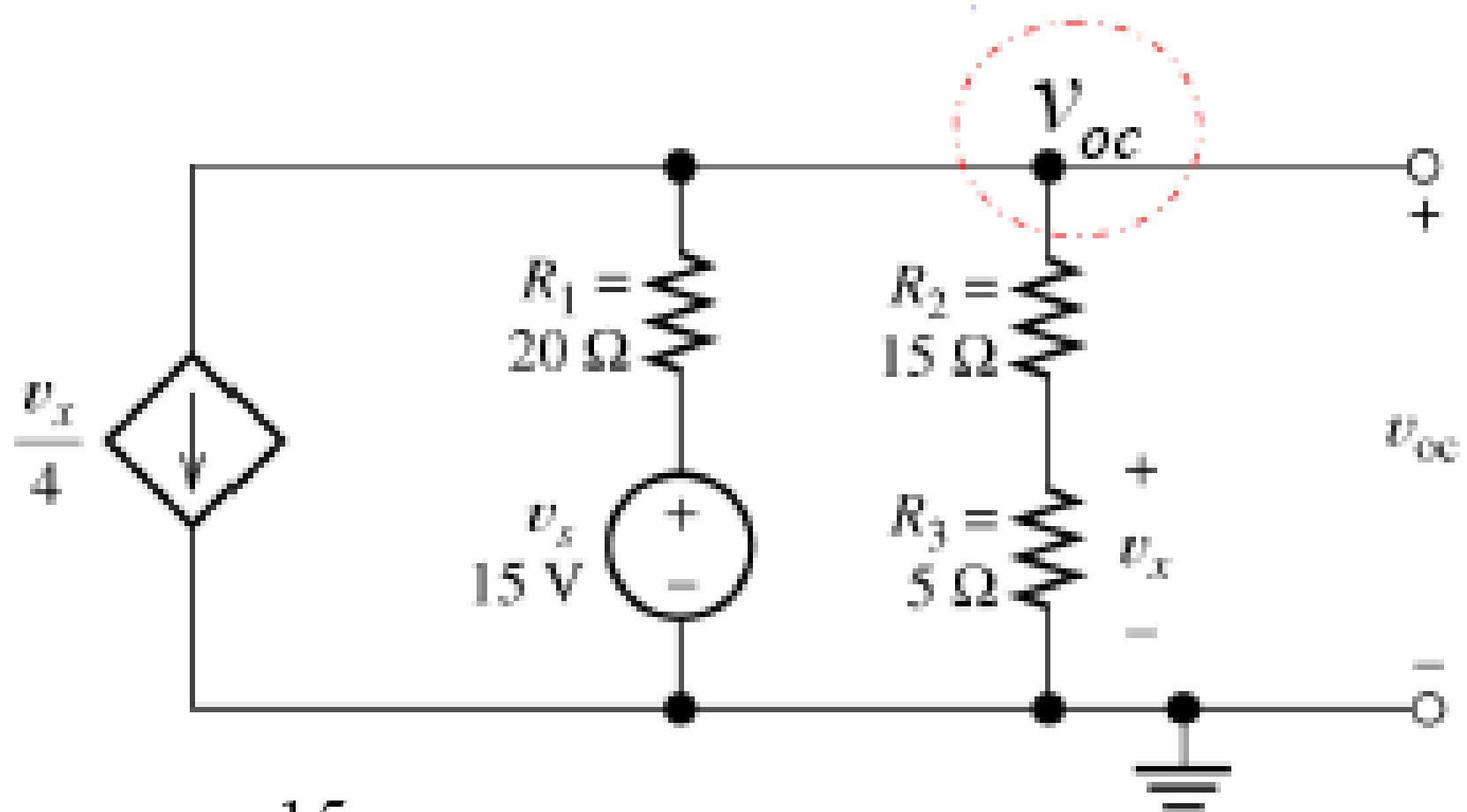

$$\frac{v_x}{4} + \frac{v_{oc} - 15}{R_1} + \frac{v_{oc}}{R_2 + R_3} = 0$$


$$v_x = \frac{R_3}{R_2 + R_3} v_{oc} = 0.25 v_{oc}$$

$$v_{oc} = 4.62\text{V}$$

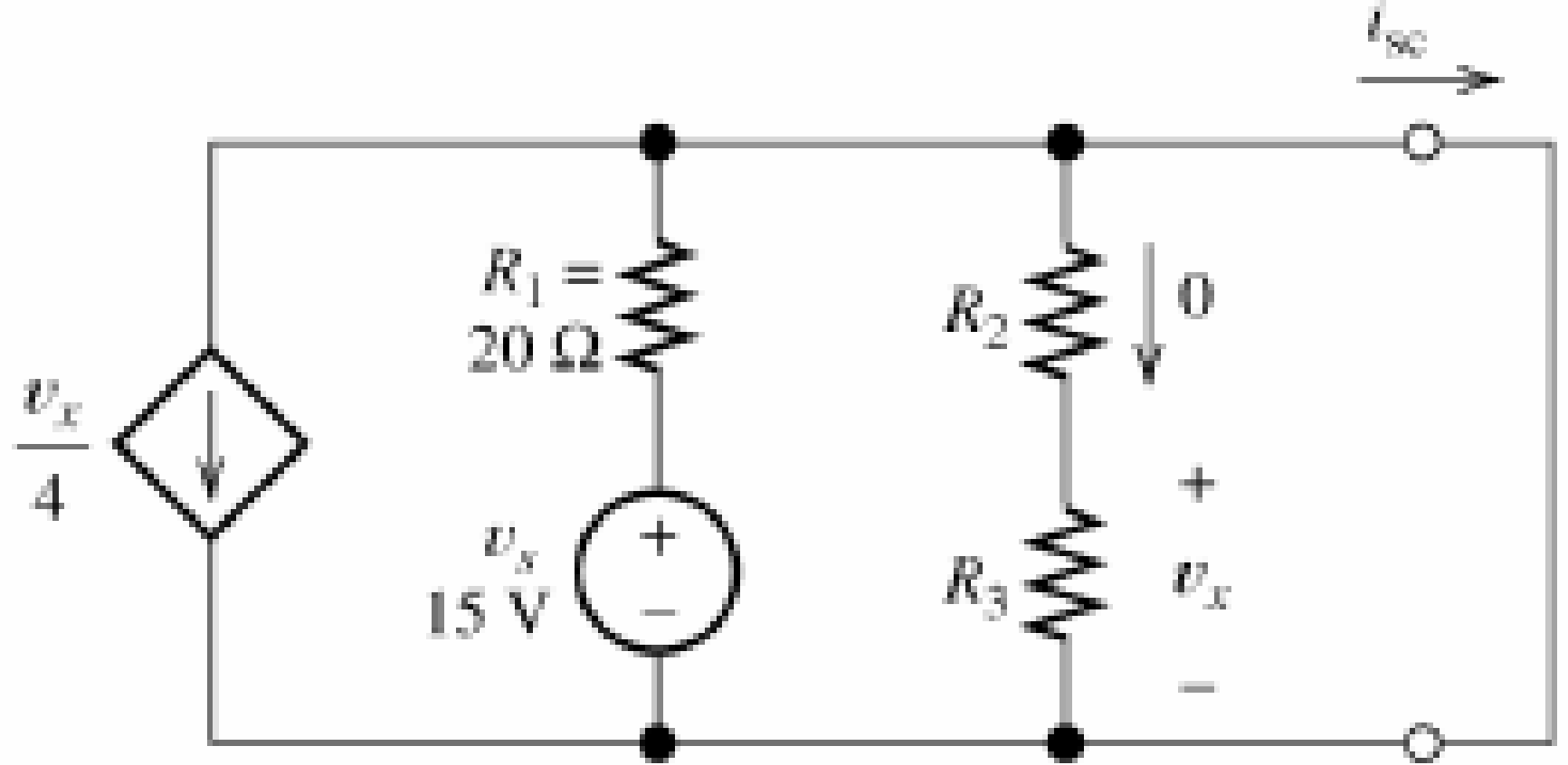

$$i_{sc} = \frac{v_s}{R_1} = \frac{15\text{V}}{20\Omega} = 0.75\text{A}$$

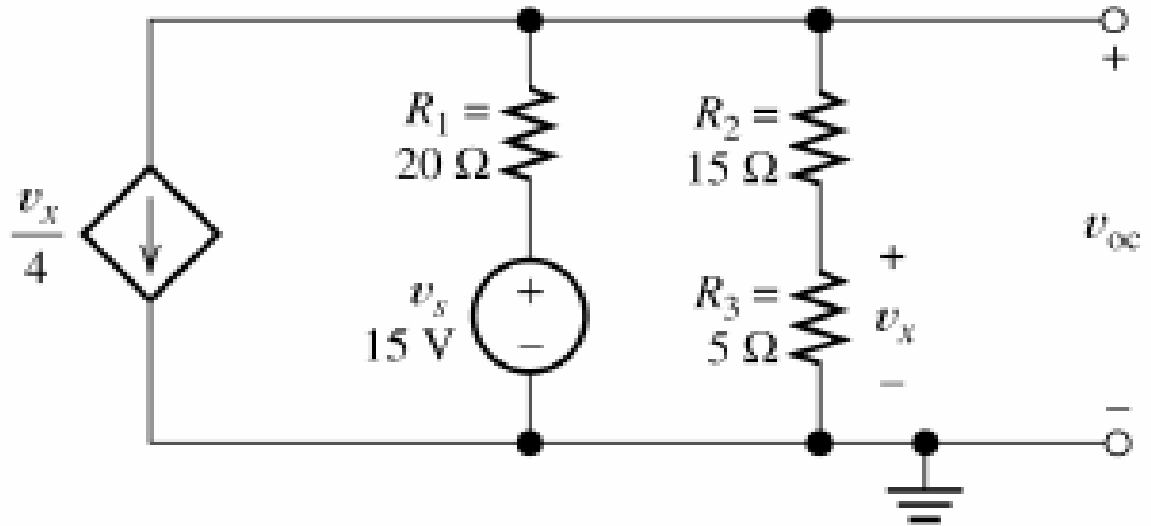
$$R_t = \frac{v_{oc}}{i_{sc}} = \frac{4.62\text{V}}{0.75\text{A}} = 6.15\Omega$$





Norton's equivalent

$$v_{oc} = 4.62V$$


$$R_t = 6.15 \Omega$$

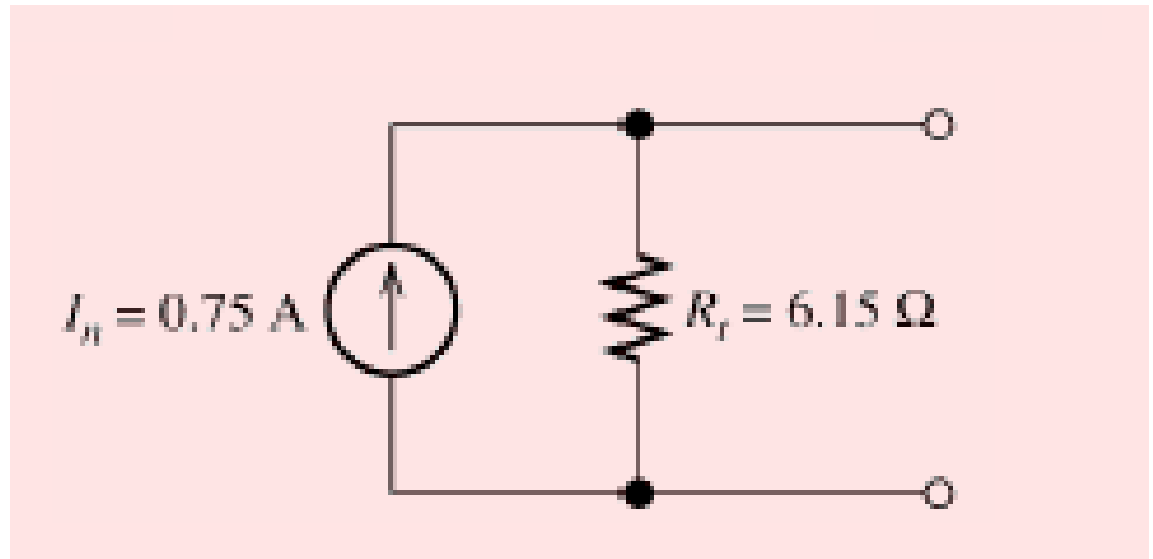

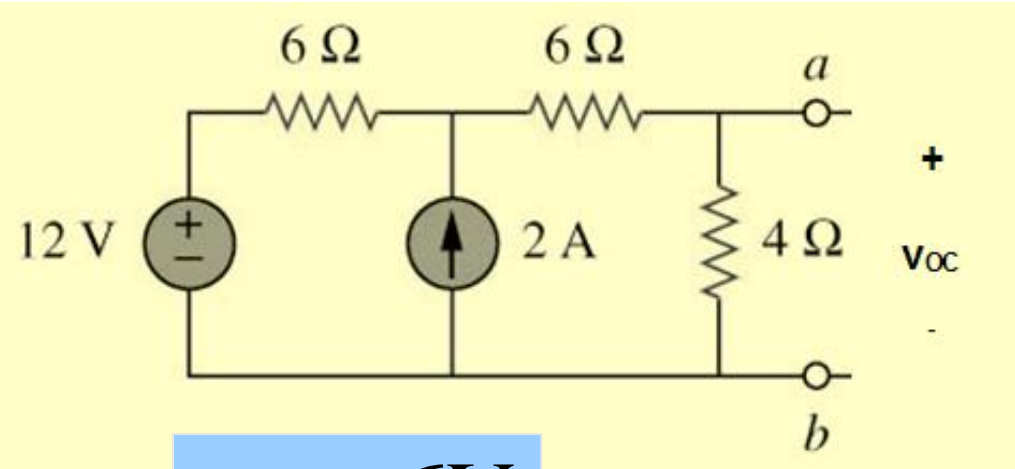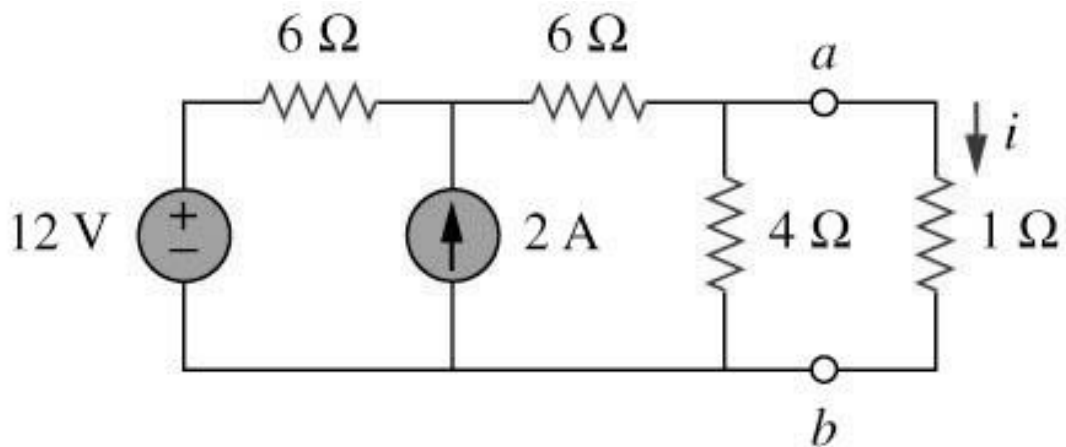
Using Thevenin's theorem, find the equivalent circuit to the left of the terminals in the circuit shown below. Hence find i .



$$V_{oc} = 6V$$

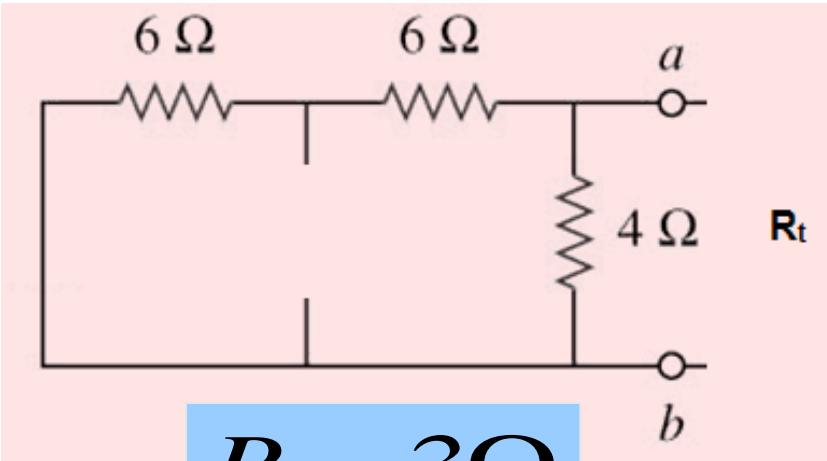


$$R_t = 3\Omega$$

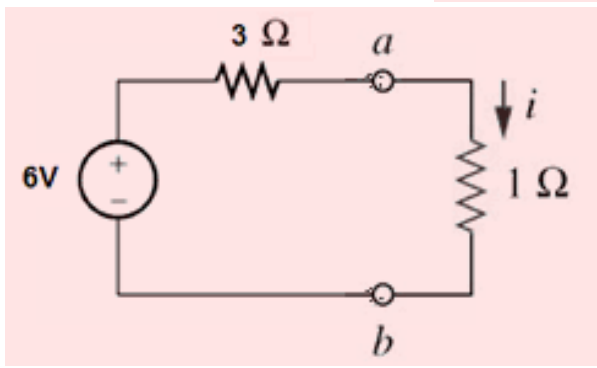


$$i = 1.5A$$

Use Superposition


$$v_{oc} = 6V$$

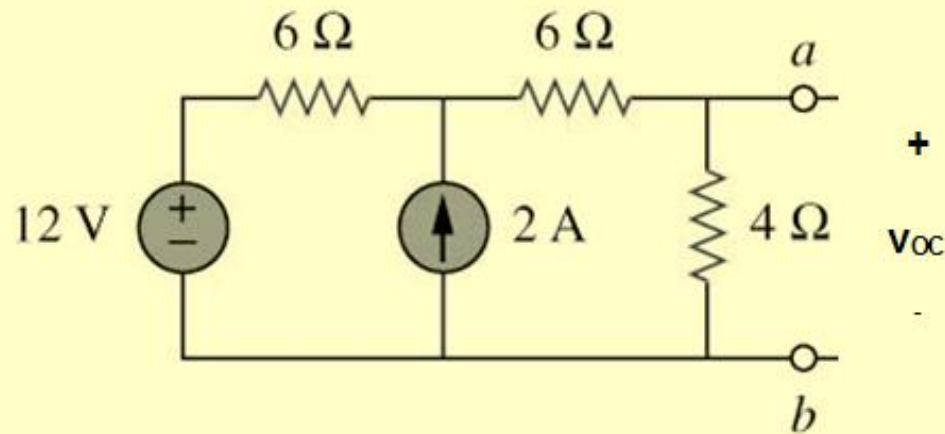

$$V_{oc} = V_{oc1} + V_{oc2} = 6$$

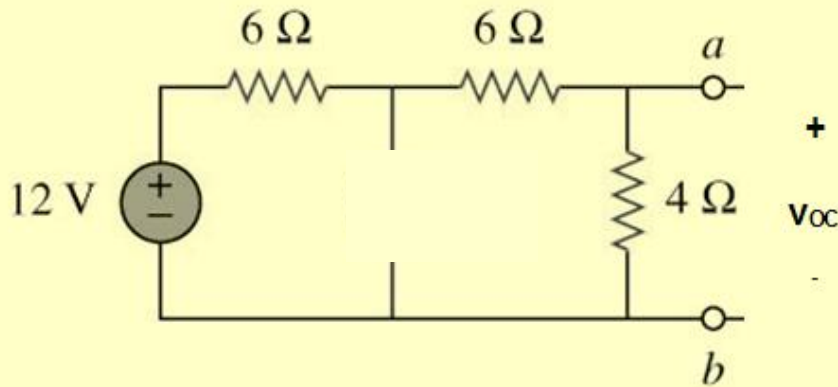

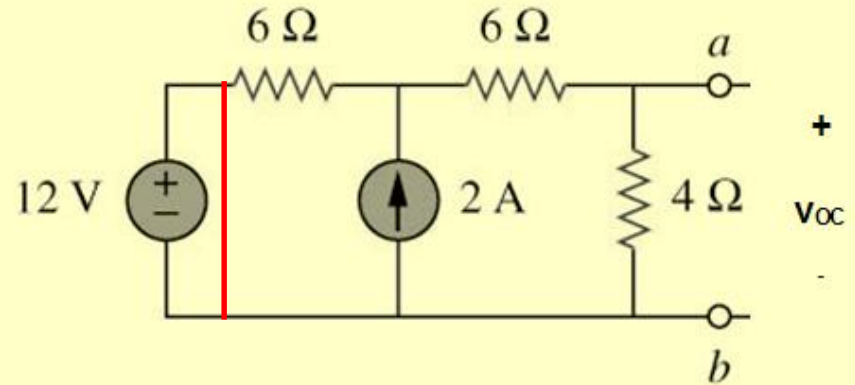
$$V_{oc1} = \frac{4}{4+12} \times 12 = 3$$






$$V_{oc2} = 4 \times \left(2 \times \frac{6}{6+10} \right) = 3$$


Source Transformation

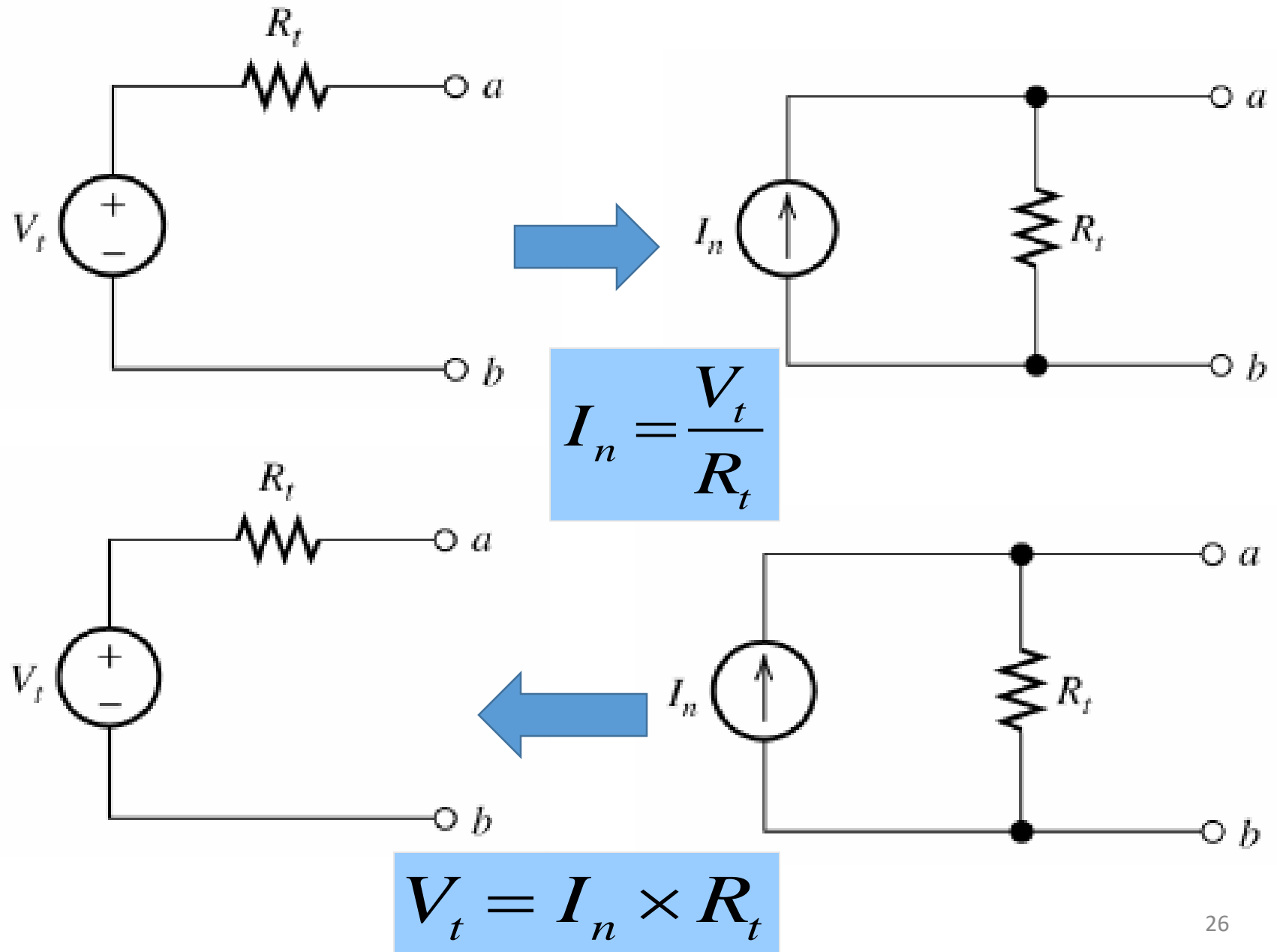


Example

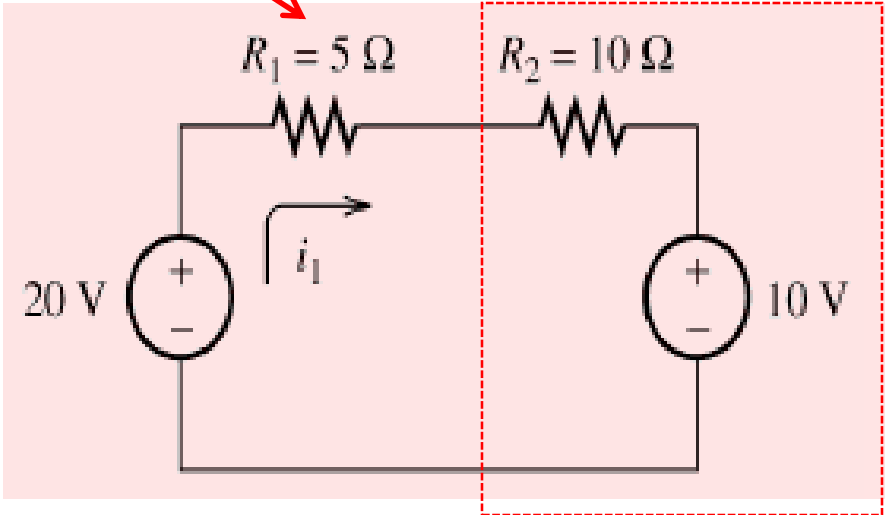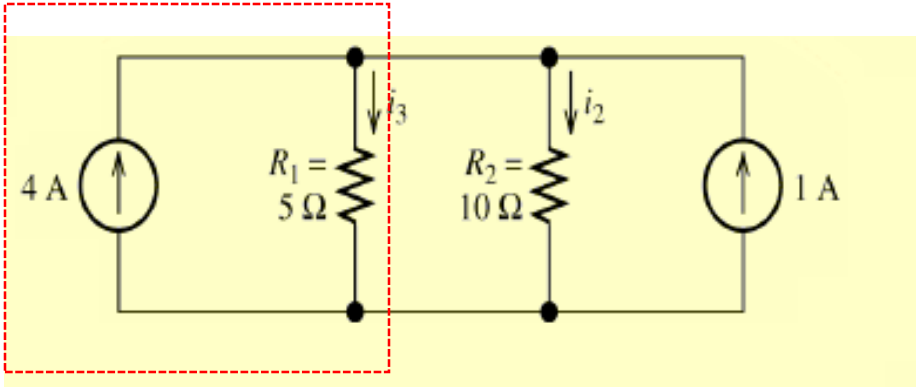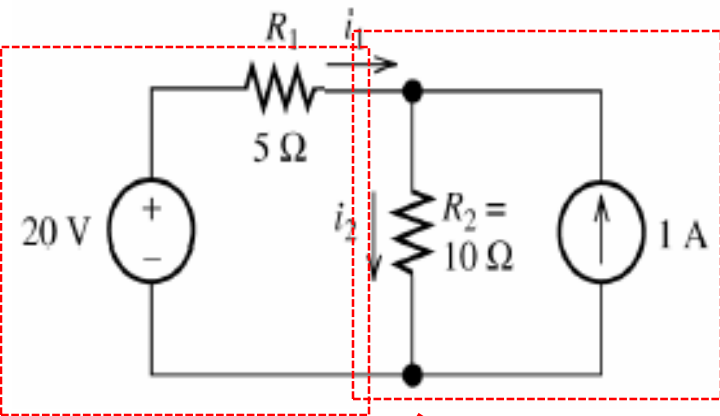

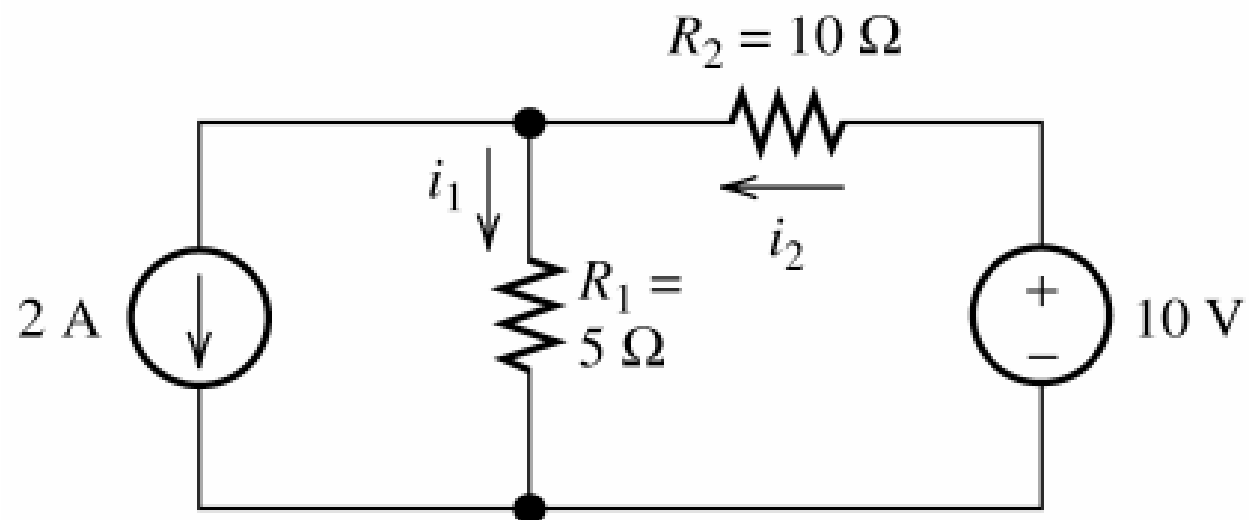Use source transformation to solve for the indicated currents



Maximum Power Transfer for dc circuits

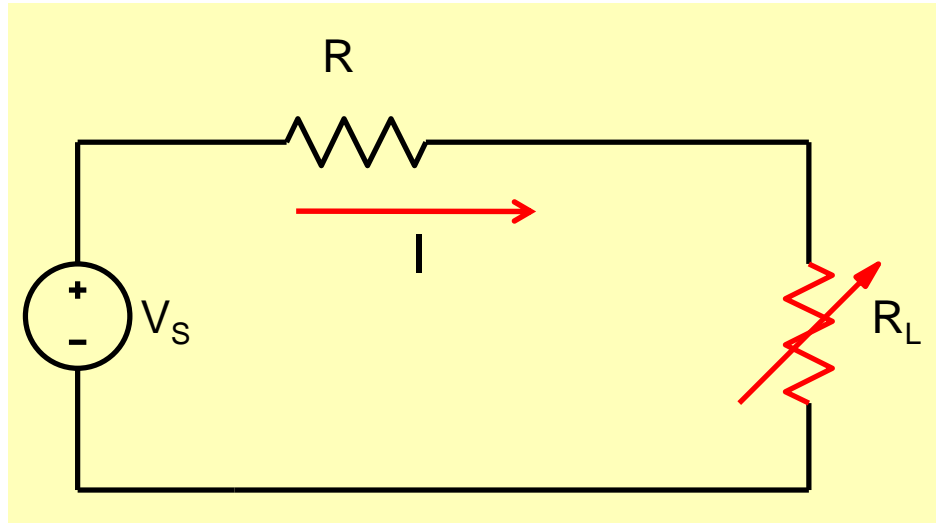

What value of R_L will give rise to maximum load power ?


$$I = \frac{V_s}{R + R_L}$$

$$P_L = I^2 R_L = V_s^2 \times \frac{R_L}{(R + R_L)^2}$$

$$\frac{\partial P_L}{\partial R_L} = 0$$

$$R_L = R$$

$$P_{L\max} = \frac{V_s^2}{4R_L}$$


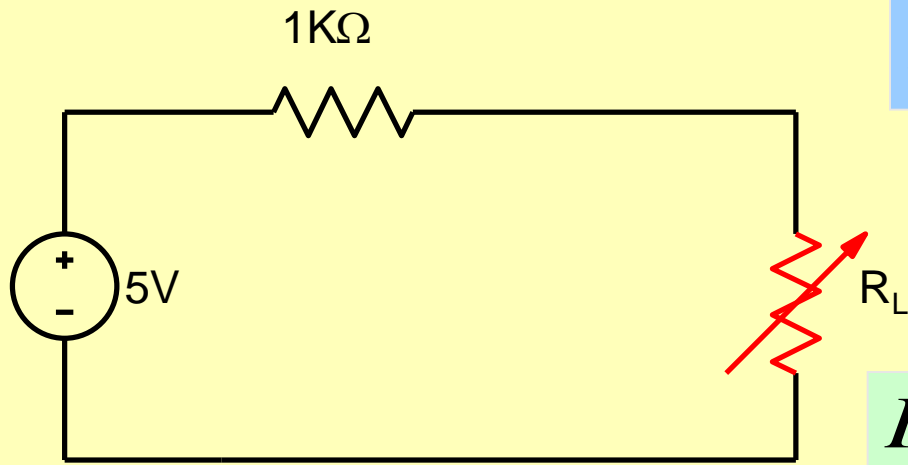


$$R_L = 1K \Rightarrow P_L = 6.25mW$$



$$R_L = 10K \Rightarrow P_L = 2mW$$

$$R_L = 0.2K \Rightarrow P_L = 3.47mW$$

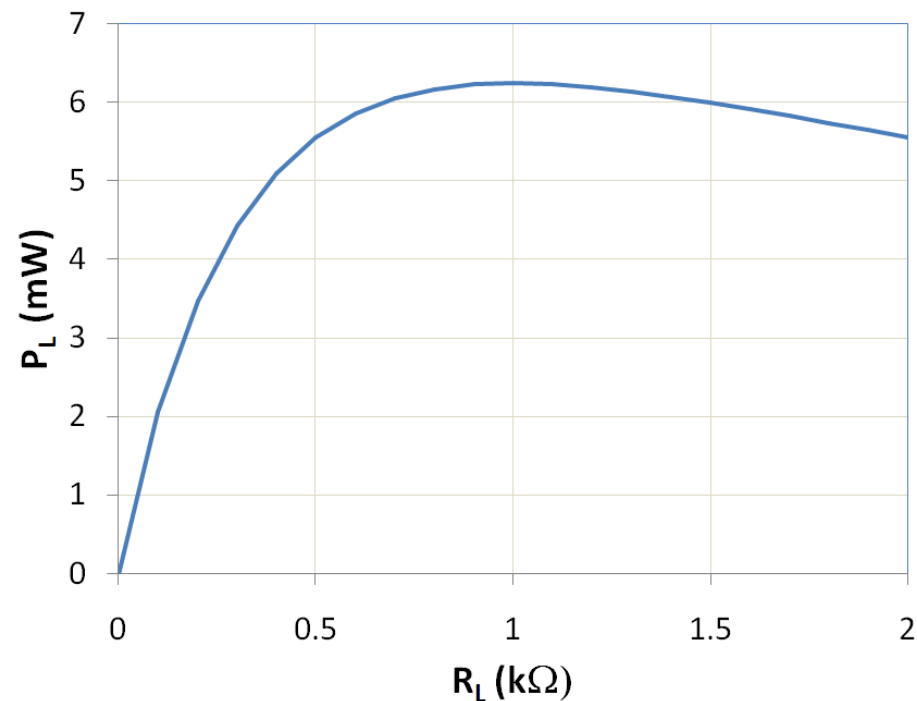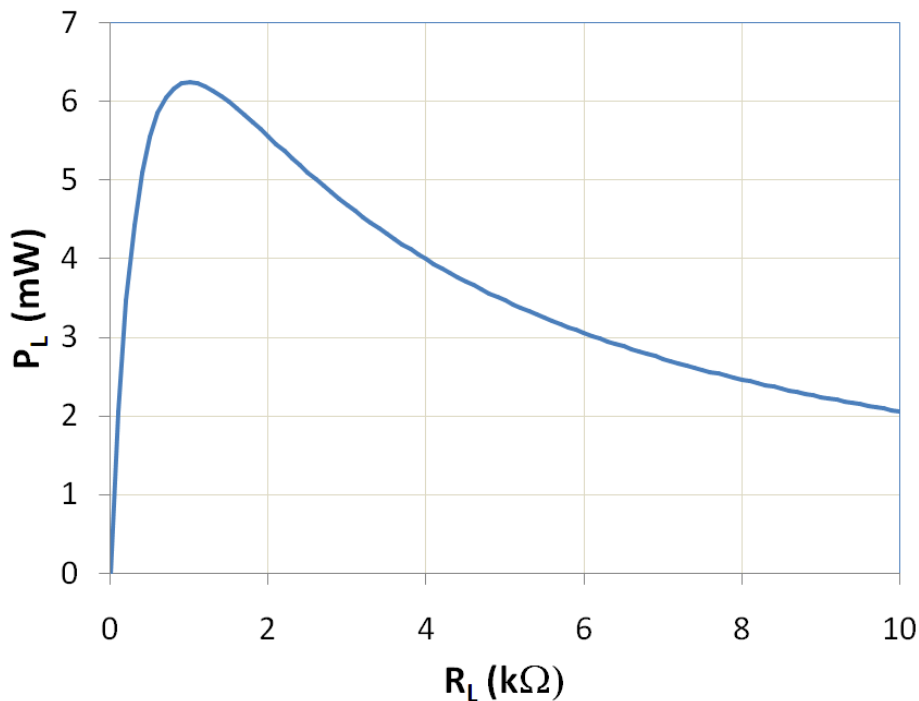Maximum power is delivered to the load when **$R_L = R$**





General Case

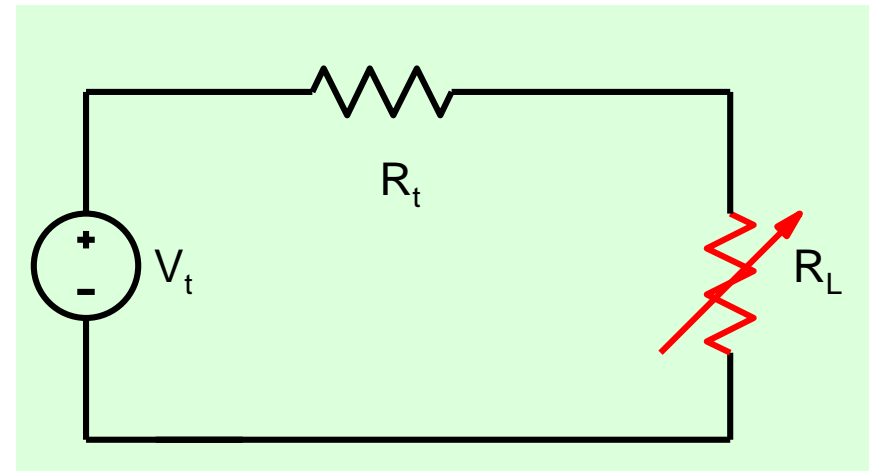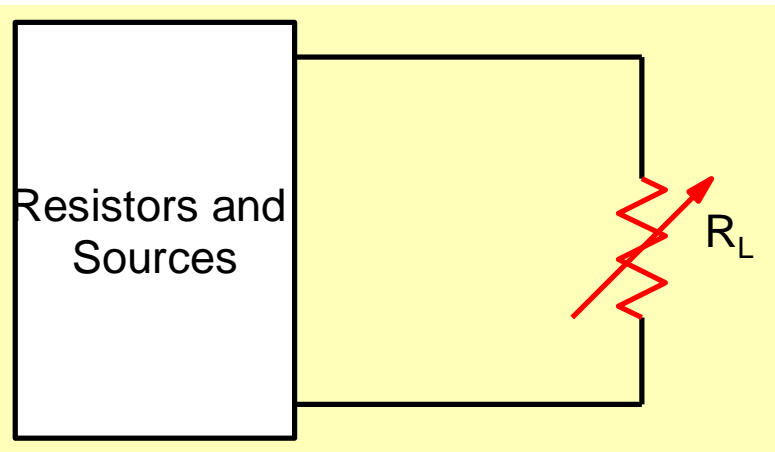


Maximum power is delivered to the load when $R_L = R_t$

Summary

Series/Parallel resistances

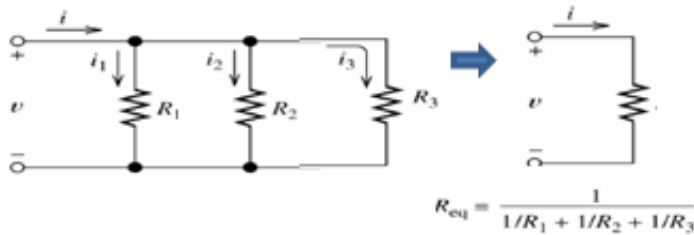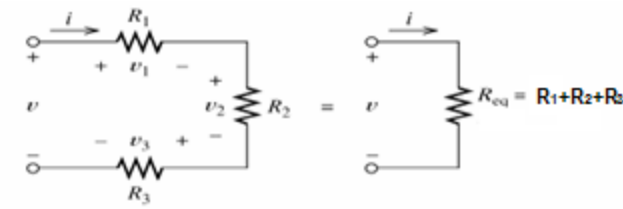


Voltage division

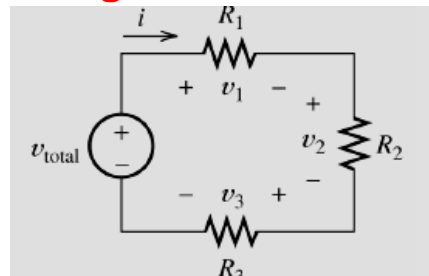

$$v_2 = R_2 i = \frac{R_2}{R_1 + R_2 + R_3} v_{total}$$

$$i_2 = \frac{v}{R_2} = \frac{R_1}{R_1 + R_2} i_{total}$$


Current division

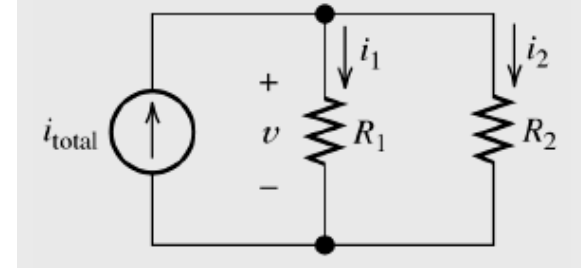

Mesh Analysis

1. Assign mesh currents i_1, i_2, \dots, i_n to the n meshes.
2. Apply KVL to each of the n meshes. Use Ohm's law to express the voltages in terms of the mesh currents.
3. Solve the resulting n simultaneous equations to get the mesh currents.

Source Transformation

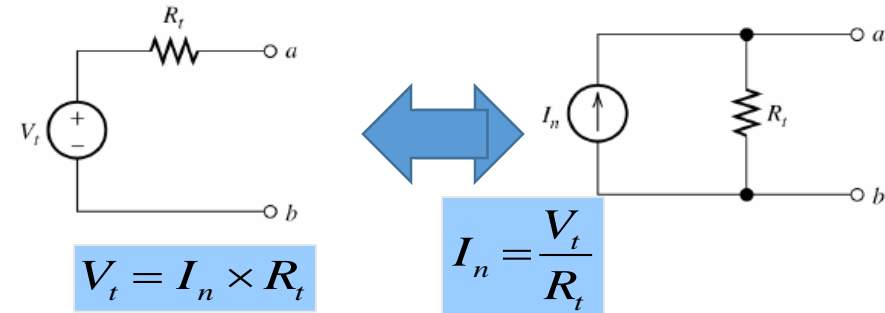


The **superposition principle** states that the total response is the sum of the responses to each of the independent sources acting individually.

Nodal Analysis:


1. Identify and number the nodes
2. Choose a reference node
3. Write KCL for each node such that

Sum of currents leaving a node is zero.


Super node

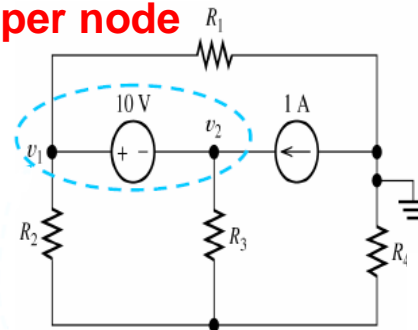


$$V_t = v_{oc}$$

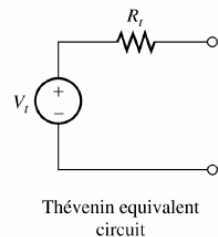

$$R_t = \frac{v_{oc}}{i_{sc}}$$

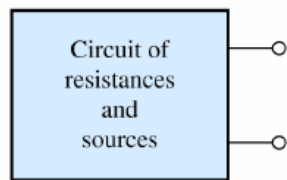

$$I_n = i_{sc}$$

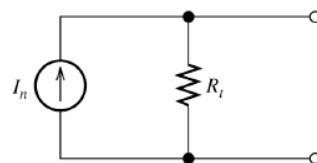

Thevenin & Norton

Labs

Link for Handouts:

https://iitk-my.sharepoint.com/:f/g/personal/mnisha_iitk_ac_in/EmZwnMY48-NGmHIMZ7ZmXyEBhKhAR4qfJhuSYm03pHGDIA?e=W8AXrz

Weekly Schedule:

Week	Monday M1 - M4	Tuesday Tu1 - Tu4	Wednesday W1 - W4	Thursday Th1 - Th4	Friday F1 - F4	Saturday
00: A01-A05						
01: A08-A12	E1	Moharram	E1	E1	E1	E1 (Tu)
02: A15-A19	Indep. Day	E2	E2	E2	Janmashtami	E2 (M)
03: A22-A26	E3	E3	E3	E3	E2	E3 (F)
04: A29-S02	E4	E4	E4	E4	E4	
05: S05-S09	E5	E5	E5	E5	E5	
06: S12-S16	Make Up					
07: S19-S23	Mid Semester Exam					
08: S26-S30	E6	E6	E6	E6	E6	
09: O03-O07	Mid Semester Recess					
10: O10-O14	E7	E7	E7	E7	E7	
11: O17-O21	E8	E8	E8	E8	E8	
12: O24-O28	Diwali	E9	E9	E9	E9	E9 (M)
13: O31-N04	Makeup					
14: N07-N11	Lab Examination					
15: N14-N18	End Semester Exam					
16: N21-N25	End Semester Exam					

Link to youtube videos for labs have also been provided in resources document