
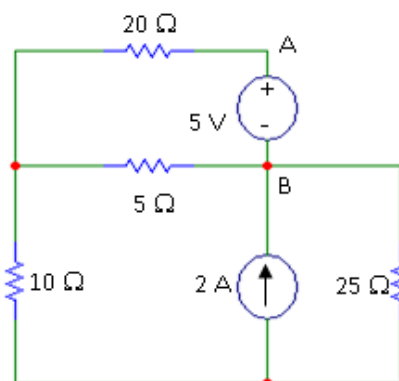


**Assignment-2**

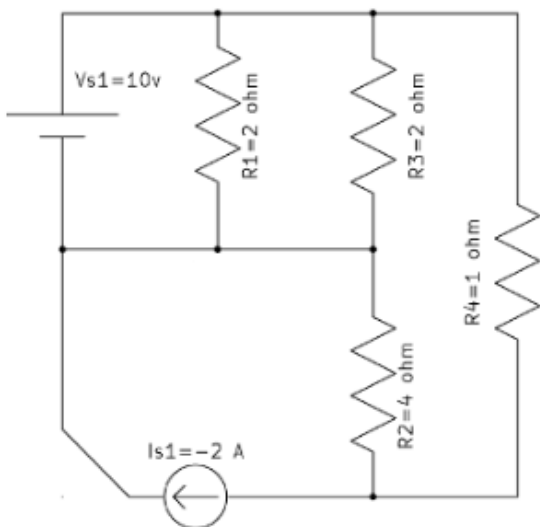
1. Determine the power supplied by the 5V source using
  - a. Mesh analysis
  - b. Nodal analysis
  - c. Superposition principle
  - d. Thevenin's equivalent circuit between terminals A and B.




2. Solve the circuit by nodal analysis and find the power through the current source IS1.



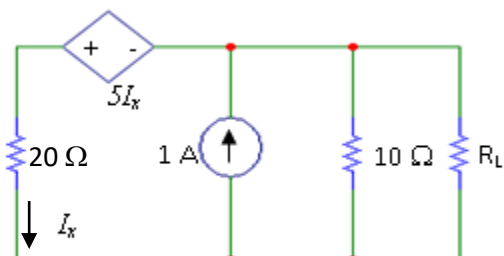
3. Determine the value of  $R_L$  in the following circuit such that maximum power is delivered into  $R_L$ . Calculate the value of the maximum power.



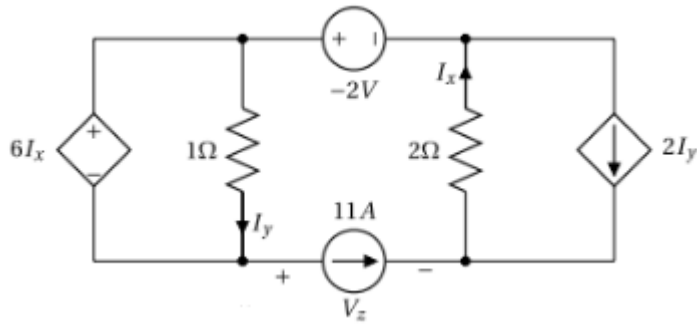4. Determine  $I_x$ ,  $I_y$  and  $V_z$  using superposition:



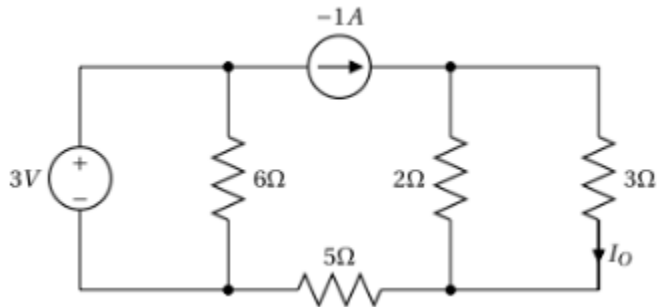5. Use Thevenin's theorem to determine  $I_o$ .



6. Determine  $V_R$  in the following circuit at  $t=0^-$  and  $0^+$ , if the device  $X$  is (a) an inductor and (b) a capacitor. The switch is closed at  $t=0$ .

