

# ESC201A Quiz2 Set B

SAMYAK SINGHANIA

TOTAL POINTS

**8 / 11**

QUESTION 1

**Q1** 6 pts

1.1 **Q1(a)** 4 / 4

✓ + 4 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1 pts VBB eq correct

+ 1 pts VBB calculation correct

+ 1 pts VCC eq correct

+ 1 pts VCC calculation correct

1.2 **Q1(b)** 1 / 2

+ 2 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1 pts  $V_s = +2V$  case analyzed correctly

✓ + 1 pts  $V_s = -2V$  case analyzed correctly

correctly

✓ + 1 pts Expressions for  $g_m$  and  $r_{pi}$  correct

+ 1 pts  $v_o/i_s$  expression correct

+ 1 pts  $v_o/i_s$  value correct

+ 2 Point adjustment

💬 small signal model only partially correct,  
partial marks for correct approach

QUESTION 2

2 **Q2** 3 / 5

+ 5 pts Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 2 pts Small signal model of circuit drawn

Name: SAMYAK SINGHANIARoll. No. 210917Section: W3

Q.1(a) Determine the value of voltage  $V_{BB}$  so that dc emitter current is 0.5mA. Determine also the minimum supply voltage  $V_{CC}$  necessary so that transistor operates in forward active mode. Assume that current gain  $\beta_F = 200$ . [4 Marks]

$$I_E = I_B + I_C \quad (\text{in forward active mode})$$

$$I_C = I_B + 200 I_B = 201 I_B$$

$$V_{BB} = 50.2K(I_B) + 0.7 + 0.5K \times 0.5m$$

$$= 50.2 \times 10^3 \times \frac{0.5 \times 10^{-3}}{201} + 0.7 + 0.25$$

$$= 0.1248 + 0.7 + 0.25 = 1.07V$$


$$\therefore V_{BB} = 1.07V$$

For forward active  $V_{CE} > 0.2V$ .

$$\text{Now, } V_{CC} = (2K)I_C + V_{CE} + 0.5K \times 0.5m$$

$$V_{CE} = V_{CC} - 0.25 - 2 \times 10^3 \times \frac{200}{201} \times 0.5 \times 10^{-3} \Rightarrow (V_{CC} - 1.25) > 0.2V$$
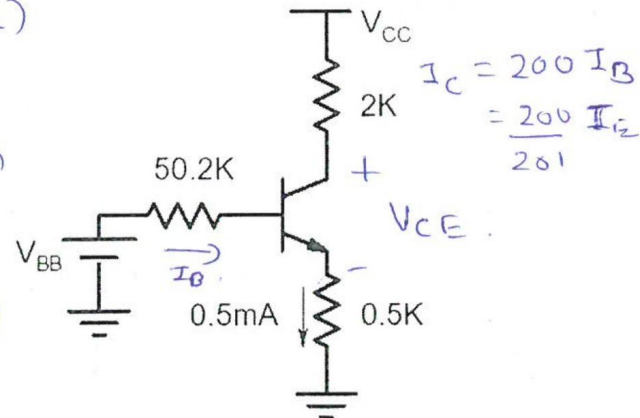
$$\therefore \boxed{V_{CC} > 1.45V} \quad \therefore \text{Minimum supply voltage } V_{CC} \text{ should be greater than } 1.45V$$



(b) Determine the output for the ideal opamp circuit shown below. Assume that diodes have cut-in voltage of 0.7V. Analyze the circuit for  $V_S = 2V$  and  $V_S = -2V$ . [2 Marks]


$$V_+ = V_- = 0V$$

$$\text{When } \boxed{V_S = -2V}$$

$$\text{Current} = \frac{2}{2K} = 1mA \text{ in left}$$

$$\Rightarrow \frac{0 - V_O}{1K} = 1mA$$
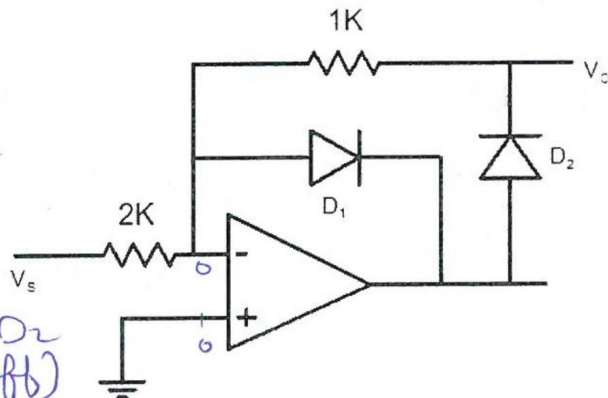
$$\Rightarrow \underline{V_O = -1V} \quad (D_1 \text{ \& } D_2 \text{ are off})$$



$$\text{When } \underline{V_S = 2V}$$



$$\text{Current} = \frac{2-0}{2K} = 1mA \text{ in right}$$

$$\Rightarrow \frac{0 - V_O}{1K} = 1mA \Rightarrow \underline{V_O = -1V} \quad (D_1 \text{ \& } D_2 \text{ are off})$$

Q.2 For the circuit shown below, carry out ac analysis to determine the ratio  $\frac{v_o}{i_s}$ , where

$v_o$  is ac output voltage and  $i_s$  is ac sinusoidal current. Assume that transistor is biased in forward active mode and current gain  $\beta_F = 200$ . [5 Marks]

Ac analysis:

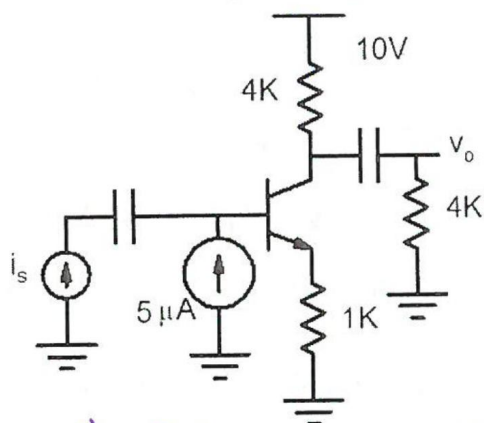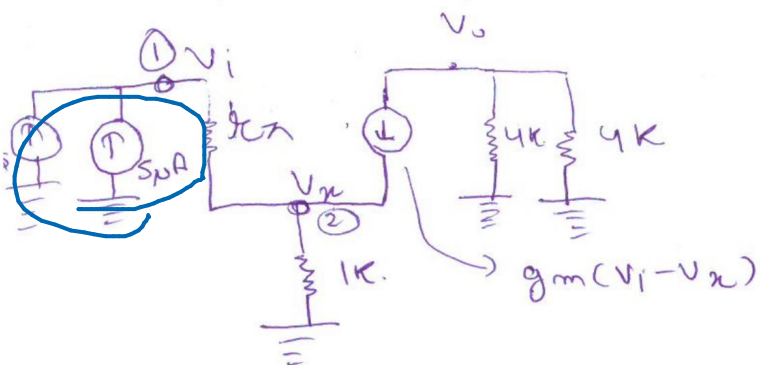

in DC analysis, clearly,  
 $I_B = 5\mu A$

$$\therefore I_C = 200 I_B = 1mA$$

$$g_m = \frac{I_C}{V_T} = \frac{1mA}{26mV} = 0.038$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{200}{g_m}$$

Applying KCL at Node ①, we get

$$5\mu A + i_s = \frac{v_i - v_{\pi}}{r_{\pi}}$$

$$v_o = -g_m(v_i - v_{\pi}) \times 2K$$

$$\text{Also, } \frac{v_{\pi}}{1K} = I_E = 201 I_B \Rightarrow v_{\pi} = 1 \times 10^3 \times 201 \times 5 \times 10^{-6} = 1005 \times 10^{-3} V$$

$$\text{Also, at node ②, } \frac{v_i - v_{\pi}}{r_{\pi}} + g_m(v_i - v_{\pi}) = \frac{v_{\pi}}{1K} \Rightarrow (v_i - v_{\pi}) \left( \frac{201 g_m}{200} \right) = \frac{v_{\pi}}{1K}$$

$$\Rightarrow 5\mu A + i_s + g_m(v_i - v_{\pi}) = 201 \times 5\mu A$$

$$\Rightarrow g_m(v_i - v_{\pi}) = 200 \times 5\mu A - i_s \quad - (1)$$

$$\frac{g_m(v_i - v_{\pi})}{r_{\pi}} = \frac{v_i - v_{\pi}}{r_{\pi}} = 5\mu A + i_s$$

$$\Rightarrow 200(v_i - v_{\pi}) = 200 \times 5\mu A + 200 i_s \quad - (2)$$

$$\text{eq ①} - \text{eq ②} \Rightarrow (v_i - v_{\pi}) \left[ \frac{200}{r_{\pi}} - g_m \right] = 201 i_s$$

$$\Rightarrow (v_i - v_{\pi}) \left( \frac{201}{200} \times 0.038 \right) = 201 \times 5\mu A \quad \Rightarrow v_{\pi} = 38.19(v_i - v_{\pi})$$

$$\Rightarrow 38.19 v_i = 39.19 v_{\pi}$$

$$v_o = -g_m \frac{v_{\pi}}{38.19} \times 2K$$

$$i_s = \frac{v_{\pi} g_m}{38.19 \times 200} - 5\mu A$$

$$i_s = \frac{v_{\pi}}{201K} - 5\mu A$$

$$\frac{v_o}{i_s} = \frac{-g_m \frac{v_{\pi}}{38.19} \times 2K}{\frac{v_{\pi}}{201K} - 5\mu A}$$