

# ESC201A MidSem Part1

SAMYAK SINGHANIA

TOTAL POINTS

**12.5 / 19**

QUESTION 1

**Q1** 7 pts

1.1 1(a) 2 / 2

- ✓ **+ 2 pts** Completely Correct
- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- + 1 pts Region I/III correctly eliminated
- + 1 pts  $I_x$  calculated correctly, region assumption verified

1.2 1(b) 2.5 / 5

- + 5 pts Completely Correct
- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- + 4 pts Four transformations correct
- + 3 pts Three transformations correct
- + 2 pts Two transformations correct
- + 1 pts One transformation correct
- + 2.5 Point adjustment

QUESTION 2

**Q2** 7 pts

2.1 2(a) 3 / 3

- ✓ **+ 3 pts** Completely Correct

- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- + 1 pts  $Z_{eq}$  calculated correctly
- + 1 pts Resonance condition identified
- + 1 pts  $L$  value found correctly

2.2 2(b) 1 / 4

- + 4 pts Completely Correct
- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- ✓ **+ 1 pts**  $i_{rms}$  correct
- + 2 pts Power Factor calculated correctly
- + 1 pts Reactive power correct


QUESTION 3

3 **Q3** 4 / 5

- + 5 pts Completely Correct
- + 0 pts Completely Incorrect
- + 0 pts Not Attempted
- + 0 pts Copied
- ✓ **+ 0.5 pts**  $v(t)$  formula correct
- ✓ **+ 0.5 pts**  $v(0+)$  calculation correct
- ✓ **+ 1.5 pts**  $v_{\infty}$  calculation correct
- ✓ **+ 1.5 pts**  $R_{eq}$  calculated correctly
- + 1 pts  $C$  calculated correctly

Name **SAMYAK SINGHANIA** Roll No. **210517** Seat/Room No. **128 / L-10**

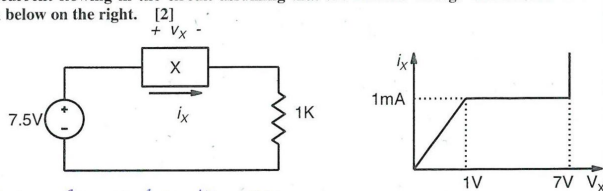1 (a). Determine the current flowing in the circuit assuming that the current-voltage characteristics of element X is as shown below on the right.



Since  $V_s = 7.5V$ , let's assume  $V_x = 7V$ .  
 $\therefore -7.5 + i_x(1K) = 0$   
 $i_x(1K) = 7.5$   
 $i_x = 7.5mA$   
 $\therefore$  not possible  
 $i_x(1K) = 0.5$   
 $i_x = 0.5mA$   
 $\therefore$  not possible

We can say that  $i_x = (7.5 - V_x) mA$ .


If  $i_x > 1mA \Rightarrow V_x < 6.5V$  (Not possible)

If  $i_x < 1mA \Rightarrow V_x > 6.5V$  (Not possible)


\*  $i_x = 1mA \Rightarrow V_x = 6.5V$  This satisfies the characteristics of element X

$\therefore i_x = 1mA$

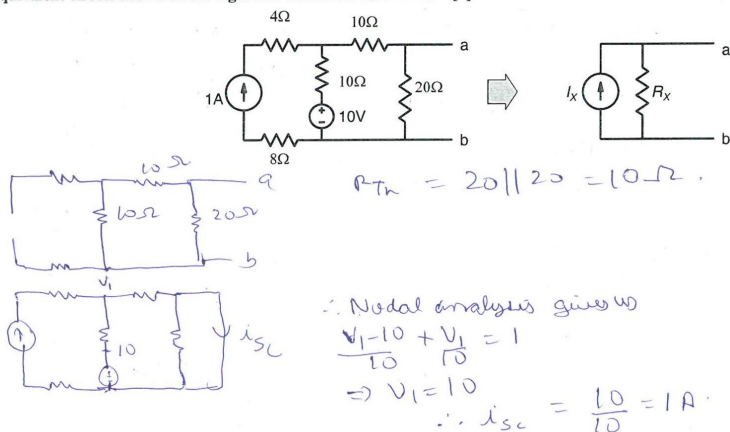
1 (b). Using Source transformation only, show that the circuit below on the left can be transformed into the equivalent circuit shown on the right and determine  $I_x$  and  $R_x$ . [5]



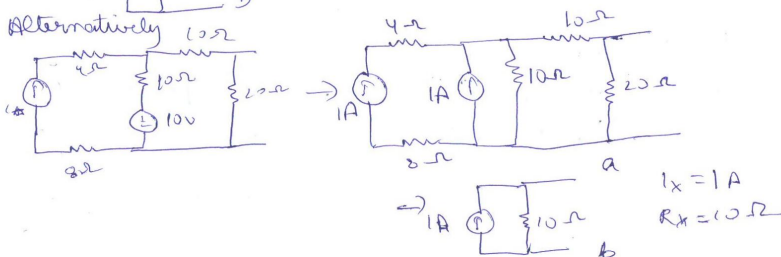Using Norton equivalent, we can transform the circuit  
 into  $I_x$  and  $R_x$  where  $I_x = 1A$   
 $R_x = 10\Omega$



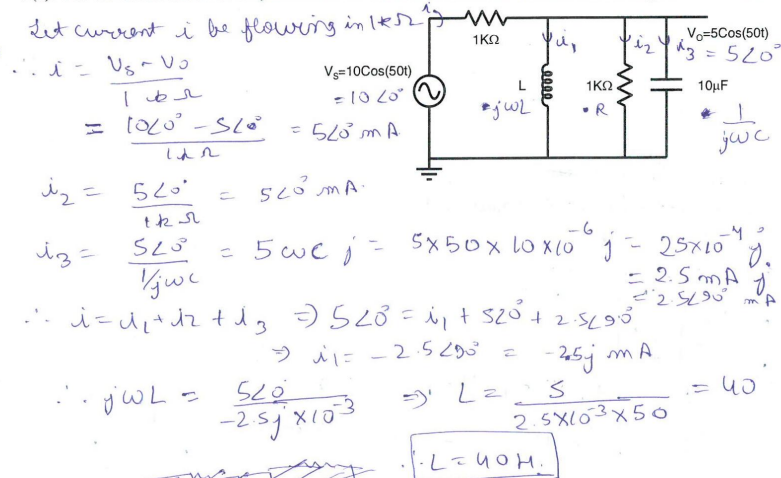2(a). For the circuit shown below, determine the value of inductor for the indicated voltages. [3]



2(b). For the circuit shown below, determine the reactive power taken from the supply if the power dissipated in each of the resistors is 5W and  $V_S = 20\cos(5t)$ . [4]


$$5W = i^2 R \Rightarrow i = 1A$$

$$= 1A$$

$$i^2 R = 5W$$

$$R' = R + \frac{1}{j\omega C}$$
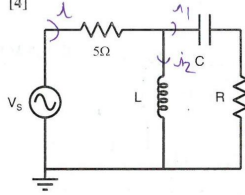
$$P' = \frac{(R + \frac{1}{j\omega C})(j\omega L)}{R + \frac{1}{j\omega C} + j\omega L}$$




~~is in phase with~~

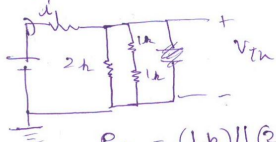3. A capacitor voltage of 1V was measured 2ms after the switch was closed in the circuit shown below. Determine the value of the capacitor assuming that switch had been open initially for a very long time. [5]

$$V(0) = V(\infty) = 0V$$



Drawing the Thevenin equivalent for the circuit



$$R_{TH} = (1k) \parallel (2k) \parallel (2k) = \frac{1}{2}k\Omega$$

$$i_1 = \frac{5}{2}mA$$
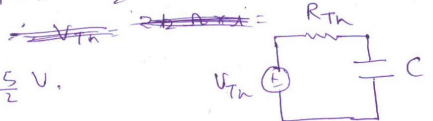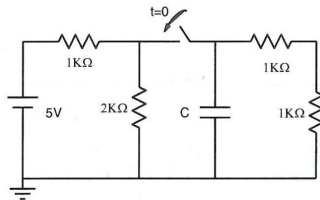
$$V_{TH} = 1k\Omega \times \frac{5}{2}mA = \frac{5}{2}V$$



$$V(t) = V(\infty) + (V(0) - V(\infty))e^{-\frac{t}{RC}}$$

$$V(\infty) = V_{TH} = \frac{5}{2}V$$

$$V(0) = 0V$$

$$\therefore V(1) = \frac{5}{2} \left(1 - e^{-\frac{1}{RC}}\right) V$$

$$V(2ms) = 1V = \frac{5}{2} \left(1 - e^{-\frac{2ms}{RC}}\right)$$

$$\Rightarrow 1V = \frac{5}{2} \left(1 - \left(1 - \frac{2ms}{RC}\right)\right)$$

$$\Rightarrow 1 = \frac{5}{2} \times \frac{2 \times 10^{-3}}{RC}$$

$$C = \frac{5 \times 10^{-3}}{\frac{1}{2} \times 10^3} = 10 \times 10^{-6} = 10\mu F$$

$$C = 10\mu F$$

Rough Work

$$12 + \frac{22 \times 20}{4221} = \frac{220}{21}$$

$$\frac{V_1}{10} + \frac{V-10}{10} = 1$$

$$2V - 10 = 10 \Rightarrow 2V = 20$$

$$V = 10$$

$$\frac{V-10}{10} + \frac{V}{30} = 1$$

$$3(V-10) + V = 30$$

$$3V - 30 + V = 30$$


$$4V = 60$$

$$V = 15$$

$$\frac{2}{2} = -0.5$$

$$\frac{1}{2} + \frac{1}{2} + \frac{1}{2}$$

$$\frac{1}{2}k\Omega$$

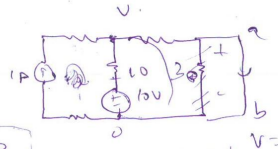

$$V = \frac{220}{21}$$

$$\frac{27 \times 5}{30} = 19$$