
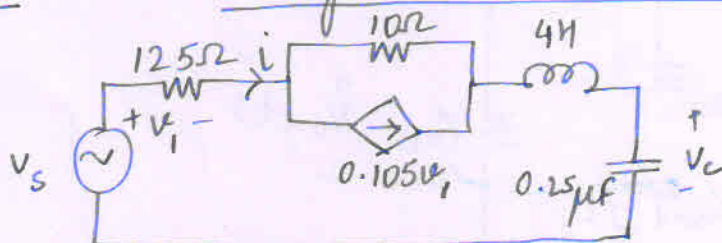


Ans 1.

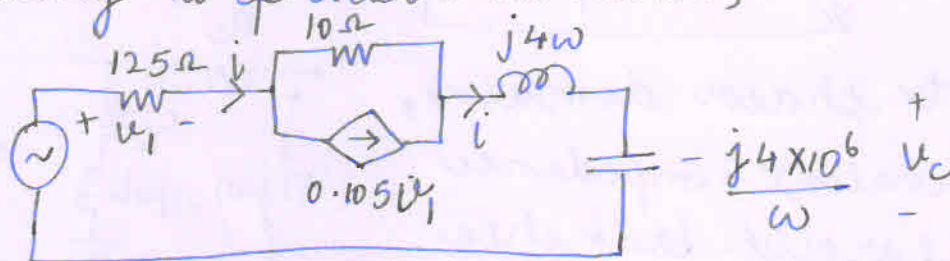

Let the current flowing in the circuit be i .

Converting to phasor domain,



$$V_1 = 125i$$

Applying KVL,

$$V_s - 125i - 10(i - 0.105V_1) - j4\omega i + \frac{j4 \times 10^6}{\omega} i = 0$$

$$\Rightarrow V_s - 125i - 10i + 1.05(125i) - j4\omega i + \frac{j4 \times 10^6}{\omega} i = 0$$

$$\Rightarrow V_s = 3.75i + j4\omega i - \frac{j4 \times 10^6}{\omega} i$$

$$\Rightarrow \frac{V_s}{i} = 3.75 + j4\left(\omega - \frac{10^6}{\omega}\right) \quad \text{--- (1)}$$

$$V_c = -\frac{j4 \times 10^6}{\omega} i$$

$$\text{or } \frac{V_c}{i} = -\frac{j4 \times 10^6}{\omega} \quad \text{--- (2)}$$

from (1) and (2),

$$\frac{V_c}{V_s} = \frac{-j4 \times 10^6 / \omega}{3.75 + j4(\omega - 10^6 / \omega)} = \frac{4 \times 10^6 / \omega}{-4(\omega - 10^6 / \omega) + j3.75}$$


$$\frac{V_c}{V_s} = \frac{4 \times 10^6 \omega}{-4(\omega - \frac{10^6}{\omega}) + j3.75} \times \frac{-4(\omega - \frac{10^6}{\omega}) - j3.75}{-4(\omega - \frac{10^6}{\omega}) - j3.75} \quad \text{Im} \left[\frac{V_c}{V_s} \right] = 0$$

$$\Rightarrow \omega^2 = 10^6 \quad \text{or } \omega = 10^3 \text{ rad/sec}$$


$$|H(j\omega)|_{\omega=1000} = \frac{4 \times 10^6 / 10^3}{3.75} = 1.066 \times 10^3$$

$$\therefore 20 \log |H(j\omega)|_{\omega=10^3} = 60.56 \text{ dB}$$

Ans 2.

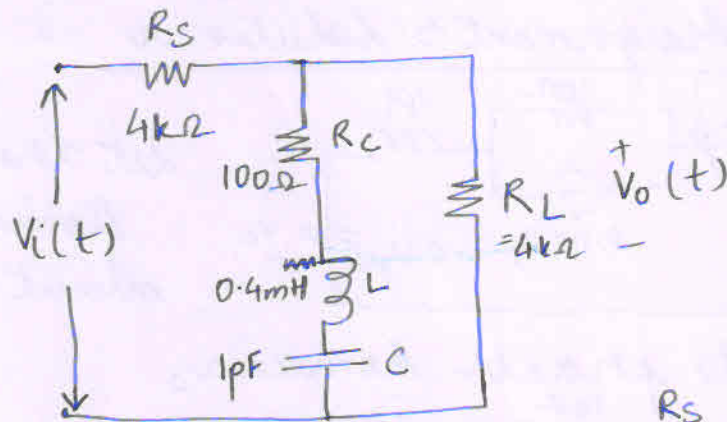

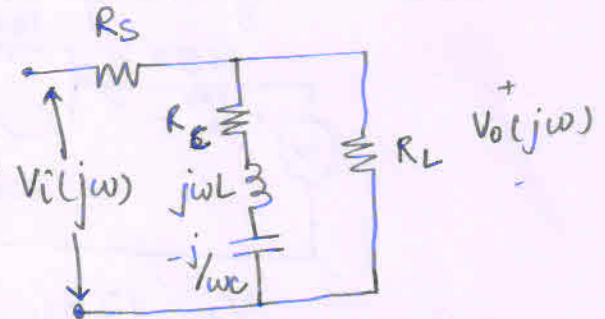Converting to phasor domain,
let the equivalent impedance
of the two parallel branches
be Z_1 .



$$\therefore Z_1 = R_L \parallel \left[R_C + j \left(\omega L - \frac{1}{\omega C} \right) \right]$$

$$\Rightarrow Z_1 = \frac{R_L \left[R_C + j \left(\omega L - \frac{1}{\omega C} \right) \right]}{R_L + R_C + j \left(\omega L - \frac{1}{\omega C} \right)}$$

Applying voltage division,

$$V_o(j\omega) = \frac{Z_1 \times V_i(j\omega)}{Z_1 + R_s}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{Z_1}{Z_1 + R_s}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L \left[R_C + j \left(\omega L - \frac{1}{\omega C} \right) \right]}{R_L + R_C + j \left(\omega L - \frac{1}{\omega C} \right) + R_s}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L R_C + j R_L \left(\omega L - \frac{1}{\omega C} \right)}{R_L R_C + j R_L \left(\omega L - \frac{1}{\omega C} \right) + R_s R_L + R_s R_C + j R_s \left(\omega L - \frac{1}{\omega C} \right)}$$

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L R_C + jR_L \left(\omega L - \frac{1}{\omega C} \right)}{R_L R_C + R_S R_L + R_S R_C + j \left(\omega L - \frac{1}{\omega C} \right) (R_S + R_L)}$$

converting to the desired form,

$$\Rightarrow \frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R_L R_C \left[1 + \frac{j}{R_C} \left(\omega L - \frac{1}{\omega C} \right) \right]}{R_L R_C + R_S R_L + R_S R_C \left[1 + \frac{j(R_S + R_L)}{(R_L R_C + R_S R_L + R_S R_C)} \left(\omega L - \frac{1}{\omega C} \right) \right]}$$

$$\therefore K = \frac{R_L R_C}{R_L R_C + R_S R_L + R_S R_C}$$

Substituting the values of R_L, R_S, R_C , $K = \frac{1}{42}$

$$a = \frac{1}{R_C} \left(\omega L - \frac{1}{\omega C} \right), \quad b = \frac{(R_S + R_L) \left(\omega L - \frac{1}{\omega C} \right)}{(R_L R_C + R_S R_L + R_S R_C)}$$

For very low frequencies, $\omega \rightarrow 0$, $X_L \rightarrow 0$ and $X_C \rightarrow \infty$.
Therefore, the R-L-C branch is open circuited.

$$|H(j\omega)|_{\omega \rightarrow 0} = \frac{R_L}{R_L + R_S} = \frac{4k}{4k + 4k} = 0.5$$

for very high frequencies, $\omega \rightarrow \infty$, $X_L \rightarrow \infty$, $X_C \rightarrow 0$.
Again, the R-L-C branch is open circuited

$$\therefore |H(j\omega)|_{\omega \rightarrow \infty} = \frac{R_L}{R_S + R_L} = 0.5$$

For resonance, $\text{Im}[H(j\omega)] = 0$

$$\therefore K \left[\frac{1+ja}{1+jb} \times \frac{1-jb}{1-jb} \right] = K \left[\frac{1-jb+ja+ab}{1+b^2} \right] = K \left[\frac{1+j(a-b)+ab}{1+b^2} \right]$$

$$\Rightarrow a - b = 0$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow f_r = \frac{1}{2\pi \sqrt{LC}}$$

$$f_r = \frac{1}{2\pi \sqrt{0.4 \times 10^{-3} \times 10^{-12}}} \text{ Hz}$$

$$f_r = 7.96 \text{ MHz}$$


$$|H(j\omega)|_{\omega=2\pi f_r} = k \left| \frac{1+ab}{1+b^2} \right| \quad \left[\begin{array}{l} \text{Substituting values,} \\ (a)_{f_r} = -0.08961 \\ (b)_{f_r} = -0.00189 \end{array} \right]$$

$$= \frac{1}{42} \left[\frac{1 + (-0.08961)(-0.00189)}{1 + (-0.00189)^2} \right]$$

$$= 23.809 \times 10^{-3}$$

$$\text{Rejection} = 20 \log_{10}(23.809 \times 10^{-3}) \text{ dB} = -32.465 \text{ dB}$$

Ans 3:

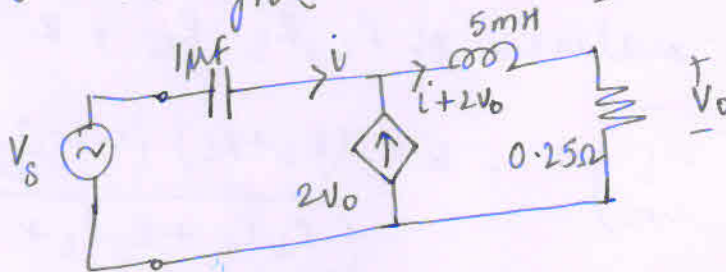


$$V_0 = (i + 2V_0) \cdot 0.25$$

$$\therefore V_0 = 0.25i + 0.5V_0$$

$$\Rightarrow 0.5V_0 = 0.25i$$

$$\text{or } \frac{V_0}{i} = \frac{0.25}{0.5} = \frac{1}{2}$$

Converting to phasor domain,

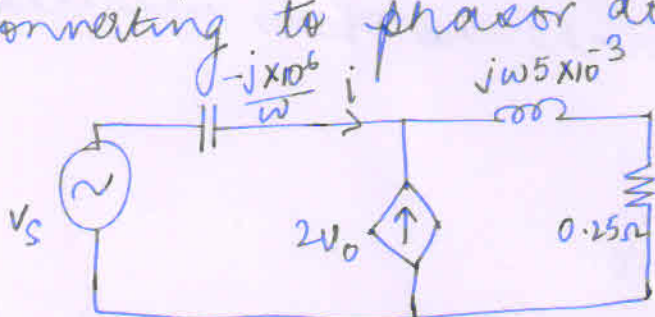

$$V_s + j \frac{10^6}{\omega} i - j\omega 5 \times 10^{-3} (i + 2V_0) - V_0 = 0$$

$$\Rightarrow V_s + j \frac{10^6}{\omega} i - j\omega 5 \times 10^{-3} i - j\omega 10^{-2} V_0 - V_0 = 0$$

$$\Rightarrow V_s = (j\omega 5 \times 10^{-3} - j \frac{10^6}{\omega}) (2V_0) + j\omega 10^{-2} V_0 + V_0$$

$$\Rightarrow \frac{V_0}{V_s} = \frac{1}{1 + j(\omega \times 2 \times 10^{-2} - \frac{2 \times 10^6}{\omega})}$$

At resonance, $X_L = X_C$

$$\therefore \omega_r = 10^4 \text{ rad/sec}$$

Ans 4. (a) $P_{av} = V_{rms} \cdot I_{rms} \cdot \cos\phi$

$$\Rightarrow 400 = 230 \times I_{rms} \times 0.8$$

$$\Rightarrow I_{rms} = 2.17 \text{ A}$$

$$\begin{aligned} \cos\phi &= \frac{V_R}{V} \Rightarrow V_R = V \cos\phi \\ &= 230 \times 0.8 \\ &= I_{rms} \times R \end{aligned}$$

$$\therefore R = \frac{230 \times 0.8}{2.17} \Omega = 84.79 \Omega$$

$$\cos\phi = 0.8 \Rightarrow \phi = \cos^{-1}(0.8) = 36.86^\circ$$

$$\therefore X_L = R \tan\phi = 84.79 \times 0.75 \Omega$$

$$\omega L = 84.79 \times 0.75$$

$$\Rightarrow L = \frac{84.79 \times 0.75}{2 \times 3.14 \times 50} \text{ H} = 0.2 \text{ H}$$

(b) Equivalent impedance, $Z_{eq} = X_C \parallel (X_L + R)$

$$Z_{eq} = \frac{-j}{\omega C} \parallel (R + j\omega L)$$

$$\Rightarrow Z_{eq} = \frac{\frac{-j}{\omega C} (R + j\omega L)}{\frac{-j}{\omega L} + R + j\omega L}$$

$$= \frac{\frac{-j}{\omega C} (R + j\omega L)}{R + j(\omega L - \frac{1}{\omega C})}$$

$$= \frac{\frac{-j}{\omega C} (R + j\omega L)}{R + j(\omega L - \frac{1}{\omega C})} \times \frac{R - j(\omega L - \frac{1}{\omega C})}{R - j(\omega L - \frac{1}{\omega C})}$$

$$\Rightarrow Z_{eq} = \frac{\left[-\frac{j}{\omega C} (R + j\omega L) \right] \left[R - j\left(\omega L - \frac{1}{\omega C}\right) \right]}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\Rightarrow Z_{eq} = \frac{\left[-\frac{jR}{\omega C} + \frac{L}{C} \right] \left[R - j\omega L + \frac{j}{\omega C} \right]}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\Rightarrow Z_{eq} = \frac{\left[-\frac{jR^2}{\omega C} - \frac{RL}{C} + \frac{R}{\omega^2 C^2} + \frac{RL}{C} - j\frac{\omega L^2}{C} + \frac{jL}{\omega C^2} \right]}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\Rightarrow Z_{eq} = \frac{\left[\frac{R}{\omega^2 C^2} + j\left(\frac{L}{\omega C^2} - \frac{\omega L^2}{C} - \frac{R^2}{\omega C}\right) \right]}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\text{Imag}[Z_{eq}] = \frac{\frac{L}{\omega C^2} - \frac{\omega L^2}{C} - \frac{R^2}{\omega C}}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = 0$$

$$\Rightarrow \frac{L}{\omega C^2} - \frac{\omega L^2}{C} - \frac{R^2}{\omega C} = 0$$

$$\Rightarrow \frac{L - \omega^2 L^2 C - R^2 C}{\omega C^2} = 0$$


$$\Rightarrow L = (\omega^2 L^2 + R^2) C$$

$$\text{or } C = \frac{L}{\omega^2 L^2 + R^2} = \frac{0.2}{(2 \times 3.14 \times 50 \times 0.2)^2 + (84.79)^2} \text{ F}$$

$$\Rightarrow C = \frac{0.2}{3943.84 + 7189.3441} \text{ F}$$

$$\Rightarrow C = 17.96 \mu\text{F}$$

Ans 5. (a)

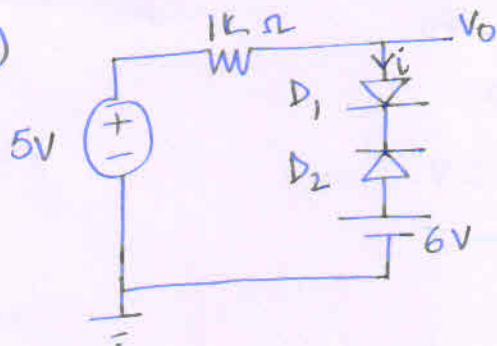

Case i) If D_1 is on and D_2 is off,


$$i = 0$$

$$\Rightarrow V_0 = 5V$$


Case ii) If D_1 is off and D_2 is on,

$$i = 0$$

$$\Rightarrow V_0 = 5V$$

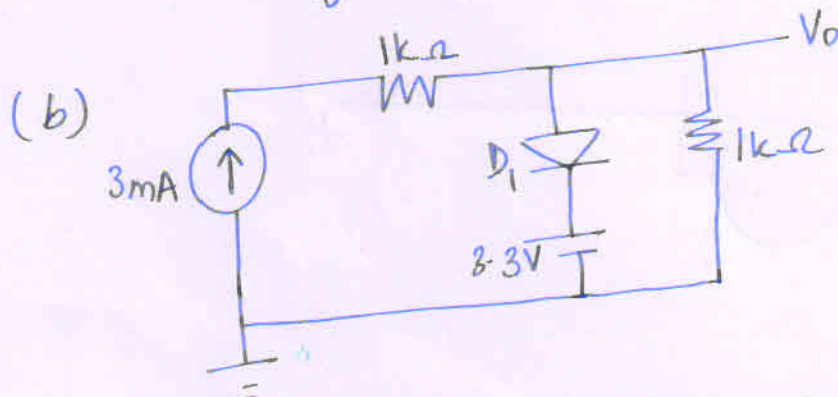

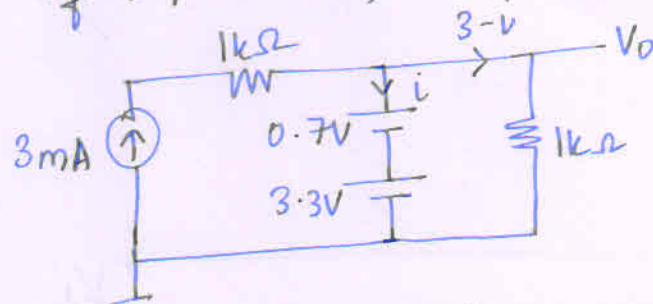Case i) If D_1 is on, the circuit becomes:






apply KVL, $4 - (3-i)1 = 0$

or $i = -1mA$ which is not possible.


$\therefore D_1$ is off.

Case ii) D_1 is off, $V_0 = 3V$.


Ans 6.

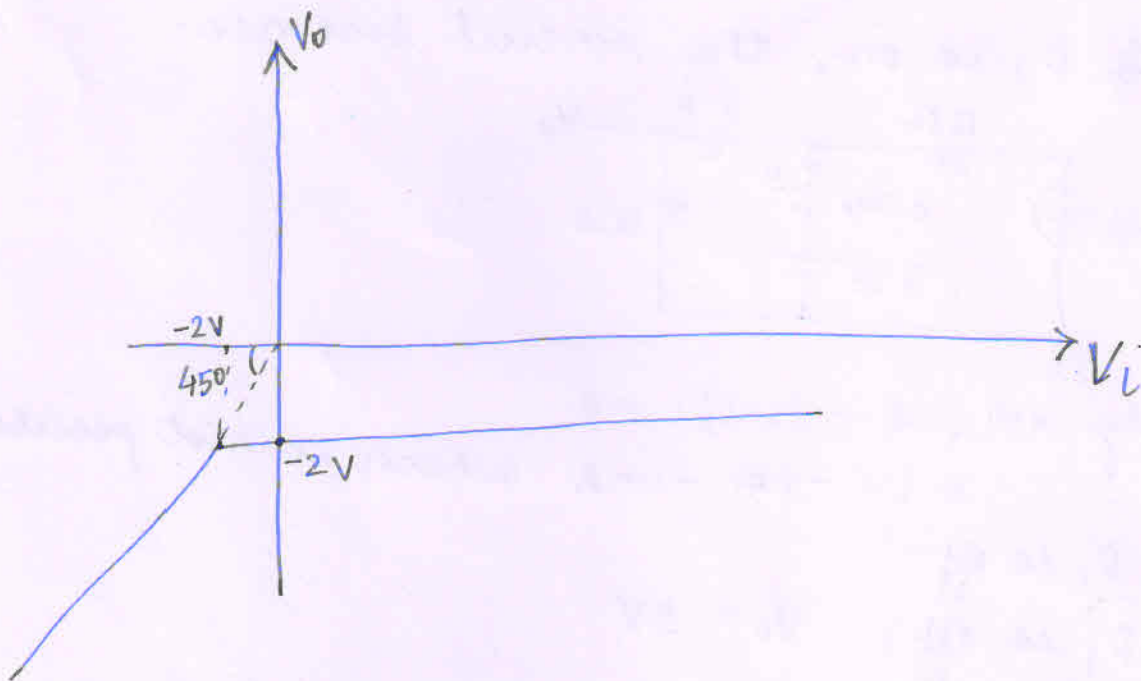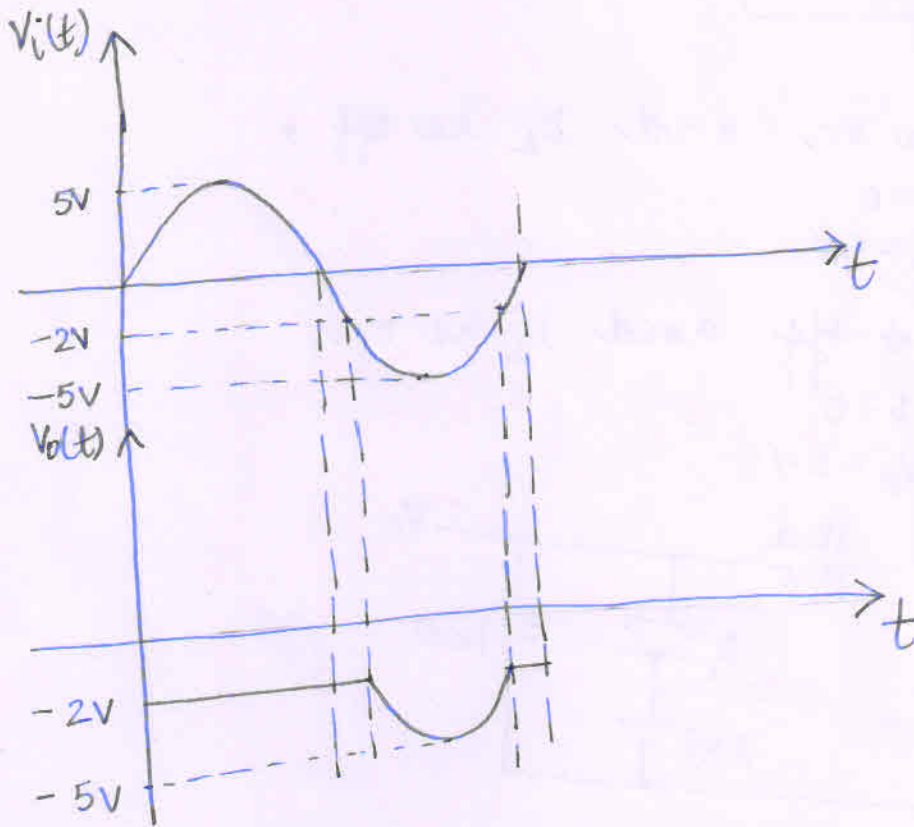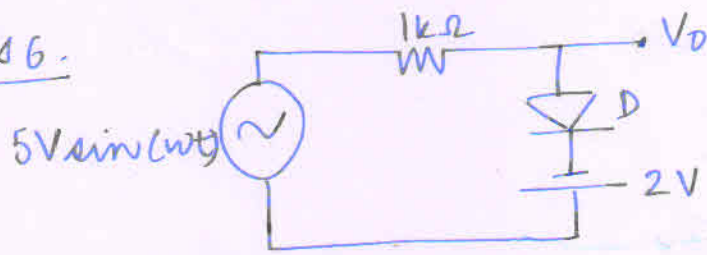

Ans 7.

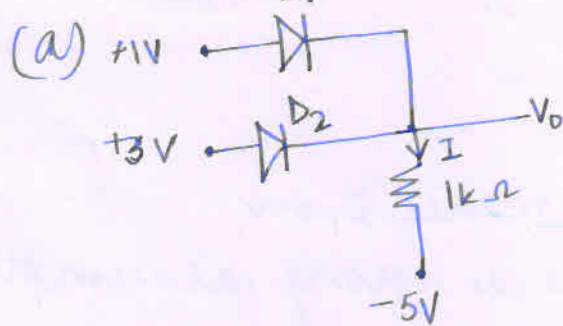


Case i) D_1 is on, D_2 is off

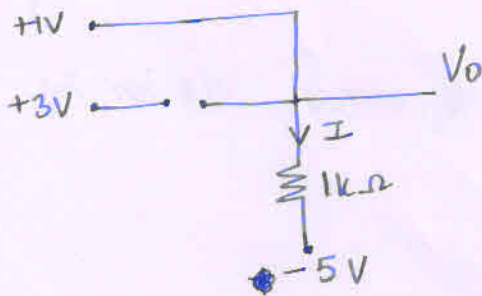

$V_0 = 1V$ which is not possible
Therefore, this is a wrong assumption.

Case ii) D_2 is on, D_1 is off.

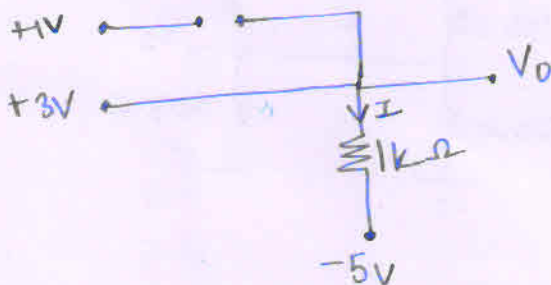


$$\therefore V_0 = 3V$$

$$I = \frac{3 - (-5)}{1k} A = 8mA$$


Case iii) Both diodes are on. This is not possible as V_0 cannot be 1V and 3V at the same time.

Case iv) Both diodes are off. $V_0 = -5V$. This is a wrong assumption as then diodes become forward biased and is contradictory.

(b)

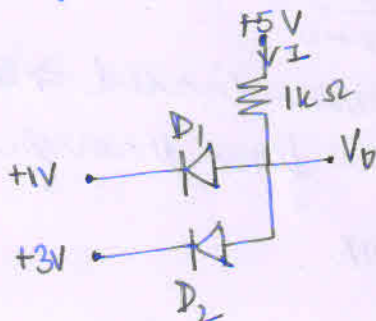

Case i) D_1 on, D_2 off

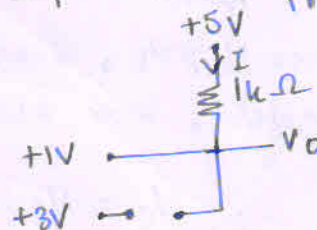


$$V_0 = 1V$$

$$I = \frac{5 - 1}{1k} A$$

$$= 4mA$$

Case ii) D_1 is off, D_2 is on

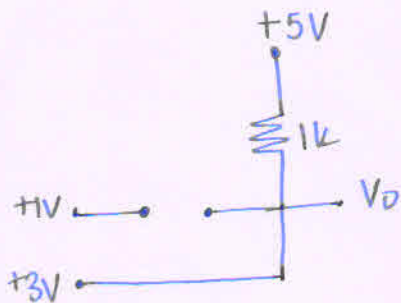


$$V_0 = 3V$$

But this makes D_1 on.



So, this is a wrong assumption.

Case iii) Both diodes are on. This is not possible.

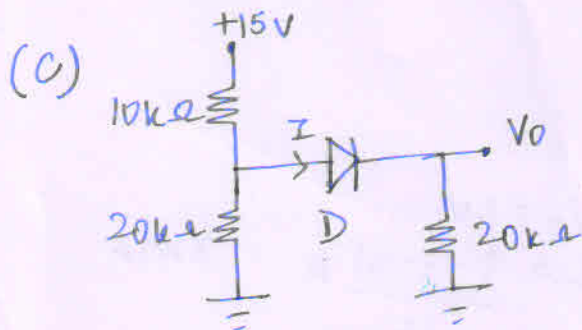Case iv) Both diodes are off. $V_0 = 5V$. This is not possible.



Case i) D is on

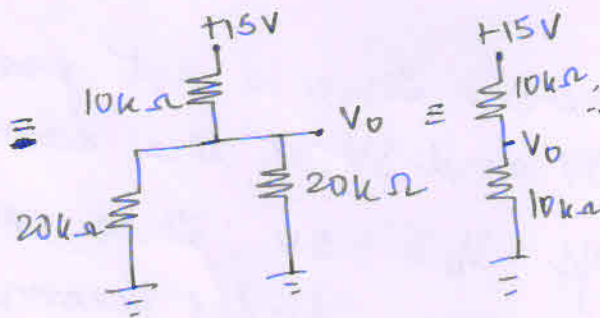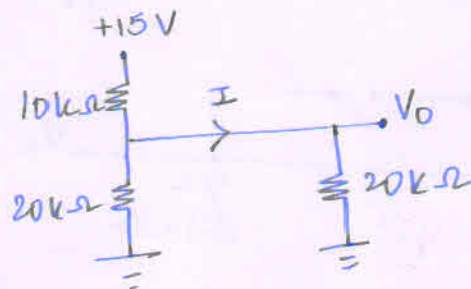


$$V_0 = \frac{15 \times 10}{20} V = 7.5 V$$

$$I = \frac{7.5}{20k} A = 0.375 mA$$

Case ii) D off is not possible.

(d) Assume that the diode is OFF.

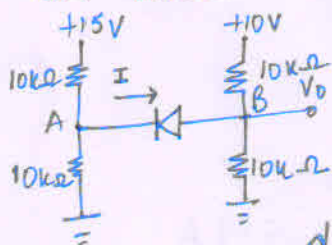

$$V_A = \frac{15 \times 10}{10 + 10} V = 7.5, \quad V_B = \frac{10 \times 10}{10 + 10} V = 5 V$$

Since $V_A > V_B$, diode is reverse biased \Rightarrow diode is off.
Therefore, no current will flow through the diode.
 $\therefore V_0 = V_B = 5V, I = 0A$.