


# **ESc201 : Introduction to Electronics**

## **Operational Amplifier**

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur
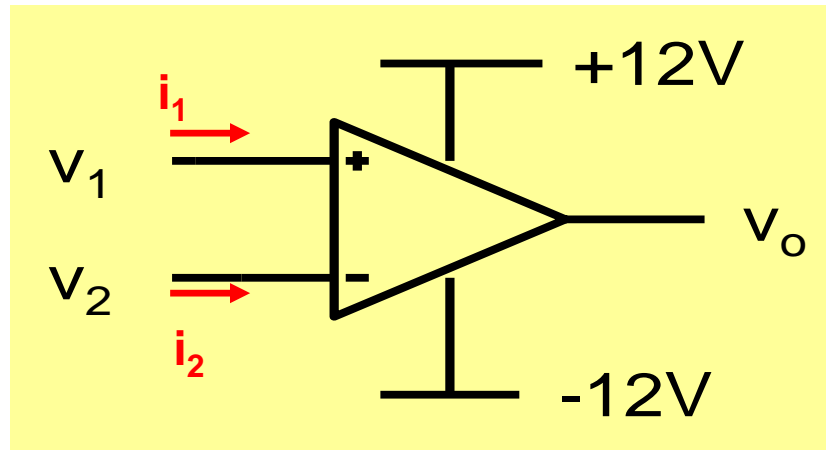
## Recap

Two important property for analyzing ideal opamp circuits under negative feedback




$$1. \quad v_1 = v_2$$

$$2. \quad i_1 = i_2 = 0$$

At the input side opamp appears to be like a short and an open circuit simultaneously !
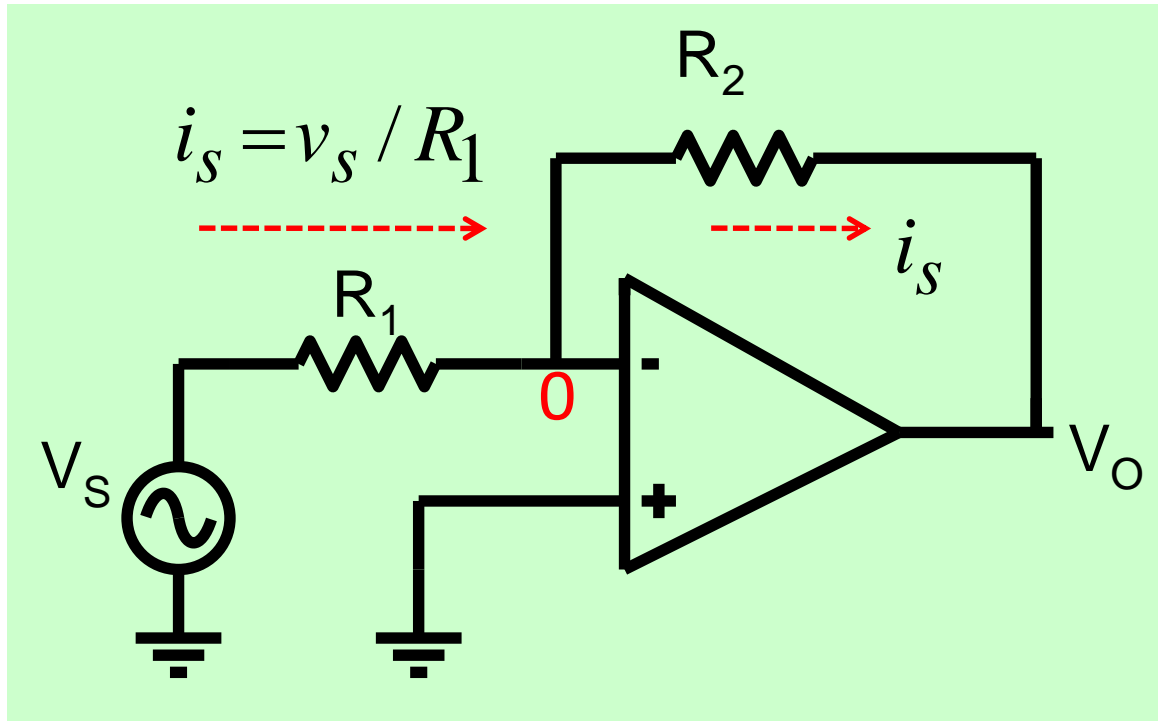
## Recap: Inverting amplifier

Re-analyze inverting amplifier with these properties




$$\frac{0 - v_o}{R_2} = i_s = \frac{v_s}{R_1}$$

$$\frac{v_o}{v_s} = -\frac{R_2}{R_1}$$

## Recap: Non-Inverting Amplifier

$$1. \quad v_1 = v_2$$


$$2. \quad i_1 = i_2 = 0$$

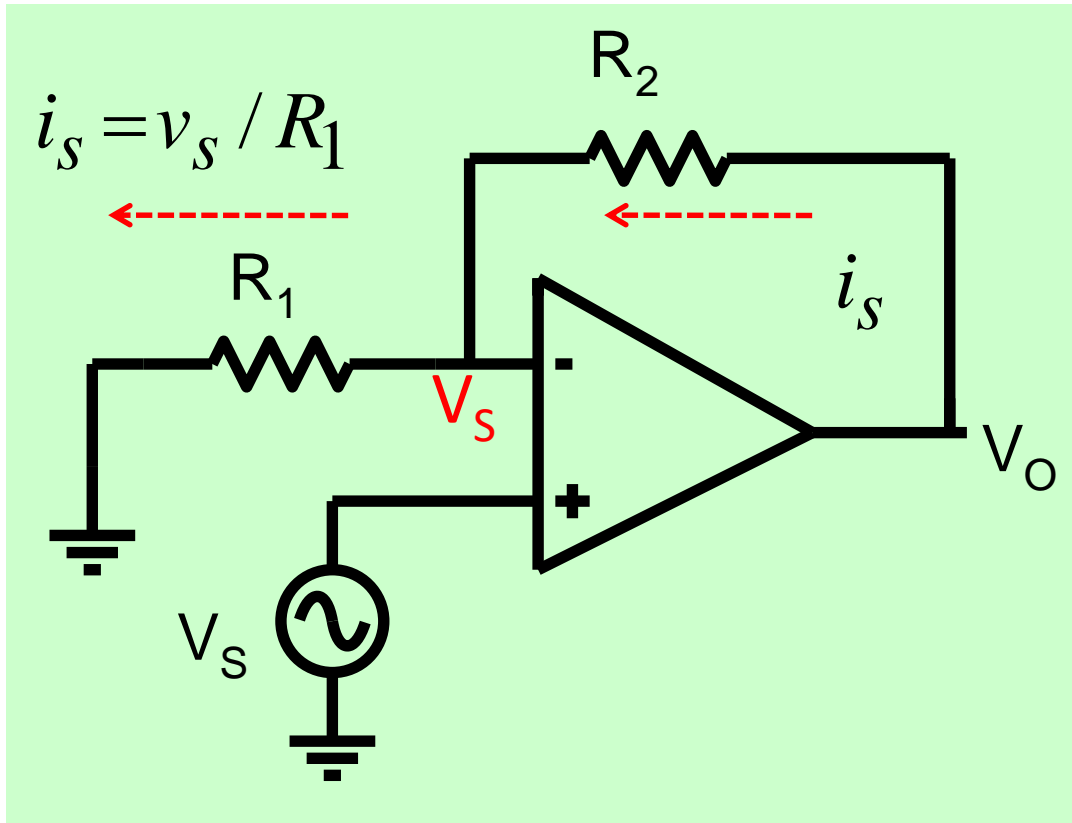


$$\frac{v_O - v_S}{R_2} = i_s = \frac{v_S}{R_1}$$

$$\frac{v_O}{v_S} = 1 + \frac{R_2}{R_1}$$


# Examples

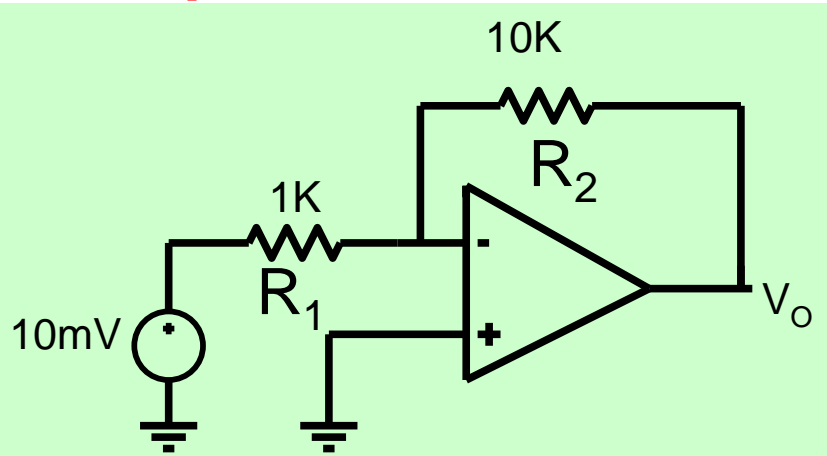
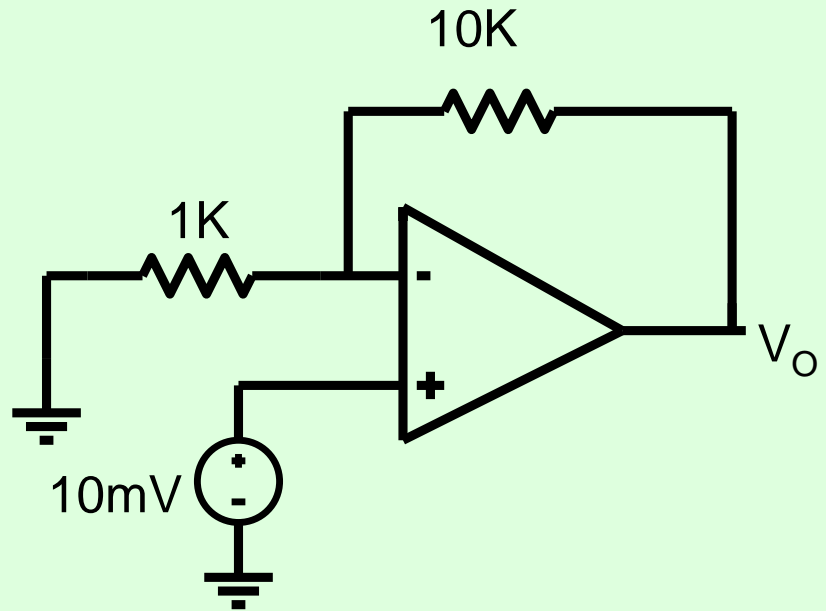
$$\frac{v_o}{v_S} = -\frac{R_2}{R_1} \Rightarrow v_o = -100mV$$



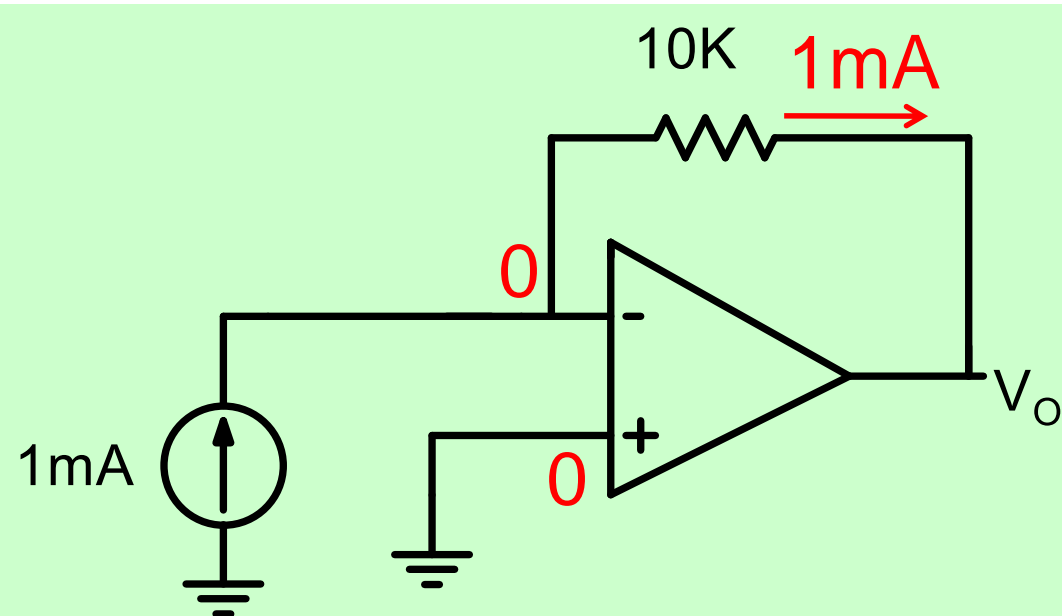
$$\frac{v_o}{v_S} = 1 + \frac{R_2}{R_1} \Rightarrow v_o = 110mV$$



$$\frac{0 - v_o}{10K} = 1mA$$

$$v_o = -10V$$

# Adder



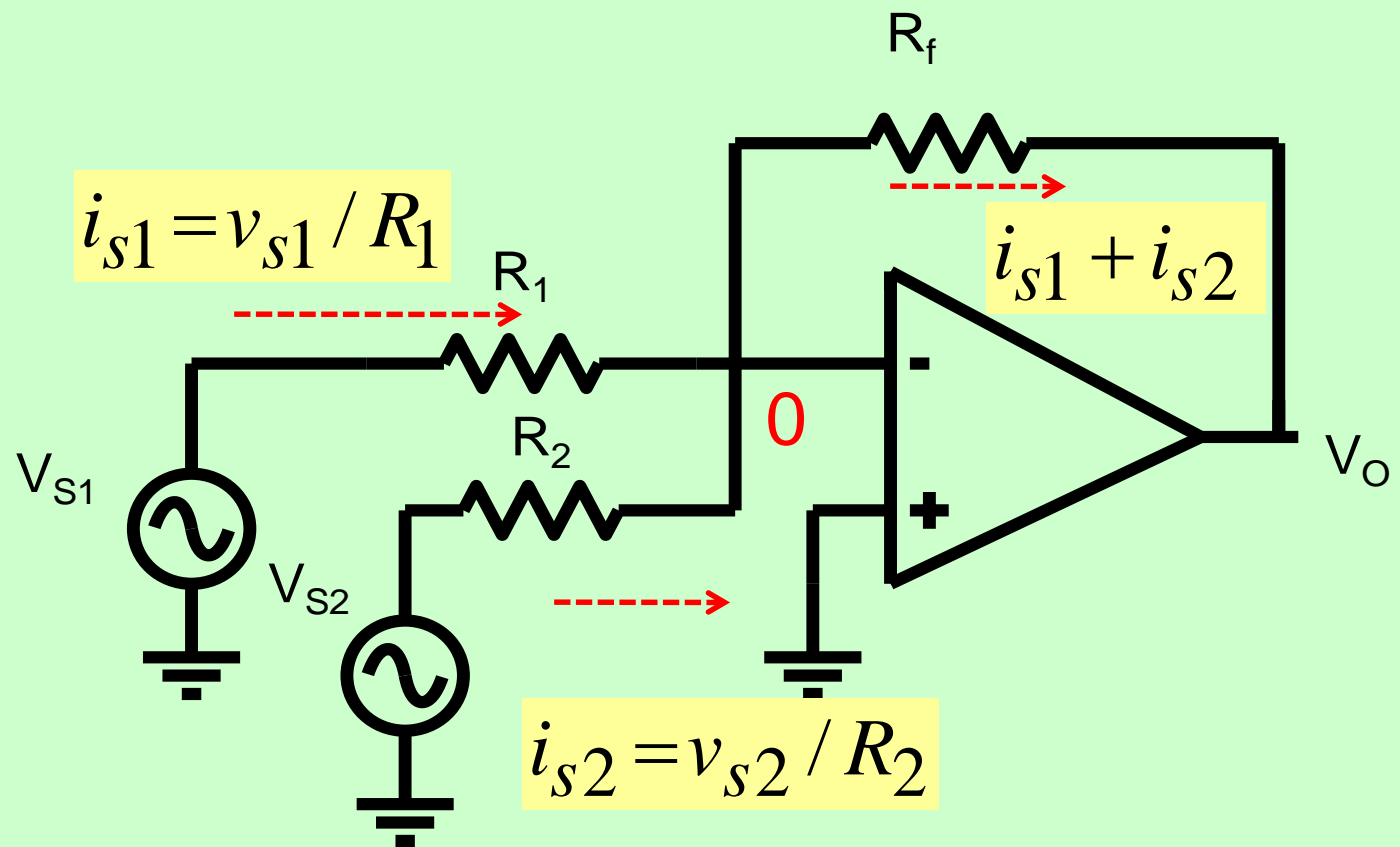


$$\frac{0 - v_o}{R_f} = i_{s1} + i_{s2} = \frac{v_{s1}}{R_1} + \frac{v_{s2}}{R_2}$$

$$v_o = -\left(\frac{R_f}{R_1} v_{s1} + \frac{R_f}{R_2} v_{s2}\right)$$

$$\text{For } R_1 = R_2 = R \quad v_o = -\frac{R_f}{R} (v_{s1} + v_{s2})$$


## Alternative Analysis

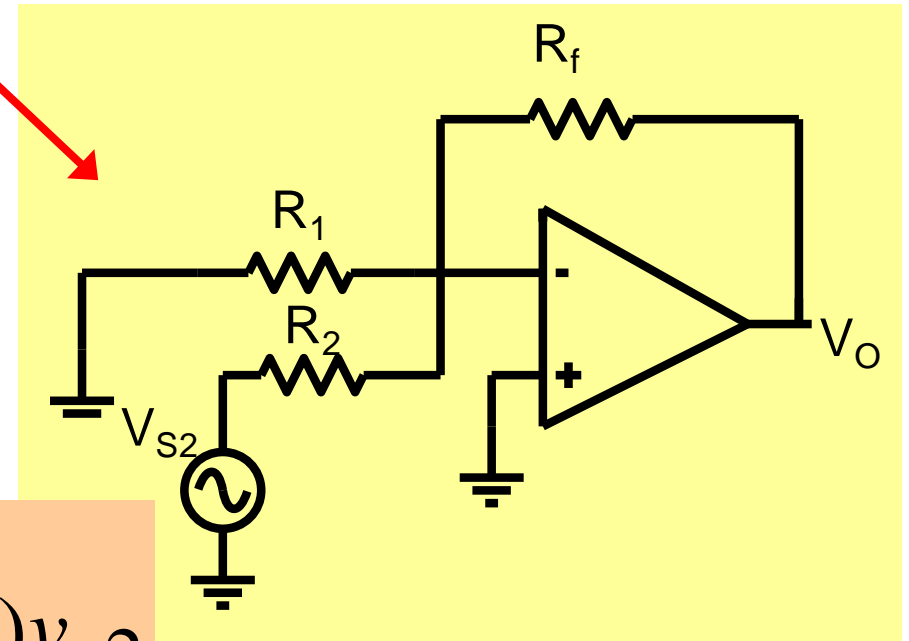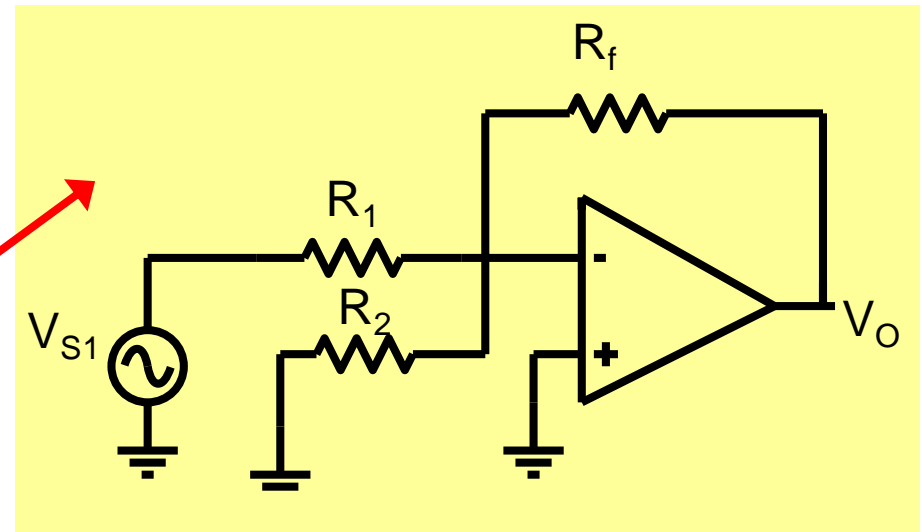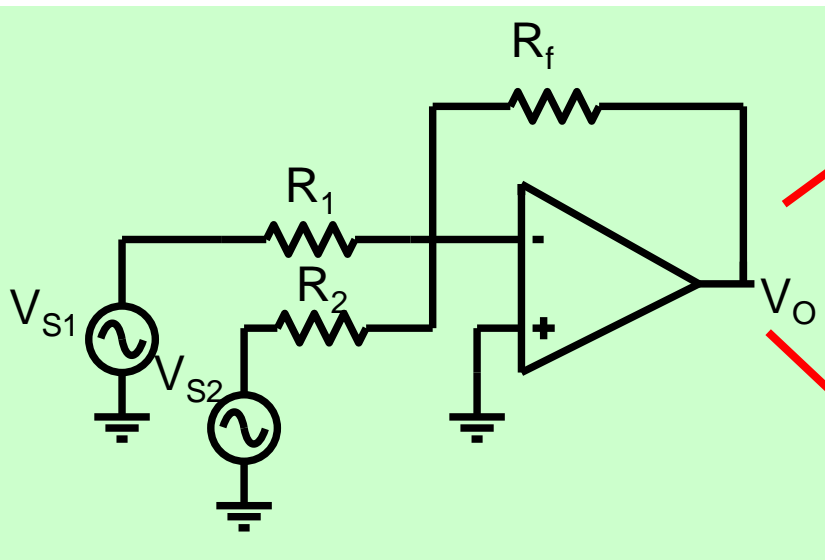

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2}$$

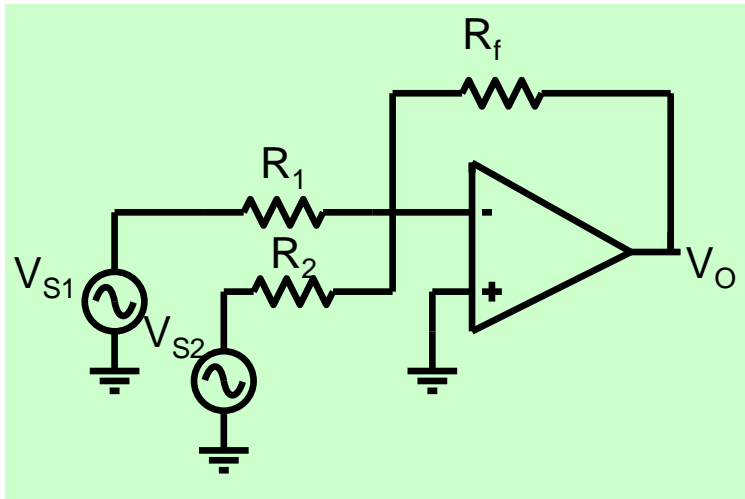
# Design Example

Design a circuit that would generate the following output given three input voltages  $v_{s1}$ ,  $v_{s2}$  and  $v_{s3}$ .



$$v_o = -10v_{s1} - 4v_{s2} - 5v_{s3}$$
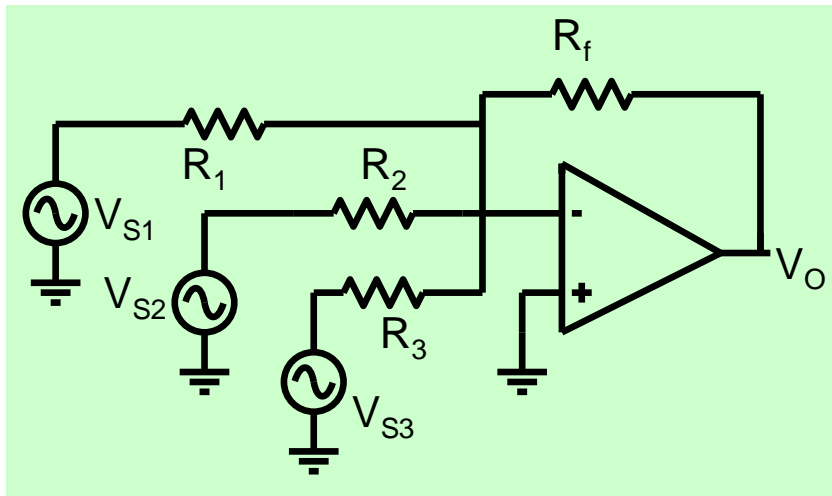
$$v_o = -\frac{R_f}{R_1}v_{s1} - \frac{R_f}{R_2}v_{s2}$$



$$v_o = -\frac{R_f}{R_1}v_{s1} - \frac{R_f}{R_2}v_{s2} - \frac{R_f}{R_3}v_{s3}$$

**Choose :**

$$R_f = 10K$$



$$\Rightarrow R_1 = 1K$$

$$\Rightarrow R_2 = 2.5K$$

$$\Rightarrow R_3 = 2K$$




# Adder

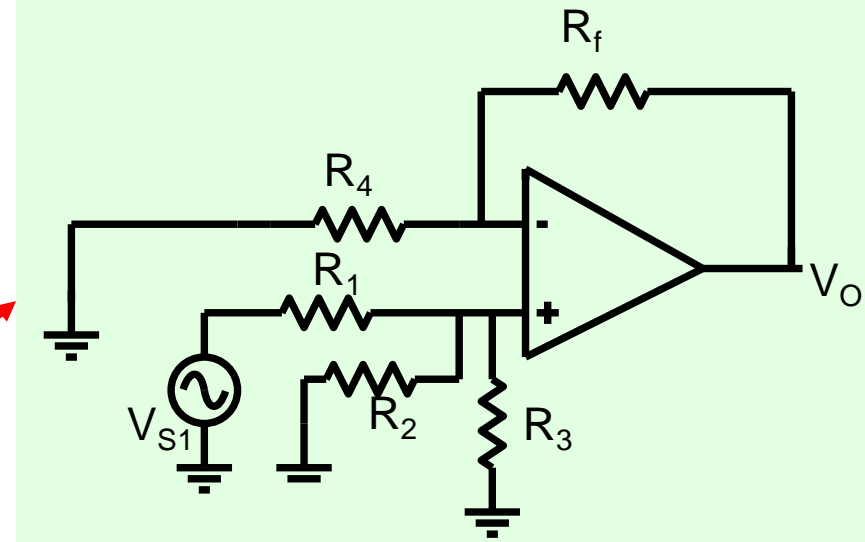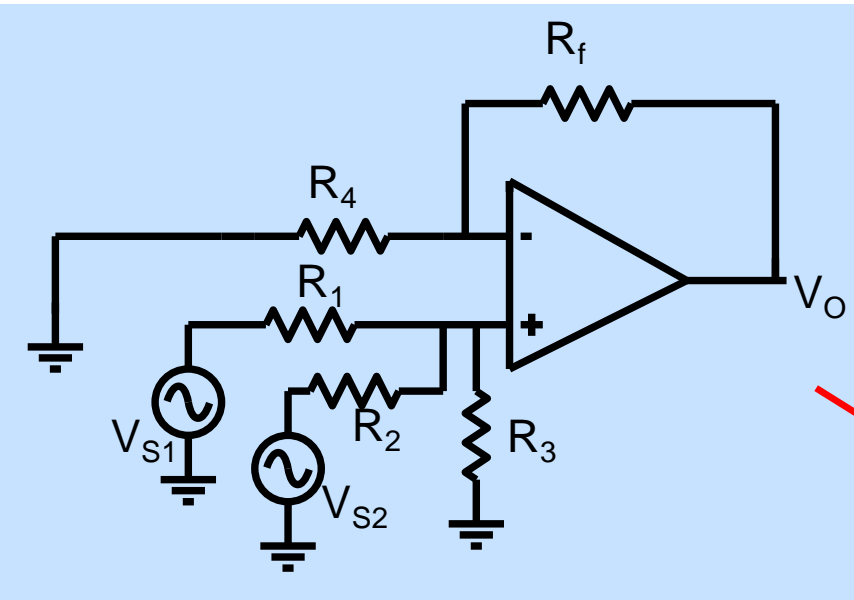


$$v_o = v_{s1} \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1} \times \left(1 + \frac{R_f}{R_4}\right)$$
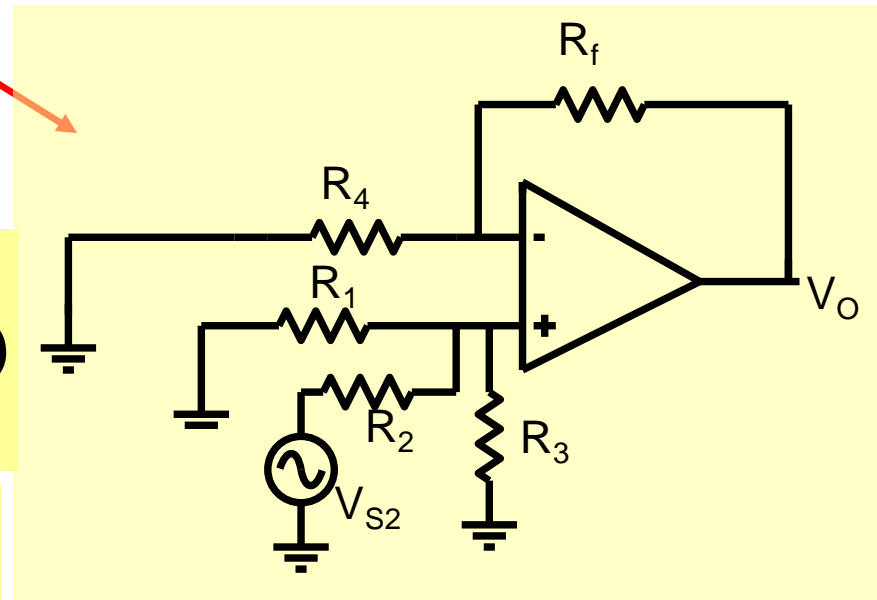
$$+ v_{s2} \frac{R_1 \parallel R_3}{R_1 \parallel R_3 + R_2} \times \left(1 + \frac{R_f}{R_4}\right)$$



# Adder

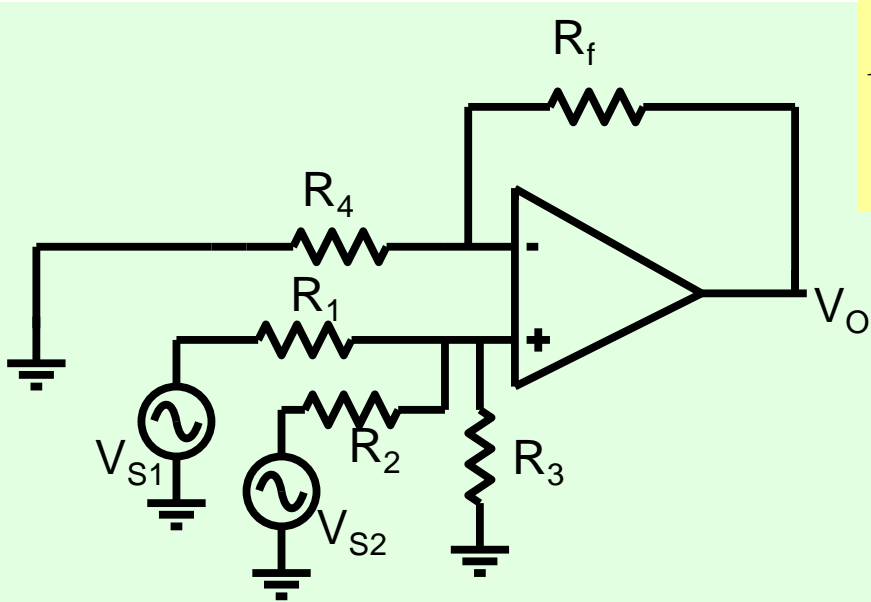

$$v_o = v_{s1} \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_1} \times \left(1 + \frac{R_f}{R_4}\right)$$

$$+ v_{s2} \frac{R_1 \parallel R_3}{R_1 \parallel R_3 + R_2} \times \left(1 + \frac{R_f}{R_4}\right)$$

$$R_p = R_1 \parallel R_2 \parallel R_3$$

**Complicated expression !!!!!**

$$v_o = \left( \frac{R_p}{R_1} v_{s1} + \frac{R_p}{R_2} v_{s2} \right) \times \left(1 + \frac{R_f}{R_4}\right)$$

$$R_p = \frac{R_1 (R_2 \parallel R_3)}{R_2 \parallel R_3 + R_1} = R_1 \parallel R_2 \parallel R_3$$


**Simple expression !**

## Design Example

Design a circuit that would generate the following output given two input voltages  $v_{s1}$  and  $v_{s2}$ .

$$v_o = 10v_{s1} + 4v_{s2}$$
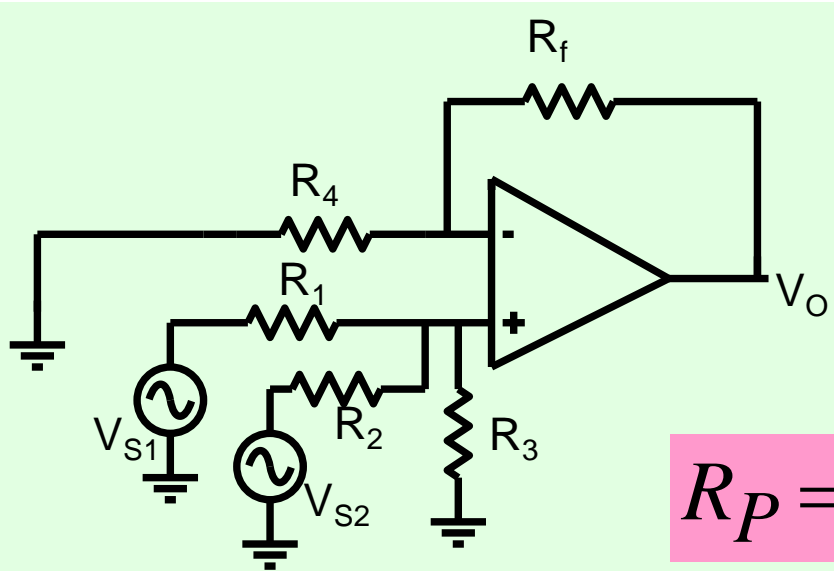
$$v_o = \left( \frac{R_p}{R_1} v_{s1} + \frac{R_p}{R_2} v_{s2} \right) \times \left( 1 + \frac{R_f}{R_4} \right)$$



$$R_p = R_1 \parallel R_2 \parallel R_3$$


DIY!

# Subtractor

$$\frac{v_{s1} - v_{s2} \frac{R_3}{R_2 + R_3}}{R_1}$$

$$v_{s2} \frac{R_3}{R_2 + R_3}$$

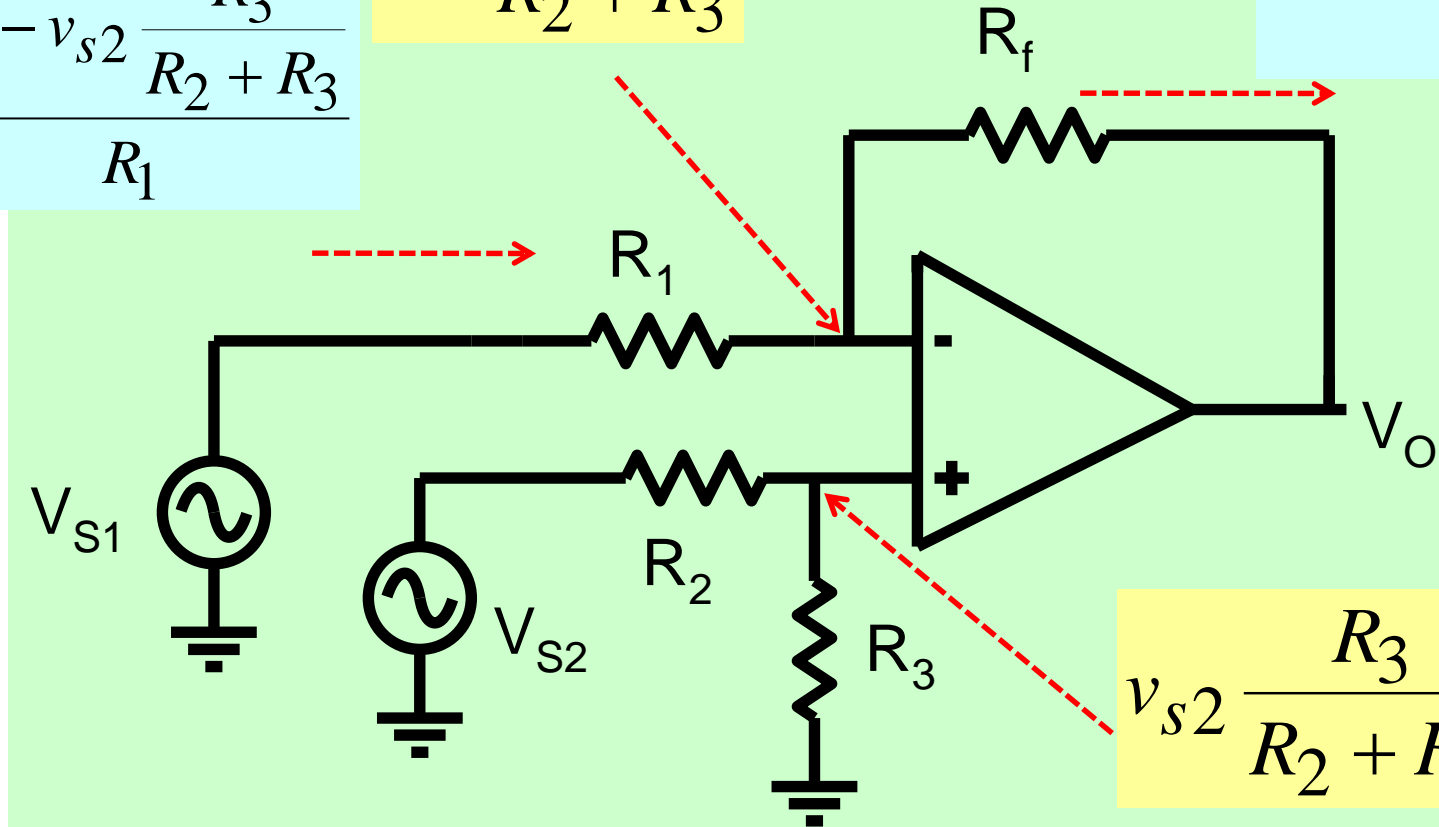
$$\frac{v_{s1} - v_{s2} \frac{R_3}{R_2 + R_3}}{R_1}$$



$$v_{s2} \frac{R_3}{R_2 + R_3}$$

$$\frac{v_{s2} \frac{R_3}{R_2 + R_3} - v_o}{R_f} = \frac{v_{s1} - v_{s2} \frac{R_3}{R_2 + R_3}}{R_1}$$
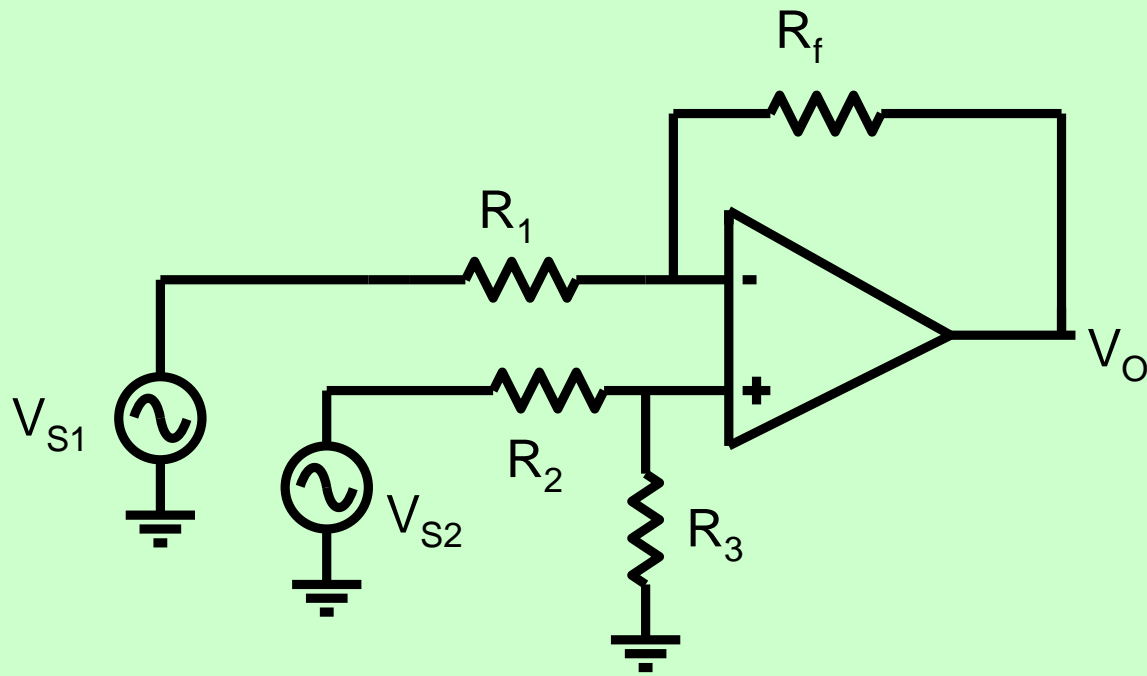
$$v_o = v_{s2} \frac{\frac{R_3}{R_2}}{(1 + \frac{R_3}{R_2})} (1 + \frac{R_f}{R_1}) - (\frac{R_f}{R_1}) v_{s1}$$






$$v_o = v_{s2} \frac{\frac{R_3}{R_2}}{(1 + \frac{R_3}{R_2})} (1 + \frac{R_f}{R_1}) - (\frac{R_f}{R_1}) v_{s1}$$

Choose  $\frac{R_3}{R_2} = \frac{R_f}{R_1}$

$$v_o = \frac{R_f}{R_1} (v_{s2} - v_{s1})$$

# Subtractor: Alternative Analysis

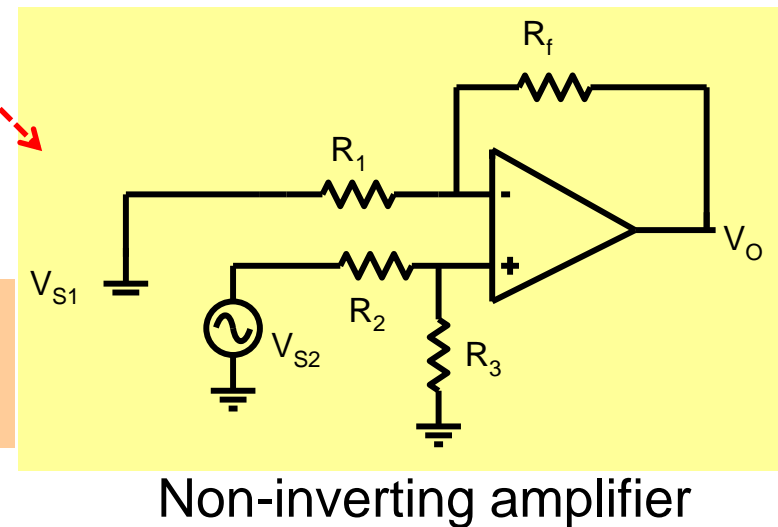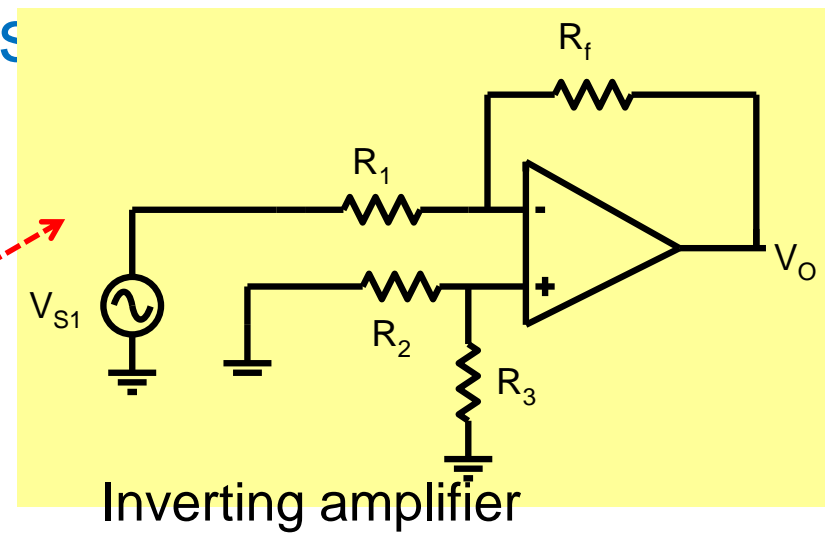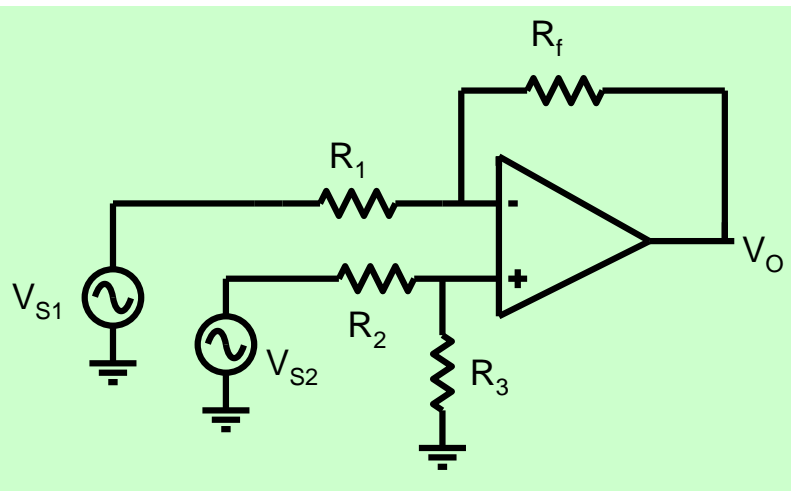


Use superposition theorem

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + v_{s2} \frac{R_3}{(R_3 + R_2)} \times \left(1 + \frac{R_f}{R_1}\right)$$


Analysis is made simpler by **Re-Using** results derived earlier

# Adder/Subtractor

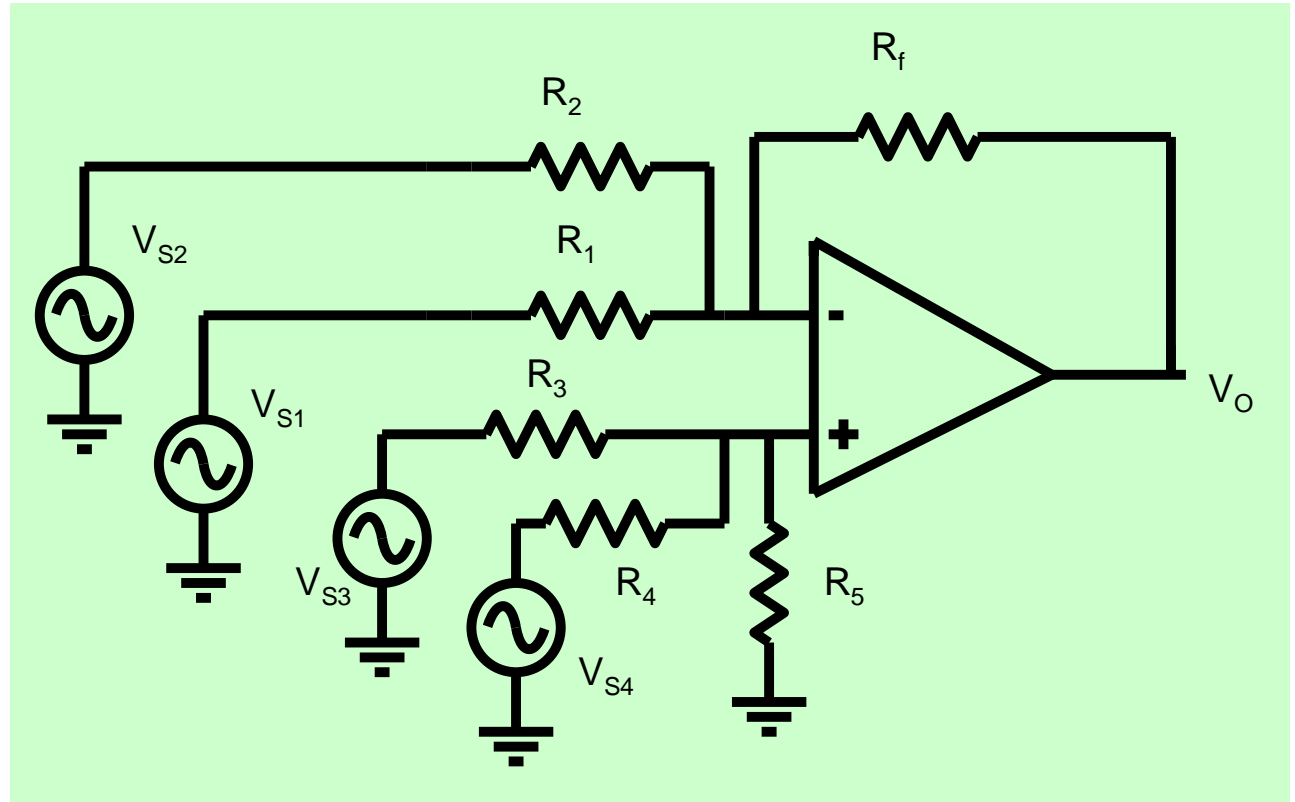

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2} + v_{s3} \frac{R_5 \parallel R_4}{R_5 \parallel R_4 + R_3} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) + v_{s4} \frac{R_5 \parallel R_3}{R_5 \parallel R_3 + R_4} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)$$

# Adder/Subtractor

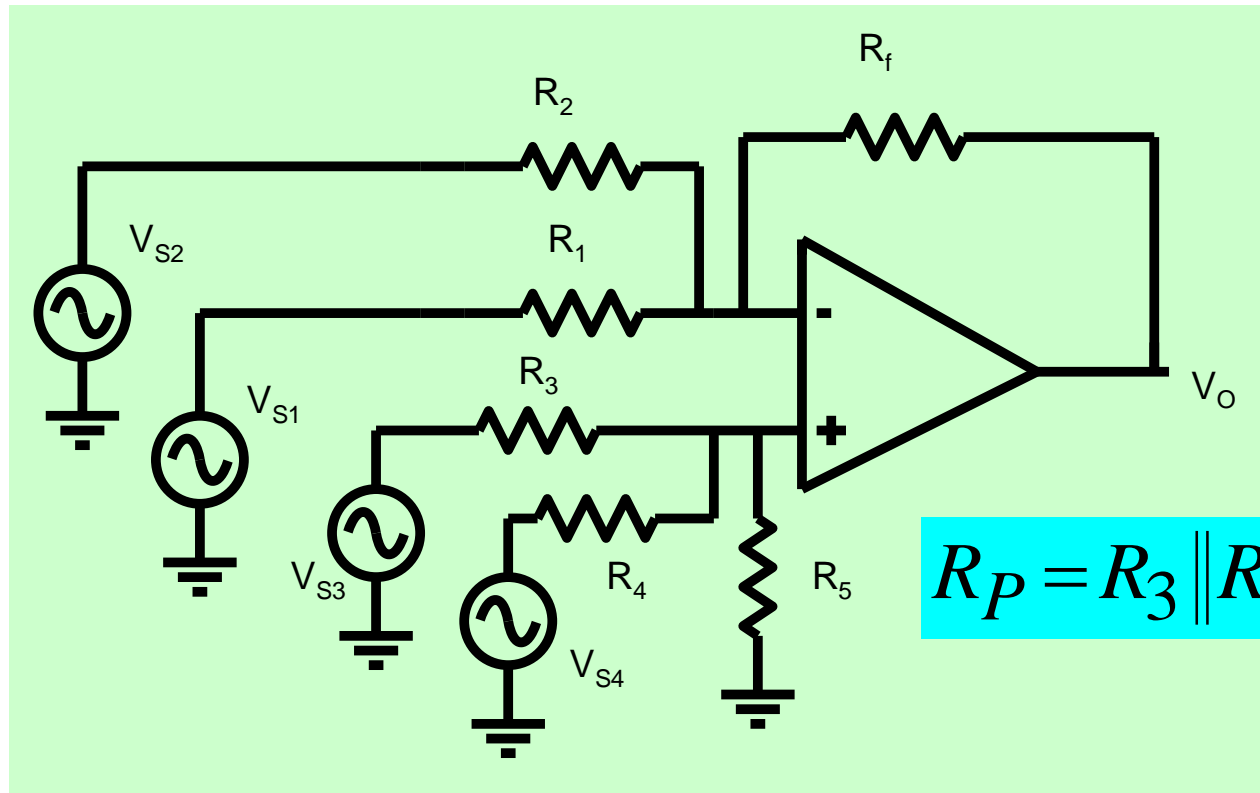


$$R_P = R_3 \parallel R_4 \parallel R_5$$

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} + -\left(\frac{R_f}{R_2}\right)v_{s2} + v_{s3} \frac{R_P}{R_3} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) + v_{s4} \frac{R_P}{R_4} \times \left(1 + \frac{R_f}{R_1 \parallel R_2}\right)$$



# Example

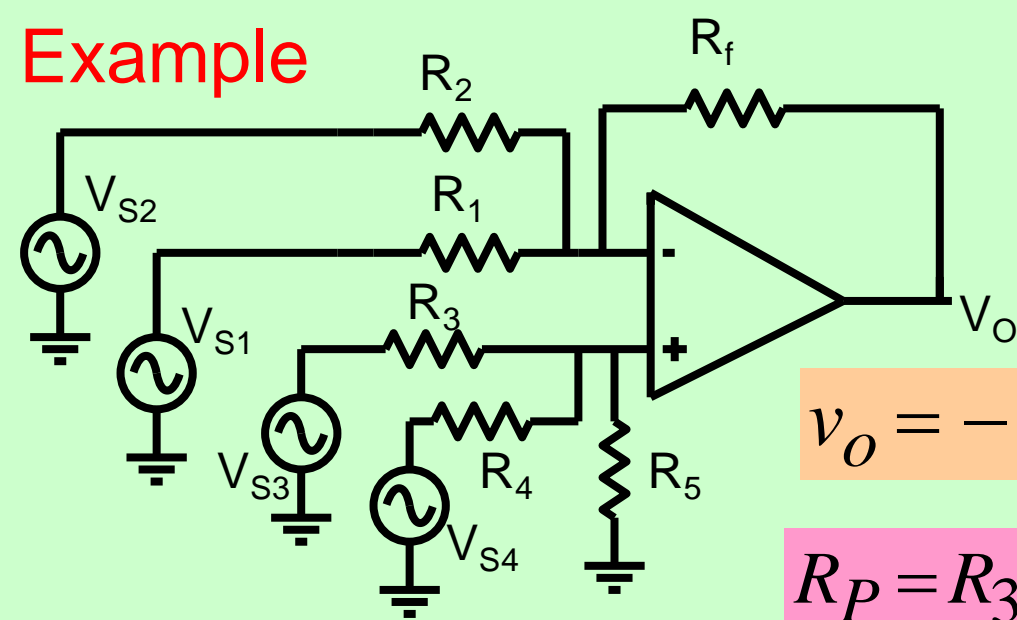

$$v_o = -10v_{s1} - 4v_{s2} + 5v_{s3} + 2v_{s4}$$

$$R_P = R_3 \parallel R_4 \parallel R_5$$

$$v_o = -\left(\frac{R_f}{R_1}\right)v_{s1} - \left(\frac{R_f}{R_2}\right)v_{s2} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_3}v_{s3} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_4}v_{s4}$$

Choose :

$$R_f = 10K$$

$$\Rightarrow R_1 = 1K$$

$$\Rightarrow R_2 = 2.5K$$

$$\Rightarrow \frac{R_P}{R_3} = 0.33$$

$$\Rightarrow \frac{R_P}{R_4} = 0.133$$

$$\Rightarrow \frac{R_4}{R_3} = 2.5$$

Choose :

$$R_3 = 1K$$



$$\Rightarrow R_4 = 2.5K$$

$$\Rightarrow R_P = 0.33K$$

$$\Rightarrow R_5 = 0.625K$$

## Discussion on loading effect

$$v_o = -(v_{s1} + v_{s2})$$

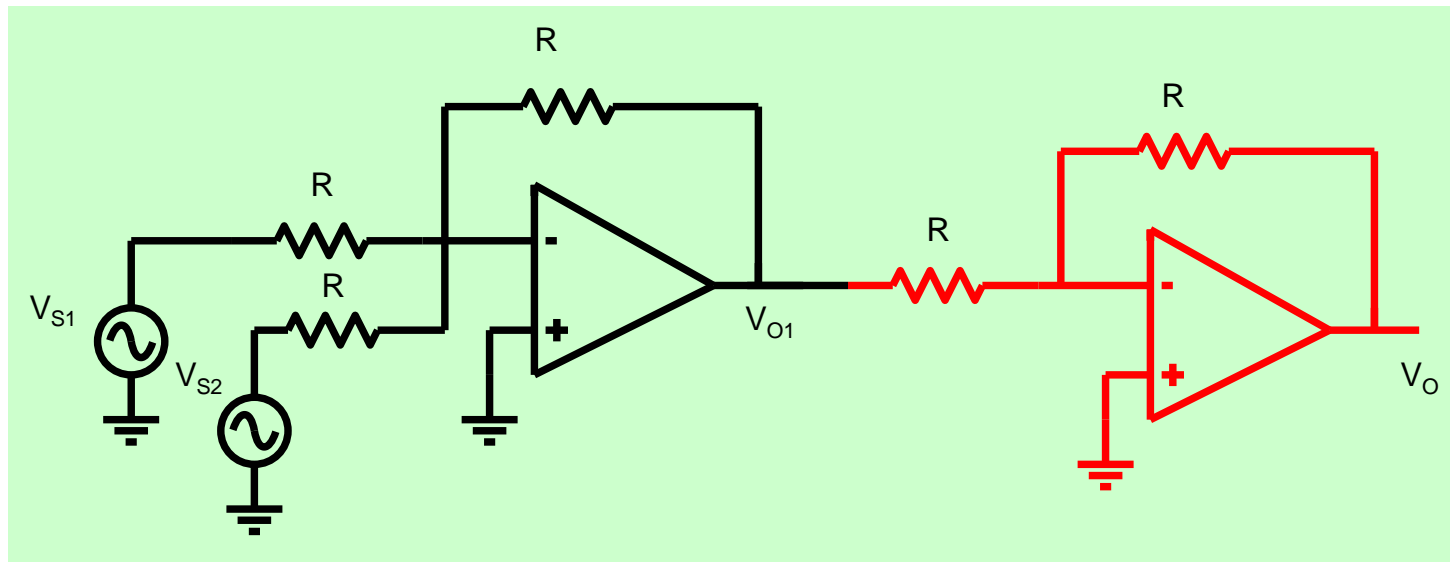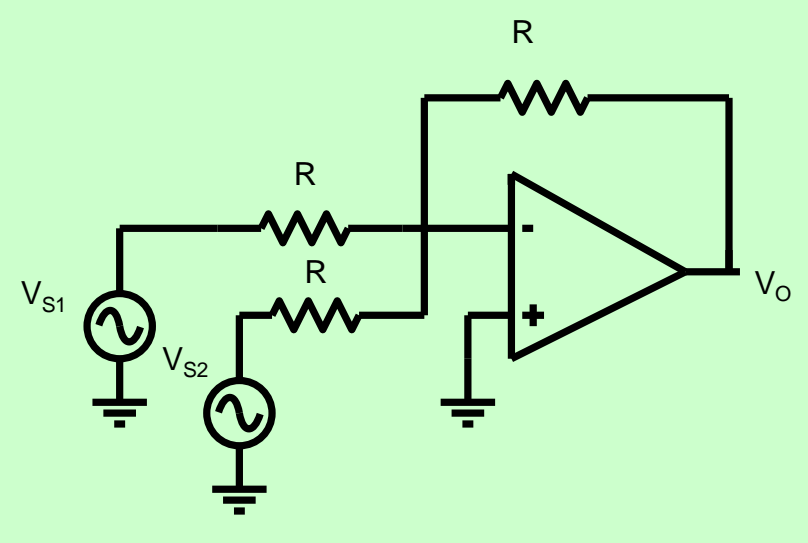


$$v_{o1} = -(v_{s1} + v_{s2})$$

$$v_o = -v_{o1}$$


$$v_o = (v_{s1} + v_{s2})$$

Have we made some assumption here ?

# Example

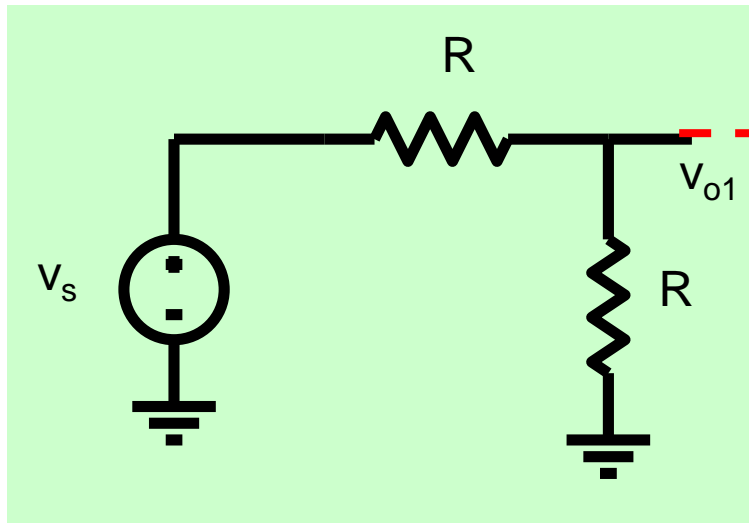

$$\frac{v_{o1}}{V_s} = 0.5$$

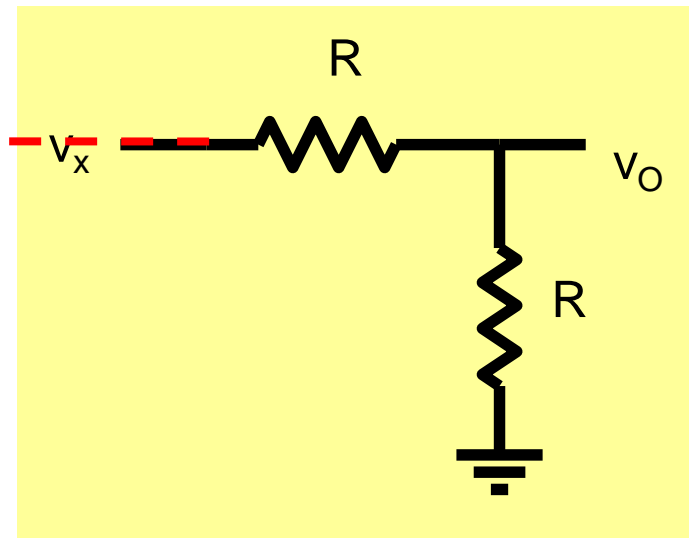


$$\frac{v_o}{v_x} = 0.5$$

$$v_{o1} = v_x$$

$$\frac{v_o}{v_x} = \frac{v_o}{v_{o1}} = 0.5$$


$$\frac{v_o}{V_s} = \frac{v_o}{v_{o1}} \times \frac{v_{o1}}{V_s} = 0.5 \times 0.5 = 0.25$$

BUT

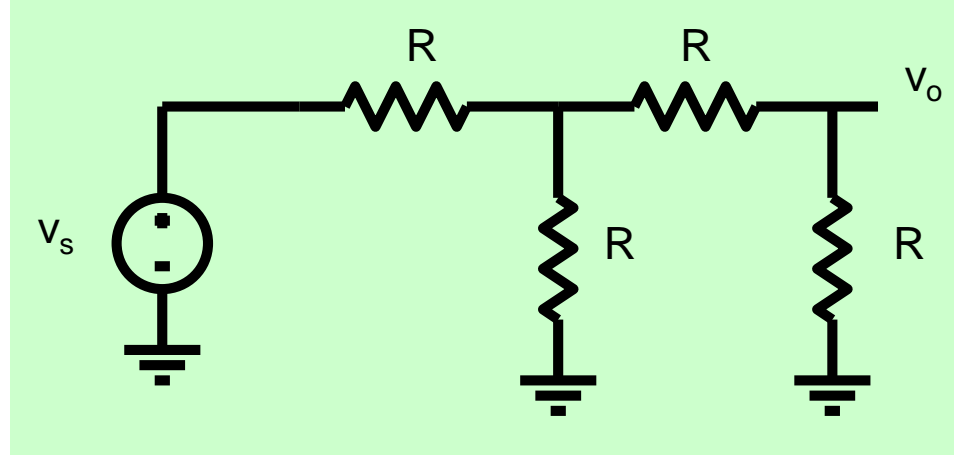

$$\frac{v_o}{v_s} = 0.2$$

Where is the error ?

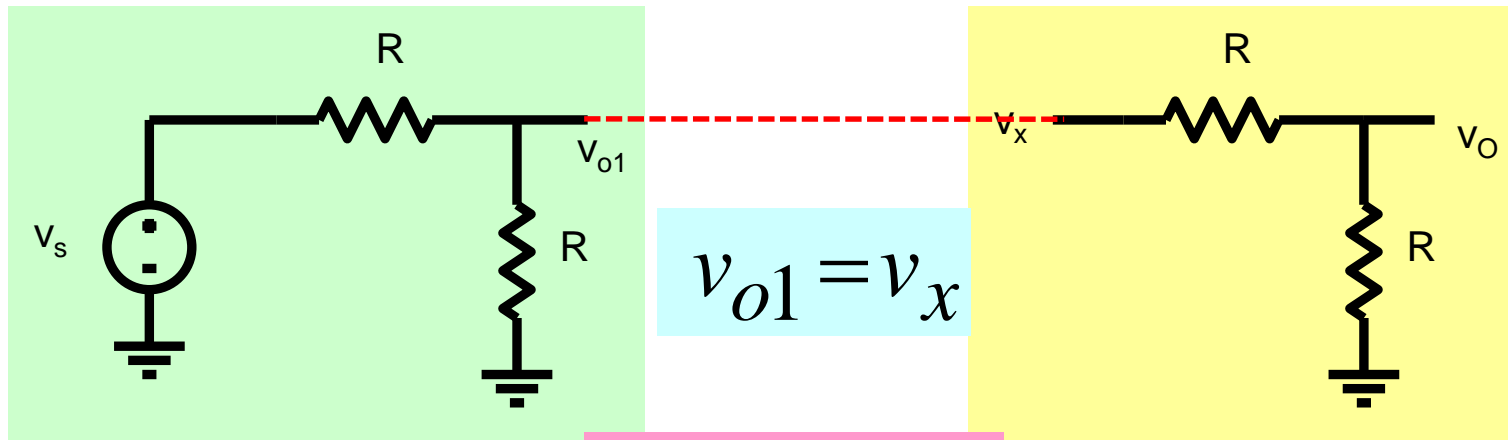

$$v_{o1} = v_x$$



$$\frac{v_{o1}}{v_s} = 0.5$$

$$\frac{v_{o1}}{v_s} \neq 0.5$$

$$\frac{v_o}{v_x} = 0.5$$

Circuit-1 gets 'loaded' by circuit-2 and its output vs. input characteristics get modified.


# Loading Effect

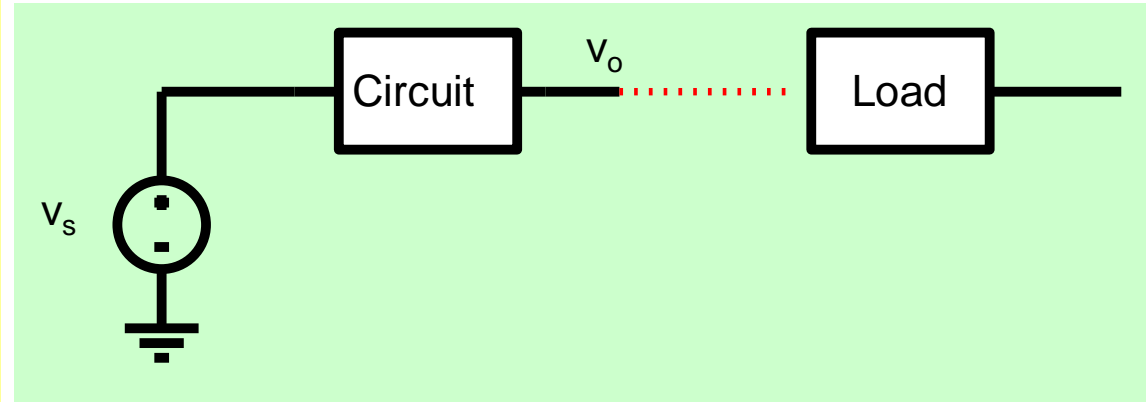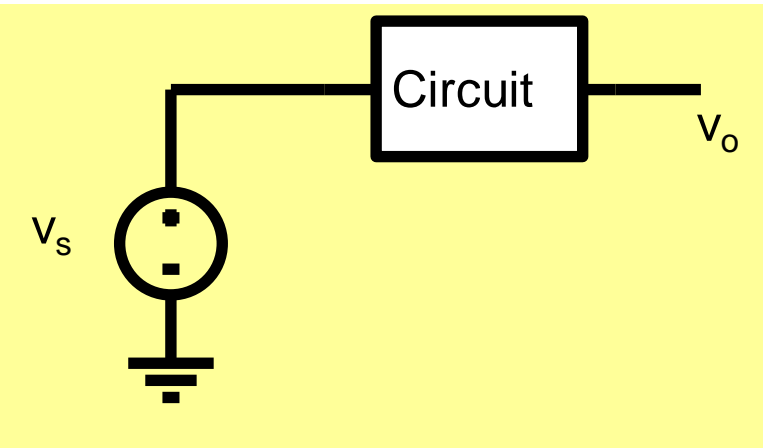


$V_o$  in general gets altered when we connect a load to it

Under what conditions is change in  $V_o$  small upon connection of a load ?

# Example

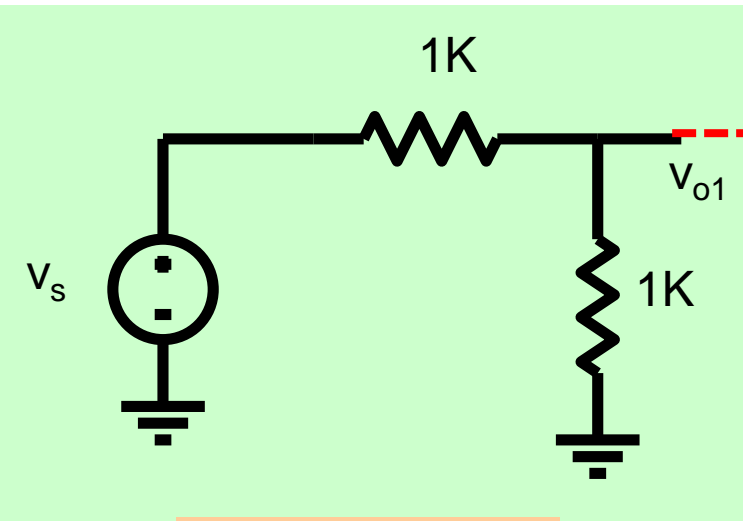


$$\frac{v_{o1}}{v_s} = 0.5$$

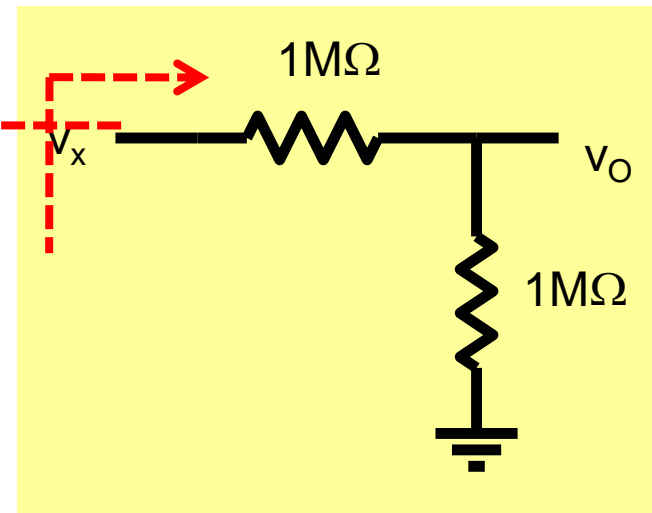

After connection of load:

$$\frac{v_{o1}}{v_s} \cong 0.5$$

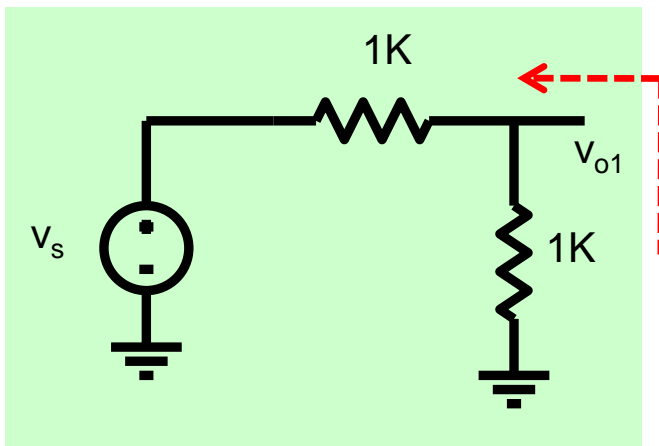We can describe this effect in terms of output resistance




$$R_o = 0.5K \quad R_L = 2M\Omega$$


# Loading Effect

Whenever output resistance of a circuit is much smaller than the load resistance, the loading effect is minimal.

$$R_o \ll R_L$$

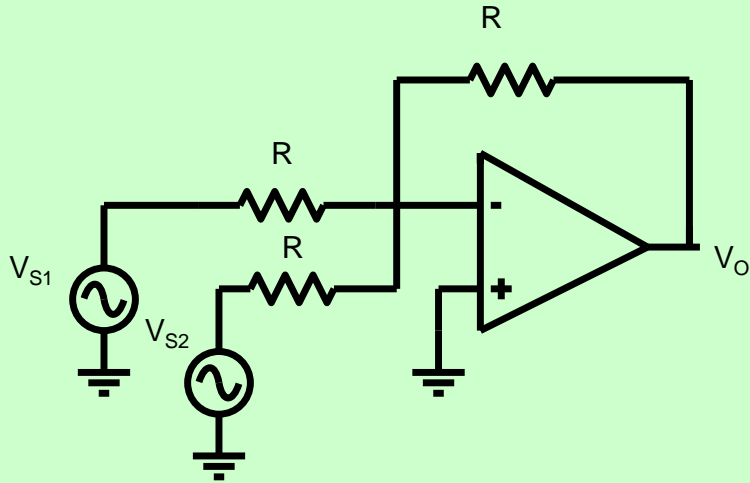

$$v_o = -(v_{s1} + v_{s2})$$

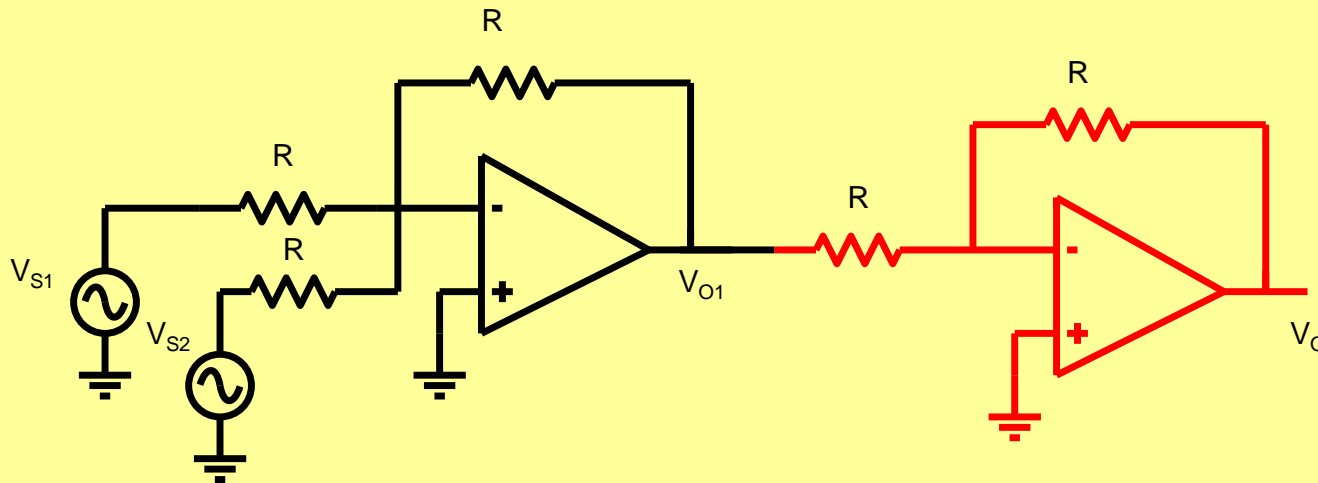

$$v_{o1} = -(v_{s1} + v_{s2})$$


$$v_o = -v_{o1}$$

$$v_o = (v_{s1} + v_{s2})$$

The assumption made here is that there is no loading which is reasonable because opamps have very low o/p resistance




# Example

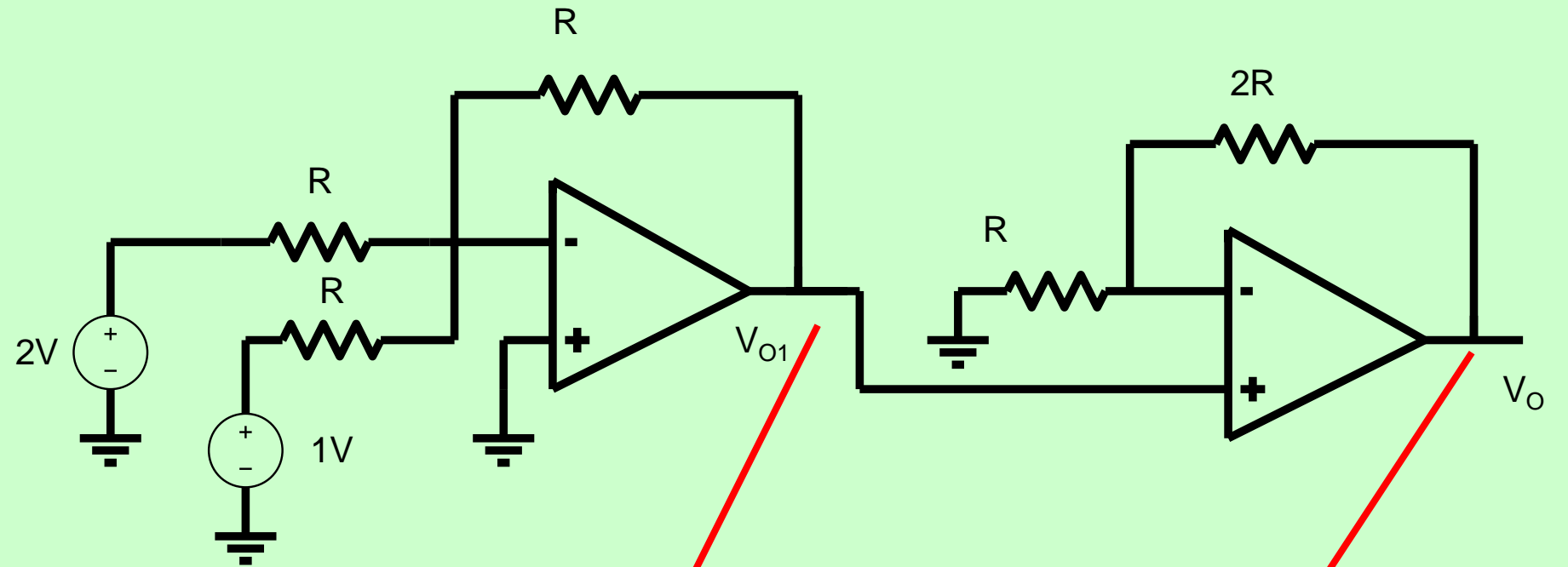

$$v_{o1} = -\left\{\frac{R}{R} \times 1 + \frac{R}{R} \times 2\right\} = -3V$$


$$\frac{v_o}{v_{o1}} = 1 + \frac{2R}{R} \Rightarrow v_o = -9V$$

# Integrator

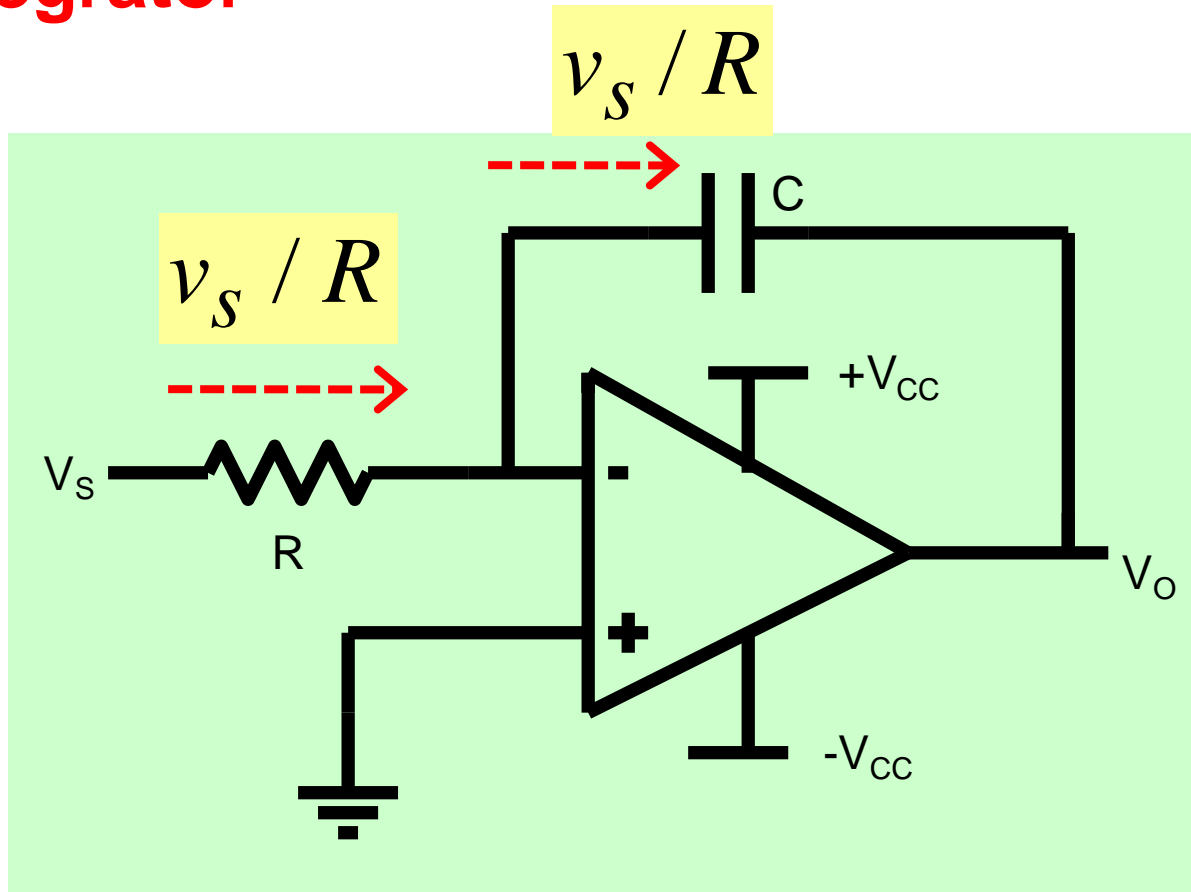


$$\frac{v_s}{R} = -C \frac{dV_o}{dt} \Rightarrow V_o(t) = -\frac{1}{RC} \int v_s dt$$

# Differentiator

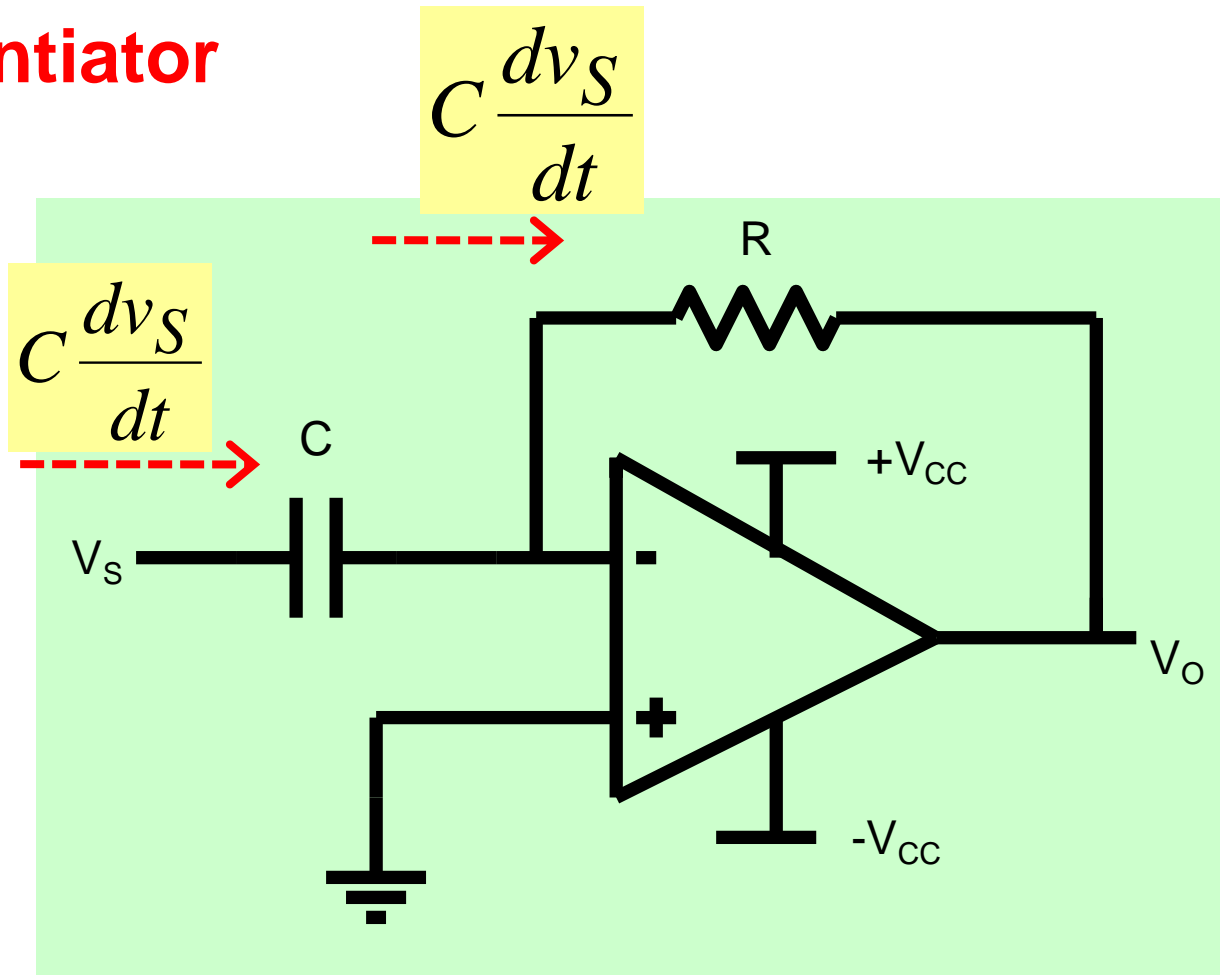

$$-\frac{V_o}{R} = C \frac{dv_s}{dt} \Rightarrow V_o(t) = -RC \frac{dv_s}{dt}$$

# Log Amplifier

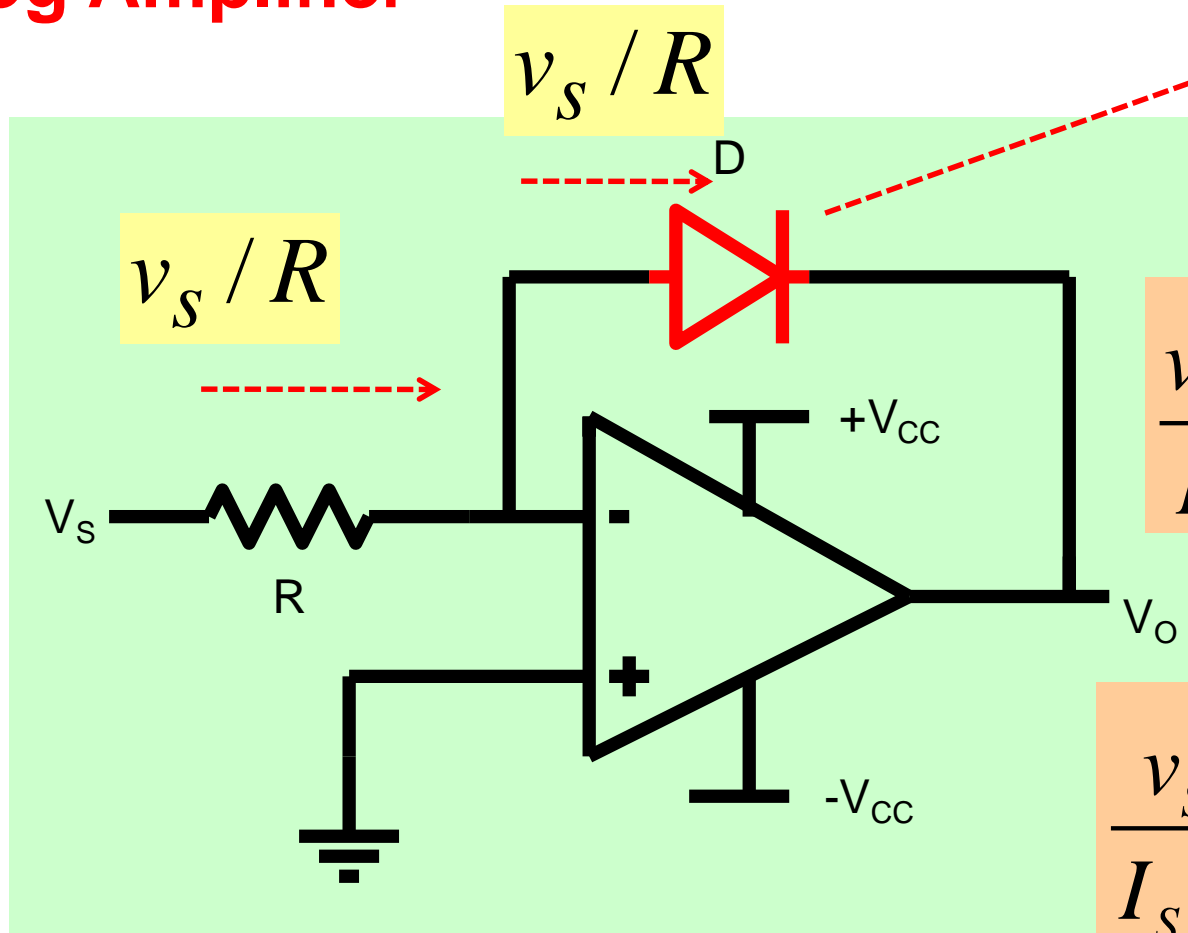


$$I = I_S (e^{\frac{V}{V_T}} - 1)$$

$$\frac{v_s}{R} = I_S (e^{-\frac{V_o}{V_T}} - 1)$$

$$\frac{v_s}{I_S R} + 1 = e^{-\frac{V_o}{V_T}}$$


$$\Rightarrow -V_o = V_T \times \ln\left(1 + \frac{v_s}{RI_S}\right) \cong V_T \times \ln\left(\frac{v_s}{RI_S}\right)$$

# Temperature Sensor ?

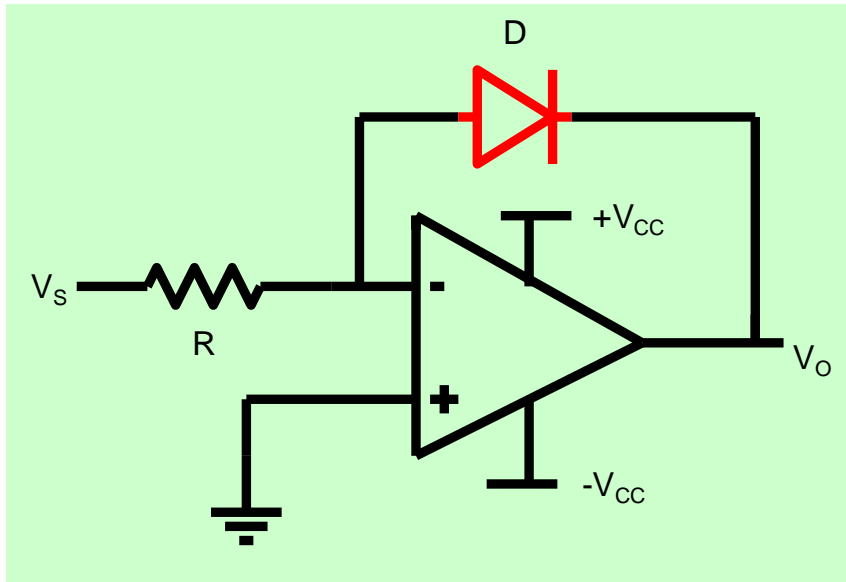


$$V_o = -V_T \times \ln\left(\frac{V_s}{RI_s}\right); V_T = \frac{k_B T}{q}$$

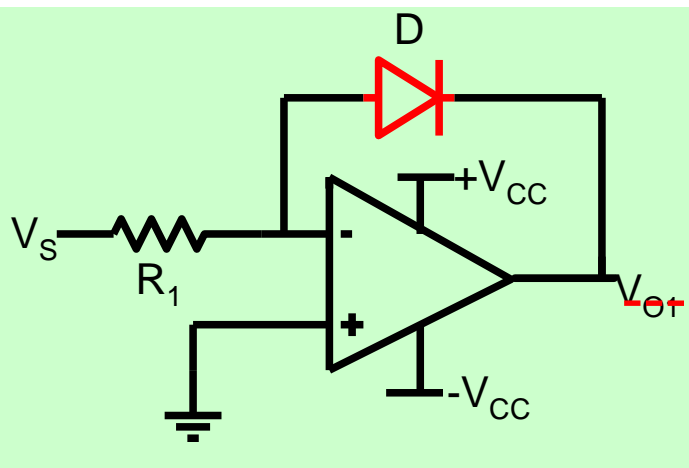
But  $I_s$  is a function of temperature as well.


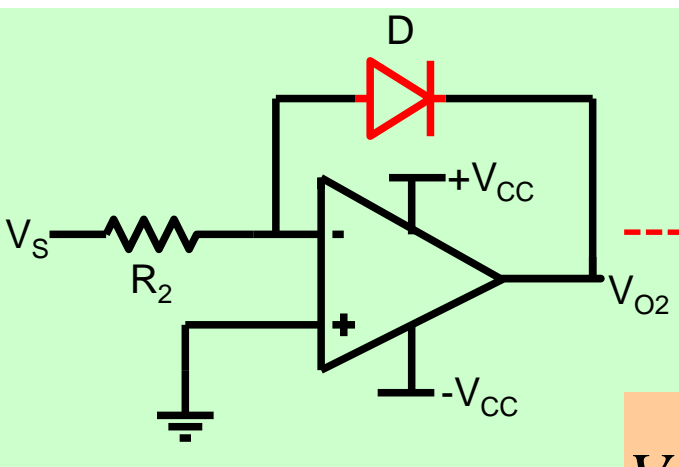
$$V_{O1} = -V_T \times \ln\left(\frac{V_S}{R_1 I_S}\right)$$



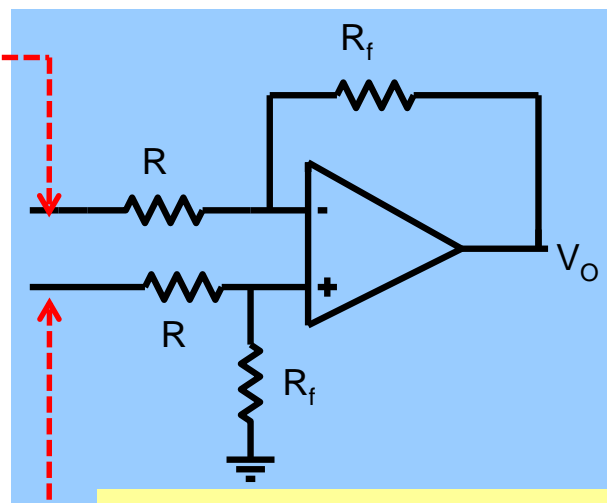
$$V_{O2} = -V_T \times \ln\left(\frac{V_S}{R_2 I_S}\right)$$




$$V_O = -\frac{R_f}{R} V_{O1} + \left(1 + \frac{R_f}{R}\right) \times \frac{R_f}{R_f + R} V_{O2}$$

$$V_O = \frac{R_f}{R} (V_{O2} - V_{O1})$$

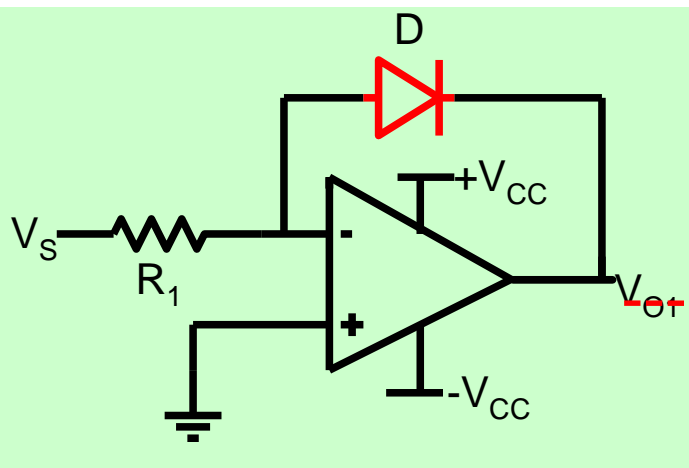
$$V_O = \frac{R_f}{R} V_T \left( -\ln\left(\frac{V_S}{R_2 I_S}\right) + \ln\left(\frac{V_S}{R_1 I_S}\right) \right)$$


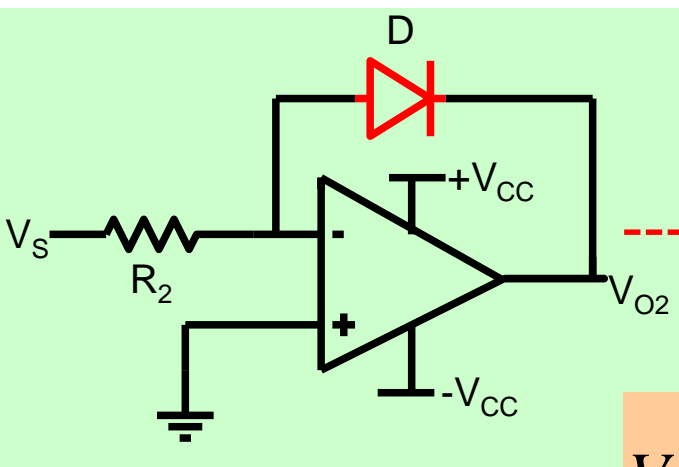
$$V_{O1} = -V_T \times \ln\left(\frac{V_S}{R_1 I_S}\right)$$


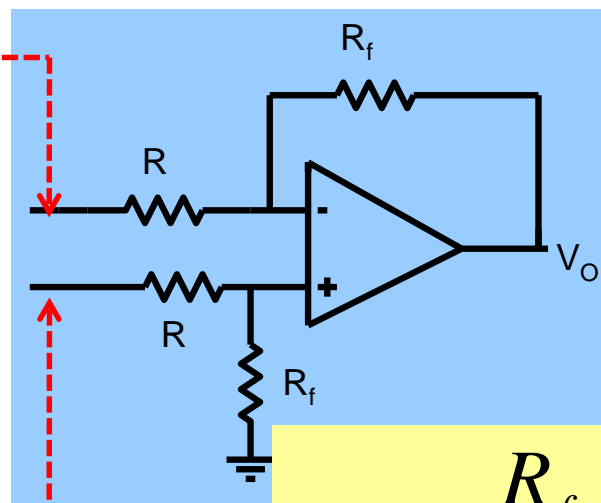
$$V_{O2} = -V_T \times \ln\left(\frac{V_S}{R_2 I_S}\right)$$




$$V_O = \frac{R_f}{R} V_T \times \ln\left(\frac{R_2}{R_1}\right)$$

Output voltage is directly proportional to temperature
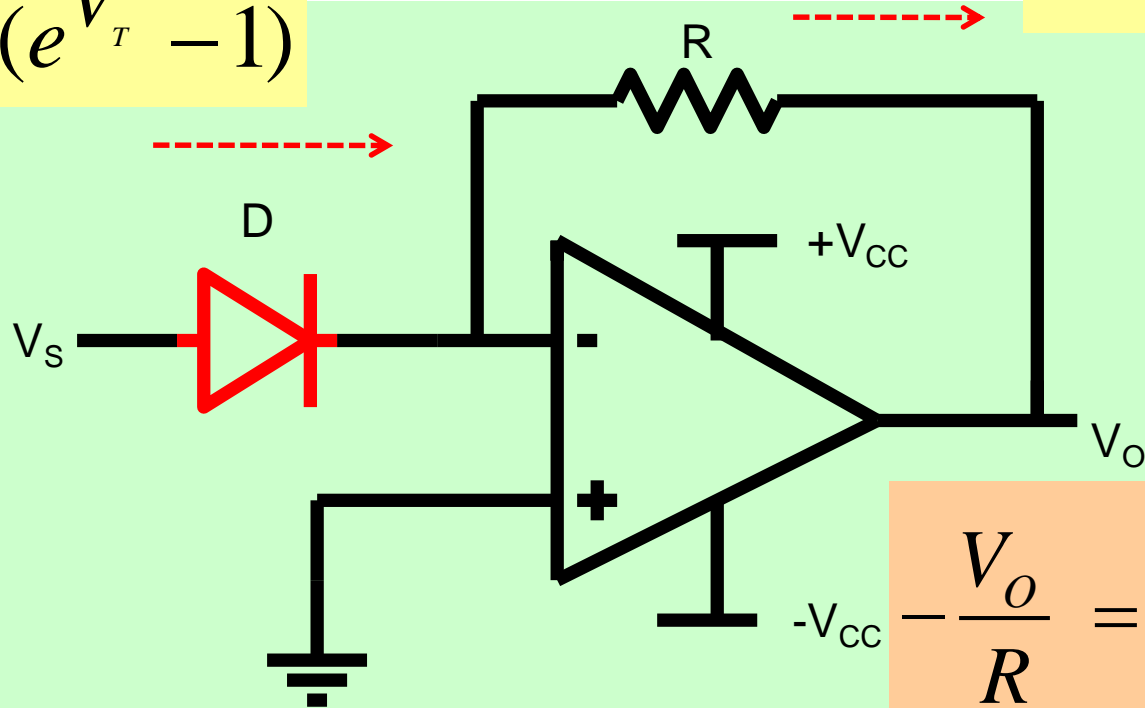
# AntiLog Amplifier

$$I = I_S \left( e^{\frac{V_S}{V_T}} - 1 \right)$$

$$I = I_S \left( e^{\frac{V_S}{V_T}} - 1 \right)$$




$$-\frac{V_O}{R} = I_S \left( e^{\frac{V_S}{V_T}} - 1 \right)$$

$$\Rightarrow V_O = -RI_S \left( e^{\frac{V_S}{V_T}} - 1 \right) \cong -RI_S \times e^{\frac{V_S}{V_T}}$$



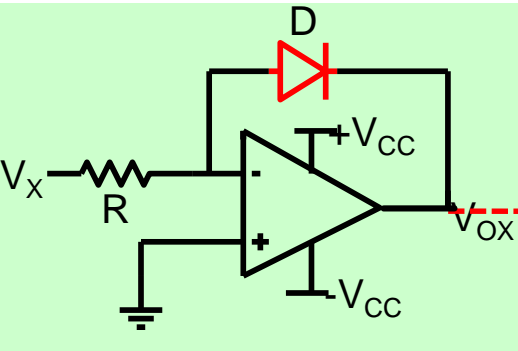
# Multiplier


$$V_{O1} = V_T \times \left( \ln\left(\frac{V_X}{RI_S}\right) + \ln\left(\frac{V_Y}{RI_S}\right) \right)$$



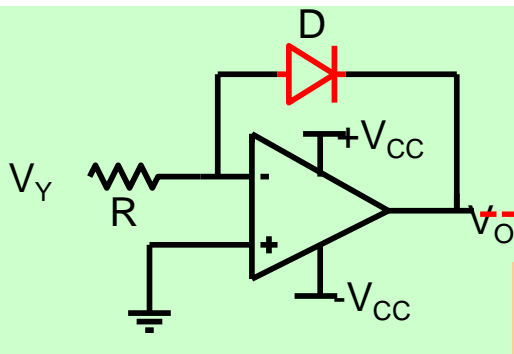
$$V_{OX} = -V_T \times \ln\left(\frac{V_X}{RI_S}\right)$$


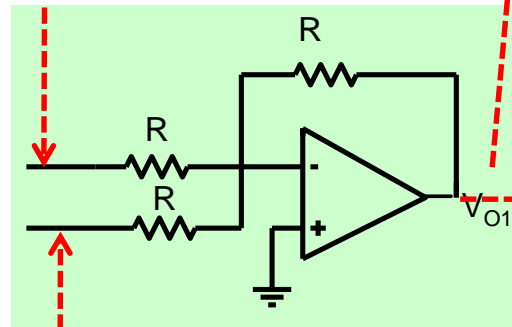
$$V_{OY} = -V_T \times \ln\left(\frac{V_Y}{RI_S}\right)$$







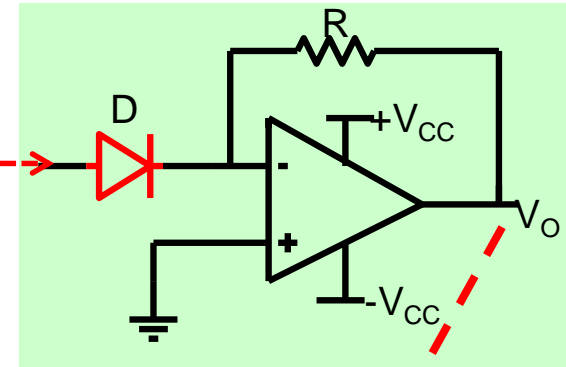
$$V_{O1} = V_T \times \ln\left(\frac{V_X V_Y}{R^2 I_S^2}\right)$$



$$V_O \cong -RI_S \times e^{\frac{V_{O1}}{V_T}} = -\frac{V_X V_Y}{RI_S}$$
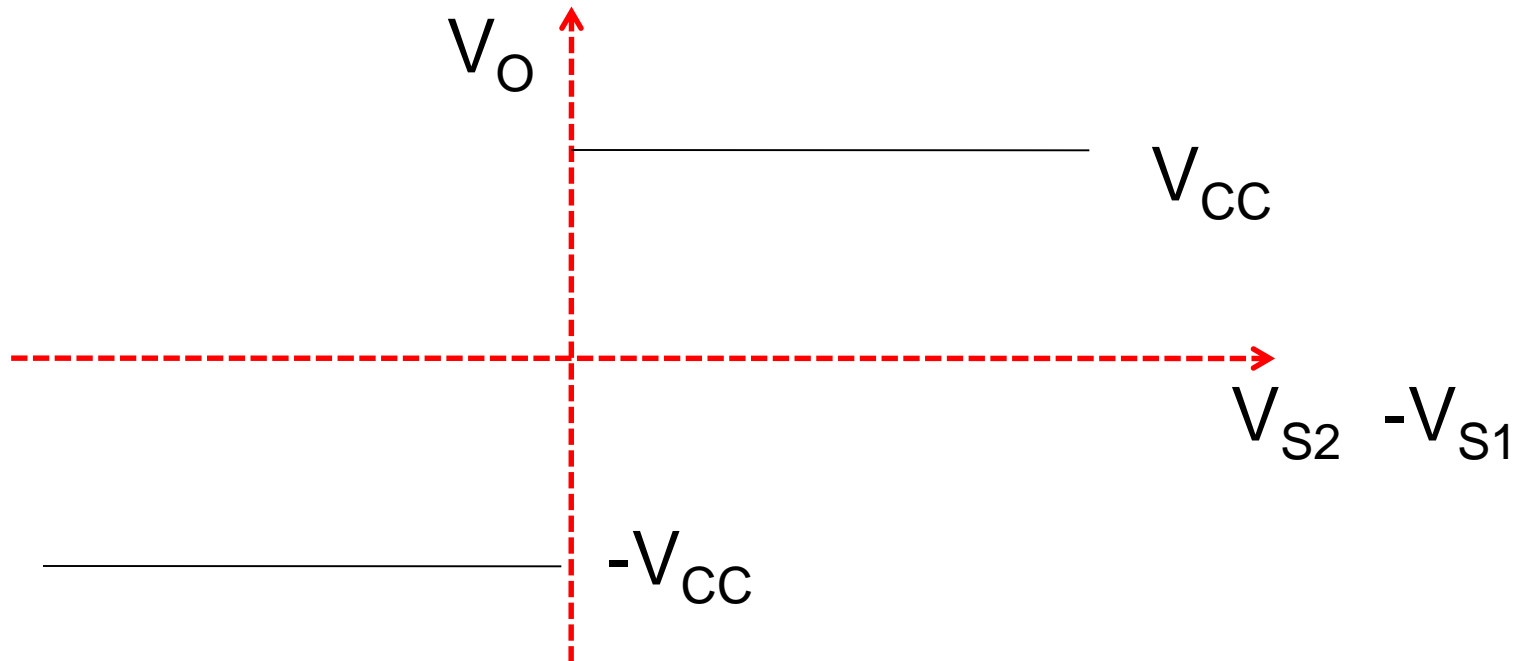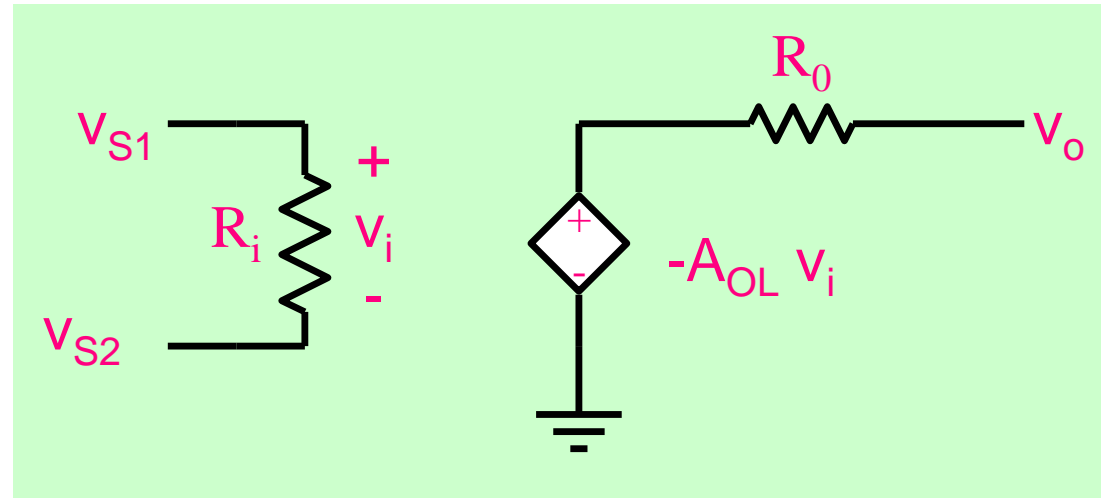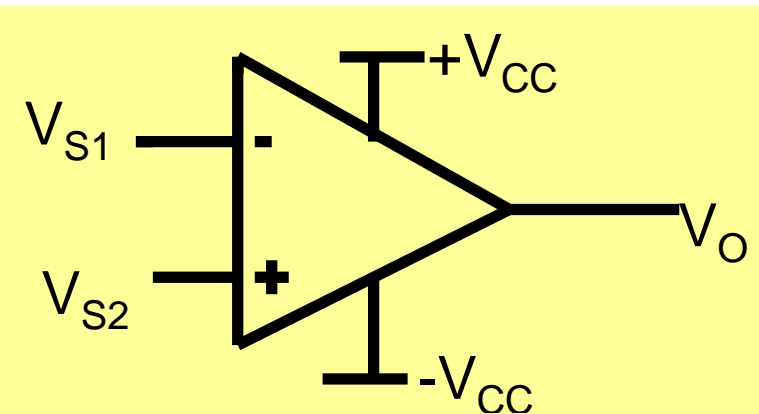
# Comparator: Opamp under open Loop condition



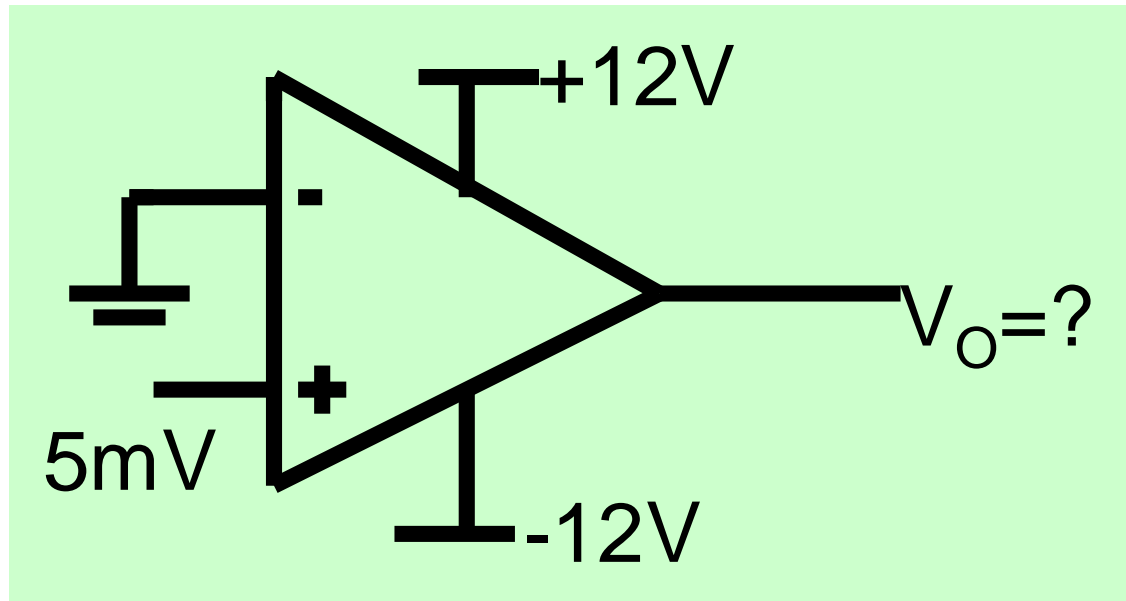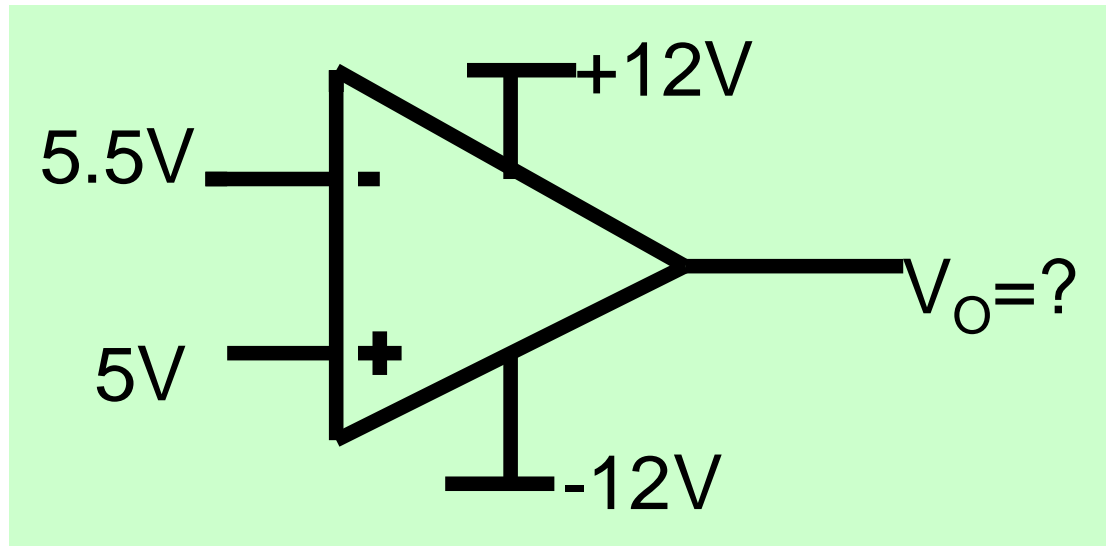



# Example 1: Plot $V_{O1}$ and $V_O$ as a function of time

$$v_{in} = 1V \sin(2\pi ft);$$

$$f = 1KHz$$

$$V_{O1} = +5V \text{ if } v_{in} > 0$$

$$= -5V \text{ if } v_{in} < 0$$

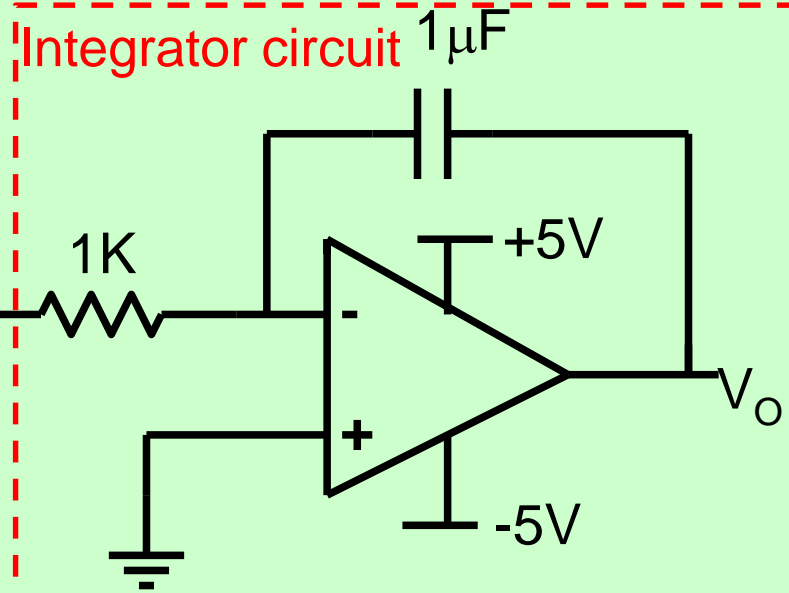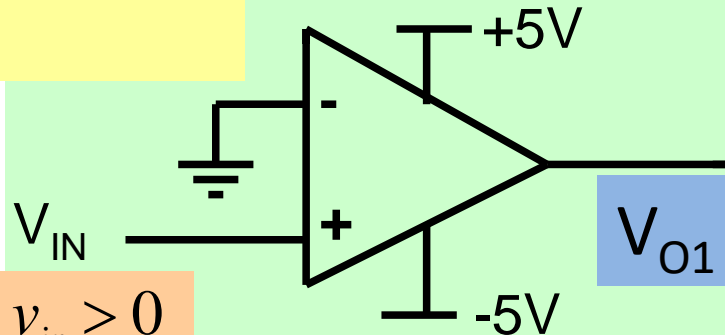

$$\frac{v_s}{R} = -C \frac{dV_o}{dt} \Rightarrow V_o(t) = -\frac{1}{RC} \int v_s dt$$

