
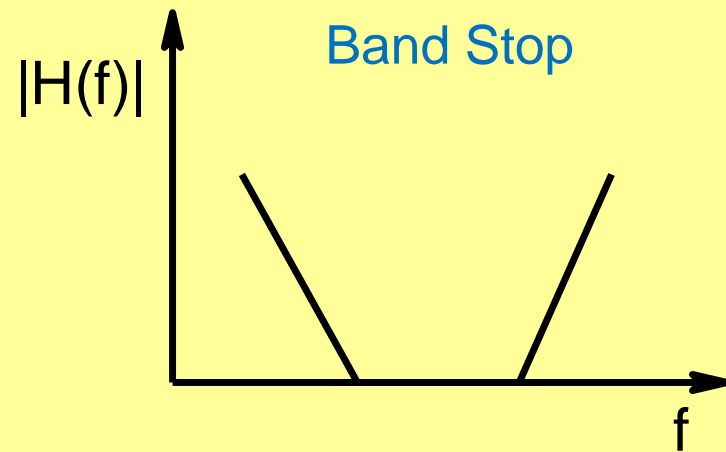
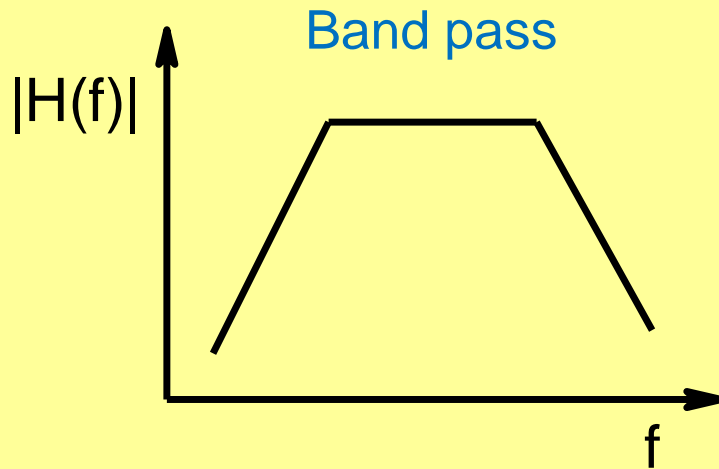
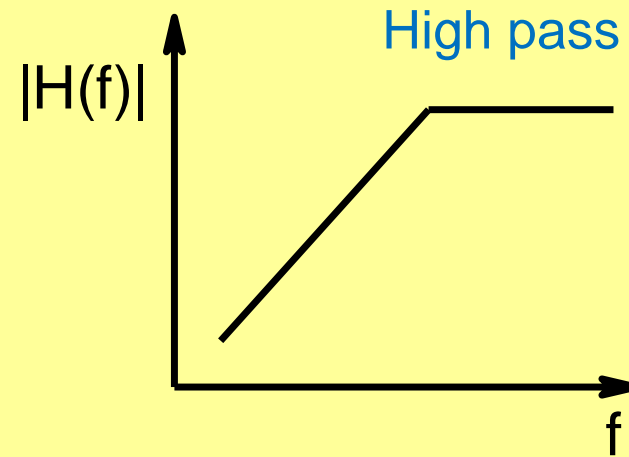


# **ESc201 : Introduction to Electronics**
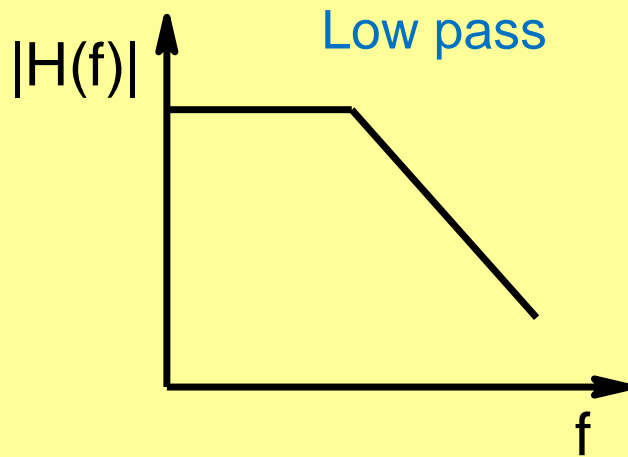
## **Frequency Domain Response**

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur


**Filter** -pass a band of frequency and reject the remaining


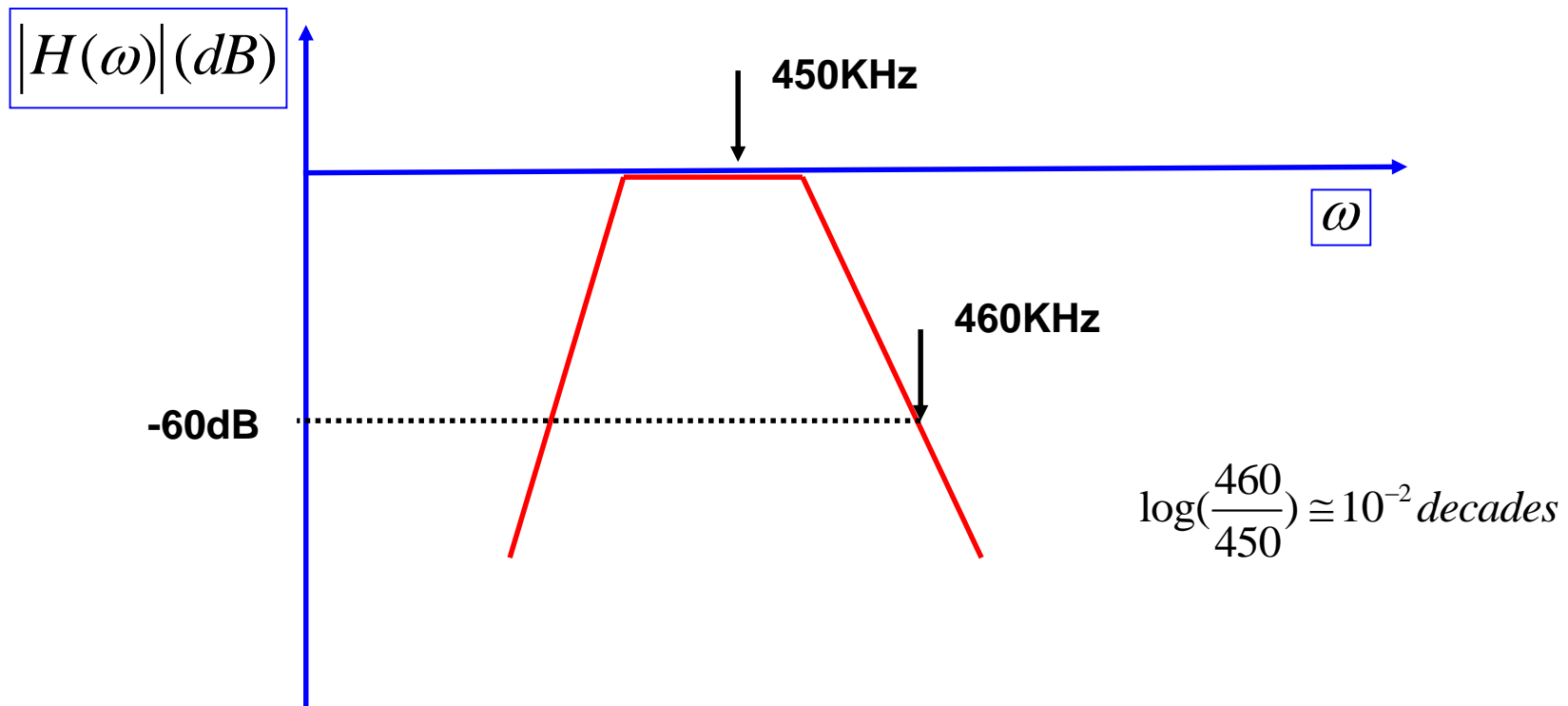
# Amplitude Modulated (AM) Radio

Different radio channels are separated by very narrow frequency interval.


For example, one may want to receive a 450KHz signal but reject 460KHz or 440KHz



This implies an attenuation of -6000 dB/decade !!
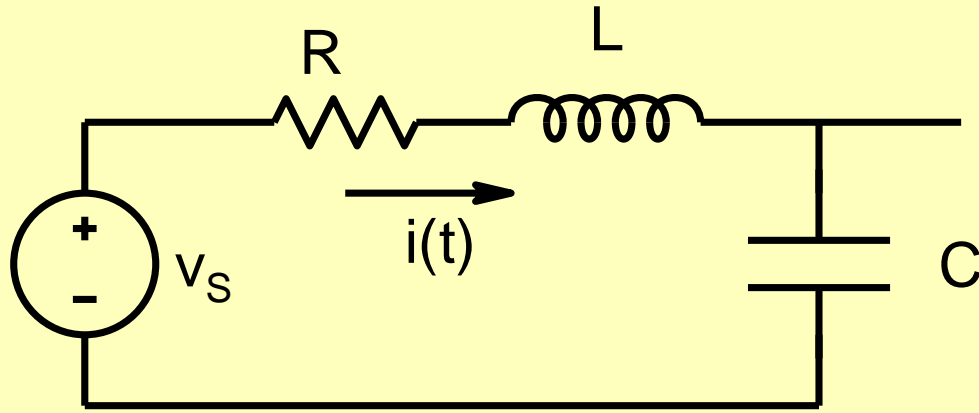
# Series Resonant Circuit

Resonance is a condition in which capacitive and inductive reactance cancel each other to give rise to a purely resistive circuit



$$Z_{eq} = R + j\omega L - j\frac{1}{\omega C}$$


Resonant frequency:

$$j\omega_o L - j\frac{1}{\omega_o C} = 0 \Rightarrow \omega_o = \frac{1}{\sqrt{LC}}$$


$$f_o = \frac{1}{2\pi\sqrt{LC}}$$


$$Z_{eq} = R$$

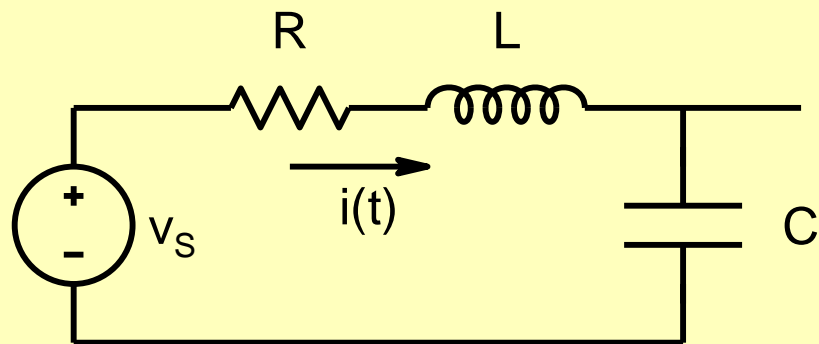Current and voltage are in phase (power factor is unity) and current is maximum !



$$|I(\omega)| = \frac{V_m}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

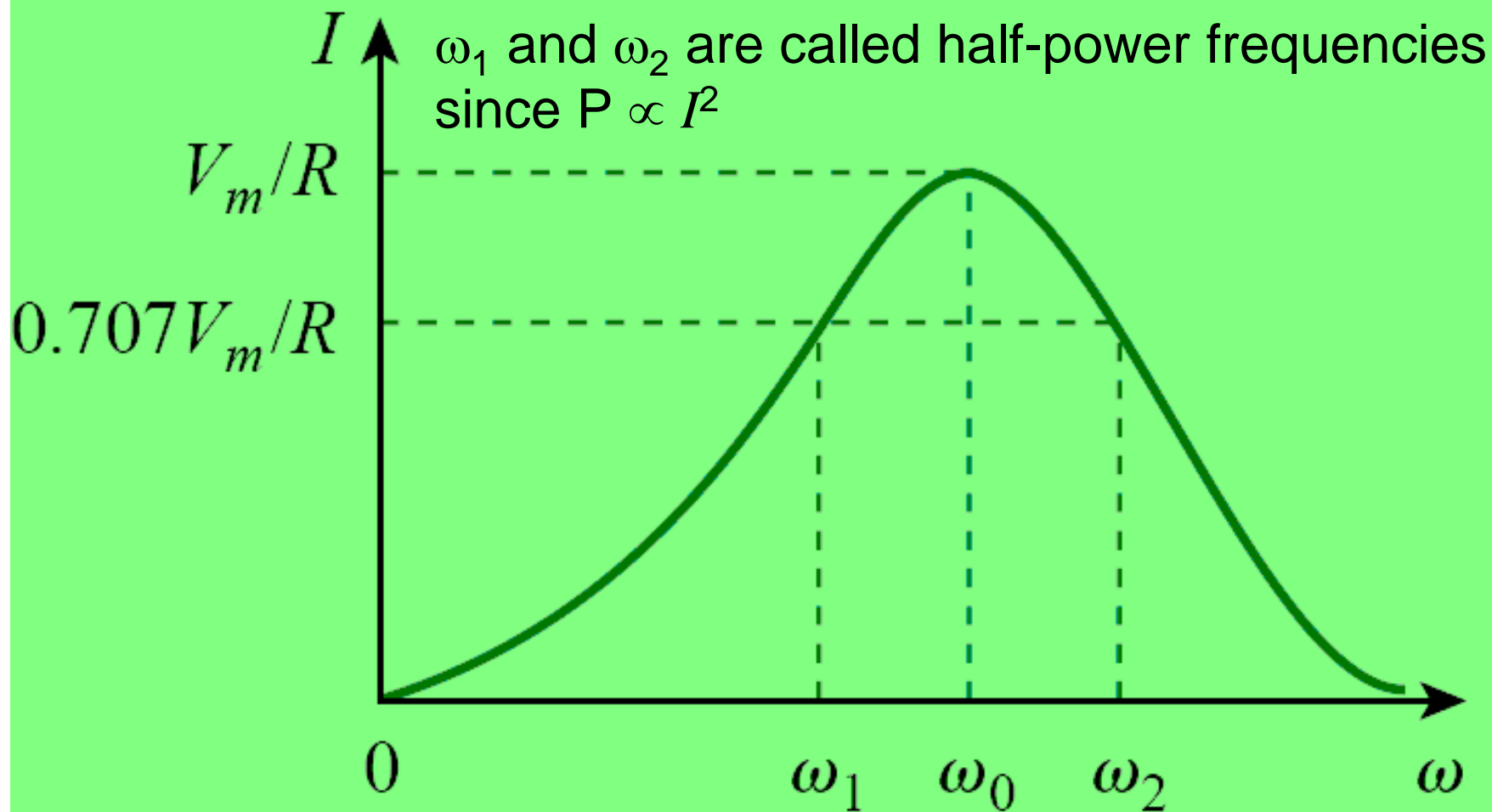

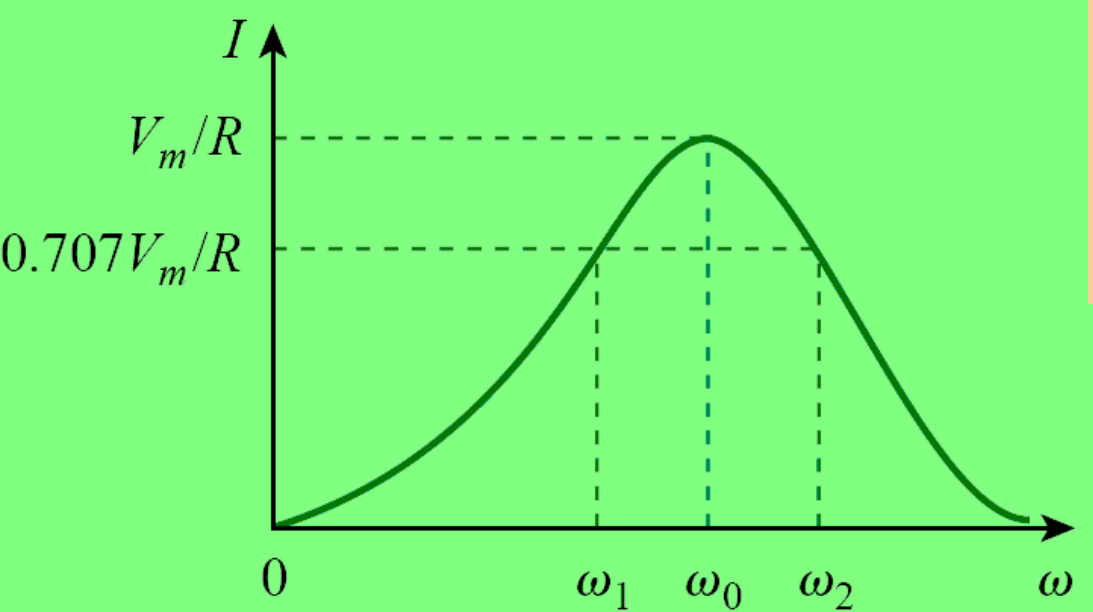

$$|I(\omega)| = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$


$$|I(\omega_1)| = \frac{V_m}{\sqrt{R^2 + (\omega_1 L - \frac{1}{\omega_1 C})^2}} = \frac{V_m}{\sqrt{2}R}$$

$$|I(\omega_2)| = \frac{V_m}{\sqrt{R^2 + (\omega_2 L - \frac{1}{\omega_2 C})^2}} = \frac{V_m}{\sqrt{2}R}$$

$\omega_1$  and  $\omega_2$  are called half-power frequencies since  $P \propto I^2$

$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$
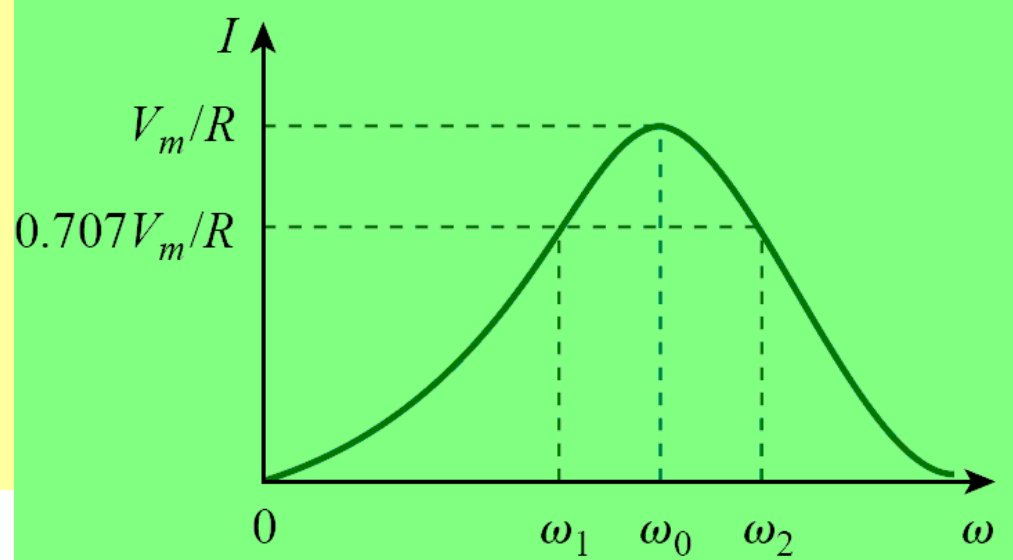
$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$



$$\omega_o = \sqrt{\omega_1 \omega_2}$$

$$B = \omega_2 - \omega_1 = \frac{R}{L}$$

**Quality (Q) factor: Sharpness of resonance**


$$Q = \frac{\omega_o L}{R}$$

$$\omega_o = \frac{1}{\sqrt{LC}} \Rightarrow Q = \frac{1}{\omega_o CR}$$

$$B = \omega_2 - \omega_1 = \frac{R}{L}$$

$$Q = \frac{\omega_o}{B} = \frac{\omega_o}{\Delta\omega}$$

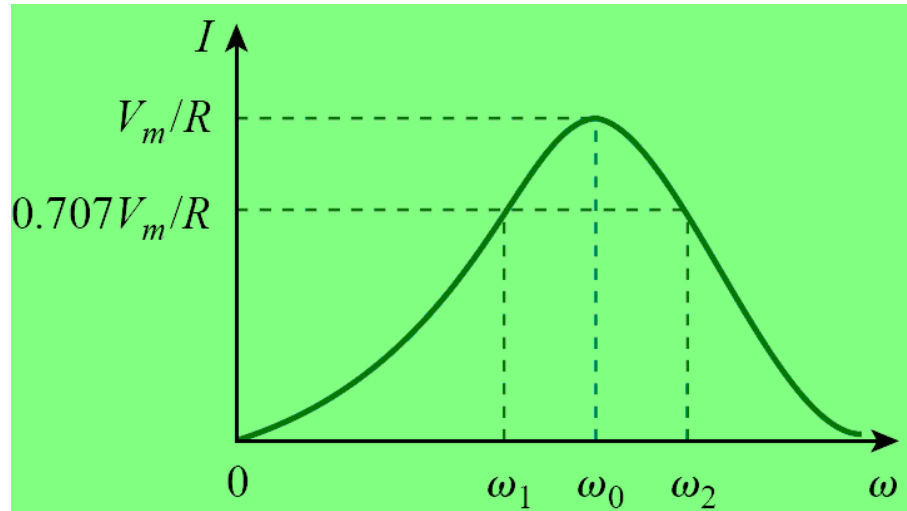Hence Q represents sharpness of resonance





For high Q circuits:





$$\omega_1 \simeq \omega_0 - \frac{B}{2}, \quad \omega_2 \simeq \omega_0 + \frac{B}{2}$$









$$Q = \frac{\omega_o L}{R}$$

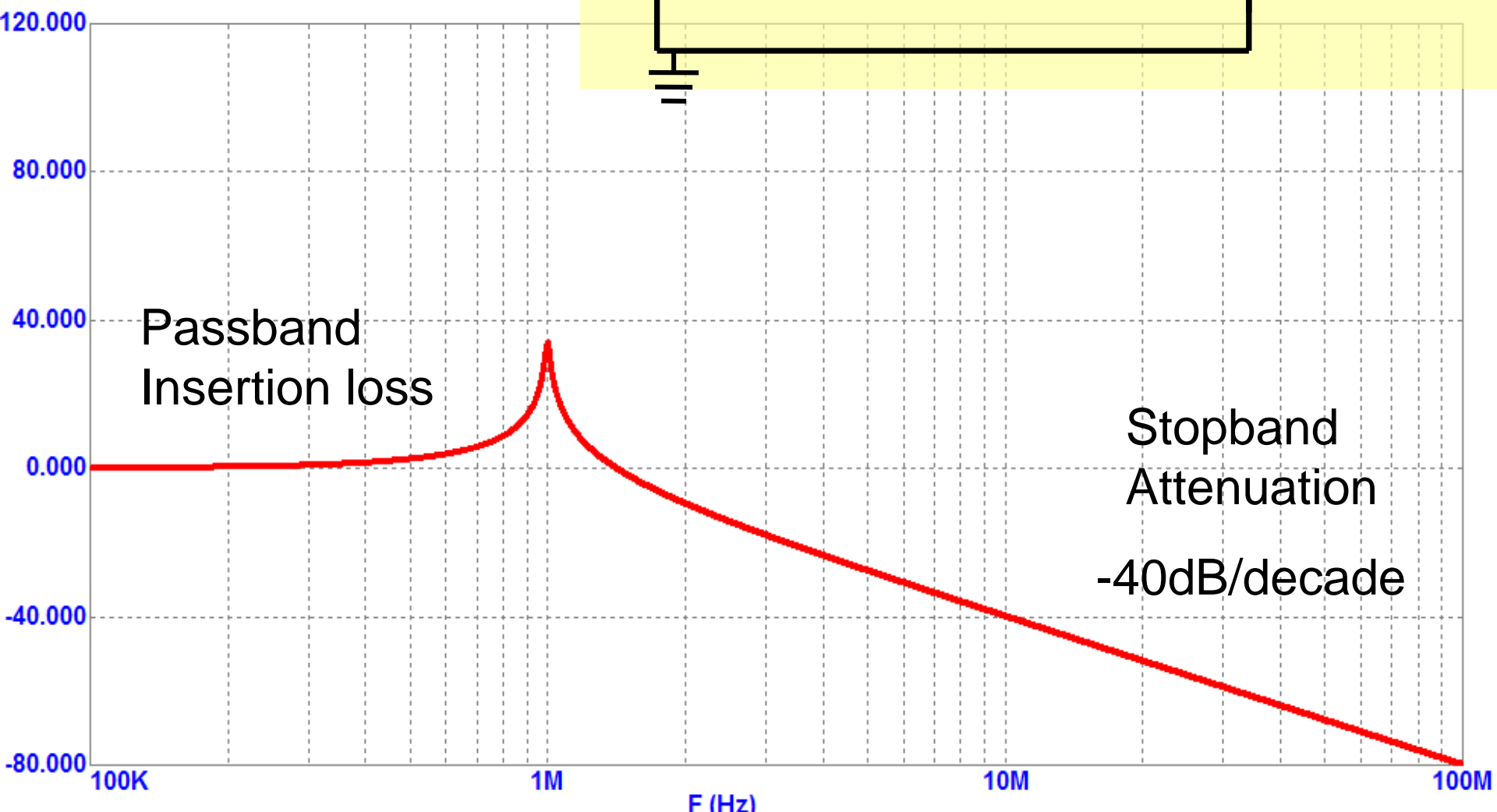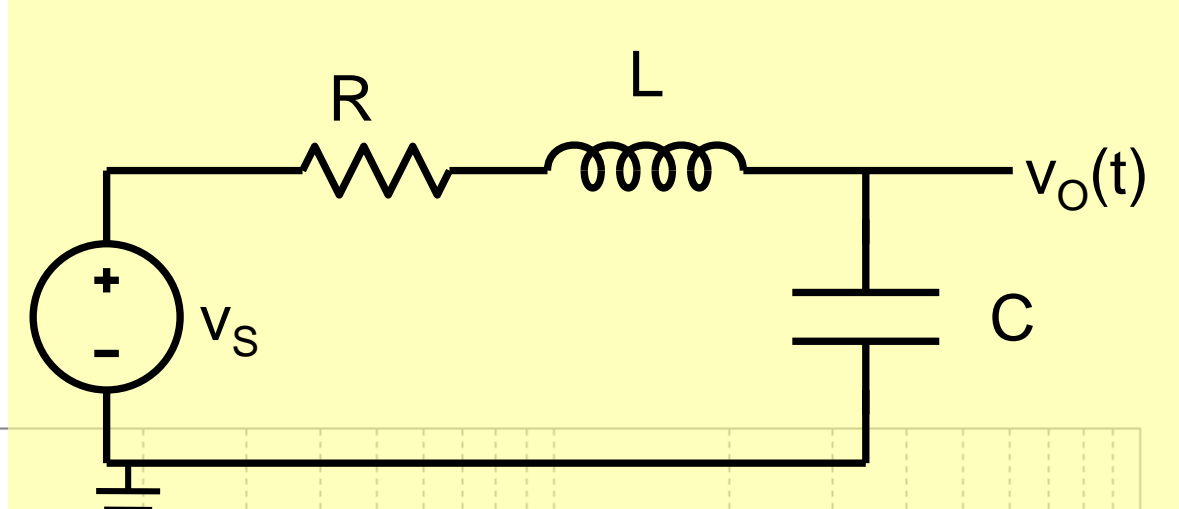

# R-L-C filters

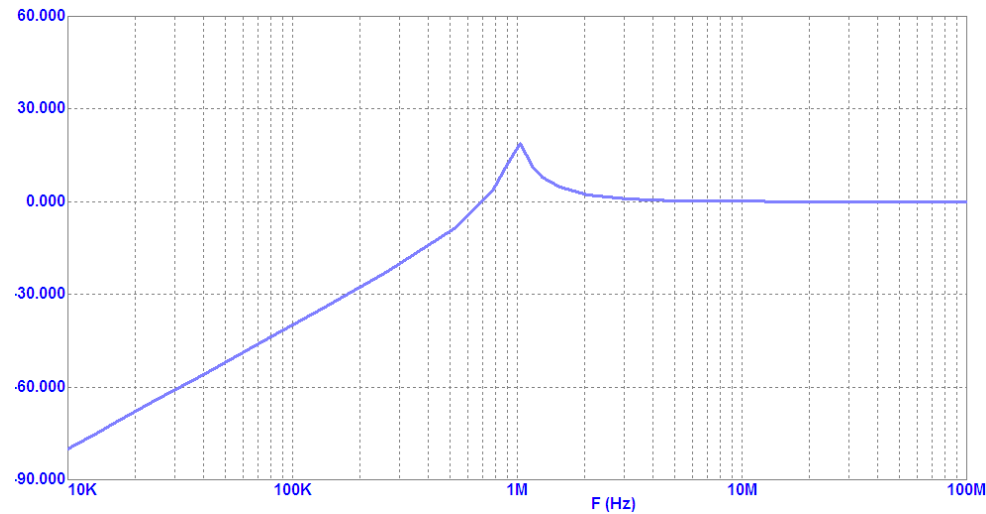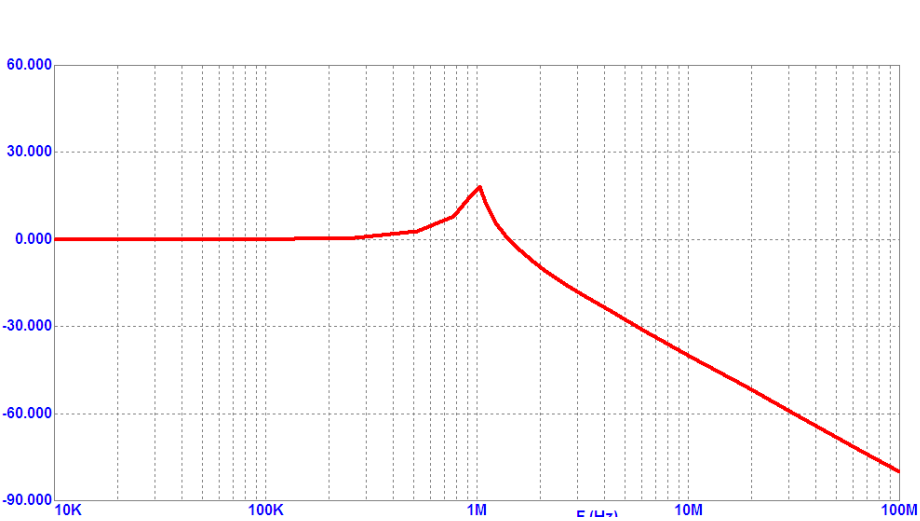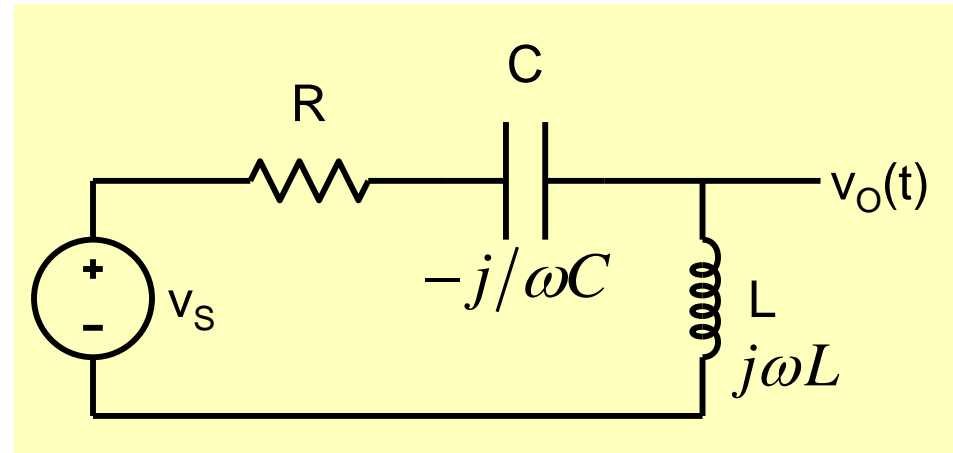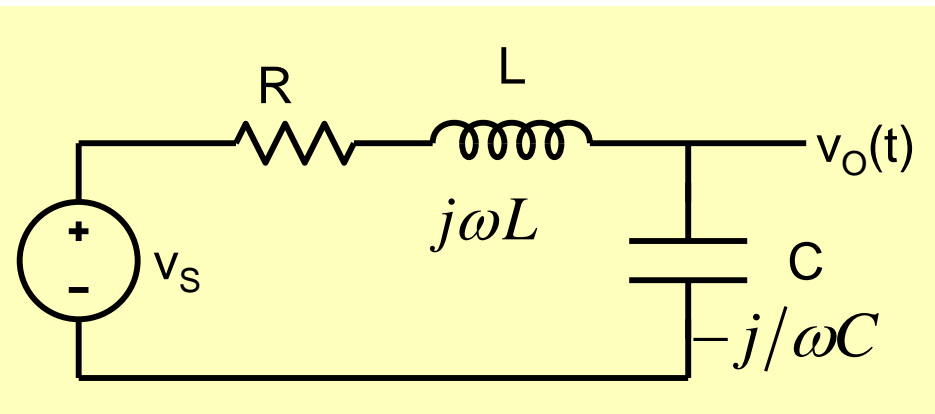

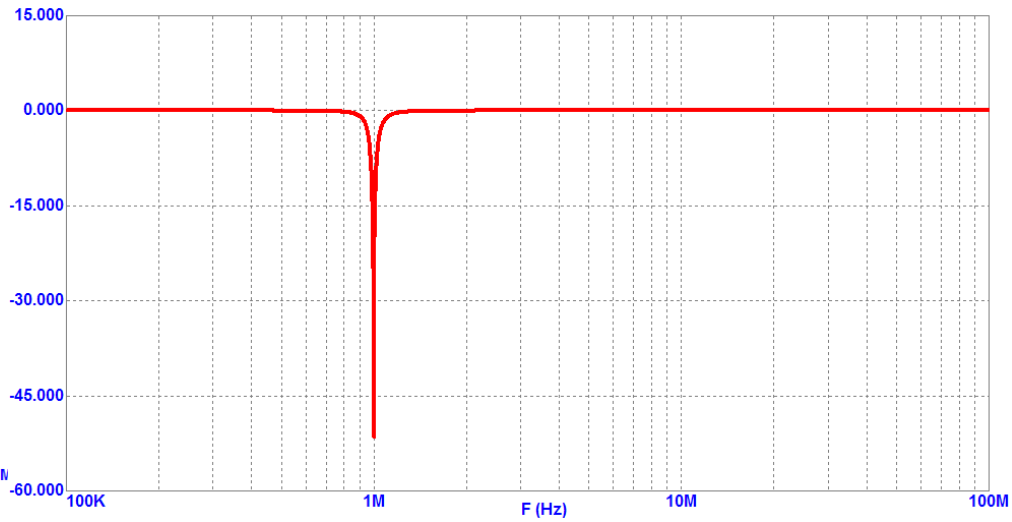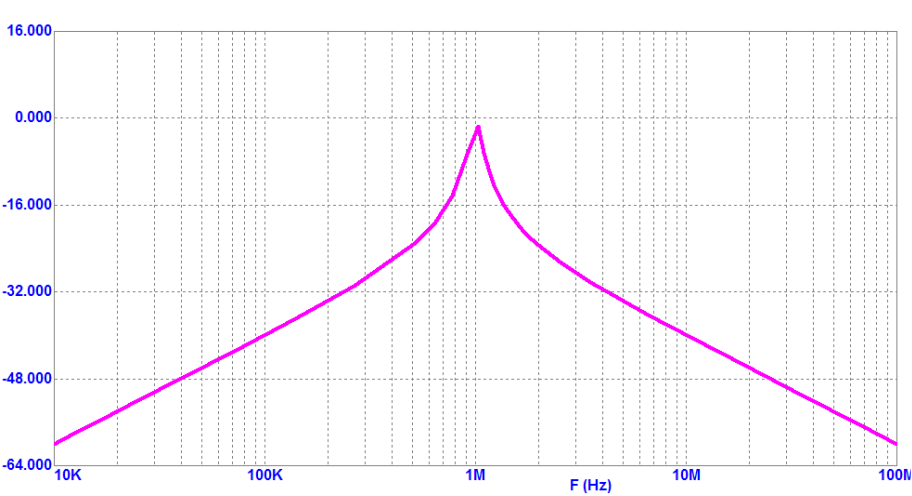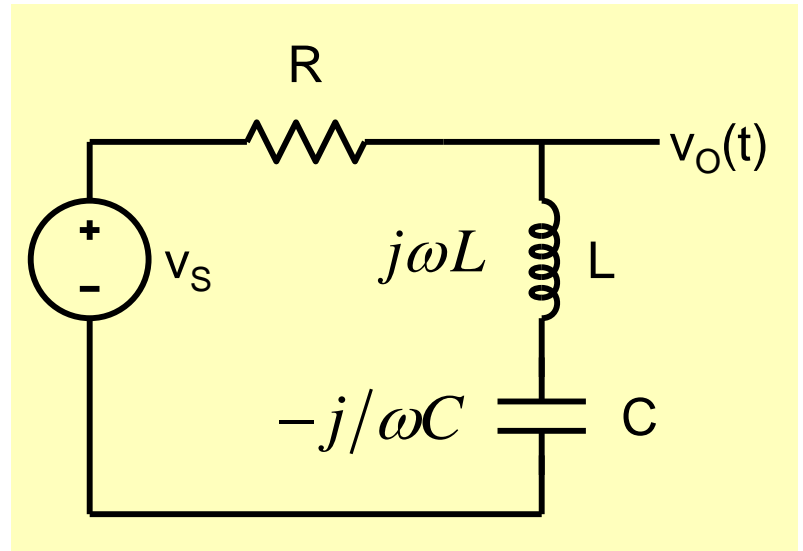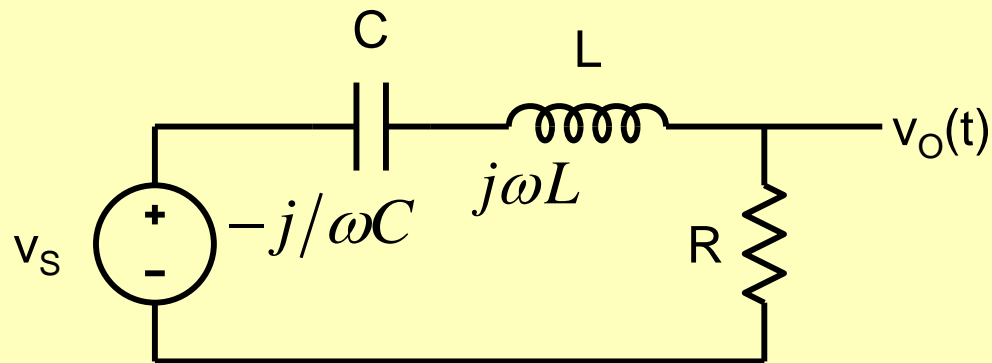

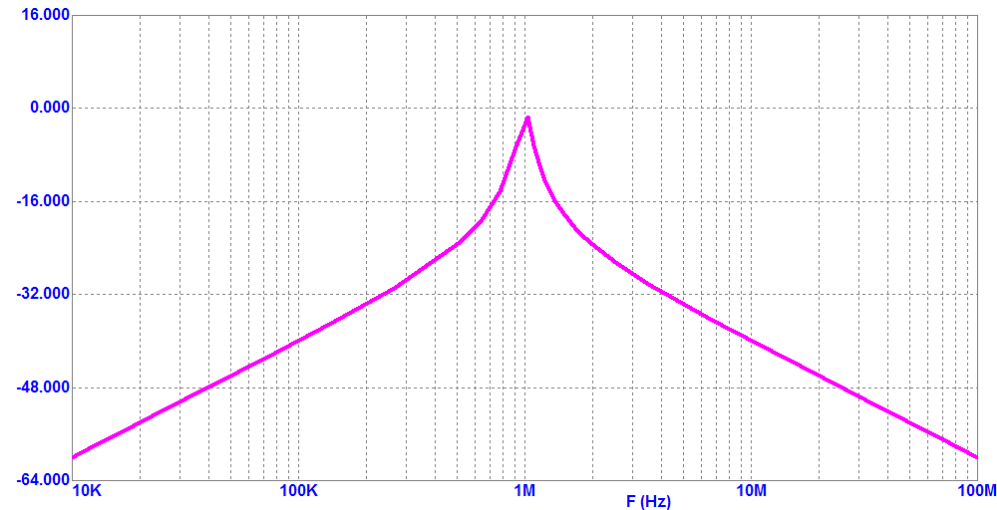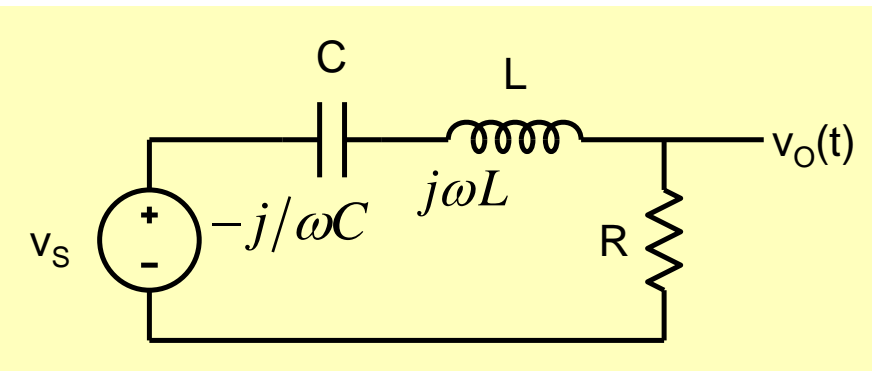

How much Q do we need to pass 450KHz but reject 460KHz by 60dB?

$$|H(\omega)| = \left| \frac{V_o(\omega)}{V_{IN}(\omega)} \right| = \frac{R}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

Assuming  $V_{IN} = 1V$  and noting that  $Q = \omega_o L/R$

$$|V_o(\omega)| = \frac{1}{\sqrt{1 + Q^2 \left( \frac{\omega^2}{\omega_o^2} - 1 \right)^2}}$$

For  $\omega = \omega_o$ ,  $V_o = 1$  so the signal simply passes through !

$$\omega_o = 2 \times \pi \times 450 \times 10^3 = 2.8 \times 10^6 \text{ rad} / s$$

$$|V_o(\omega)| = \frac{1}{\sqrt{1 + Q^2 \left(1 - \frac{\omega_o^2}{\omega^2}\right)^2}}$$


$$\omega_0 = 2\pi \times 450 \times 10^3 = 2.827 \times 10^6 \text{ rad} / \text{s}$$

$$\omega = 2\pi \times 460 \times 10^3 = 2.89 \times 10^6 \text{ rad} / \text{s}$$


For an attenuation of -60dB or  $10^{-3}$  at  $\omega$ : **Q=23,000**

This is a large value of Q!

# Parallel Resonance

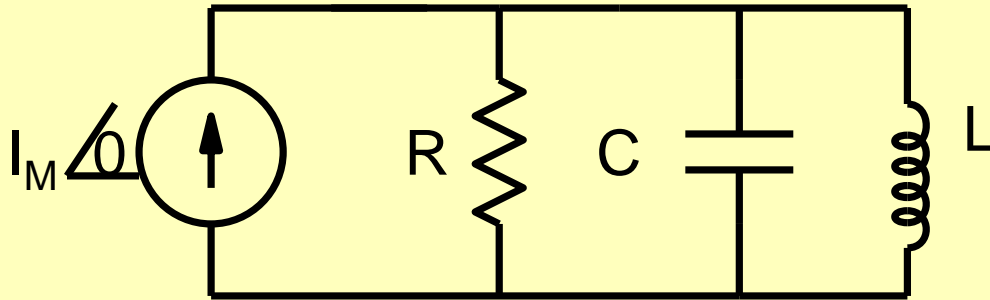
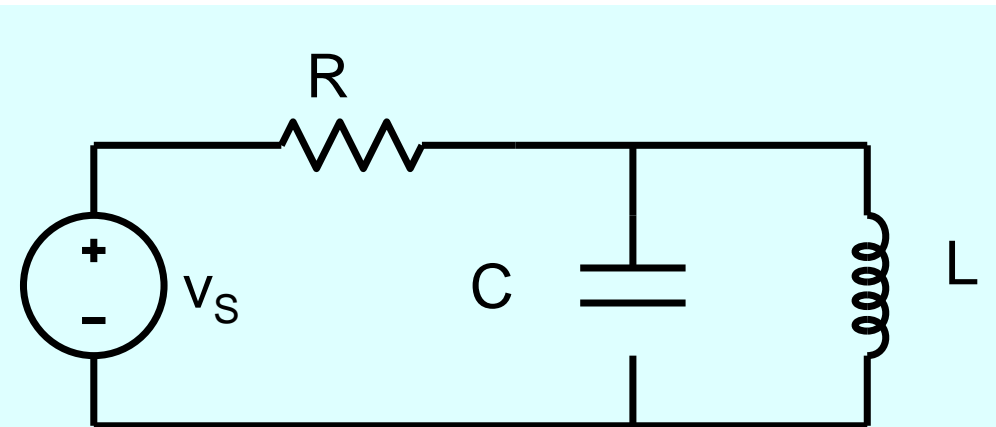
$$Y_{eq} = \frac{1}{R} + j\omega C - j\frac{1}{\omega L}$$




Resonant frequency:


$$f_o = \frac{1}{2\pi\sqrt{LC}}$$

$$j\omega_o C - j\frac{1}{\omega_o L} = 0 \Rightarrow \omega_o = \frac{1}{\sqrt{LC}}$$

$$Z_{eq} = R$$

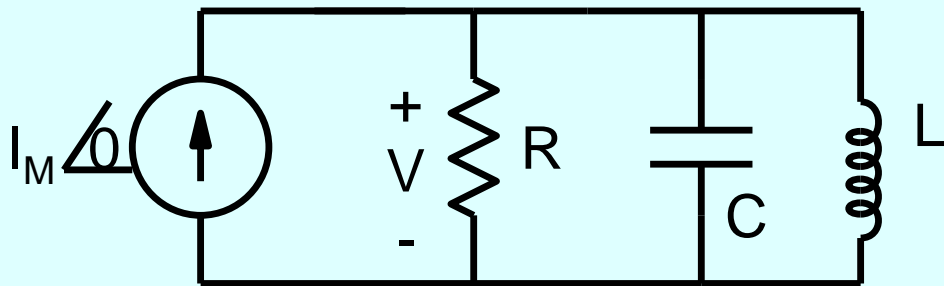

$$|V(\omega)| = \frac{I_m R}{\sqrt{1 + \frac{R^2 C^2}{L^2} \left( \omega L - \frac{1}{\omega C} \right)^2}}$$

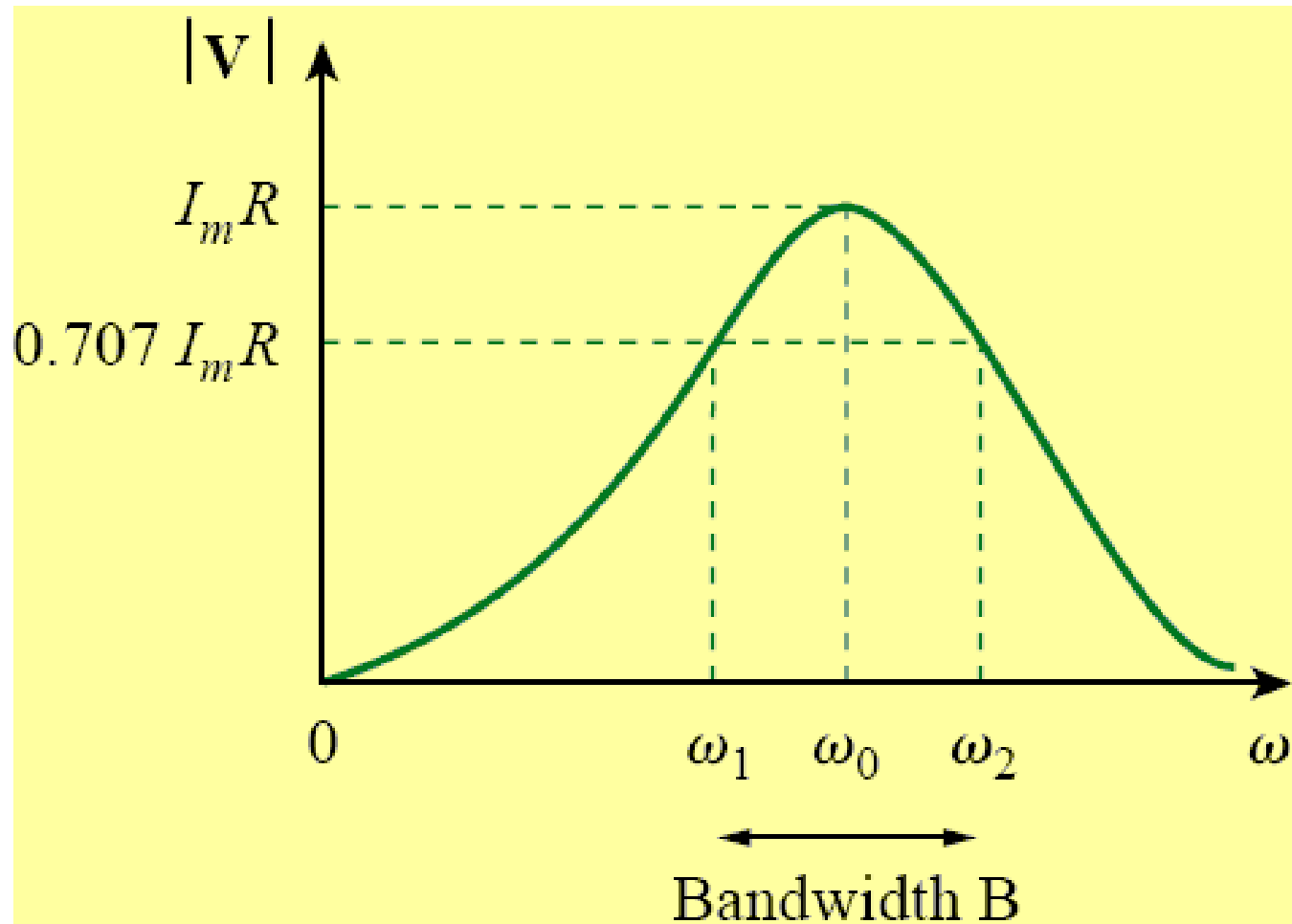

$$|V(\omega)| = \frac{I_m R}{\sqrt{1 + \frac{R^2 C^2}{L^2} \left( \omega L - \frac{1}{\omega C} \right)^2}}$$

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left( \frac{1}{2RC} \right)^2 + \frac{1}{LC}}$$


$$\omega_2 = \frac{1}{2RC} + \sqrt{\left( \frac{1}{2RC} \right)^2 + \frac{1}{LC}}$$

$$B = \omega_2 - \omega_1 = \frac{1}{RC}$$

$$\omega_1 = \omega_0 \sqrt{1 + \left( \frac{1}{2Q} \right)^2} - \frac{\omega_0}{2Q}, \quad \omega_2 = \omega_0 \sqrt{1 + \left( \frac{1}{2Q} \right)^2} + \frac{\omega_0}{2Q}$$

For high Q:

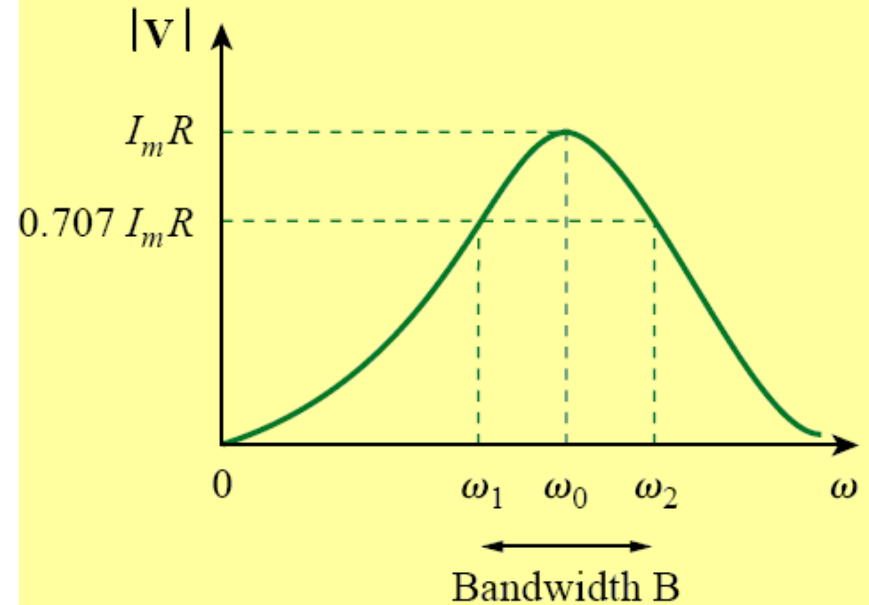
$$\omega_1 \simeq \omega_0 - \frac{B}{2}, \quad \omega_2 \simeq \omega_0 + \frac{B}{2}$$



$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$



## What is the resonant frequency ?

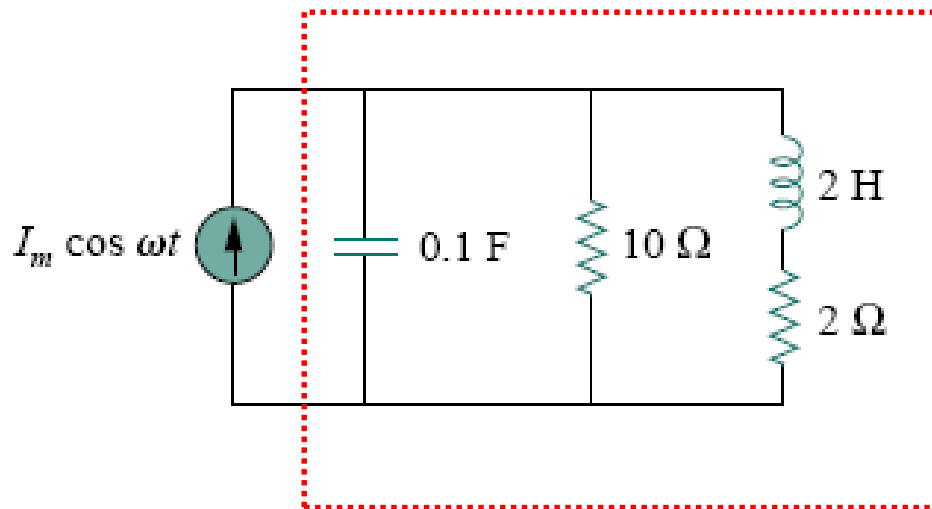


$$\mathbf{Y} = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

At resonance,  $\text{Im}(\mathbf{Y}) = 0$

$$\omega_0 0.1 - \frac{2\omega_0}{4 + 4\omega_0^2} = 0 \quad \implies \quad \omega_0 = 2 \text{ rad/s}$$

$$f_o = \frac{\omega_o}{2\pi}$$

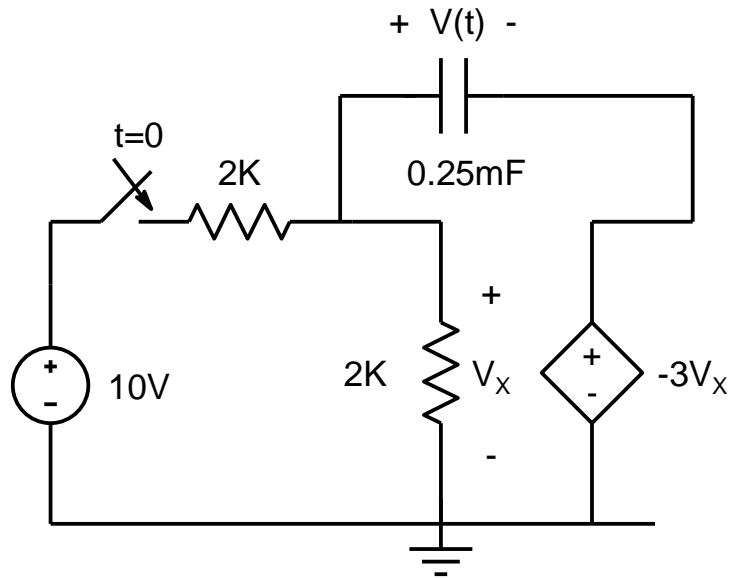
Q.1 Assuming that the capacitor does not have any initial charge, determine the voltage across the capacitor  $V(t)$  as a function of time after the switch is closed at  $t = 0$ . Also find the energy stored in the capacitor at  $t = 1$  s.



$$v(t) = v(\infty) + \{v(0^+) - v(\infty)\}e^{-\frac{t}{\tau}}$$

$$v(0^-) = v(0^+) = 0$$

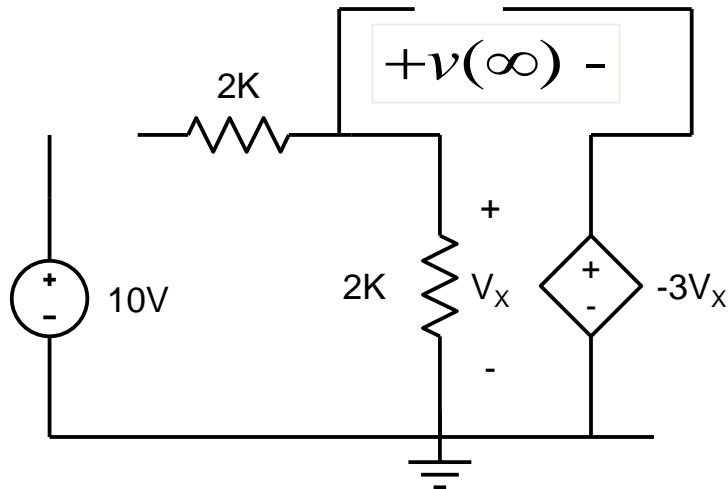$v(\infty)$  can be found from the circuit




$$v_x = \frac{2K}{2K + 2K} \times 10 = 5V$$

$$v(\infty) = V_x - (-3V_x) = 4V_x = 20V$$

$$\tau = CR_{eq}$$

$R_{eq}$  can be found from the circuit:

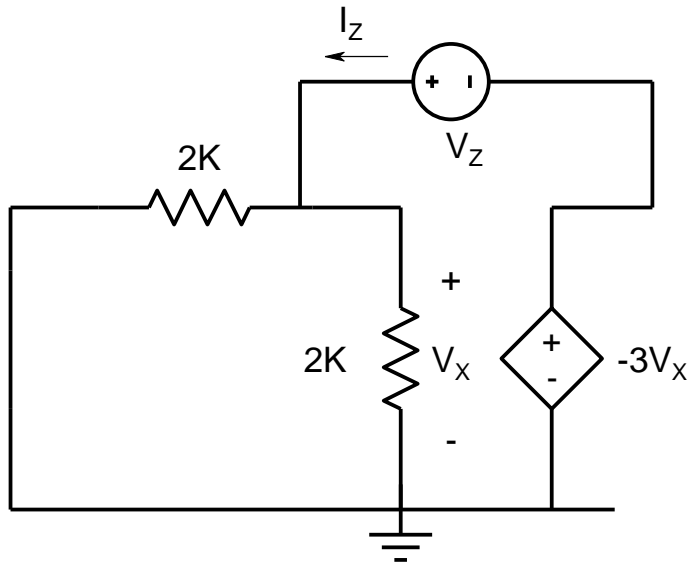

$$R_{eq} = \frac{v_Z}{i_Z}$$

$$v_Z = v_X - (-3v_X) = 4v_X$$

$$i_Z = \frac{v_X}{1K}$$


$$R_{eq} = \frac{v_Z}{i_Z} = 4K$$

$$\tau = CR_{eq} = 1s$$

$$v(t) = 20\{1 - e^{-t}\}$$

$$\text{Energy Stored} = \frac{1}{2} * C * v(t = 1)^2 = 20 \text{ mJ}$$

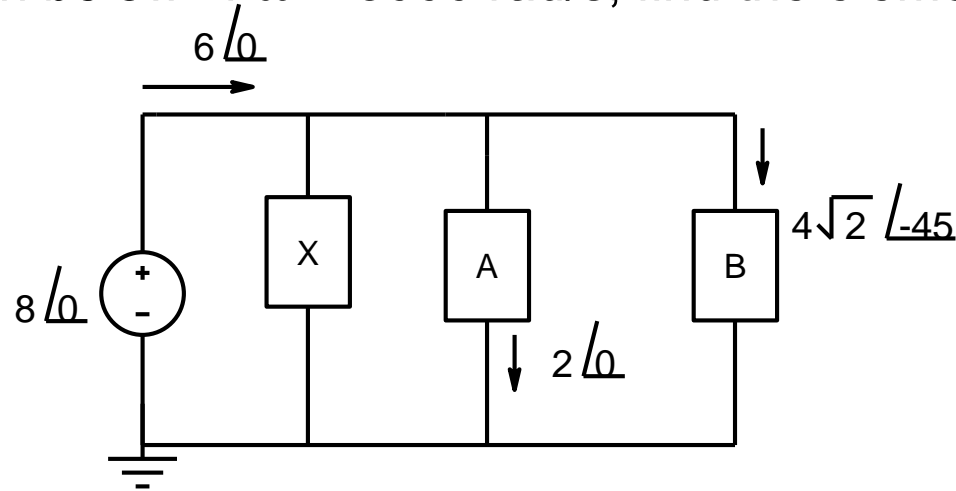Q.2 Determine the impedance of element X for the given currents and voltages in the circuit shown below. If  $\omega = 5000$  rad/s, find the element X value ?



$$6\angle 0 = i_X + 2\angle 0 + 4\sqrt{2}\angle -45$$

$$= i_X + 2 + 4 - 4j$$

$$\Rightarrow i_X = 4j$$

$$\Rightarrow Z_X = \frac{8}{4j} = -2j$$

Element X is a capacitor

$$-\frac{j}{\omega C} = -2j \rightarrow C = \frac{1}{2\omega} \rightarrow C = 100 \mu F$$