

# **ESc201 : Introduction to Electronics**

## **DC Power Supply**


Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur

# Recap: Diode Models


$$i_D = I_S \times \left\{ \exp\left(\frac{v_d}{V_T}\right) - 1 \right\}$$

Simplicity



Accuracy


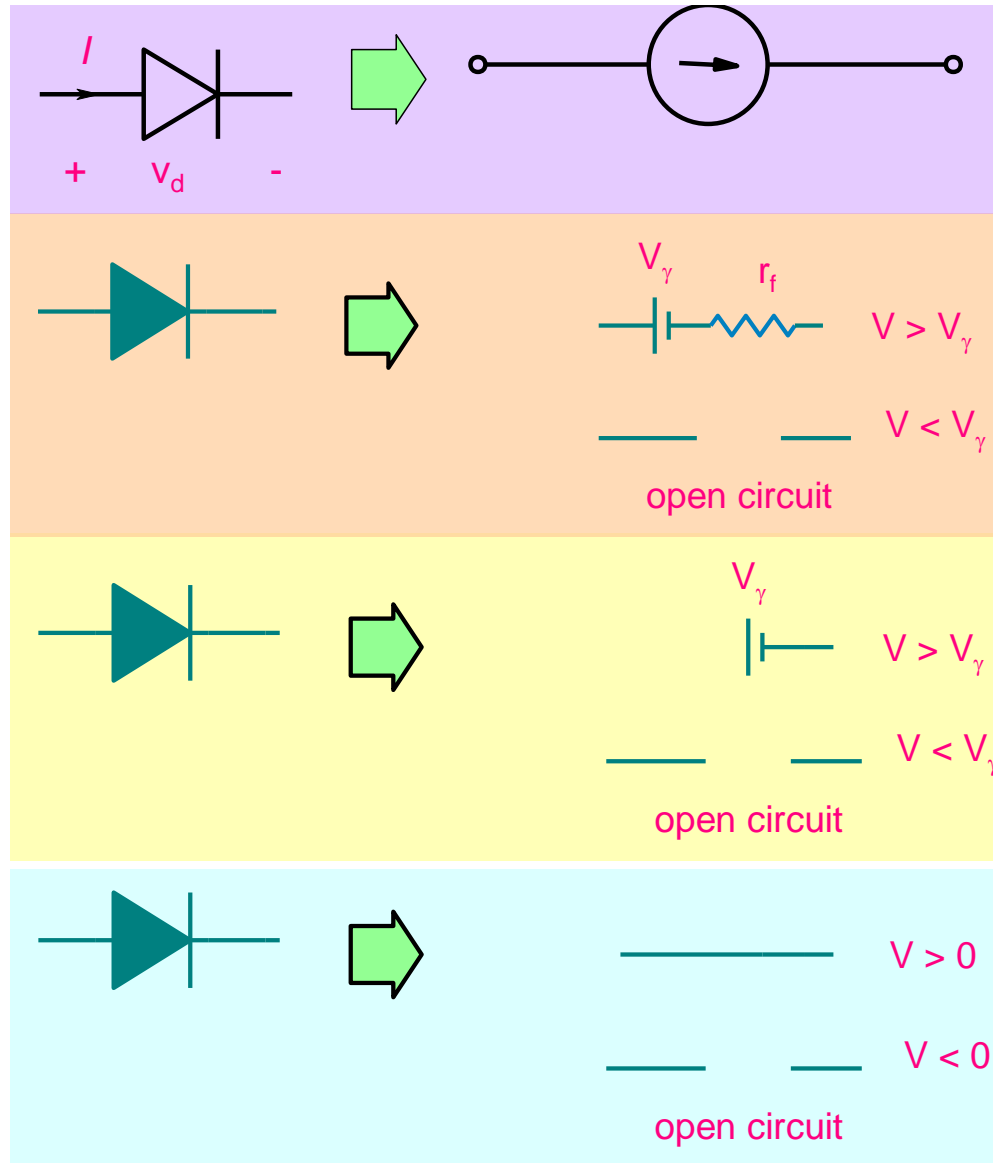



# Half vs Full wave Rectifier

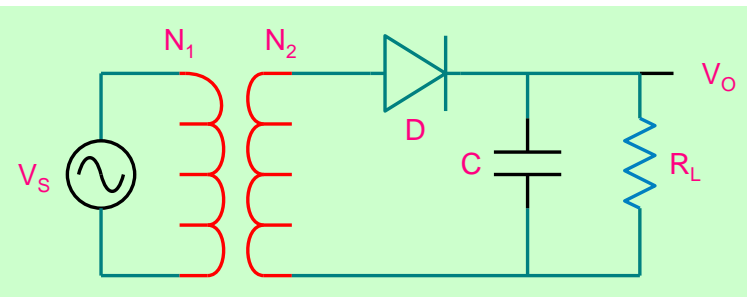

$$V_r \cong \frac{V_M}{fR_L C}$$

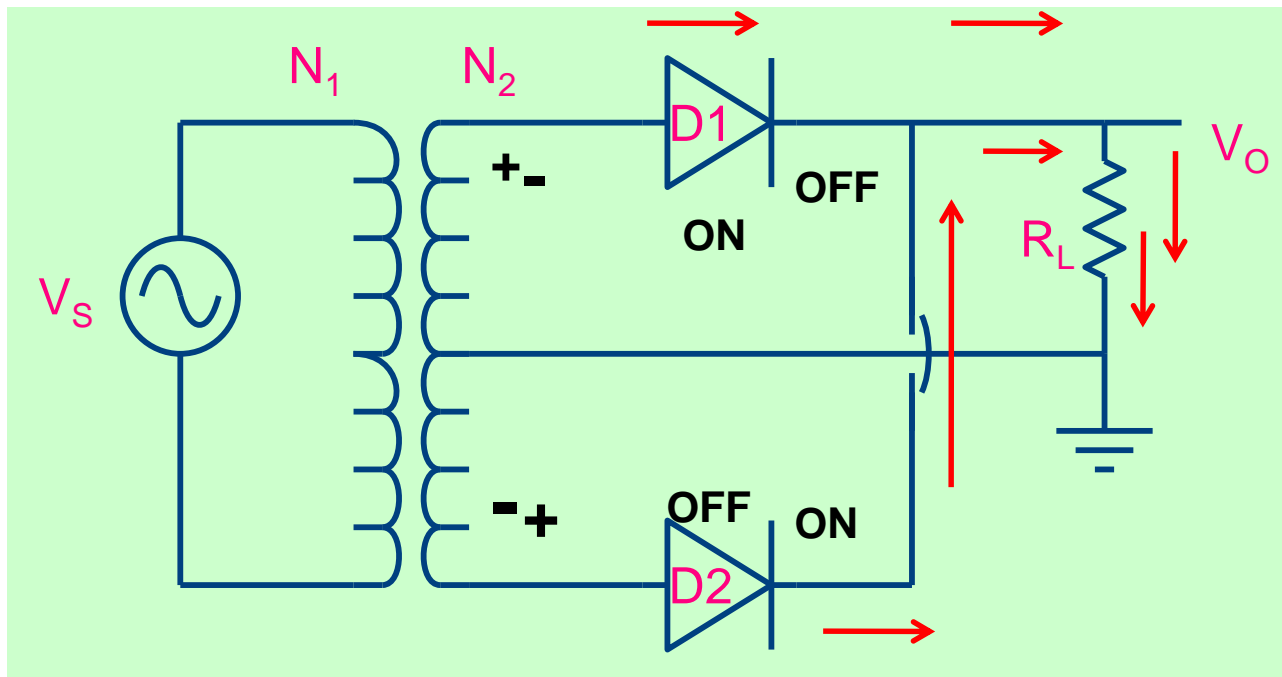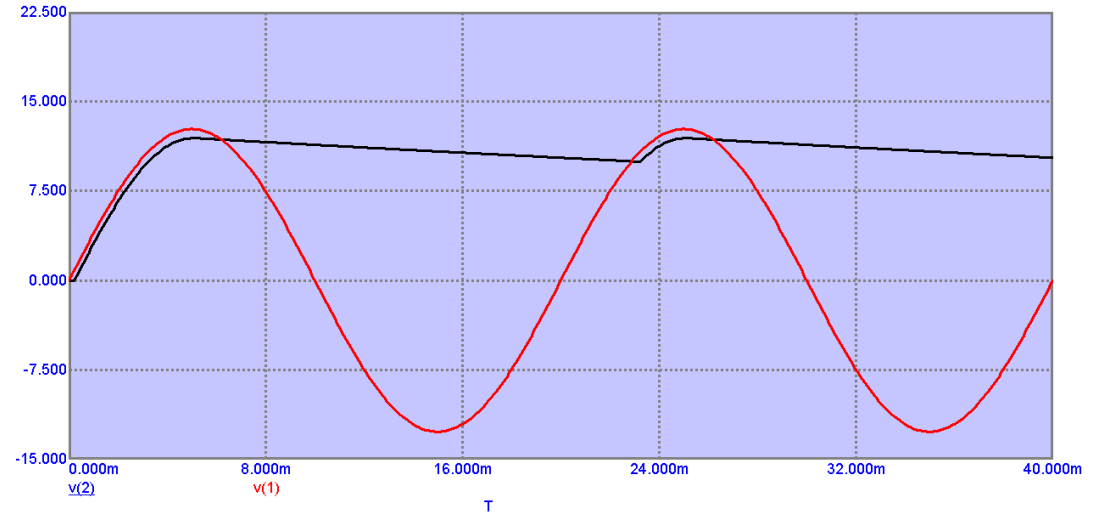


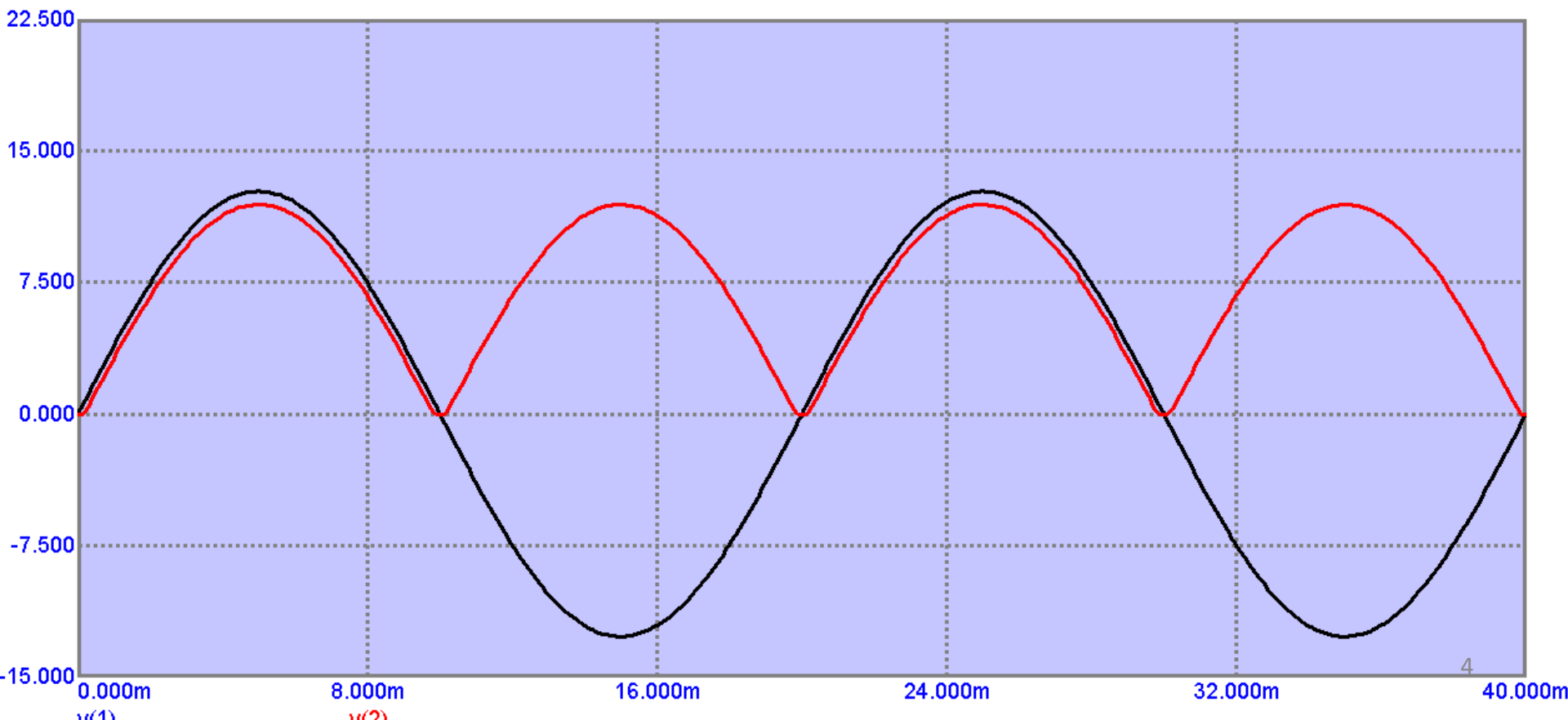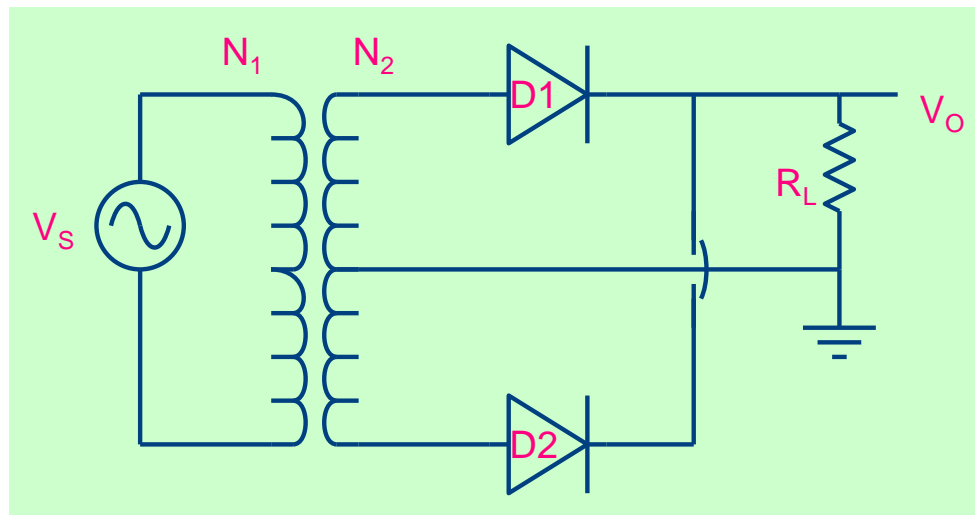

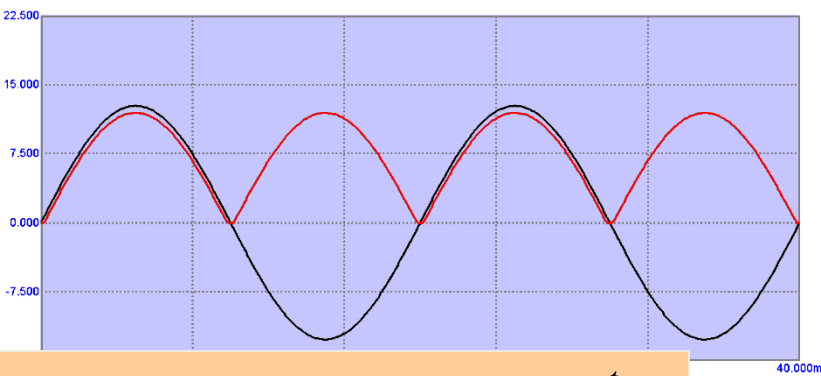


$$V_r = V_M - V_L = V_M \times (1 - e^{-\frac{t_1}{R_L C}})$$
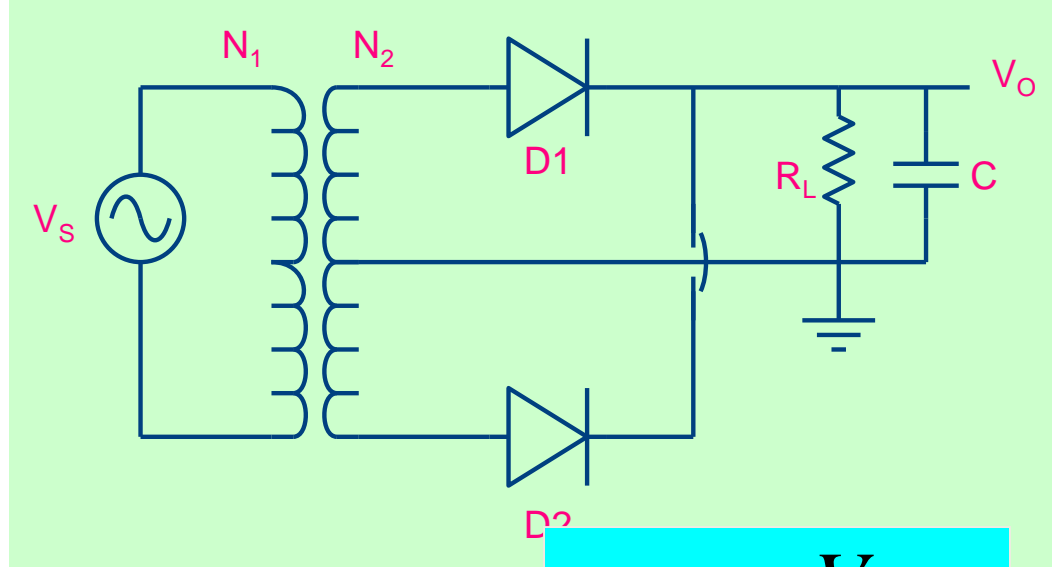
$$V_r \cong V_M \times \left\{ 1 - \left( 1 - \frac{t_1}{R_L C} \right) \right\} = \frac{V_M t_1}{R_L C}$$




$$V_r = \frac{V_M t_1}{R_L C} \cong \frac{V_M T}{2 R_L C}$$


$$V_r \cong \frac{V_M}{2 f R_L C}$$

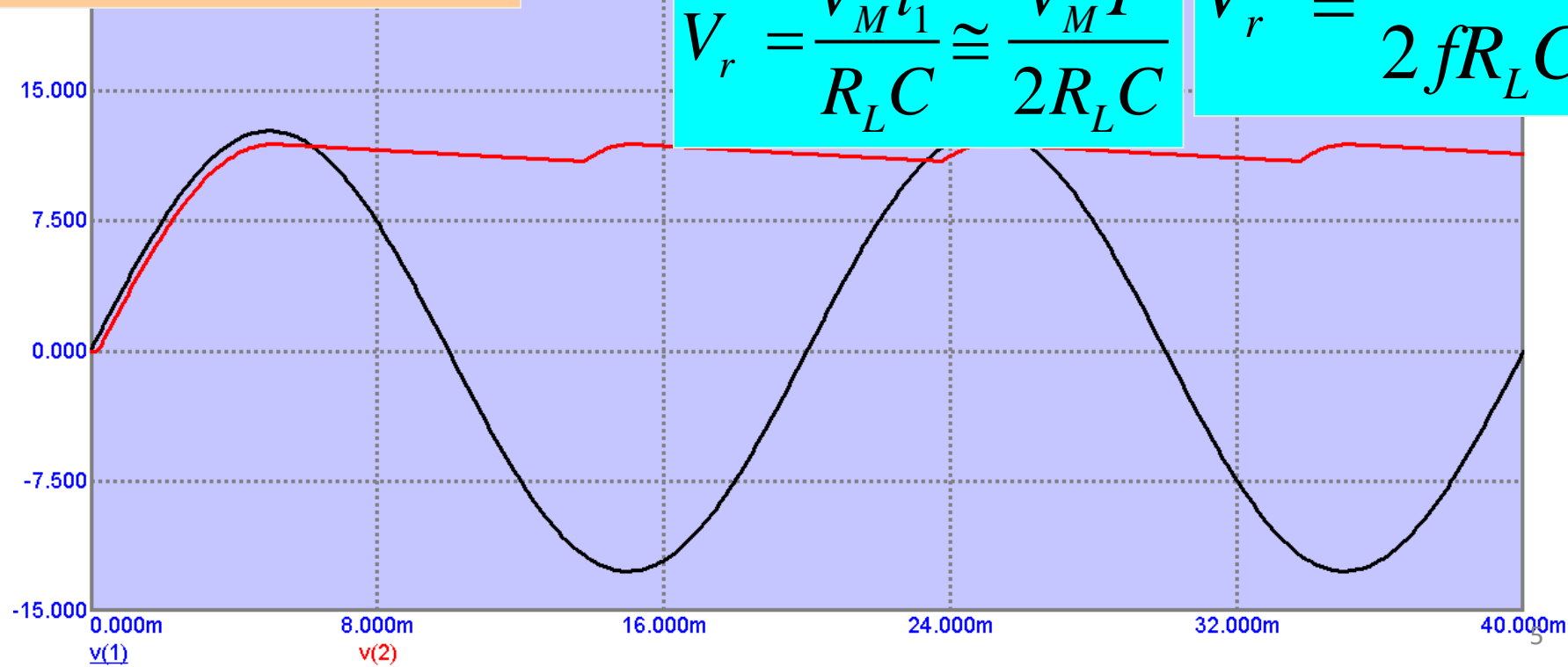

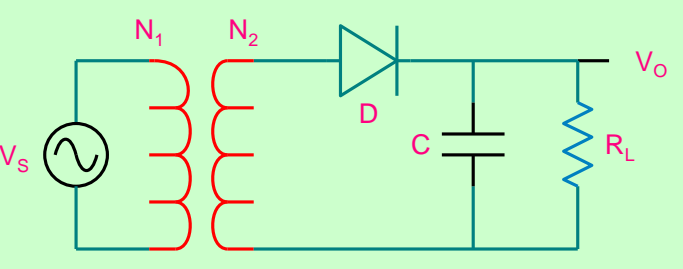
# Comparison of Full and Half Wave Rectifier




$$V_r \cong \frac{V_M}{fR_L C}$$

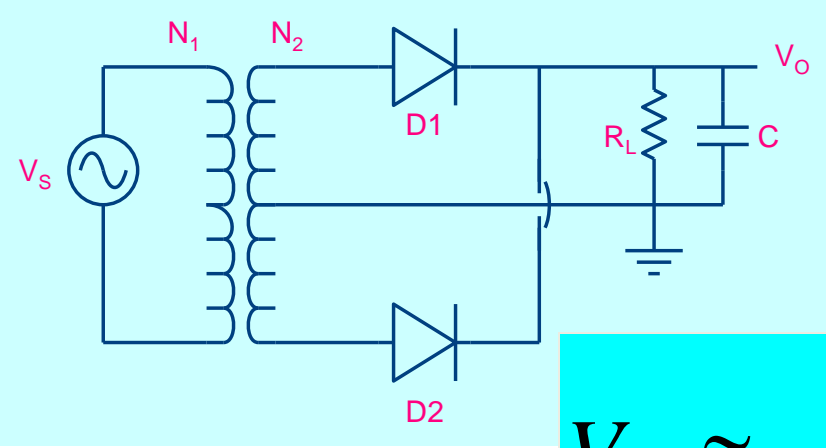

$$V_r \cong \frac{V_M}{2fR_L C}$$


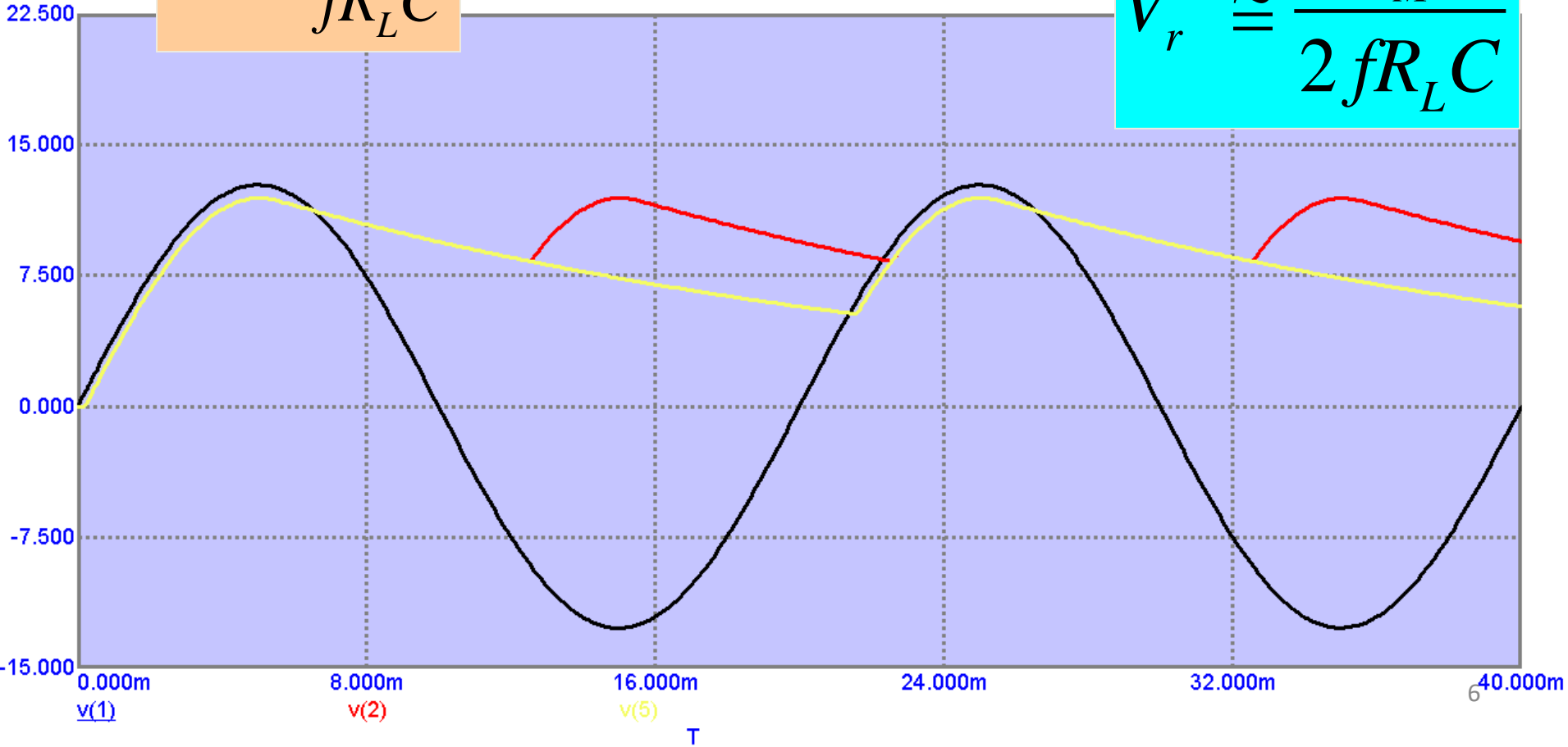


# Diode Currents in Full wave Rectifier

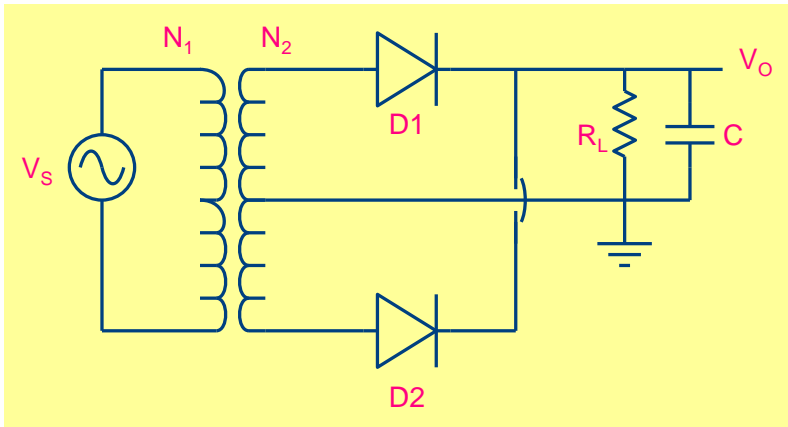


$$i_{D_{\max}} \cong \omega C \times \sqrt{2V_r V_M} + \frac{V_M}{R_L}$$
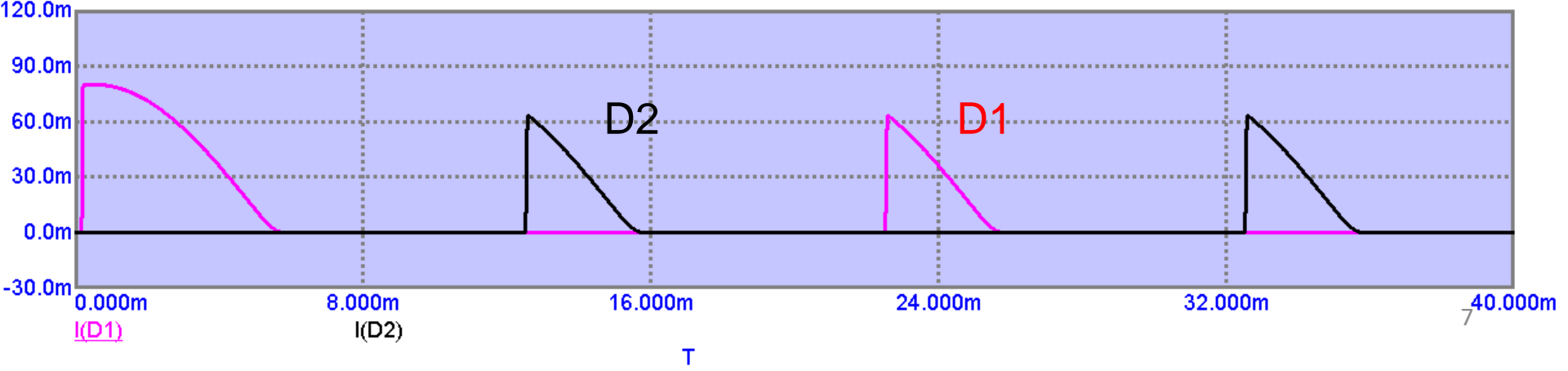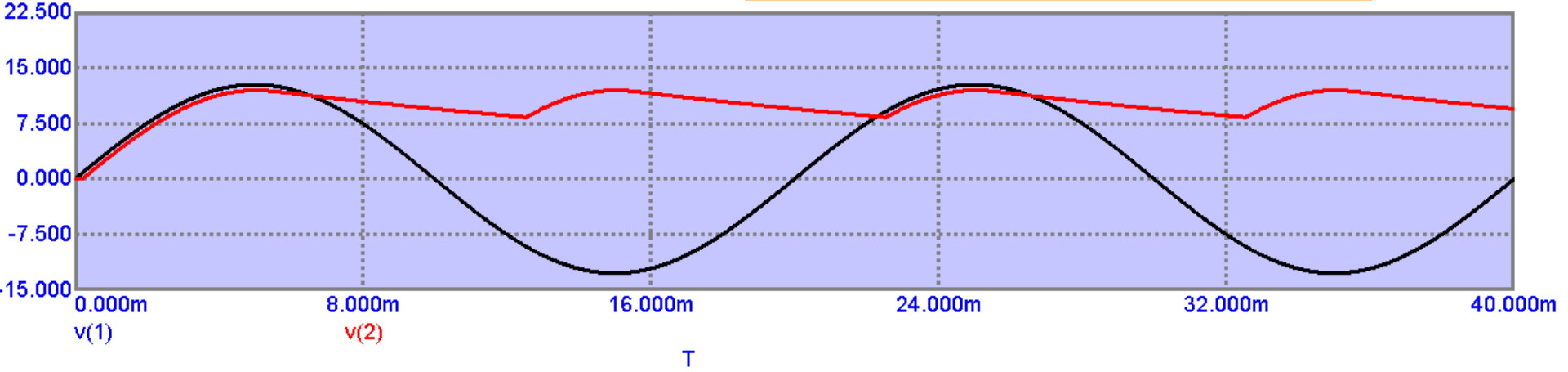
$$i_{D_{\max}} = \frac{V_M}{R_L} \left[ 1 + \pi \sqrt{\frac{2V_M}{V_r}} \right]$$



# Peak Inverse Voltage

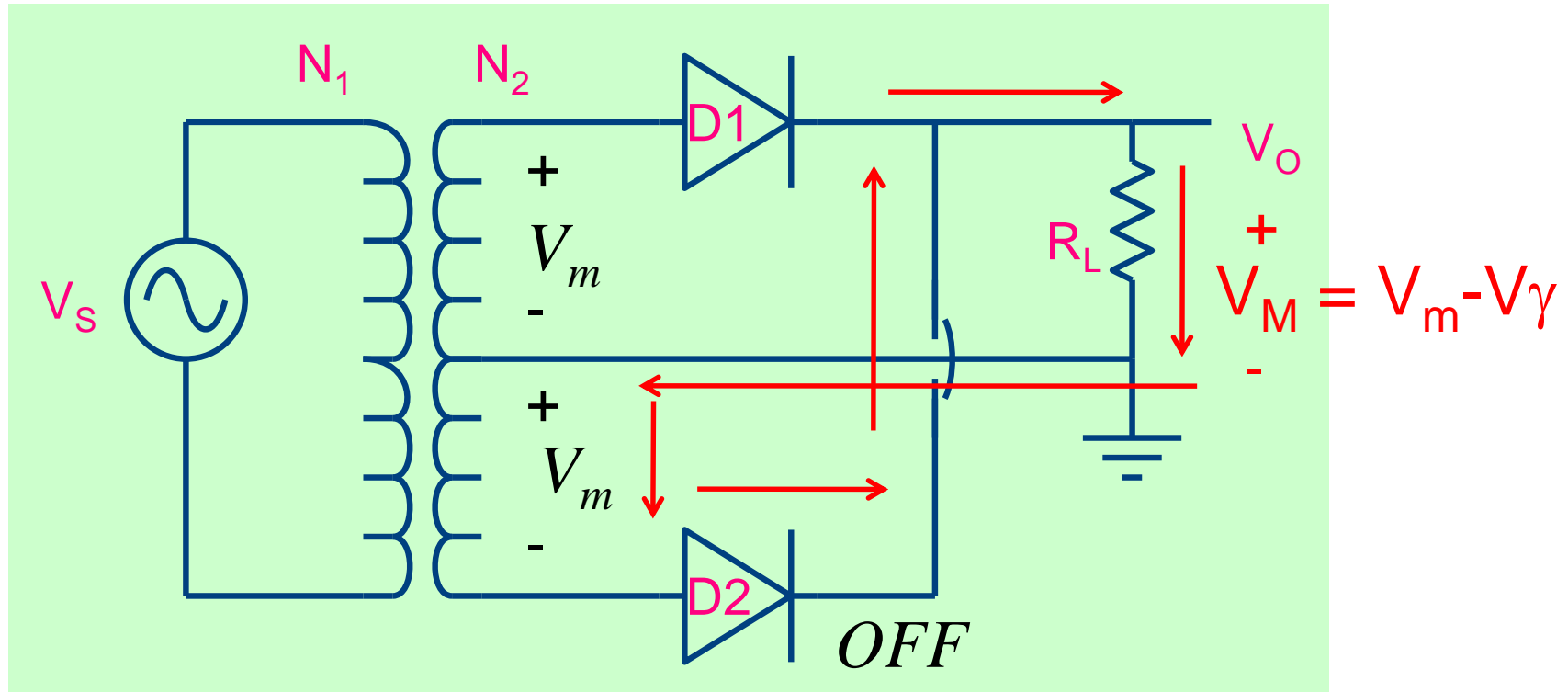


$$V_m + V_D + V_m - V_\gamma = 0$$


$$V_D = -(2V_m - V_\gamma)$$

$$PIV = 2V_m - V_\gamma$$








# Bridge Rectifier

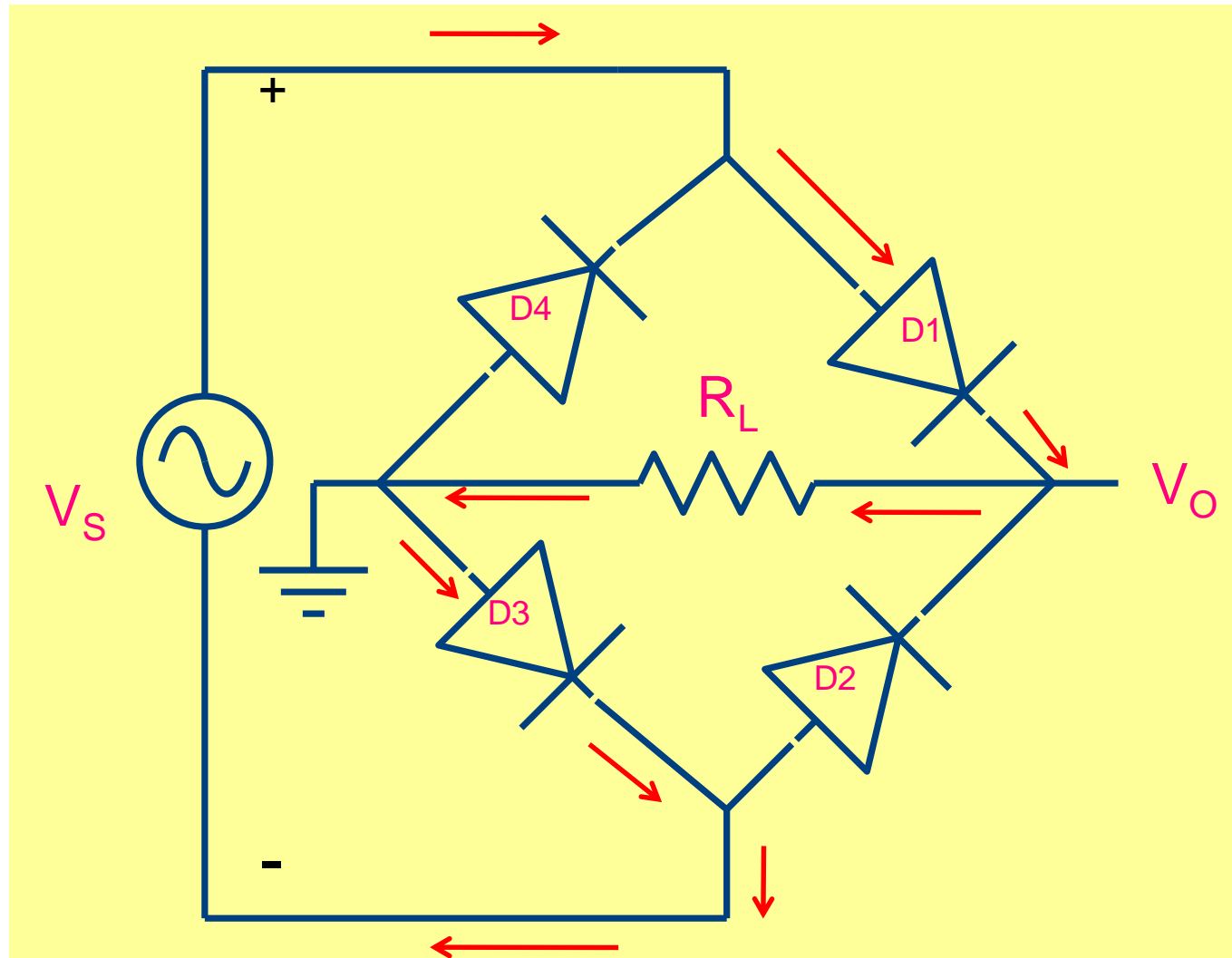

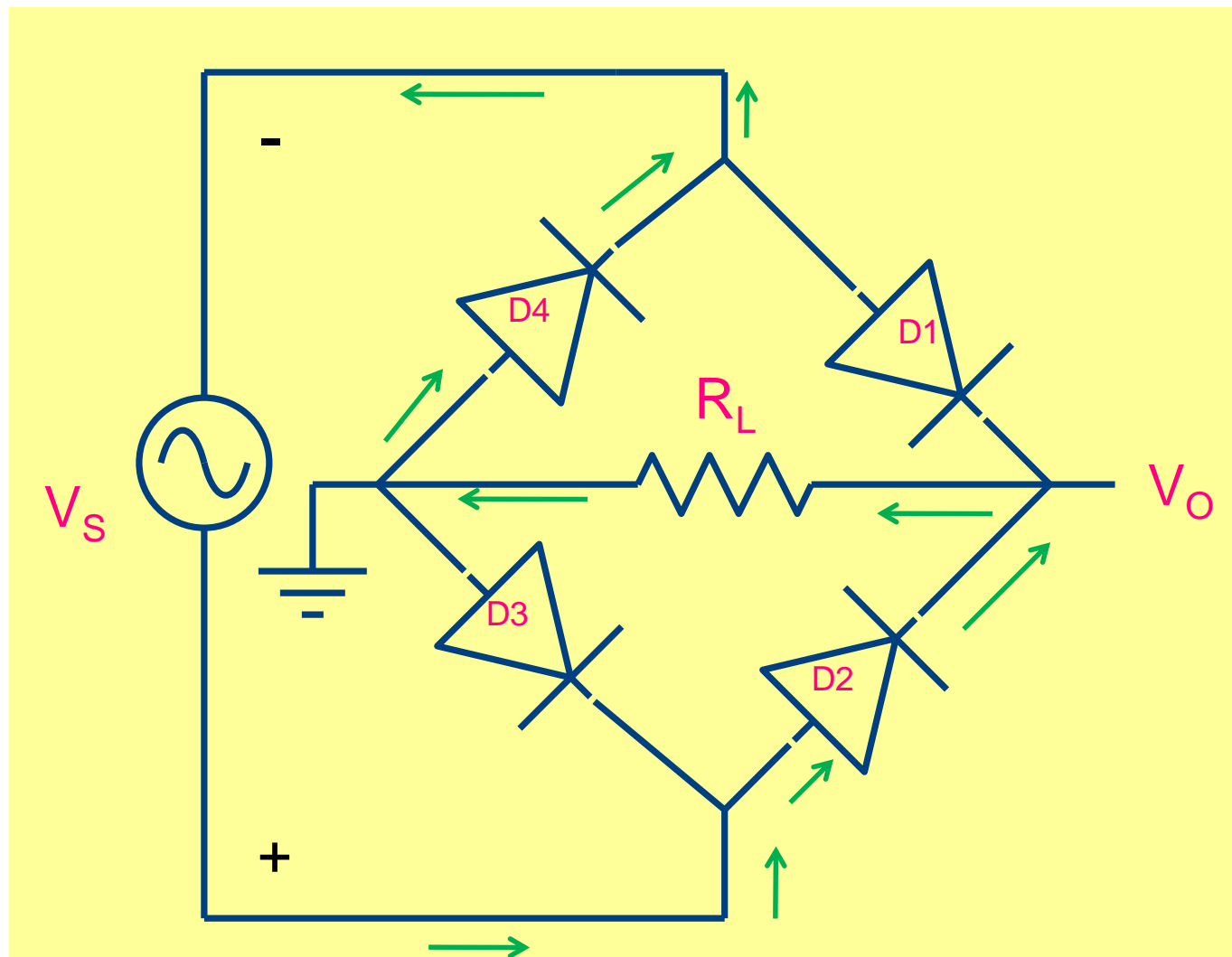
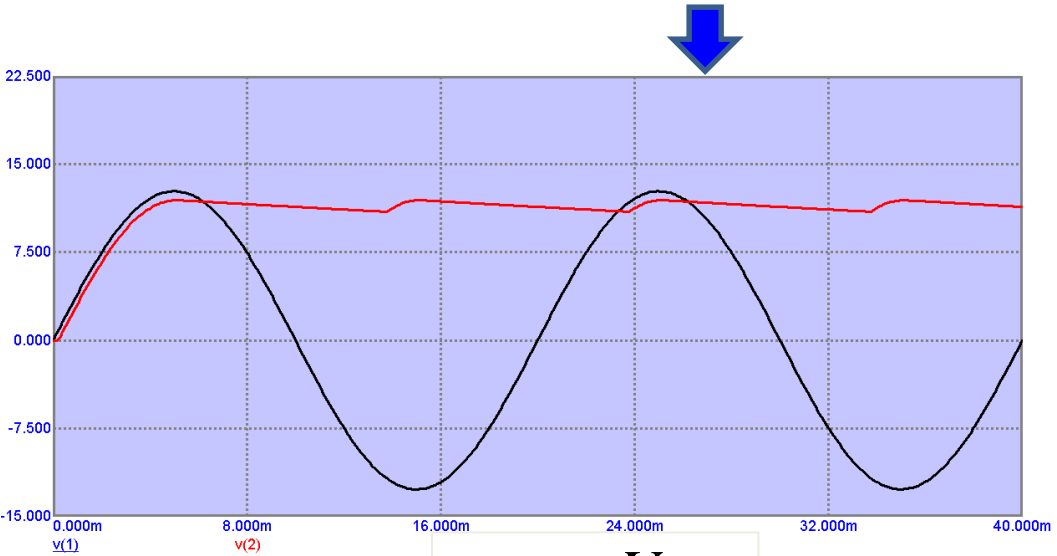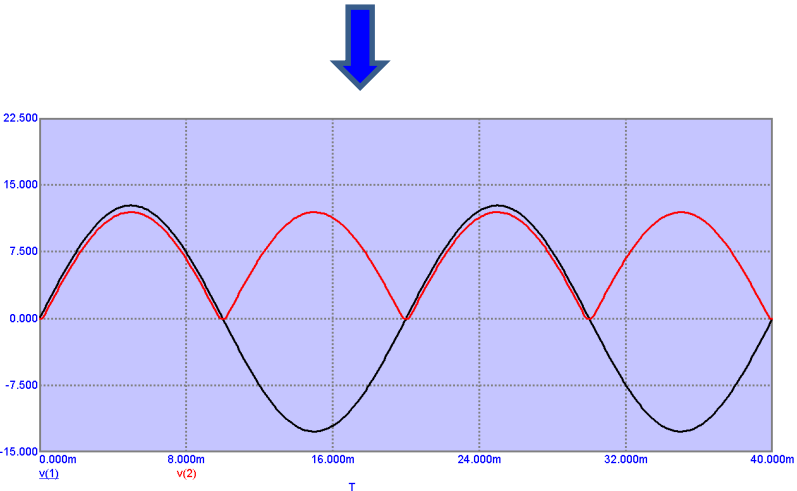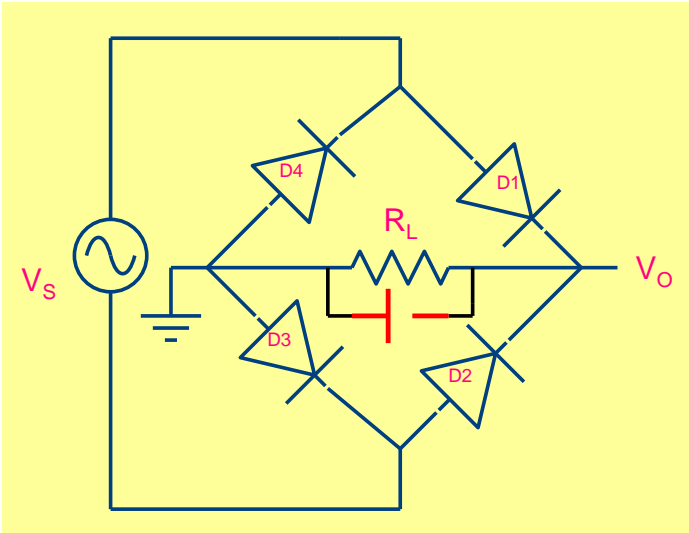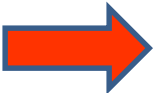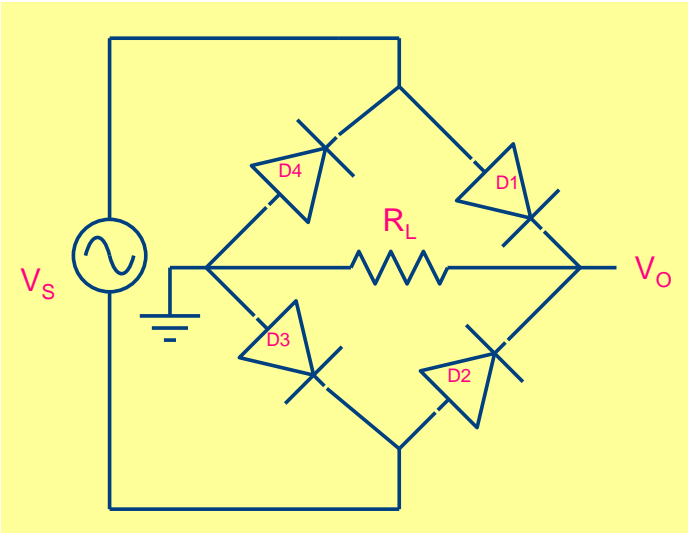
# Power supply using full wave Bridge Rectifier




Ripple is smaller in full wave rectifier based power supply



$$V_r \cong \frac{V_M}{2fR_L C}$$

# Peak Inverse Voltage

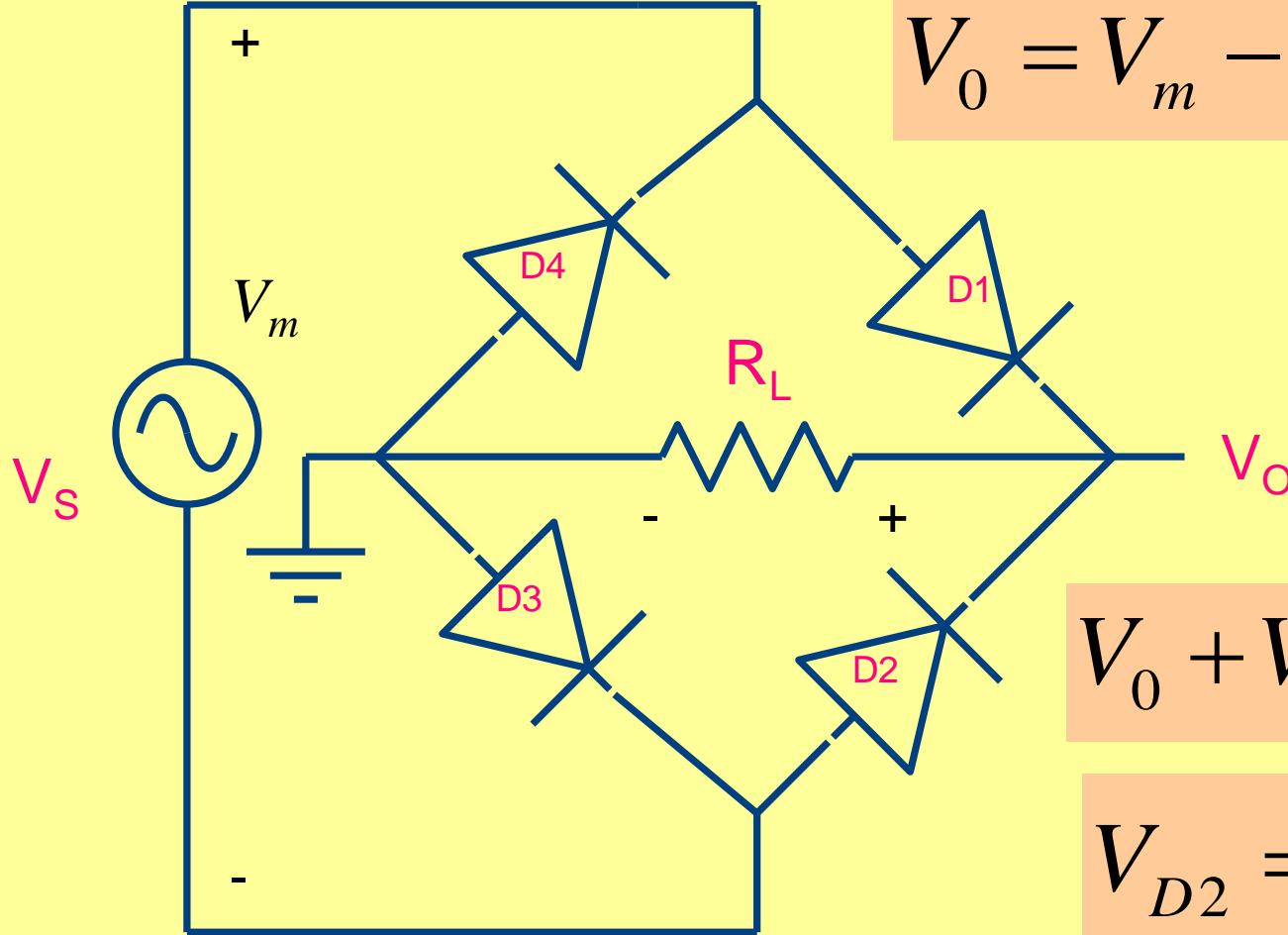

$$-V_m + V_{\gamma 1} + V_o + V_{\gamma 3} = 0$$


$$V_o = V_m - 2V_{\gamma}$$

$$V_o + V_{\gamma 3} + V_{D2} = 0$$

$$V_{D2} = -(V_o + V_{\gamma})$$


$$PIV = V_o + V_{\gamma} = V_m - V_{\gamma}$$

## Full wave Rectifier

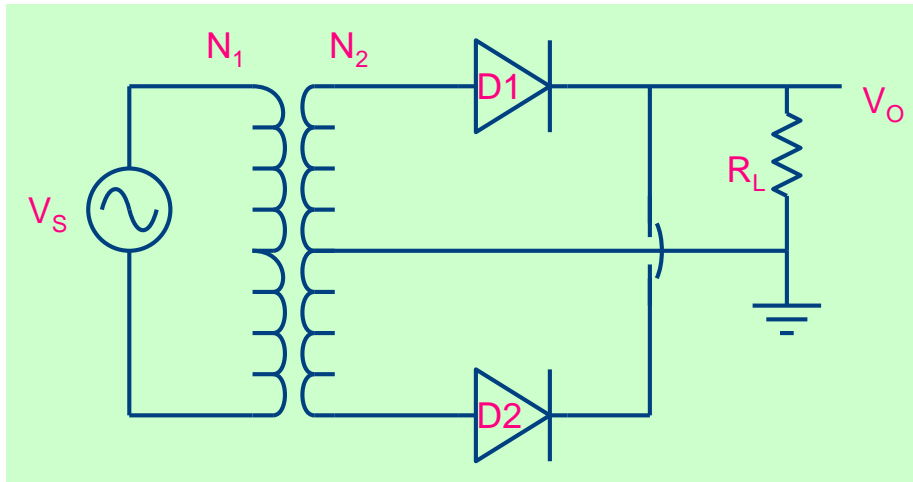

$$PIV = 2V_m - V_\gamma$$




## Bridge Rectifier

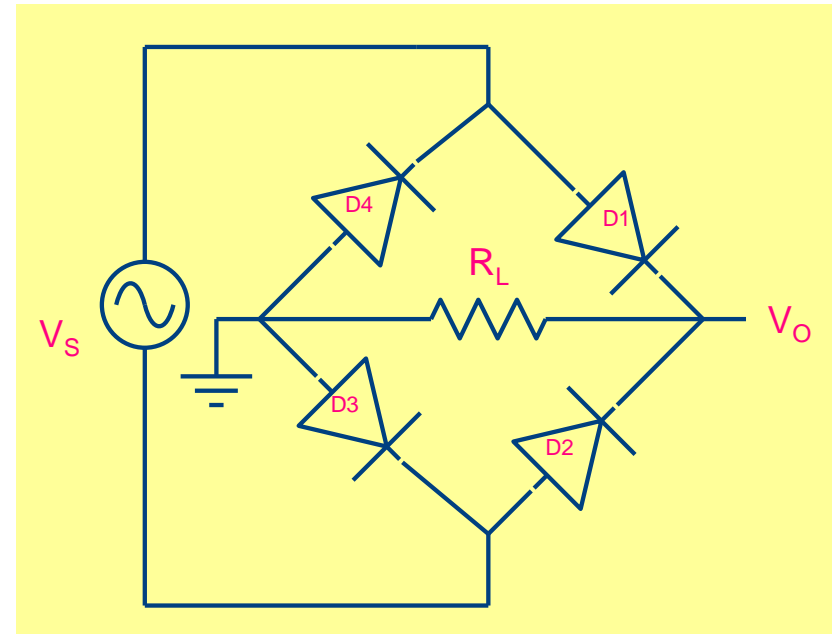



$$PIV = V_m - V_\gamma$$
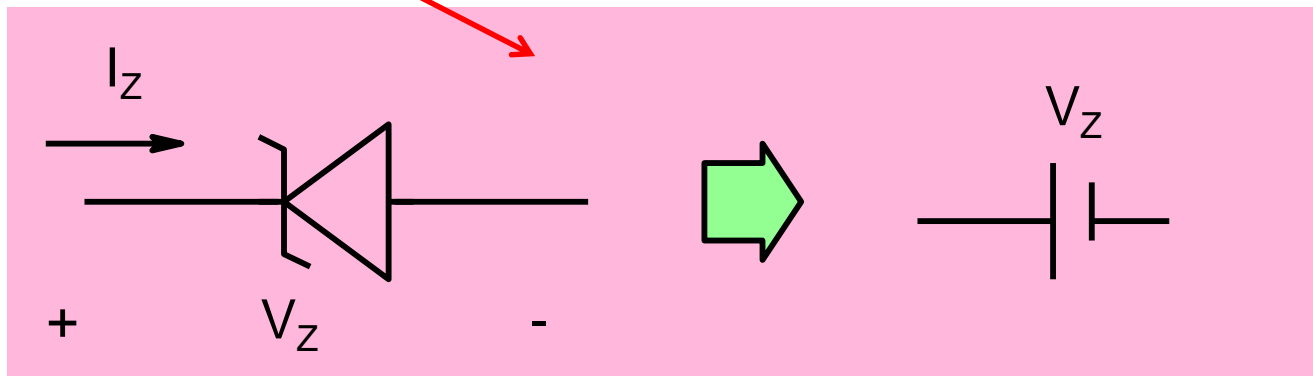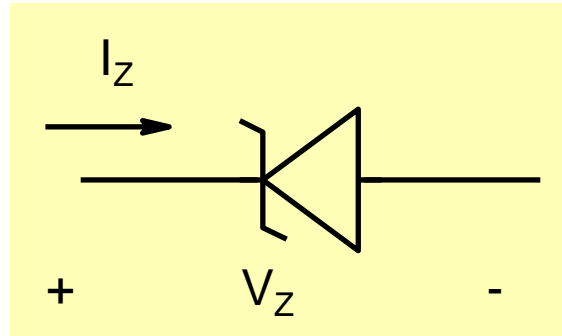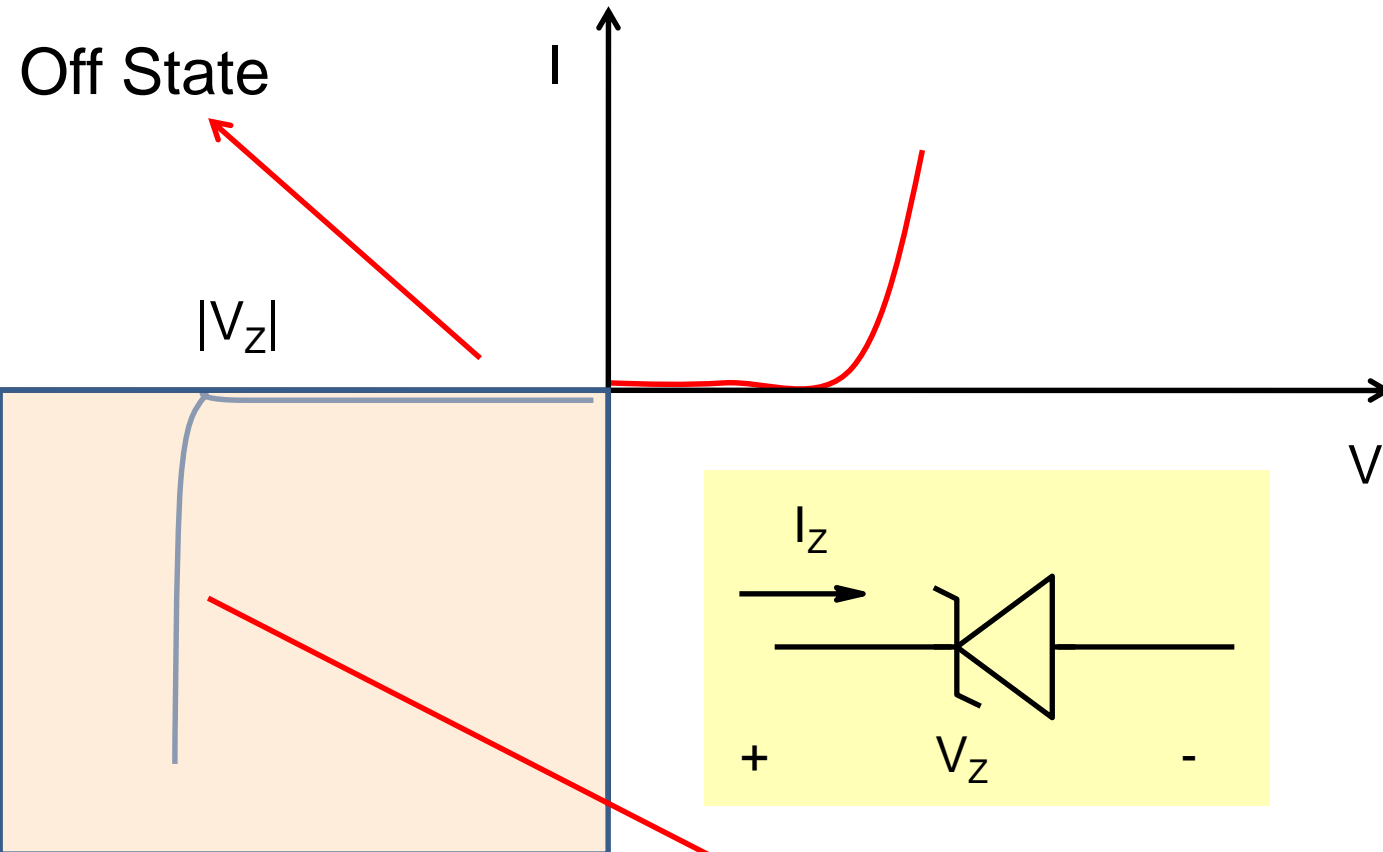
# Zener Diode

A diode specially designed to operate in reverse bias and in 'breakdown' region



# Model

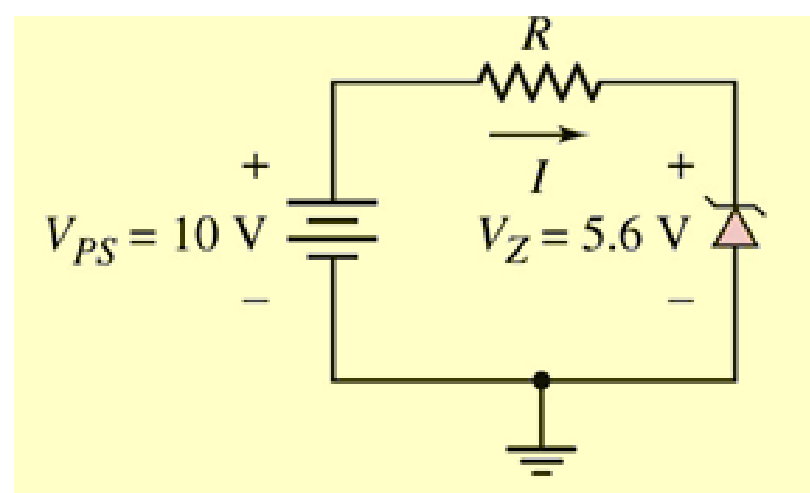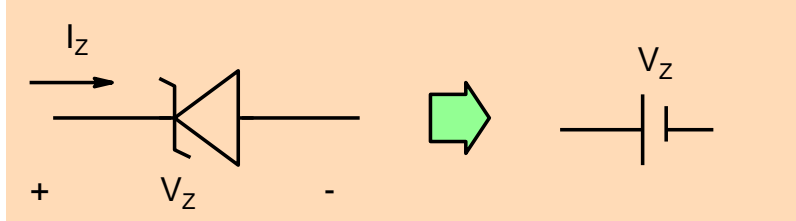

# Example


Given  $V_Z = 5.6\text{ V}$

$$r_Z = 0\Omega$$


Find a value for  $R$  such that the current through the diode is limited to  $3\text{ mA}$

$$I = \frac{V_{PS} - V_Z}{R}$$
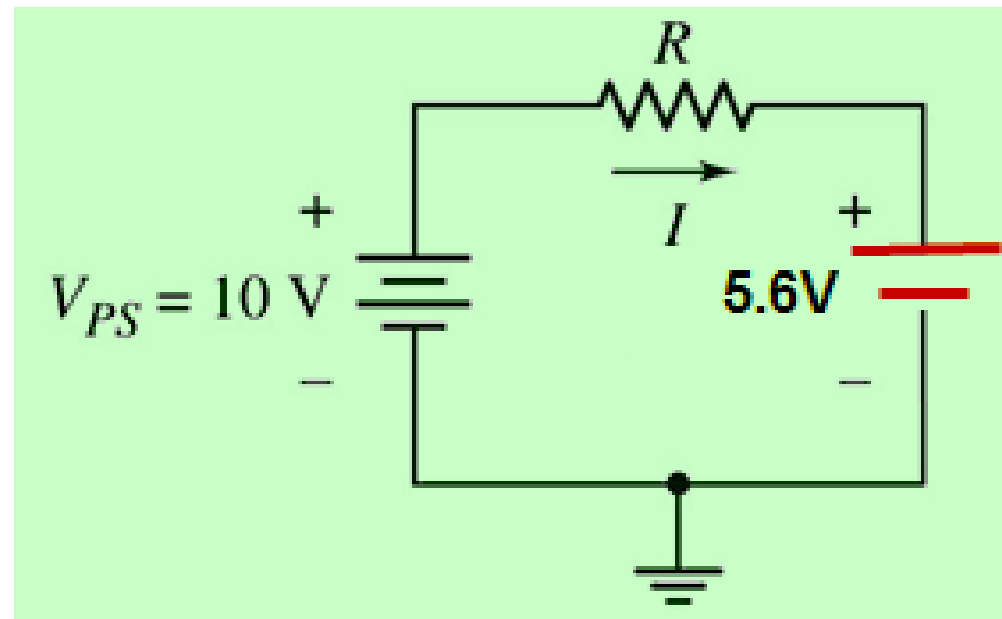
$$R = \frac{V_{PS} - V_Z}{I} = \frac{10\text{ V} - 5.6\text{ V}}{3\text{ mA}} = 1.47\text{ k}\Omega$$






# Zener diode: Important Characteristics




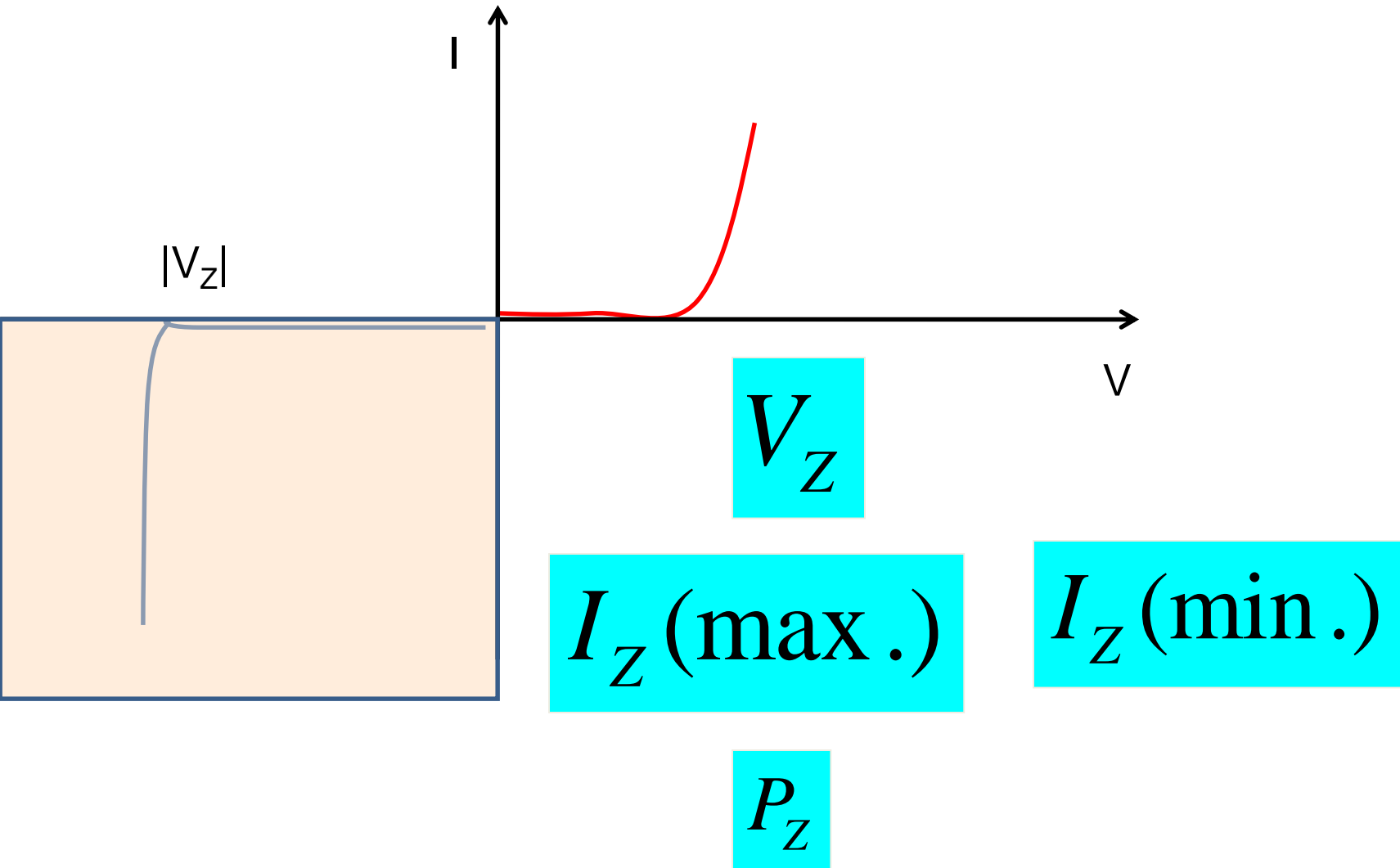






# Voltage Reference Circuit

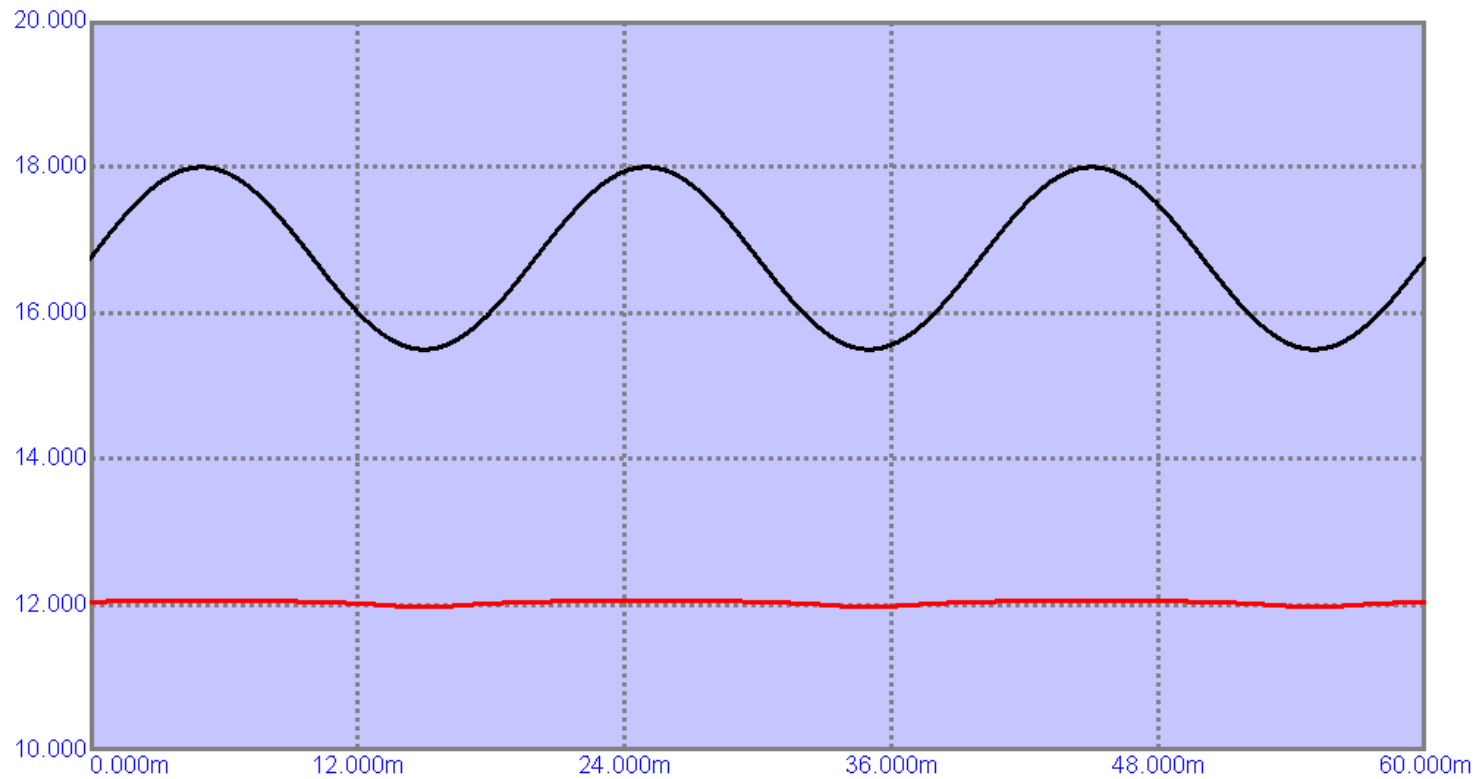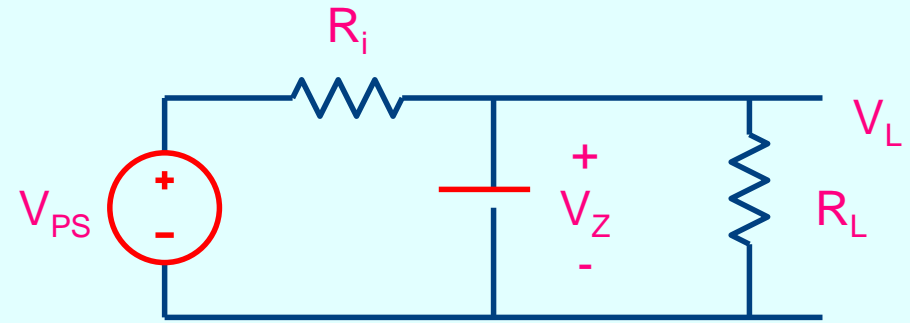
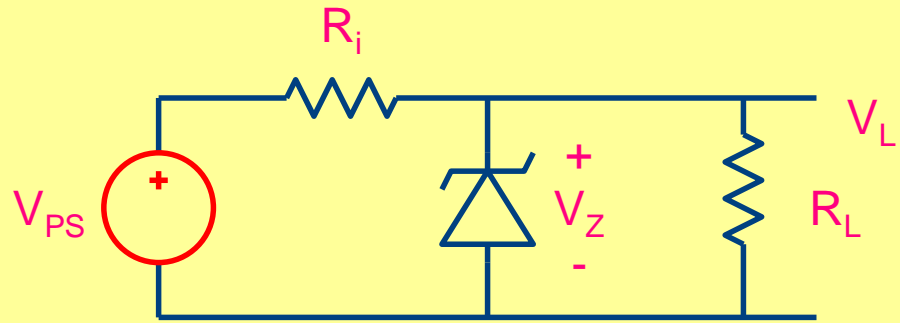


# Power supply with regulator

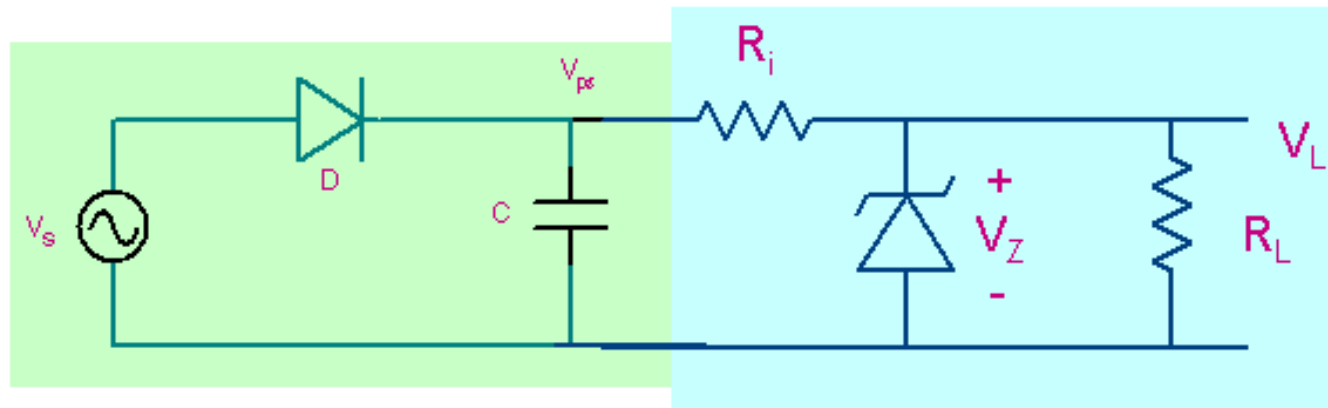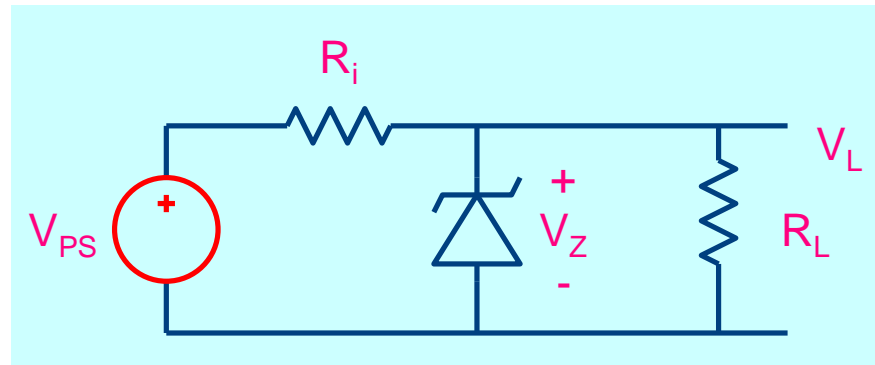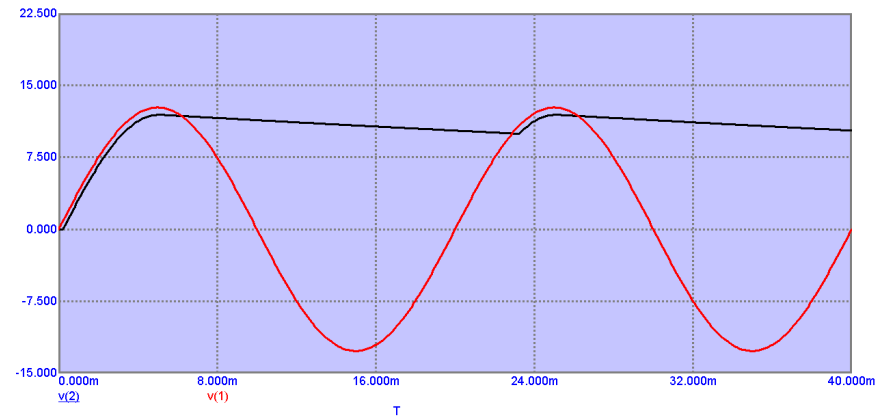
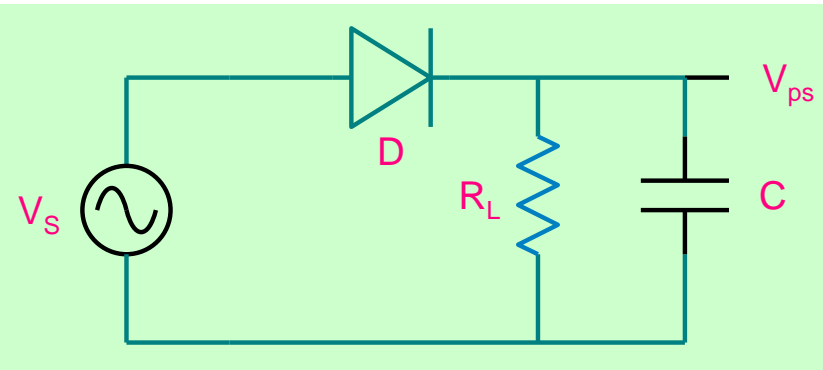


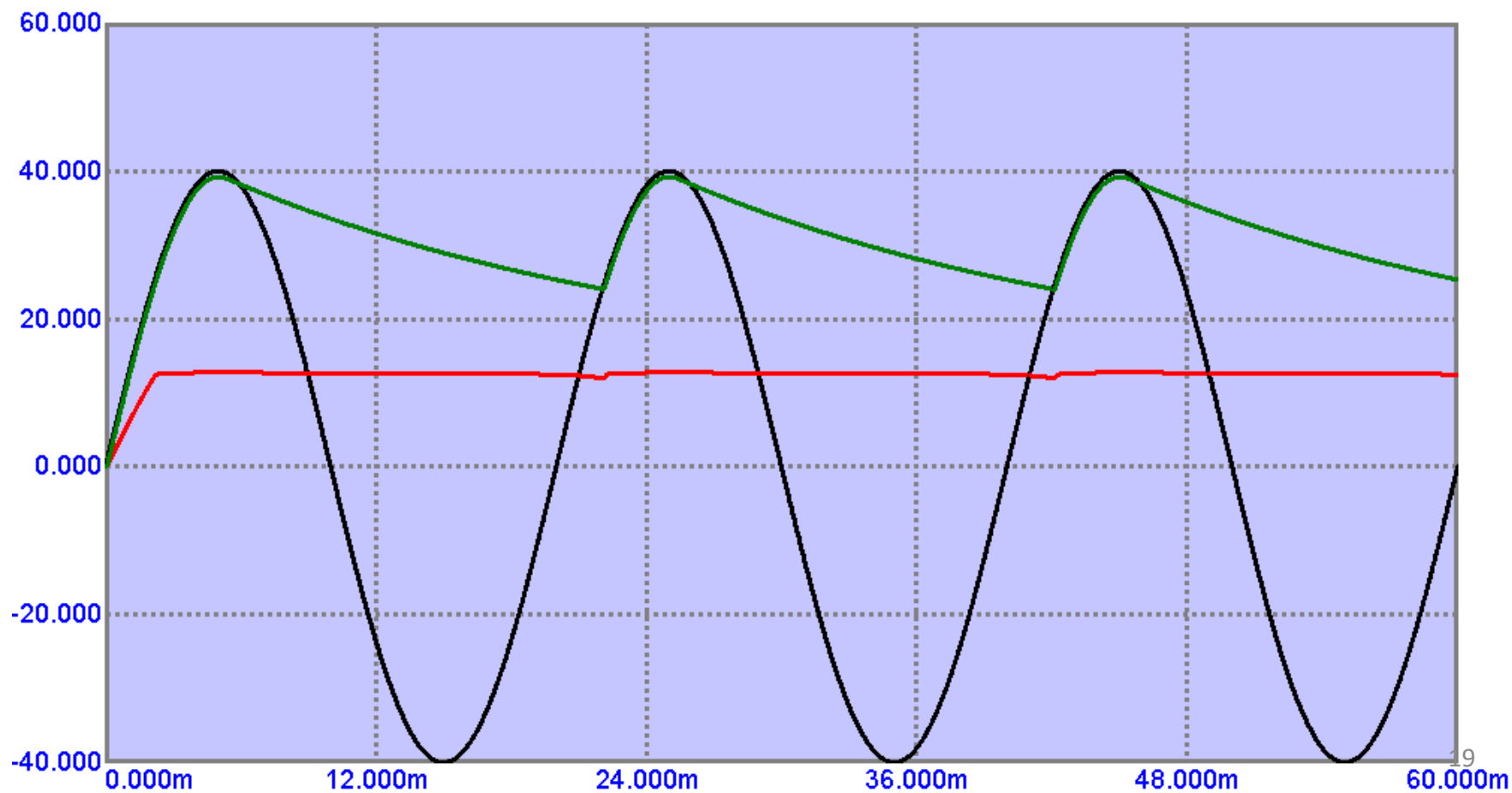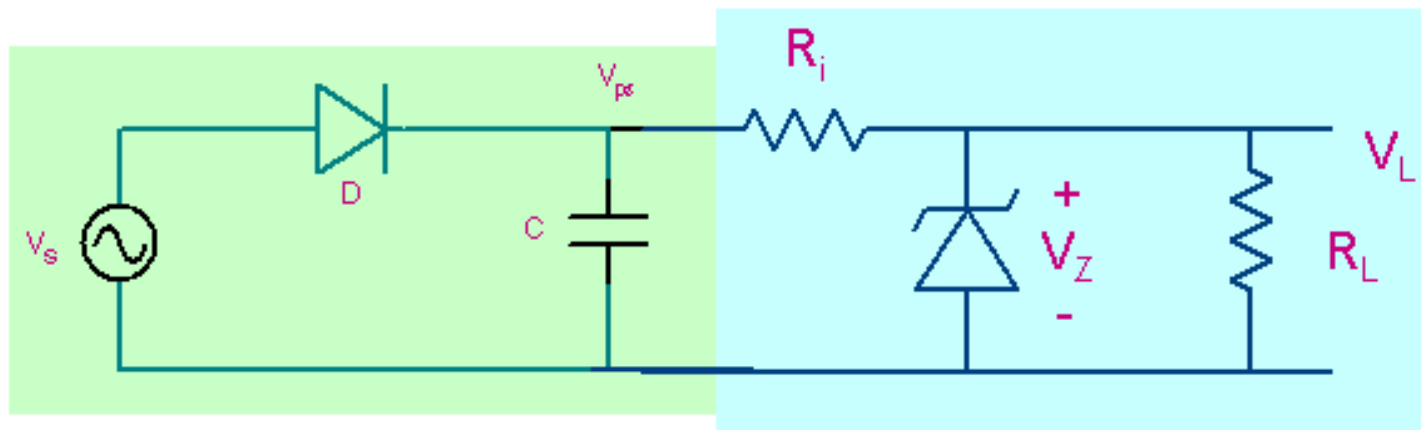

# Zener diode as Voltage Regulator

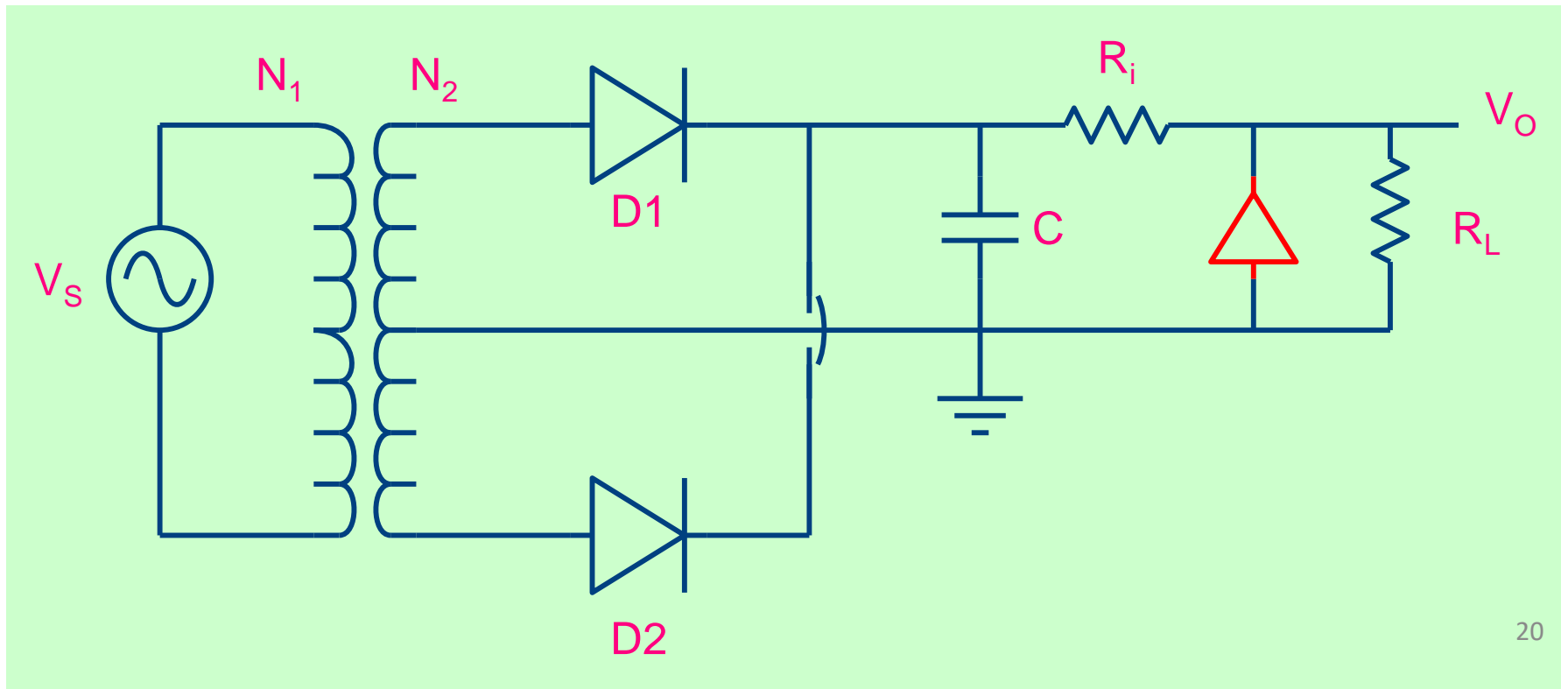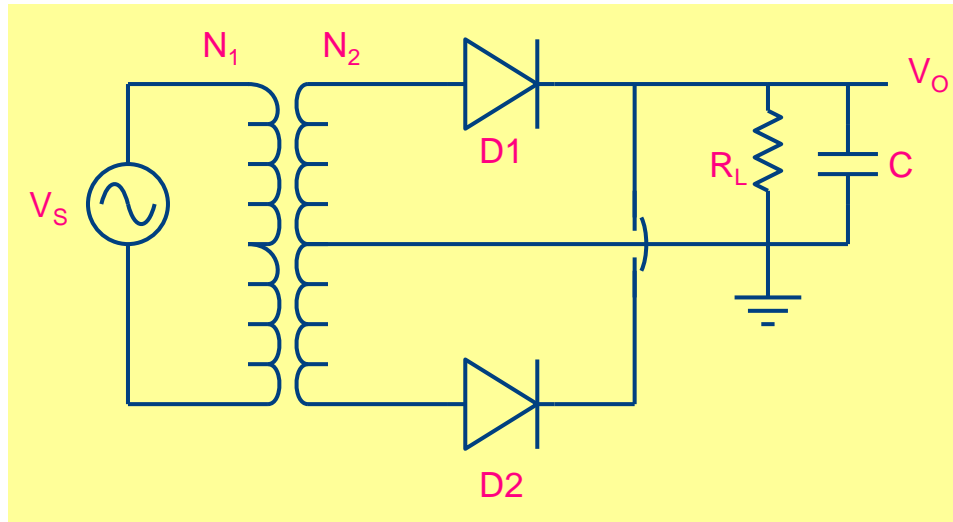


# Voltage Reference Circuit

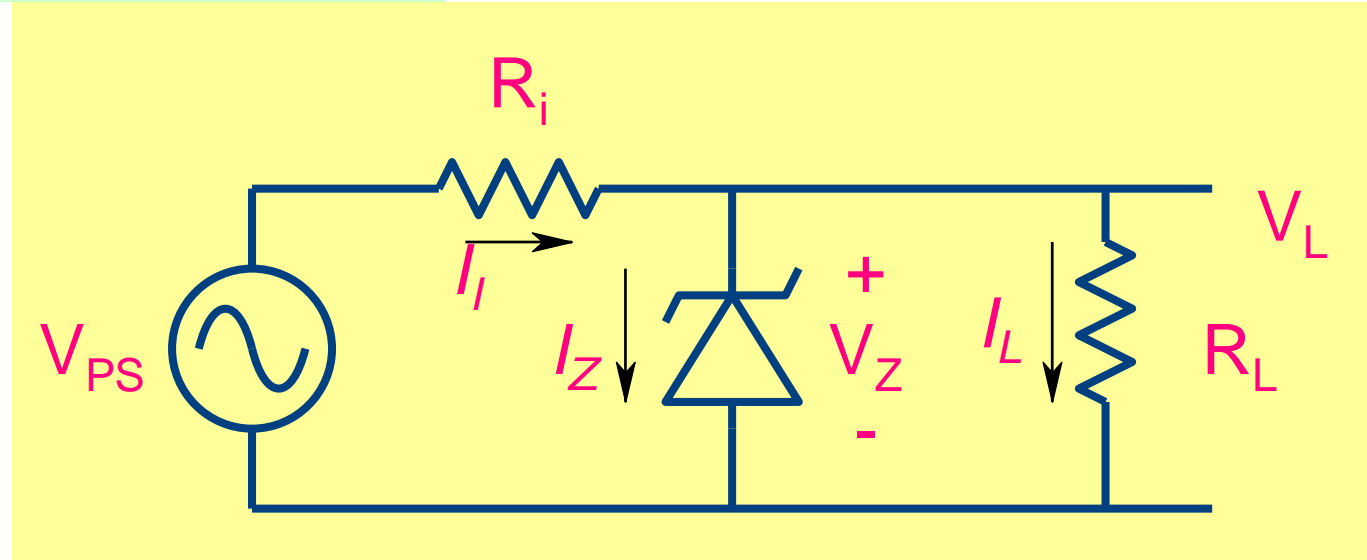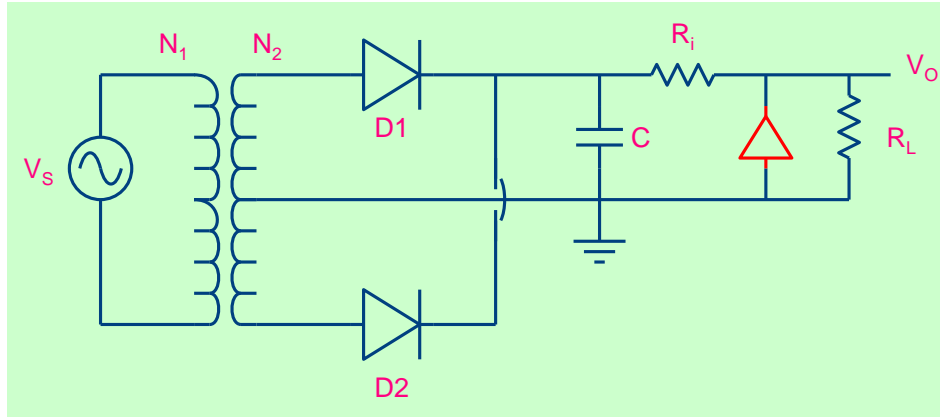

Design Problem: Determine  $R_i$  and zener diode specifications such that output voltage is +12 V and ratio of maximum to minimum zener current is 10. The input voltage may vary between 18 to 15.5V.  $R_L = 108 \Omega$ .

# Design Equations

$$P_{Z \max} = V_Z I_{Z \max}$$

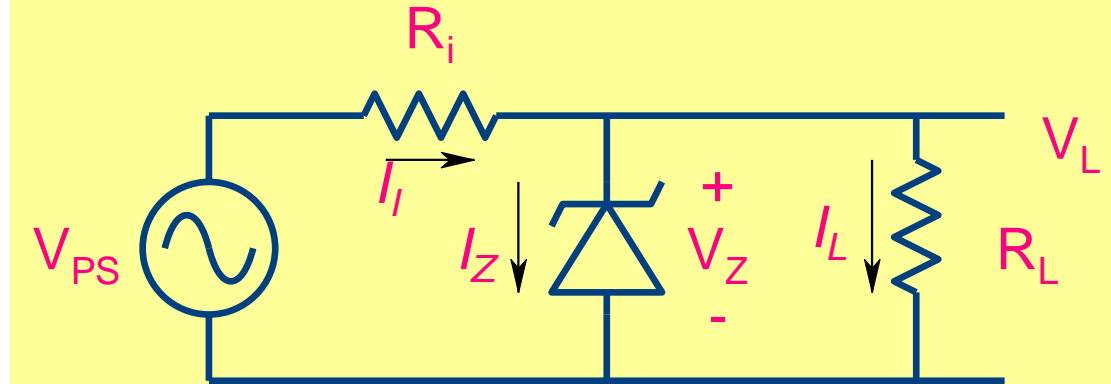

$$I_i = \frac{V_{PS} - V_Z}{R_i} = I_Z + I_L$$

$$I_Z = \frac{V_{PS} - V_Z}{R_i} - I_L$$

$$I_{Z \max} = \frac{V_{PS \max} - V_Z}{R_i} - I_L$$

$$I_{Z \min} = \frac{V_{PS \min} - V_Z}{R_i} - I_L$$

$$\frac{I_{Z \max}}{I_{Z \min}} \cong 10$$

$$R_i = \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{0.9I_L}$$


**Design Problem contd.:** Determine  $R_i$  and zener diode specifications such that output voltage is +12V and ratio of maximum to minimum zener current is 10. The input voltage may vary between 18 to 15.5V.  $R_L = 108 \Omega$ .

$$I_L = \frac{V_L}{R_L} = \frac{12}{108} = \frac{1}{9}$$


$$\begin{aligned} R_i &= \frac{V_{PS \min} - 0.1V_{PS \max} - 0.9V_Z}{0.9I_L} \\ &= \frac{15.5 - 0.1 \cdot 18 - 0.9 \cdot 12}{0.9(1/9)} \\ &= \frac{15.5 - 1.8 - 10.8}{0.1} = \frac{2.9}{0.1} = 29 \Omega \end{aligned}$$

$$\begin{aligned} I_{Z \max} &= \frac{V_{PS \max} - V_Z}{R_i} - I_L \\ &= \frac{18 - 12}{29} - \frac{1}{9} = \frac{6}{29} - \frac{1}{9} = 0.096 \text{ A} \end{aligned}$$
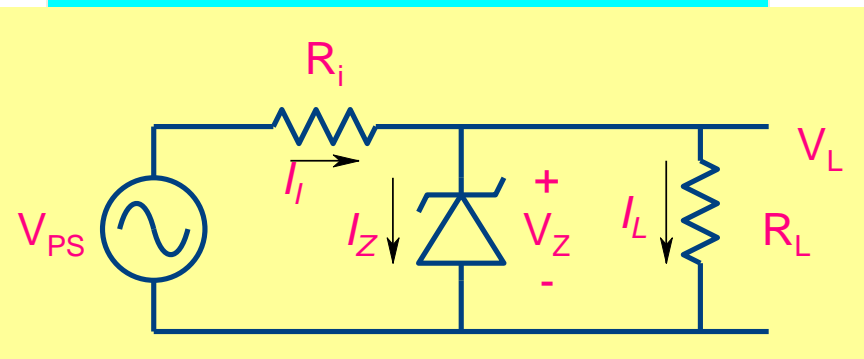
$$\begin{aligned} I_{Z \min} &= \frac{V_{PS \min} - V_Z}{R_i} - I_L \\ &= \frac{15.5 - 12}{29} - \frac{1}{9} = \frac{3.5}{29} - \frac{1}{9} \\ &= 0.0096 \text{ A} \end{aligned}$$


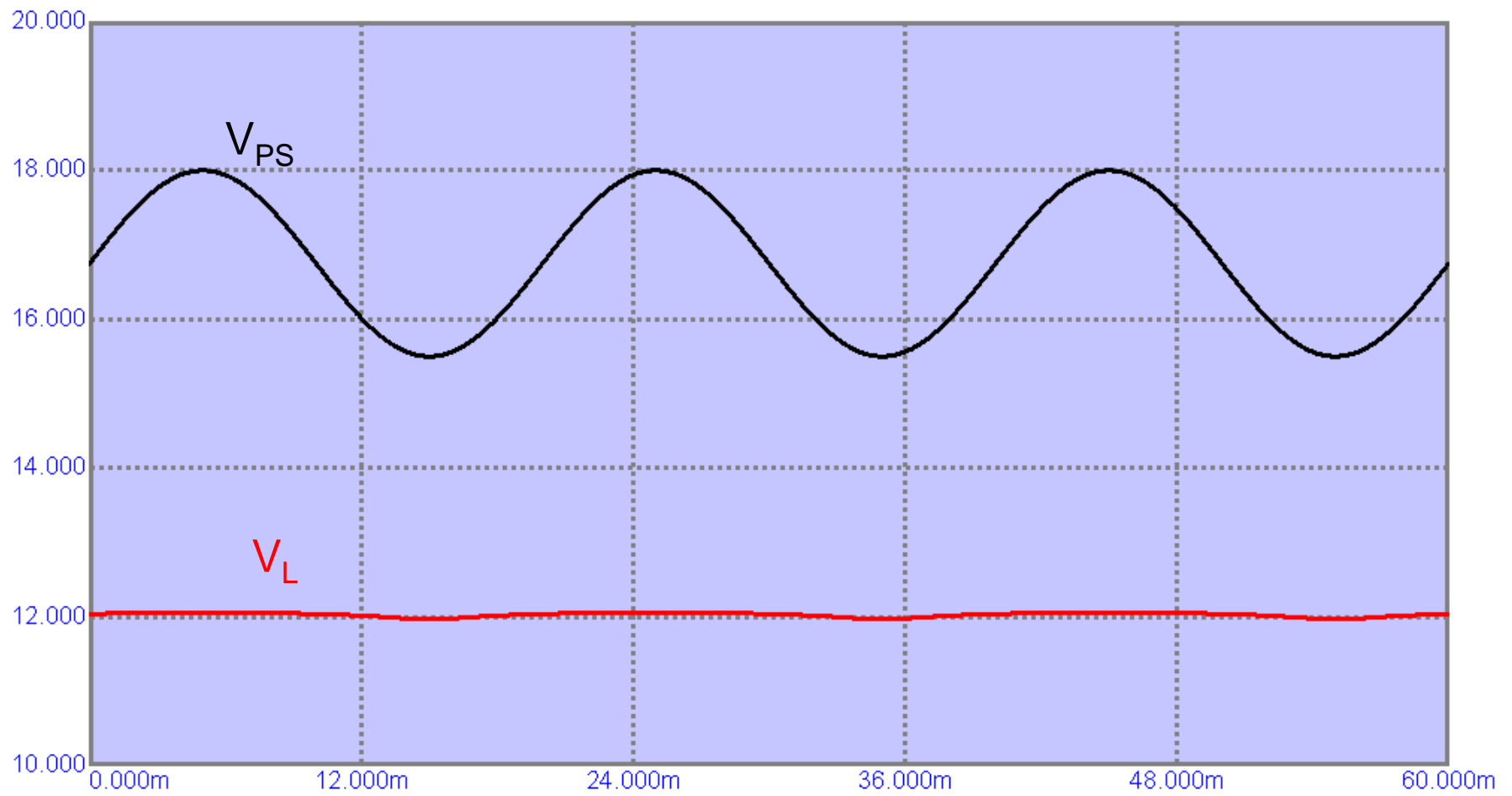
$$\begin{aligned} P_{Z \max} &= V_Z I_{Z \max} \\ &= 12 \cdot 0.096 = 1.152 \text{ W} \end{aligned}$$





# Amplifiers

# Objective

1. Learn ideal Transistor characteristics required for Voltage Amplification
2. Learn to build amplifiers using elements which have non-ideal characteristics.

1. Class tomorrow 10/09/2022 (Working Wednesday)

2. Tutorial Attendance