

ESc201 : Introduction to Electronics

Digital Circuits

Amit Verma
Dept. of Electrical Engineering
IIT Kanpur

Comparator

$$A = A_3A_2A_1A_0$$

$$x_i = A_i.B_i + \overline{A_i}.\overline{B_i} \quad \text{for } i = 0,1,2,3$$


$$B = B_3B_2B_1B_0$$

where $x_i = 1$ only if the pair of bits in position i are equal (i.e., if both are 1 or both are 0).

$$(A = B) = x_3x_2x_1x_0 \quad \text{all } x_i \text{ variable must be equal to 1}$$

$$(A > B) = A_3\overline{B_3} + x_3A_2\overline{B_2} + x_3x_2A_1\overline{B_1} + x_3x_2x_1A_0\overline{B_0}$$
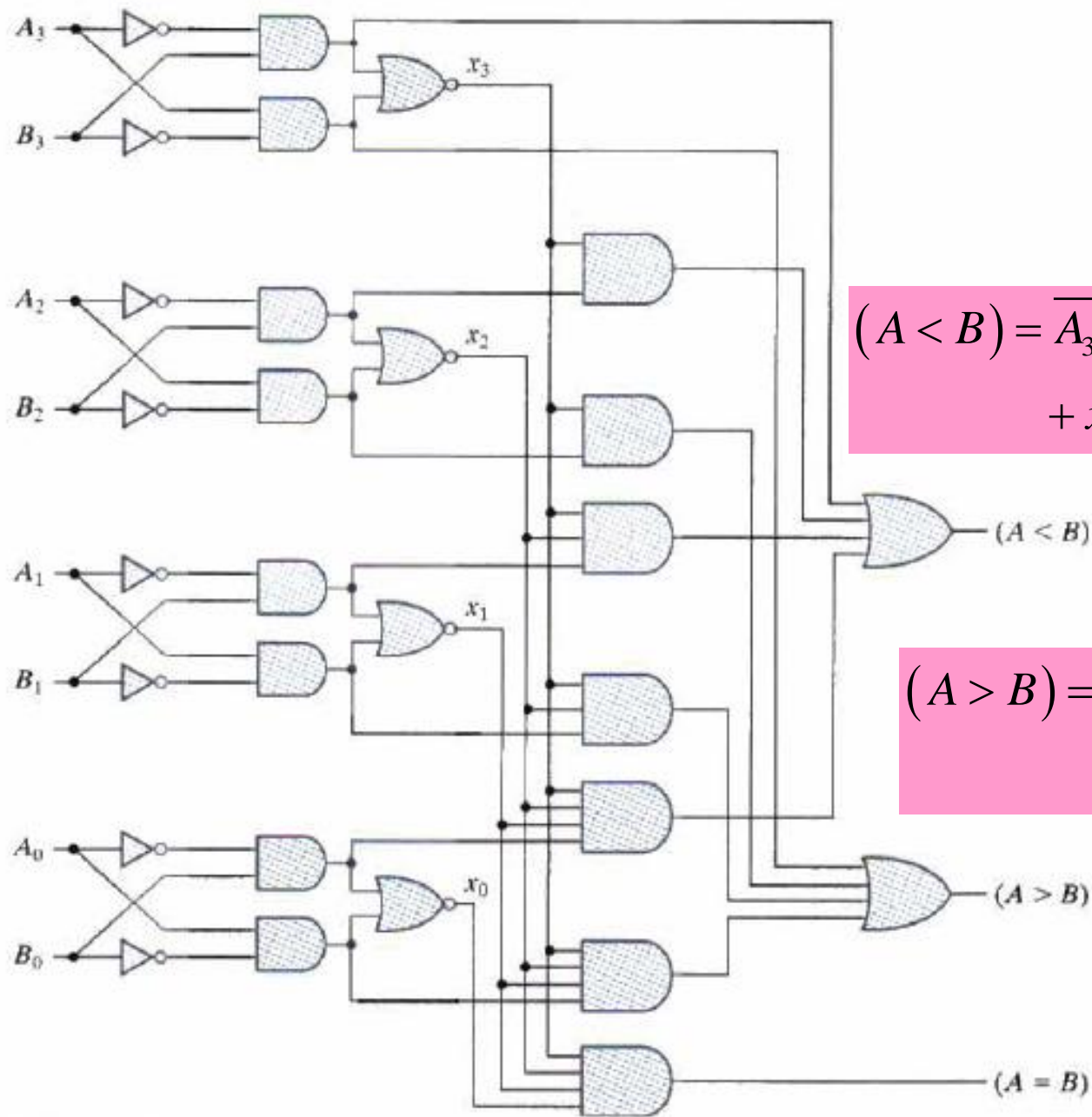
$$(A < B) = \overline{A_3}B_3 + x_3\overline{A_2}B_2 + x_3x_2\overline{A_1}B_1 + x_3x_2x_1\overline{A_0}B_0$$




$$(A < B) = \overline{A_3}B_3 + x_3\overline{A_2}B_2 \\ + x_3x_2\overline{A_1}B_1 + x_3x_2x_1\overline{A_0}B_0$$


$$(A > B) = A_3\overline{B_3} + x_3A_2\overline{B_2} \\ + x_3x_2A_1\overline{B_1} + x_3x_2x_1A_0\overline{B_0}$$

$$(A = B) = x_3x_2x_1x_0$$

Adder

 



a	b	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

$S = \bar{a}.b + a.\bar{b}; C = a.b$

1
1 1 1
1 1 0

1 1 0 1

  

a	b	C _{in}	S	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in};$$
$$C_{out} = \bar{a}.b.c_{in} + a.\bar{b}.c_{in} + a.b.\bar{c}_{in} + a.b.c_{in}$$

$$S = \bar{a}.\bar{b}.c_{in} + \bar{a}.b.\bar{c}_{in} + a.\bar{b}.\bar{c}_{in} + a.b.c_{in}$$

$$S = C_{in} \oplus (a \oplus b)$$


$$C_{out} = \bar{a}.b.C_{in} + a.\bar{b}.C_{in} + a.b.\bar{C}_{in} + a.b.C_{in}$$
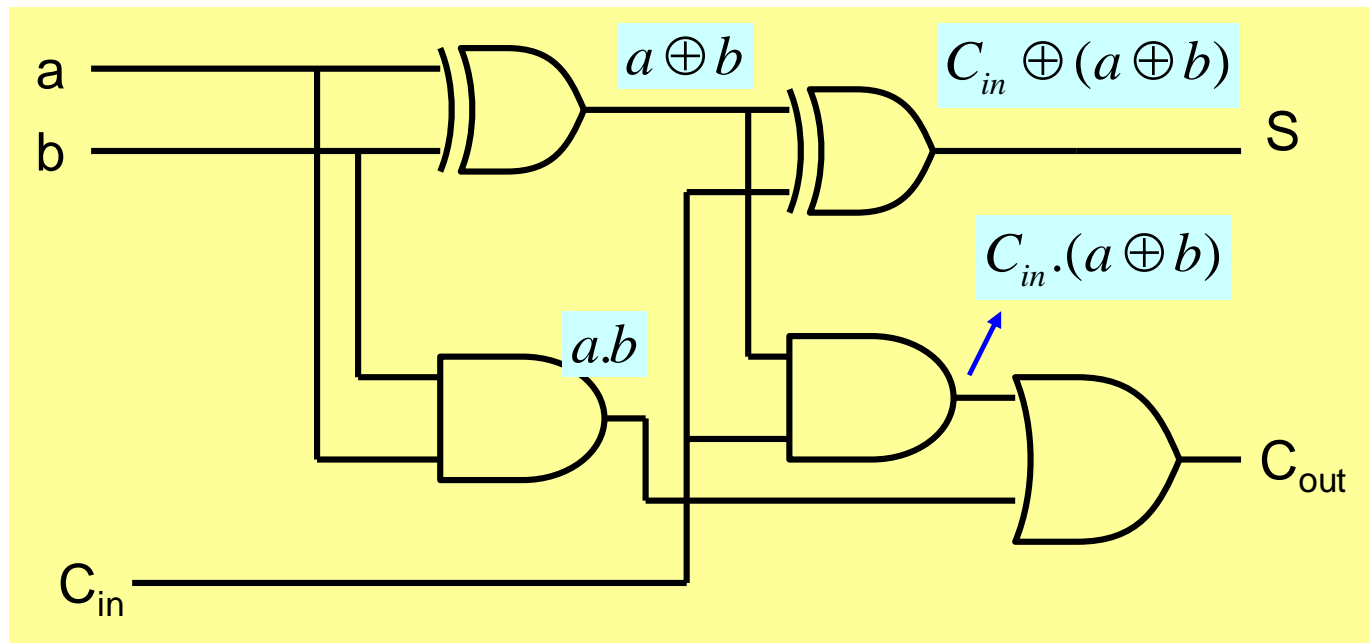
$$C_{out} = C_{in}(a.\bar{b} + \bar{a}.b) + a.b = C_{in}.(a \oplus b) + a.b$$




a	b	C_{in}	S	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

4-bit Adder

 

$A_3A_2A_1A_0$	$B_3B_2B_1B_0$	$S_3S_2S_1S_0$	C_{out}
0000	0000	0000	0
0000	0001	0001	0
0001	0000	0001	0
⋮	⋮	⋮	⋮
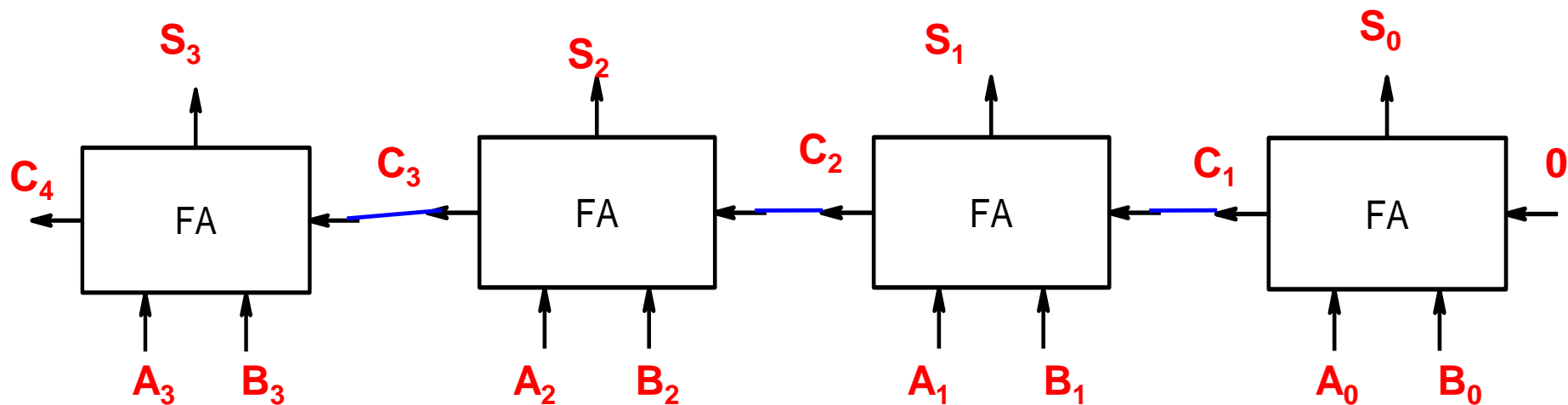
$$\begin{array}{r} C_3C_2C_1 \\ A_3A_2A_1A_0 \\ B_3B_2B_1B_0 \\ \hline C_4S_3S_2S_1S_0 \end{array}$$




FA = Full Adder

Subtraction

$$A - B = A + 2\text{'s complement of } B$$




$$A - B = A + \overline{B} + 1$$
 
$$A - B = A + 1\text{'s complement of } B + 1$$



$$B_0 \oplus 1 = B_0 \cdot \bar{1} + \overline{B_0} \cdot 1 = \overline{B_0}$$

Adder/Subtractor

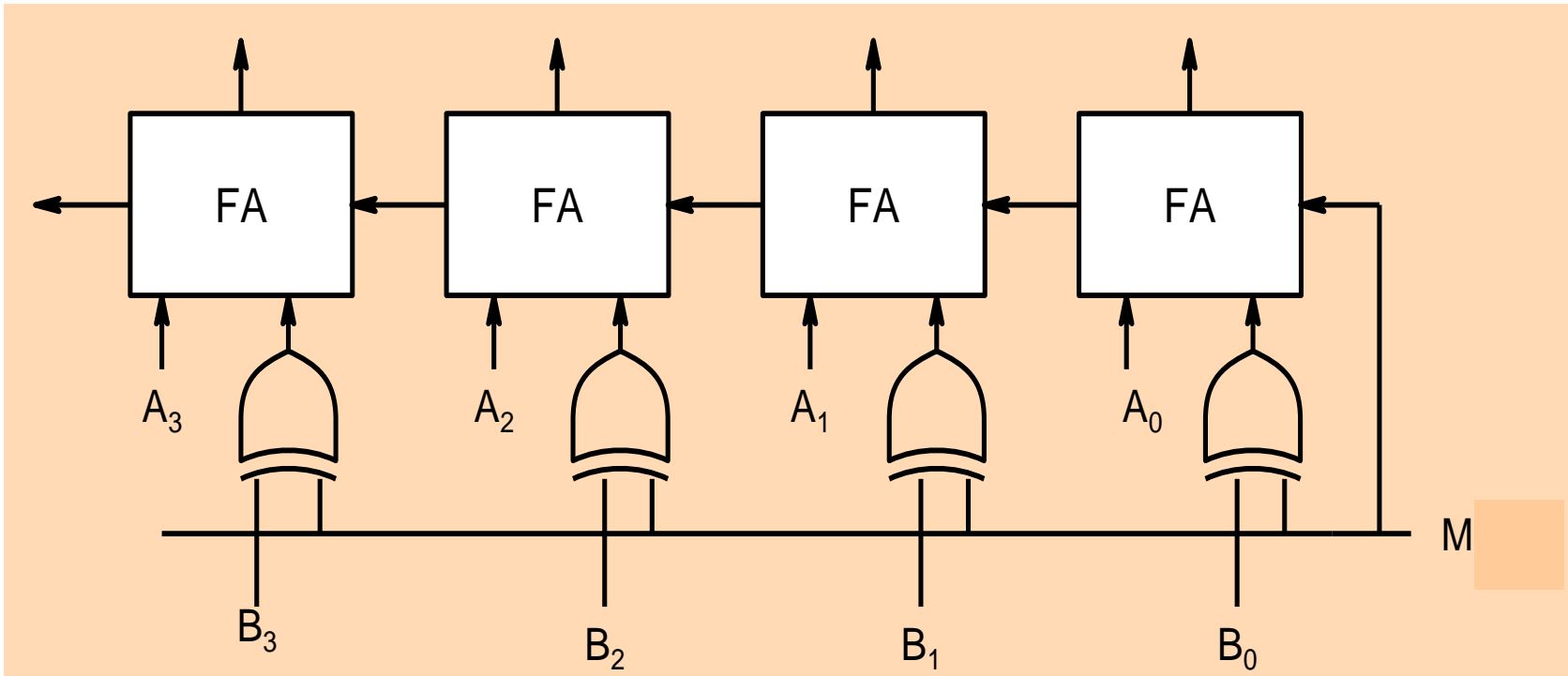 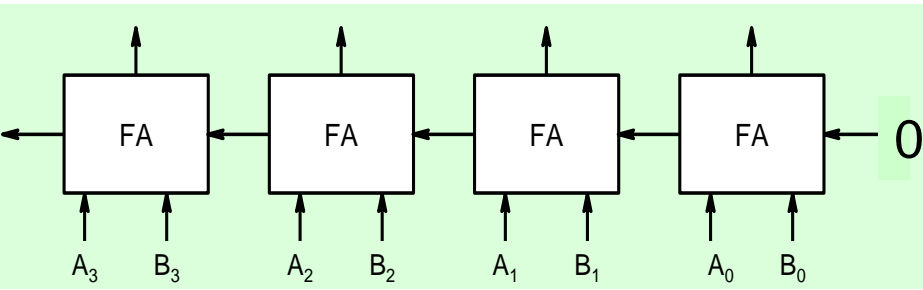


$$B_0 \oplus 0 = B_0 \cdot \bar{0} + \bar{B_0} \cdot 0 = B_0$$
$$B_0 \oplus 1 = B_0 \cdot \bar{1} + \bar{B_0} \cdot 1 = \bar{B_0}$$

M = 0 for Adder
M=1 for Subtractor


Digital Circuits

Combinational Circuits

 


Output is determined by current values of inputs only.

Sequential Circuits

 

Output is determined in general by current values of inputs and past values of inputs/outputs as well.

NOR SR Latch (Set-Reset Latch)

 


$Q = 1; \bar{Q} = 0$ Set State

$Q = 0; \bar{Q} = 1$ Reset State

S	R	Q	\bar{Q}	State
1	0	1	0	SET

NOR SR Latch

 


$Q = 1; \overline{Q} = 0$ Set State

$Q = 0; \overline{Q} = 1$ Re set State

S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET


HOLD State

 

S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	0	1	0	HOLD
0	1	0	1	RESET
0	0	0	1	HOLD




S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID

1 bit memory?


 


Both the outputs are well defined and 0.
The first problem is that we do not get complementary output.

   
A more serious problem occurs when we switch the latch to the hold state by changing RS from 11 \rightarrow 00. Suppose the inputs do not change simultaneously and we get the situation 11 \rightarrow 01* \rightarrow 00





Q = 1

  


$Q = 1$

 

  Suppose the inputs change as $RS = 11 \rightarrow 10^* \rightarrow 00$



$Q = 0$

 

So although output is well defined when we apply $RS = 11$, it becomes unpredictable once we switch the latch to hold state by applying $RS = 00$. That is why $RS = 11$ is not used as an input combination.