


ESc201 : Introduction to Electronics

Digital Circuits

Amit Verma
Dept. of Electrical Engineering
IIT Kanpur


Digital Circuits

Combinational Circuits

 


Output is determined by current values of inputs only.

Sequential Circuits

 

Output is determined in general by current values of inputs and past values of inputs/outputs as well.

NOR SR Latch (Set-Reset Latch) (recap)

 


$Q = 1; \overline{Q} = 0$ Set State

$Q = 0; \overline{Q} = 1$ Reset State

S	R	Q	\overline{Q}	State
1	0	1	0	SET

NOR SR Latch (recap)

 


$Q = 1; \overline{Q} = 0$ Set State

$Q = 0; \overline{Q} = 1$ Re set State

S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET

HOLD State (recap)

 


S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	0	1	0	HOLD
0	1	0	1	RESET
0	0	0	1	HOLD

S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID


1 bit memory?

NAND Latch

 


S	R	Q	\overline{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	HOLD
0	0	1	1	INVALID

RS NAND Latch with Enable

 


Hold State

 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid

D latch

 


Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid

 


If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state



Latch with clock

 

 Circuits are designed with the idea there would be single change in output or memory state in single clock cycle.





Edge Triggered Latch or Flip-flop


 
 


Positive edge triggered flipflop

  Negative Edge Triggered Latch or Flip-flop




Master-Slave D Flip-flop

   

Characteristic table

 
Given a input and the present state of the flip-flop, what is the next state of the flip-flop



Inputs (D)	Q(t+1)
0	0
1	1

Characteristic equation: $Q(t + 1) = D$

JK Flip-flop

 

Inputs J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

Characteristic equation: $Q(t + 1) = J\overline{Q}(t) + \overline{K}Q(t)$

JK flip flop is refinement of RS flip flop where indeterminate state of RS flip flop is defined in JK Flip Flop


JK Flip-flop (characteristic equation)

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

		JK			
		00	01	11	10
Q	0			1	1
	1	1			1

$$Q(t+1) = J\bar{Q}(t) + \bar{K}Q(t)$$

Toggle or T Flip-flop

 


Inputs (T)	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$

Characteristic equation: $Q(t+1) = T \oplus Q(t)$

T	Q(t)	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

Toggle or T Flip-flop

 

Inputs (T)	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

Characteristic equation:

$$Q(t+1) = T \oplus Q(t)$$

Excitation Table

What inputs are required to effect a particular state change


Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table

Inputs

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

JK Flip-flop excitation table

 

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$

Characteristic Table

Inputs		
Q(t)	Q(t+1)	J K
0	0	0 X
0	1	1 X
1	0	X 1
1	1	X 0

Excitation Table

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0