

# ESC201A Assignment 3

Instructor Abhishek Gupta


2023-2024 Semester I

## Topics


Transient analysis, Steady state, Sinusoidal sources, Phasors

## Questions

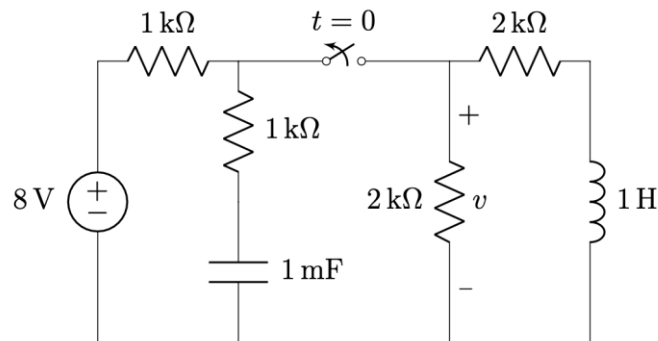
1. For the circuit shown below, determine the voltage across the 2K resistor (vertical) as a function of time after the switch is opened at  $t = 0$ .



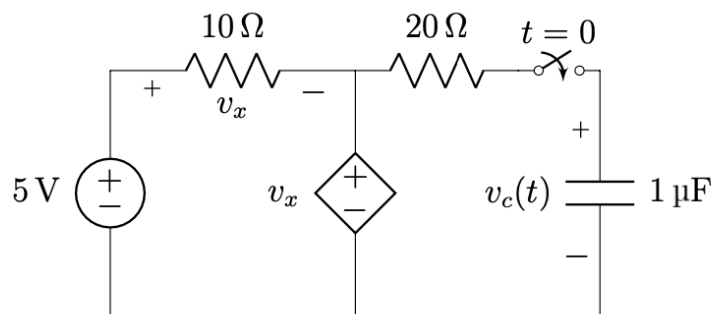
2. Find  $v_c(t)$  for  $t > 0$  in the following circuit if the capacitor voltage is zero for  $t < 0$ .



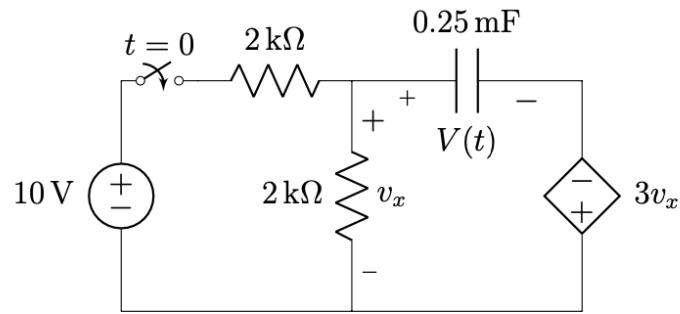3. Assuming that the capacitor does not have any initial charge, determine the voltage across the capacitor  $V(t)$  as a function of time after the switch is closed at  $t = 0$ .



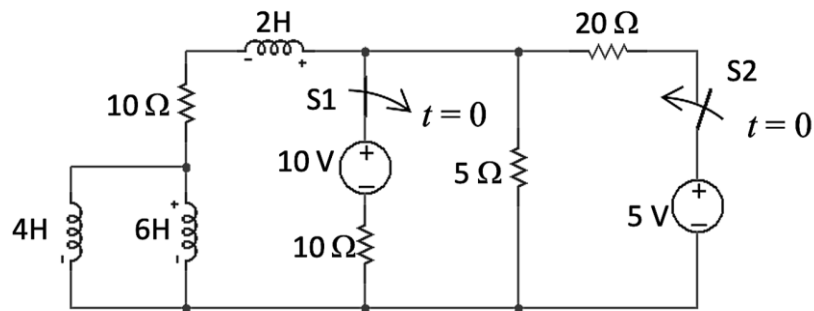4. In the following circuit the switch S1 is closed and S2 is left open for a long time. At  $t=0$ , S1 is opened and S2 is closed. Determine the current,  $i_5$ , through the  $5\Omega$  resistor for all time



5. Express the following sinusoidal signals in the canonical form  $V_m \cos(\omega t + \theta)$ :

(i)  $v(t) = -110 \cos(\omega t + 30^\circ) V$

(ii)  $v(t) = 220 \sin(\omega t + 220^\circ) V$

(iii)  $v(t) = 10 \sin(\omega t + 110^\circ) + 4 \cos(\omega t + 110^\circ) V$

(iv)  $v(t) = 10 \cos(\omega t + 370^\circ) * 4 \sin(\omega t + 10^\circ) V$

Wherever needed, you may use phasors to make your task easier.

6. Determine the output voltage as a function of time using the method of phasors for an input voltage of  $V_s = 5 \cos(100t) V$ .

