

# ESC 201 Assignment 10 Solutions

Ans 1.

$$f = (x \cdot y + z) \cdot (y + x \cdot z)$$


x	y	z	$(x \cdot y + z)$	$(y + x \cdot z)$	f
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

SOP:  $f = \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$


POS:  $f = (x+y+z)(x+y+\bar{z})(x+\bar{y}+z)(\bar{x}+y+z)$

Ans 2.


$$\begin{aligned}
 f &= x_1 + x_2 + x_3 + x_4 + x_5 + x_6 + x_7 + x_8 \\
 &= (x_1 + x_2) + (x_3 + x_4) + (x_5 + x_6) + (x_7 + x_8) \\
 &= A_1 + A_2 + A_3 + A_4 \\
 &= (A_1 + A_2) + (A_3 + A_4) \\
 &= B_1 + B_2
 \end{aligned}$$

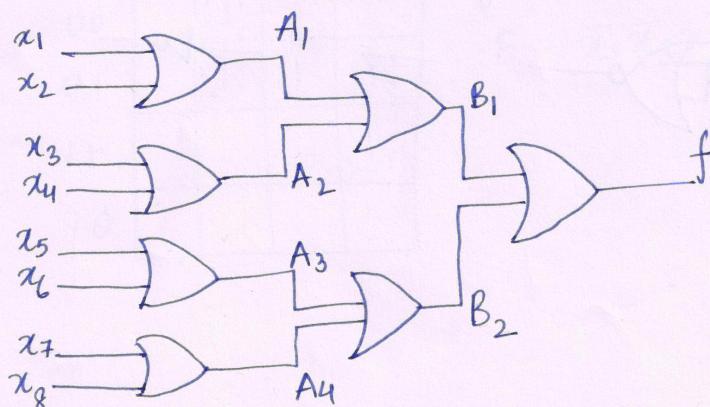

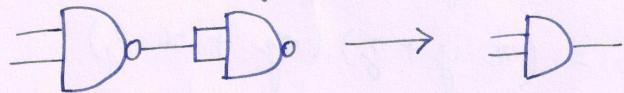Ans 3. 2-input AND gate using 2-input NAND gate:



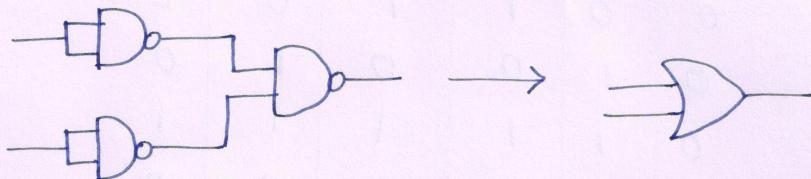
2-input OR gate using 2-input NAND gates:



NOT gate using 2-input NAND gate:



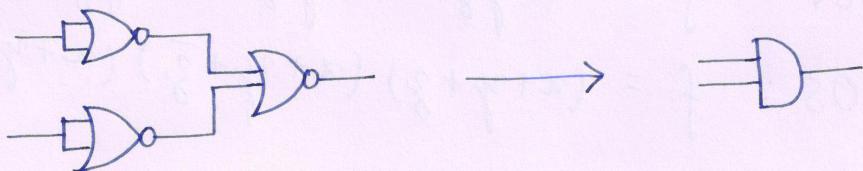
2-input AND gate using 2-input NOR gates:



2-input OR gate using 2-input NOR gates:





NOT gate using 2-input NOR gate:

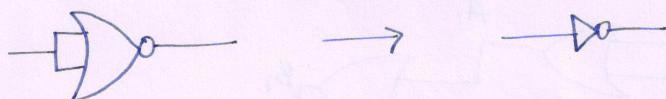


Q4.

$$f = \bar{x}y + x\bar{y}$$

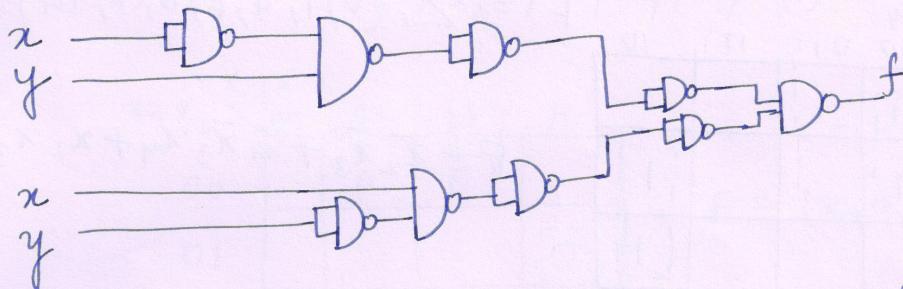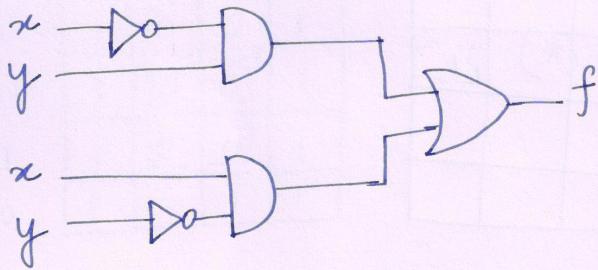

Two NOT gates in series cancel.

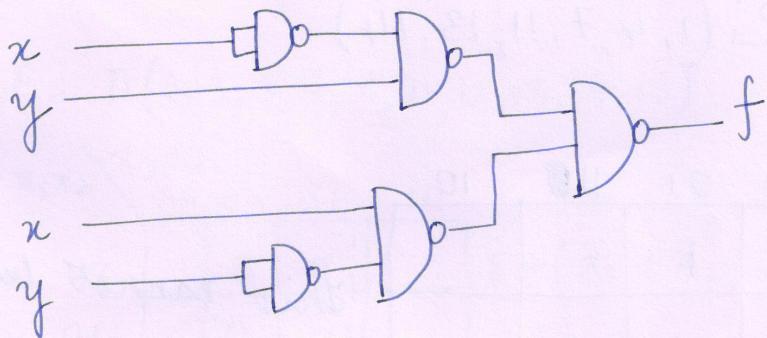

Ans 5. (a)

$x_1x_2$	$x_3x_4$	00	01	11	10
00		1	1	1	1
01		1	1	1	1
11				1	1
10					

$$F = \sum(1, 5, 6, 7, 14)$$

$$F = \bar{x}_1\bar{x}_3x_4 + \bar{x}_1x_2x_3 + x_2x_3\bar{x}_4$$

$$(b) F = \sum(0, 4, 6, 8)$$

$x_1x_2$	$x_3x_4$	00	01	11	10
00	11				
01	11				11
11					
10	11				

$$F = \bar{x}_2\bar{x}_3x_4 + \bar{x}_1x_2\bar{x}_4$$

(c)

$x_1x_2$	$x_3x_4$	00	01	11	10
00	11	11			
01	11				11
11					
10	11	11			

$$F = \sum(0, 1, 4, 6, 8, 9, 14)$$

$$F = \bar{x}_2\bar{x}_3 + \bar{x}_1\bar{x}_3x_4 + x_2x_3\bar{x}_4$$

$$(d) F = \sum(1, 4, 7, 11, 13, 14)$$

$x_1x_2$	$x_3x_4$	00	01	11	10
00			1		
01		1		1	
11			1		1
10				1	

This cannot be minimized.

a6 (a)  $F = \Pi(1, 3, 5, 7, 13, 15)$

$x_1x_2$	$x_3x_4$	00	01	11	10
00	1	10	01	1	
01	1	10	01	1	
11	1	0	01	1	
10	1	1	1	1	

$$F = (x_1 + \bar{x}_4)(\bar{x}_2 + \bar{x}_4)$$

(b)  $F = \Pi(1, 3, 6, 9, 11, 12, 14)$

$x_1x_2$	$x_3x_4$	00	01	11	10
00	10	01			
01				10	
11	01			10	
10	10	01			

$$F = (x_2 + \bar{x}_4)(\bar{x}_1 + \bar{x}_2 + x_4),$$

$$(\bar{x}_2 + \bar{x}_3 + x_4)$$

(c)  $F = \Pi(1, 3, 5, 7, 9, 11, 12, 13, 14, 15)$

$x_1x_2$	$x_3x_4$	00	01	11	10
00	10	01			
01	10	01			
11	10	10	01	10	
10	10	01			

$$F = (\bar{x}_1 + \bar{x}_2)(\bar{x}_4)$$

(d)  $F = (0, 1, 3, 4, 5, 7, 12, 13, 15)$

$x_1x_2$	$x_3x_4$	00	01	11	10
00	10	10	01		
01	10	10	01		
11	10	10	01		
10					

$$F = (x_1 + x_3)(x_1 + \bar{x}_4)(\bar{x}_2 + x_3)(\bar{x}_2 + \bar{x}_4)$$

Ans 7. (a)  $F(A, B, C, D) = \sum(4, 5, 7, 12, 13, 14)$

$$d(A, B, C, D) = \sum(1, 9, 11, 15)$$

AB	CD	00	01	11	10
00		X			
01	11	111	111	11	
11	11	111	111	X1	1
10		X	X		

$$F = AB + B\bar{C} + BD$$

(b)

AB	CD	00	01	11	10
00		11			11
01					
11	11	11	11	11	
10	11	X1	X1	X	X1

$$F(A, B, C, D) = \sum(1, 2, 12, 13, 14)$$


$$d(A, B, C, D) = \sum(8, 9, 10, 11)$$

$$F = A\bar{C} + A\bar{D} + \bar{B}\bar{C}D + \bar{B}CD$$

Ans 8.  $F = (ab+cd)(\bar{a}b+\bar{c}d+a\bar{c})$


$$F = ab\bar{c}d + ab\bar{c} + \bar{a}bcd$$

AND-OR:

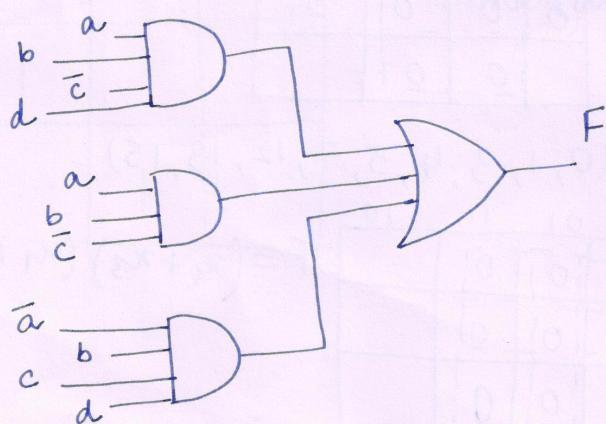

OR - AND : Implement  $\bar{F}$  and then invert it:
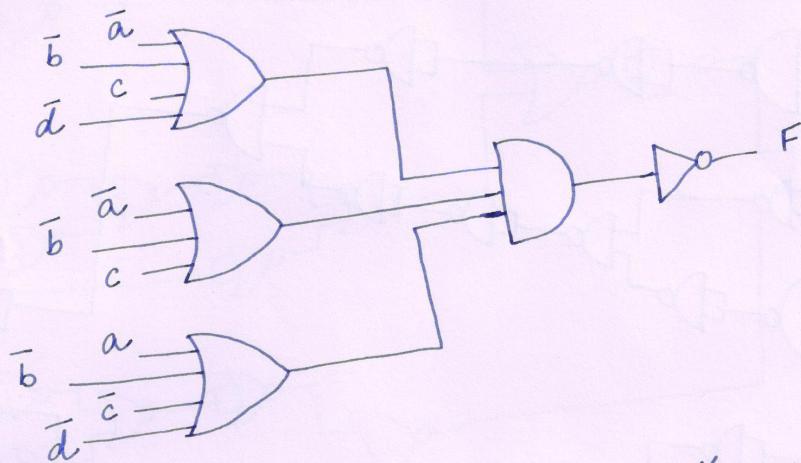
$$\bar{F} = (\bar{a} + \bar{b} + c + \bar{d}) \cdot (\bar{a} + \bar{b} + c) \cdot (a + \bar{b} + \bar{c} + \bar{d})$$




An alternate is to obtain Pos from K-map:

$$F = ab\bar{c}\bar{d} + ab\bar{c} + \bar{a}bcd$$

↳ Can be minimized further.



		cd		ab	
		00	01	11	10
ab	00	1		1	1
	01	1	1		1
ab	11	1	1	0	1
	10	1	0	1	1

$$F = (b + \bar{c})(\bar{b} + d)(\bar{b} + c)\bar{a}$$

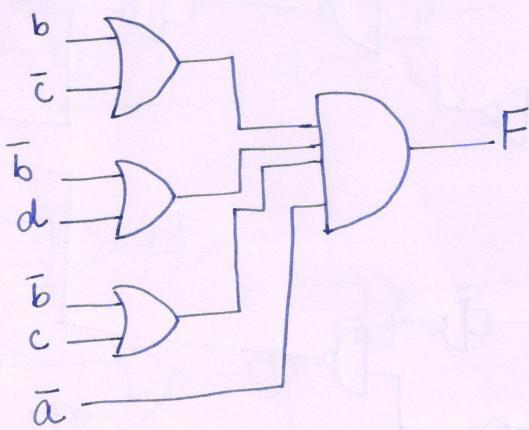


Ans 9.  $F(a, b, c, d) = ab + \bar{a}bc + \bar{a}\bar{b}\bar{c}d$


Using 2-input NAND gates:

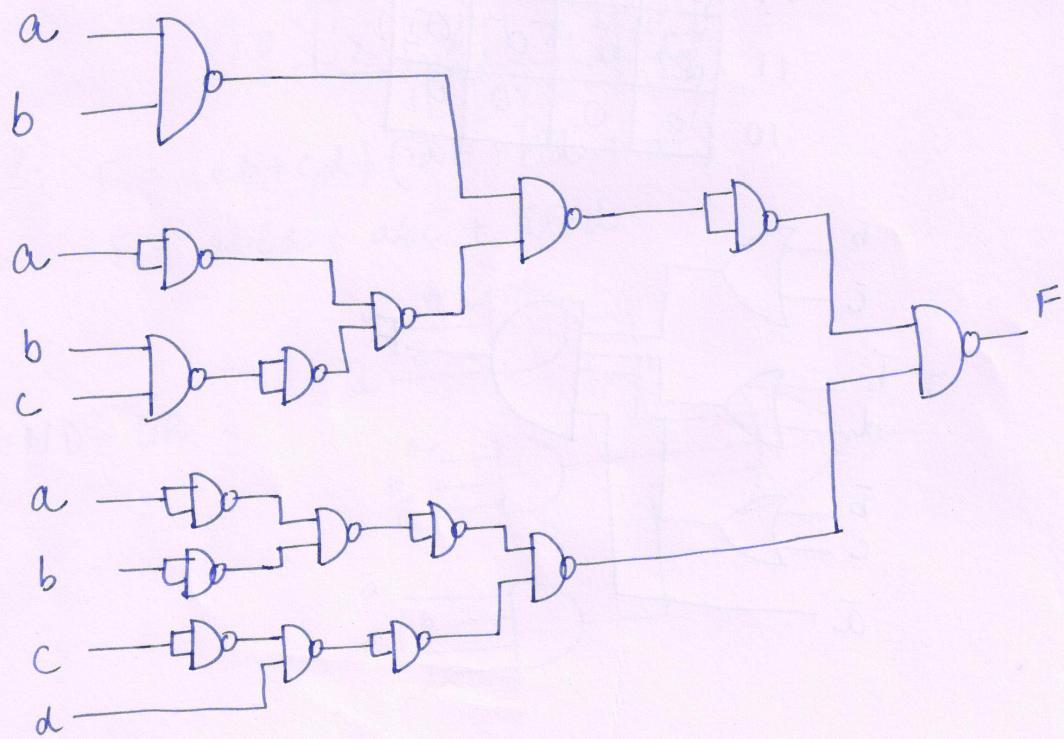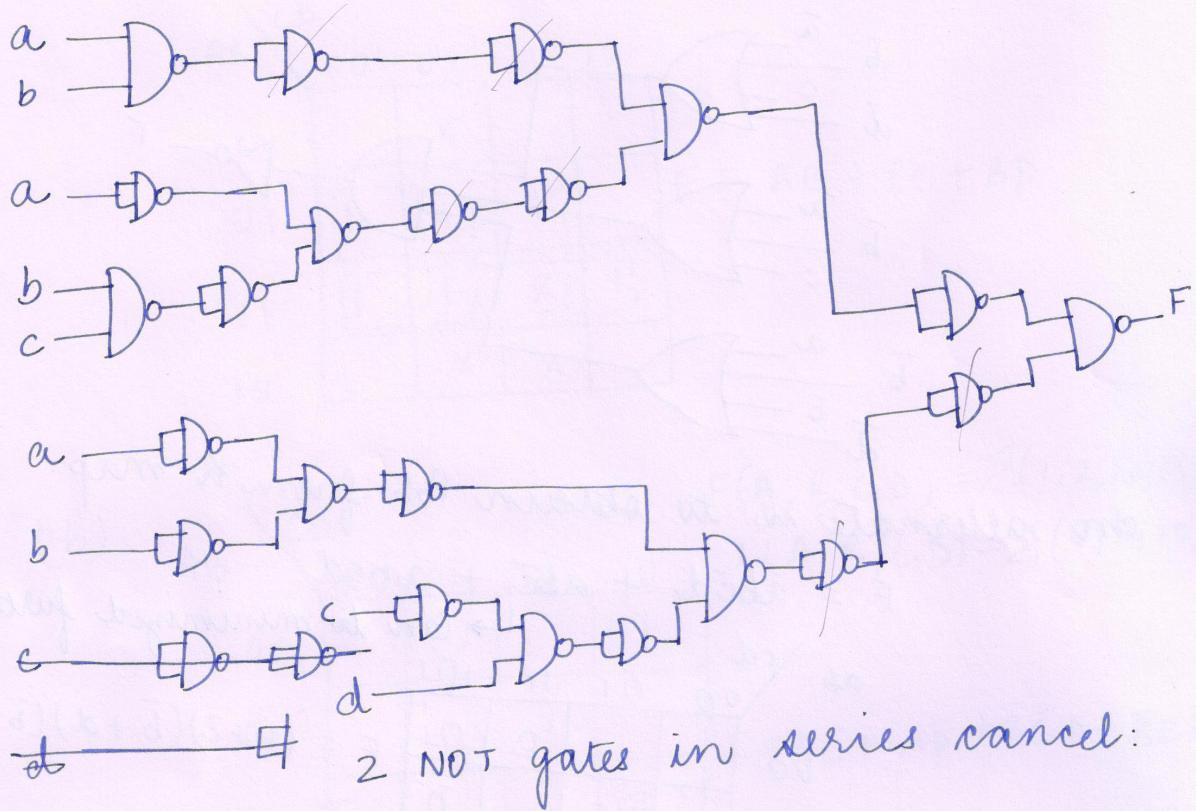

using 2-input NOR gates:


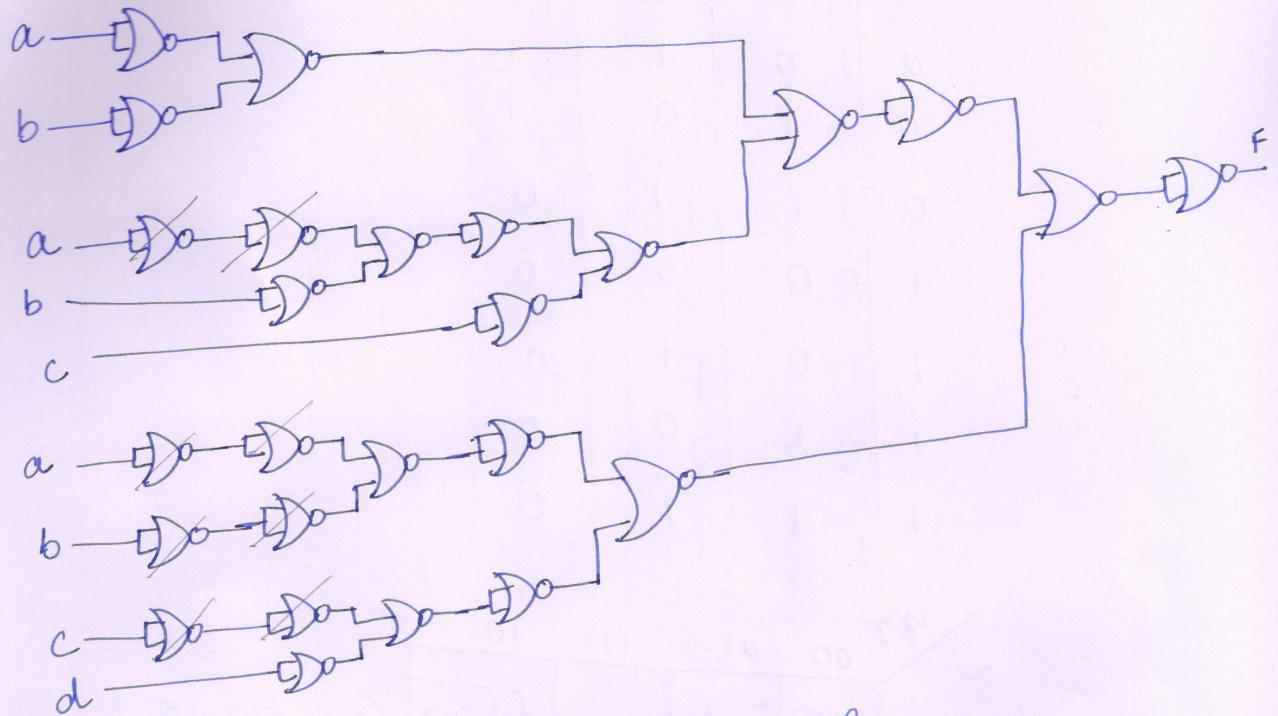


2 NOT gates in series cancel:

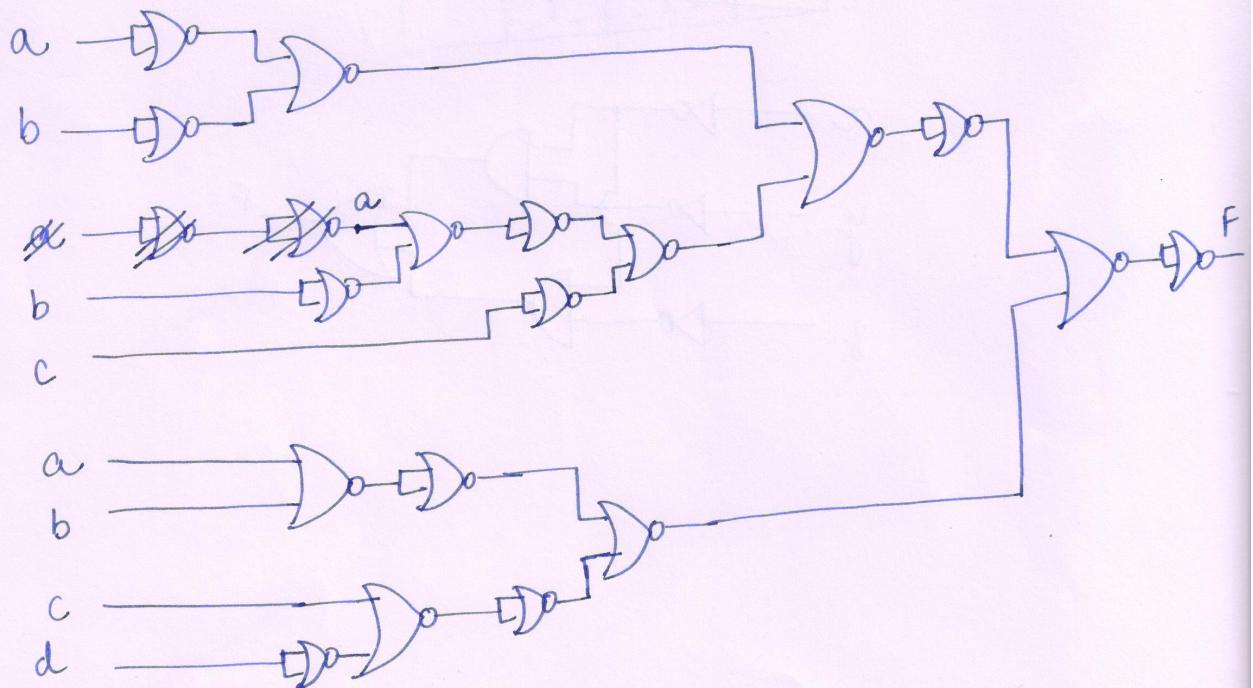

Ana 10. (a)

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

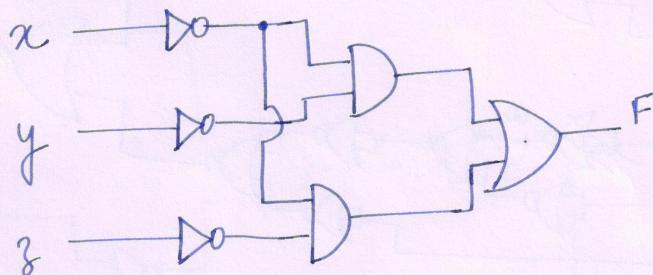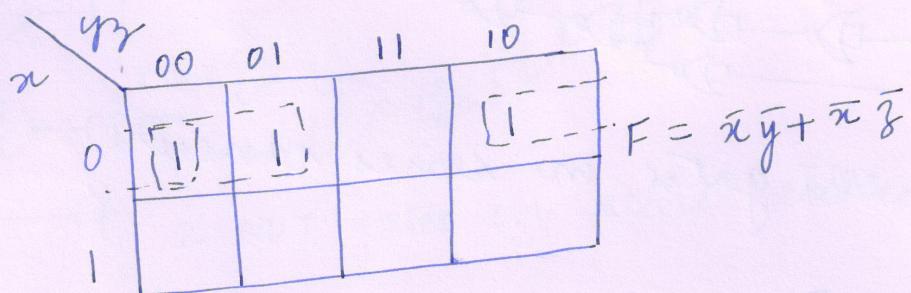

(b)

$x$	$y$	$z$	$f$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$x \swarrow y \searrow z$

	00	01	11	10
0	00	01	11	10
1	11	10	01	00

$F = 8$