

ESc201 : Introduction to Electronics

DC Power Supply


Amit Verma
Dept. of Electrical Engineering
IIT Kanpur

Recap: Diode Models





$$i_D = I_S \times \left\{ \exp\left(\frac{v_d}{V_T}\right) - 1 \right\}$$

Simplicity

Accuracy




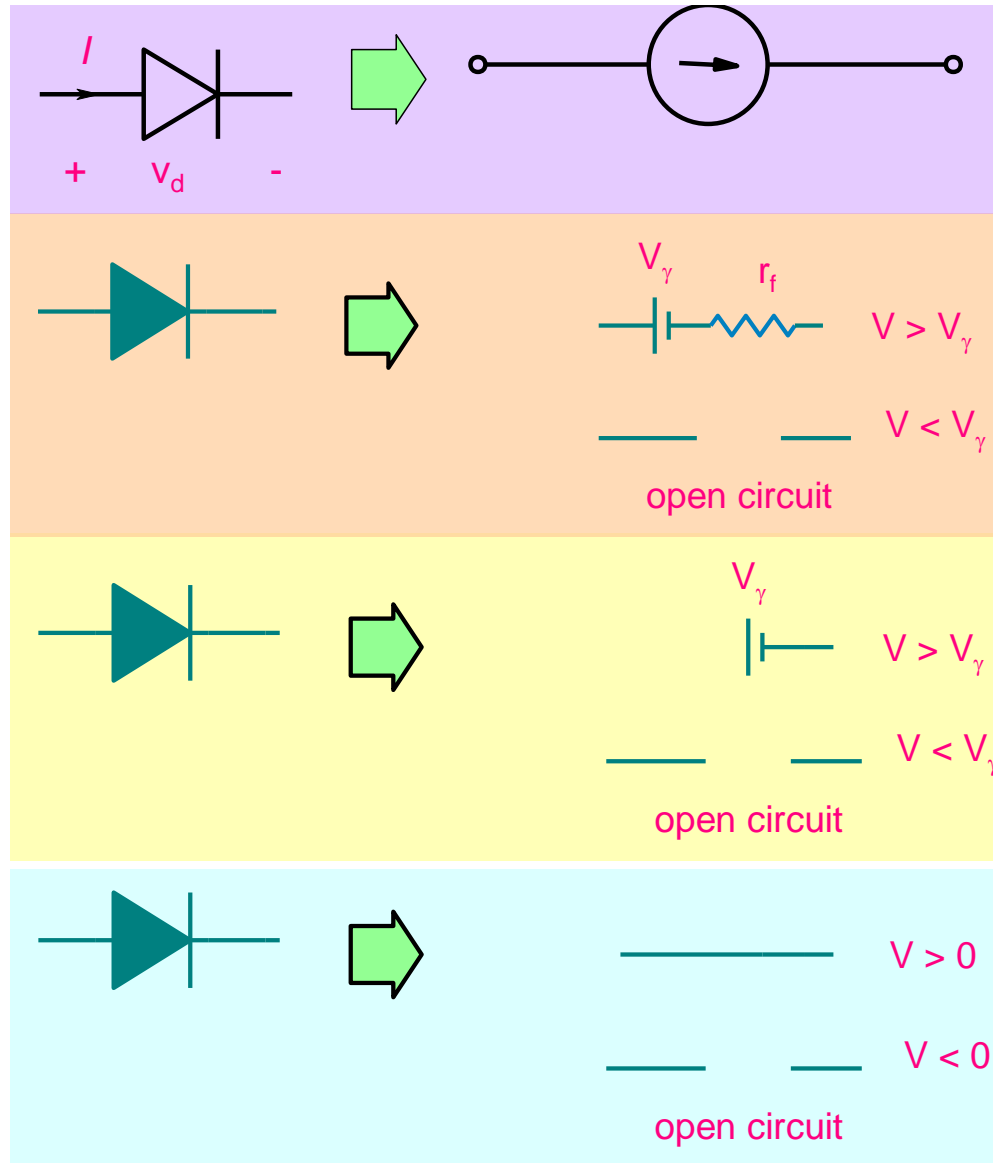


Analysis using ideal diode model

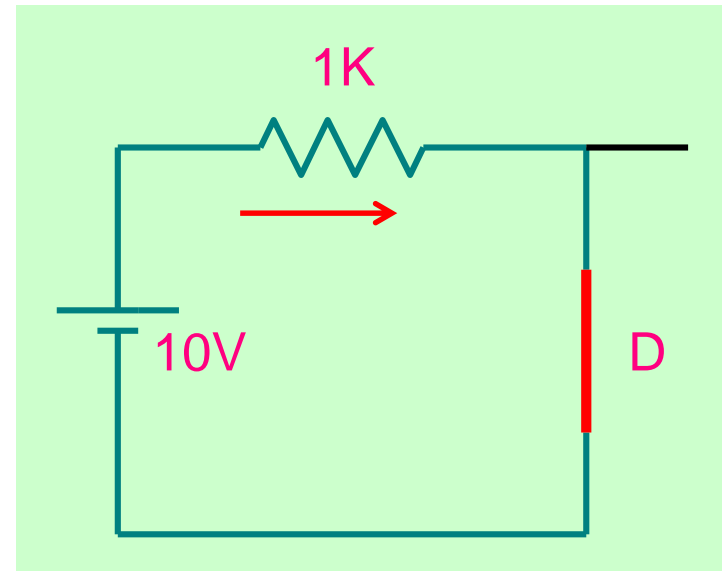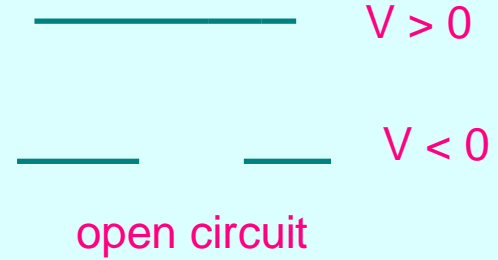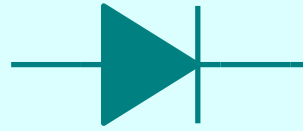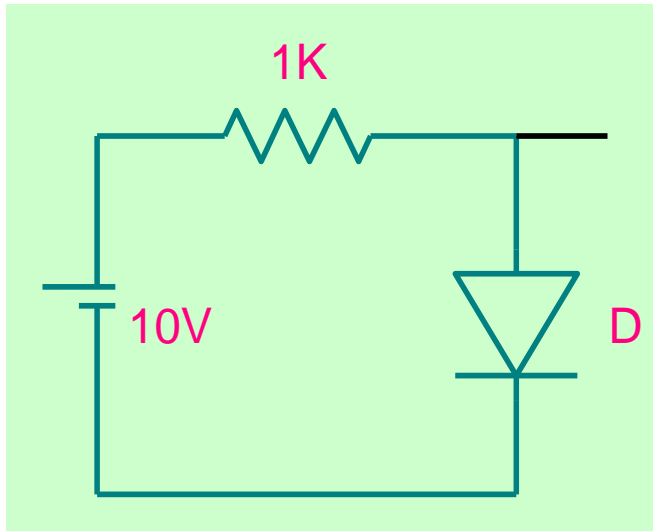



$$I = \frac{10}{1k} = 10mA$$

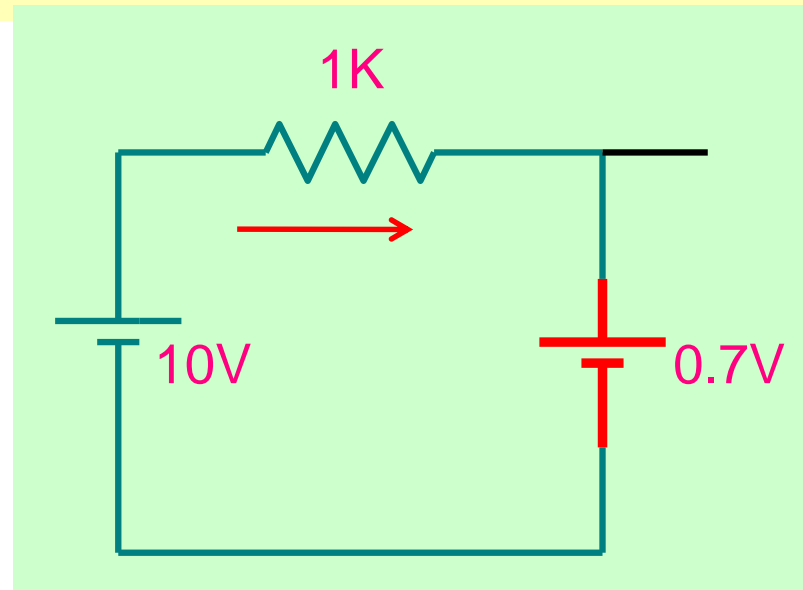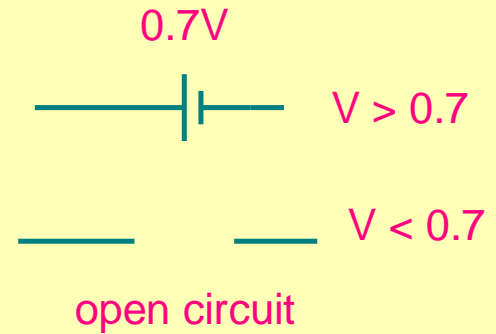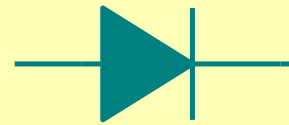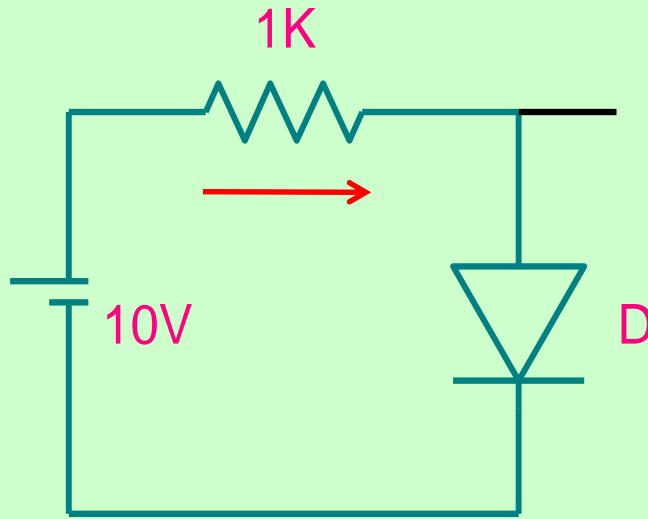Analysis with a constant voltage diode model



$$I = \frac{10 - 0.7}{1k} = 9.3mA$$

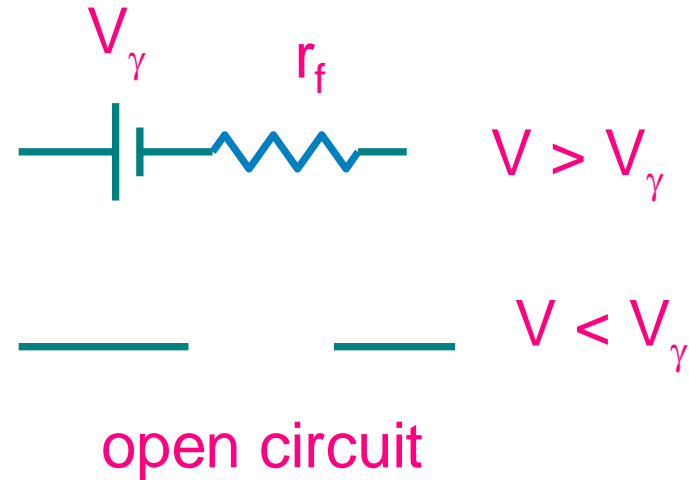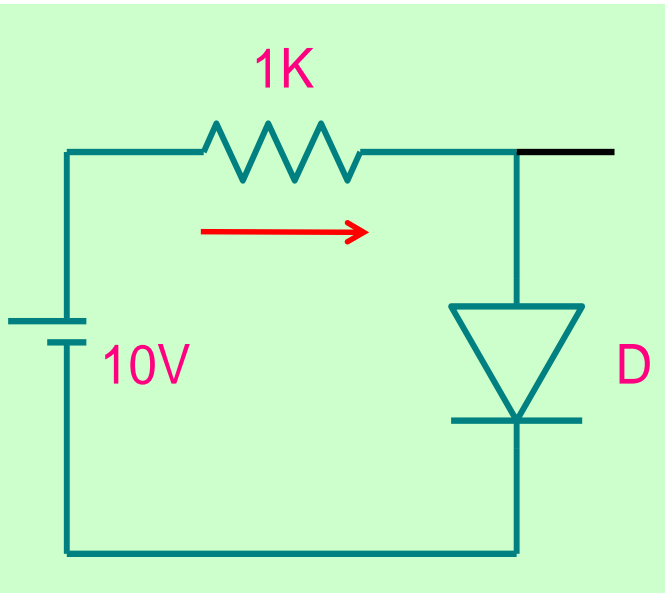
Analysis with a constant voltage plus resistor diode model



$$I = \frac{10 - 0.7}{1000 + 10} = 9.208mA$$

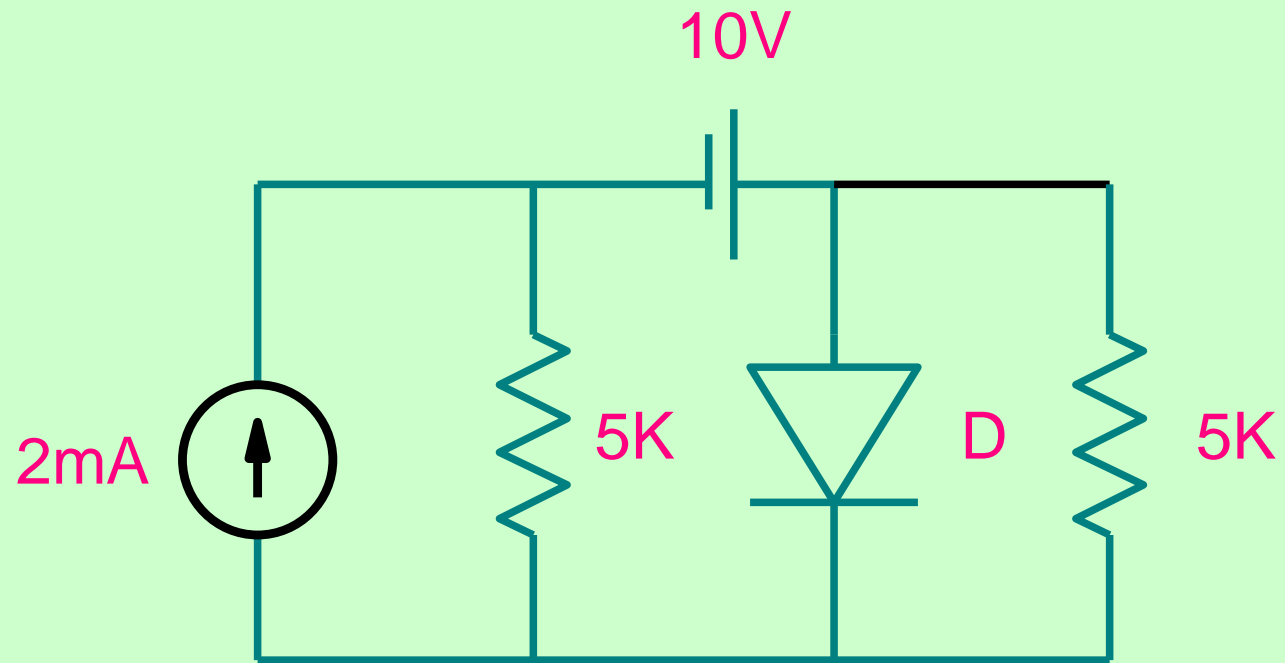Example

Find the current through the diode using ideal diode model



Is the diode forward biased? – Not Sure!!



Assume that it is forward biased 😊

Carry out analysis and then check if current through the diode is in **appropriate** direction.

If not, diode is reverse biased and we carry out the analysis again!!

Example

Assume forward bias

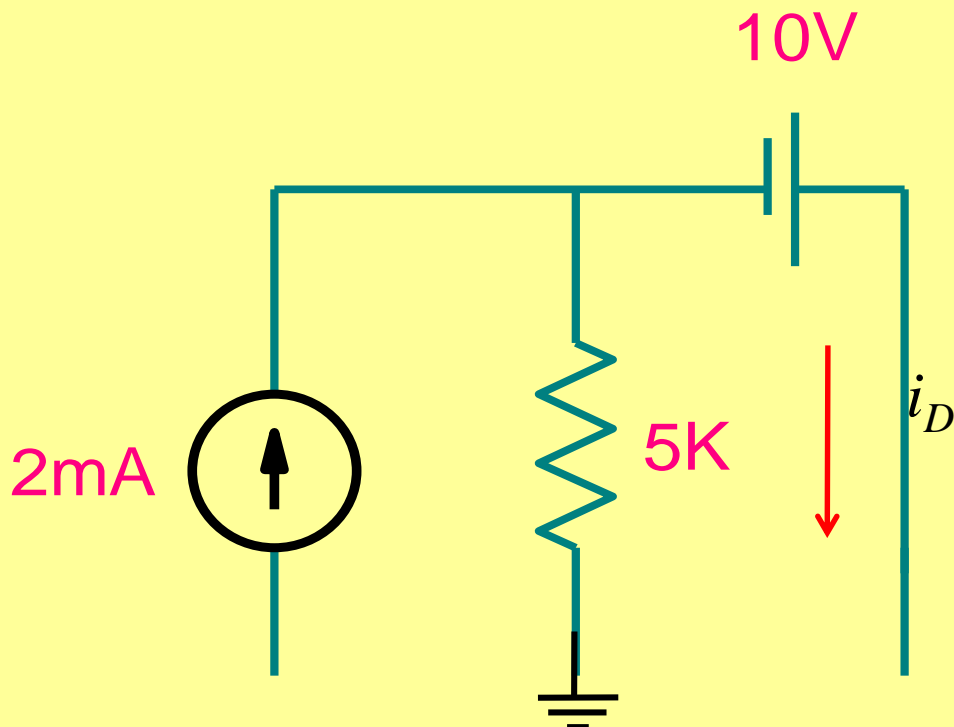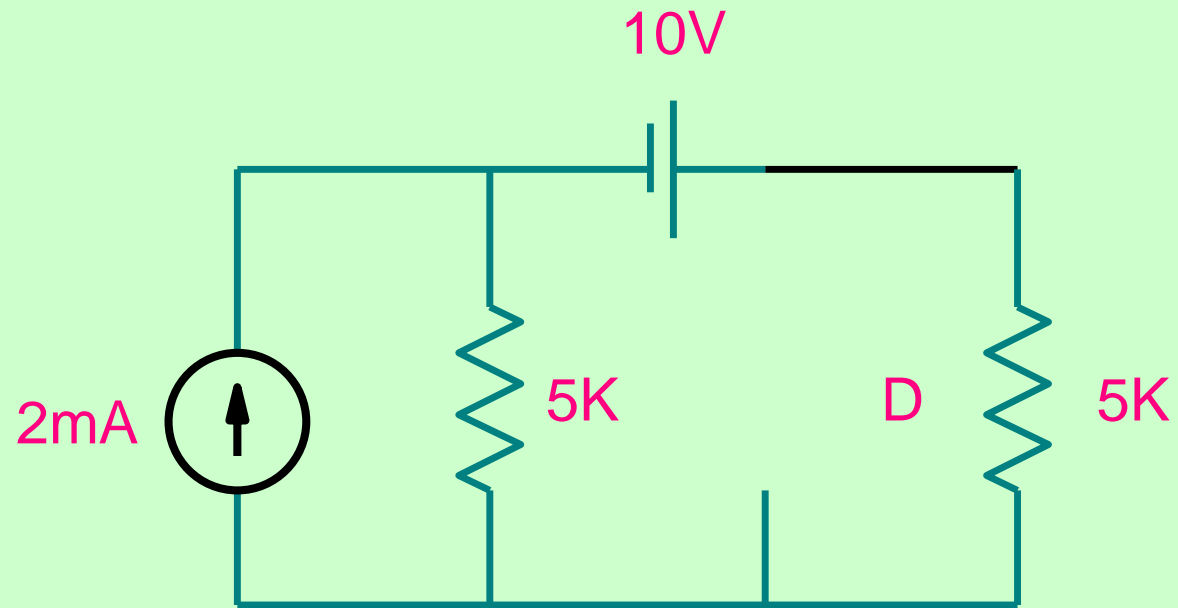


$$-2mA + \frac{-10}{5K} + i_D = 0$$


$$i_D = 4mA$$


Current is positive, so our assumption is correct

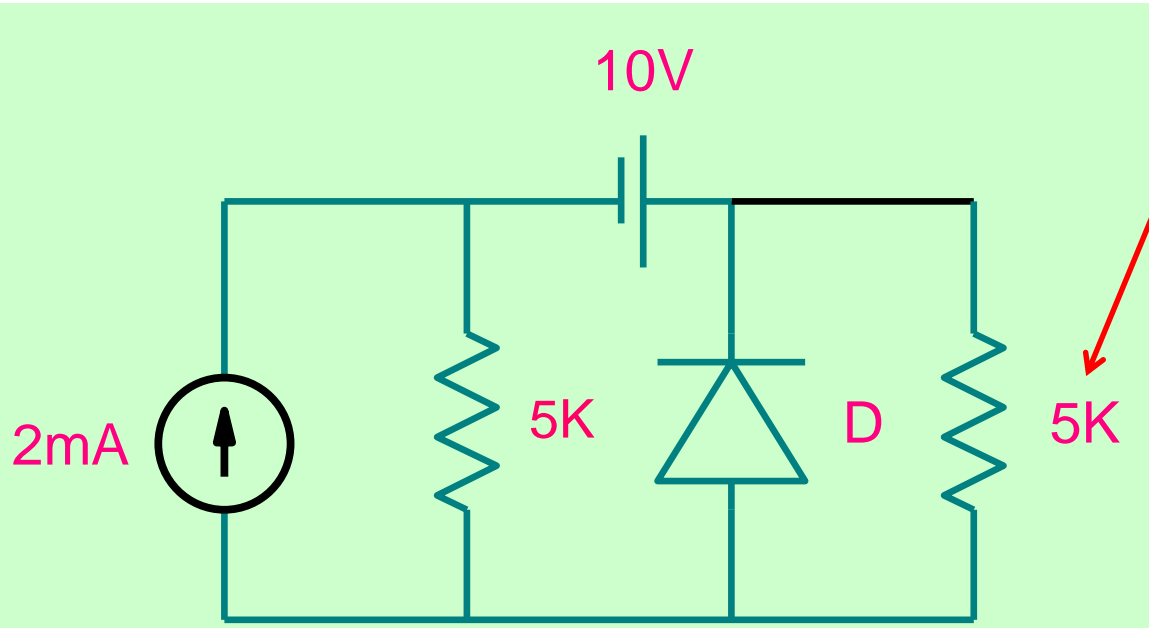Example Find the current through the 5K resistor using ideal diode model



Assume forward bias

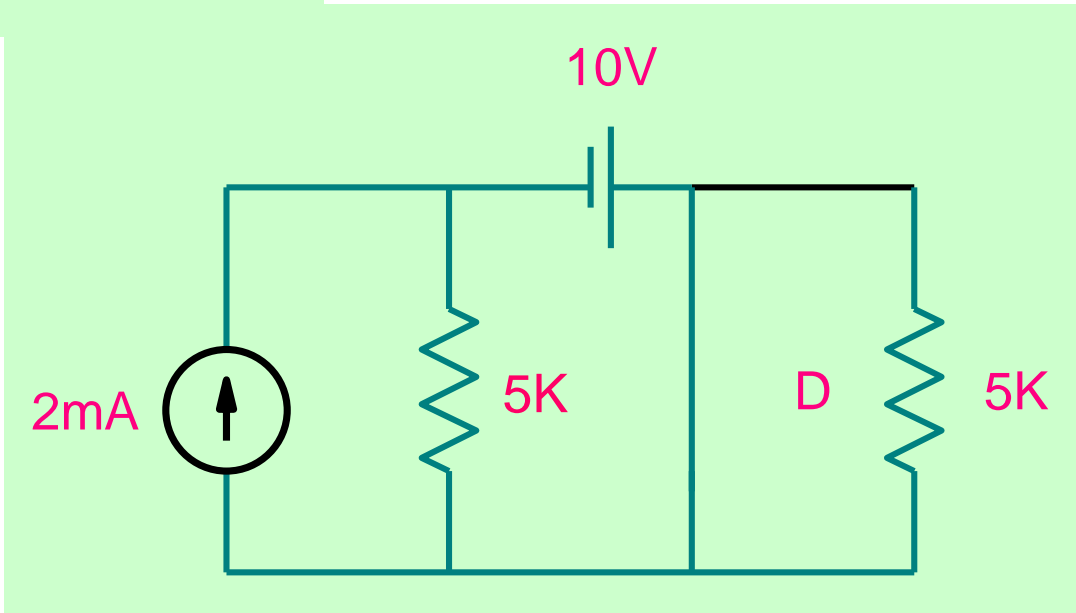

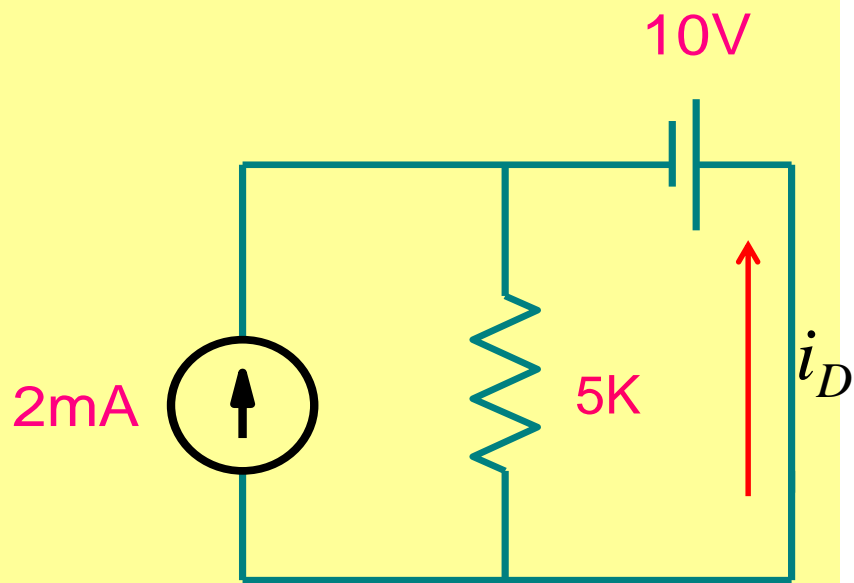



$$-2mA + \frac{-10}{5K} - i_D = 0$$

$$i_D = -4 \text{ mA}$$

This is not possible.

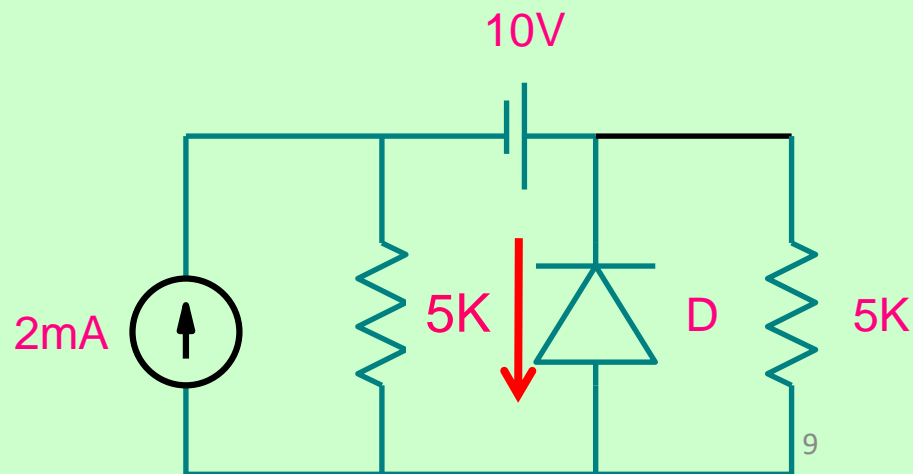**Therefore, our assumption
is incorrect**



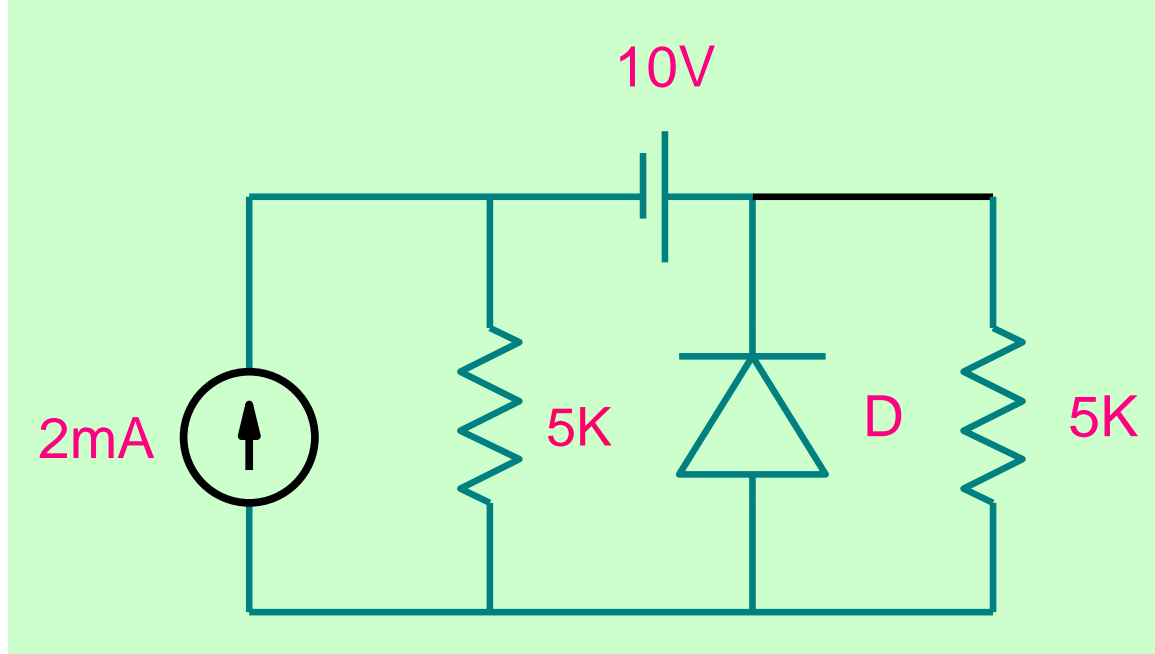


Assume reverse bias

$$-2mA + \frac{V_1}{5k} + \frac{V_1 + 10}{5k} = 0$$

$$V_1 = 0$$

$$V_2 = 10V$$


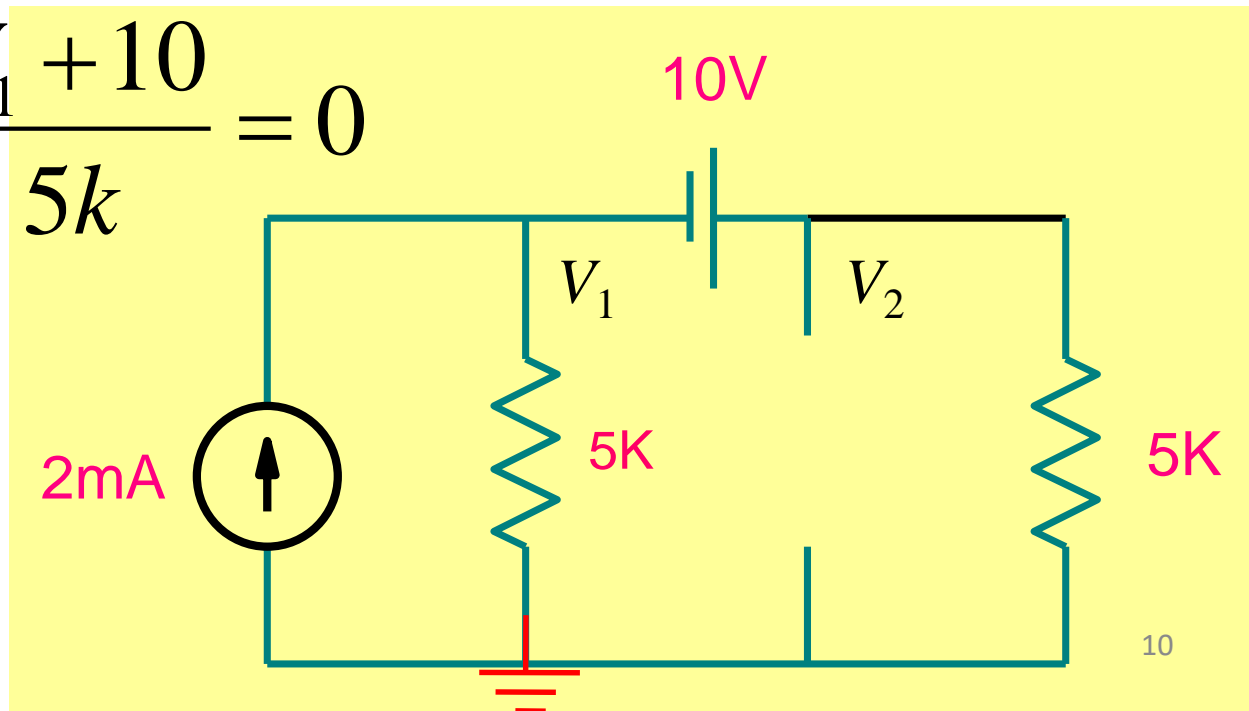




DC Power Supply

Half wave Rectifier circuit



$220V \text{ rms}$
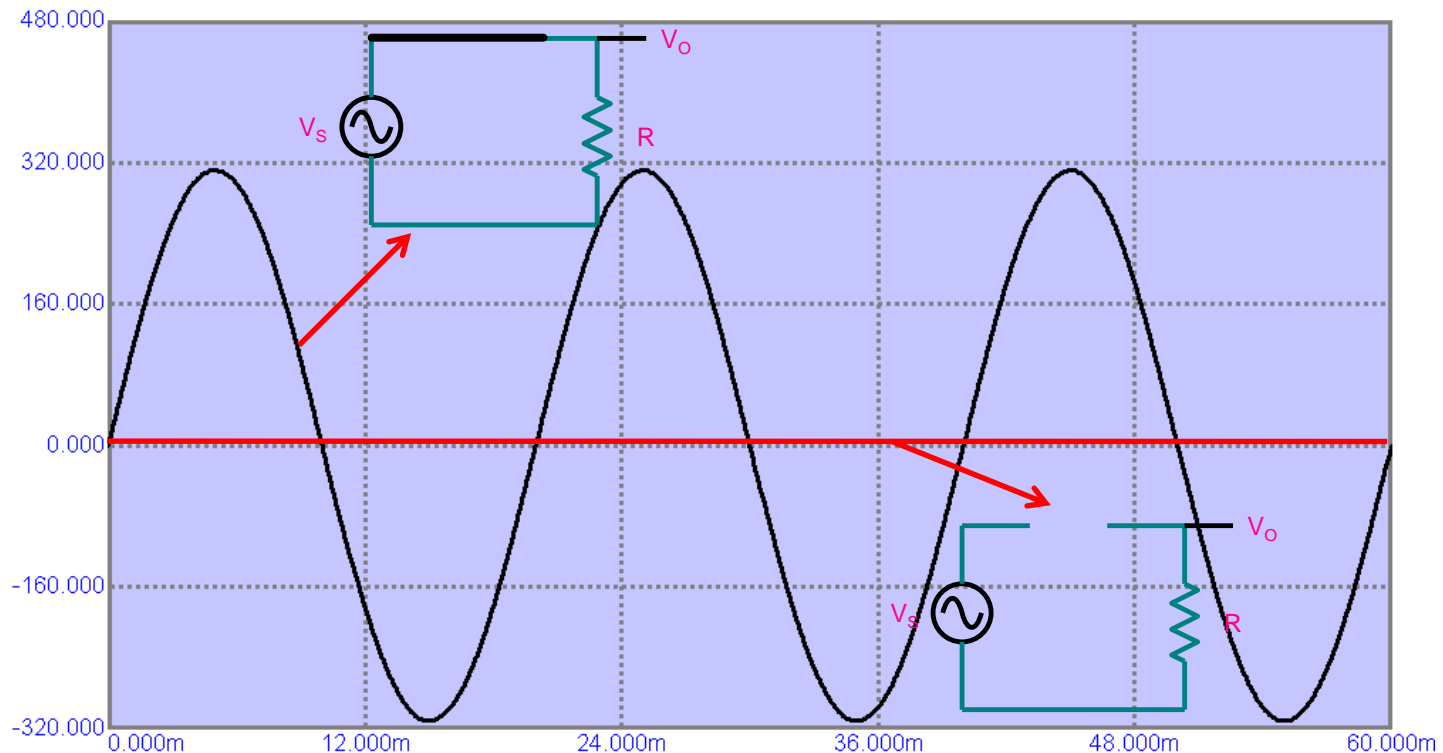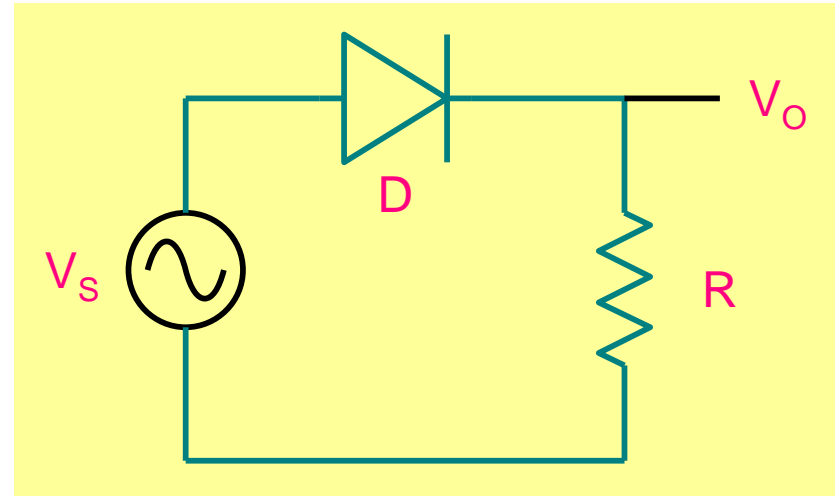
$$220V \times \sqrt{2} \\ = 311.127V \text{ peak value}$$



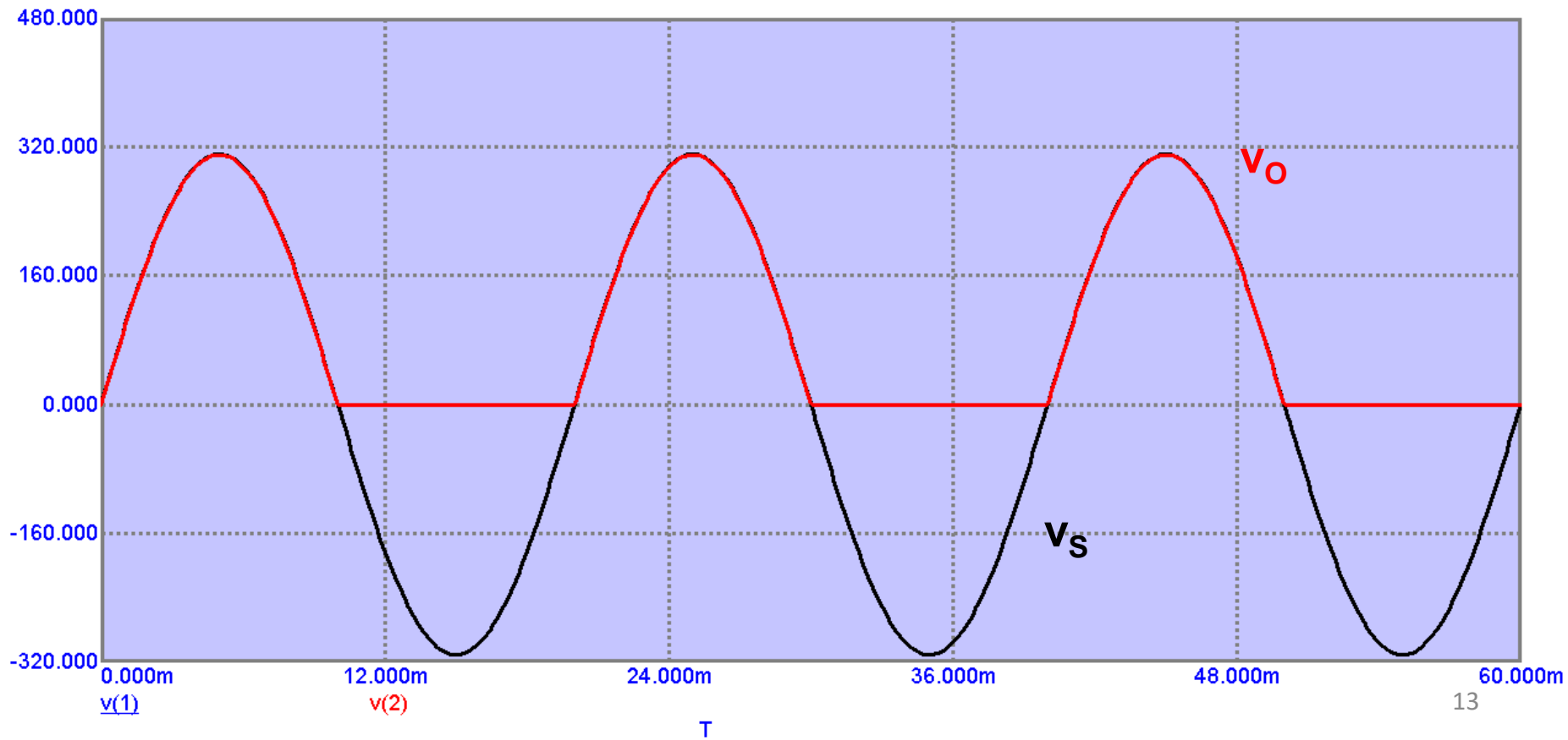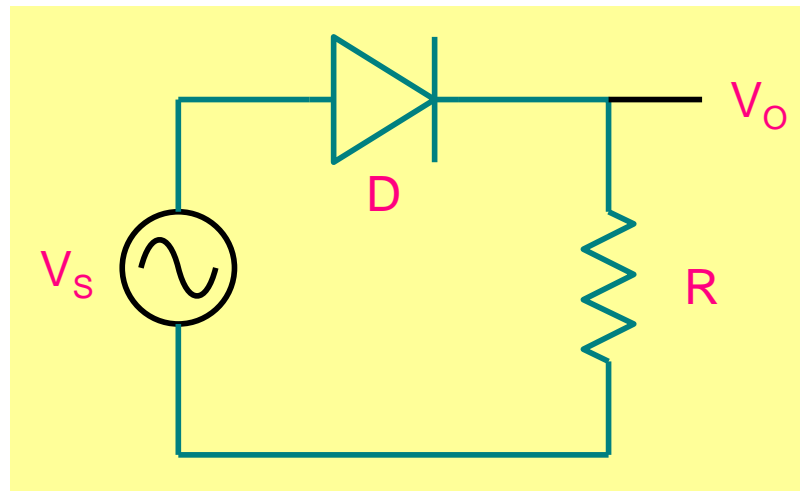



Transformer

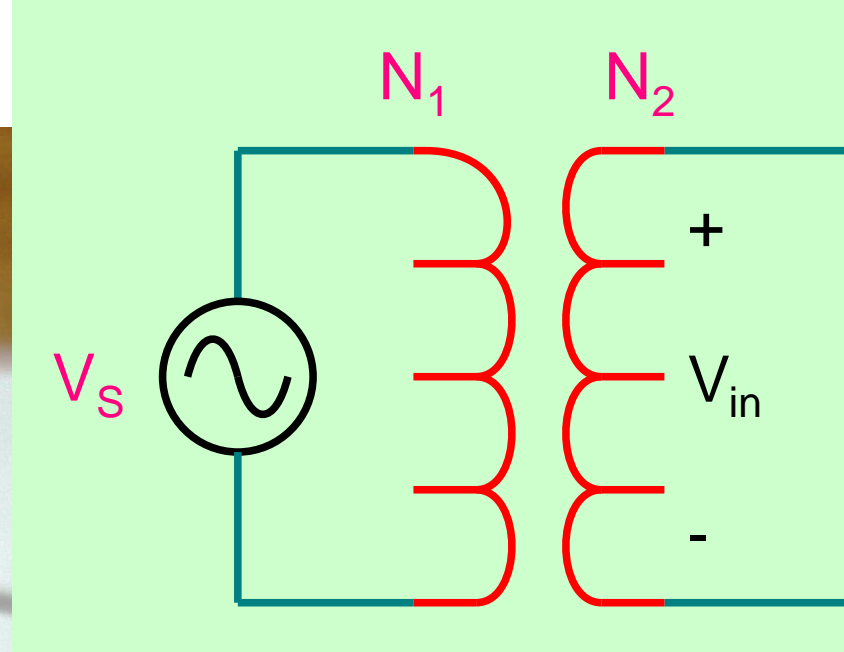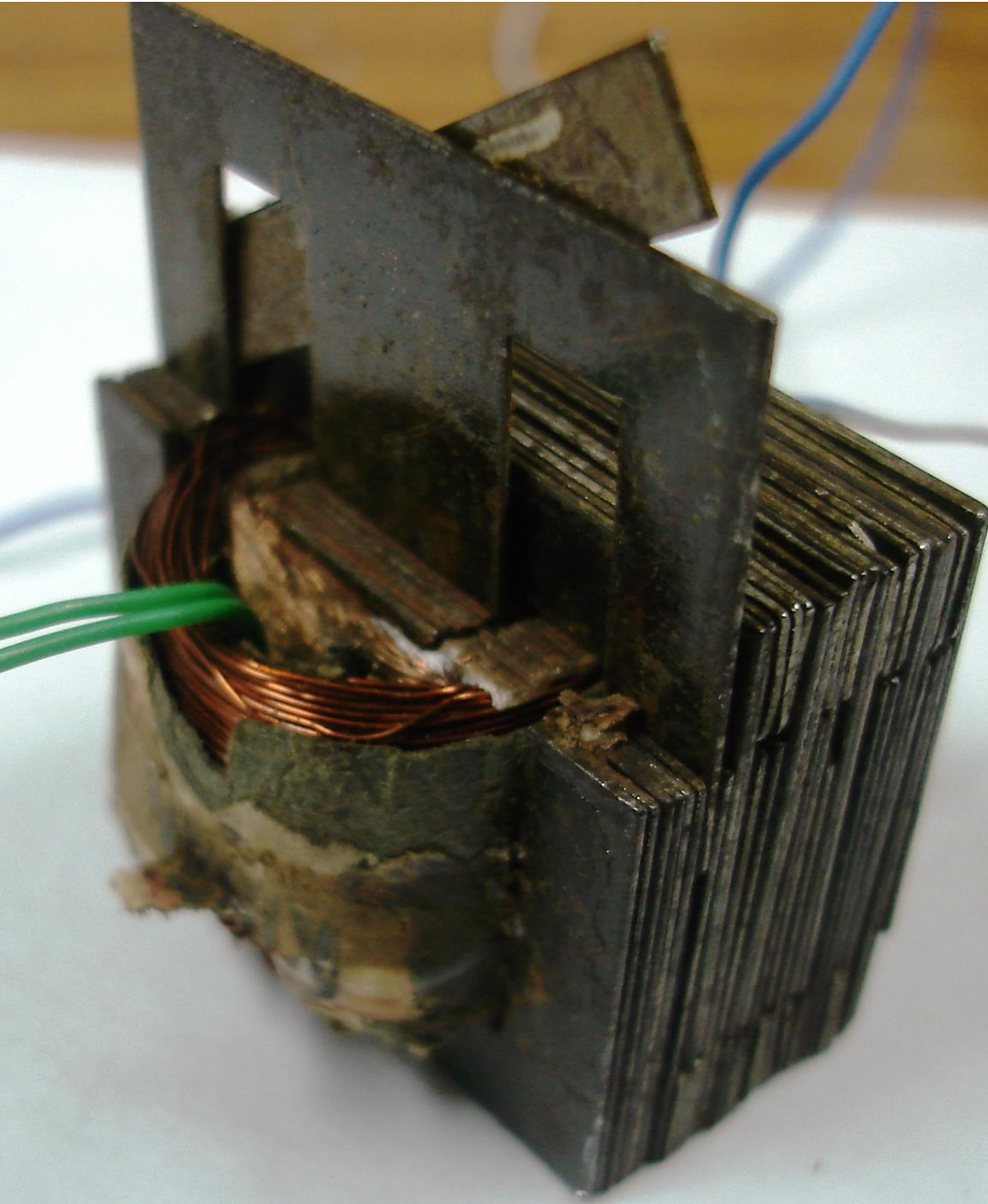

$$\frac{V_S}{V_{IN}} = \frac{N_1}{N_2}$$

Half Wave Rectifier

$$\frac{V_S}{V_{IN}} = \frac{N_1}{N_2}$$

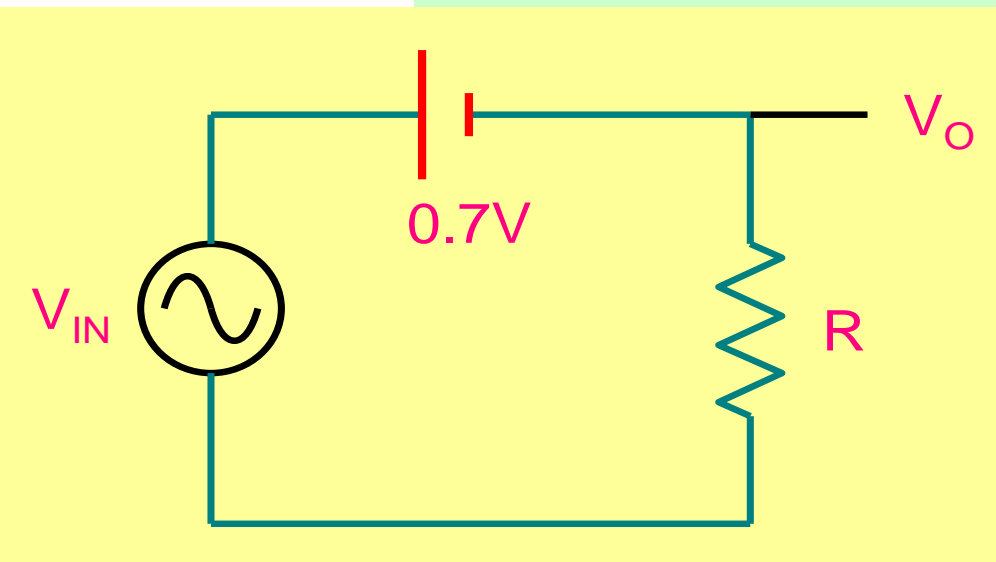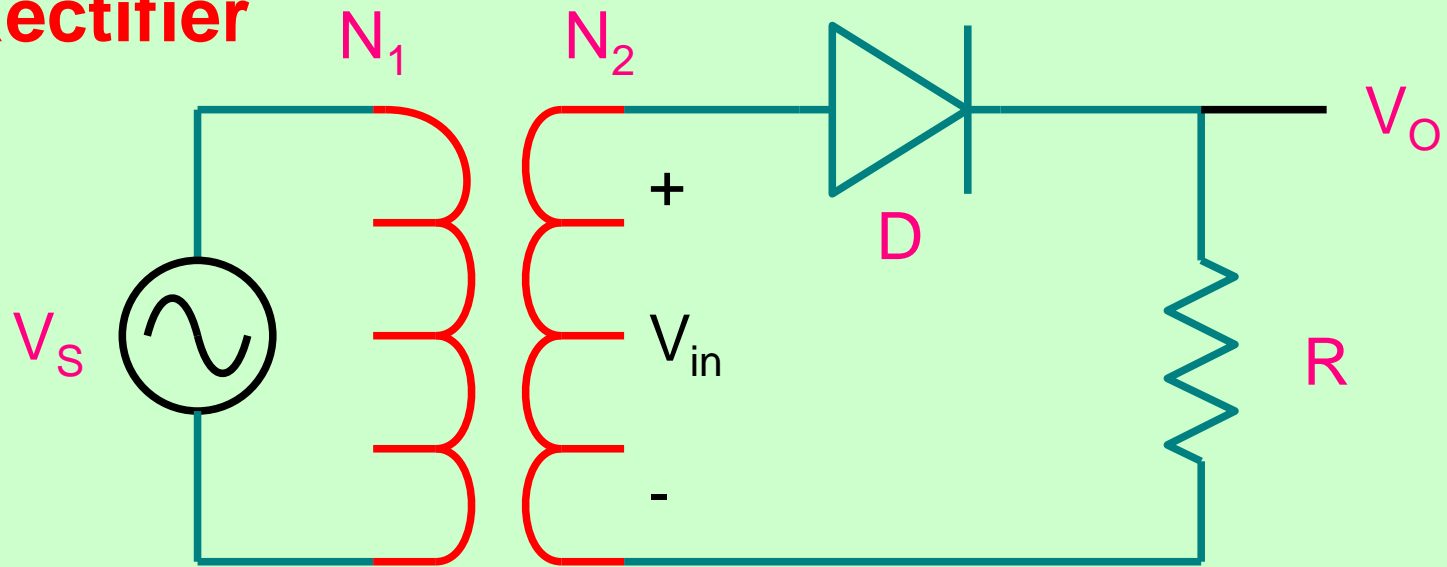



$$V_S = 220V \times \sqrt{2}$$

$$= 311.127V \text{ peak value}$$

For V_O to be 12V, the input V_{IN} should be ~12.7V




$$\frac{N_1}{N_2} = \frac{311}{12.7} = 24.5$$




$$V_o = V_{IN} - 0.7$$

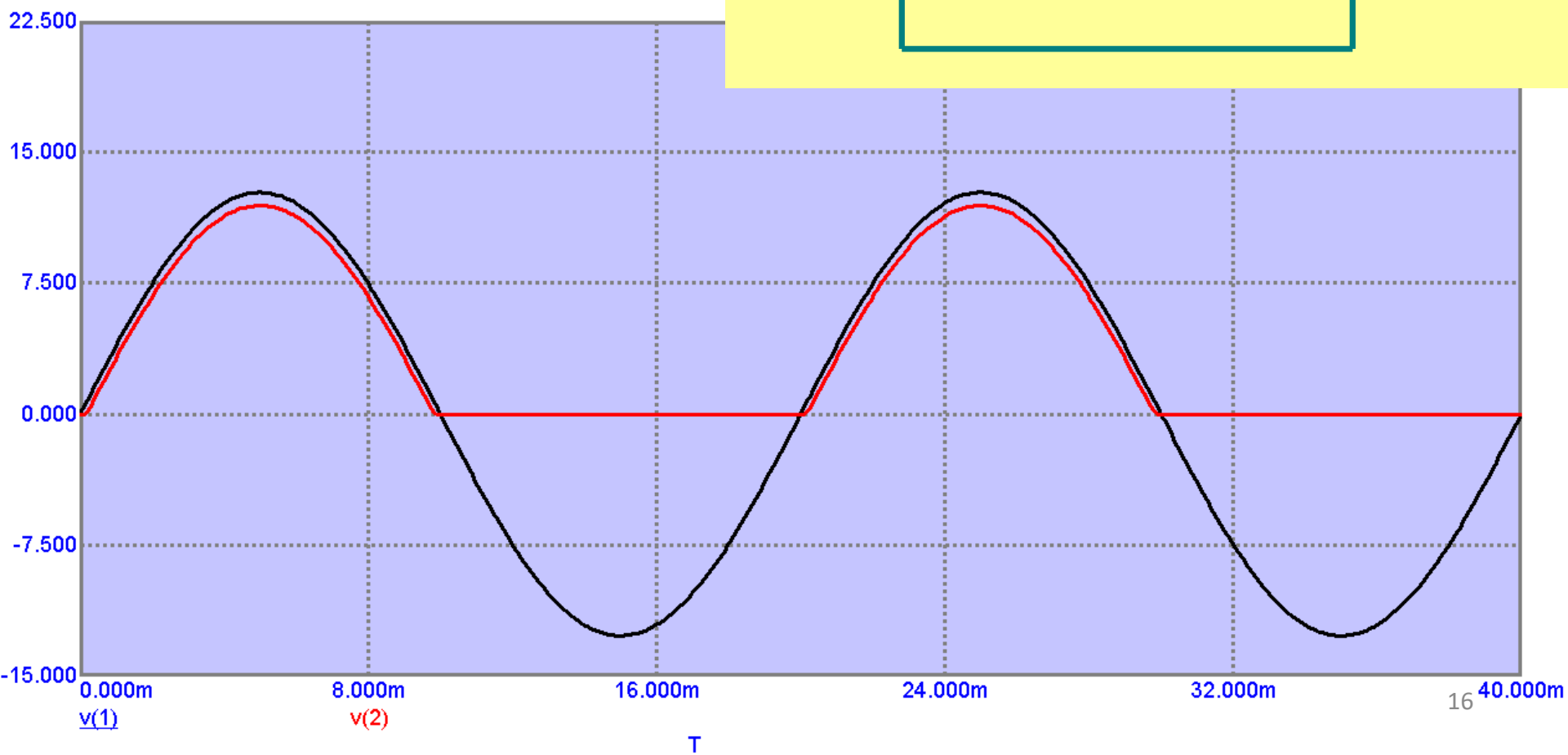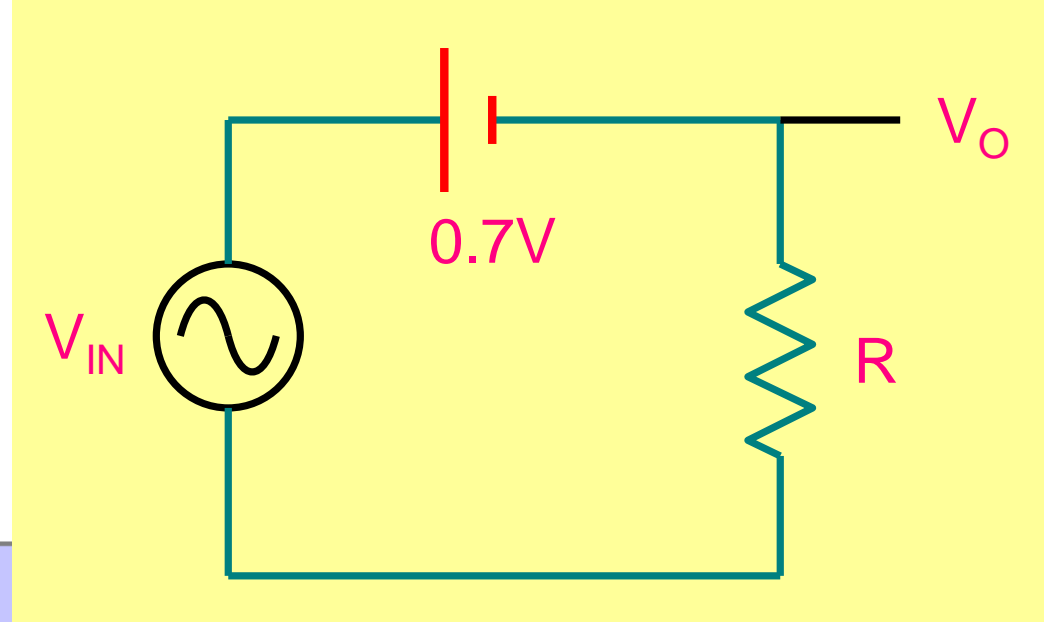


Zoomed view




$$V_o = V_{IN} - 0.7$$

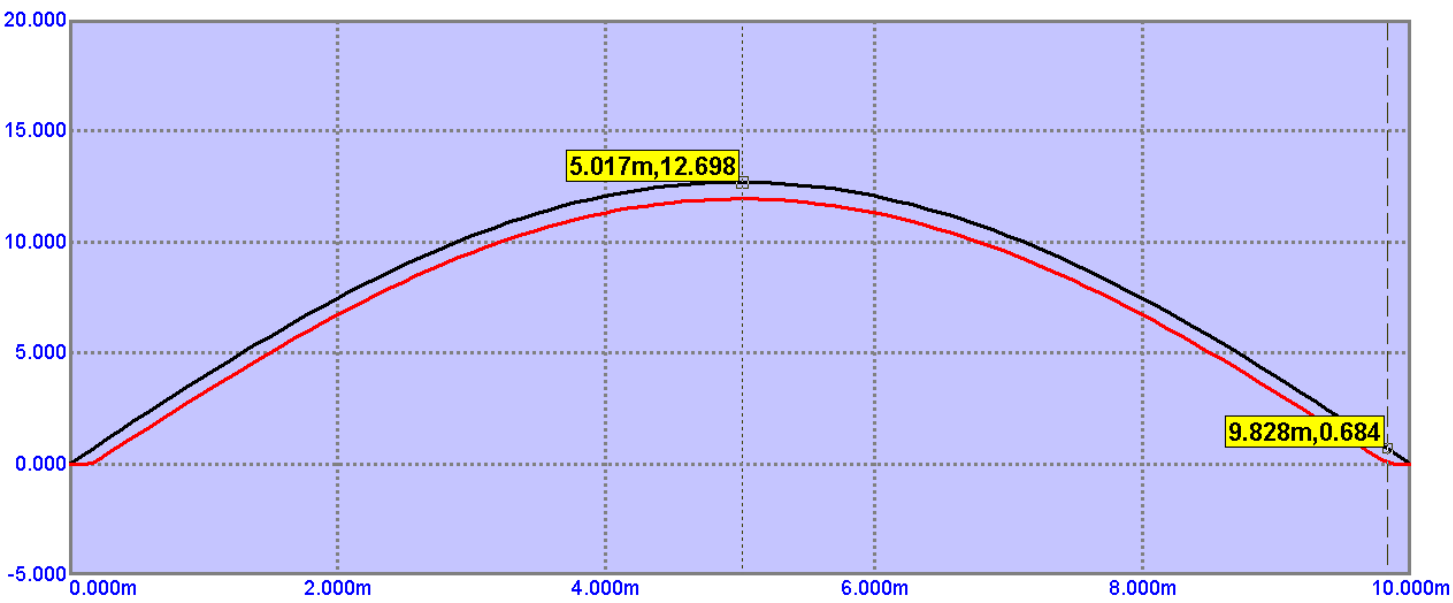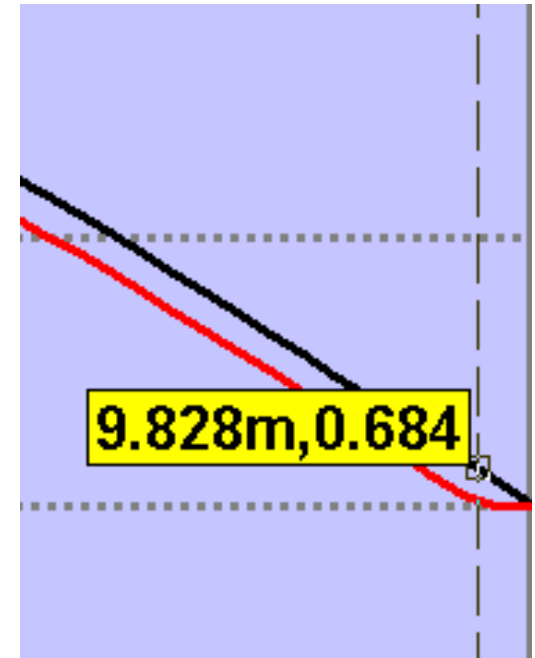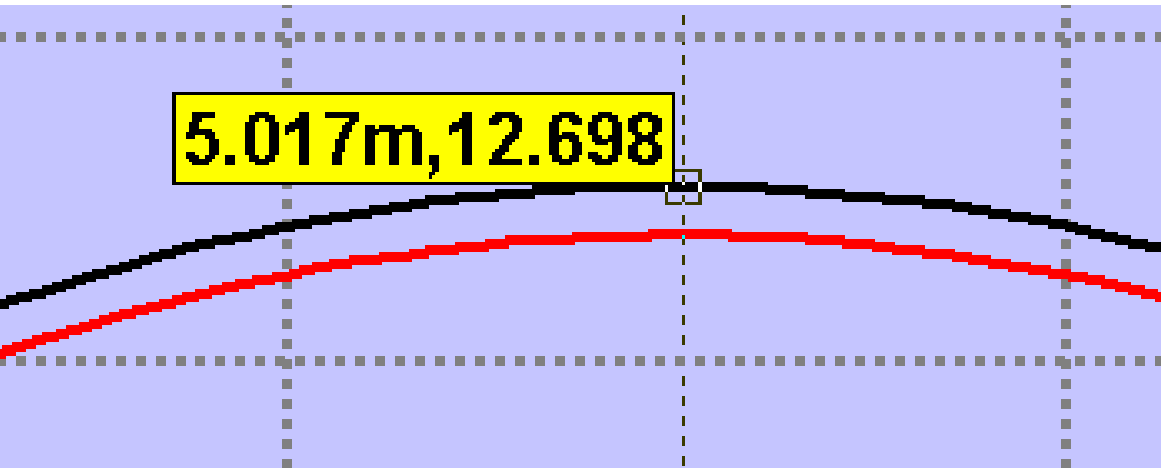

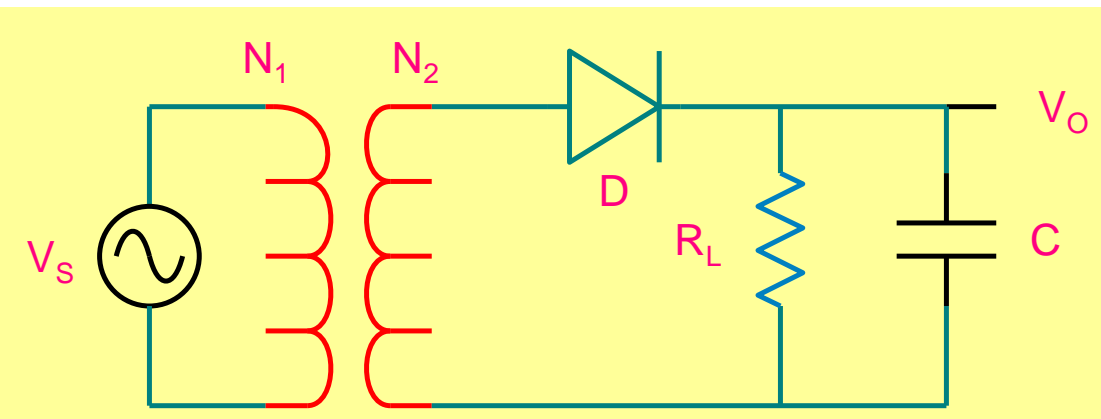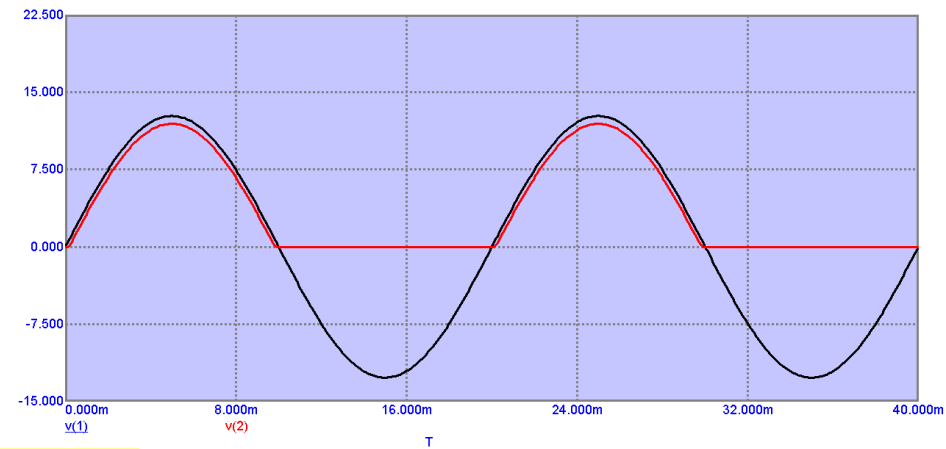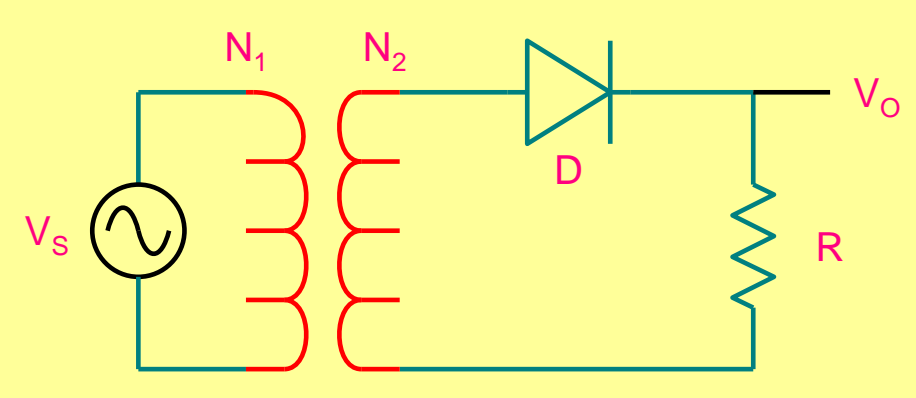

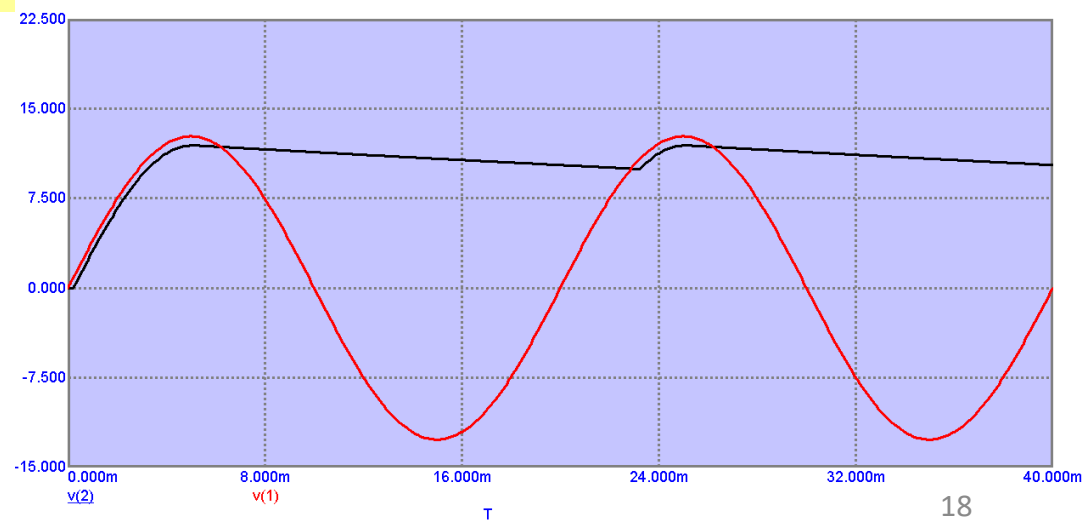Want to hold that voltage during negative half cycle




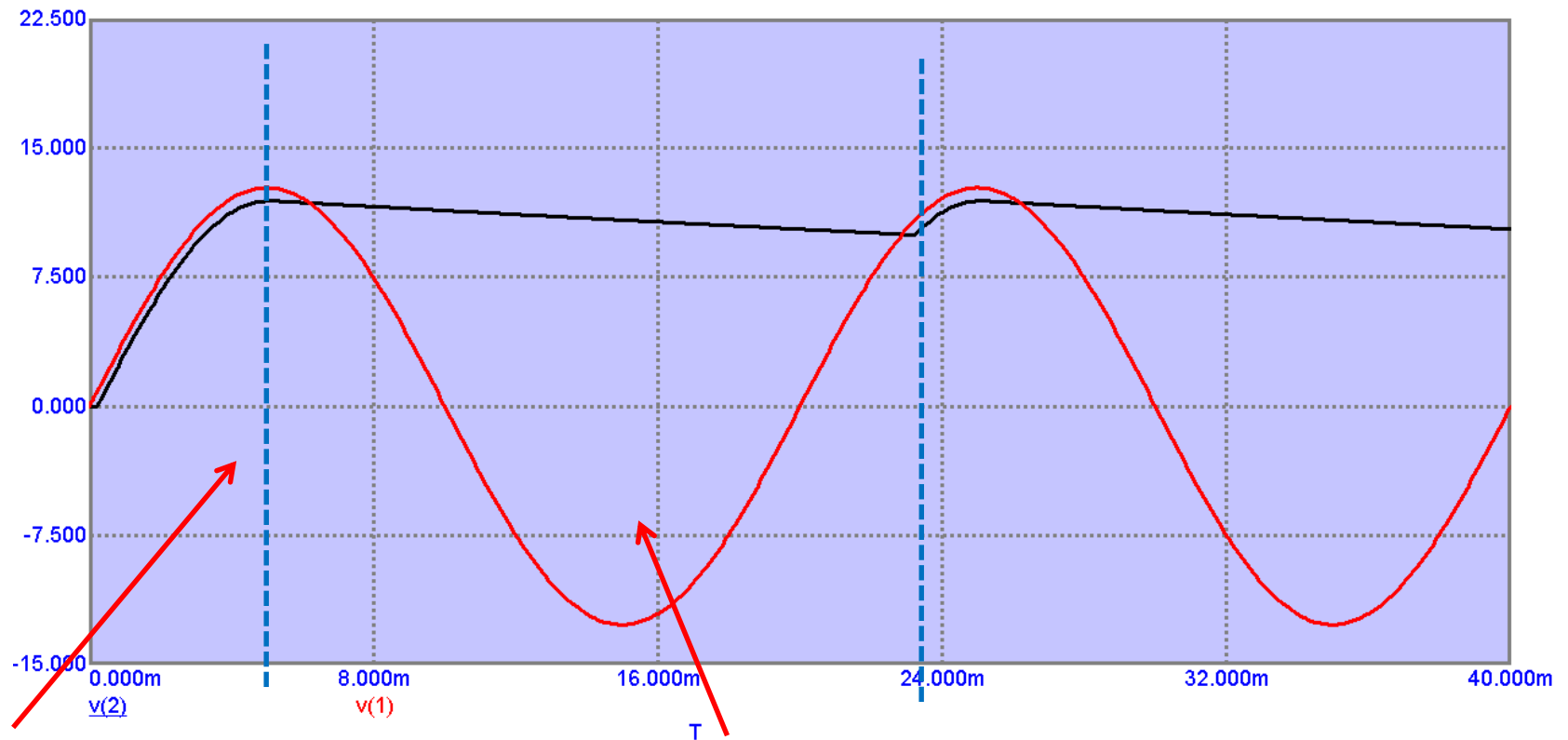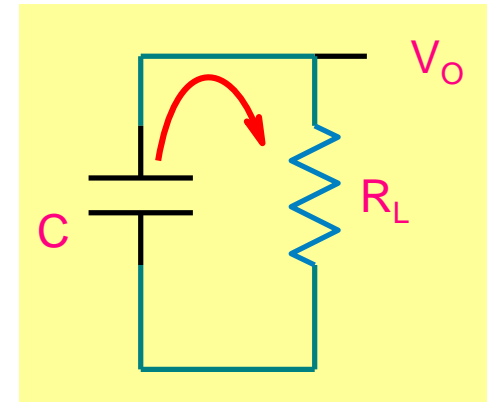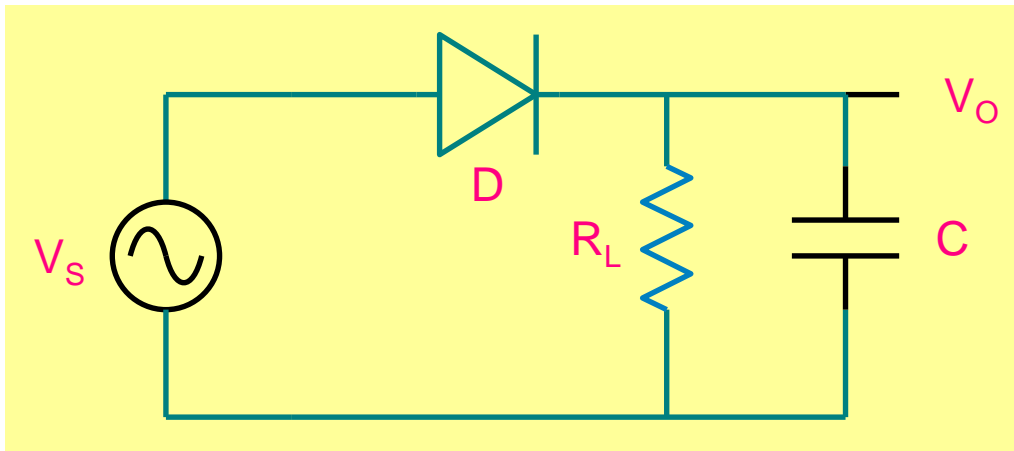

Diode is forward biased

Diode is reverse biased




Output has a ripple

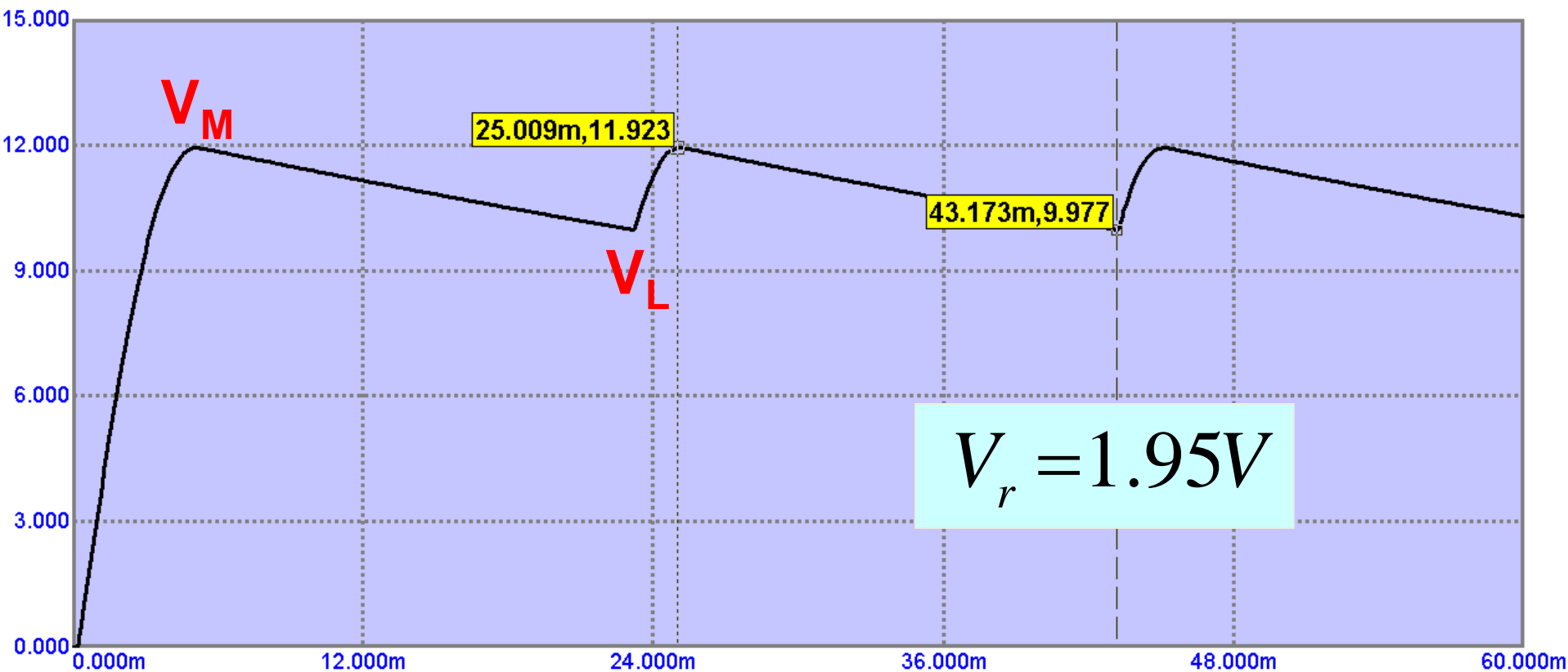

Ripple Voltage : $V_r = V_M - V_L$


Average Output Voltage : $V_o(avg) \cong V_M - \frac{V_R}{2}$

What does ripple voltage depend on?

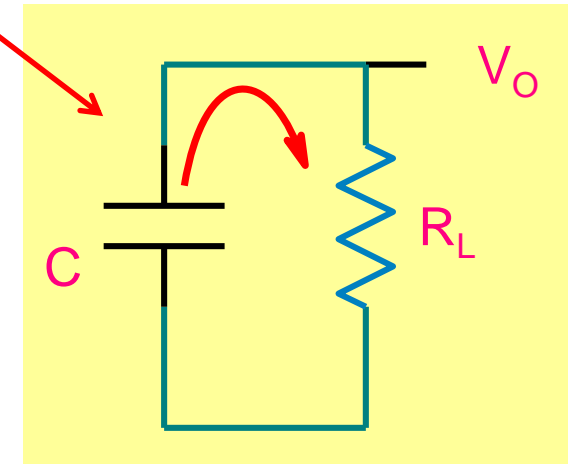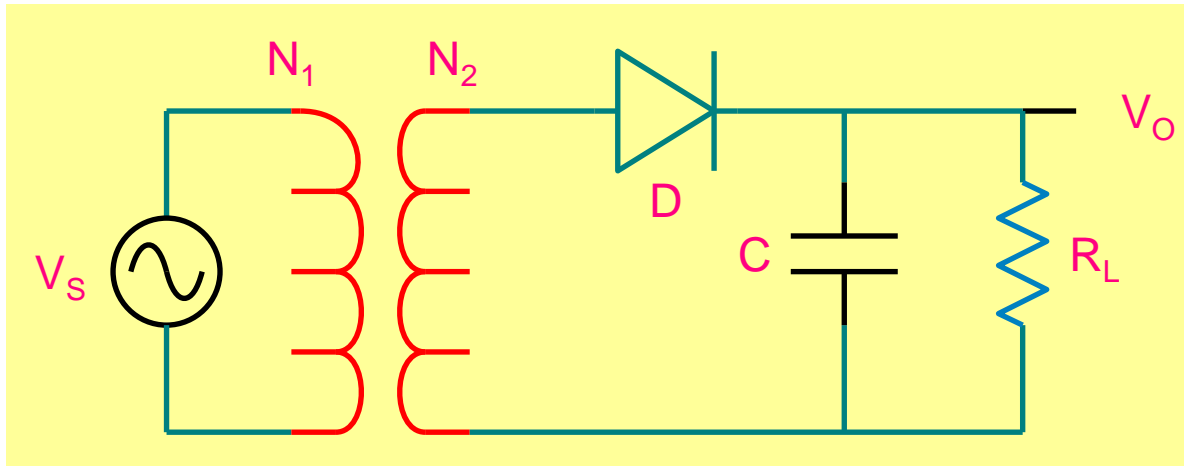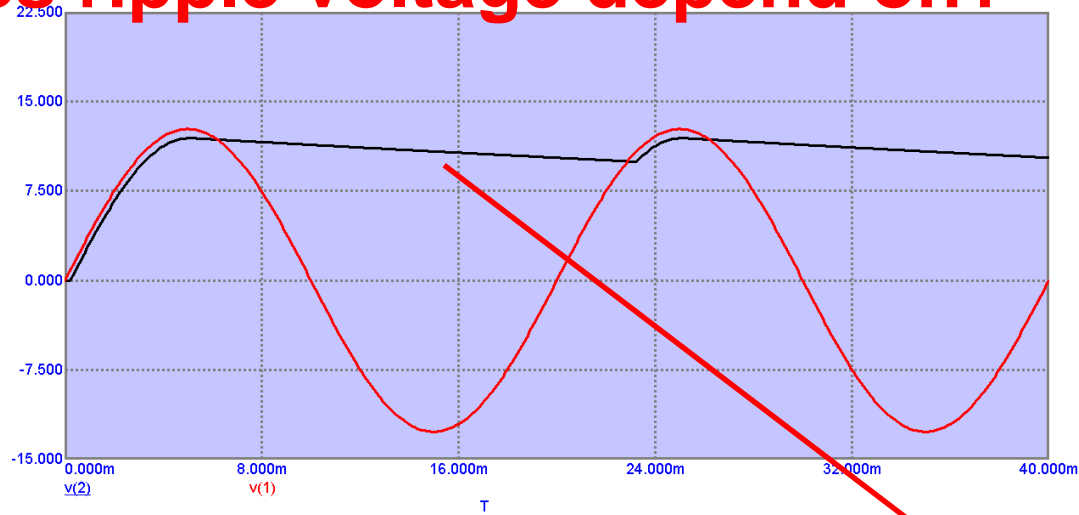

$$C \frac{dV_o}{dt} + \frac{V_o}{R_L} = 0 \Rightarrow \frac{dV_o}{dt} = -\frac{V_o}{R_L C}$$
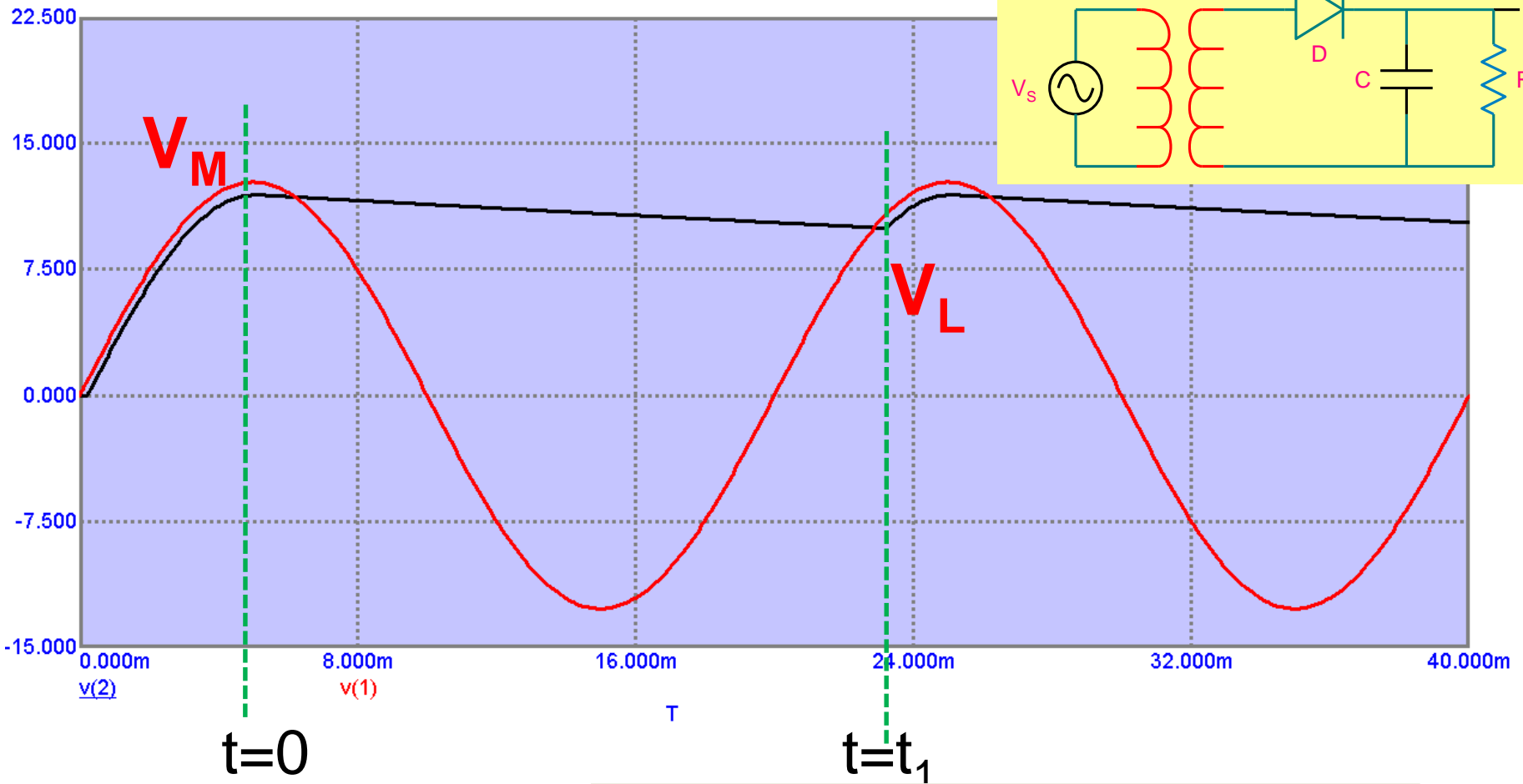
$$V_o(t) = V_M \times e^{-\frac{t}{R_L C}}$$




$$V_L = V_M \times e^{-\frac{t_1}{R_L C}}$$

$$V_r = V_M - V_L = V_M \times (1 - e^{-\frac{t_1}{R_L C}})$$

Assuming that $t_1 \ll R_L C$
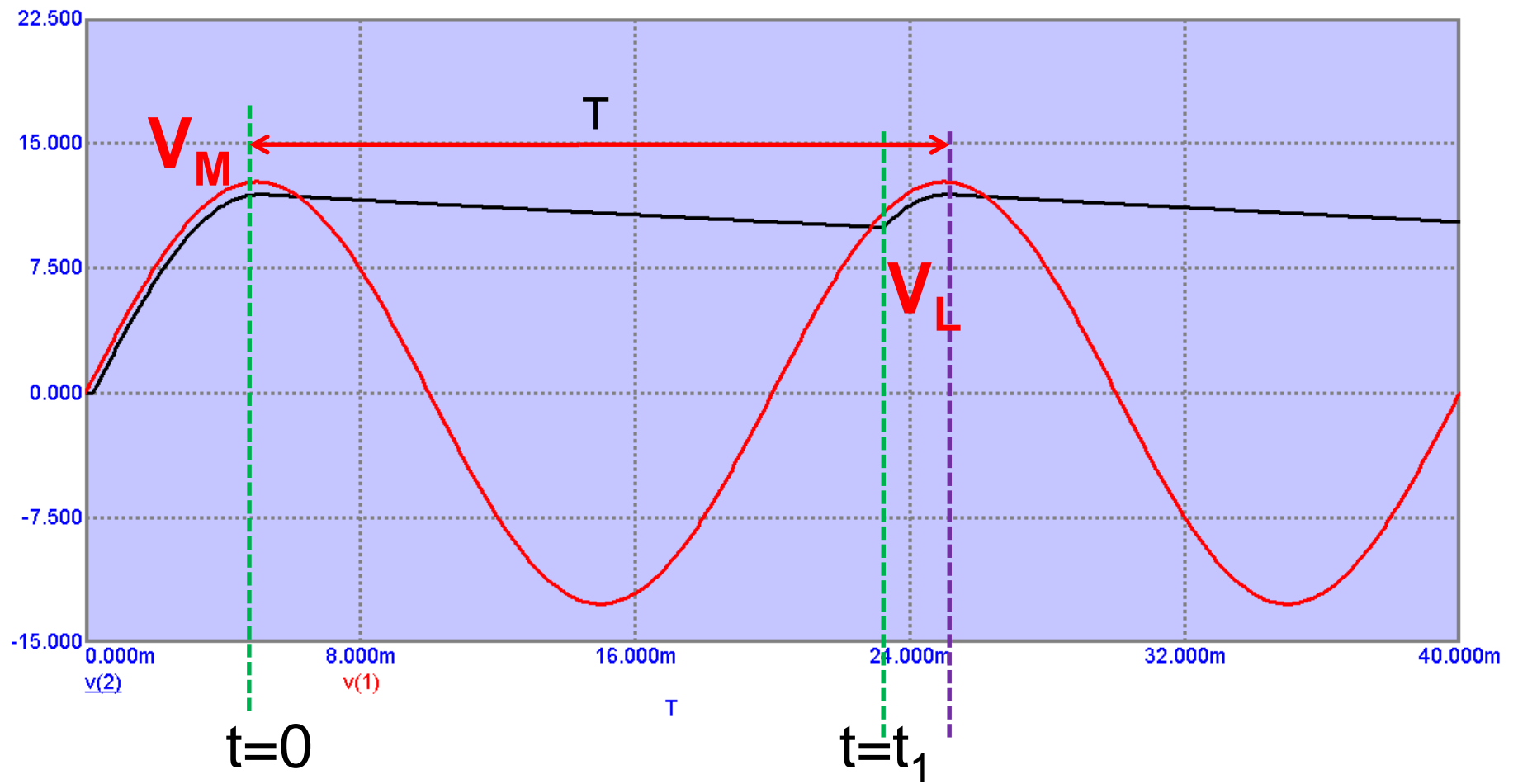
$$V_r \cong V_M \times \left\{ 1 - \left(1 - \frac{t_1}{R_L C} \right) \right\} = \frac{V_M t_1}{R_L C}$$





$$t_1 \cong T$$

$$V_r = \frac{V_M t_1}{R_L C} \cong \frac{V_M T}{R_L C}$$

$$V_r \cong \frac{V_M}{f R_L C}$$



Example

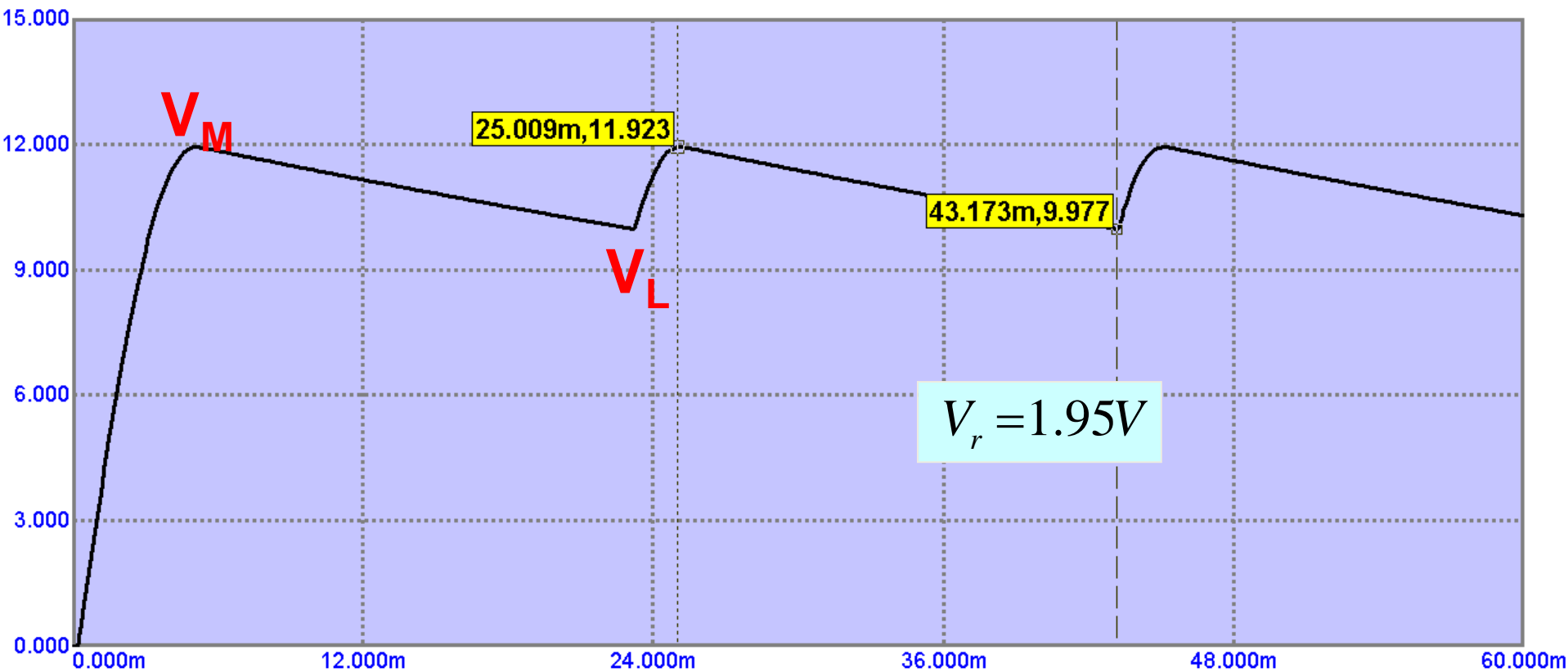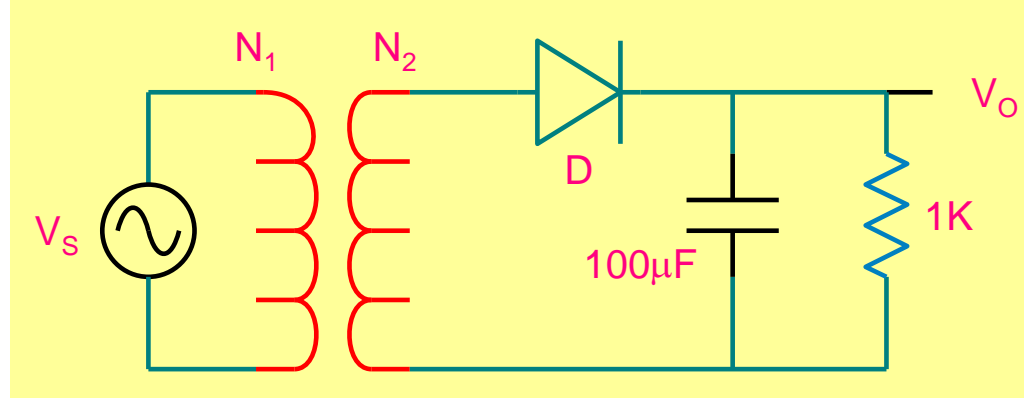

$$V_r \cong \frac{V_M}{fR_L C} = \frac{11.923}{50 \times 10^3 \times 100 \times 10^{-6}} = 2.385V$$

$$\frac{R_L C}{T} = 5$$

Example

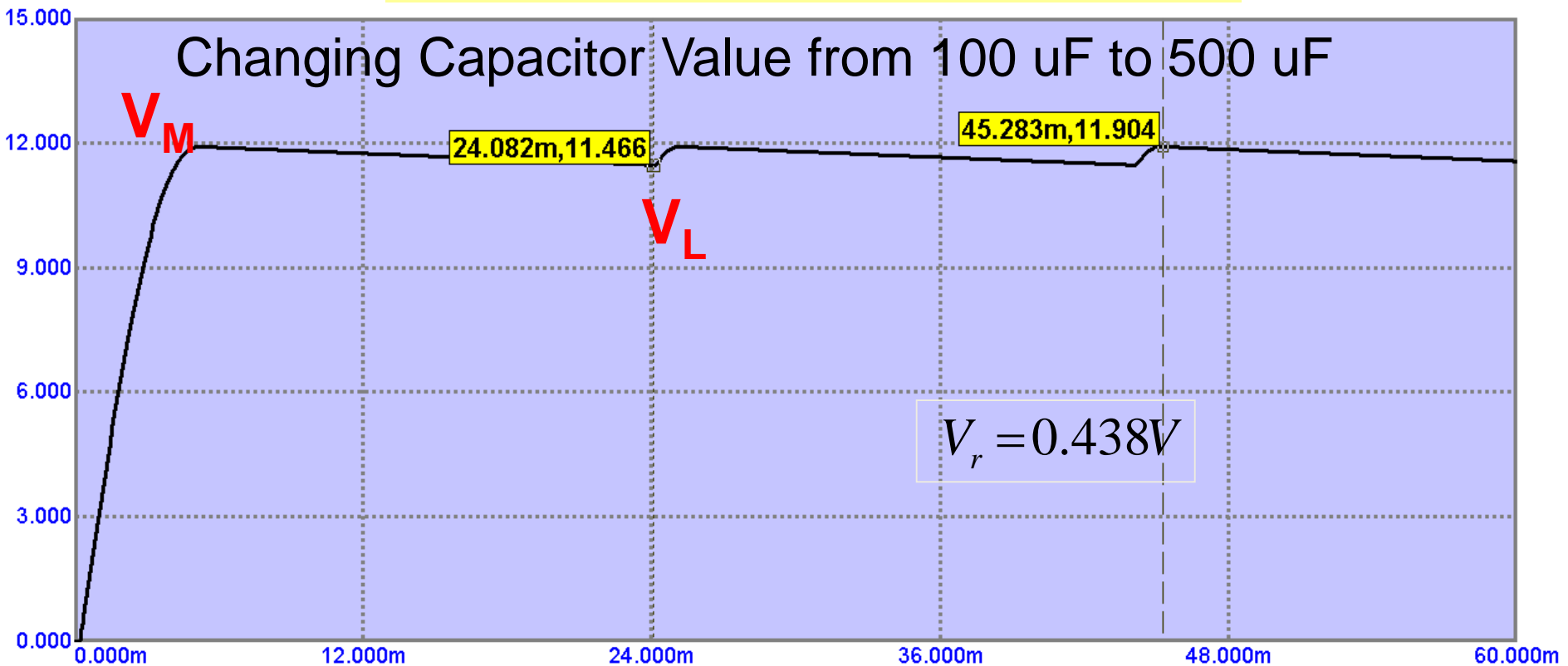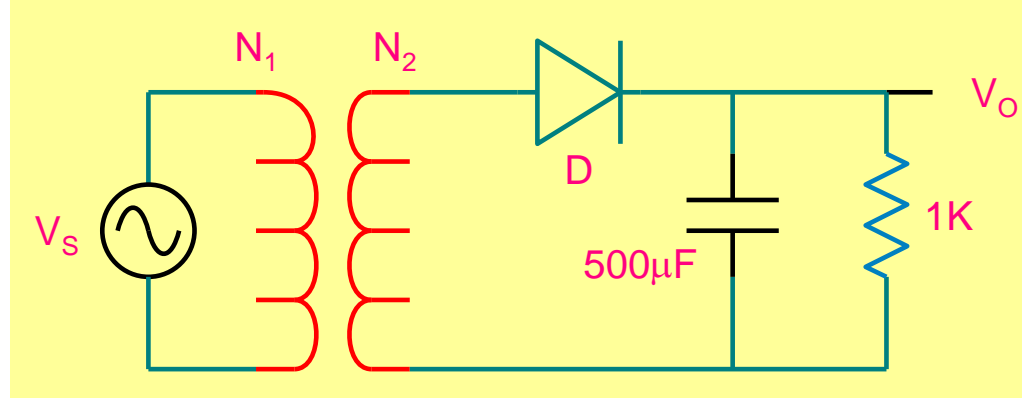


$$V_r \cong \frac{V_M}{fR_L C} = \frac{11.904}{50 \times 10^3 \times 500 \times 10^{-6}} = 0.476V$$

$$\frac{R_L C}{T} = 25$$

Design Example

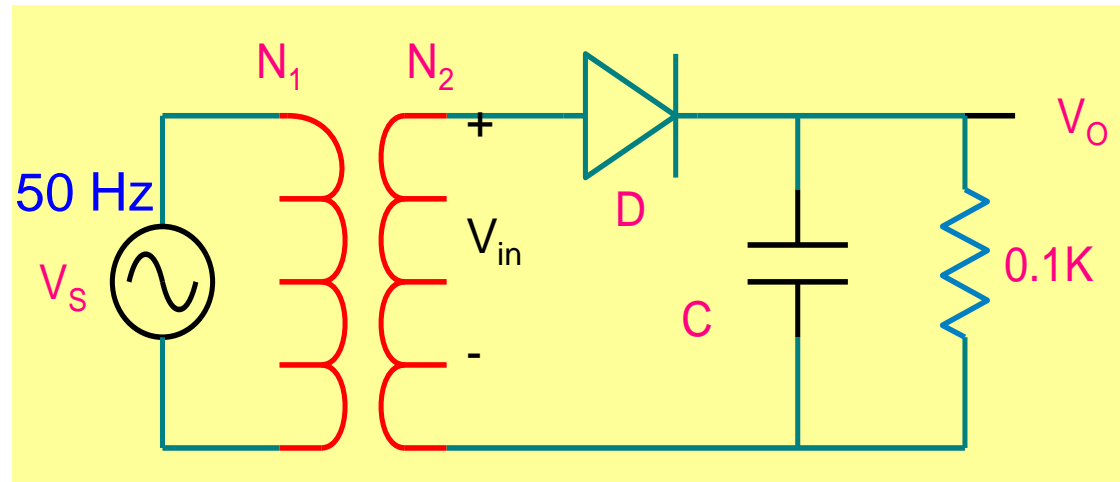Design a power supply that will supply 6V to a load of 100Ω with ripple voltage less than 0.1V.




For V_o to be 6V, the input V_{in} should be $\sim 6.7V$ $\frac{N_1}{N_2} = \frac{311.127}{6.7} = 46.4$


$$V_r \cong \frac{V_M}{fR_L C} = 0.1 \Rightarrow C = 12mF$$

How do we choose a diode for this application?

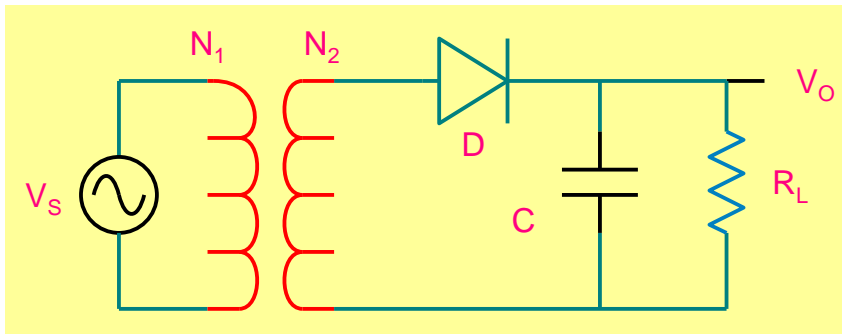
How do we choose a diode for this application?



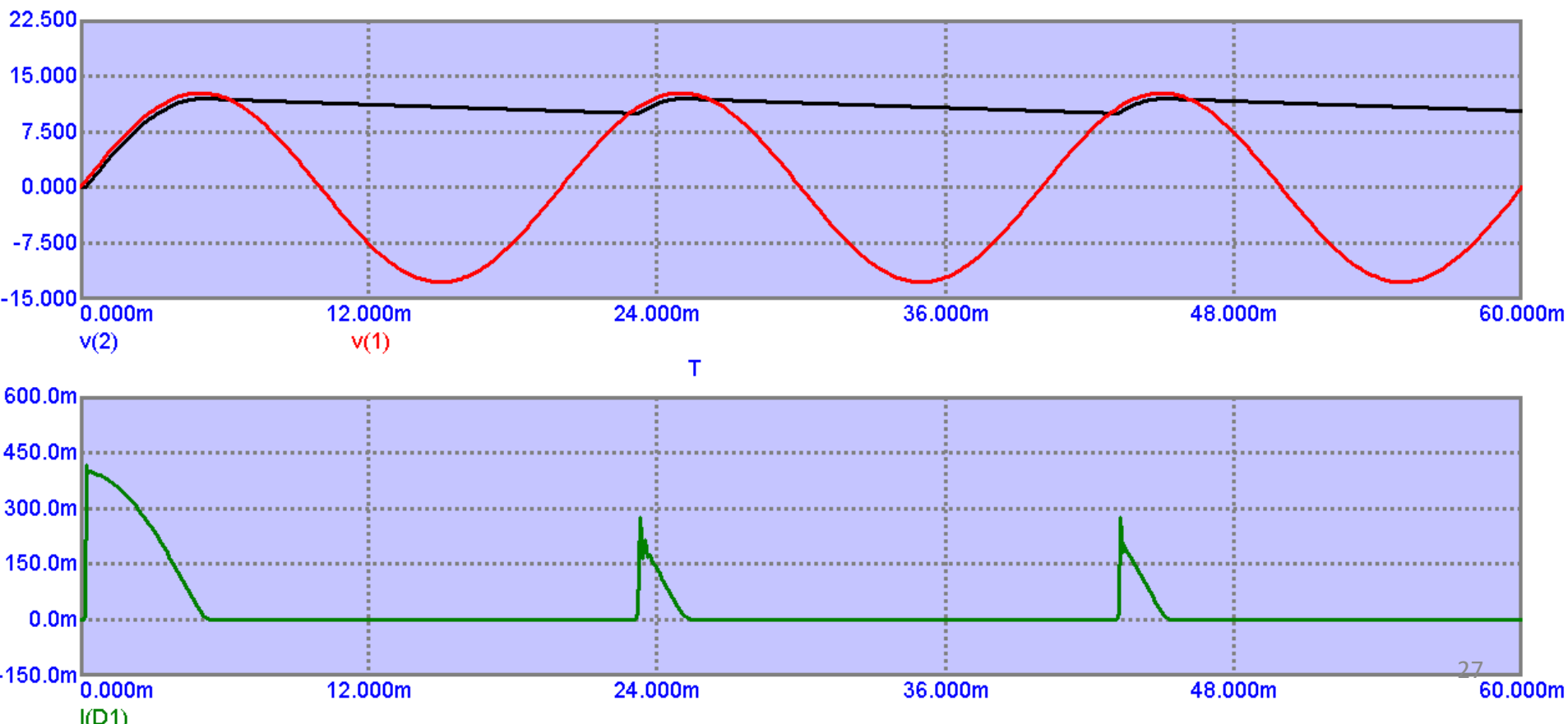
Peak diode current, average diode current and peak inverse voltage



Diode forward bias current

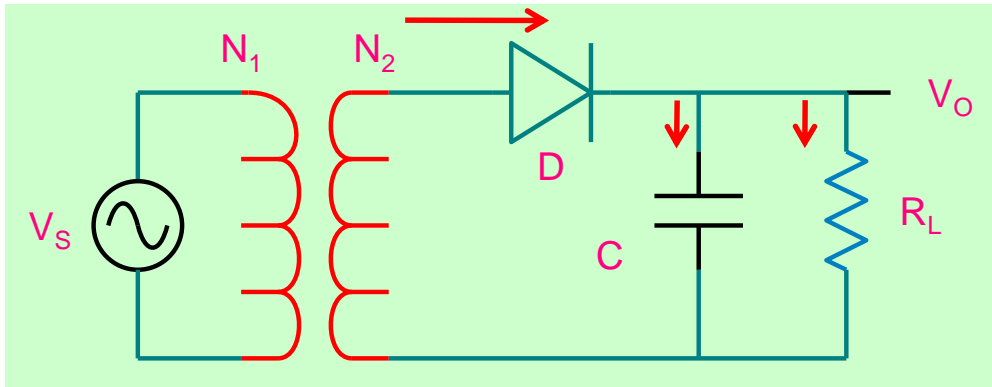

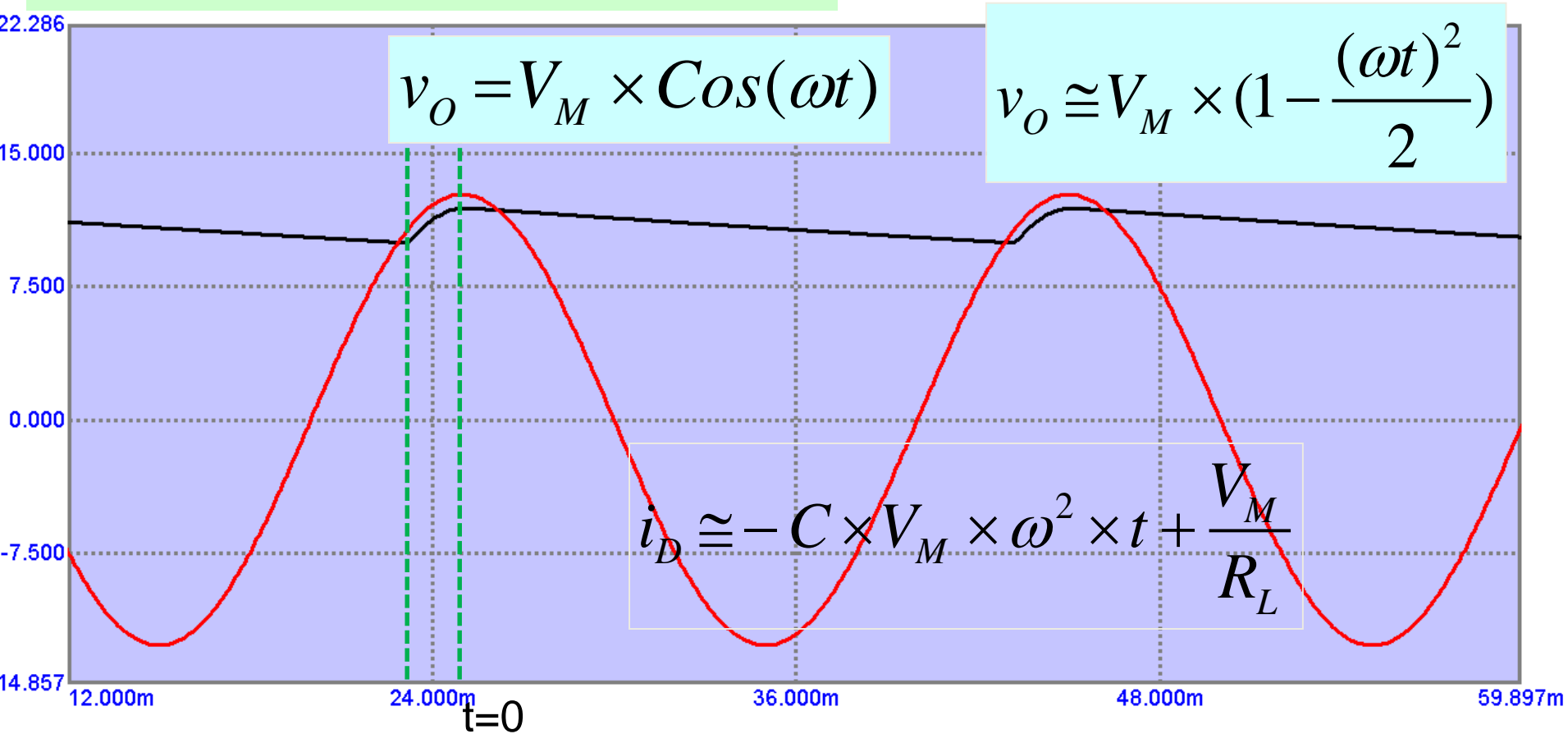
$$i_D = C \times \frac{dv_o}{dt} + \frac{v_o}{R_L}$$



$$v_O \cong V_M \times \left(1 - \frac{(\omega t)^2}{2}\right)$$
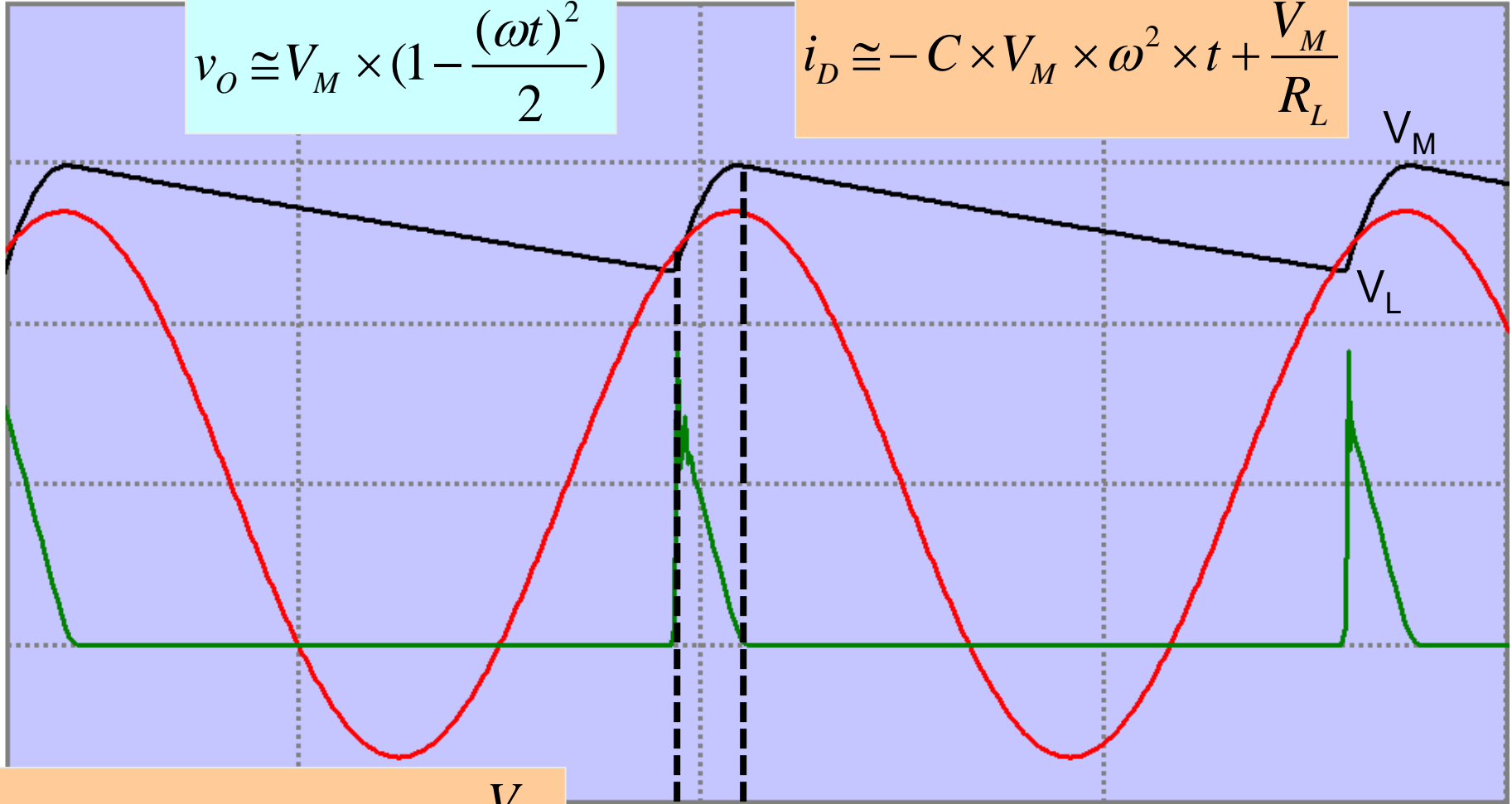
$$i_D \cong -C \times V_M \times \omega^2 \times t + \frac{V_M}{R_L}$$



$$i_{D\max} \cong C \times V_M \times \omega^2 \times \Delta t + \frac{V_M}{R_L} \quad t = -\Delta t \quad t = 0$$

$$V_L \cong V_M \times \left(1 - \frac{(\omega \Delta t)^2}{2}\right) \Rightarrow \Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_M}}$$

$$i_{D\max} \cong \omega C \times \sqrt{2V_r V_M} + \frac{V_M}{R_L}$$

Peak Diode Current

$$i_{D\max} \cong \omega C \times \sqrt{2V_r V_M} + \frac{V_M}{R_L}$$


$$V_r \cong \frac{V_M}{fR_L C}$$

$$\Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_M}}$$

$$i_{D\max} = \frac{V_M}{R_L} \left[1 + 2\pi \sqrt{\frac{2V_M}{V_r}} \right]$$

Average Diode Currents

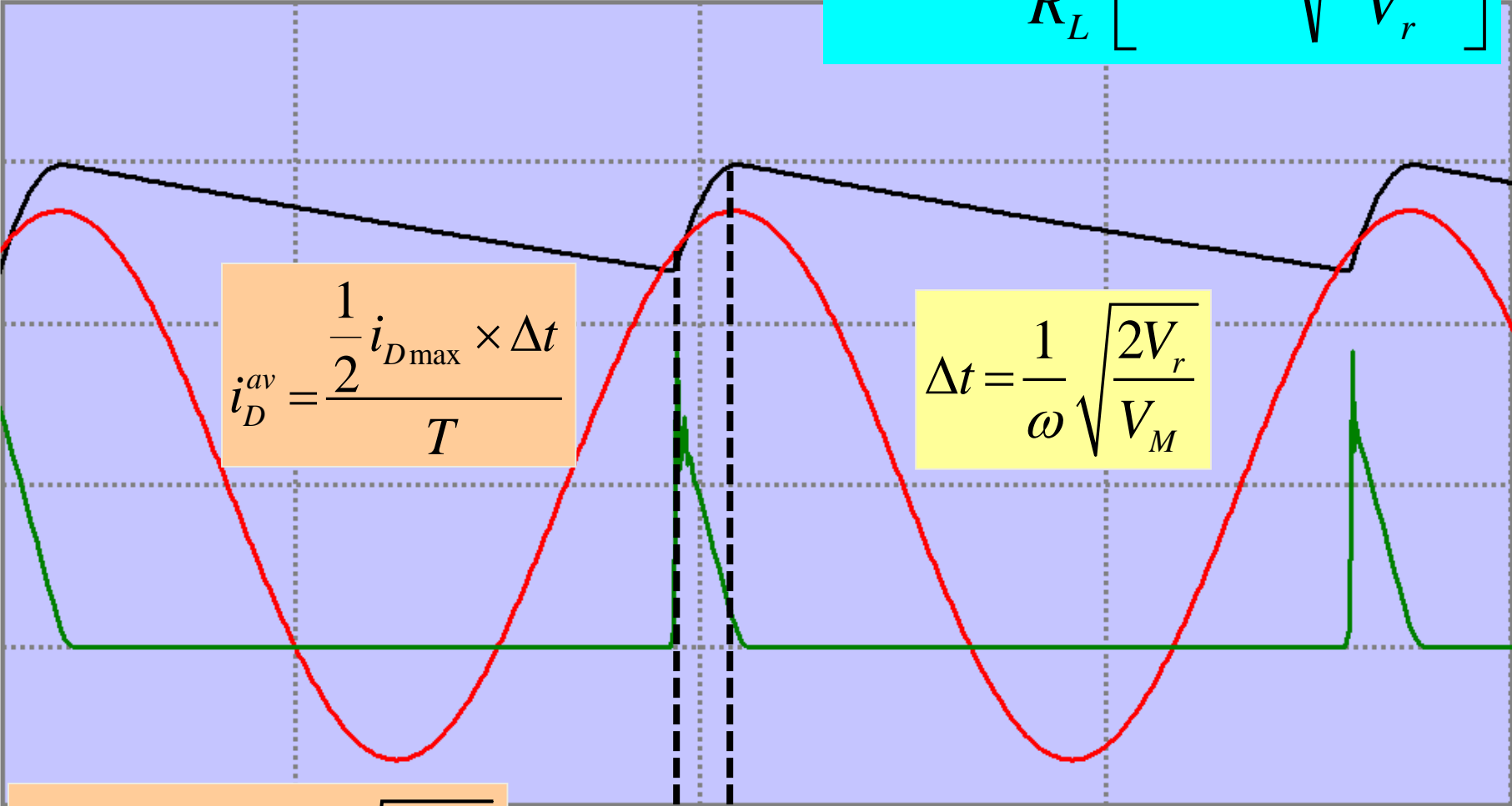
$$i_{D\max} = \frac{V_M}{R_L} \left[1 + 2\pi \sqrt{\frac{2V_M}{V_r}} \right]$$



$$i_D^{av} = \frac{i_{D\max}}{4\pi} \times \sqrt{\frac{2V_r}{V_M}}$$

$$i_D^{av} = \frac{V_M}{R_L} + \frac{\sqrt{2V_r V_M}}{4\pi R_L} \cong \frac{V_M}{R_L}$$



Peak and Average Diode Currents

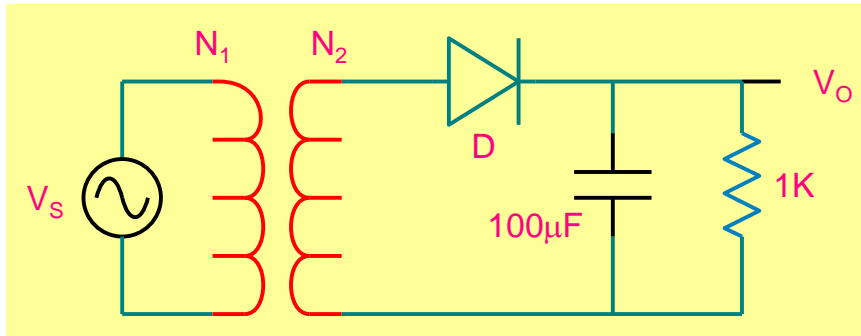

$$V_r = 1.95\text{V}$$

$$i_D^{av} \cong \frac{V_M}{R_L} = 12\text{mA}$$


$$i_{D\max} \cong 250\text{mA}$$

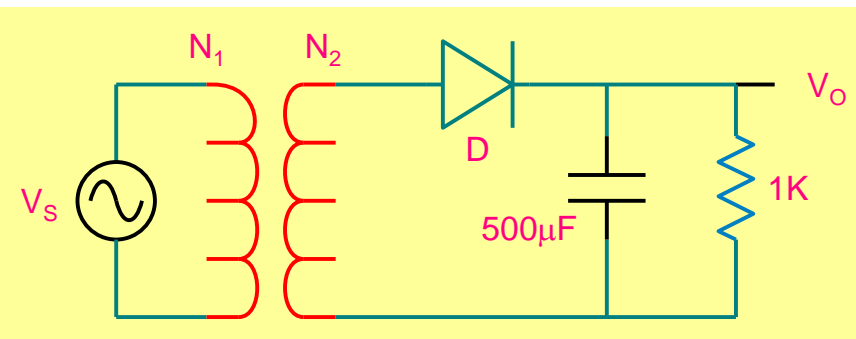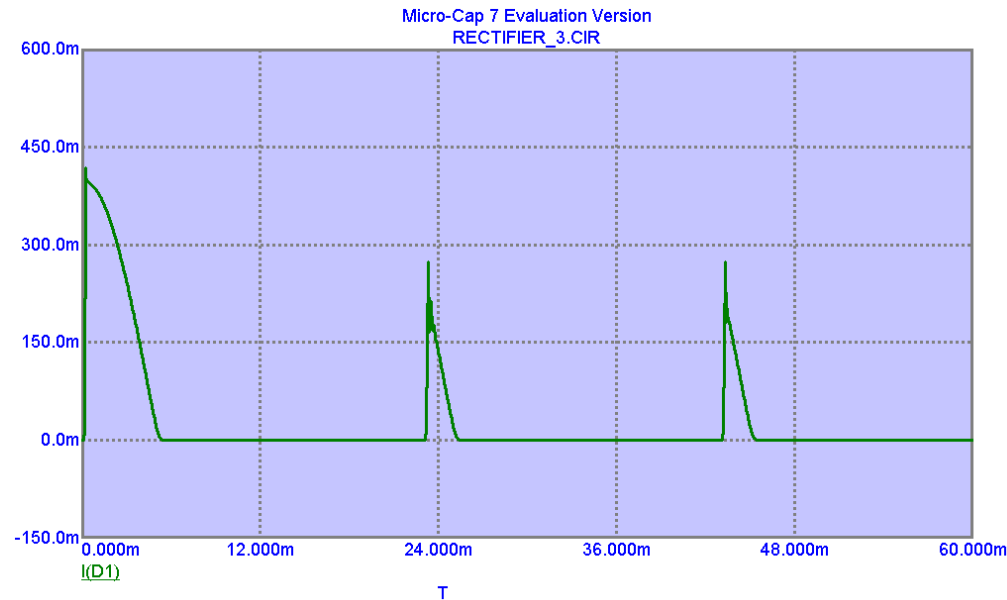

$$V_r = 0.438\text{V}$$



$$i_D^{av} \cong \frac{V_M}{R_L} = 12\text{mA}$$

$$i_{D\max} \cong 545\text{mA}$$

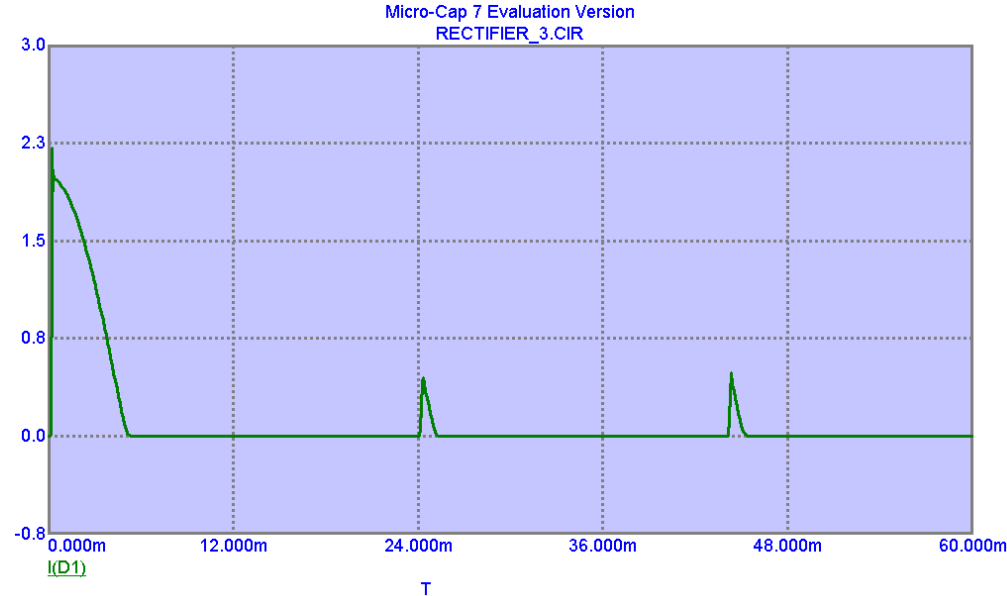


Peak diode current increases as ripple reduces³²

Peak Inverse Voltage

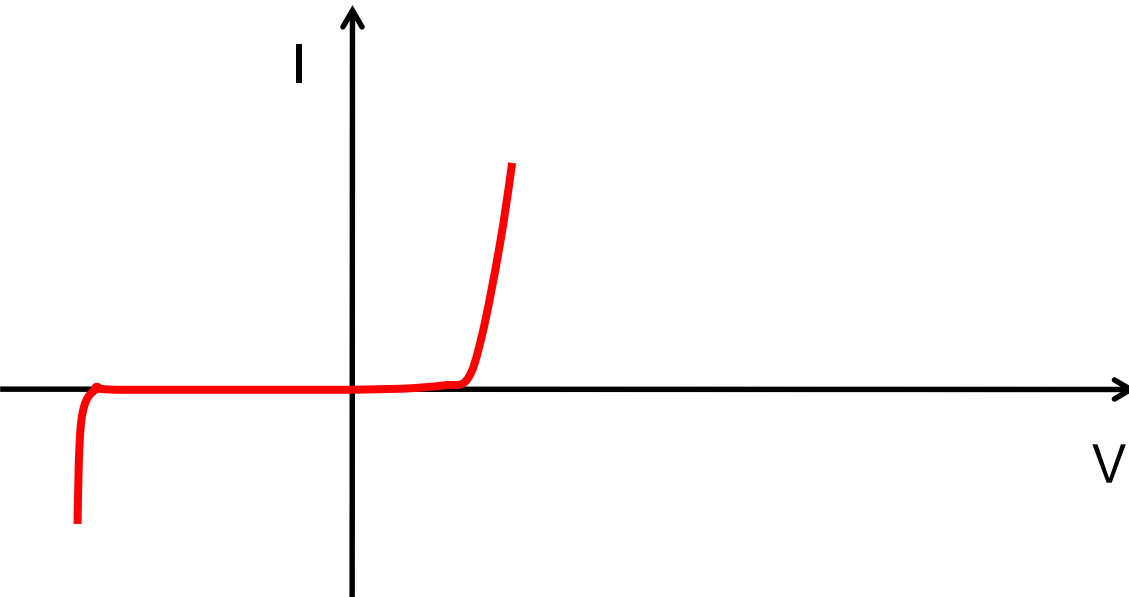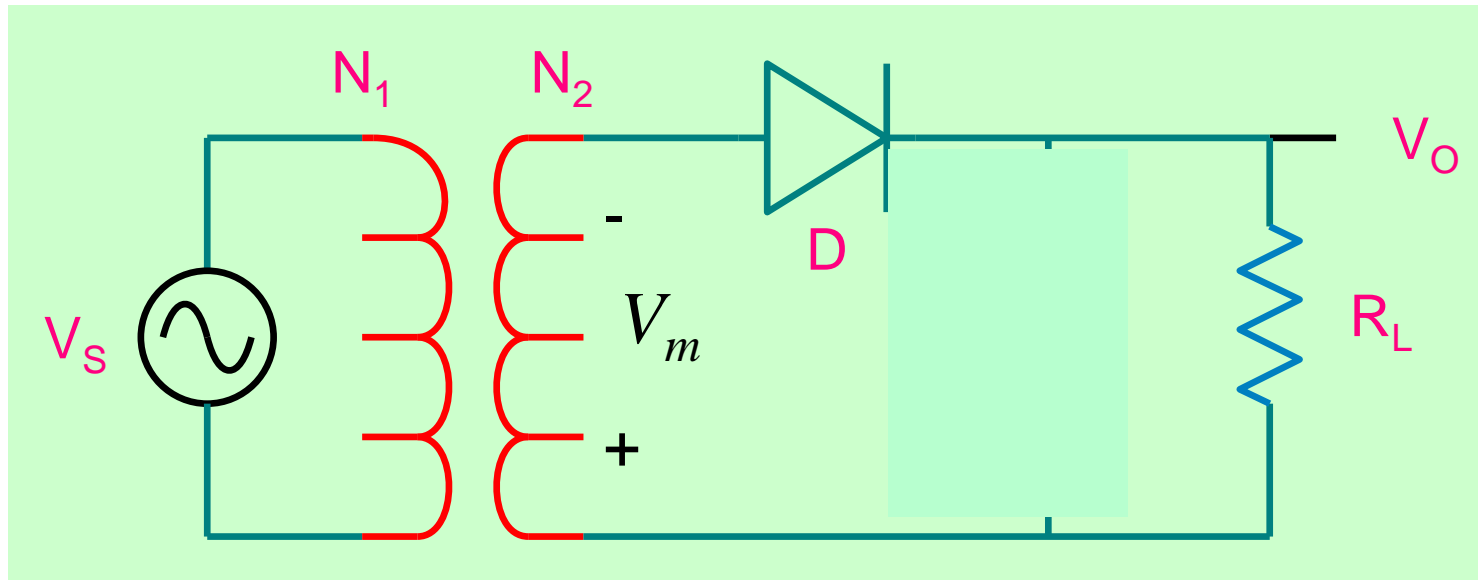

$$PIV = V_m$$

Peak Inverse Voltage

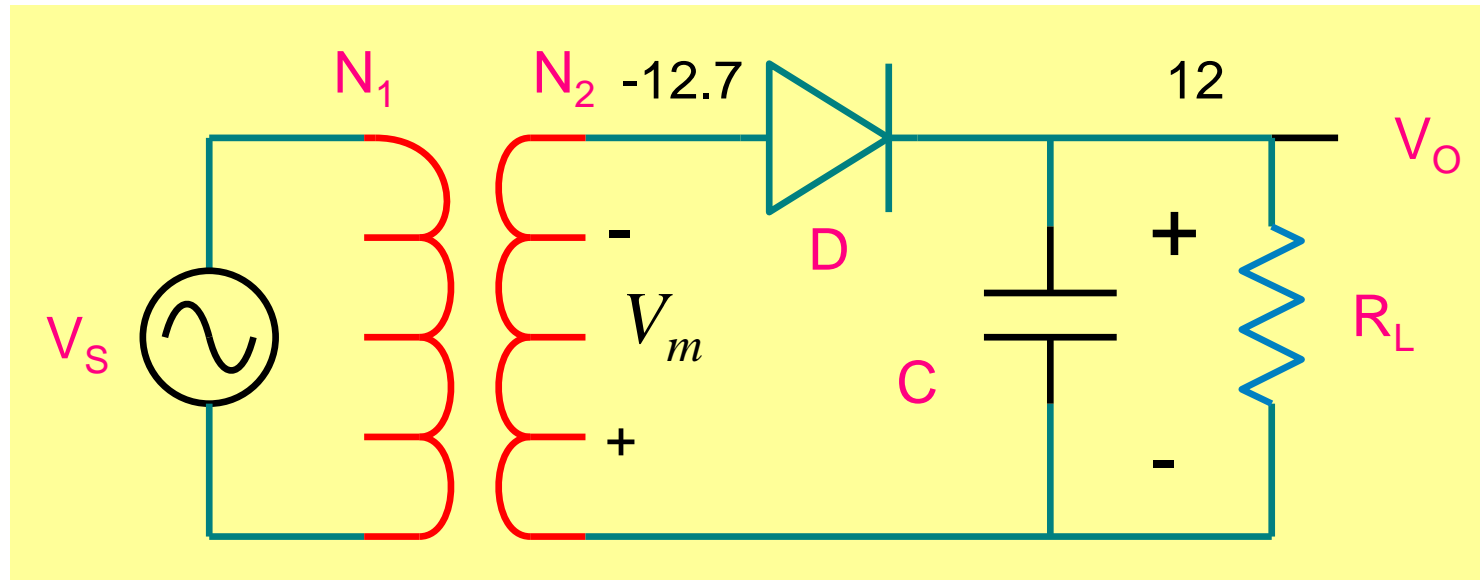

$$V_m = 12.7$$

$$12 + 12.7 = 24.7V$$

$$PIV \cong 2v_o + 0.7$$

$$PIV = 2V_M + V_\gamma$$