


# **ESc201 : Introduction to Electronics**

## **Sinusoidal Steady state Analysis**

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur
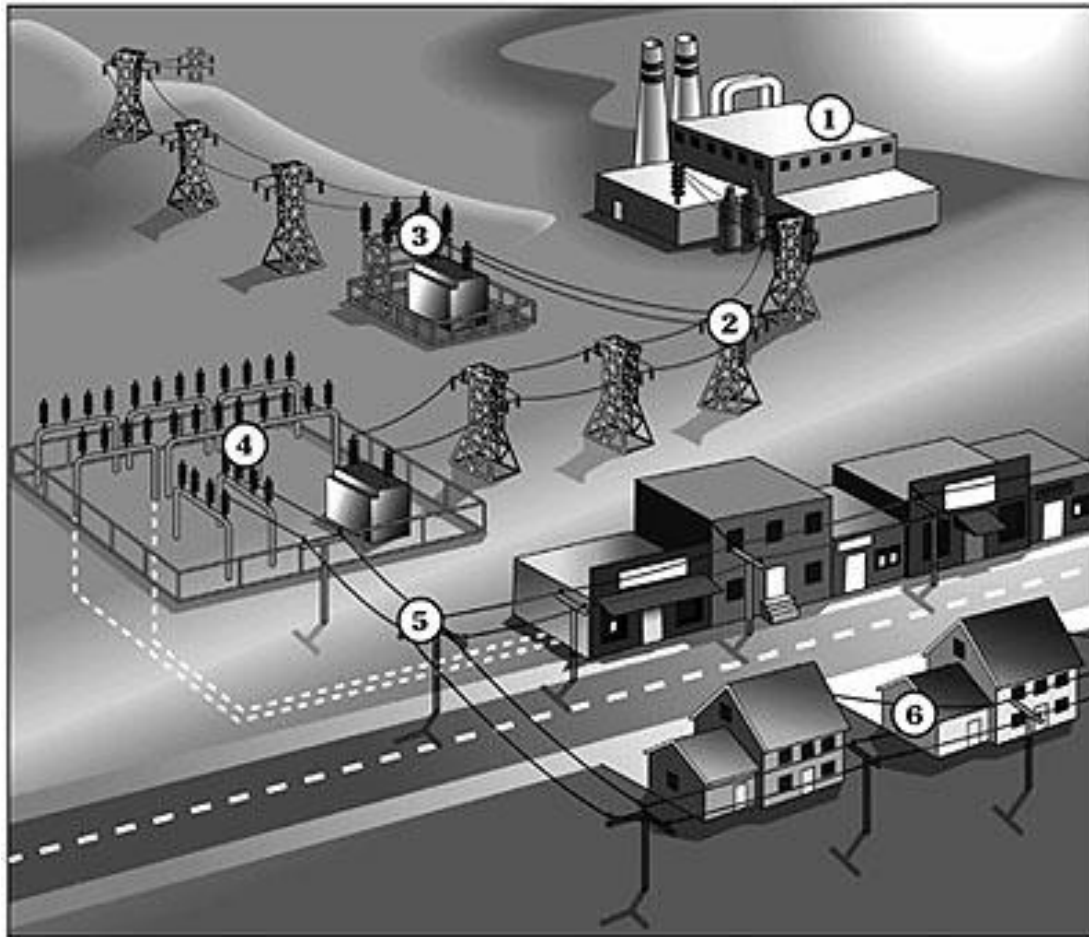
# Importance of Sinusoidal Sources

- Appear in many practical applications
  - Electric power is distributed by sinusoidal currents and voltages
  - Sinusoidal signals are used widely in radio communications




$$Loss = i^2 R_{wire}$$

$$p = v \times i$$

$$2.2KW = 2.2KV \times 1A$$

$$2.2KW = 220V \times 10A$$

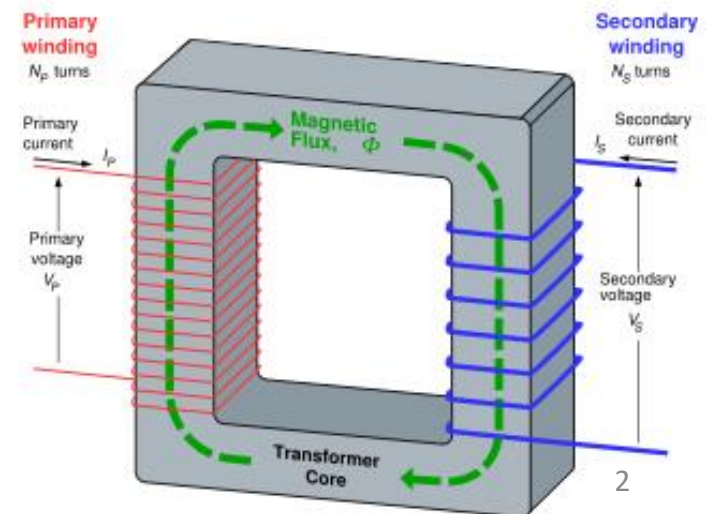

# Communication




20 Hz -20KHz


From Computer Desktop Encyclopedia  
© 2007 The Computer Language Co., Inc.




Carrier

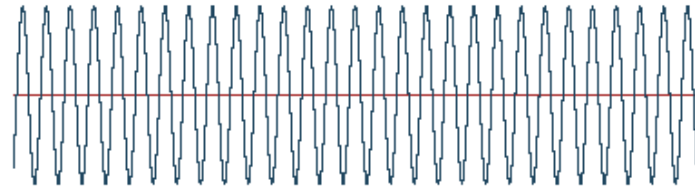


Modulating Wave

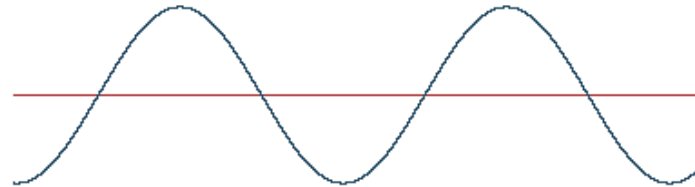

Modulated Result

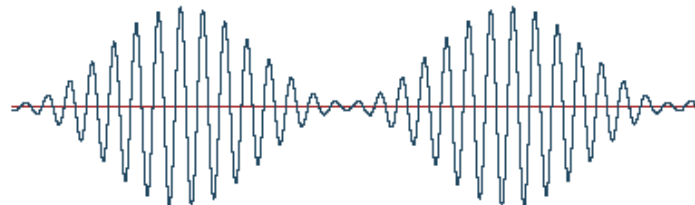

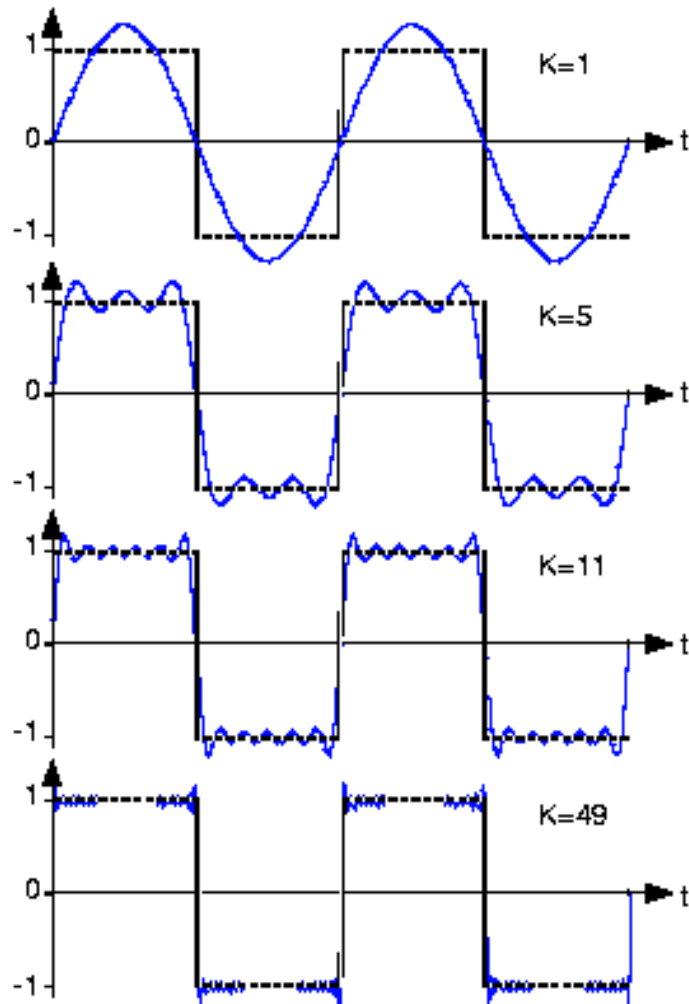- Any signal can be represented by a sum of sinusoidal components (Fourier Analysis)



$$f(t) = \frac{4}{\pi} \sum_{n=1,3,5}^{\infty} \frac{1}{n} \sin\left(\frac{n\pi t}{T}\right)$$

- Sinusoids have good mathematical properties
  - Derivative is a sinusoid
  - Integral is a sinusoid

$$\frac{d(\sin x)}{dx} = \cos x = \sin(90 - x)$$





$$i_c = C \frac{dv_c}{dt}$$



$$\int \sin x \, dx = -\cos x = \sin(x - 90)$$

$$v = L \frac{di}{dt}$$


So as a sinusoidal signal goes through a circuit, it remains a sinusoid

This makes analysis easier

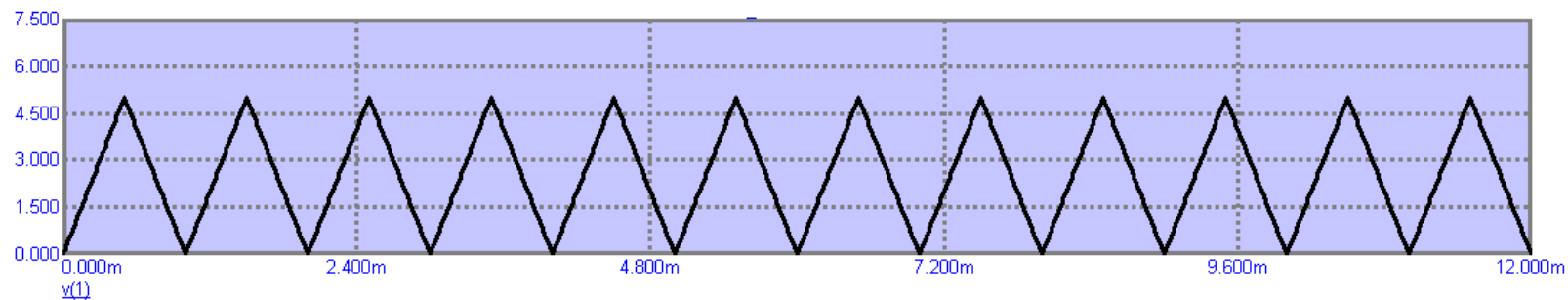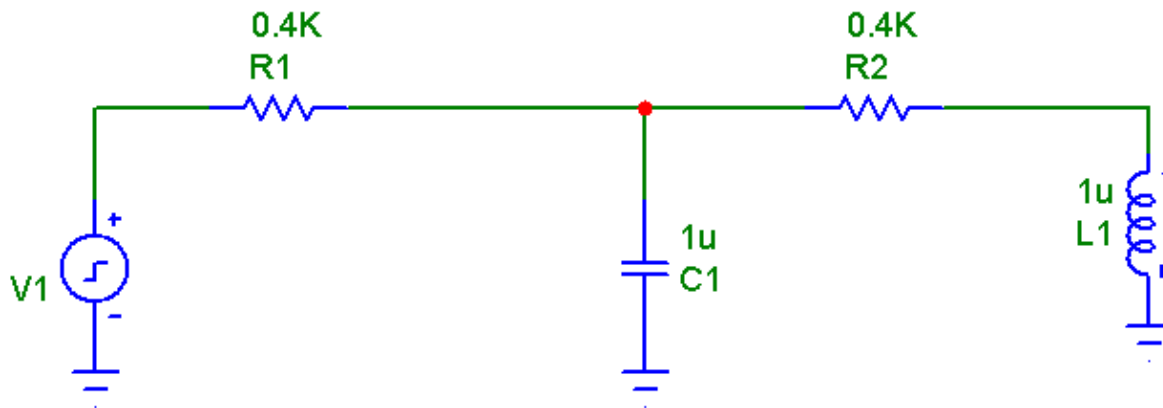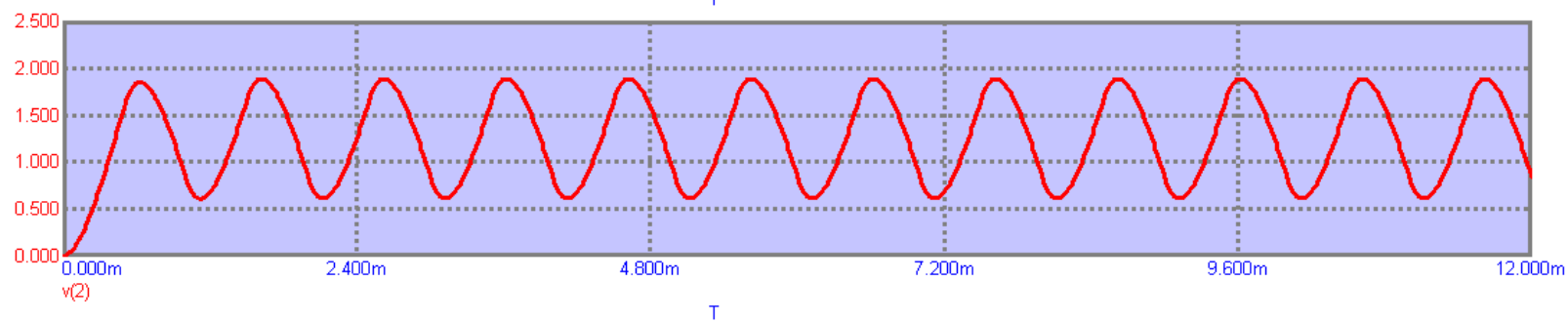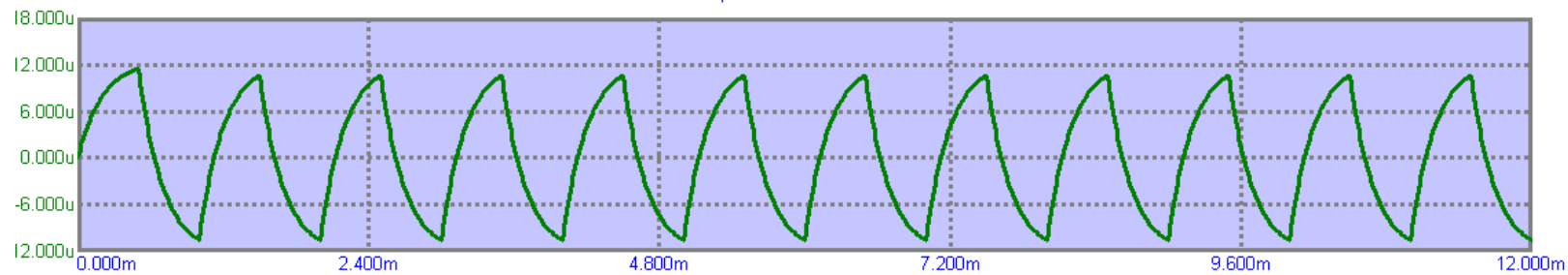

 $V_{IN}$ 

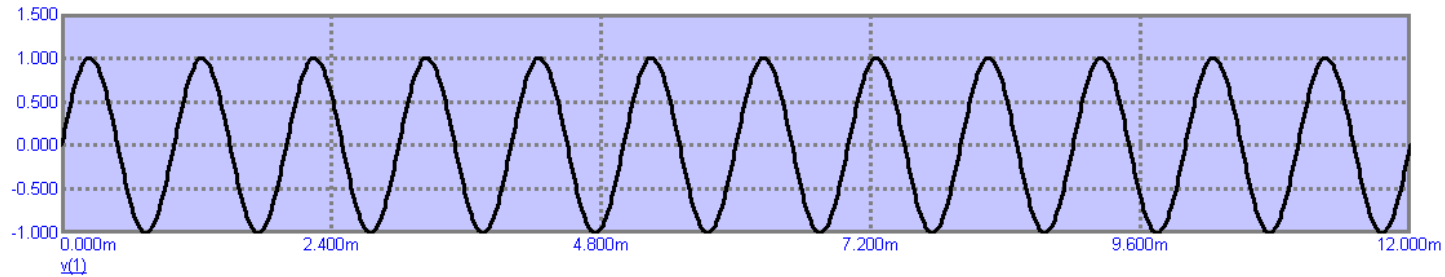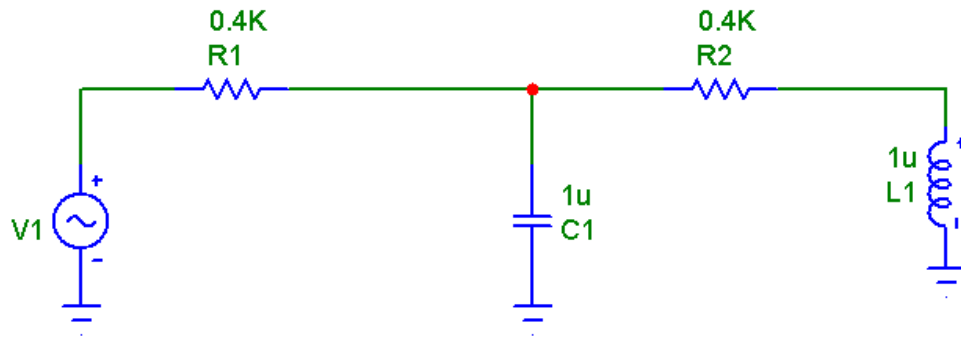 $V_C$ 

 $V_L$   
6

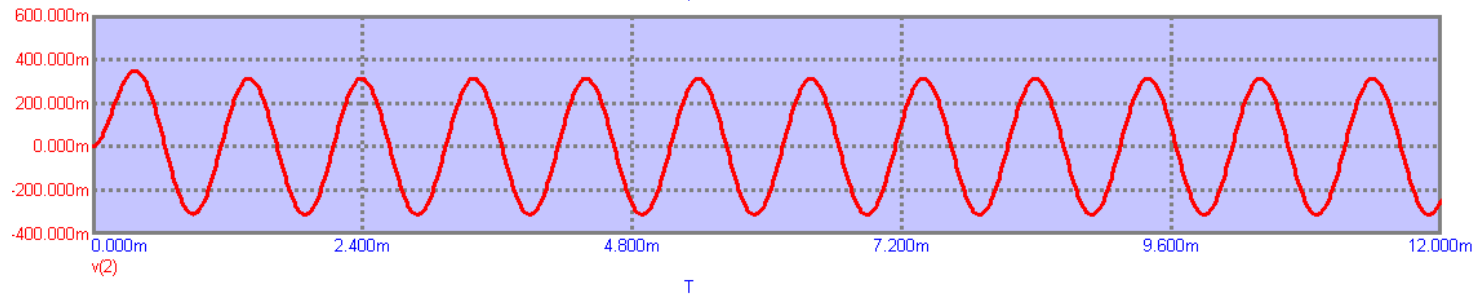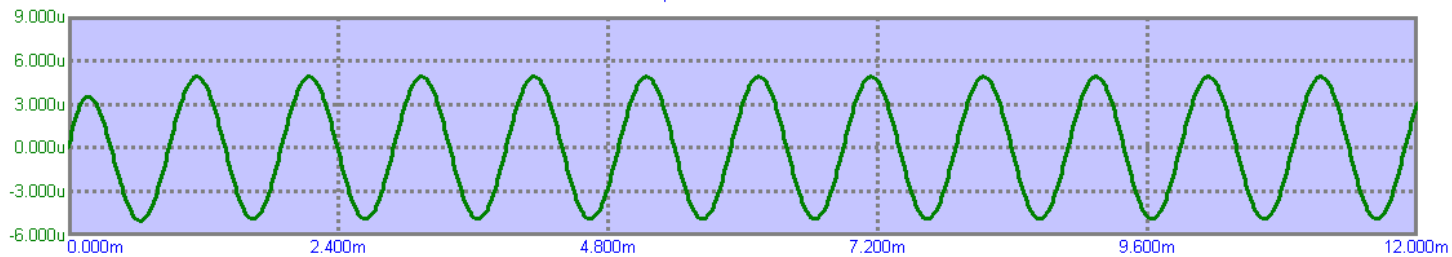

$V_{IN}$




$V_C$



$V_L$

Voltage everywhere in the circuit is sinusoidal


# Transient and Forced Response

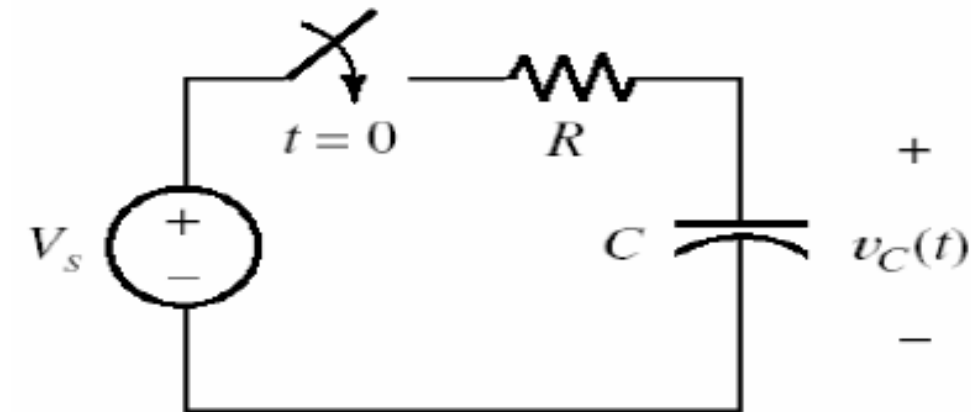

$$v_C(t) = \underbrace{V_s}_{\text{Steady-state or forced response}} - \underbrace{V_s e^{-t/\tau}}_{\text{Transient response}}$$



Steady-state or forced response

Transient response

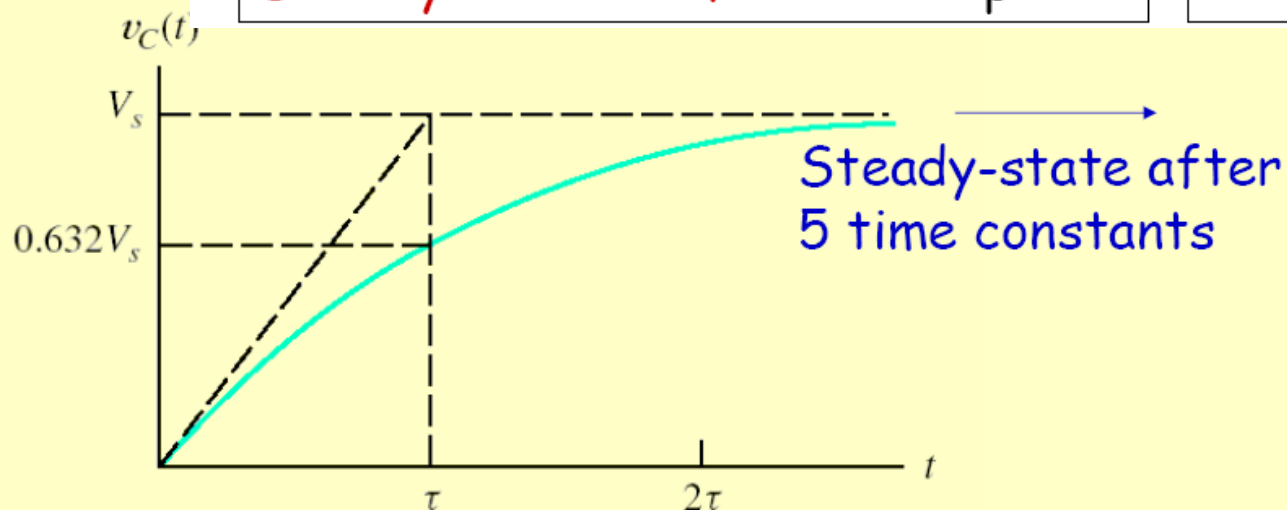





# Transient and Forced Response

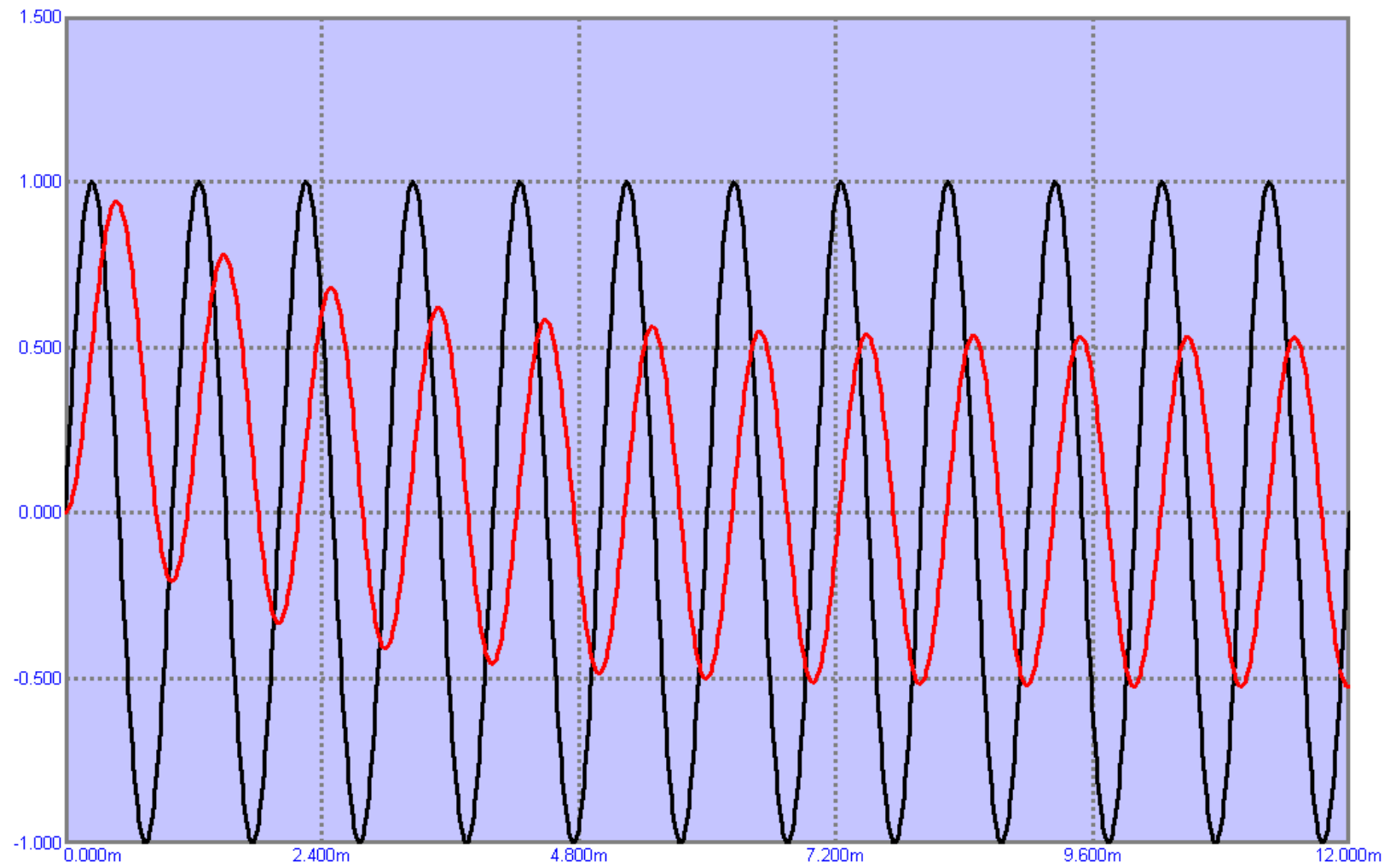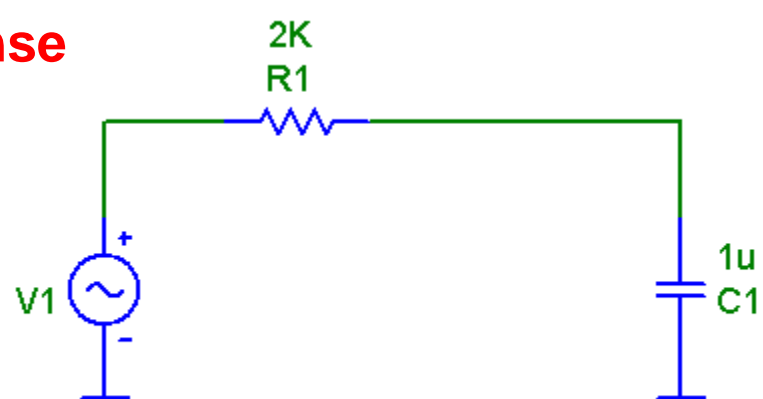
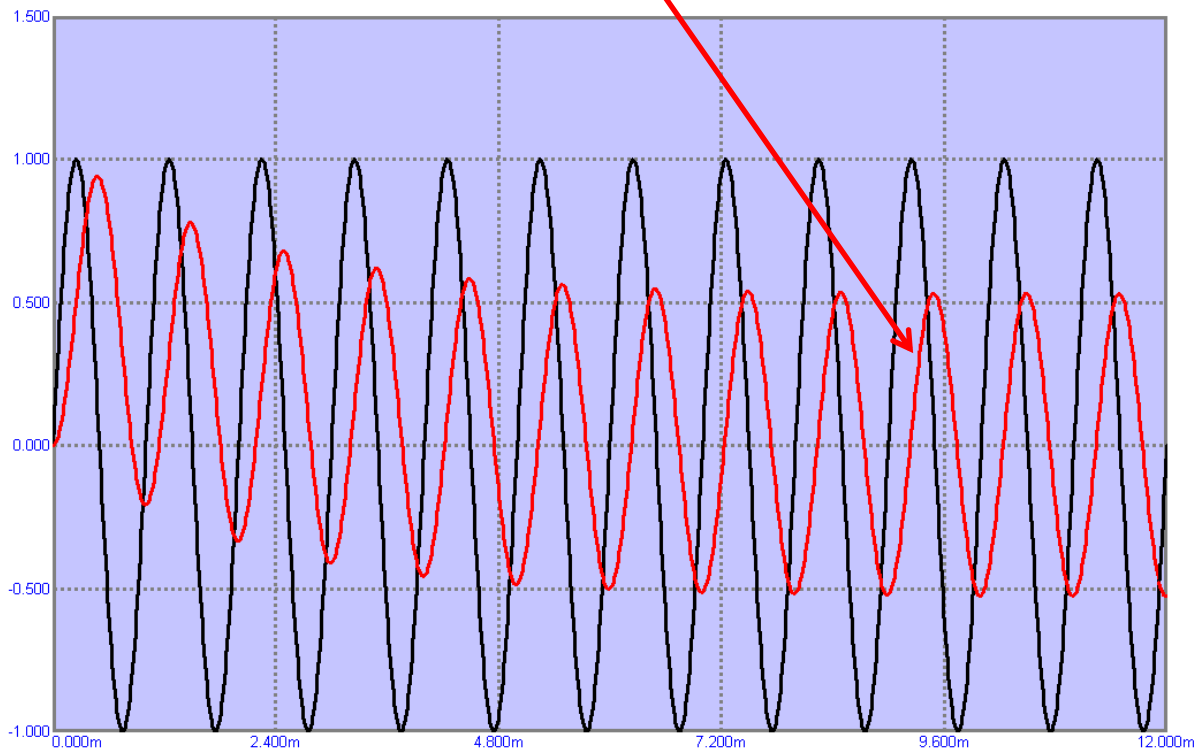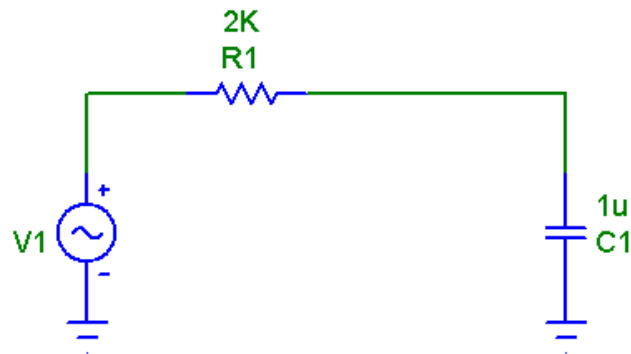
# Sinusoidal Steady-State

- Whenever the forced input to the circuit is sinusoidal the response will be sinusoidal
- If the input persists, the response will persist and we call it steady-state response




# Sinusoidal Currents and Voltages


Canonical Form

$$v(t) = V_m \cos(\omega t + \theta)$$

$V_m$  is the peak value

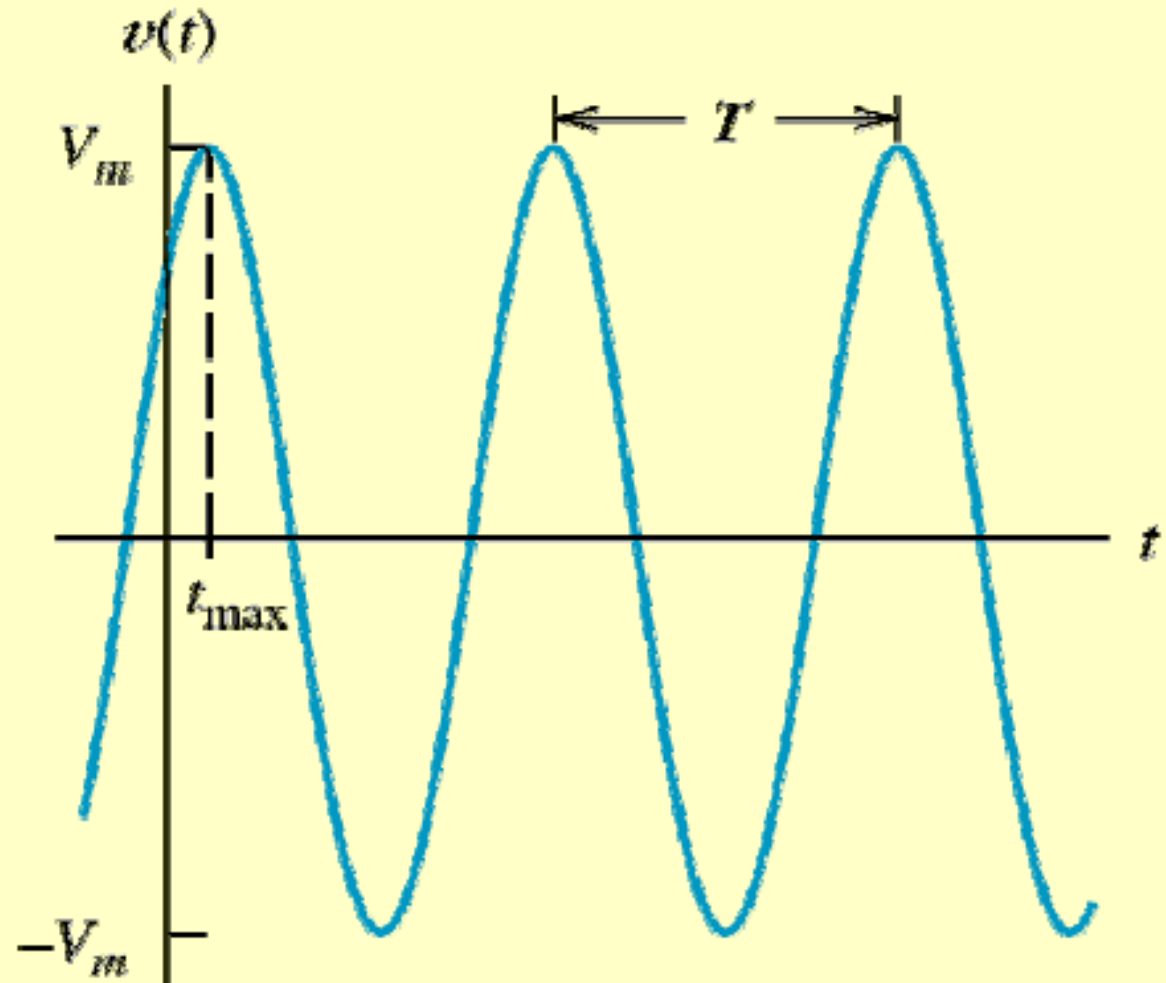


# Sinusoidal Currents and Voltages

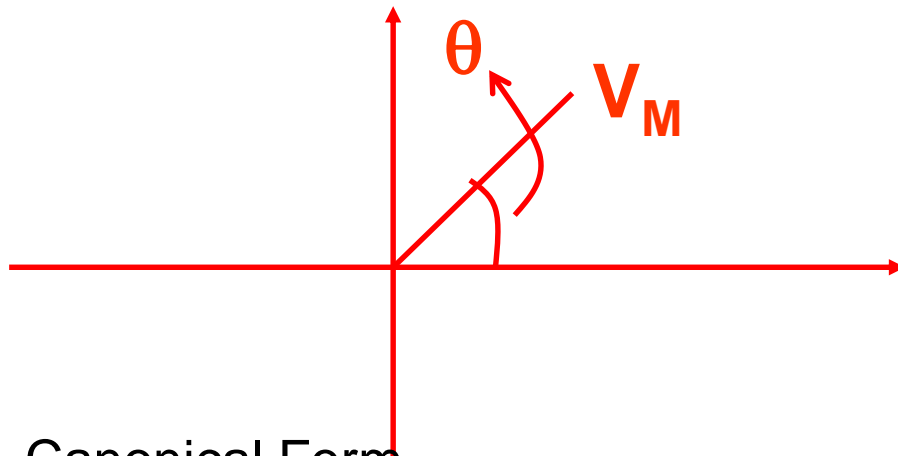

Canonical Form

$$v(t) = V_m \cos(\omega t + \theta)$$

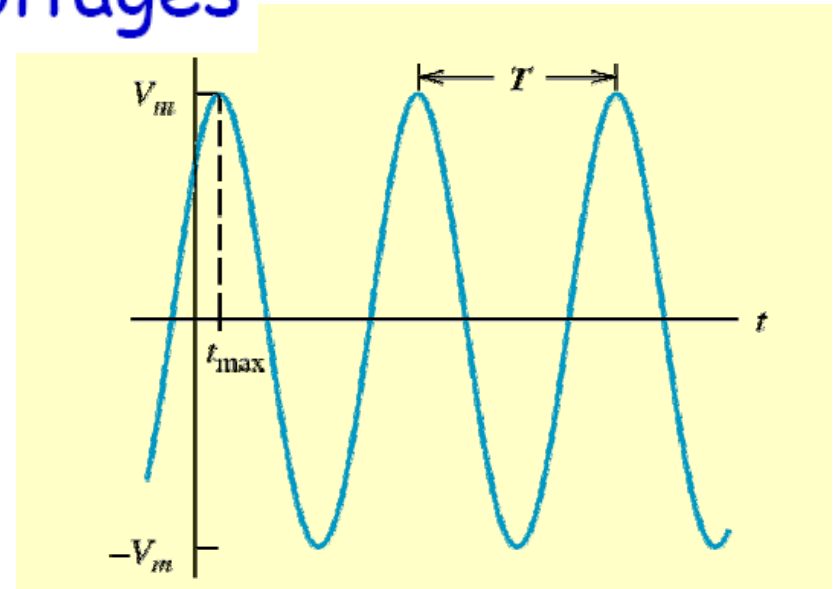

$\omega$  is the **angular frequency** in radians per second

$T$  is the **period**, where  $f = \frac{1}{T}$  is the **frequency**

$$\omega = \frac{2\pi}{T}$$

$$\omega = 2\pi f$$

$\theta$  is the **phase angle**

## Example-1

$$5 \sin(4\pi t - 60^\circ)$$

What is the amplitude, phase, angular frequency, time period, frequency?

$$v(t) = V_m \cos(\omega t + \theta)$$

$$\sin(z) = \cos(z - 90^\circ)$$

$$v(t) = 5 \cos(4\pi t - 60^\circ - 90^\circ)$$

Amplitude = 5 ; Phase =  $-150^\circ$

Phase in radians:

$$360^\circ = 2\pi$$

$$\theta = \frac{-150}{360} \times 2\pi = -2.618 \text{ radians}$$

$$\omega = 4\pi \text{ r / s}$$

$$\omega = \frac{2\pi}{T} = 4\pi \Rightarrow T = 0.5s$$

$$f = \frac{1}{T} = 2\text{Hz}$$

**Example-2** Find the phase difference between the two currents

$$i_1 = 4 \sin(377t + 25^\circ)$$

$$i_2 = -5 \cos(377t - 40^\circ)$$

$$x(t) = x_m \cos(\omega t + \theta) \quad \text{Canonical Form}$$

$$i_1 = 4 \cos(377t + 25^\circ - 90^\circ)$$

$$\theta_1 = -65^\circ$$

$$i_2 = 5 \cos(377t - 40^\circ + 180^\circ)$$

$$\theta_2 = 140^\circ$$

$$\theta_1 - \theta_2 = -205^\circ$$

Which signal leads and by how much?


$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$


# Phase Relationships

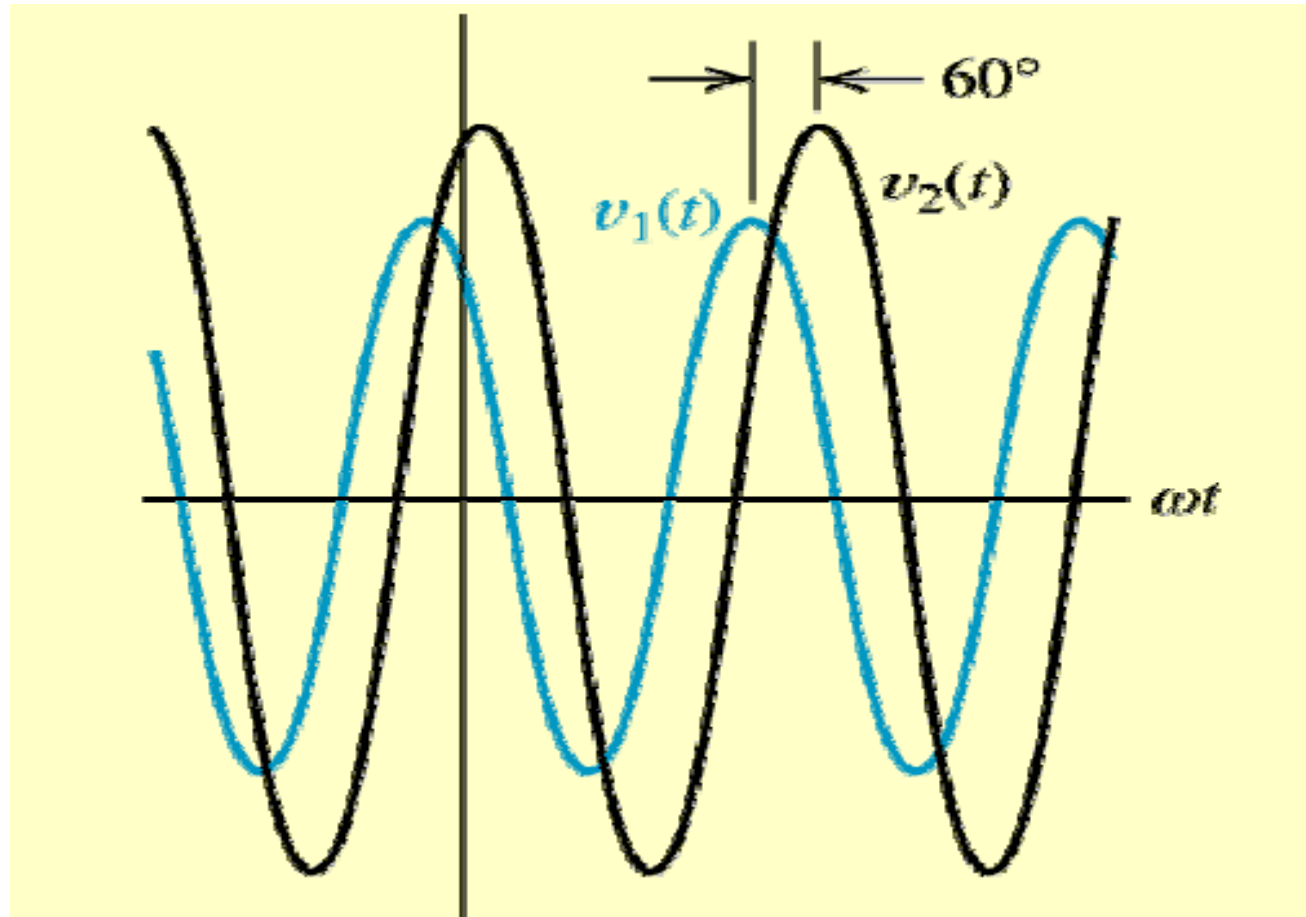

$$v_2(t) = v_{2m} \cos(\omega t)$$

$$v_1(t) = v_{1m} \cos(\omega t + 60^\circ)$$

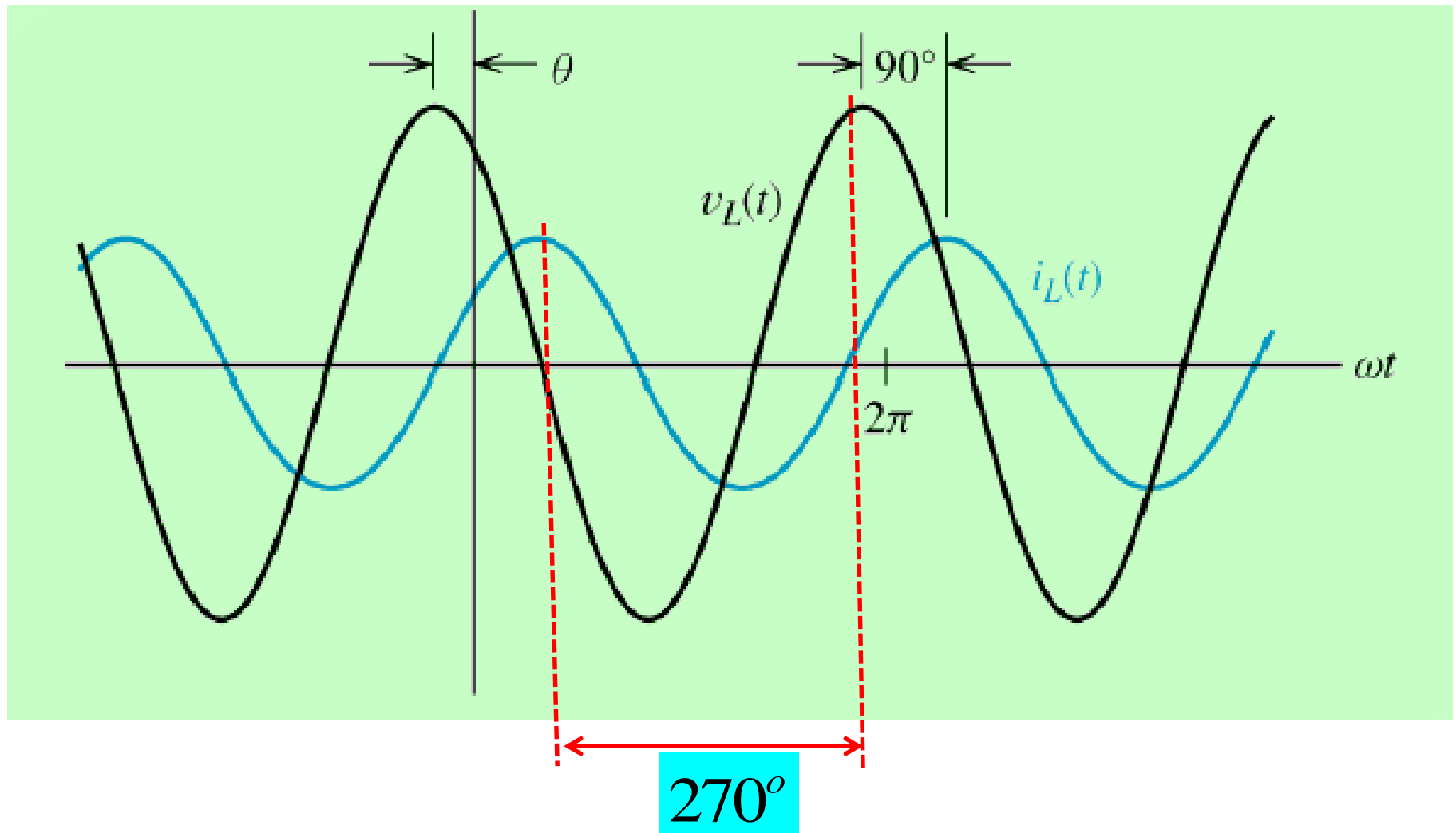The peaks of  $v_1(t)$  occur  $60^\circ$  before the peaks of  $v_2(t)$ . In other words,  $v_1(t)$  leads  $v_2(t)$  by  $60^\circ$ .



Voltage leads current by  $90^\circ$  or lags current by  $270^\circ$  ?

Phase difference is usually considered between  $-180$  to  $180^\circ$

Add or subtract  $360^\circ$  to bring the phase between  $-180$  to  $180^\circ$



$$i_1 = 4 \cos(377t - 65^\circ)$$

$$i_2 = 5 \cos(377t + 140^\circ)$$


Does  $i_2$  lead  $i_1$  ?

$$\theta_1 - \theta_2 = -205^\circ$$

$$\theta_1 - \theta_2 = -205^\circ + 360^\circ = 155^\circ$$


$i_1$  leads  $i_2$  by  $155^\circ$
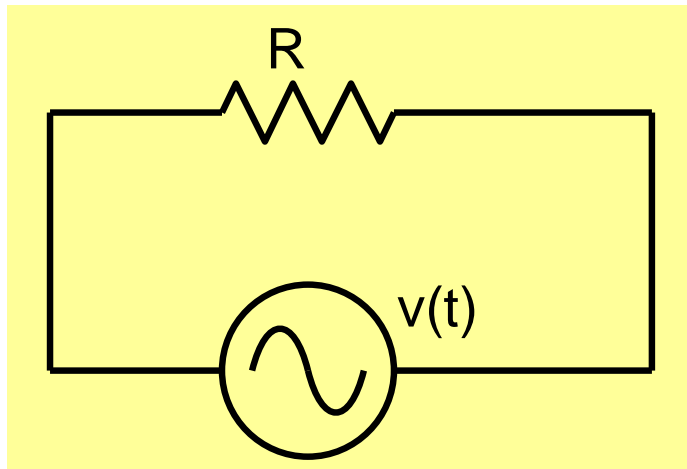
# Power dissipation with sinusoidal Voltage




$$p = \frac{v(t)^2}{R}$$

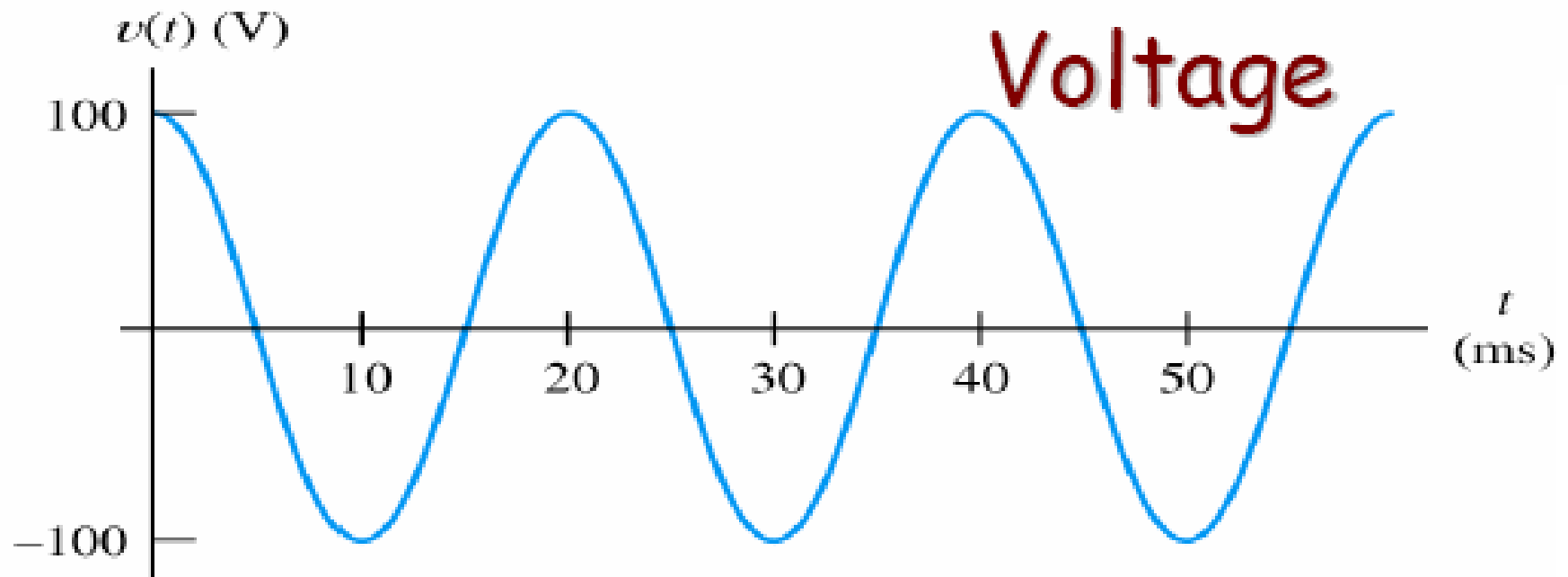Voltage applied to a 50- $\Omega$  resistance




(a)

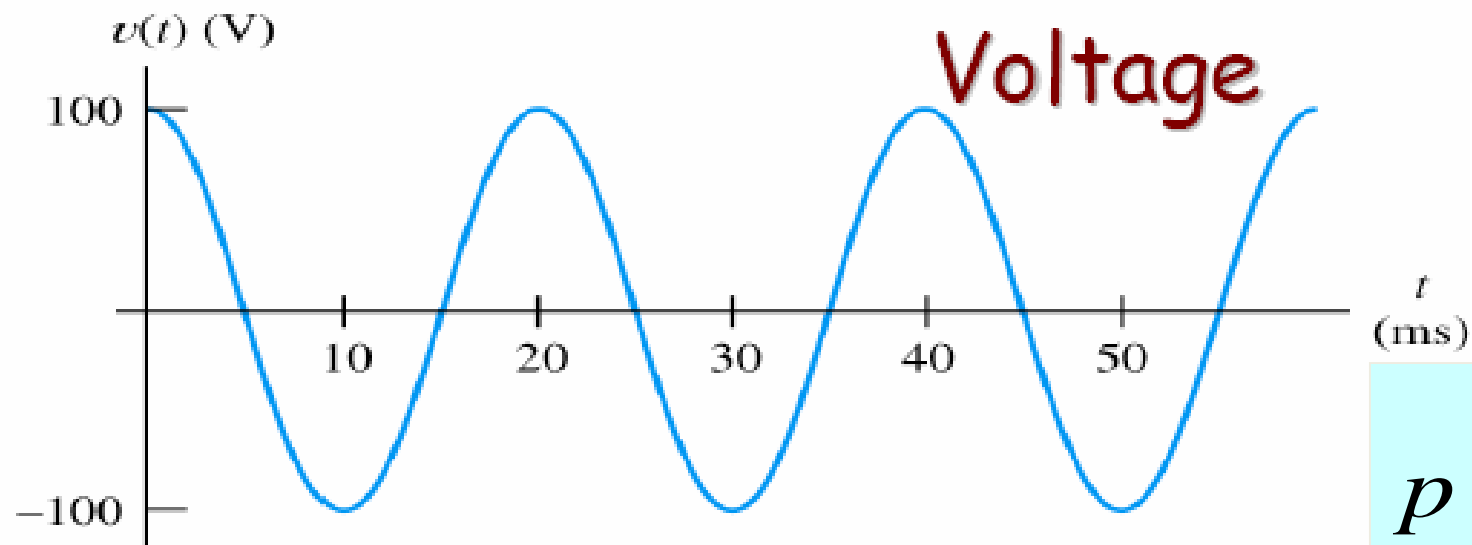

$$p = \frac{v(t)^2}{R}$$

(a)

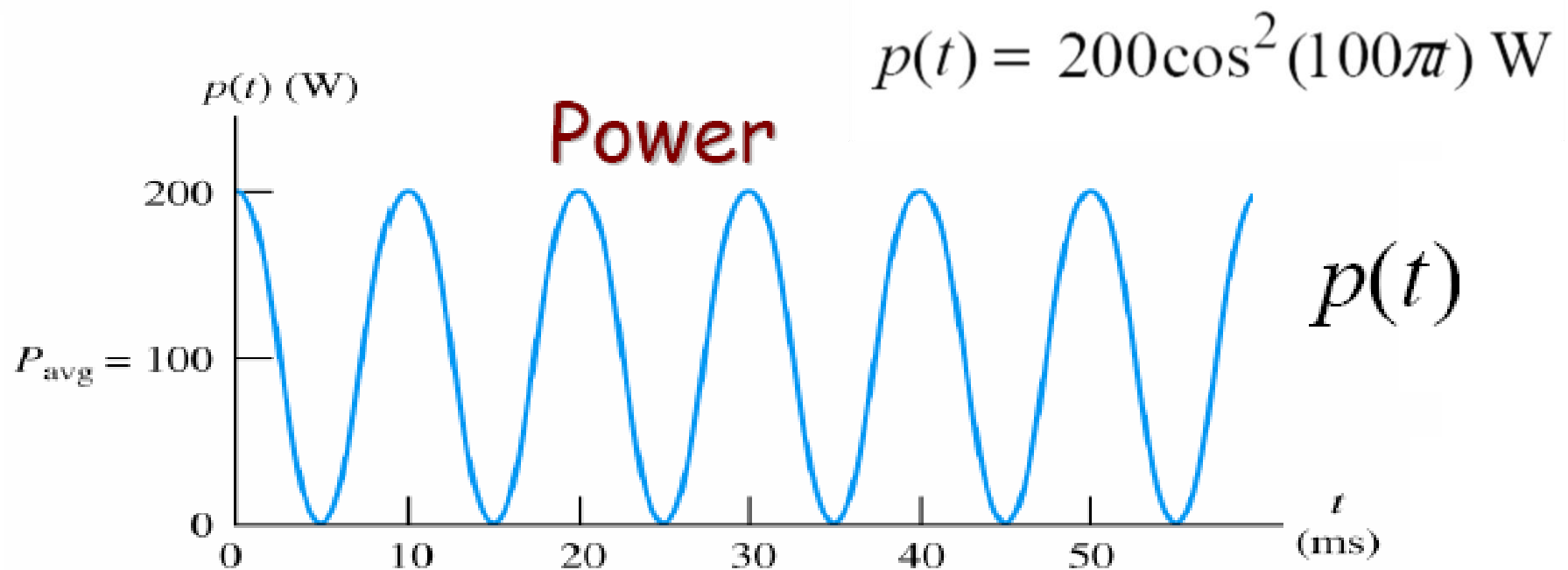

# Average


**X:**  $x_1, x_2, x_3, \dots, x_N$

$$x_{avg} = \frac{1}{N} \sum x_i$$

If  $x$  is continuous, its average over a time  $t_1$

$$x_{avg} = \frac{1}{t_1} \int_0^{t_1} x(t) dt$$

For periodic signals

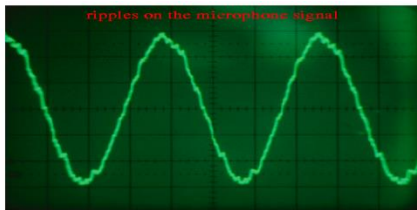

$$x_{avg} = \frac{1}{T} \int_0^T x(t) dt$$

## Average Power

$$P_{avg} = \frac{1}{T} \int_0^T \frac{v(t)^2}{R} dt$$

We would like to express it like the dc power dissipated in a resistor

$$P_{avg} = \frac{\left[ \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} \right]^2}{R}$$

$$p = \frac{V^2}{R}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

**This is true for any periodic waveform**

# RMS Value of a Sinusoid

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt}$$


$$v(t) = V_m \cos(\omega t + \theta)$$

$$\begin{aligned} \int_0^T \cos^2(\omega t + \theta) dt &= \int_0^T \frac{1 - \cos(2\omega t + 2\theta)}{2} dt \\ &= 0.5T - \frac{1}{4\omega} \sin(2\omega t + 2\theta) \Big|_0^T = 0.5T \end{aligned}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

The **RMS** value **for a sinusoid** is the peak value divided by the square root of 2
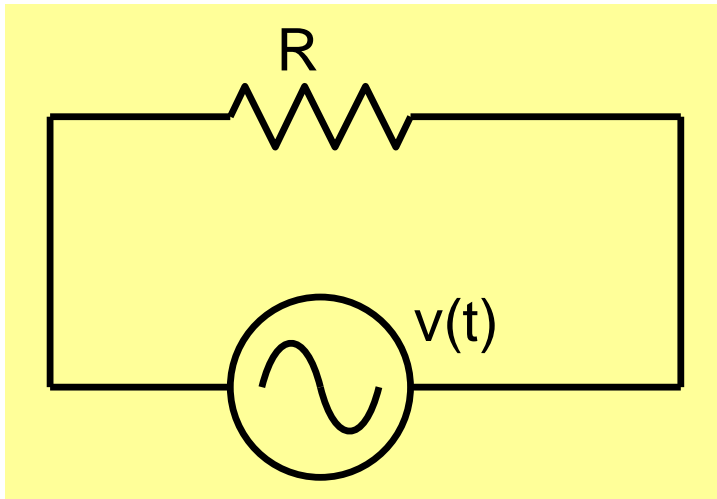
# Power dissipation with sinusoidal Voltage



$$v(t) = V_m \cos(\omega t + \theta)$$

$$P_{avg} = \frac{V_{rms}^2}{R}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$P_{avg} = \frac{V_m^2}{2R}$$


$$i(t) = I_m \cos(\omega t + \theta)$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = \frac{1}{2} I_m^2 R$$

### Example-3

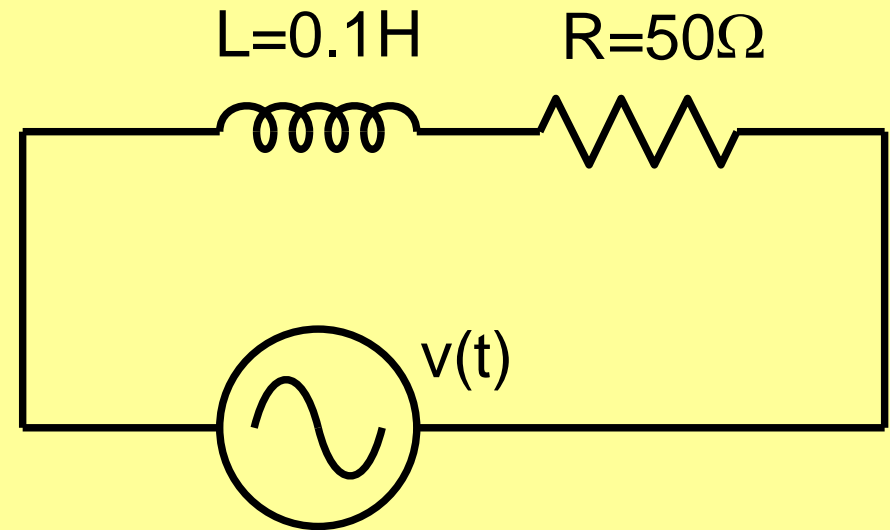

$$v(t) = 2 \cos(200t + 45)$$

$$v_R(t) = 1.85 \cos(200t + 23.2)$$

$$\begin{aligned} v_L(t) &= v(t) - v_R(t) \\ &= 2 \cos(200t + 45) - 1.85 \cos(200t + 23.2) \end{aligned}$$

Solving such circuits requires us to add/subtract sinusoids !




# Performing algebra on sinusoids by representing them as complex numbers

$$v_1(t) = 20 \cos(\omega t - 45^\circ) \quad v_2(t) = 10 \sin(\omega t + 60^\circ)$$

$$v_1(t) + v_2(t) = ?$$

## Strategy

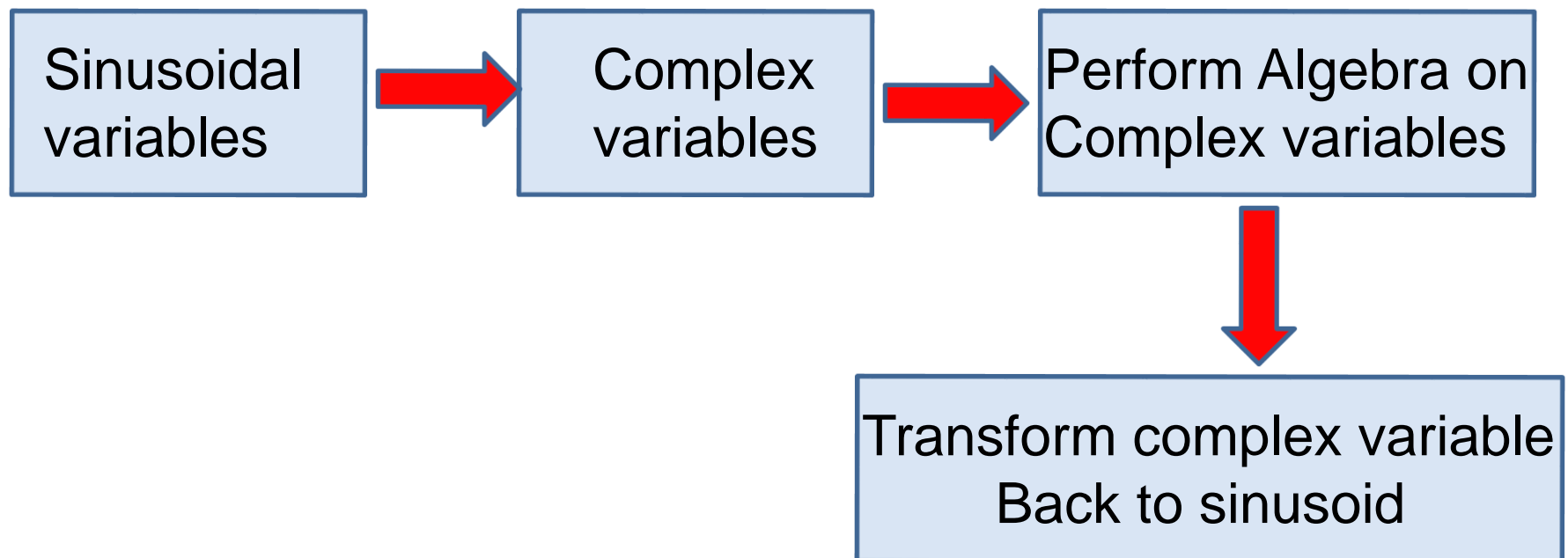

$$20 \cos(\omega t - 45^\circ) \longrightarrow \mathbf{V}_1 = 20 \angle -45^\circ$$

$$14.14 - j14.14$$

$$10 \sin(\omega t + 60^\circ) \longrightarrow \mathbf{V}_2 = 10 \angle -30^\circ$$

$$8.660 - j5$$

$$\begin{aligned} \mathbf{V}_s &= \mathbf{V}_1 + \mathbf{V}_2 \\ &= 20 \angle -45^\circ + 10 \angle -30^\circ \\ &= 14.14 - j14.14 + 8.660 - j5 \\ &= 23.06 - j19.14 \\ &= 29.97 \angle -39.7^\circ \end{aligned}$$

$$v_s(t) = 29.97 \cos(\omega t - 39.7^\circ)$$

# Complex Numbers

$$z = x + jy$$

Real part  $\nearrow$   $\nwarrow$   $\nearrow$   $\nwarrow$  Imaginary part

$\sqrt{-1}$

$$z_1 = 5 + j5$$

$$z_2 = 3 - j4$$

$$z_1 + z_2 = (5 + j5) + (3 - j4) = 8 + j1$$

$$z_1 - z_2 = (5 + j5) - (3 - j4) = 2 + j9$$

Complex conjugate of  $z$  is:

$$z^* = x - jy$$

# Complex Numbers


$$z_1 = 5 + j5 \quad z_2 = 3 - j4$$

$$\begin{aligned} z_1 z_2 &= (5 + j5)(3 - j4) \\ &= 15 - j20 + j15 - j^2 20 \\ &= 15 - j20 + j15 + 20 \\ &= 35 - j5 \end{aligned}$$

$$\begin{aligned} \frac{z_1}{z_2} &= \frac{5 + j5}{3 - j4} \times \frac{z_2^*}{z_2^*} \\ &= \frac{5 + j5}{3 - j4} \times \frac{3 + j4}{3 + j4} \end{aligned}$$

$$\begin{aligned} &= \frac{15 + j20 + j15 + j^2 20}{9 + j12 - j12 - j^2 16} \\ &= \frac{15 + j20 + j15 - 20}{9 + j12 - j12 + 16} \\ &= \frac{-5 + j35}{25} \\ &= -\frac{5}{25} + j\frac{35}{25} \\ &= 0.2 + j1.4 \end{aligned}$$

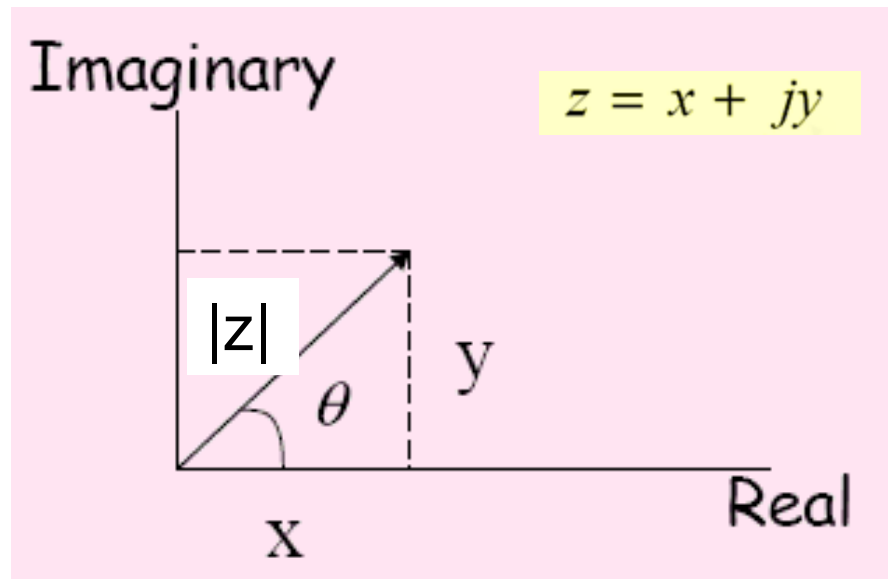A complex number can be represented as a **point** in the complex Plane



Represent the complex number by the length of the arrow and the angle between the arrow and the positive real axis

$$|z| = \sqrt{x^2 + y^2}$$

$$\tan \theta = \frac{y}{x} \quad \text{or} \quad \theta = \tan^{-1} \frac{y}{x}$$


Polar form:

$$z = |z| \angle \theta$$

Rectangular  $\rightarrow$  Polar form

$$z_2 = 10 + j5$$
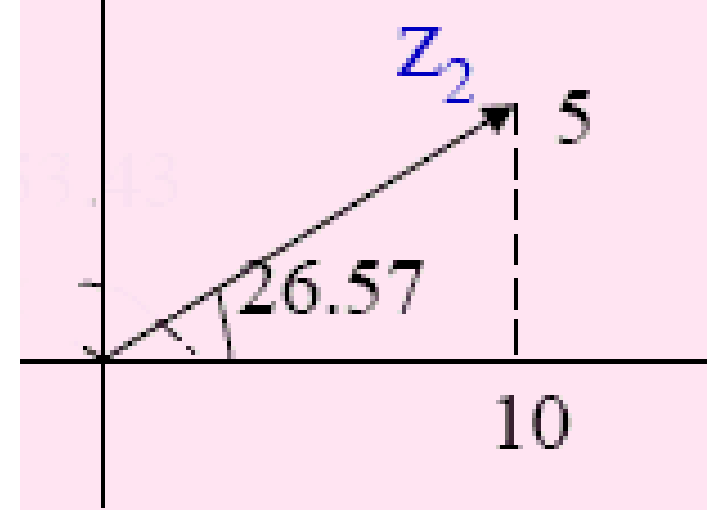
$$z_2 = \sqrt{(10)^2 + (5)^2} \angle \tan^{-1}\left(\frac{5}{10}\right)$$
$$= 11.18 \angle 26.57^\circ$$




$$z_3 = -10 + j5$$

$$z_3 = \sqrt{(10)^2 + (5)^2} \angle \tan^{-1}\left(\frac{5}{-10}\right)$$

$$= 11.18 \angle -26.57^\circ$$

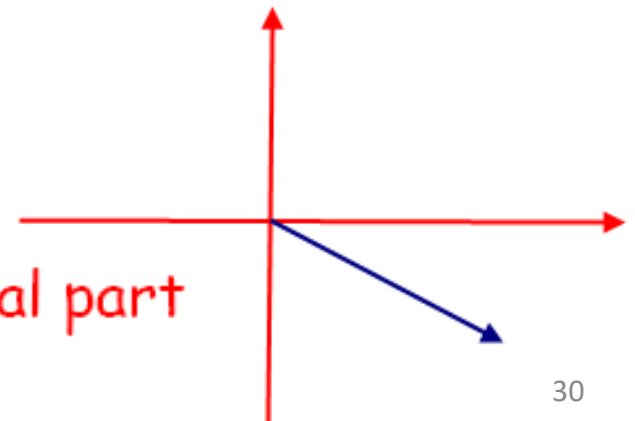Wrong angle since real part  
is negative;



Rectangular  $\rightarrow$  Polar form:

$$z_3 = -10 + j5$$

$$z_3 = \sqrt{(10)^2 + (5)^2} \angle \tan^{-1}\left(\frac{5}{-10}\right)$$

the true angle is:

$$\theta = \tan^{-1}(y/x) \pm 180^\circ$$

$$= -26.57 + 180 = 153.43^\circ$$

Be careful while determining the phase angle

