

ESC201A Assignment 9

Instructor Abhishek Gupta

2023-2024 Semester I

Topics

Truth Tables, Boolean Expressions, Minimization

Questions

1. Show that the Boolean expression $x + \bar{x}.y$ is equivalent to $x + y$ using basic postulates and theorems of Boolean algebra.
2. Reduce the following expressions to a minimum number of literals using basic postulates and theorems of Boolean algebra.
 - (a) $f = (x + y).(\bar{y} + \bar{x})$
 - (b) $f = ABCD + \bar{A}BD + AB\bar{C}D$
3. Consider four-input function $F(A, B, C, D)$ that outputs 1 whenever an odd number of its inputs are 1, (a) construct the truth table (b) write down the Boolean expressions, present an implementation of the function using two-input XOR gate
4. Four switches operate a lamp as follows: the lamp lights up if switches 1,3 and 4 are closed and switch 2 is open, or if 2, 4 are closed and 3 is open, or if all the switches are kept closed. Express this as a boolean function in a standard sum of product form and solve it using k- map. (Use bit '1' when switch is closed and bit '0' when switch is open).
5. Obtain the truth table for the following function: $(x.y + z)(y + x.z)$ and write it as sum of products (SOP) and product of sums (POS).
6. Simplify the following 4-variable functions into sum-of-products form using K-map.
 - a. $\sum(1,5,6,7,14)$
 - b. $\sum(0,4,6,8)$
 - c. $\sum(0,1,4,6,8,9,14)$
 - d. $\sum(1,4,7,11,13,14)$
7. Simplify the following 4-variable functions into product-of-sums form using K-map
 - a. $\Pi(1,3,5,7,13,15)$
 - b. $\Pi(1,3,6,9,11,12,14)$
 - c. $\Pi(1,3,5,7,9,11,12,13,14,15,)$
 - d. $\Pi(0,1,3,4,5,7,12,13,15)$
8. Design a combinational circuit with 3 inputs and 1 output
 - (a) The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise
 - (b) The output is 1 when the binary value of inputs is an odd number.