


ESc201 : Introduction to Electronics

Counters and Registers

Amit Verma
Dept. of Electrical Engineering
IIT Kanpur


Recap: Counters

A	B	C
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

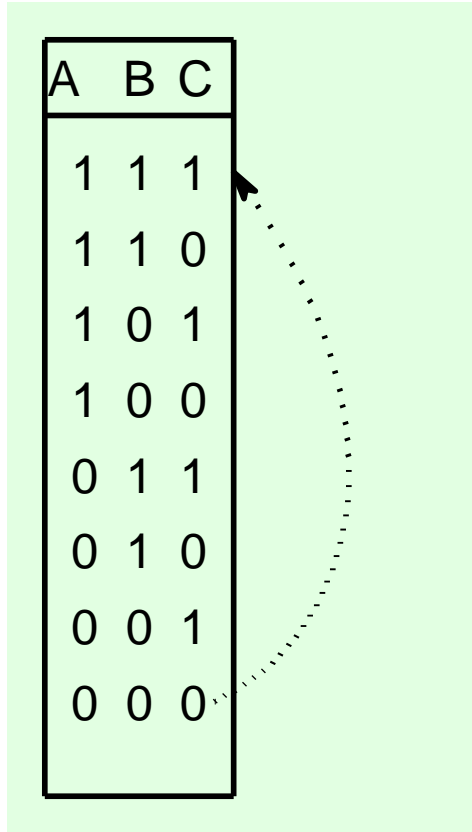

Binary down counter


A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

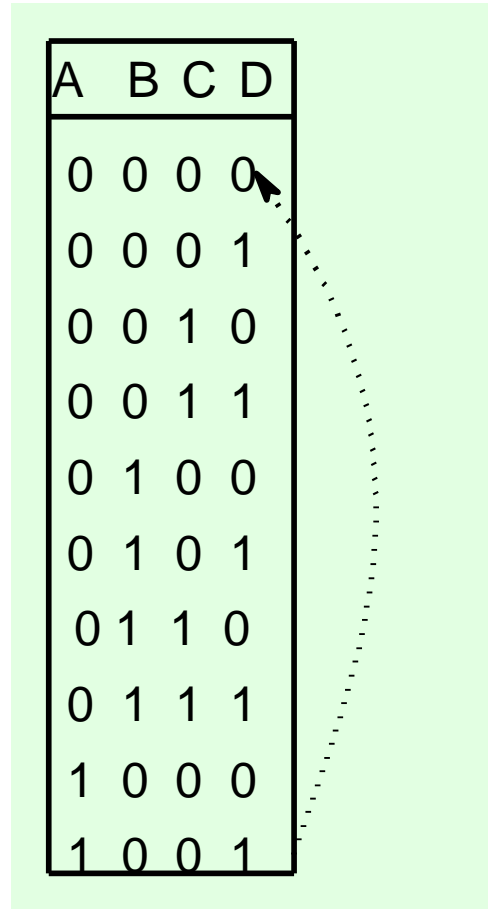

Decade counter

Modulo-10 Counter

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

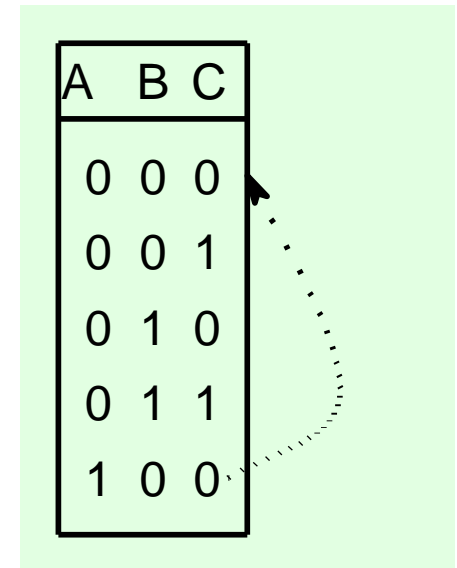



Modulo-5 Counter

Recap: Counter with Unused States

PS			NS			J _A	K _A	J _B	K _B	J _C	K _C
A	B	C	A	B	C						
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X


There are two unused states 011 and 111. one approach to handle this situation is that, while evaluating expressions for J K , we use don't care conditions corresponding to these unused states

Recap:

  


We can see that if by chance the counter goes into unused states 111 or 011, then after a clock cycle it enters one of the used states.


Recap: Counter as frequency divider

 


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

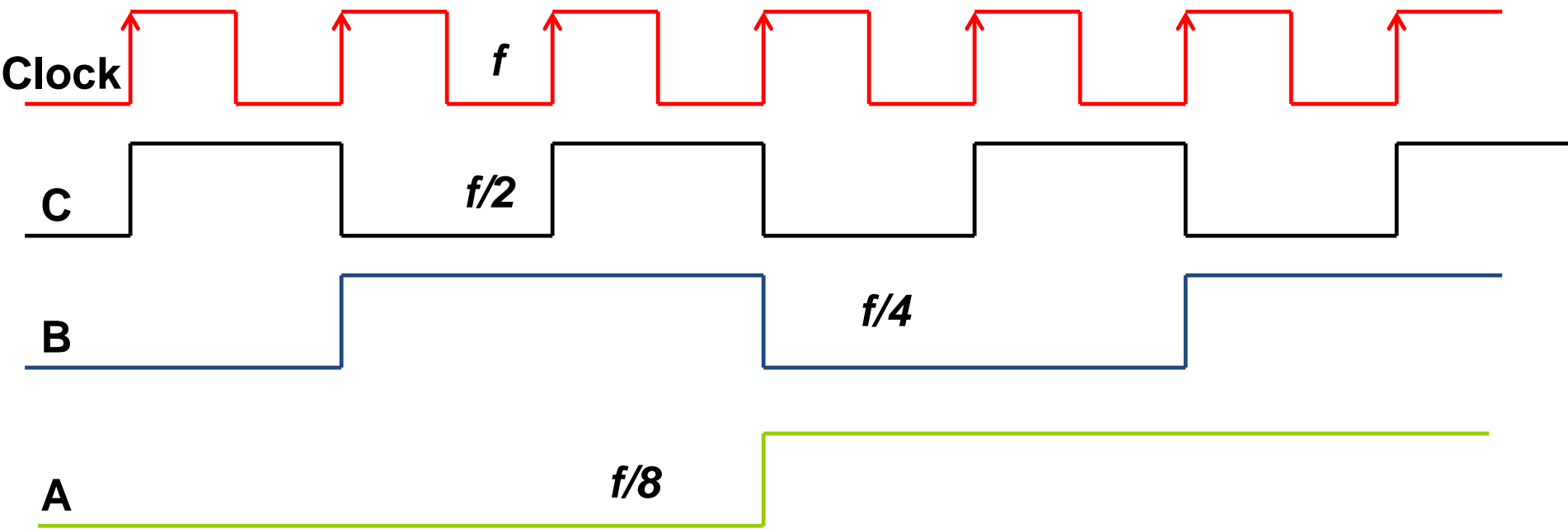

 Example From a frequency of 10KHz, generate the following signal of frequency 2KHz




 A divide by 5 counter is required that has 5 states.



A will give the required waveform.


Ripple Counter

 

T FF toggles when $T = 1$; otherwise Hold state


FF is negative edge Triggered

Ripple Counter

 

0	1	2	3	4	5	-----15	
0	1	0	1	0	1	-----1	0
0	0	1	1	0	0	-----1	0
0	0	0	0	1	1	-----1	0
0	0	0	0	0	0	-----1	0

Ripple Down Counter

 

0 1 0

0 1 1

0 1 1


0 1 1

Example: A flip-flop has a 3ns delay from the time the clock edge occurs to the time the output is complemented. What is the maximum delay in a 10-bit counter that uses this type of flip-flop?


The worst case is when all 10 flip-flops are complemented. The maximum delay is $10 \times 3\text{ns} = 30\text{ns}$.

The maximum frequency then will be: $f = \frac{1}{30\text{ns}} = 33.3\text{MHz}$


Register

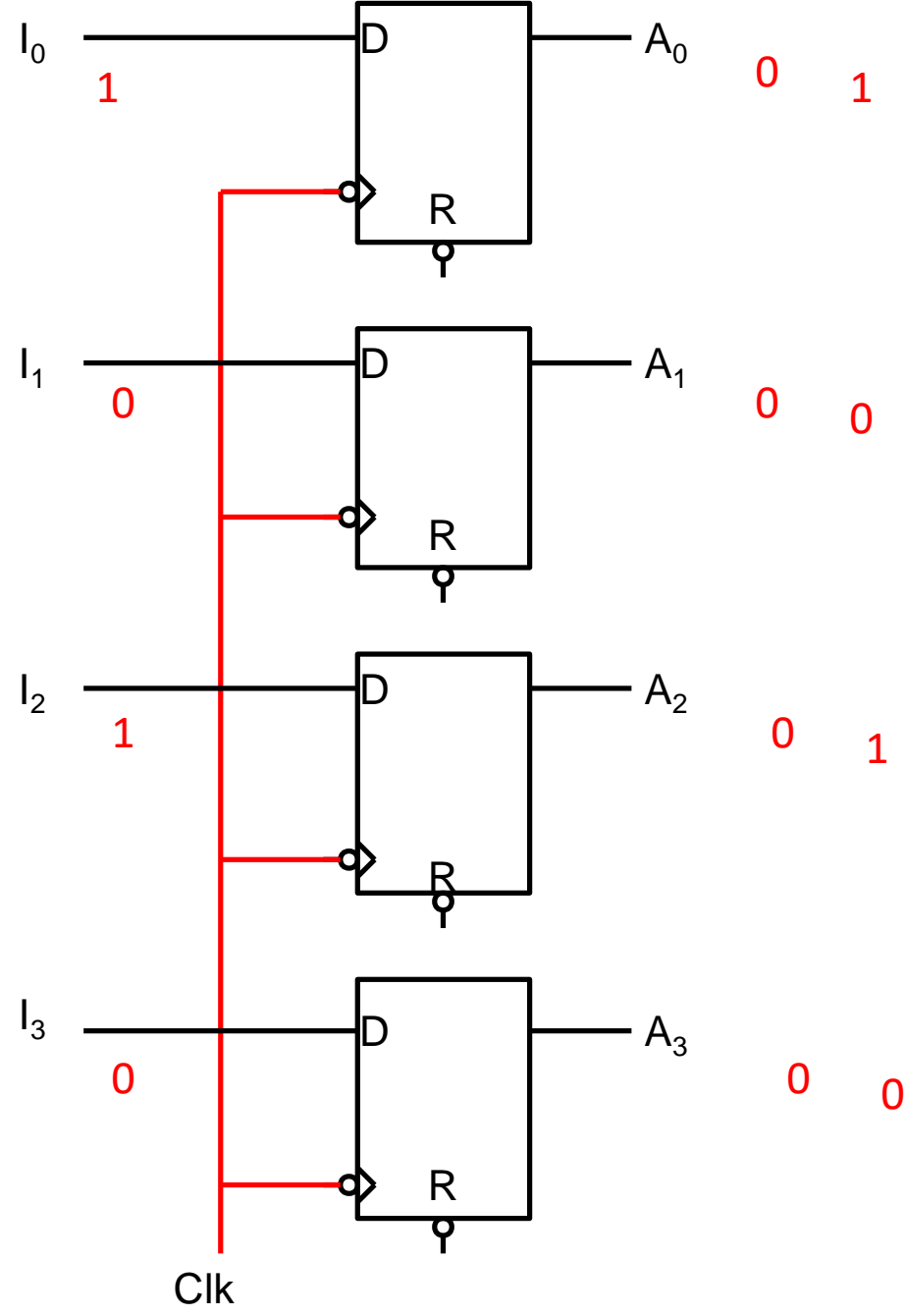


4-bit Register with parallel load

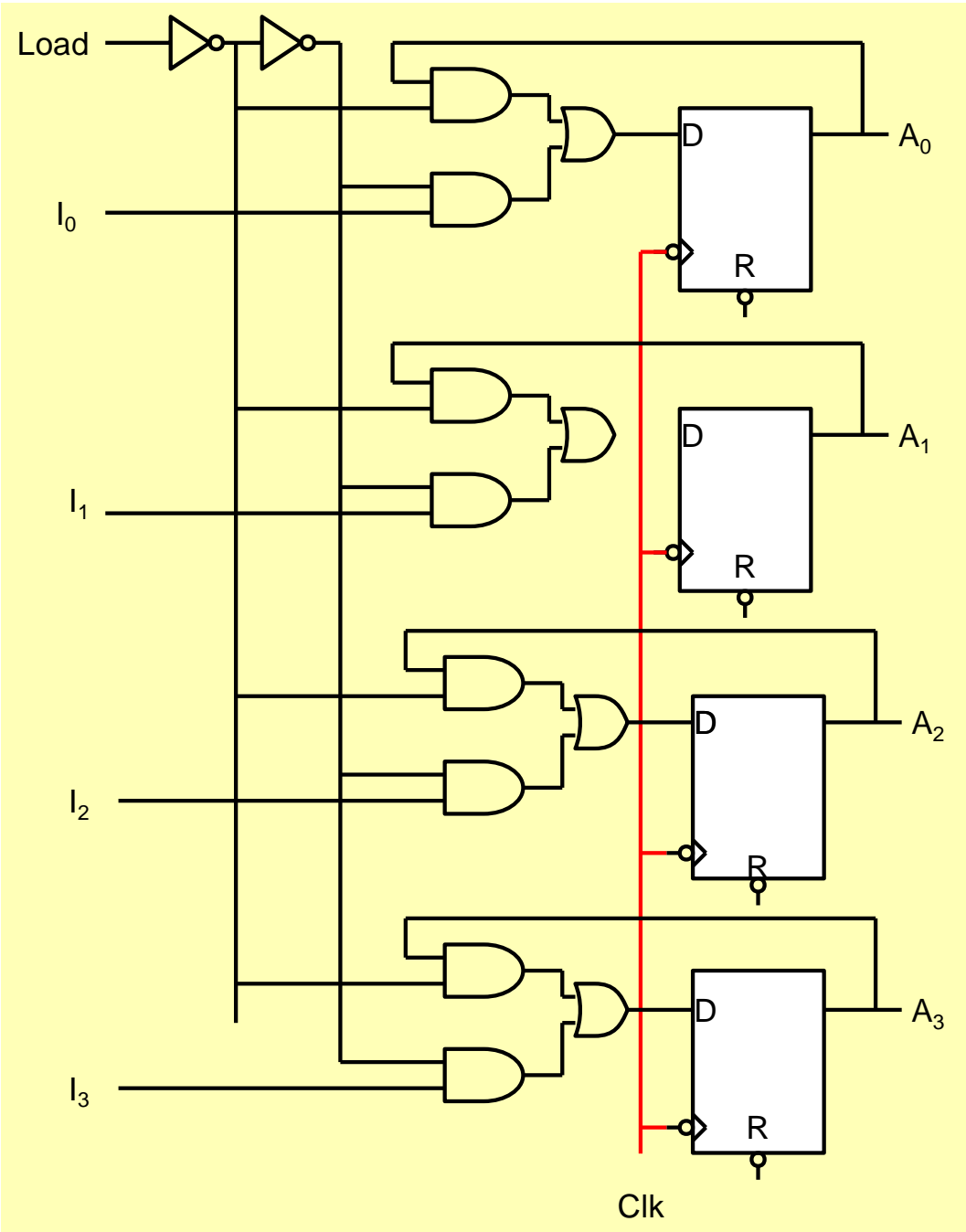


Load = 0

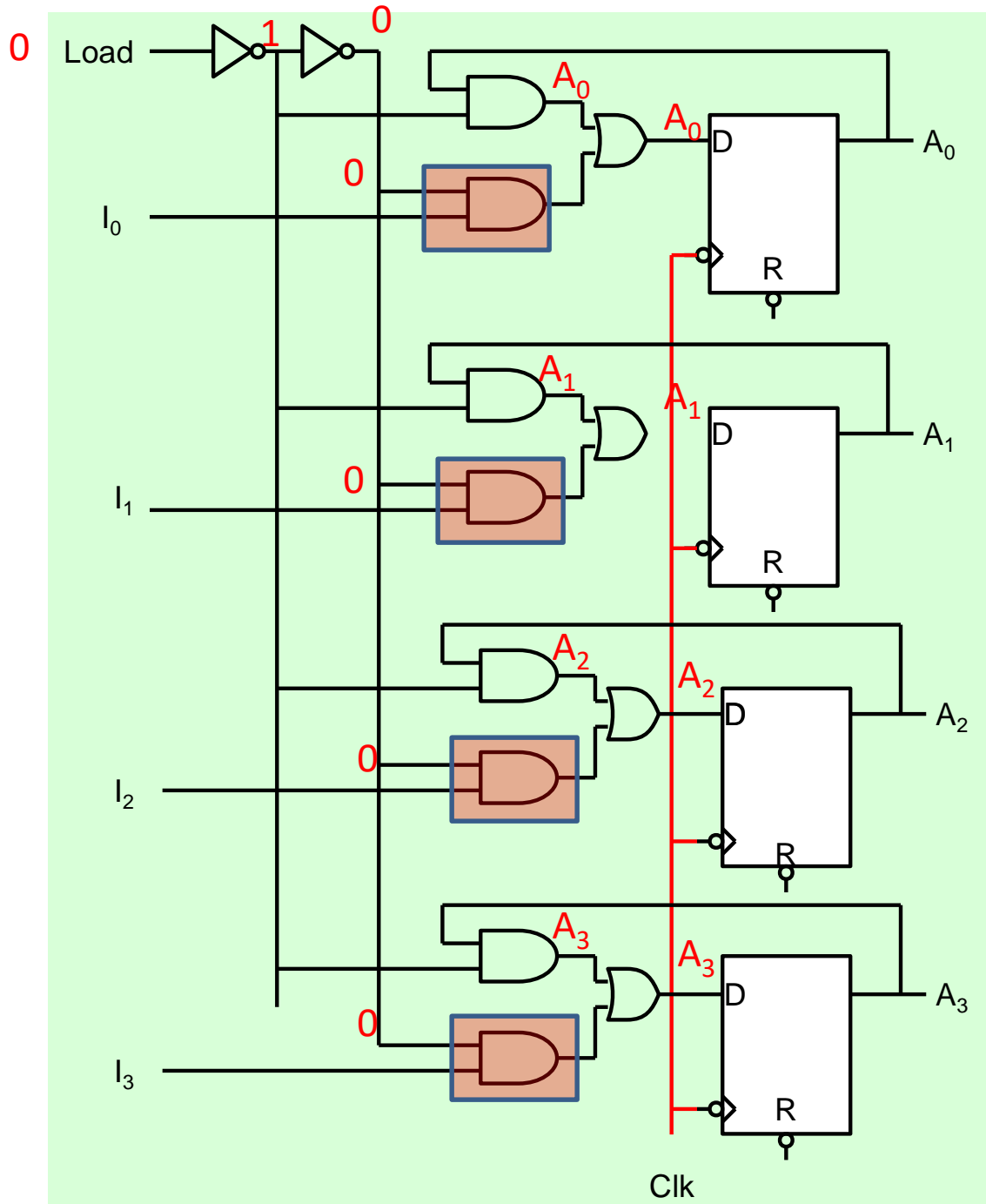


Equivalent Circuit

 


Load = 1

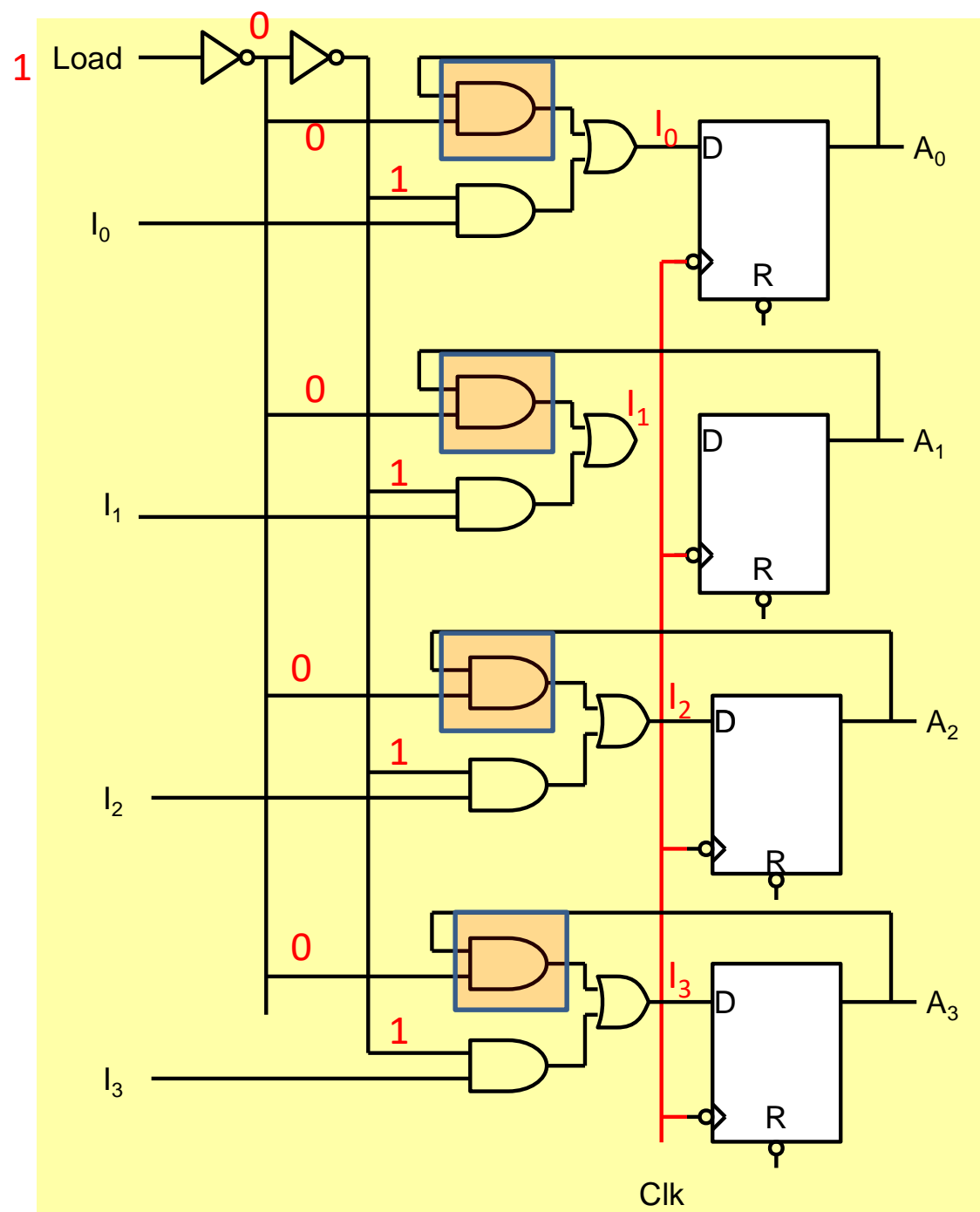


Equivalent Circuit

 

4-bit Shift Register

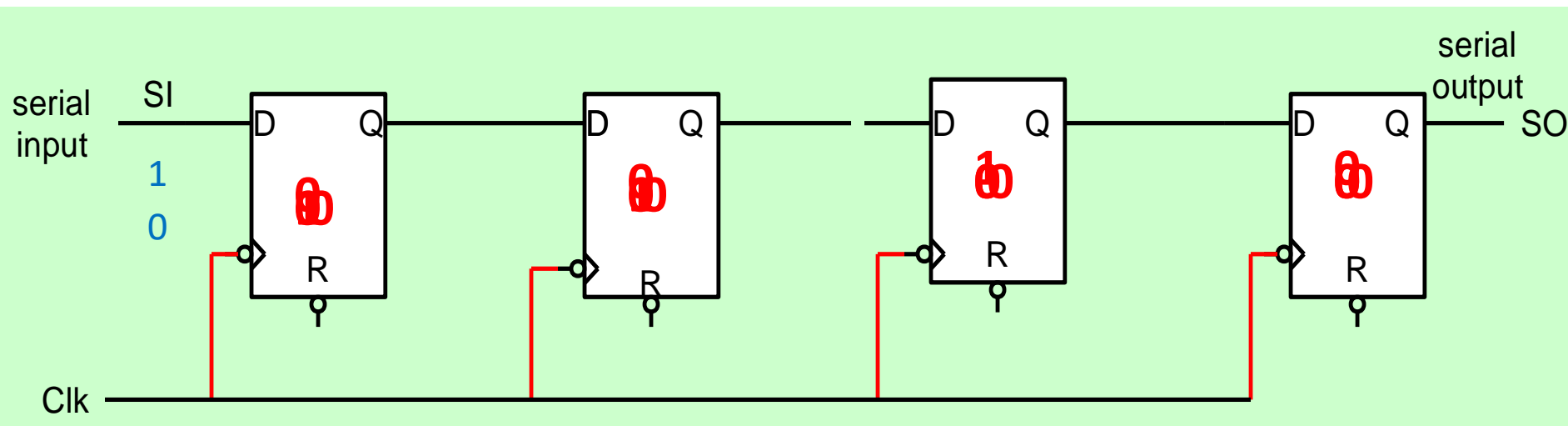


4-bit universal Register

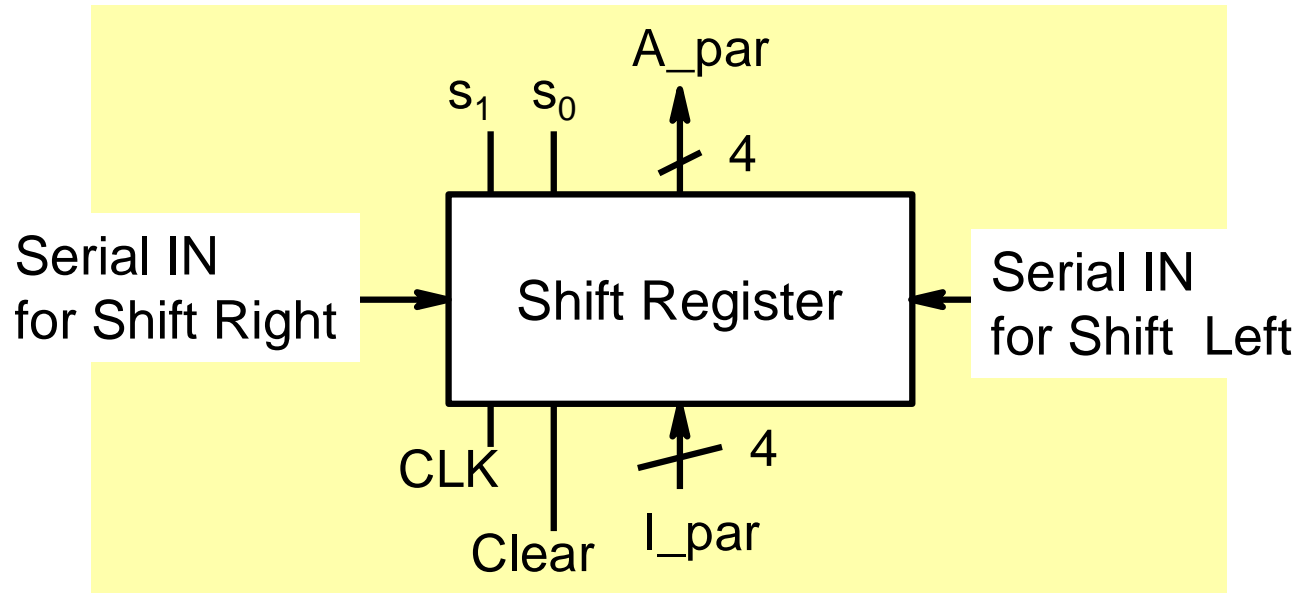


Function

S_1	S_0	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel Load

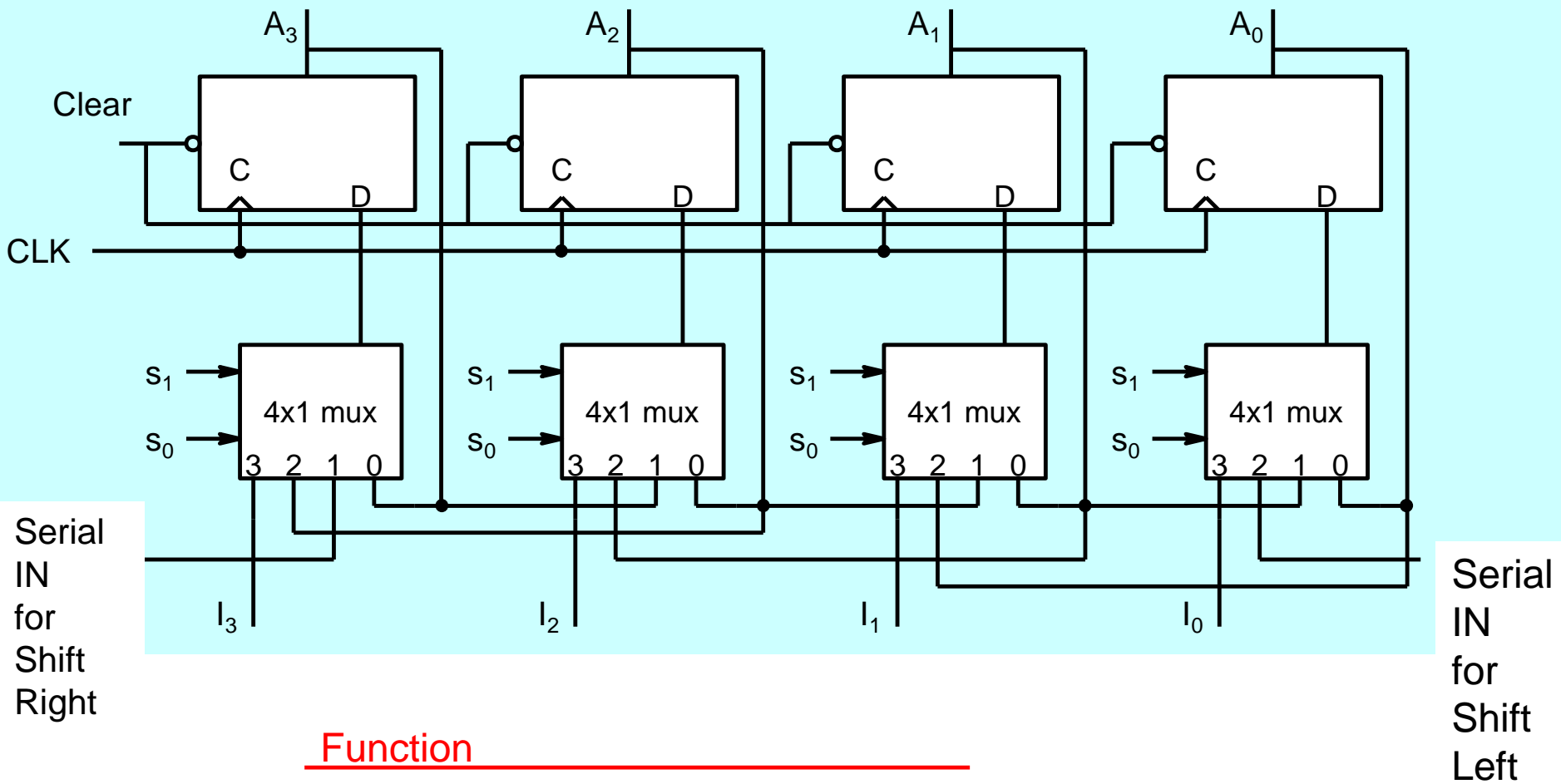


Function

S ₁	S ₀	Register Operation
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel Load

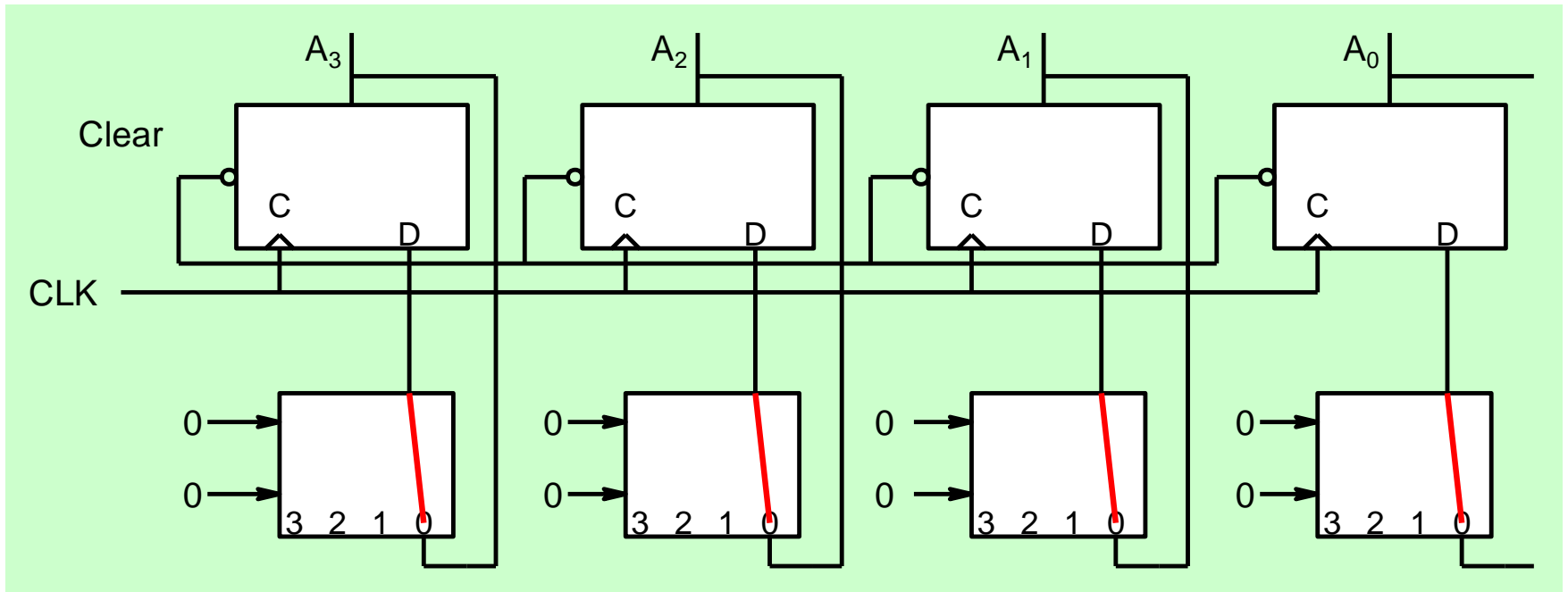


The register maintains its state

$S_1 S_0 = 01$: Shift right

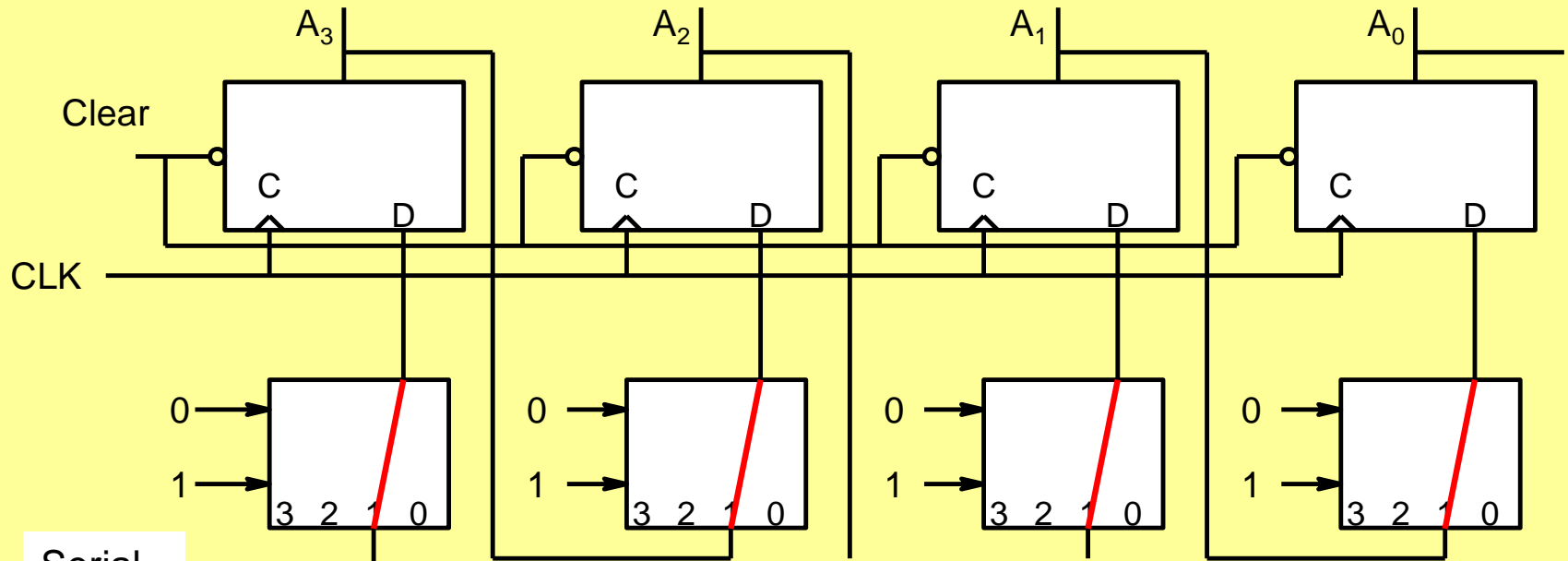


Serial
IN
for
Shift
Right

$S_1 S_0 = 10$: Shift left

 


$S_1 S_0 = 11$: Parallel Load

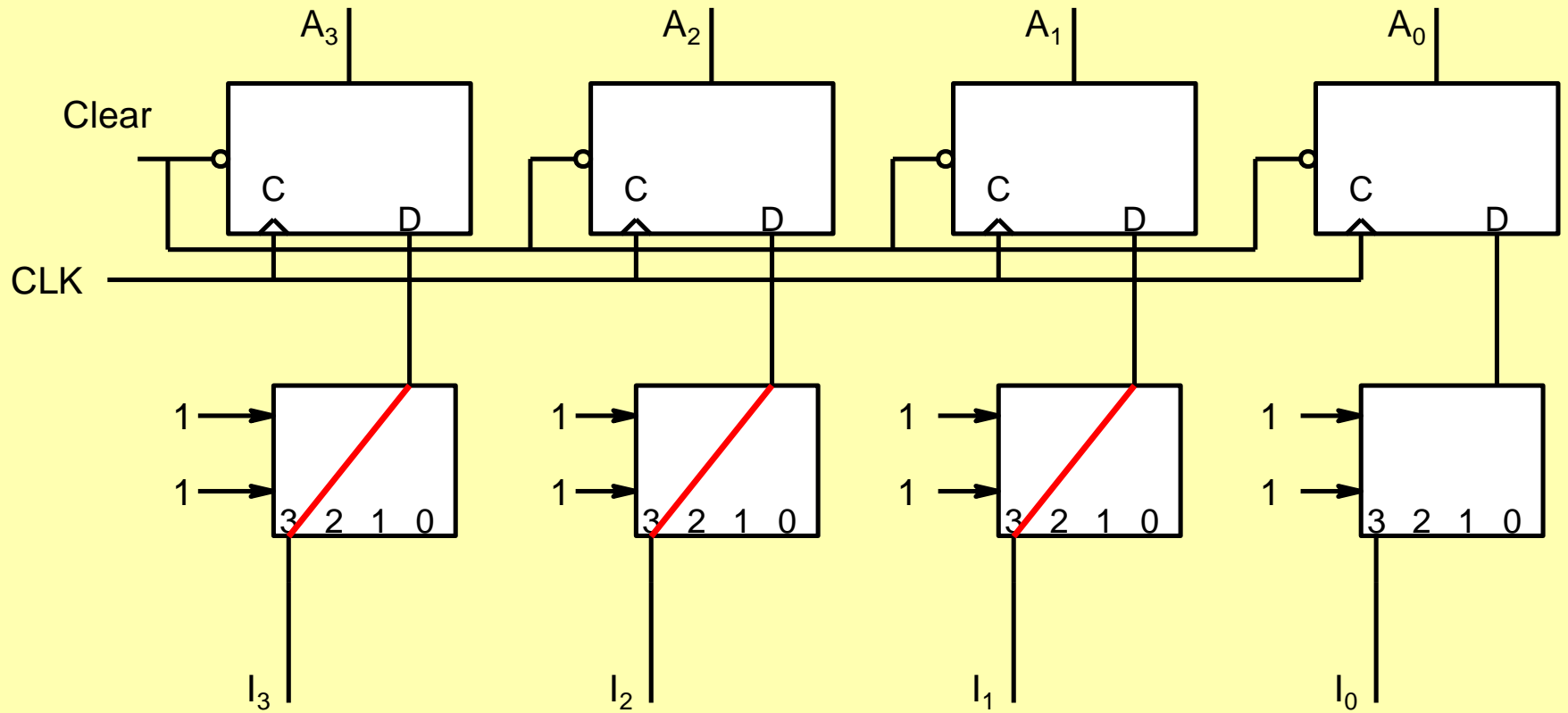

 Example: Design a 4-bit register with 4 D FFs and four 4-to-1 multiplexers with control inputs s_1 and s_2 such that when $S_1S_2 = 00$, there is no change in the register content; when 01 the outputs are complemented; when 10 the register is cleared to 0 synchronously and when 11 the parallel data is synchronously loaded

The register is made of 4 stages each of which has the structure shown below



Quiz-3 Discussion

All the best for the exams!