


# **ESc201 : Introduction to Electronics**





## **Frequency Domain Response**

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur





# Time domain vs. Frequency domain analysis

Signal

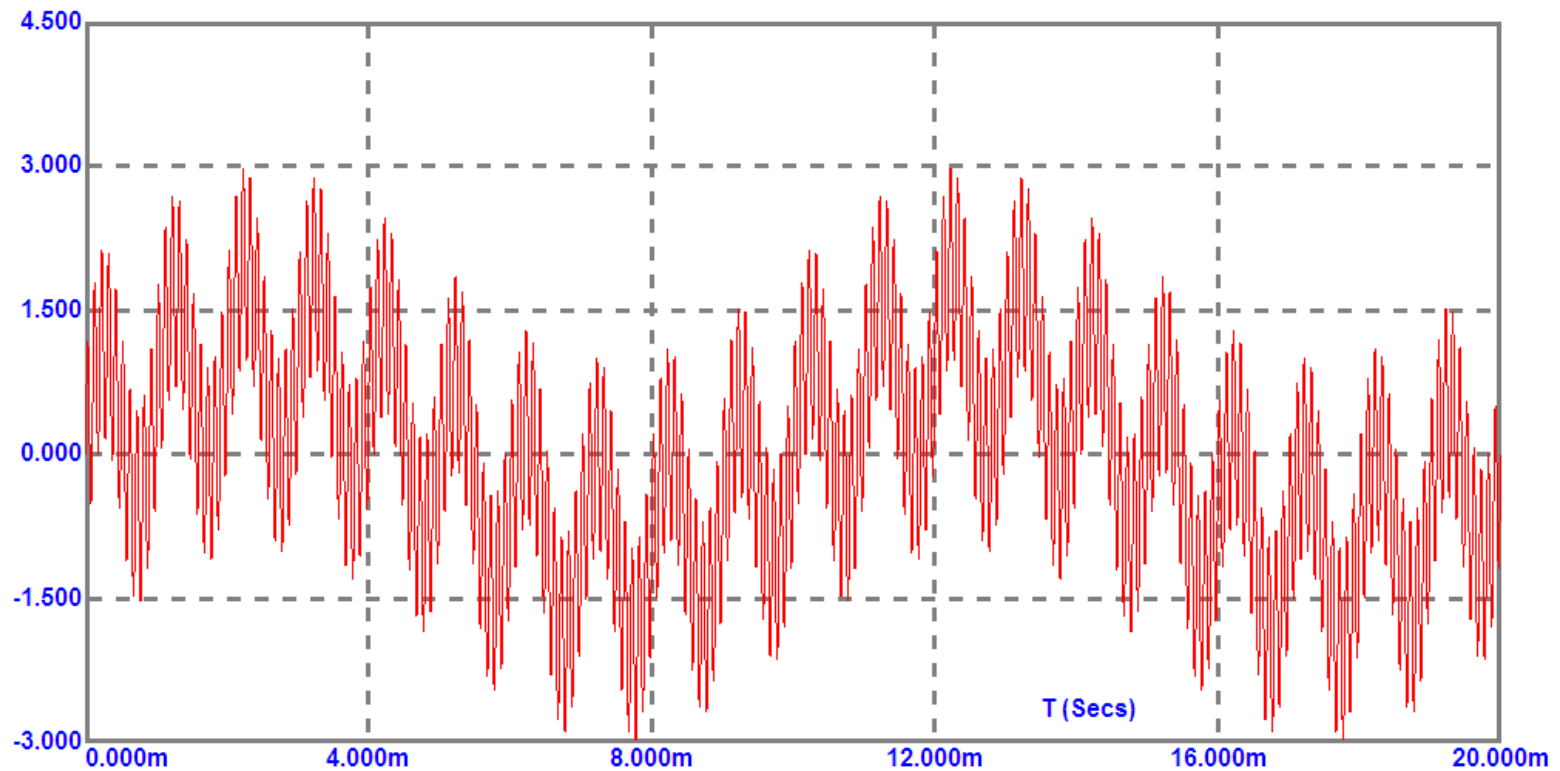

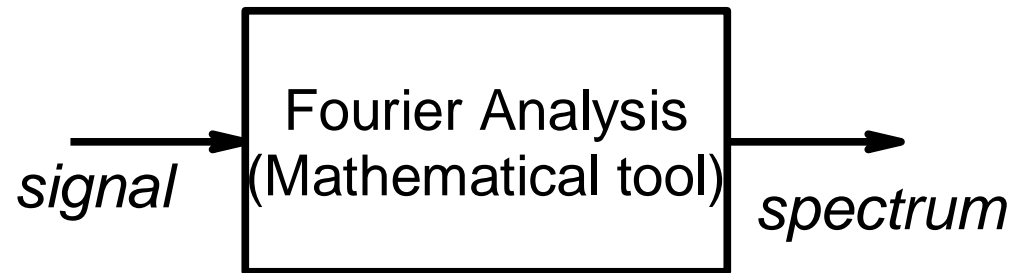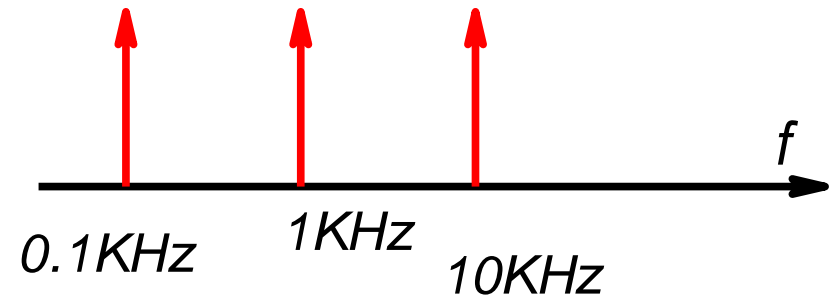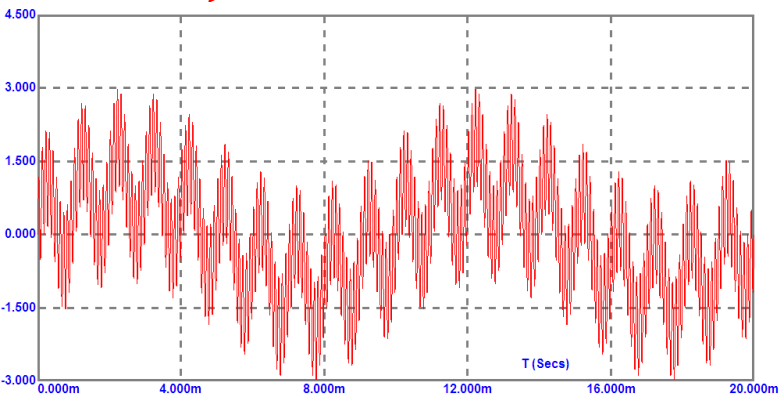
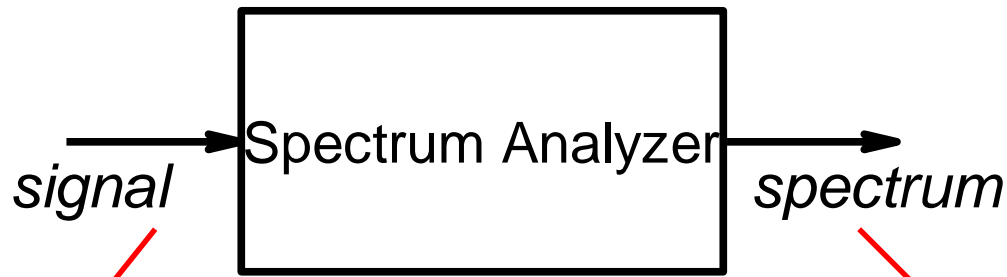


## Speech signal

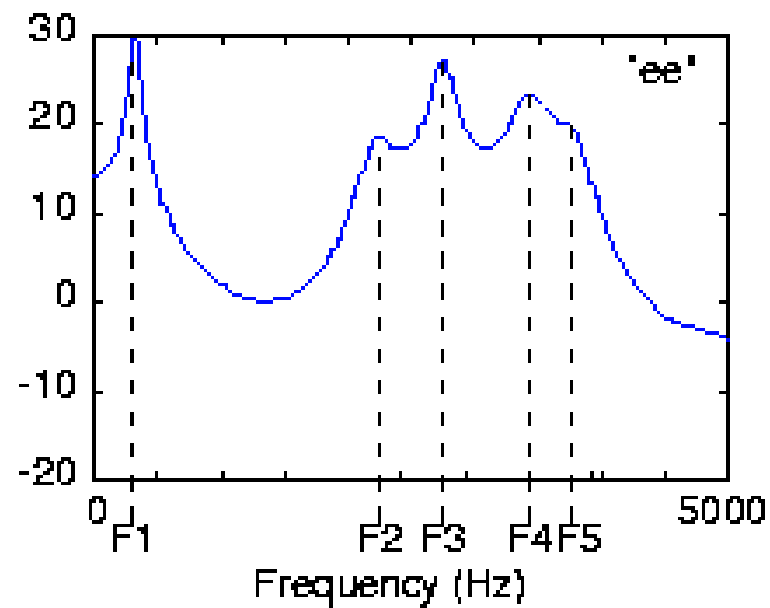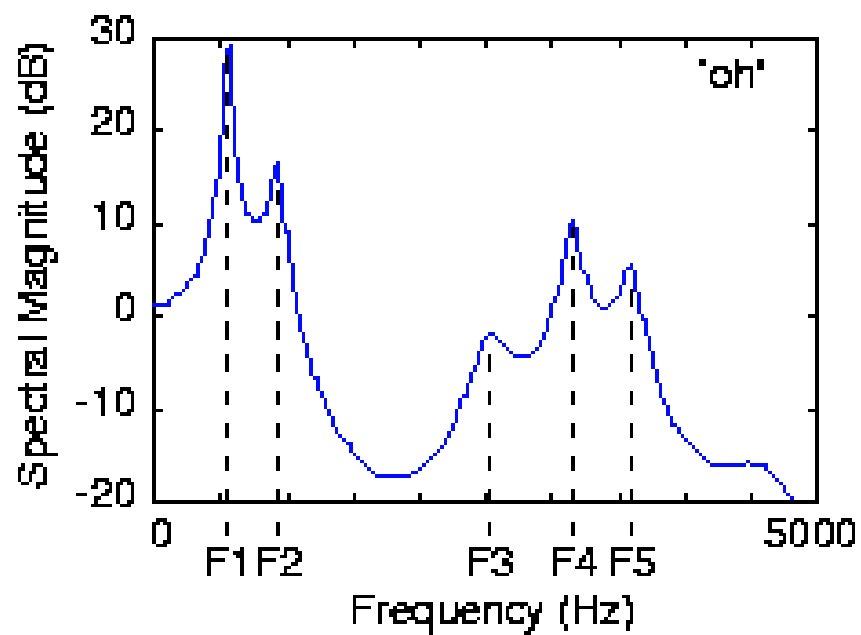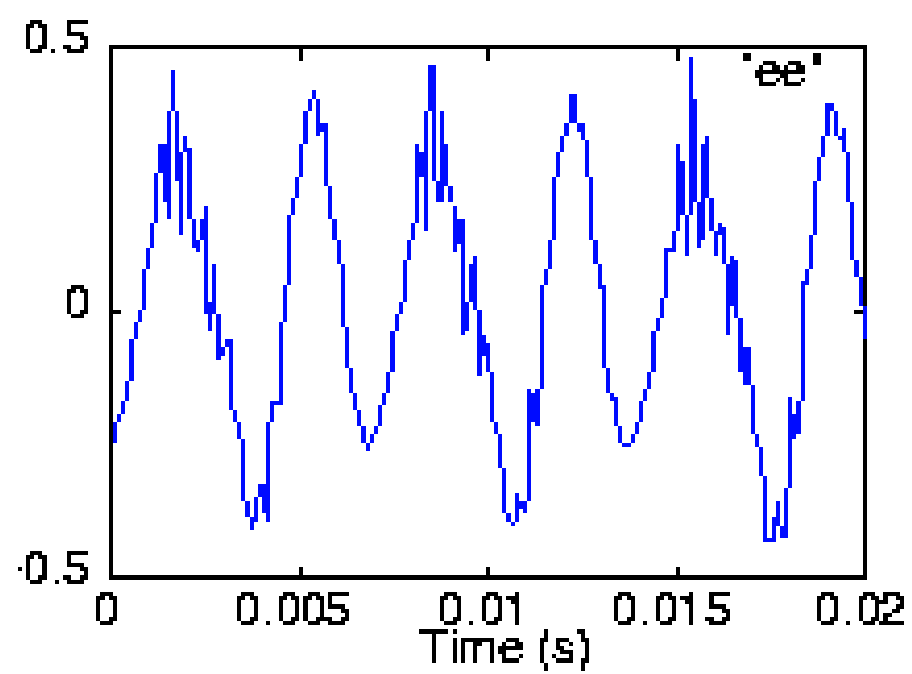
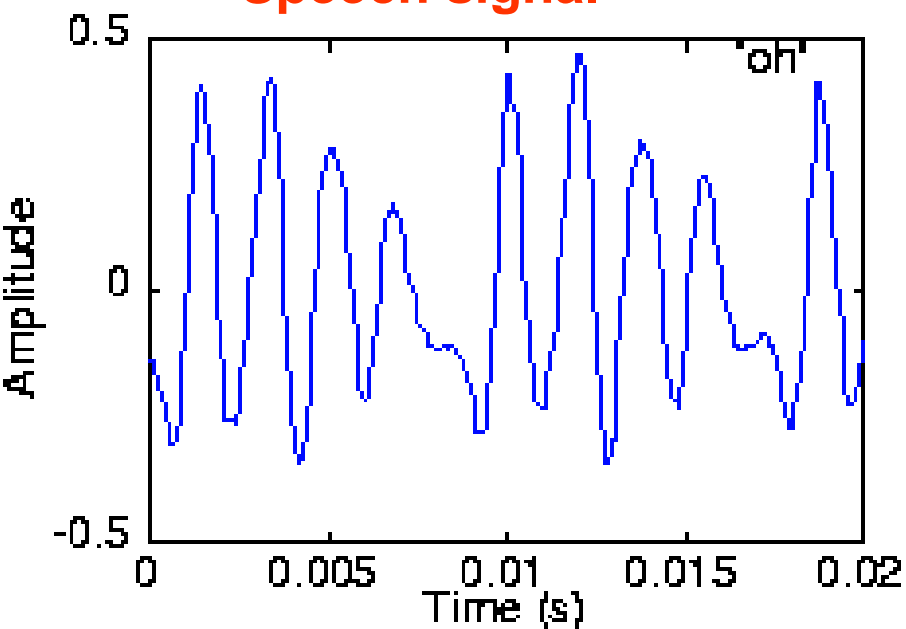


# System

What does this circuit do ?

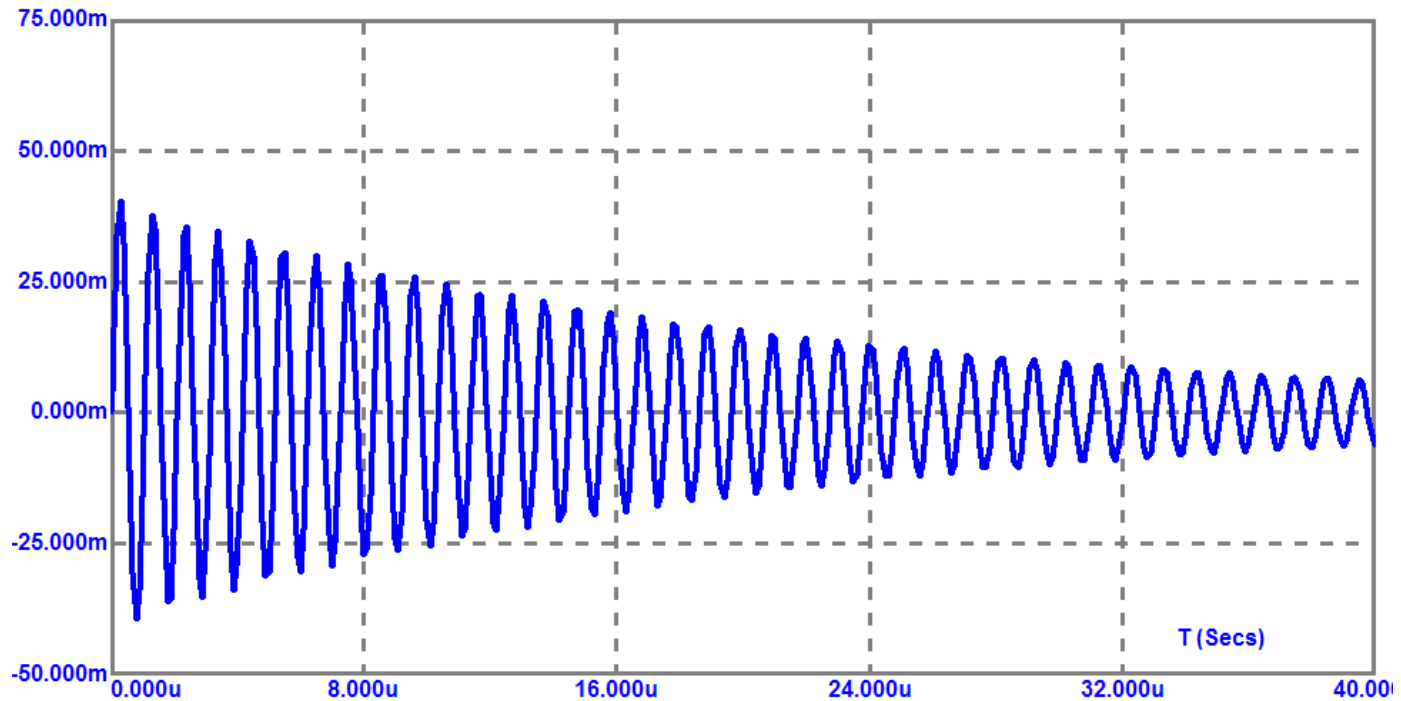
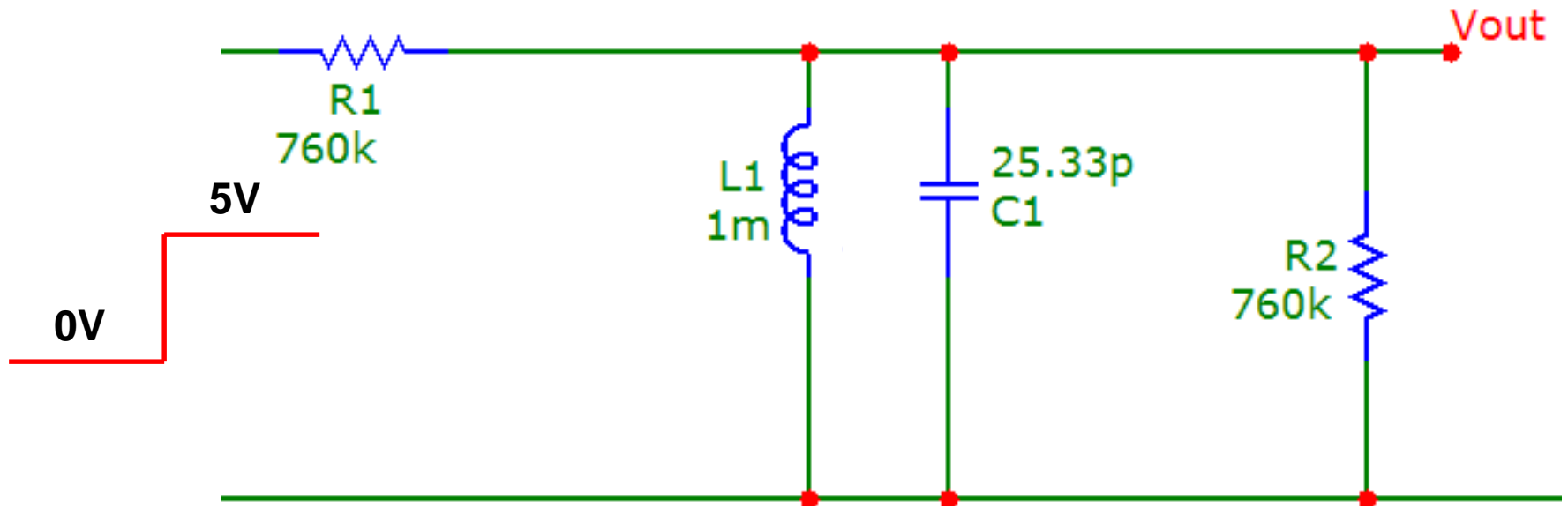


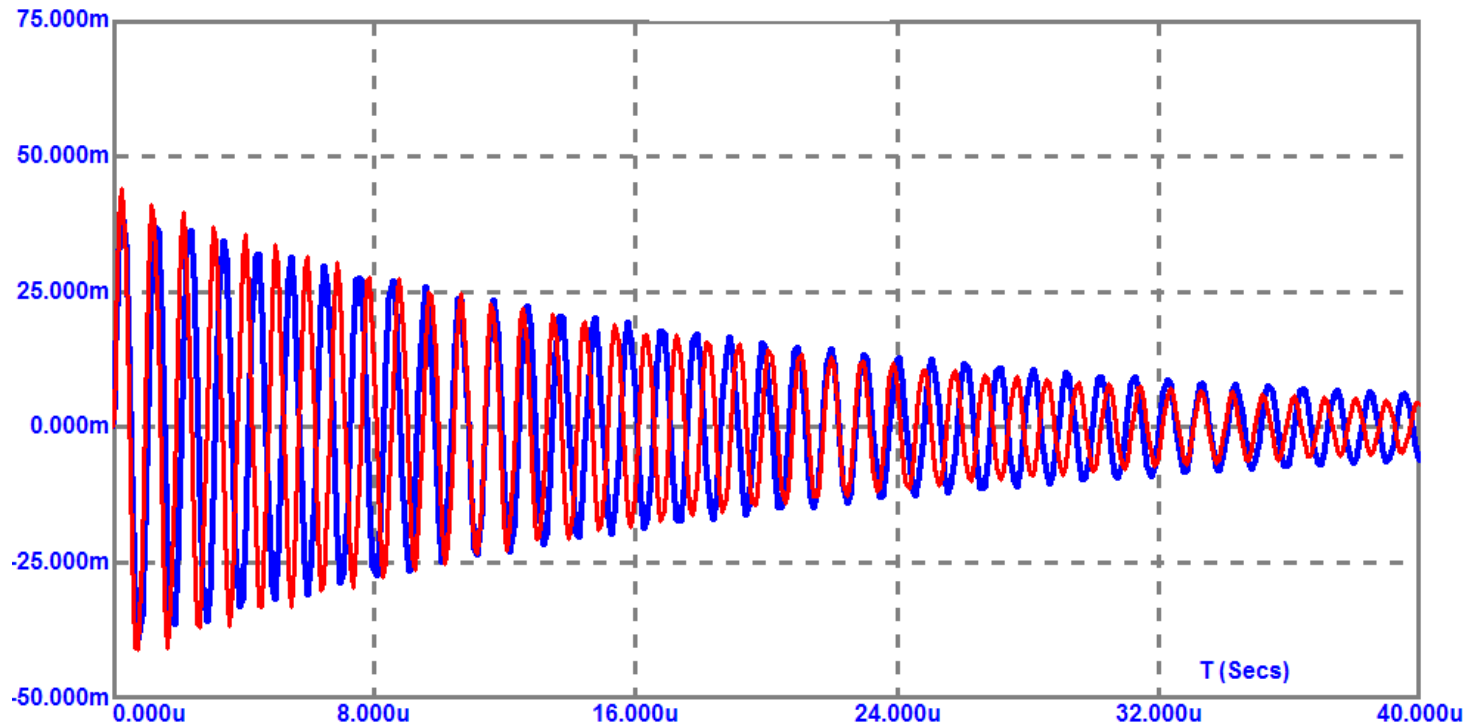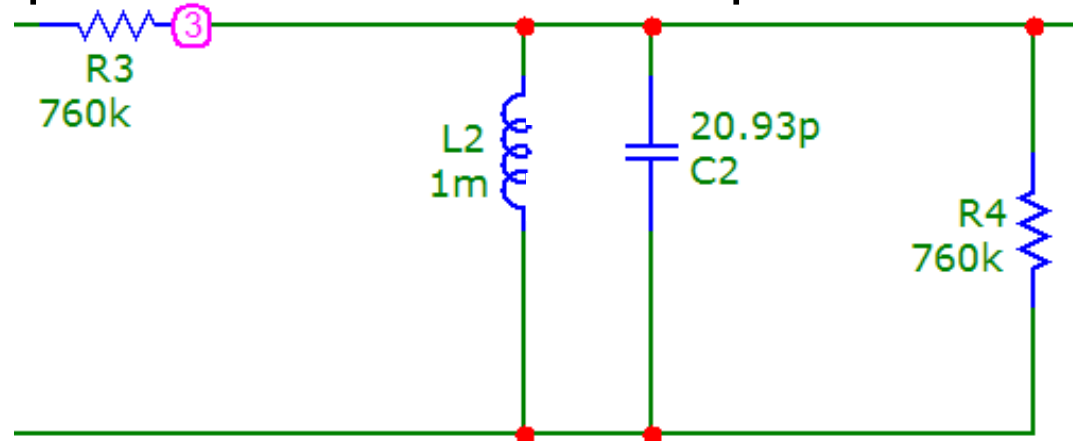Suppose the capacitor is reduced to  $\sim 21\text{pF}$ .





It is hard to find out what impact the change in capacitor has on circuit behavior

# Frequency domain analysis

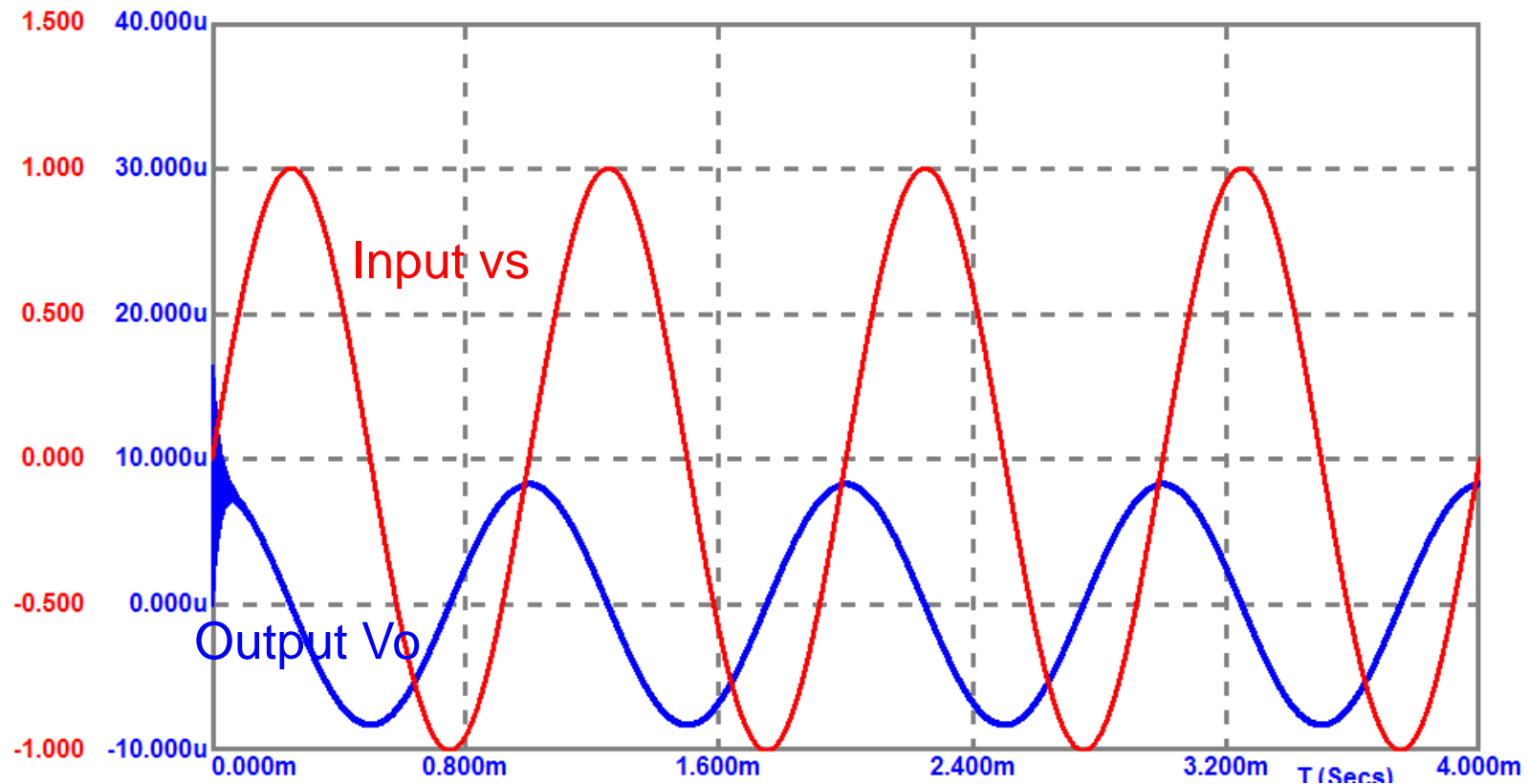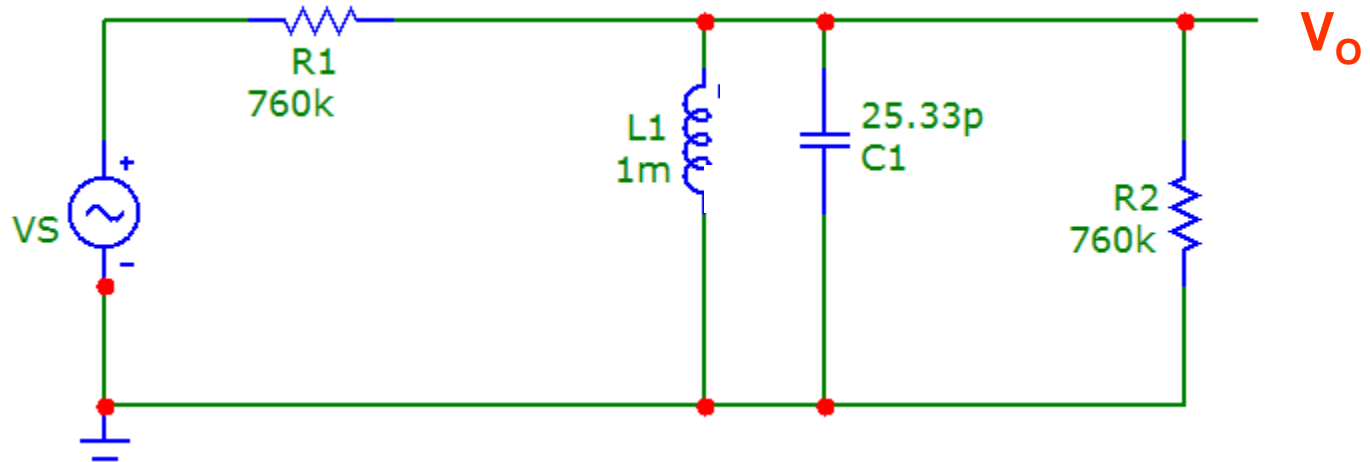


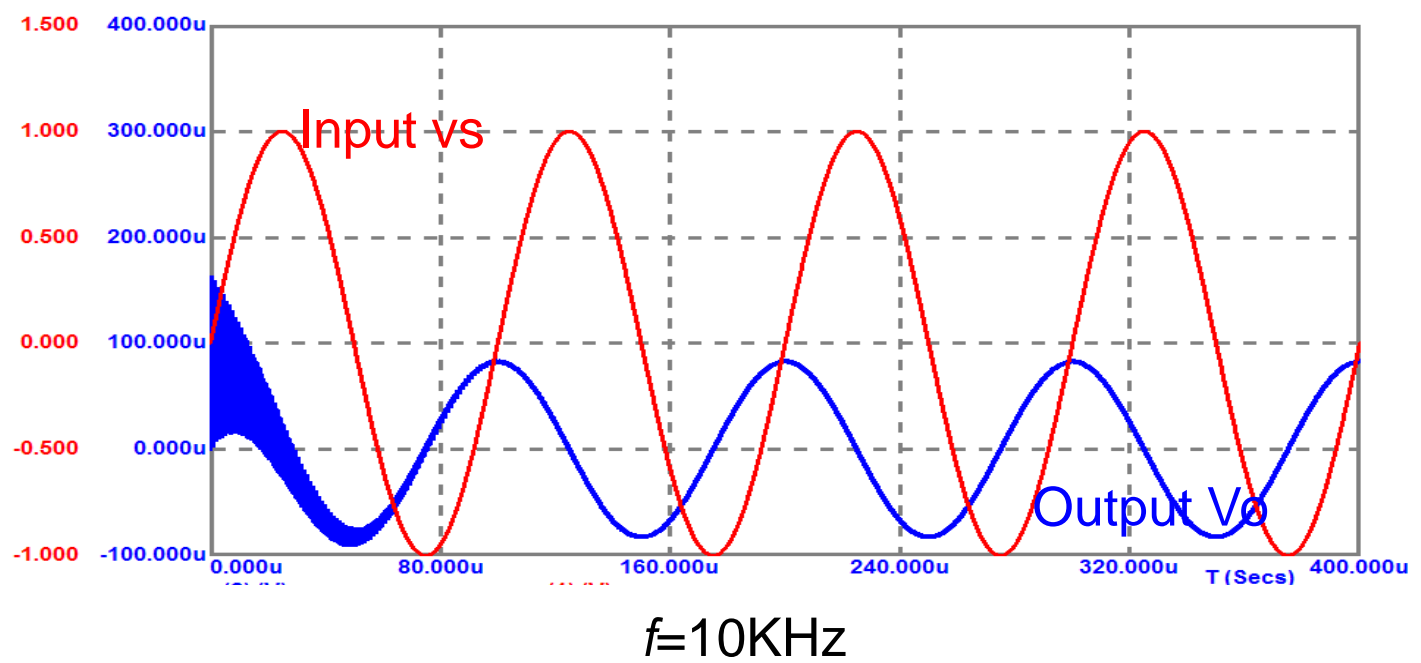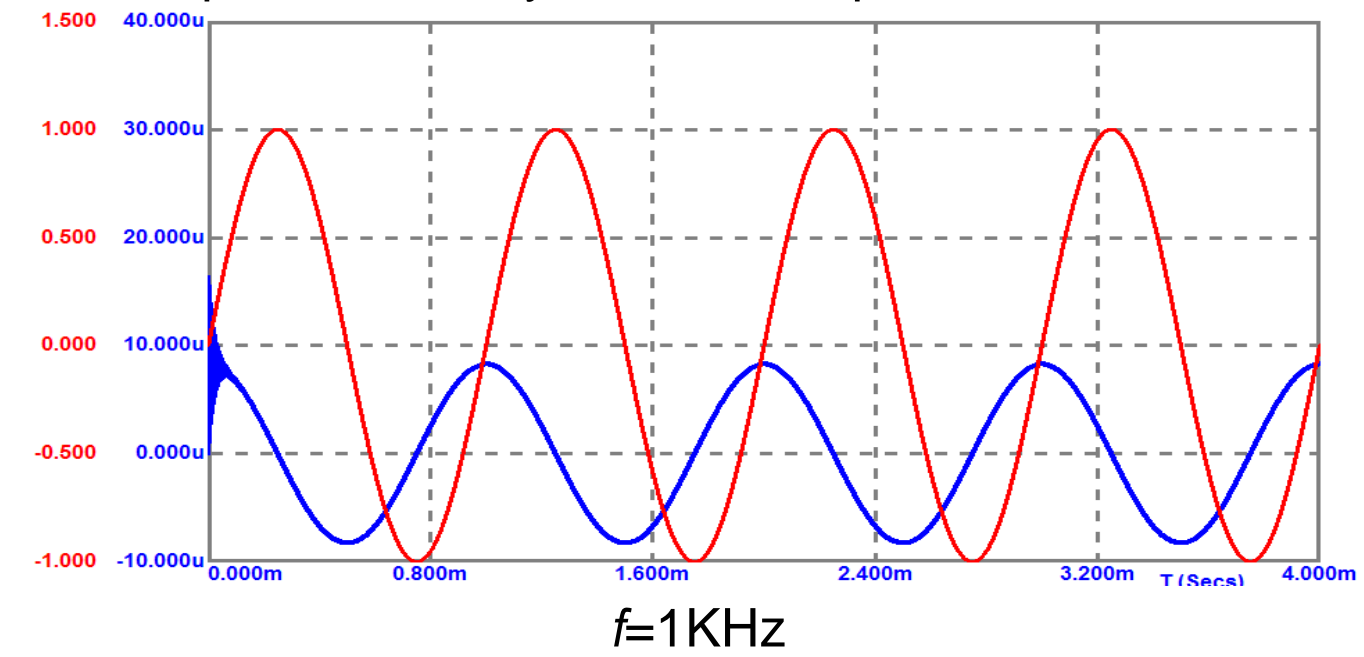Measure response at many different frequencies for a constant input amplitude






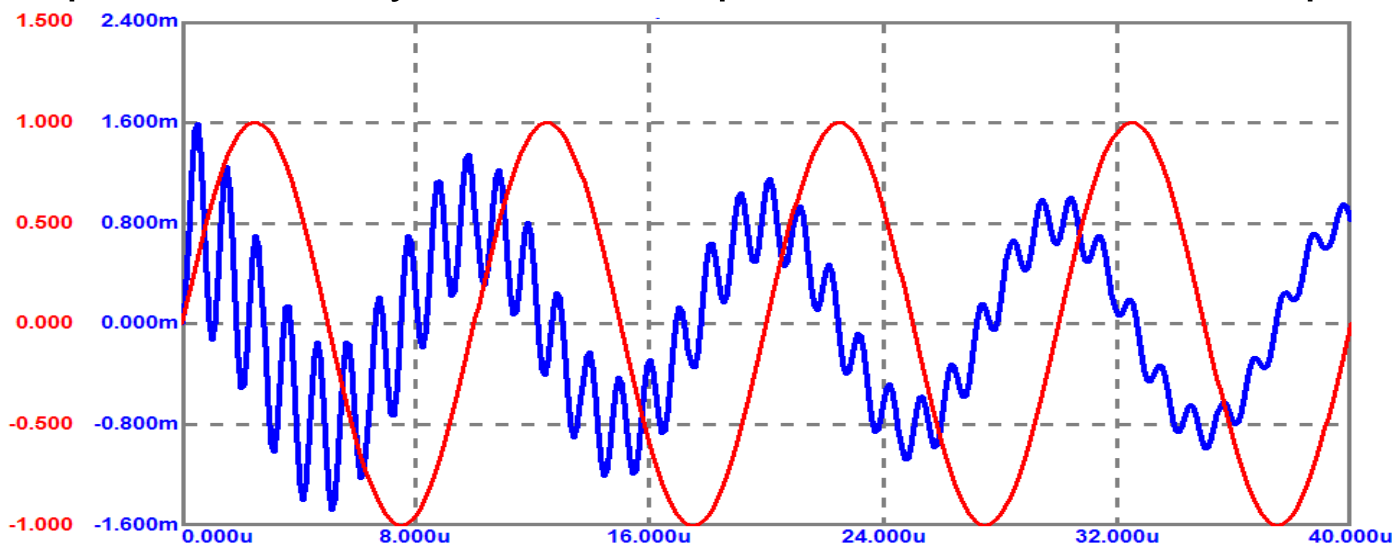Measure response at many different frequencies for a constant input amplitude




$f=100\text{KHz}$

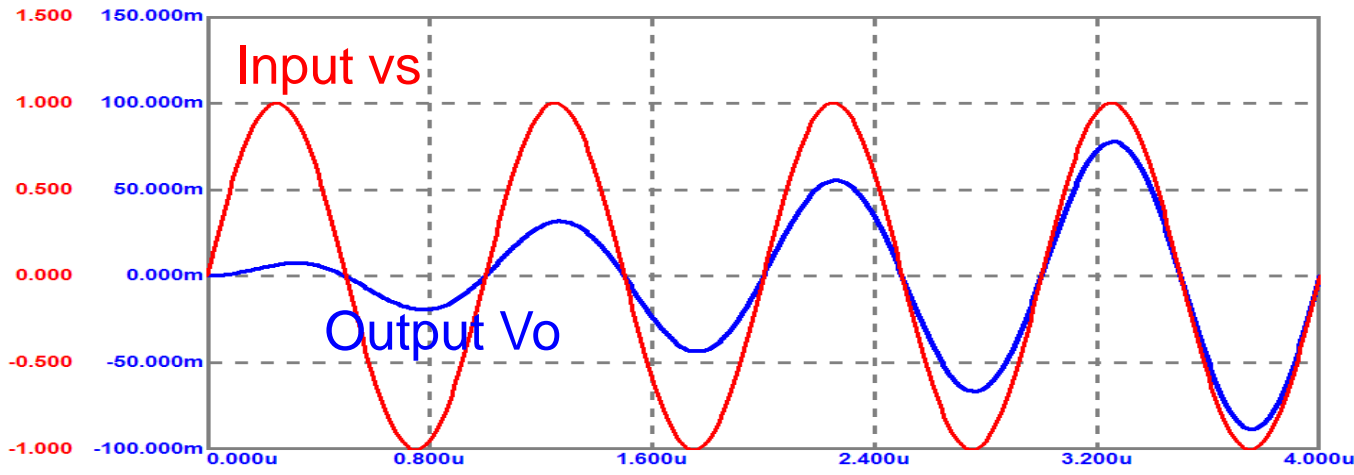

$f=1000\text{KHz}$


Plot the amplitude and phase as a function of frequency

Amplitude as a function of frequency



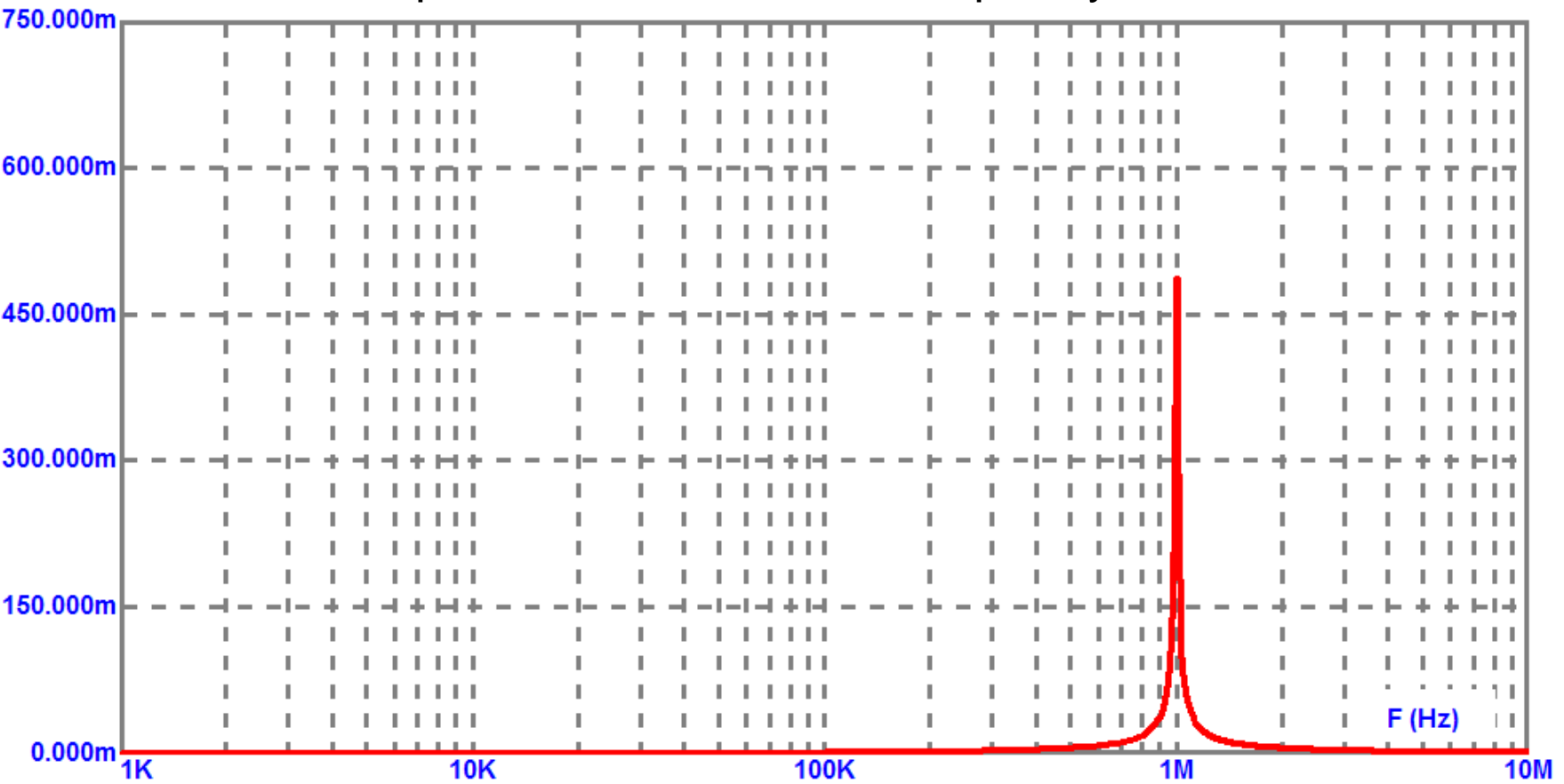


One can clearly see the frequency selective (often called a filter) nature of the circuit

Phase as a function of frequency

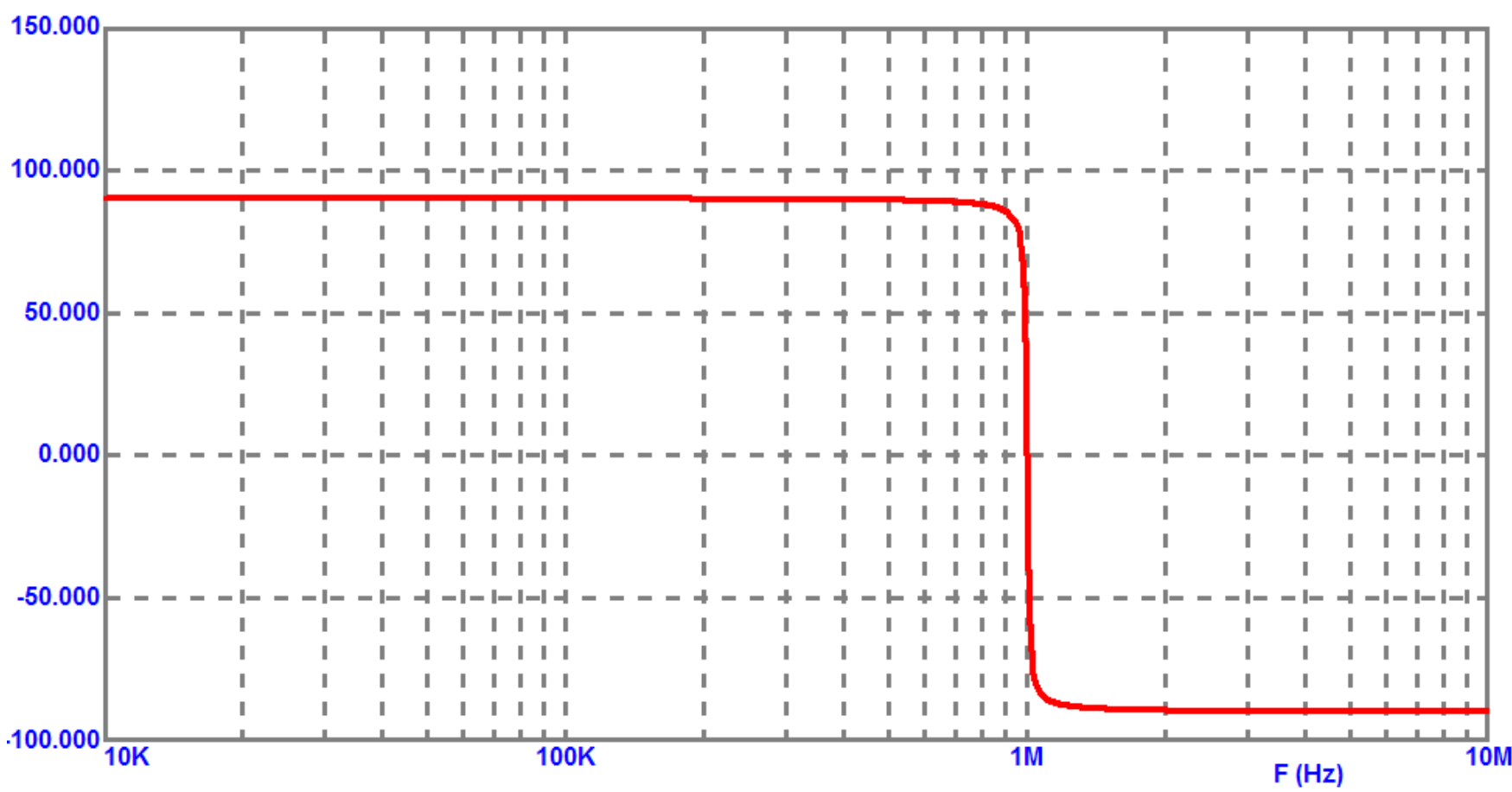

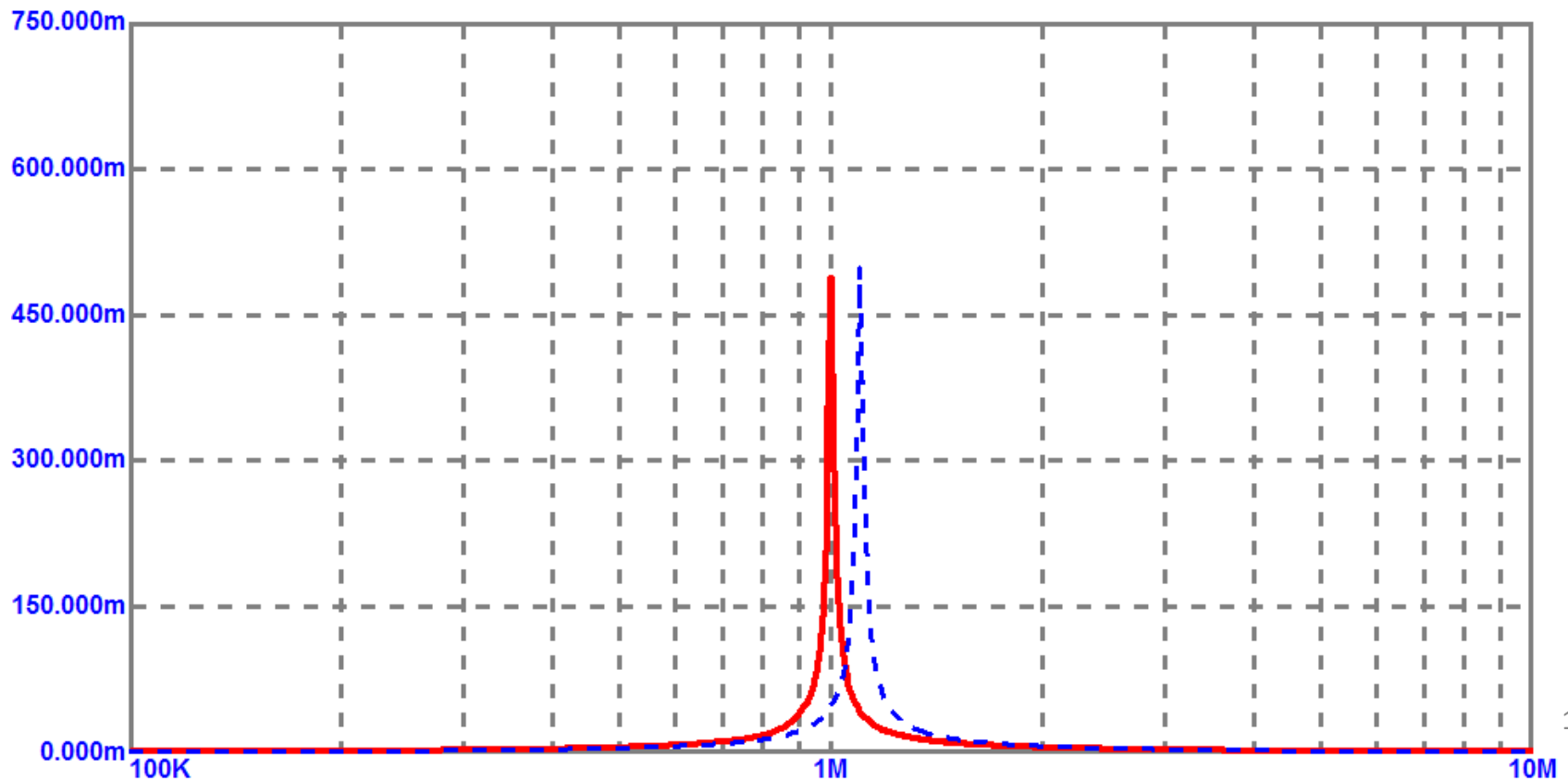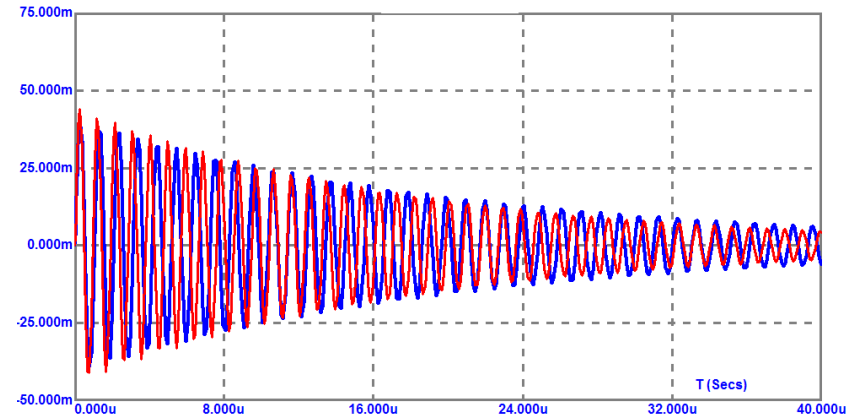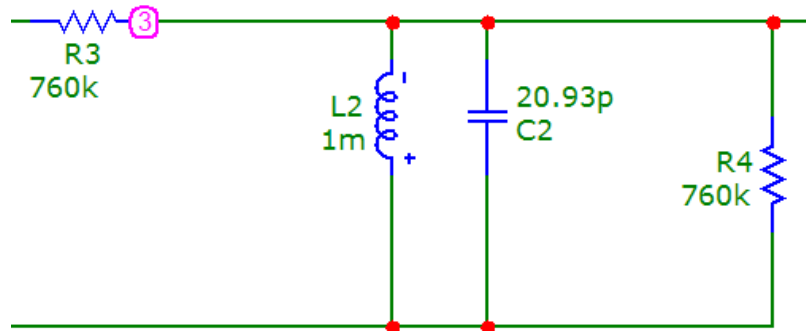
Suppose the capacitor is reduced to  $\sim 21\text{pF}$ .



***Analysis of signals and systems in frequency domain often provides useful insight into their behavior.***
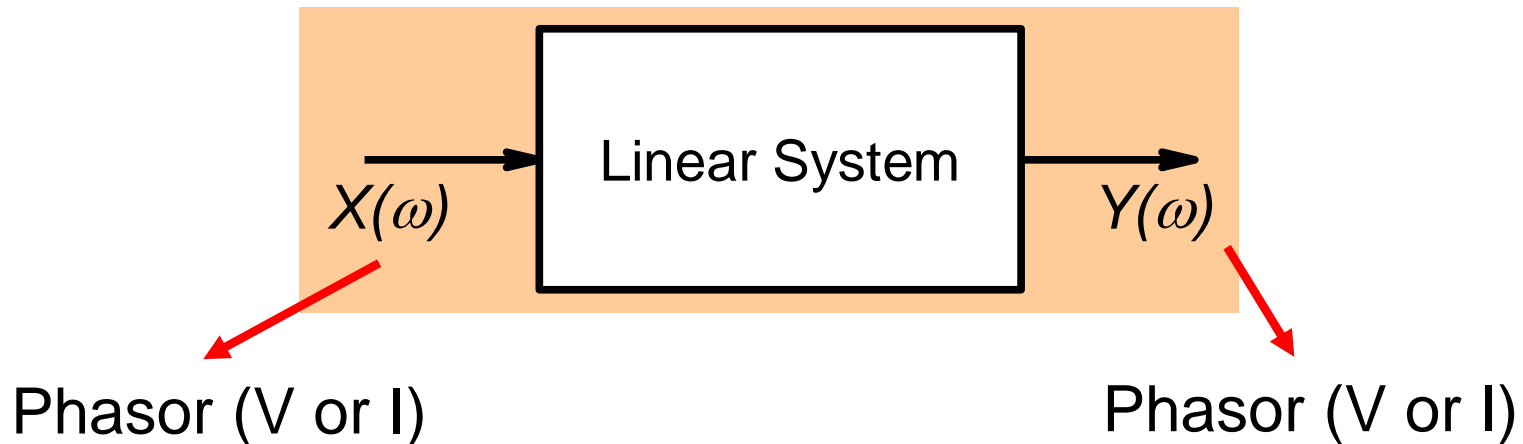
# Frequency domain analysis

Transfer function is a useful tool for finding the frequency response of a system



$$\text{Transfer Function: } H(\omega) = \frac{Y(\omega)}{X(\omega)}$$

Transfer function has a magnitude and a phase

$$H(\omega) = \frac{Y(\omega)}{X(\omega)}$$



$$\mathbf{H}(\omega) = \text{Voltage gain} = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Current gain} = \frac{\mathbf{I}_o(\omega)}{\mathbf{I}_i(\omega)}$$

$$\mathbf{H}(\omega) = \text{Transfer Impedance} = \frac{\mathbf{V}_o(\omega)}{\mathbf{I}_i(\omega)}$$


$$\mathbf{H}(\omega) = \text{Transfer Admittance} = \frac{\mathbf{I}_o(\omega)}{\mathbf{V}_i(\omega)}$$

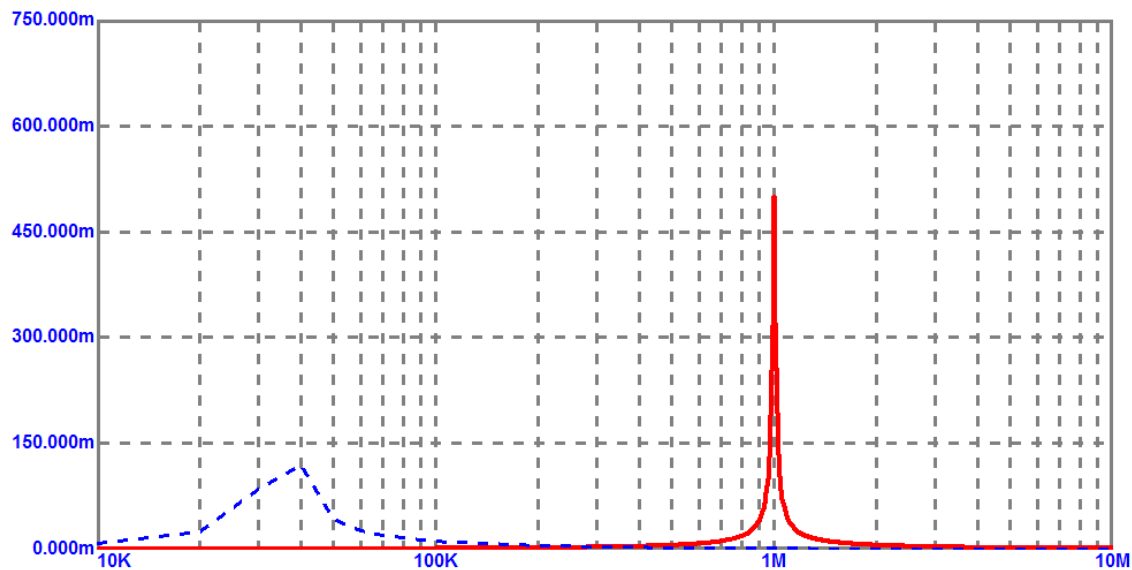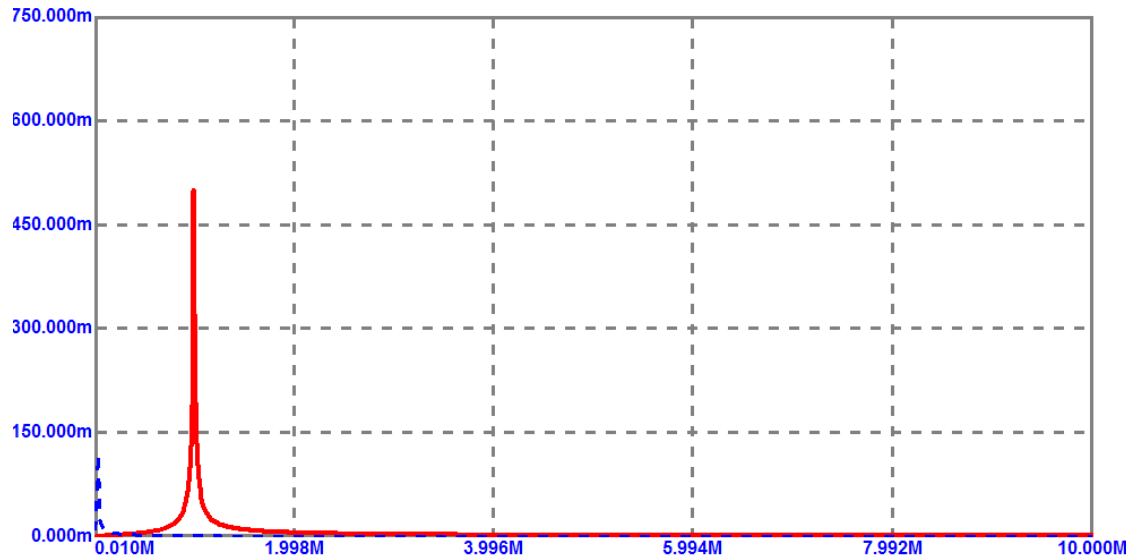Because of the wide dynamic range of frequency, plotting frequency on log axis is often more revealing !






# Logarithmic frequency scale

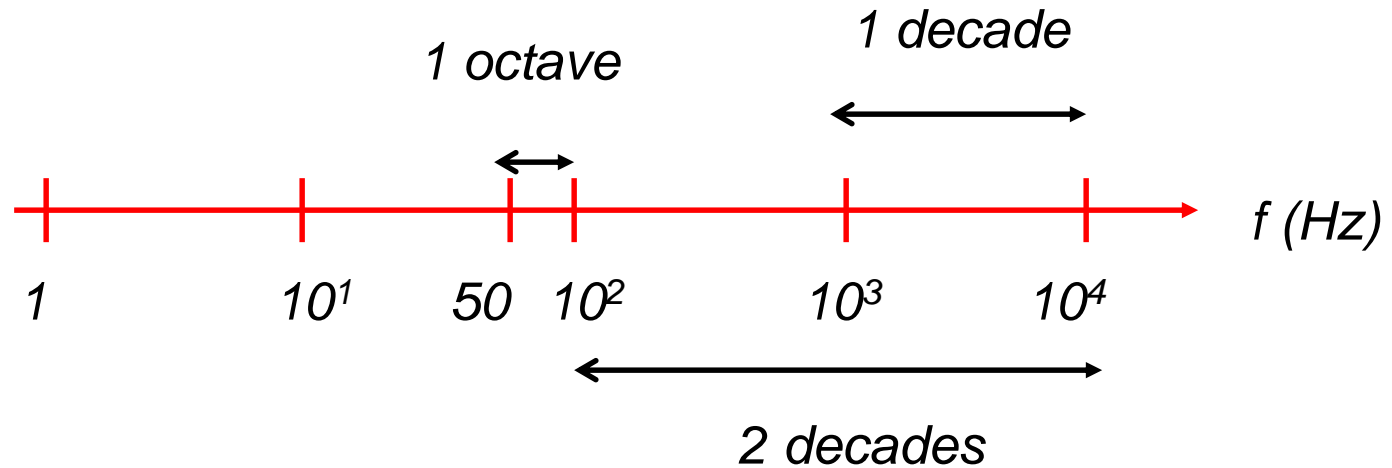

$$\text{No. of decades} = \log_{10}\left(\frac{f_2}{f_1}\right)$$

$$\text{No. of octaves} = \log_2\left(\frac{f_2}{f_1}\right) = \frac{\log_{10}\left(\frac{f_2}{f_1}\right)}{\log_{10}(2)}$$
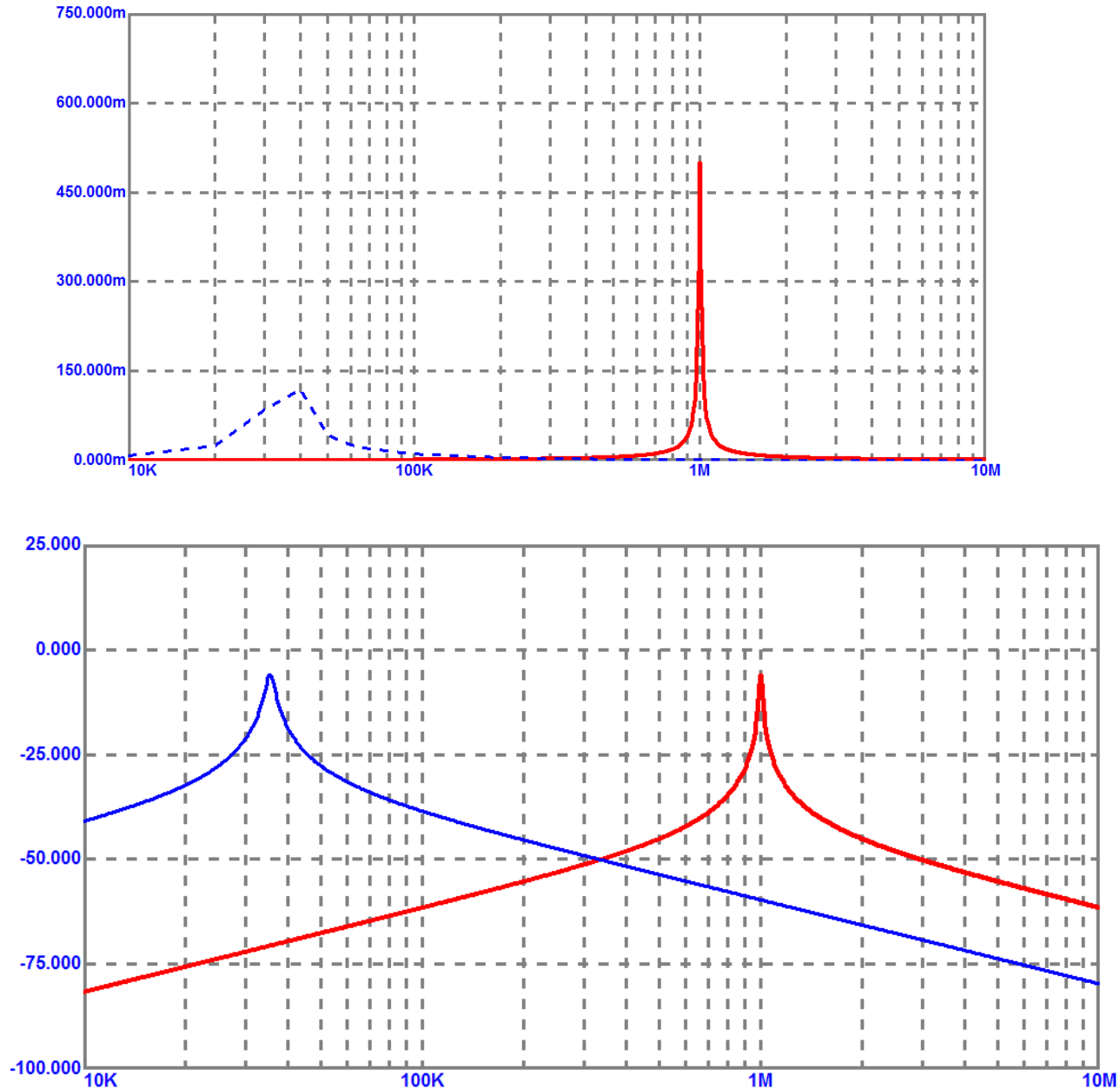
# Decibel scale often reveals more information about behavior



The magnitude of transfer function is often specified in **decibels**

$$G_{dB} = 10 \log_{10} \left( \frac{P_2}{P_1} \right)$$

Because power is proportional to  $V^2$  or  $I^2$ , voltage gain and current gain in decibels is specified as


$$G_{dB} = 20 \log_{10} \left( \frac{V_2}{V_1} \right)$$

$$G_{dB} = 20 \log_{10} \left( \frac{I_2}{I_1} \right)$$

# Decibel Scale


$ H $	$20\text{Log}_{10}( H )$
1000	60
100	40
10	20
2	6
$\sqrt{2}$	3
1	0
$1/\sqrt{2}$	-3
0.5	-6
0.1	-20
0.01	-40

# dB Scale

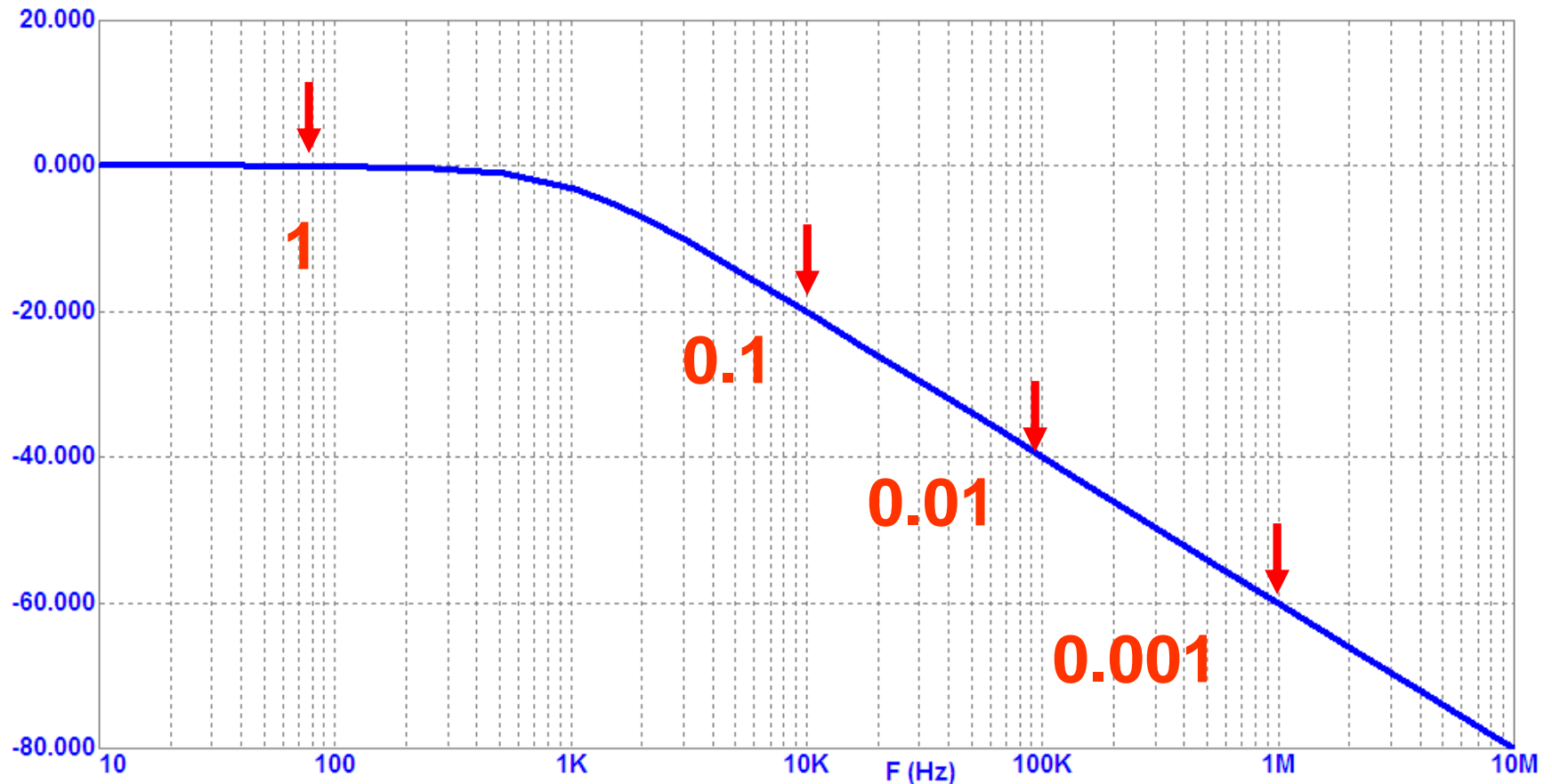

A plot of the decibel magnitude of transfer function versus frequency using a logarithmic scale for frequency is called a **Bode plot**
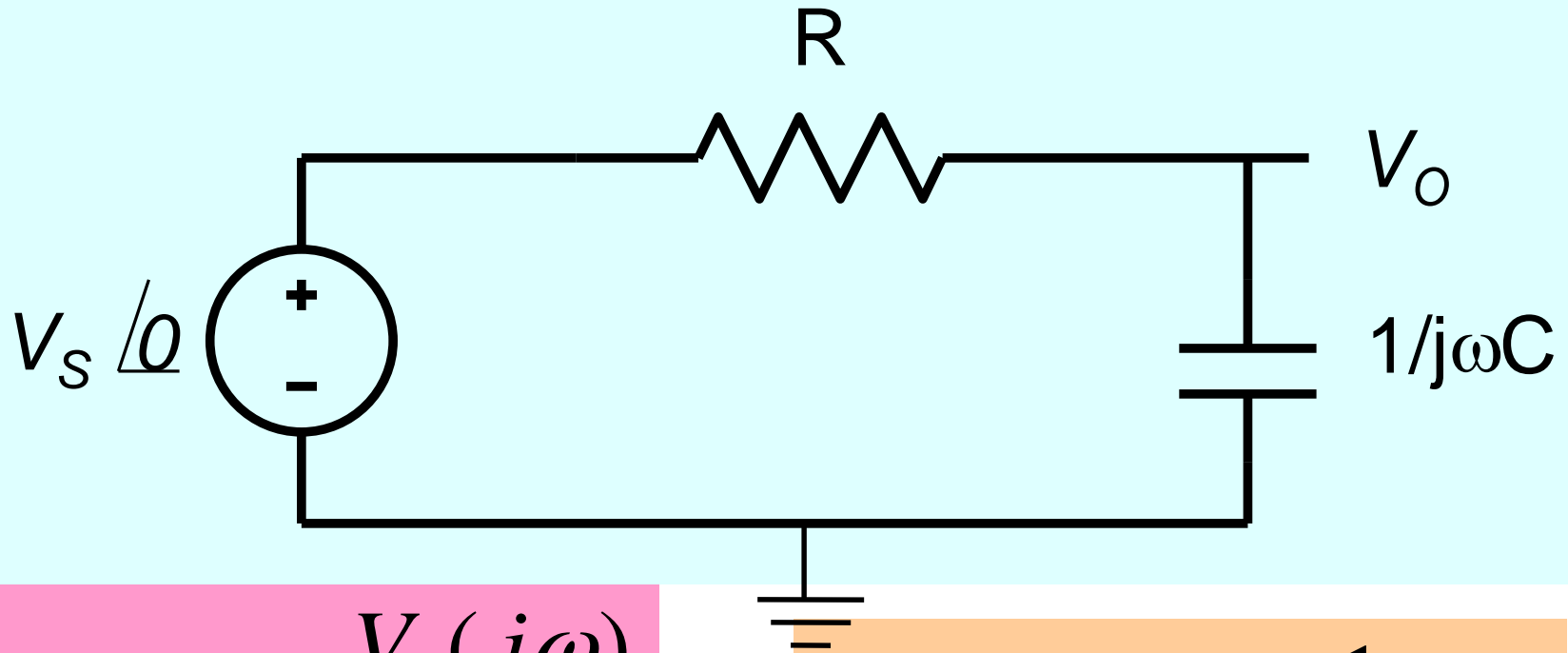
# How to determine the transfer function?



$$H(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$\phi(\omega) = -\tan^{-1}(\omega CR)$$

# Plot Magnitude

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

$$H_{dB} = -20 \log_{10} \sqrt{1 + (\omega RC)^2}$$

$$\omega_{3dB} = \frac{1}{RC}$$

$$H_{dB} = -20 \log_{10} \sqrt{1 + \left( \frac{\omega}{\omega_{3dB}} \right)^2}$$

$$\omega \ll \omega_{3dB}$$

$$H_{dB} \approx -20 \log_{10}(1) = 0$$

$$\omega \gg \omega_{3dB}$$

$$H_{dB} \approx -20 \log_{10} \left( \frac{\omega}{\omega_{3dB}} \right)$$

$$\omega \gg \omega_{3dB}$$

$$H_{dB} \approx -20 \log_{10} \left( \frac{\omega}{\omega_{3dB}} \right)$$

$\omega$	$H_{dB}$
$\omega_{3dB}$	0
$10 \omega_{3dB}$	-20
$100 \omega_{3dB}$	-40


-20 dB per decade

$$\log_{10} 10 = 1$$



3dB point

$$\omega_{3dB} = \frac{1}{RC}$$

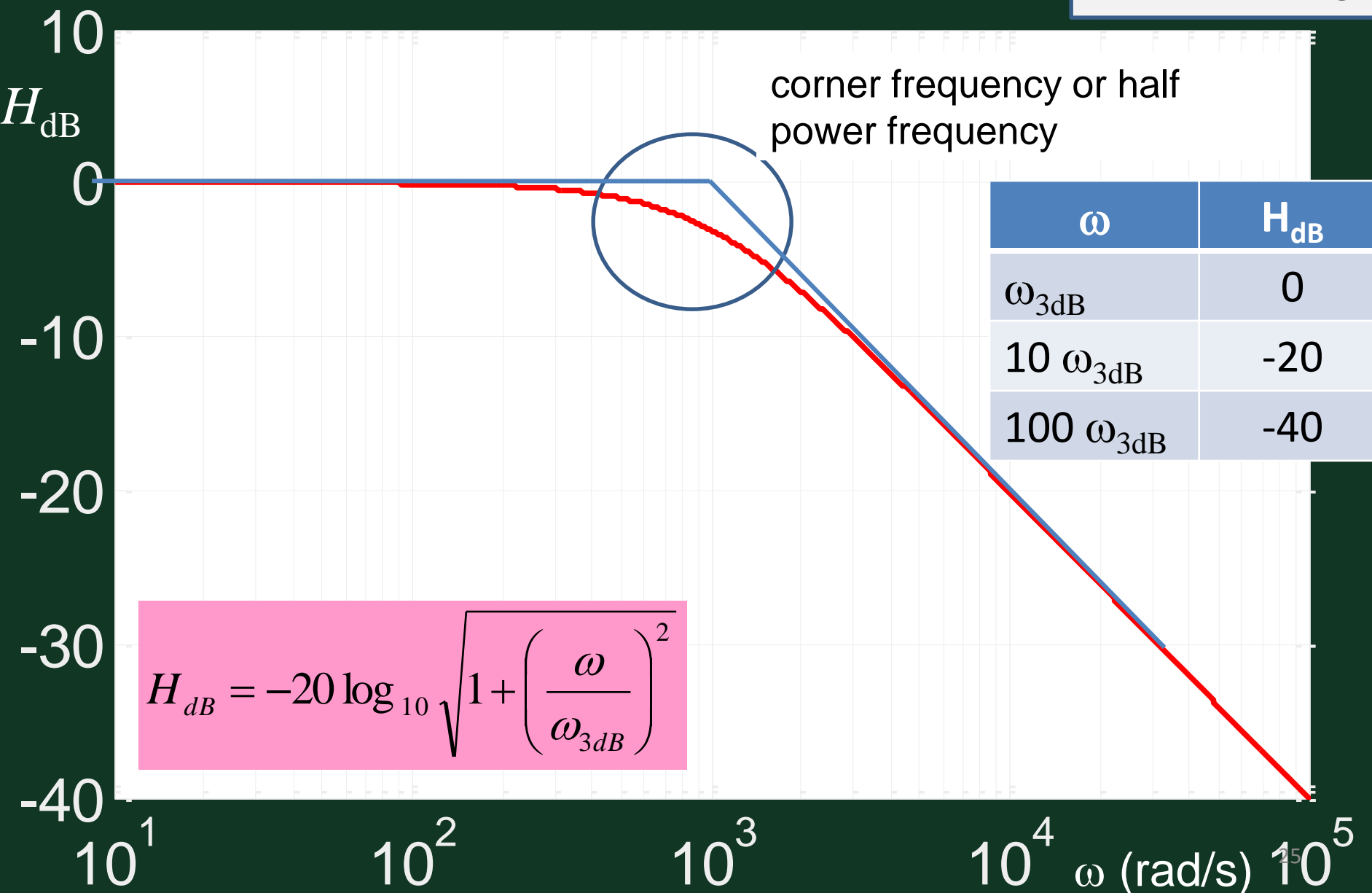

# Example


$$H(j\omega) = \frac{10}{1 + j\omega 10^{-3}}$$




$$\omega_{3dB} = 10^3$$

$$H_{dB} = 20 - 20 \log_{10} \sqrt{1 + \left( \frac{\omega}{10^3} \right)^2}$$

$$\omega \ll 10^3 : 0dB$$

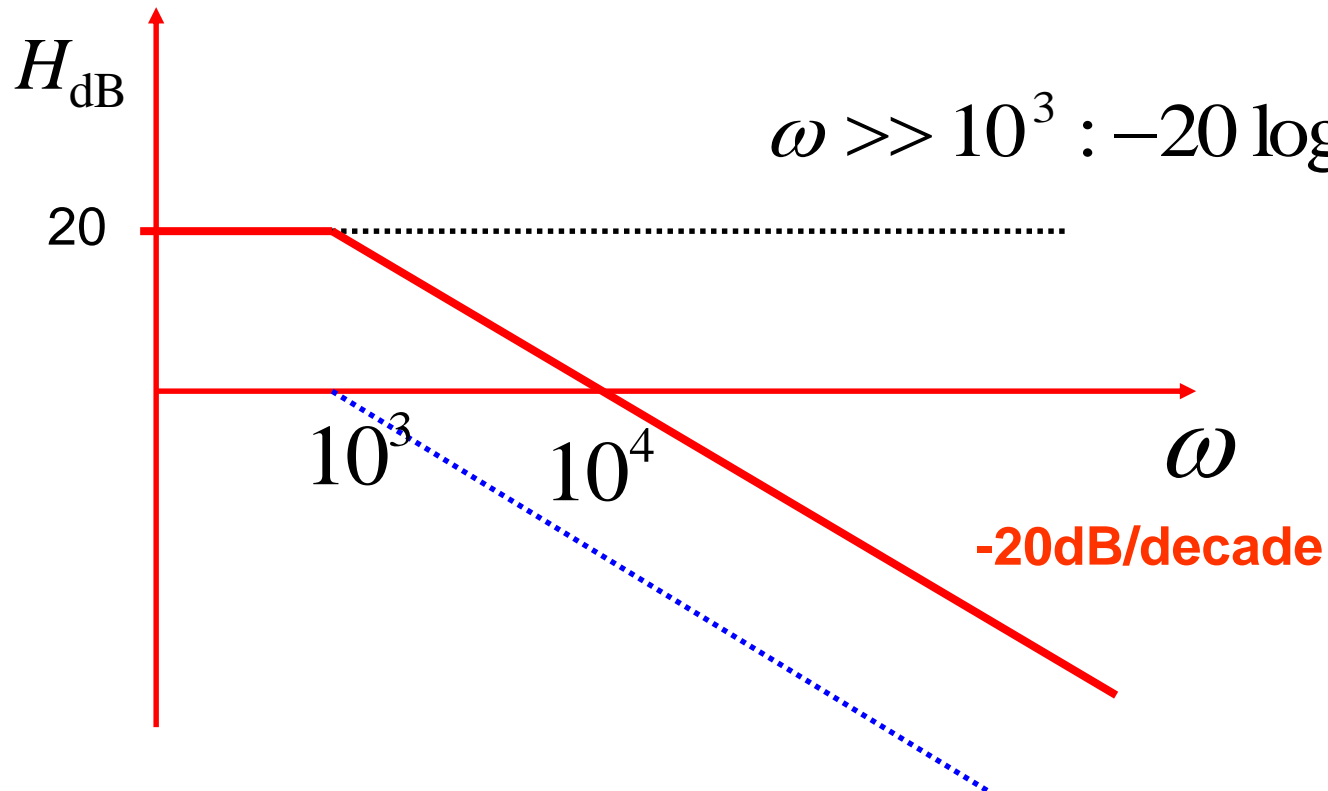
$$\omega \gg 10^3 : -20 \log_{10} \frac{\omega}{10^3}$$



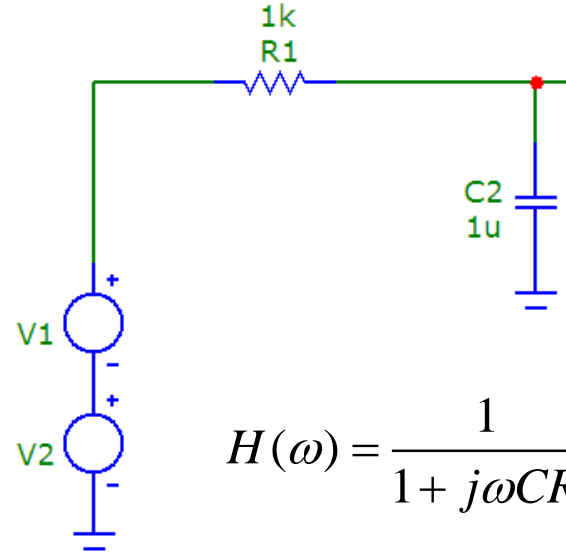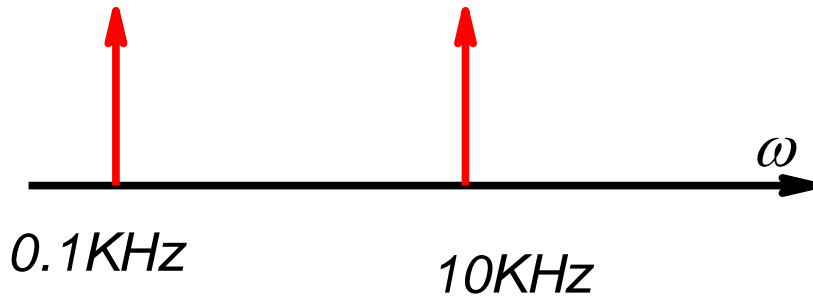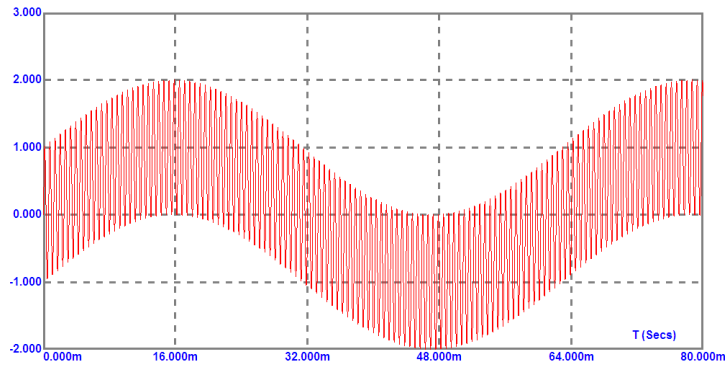






$$H(\omega) = \frac{1}{1 + j\omega CR}$$



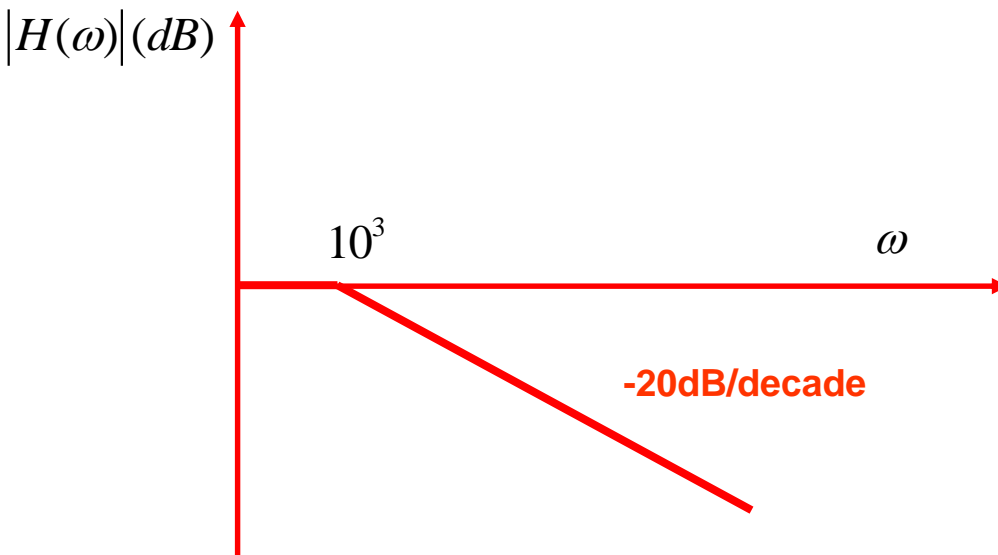
$$H(\omega) = \frac{1}{1 + j\omega 10^{-3}} = \frac{1}{1 + j \frac{\omega}{10^3}}$$


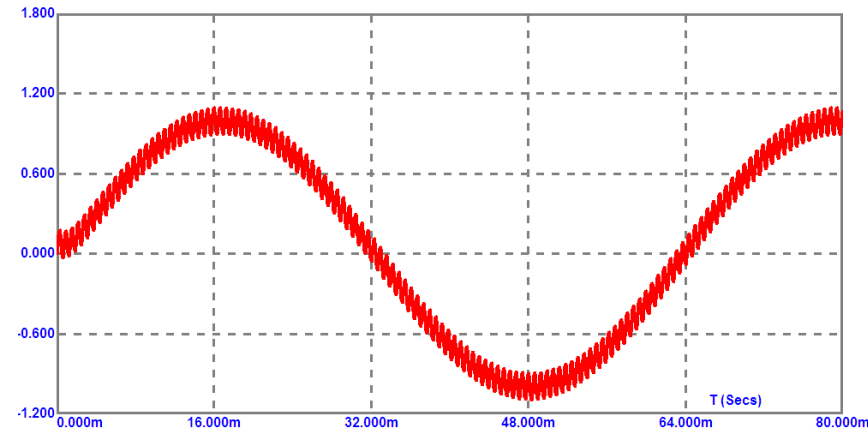
$$V_o(t) = 1\sin(100t) + 0.1\sin(10^4 t)$$



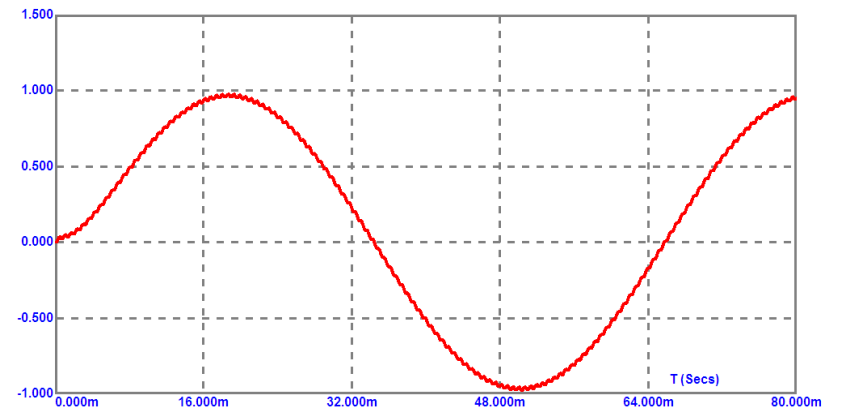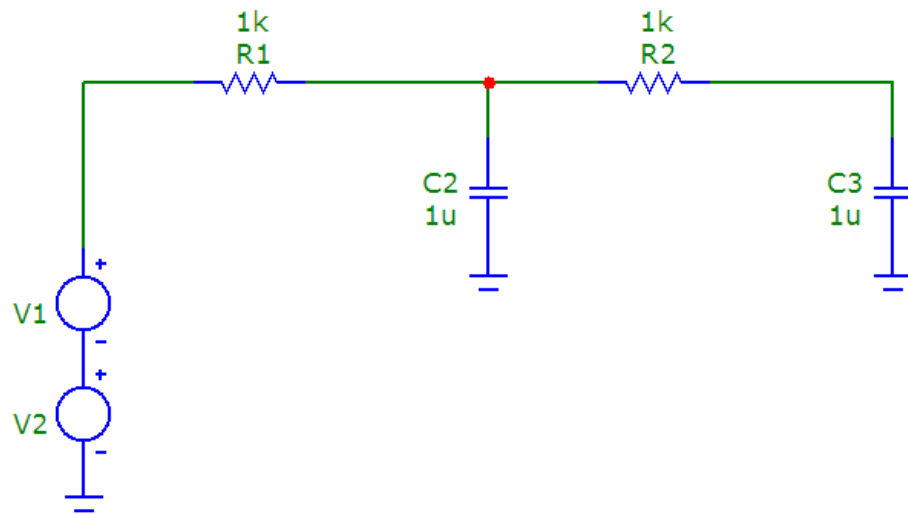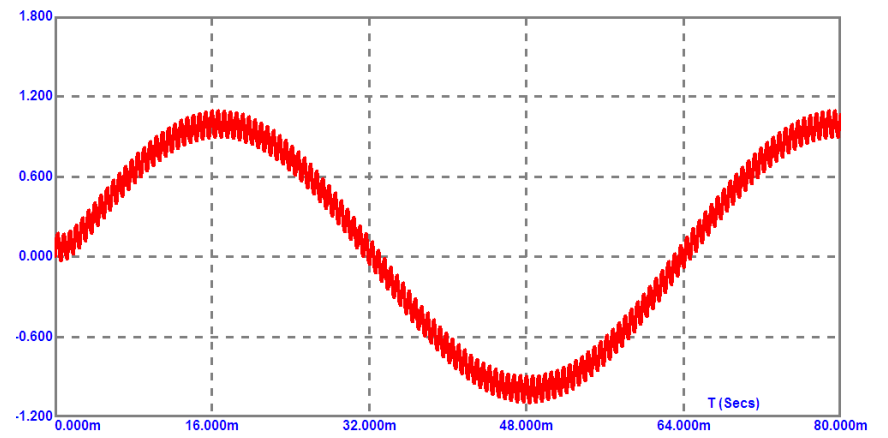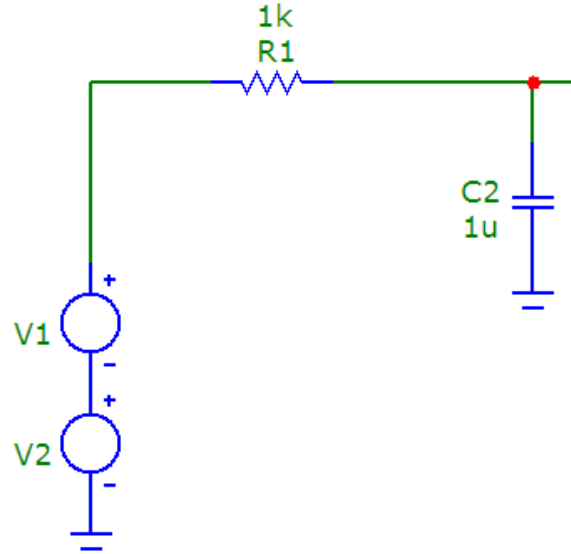

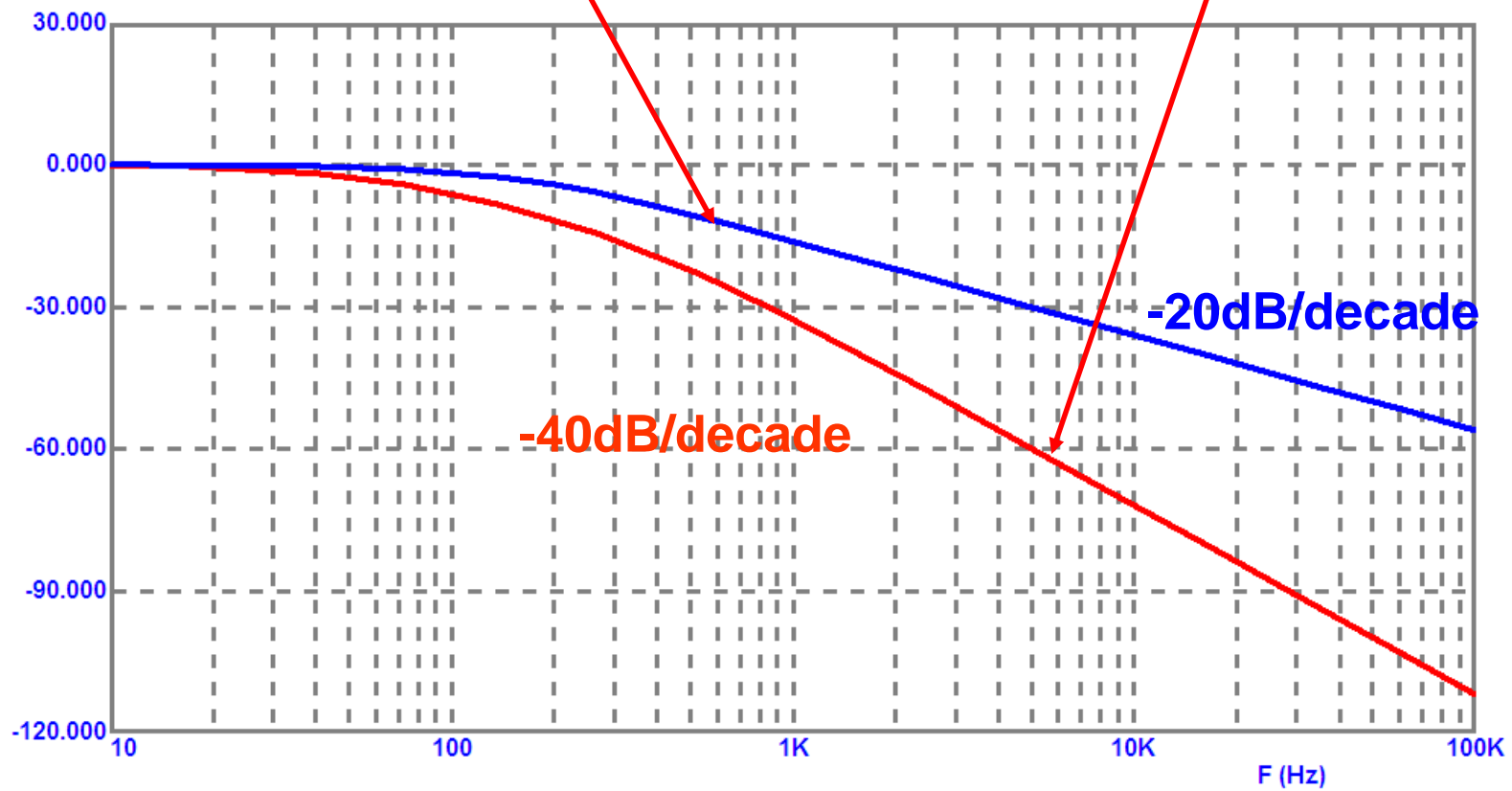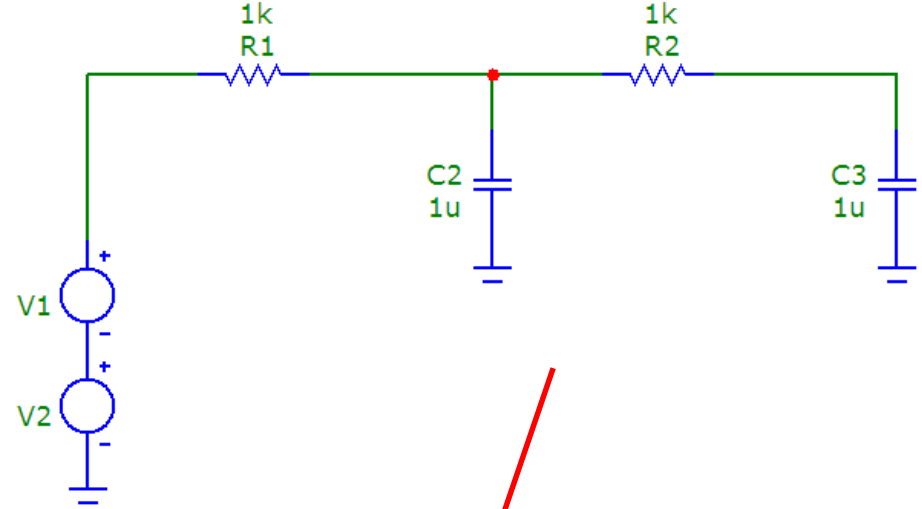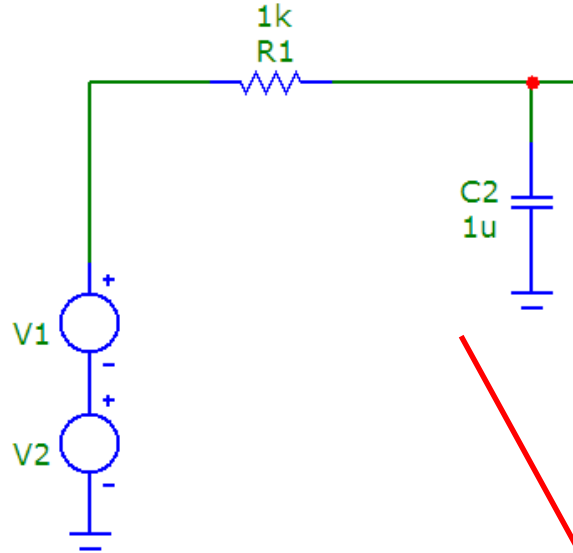

Adding more RC stages, makes the characteristics sharper

