

# **ESc201 : Introduction to Electronics**



## **Logic Gates and Minimization**

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur



How do we get the chocolate?


# Design Flow

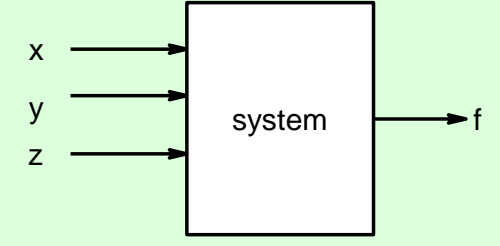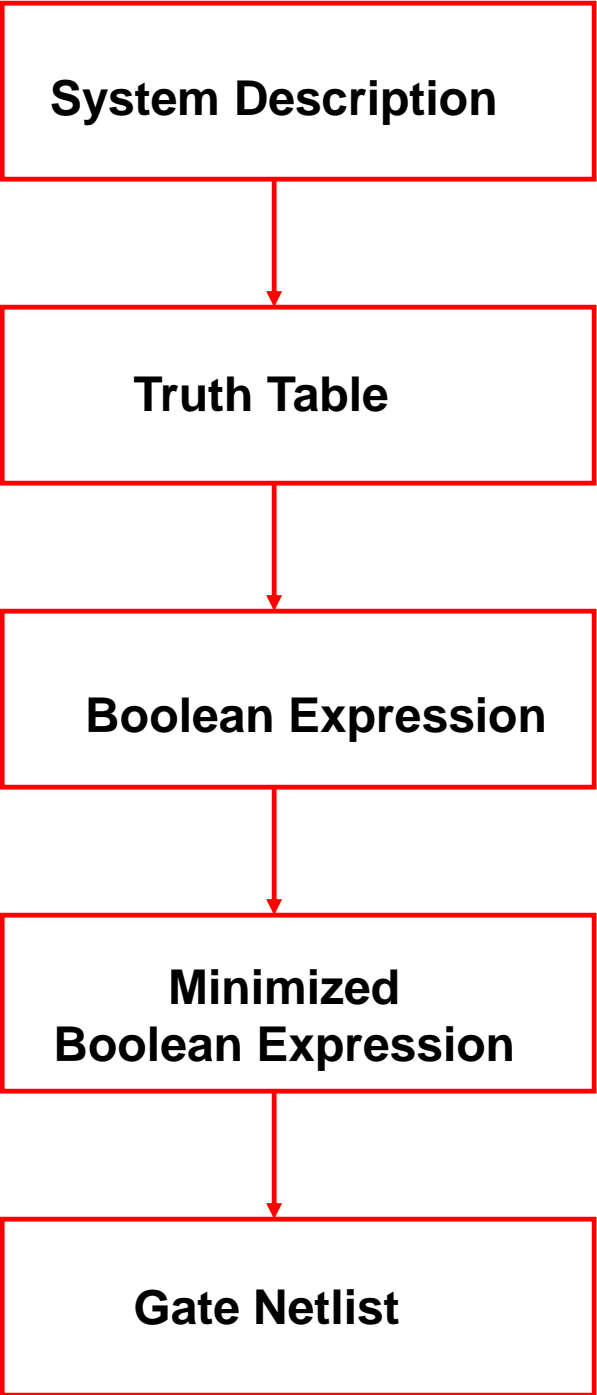

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1


$$f = \bar{x}.\bar{y}.z + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$
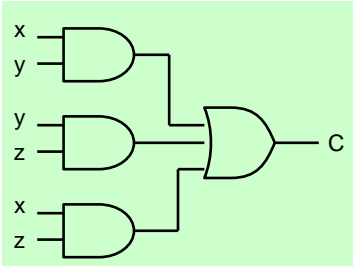
$$\Rightarrow f = \bar{x}.\bar{z} + x.z$$



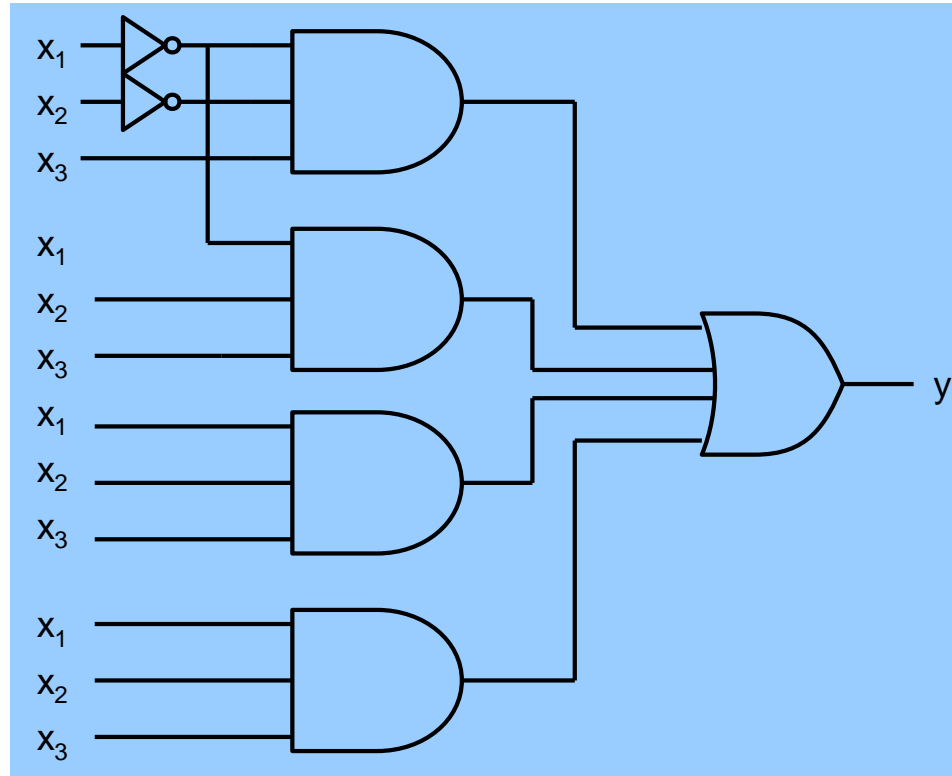
# Goal of Simplification

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$




Goal of simplification is to reduce the complexity of gate circuit. This requires that we minimize the number of gates.
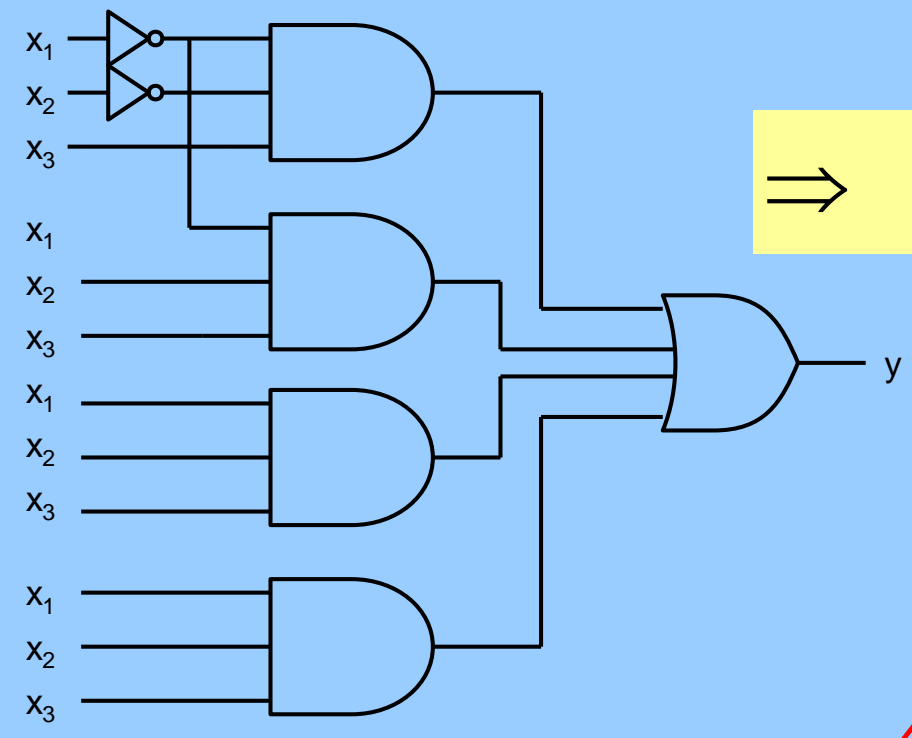
$$y = \bar{x}_1 \cdot \bar{x}_2 \cdot x_3 + \bar{x}_1 \cdot x_2 \cdot x_3 + x_1 \cdot \bar{x}_2 \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



$\Rightarrow$
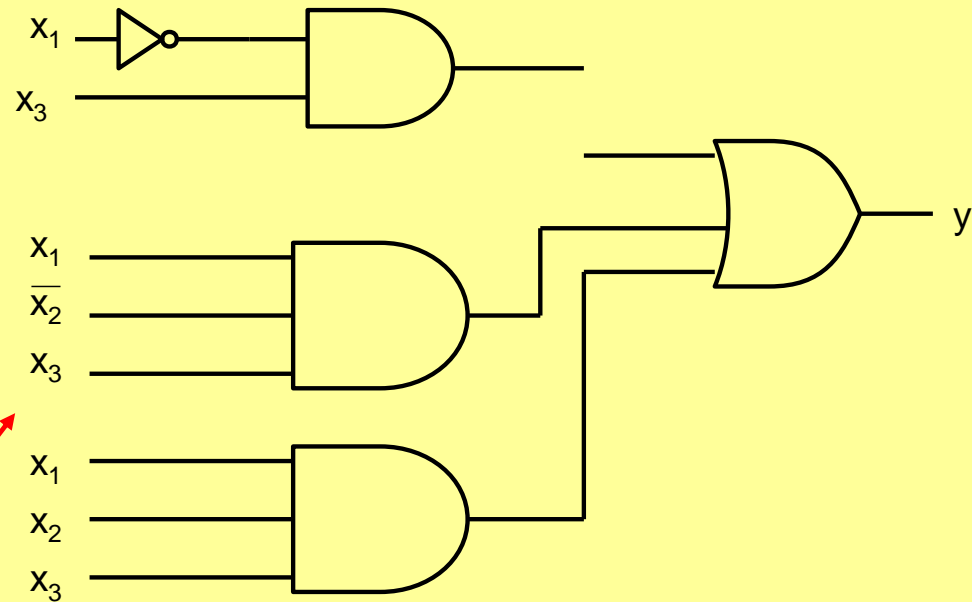
$$y = \bar{x}_1 \cdot x_3 + x_1 \cdot \bar{x}_2 \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$



This circuit is simpler not just because it uses **4 gates instead of 5** but also because circuit-2 uses **one 2-input and three 3-input gates** as compared **to five 3-input gates used in circuit-1**

# Minimization

$$y = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + \overline{x_1} \cdot x_2 \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_3 + x_1 \cdot x_2 \cdot x_3$$

$$y = \overline{x_1} \cdot x_3 \cdot (\overline{x_2} + x_2) + x_1 \cdot x_3 \cdot (\overline{x_2} + x_2)$$

$$y = \overline{x_1} \cdot x_3 + x_1 \cdot x_3$$

$$y = (\overline{x_1} + x_1) \cdot x_3$$

$$y = x_3$$

Principle used:  $x + \overline{x} = 1$

$$f = \bar{x} \cdot \bar{y} + \bar{x} \cdot y + x \cdot \bar{y}$$

Apply the Principle:  $x + \bar{x} = 1$  to simplify

$$f = \bar{x} \cdot (\bar{y} + y) + x \cdot \bar{y}$$

$$f = \bar{x} + x \cdot \bar{y}$$

$$f = (\bar{x} + x) \cdot (\bar{x} + \bar{y})$$

$$f = (\bar{x} \cdot \bar{x} + x \bar{x} + \bar{x} \cdot \bar{y} + x \cdot \bar{y})$$

$$f = (\bar{x} + \bar{x} \cdot \bar{y} + x \cdot \bar{y})$$

$$f = (\bar{x} + \bar{y} \cdot (\bar{x} + x))$$

$$f = (\bar{x} + \bar{y})$$

Principle:  $x + \bar{x} = 1$  and  $x + x = x$

## Need a systematic and simpler method

Karnaugh Map (K map) is a popular technique for carrying out simplification

It represents the information in problem in such a way that the two principles become easy to apply

Principle:  $x + \bar{x} = 1$  and  $x + x = x$



# Representation of Boolean Expressions

x	y	$f_1$
0	0	0
0	1	1
1	0	1
1	1	0

x	y	min term
0	0	$\bar{x} \cdot \bar{y}$ m0
0	1	$\bar{x} \cdot y$ m1
1	0	$x \cdot \bar{y}$ m2
1	1	$x \cdot y$ m3

$$f_1 = \bar{x} \cdot y + x \cdot \bar{y}$$

$$f_1 = m_1 + m_2$$

$$f_1 = \sum (1, 2)$$

$$f_2 = \sum (0, 2, 3) = ?$$

$$f_2 = \bar{x} \cdot \bar{y} + x \cdot \bar{y} + x \cdot y$$

A minterm is a product that contains all the variables used in a function

# Three variable functions

x	y	z	min terms
0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$ m0
0	0	1	$\bar{x} \cdot \bar{y} \cdot z$ m1
0	1	0	$\bar{x} \cdot y \cdot \bar{z}$ m2
0	1	1	$\bar{x} \cdot y \cdot z$ m3
1	0	0	$x \cdot \bar{y} \cdot \bar{z}$ m4
1	0	1	$x \cdot \bar{y} \cdot z$ m5
1	1	0	$x \cdot y \cdot \bar{z}$ m6
1	1	1	$x \cdot y \cdot z$ m7

$$f_2 = \sum (1, 4, 7) = ?$$

$$f_2 = \bar{x} \cdot \bar{y} \cdot z + x \cdot \bar{y} \cdot \bar{z} + x \cdot y \cdot z$$

# Product of Sum Terms Representation

x	y	$f_1$
0	0	0
0	1	1
1	0	1
1	1	0

x	y	Max term
0	0	$x + \underline{y}$ M0
0	1	$\underline{x} + y$ M1
1	0	$\underline{x} + \underline{y}$ M2
1	1	$x + y$ M3

A maxterm is a sum that contains all the variables used in a function

$$f_1 = (x + y) \cdot (\bar{x} + \bar{y})$$

$$f_1 = M_0 \cdot M_3$$

$$f_1 = \prod(M_0, M_3)$$

x	y	z	Max. terms
0	0	0	$x + y + z$ M0
0	0	1	$x + y + \bar{z}$ M1
0	1	0	$x + y + z$ M2
0	1	1	$x + \bar{y} + \bar{z}$ M3
1	0	0	$\bar{x} + y + z$ M4
1	0	1	$\bar{x} + y + \bar{z}$ M5
1	1	0	$\bar{x} + \bar{y} + z$ M6
1	1	1	$\bar{x} + \bar{y} + \bar{z}$ M7

$$f_1 = \Pi(1, 5, 7) = ?$$

$$f_2 = (x + y + \bar{z}).(\bar{x} + y + \bar{z}).(\bar{x} + \bar{y} + \bar{z})$$

## Recall K map

Karnaugh Map (K map) is a popular technique for carrying out simplification

It represents the information in problem in such a way that the two principles become easy to apply

Principle:  $x + \bar{x} = 1$  and  $x + x = x$

# K-map representation of truth table

x	y	min term
0	0	$\overline{x} \cdot \overline{y}$ m0
0	1	$\overline{x} \cdot y$ m1
1	0	$x \cdot \overline{y}$ m2
1	1	$x \cdot y$ m3

		y	
		0	1
x	0	m <sub>0</sub>	m <sub>1</sub>
	1	m <sub>2</sub>	m <sub>3</sub>

x	y	f <sub>1</sub>
0	0	0
0	1	1
1	0	1
1	1	0



		y	
		0	1
x	0	0	1
	1	1	0

$$f_2 = \sum (1,2,3)$$



		y	
		0	1
x	0	0	1
	1	1	1

		y	
		0	1
x	0	1	0
	1	0	1



$$f = \bar{x}.\bar{y} + x.y$$

# 3-variable K-map representation

x	y	z	min terms
0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$ m0
0	0	1	$\bar{x} \cdot \bar{y} \cdot z$ m1
0	1	0	$\bar{x} \cdot y \cdot \bar{z}$ m2
0	1	1	$\bar{x} \cdot y \cdot z$ m3
1	0	0	$x \cdot \bar{y} \cdot \bar{z}$ m4
1	0	1	$x \cdot \bar{y} \cdot z$ m5
1	1	0	$x \cdot y \cdot \bar{z}$ m6
1	1	1	$x \cdot y \cdot z$ m7

		yz			
x		00	01	11	10
	0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
1		m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>



# 3-variable K-map representation

x	y	z	min terms
---	---	---	-----------

0	0	0	$\bar{x} \cdot \bar{y} \cdot \bar{z}$ m0
0	0	1	$\bar{x} \cdot \bar{y} \cdot z$ m1
0	1	0	$\bar{x} \cdot y \cdot \bar{z}$ m2
0	1	1	$\bar{x} \cdot y \cdot z$ m3
1	0	0	$x \cdot \bar{y} \cdot \bar{z}$ m4
1	0	1	$x \cdot \bar{y} \cdot z$ m5
1	1	0	$x \cdot y \cdot \bar{z}$ m6
1	1	1	$x \cdot y \cdot z$ m7

x	y	z	f
---	---	---	---

0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

x \ yz	00	01	11	10
0	m <sub>0</sub>	m <sub>1</sub>	m <sub>3</sub>	m <sub>2</sub>
1	m <sub>4</sub>	m <sub>5</sub>	m <sub>7</sub>	m <sub>6</sub>

x \ yz	00	01	11	10
0	0	1	1	0
1	0	1	1	0

What is the function represented by this K map?

$x \backslash yz$	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.z + x.\bar{y}.z + x.y.z$$

# 4-variable K-map representation

w	x	y	z	min terms
0	0	0	0	$m_0$
0	0	0	1	$m_1$
0	0	1	0	$m_2$
0	0	1	1	$m_3$
⋮	⋮	⋮	⋮	⋮
1	1	1	0	$m_{14}$
1	1	1	1	$m_{15}$



wx \ yz	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

wx \ yz	00	01	11	10
00	1	0	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	0

$$f = \overline{w}. \overline{x}. \overline{y}. \overline{z} + \overline{w}. \overline{x}. y. \overline{z} + \overline{w}. x. \overline{y}. \overline{z} + \overline{w}. x. y. \overline{z} \\ + w. \overline{x}. \overline{y}. \overline{z} + w. \overline{x}. y. \overline{z} + w. x. \overline{y}. \overline{z}$$

# Minimization using Kmap

$$f_2 = \sum (2, 3)$$

$$f = x.\bar{y} + x.y$$

$$f = x.(\bar{y} + y)$$

$$f = x$$

A Karnaugh map for a two-variable function f2. The map is a 2x2 grid with variables x and y. The columns are labeled y=0 and y=1. The rows are labeled x=0 and x=1. The values in the cells are: (0,0)=0, (0,1)=0, (1,0)=1, (1,1)=1. A red oval encircles the two cells where x=1, and a red arrow points from the simplified expression f=x to this oval.

	y	0	1
x	0	0	0
1	1	1	1

Combine terms which differ in only one bit position. As a result, whatever is common remains.

		y	
		0	1
x	0	0	1
	1	0	1

$$f = \bar{x}.y + x.y$$

$$f = (\bar{x} + x).y$$

$$\Rightarrow f = y$$


		y	
		0	1
x	0	1	0
	1	1	0

$$\Rightarrow f = \bar{y}$$

		y	
		0	1
x	0	1	1
	1	0	0

$$\Rightarrow f = \bar{x}$$

$$f_2 = \sum (1, 2, 3)$$

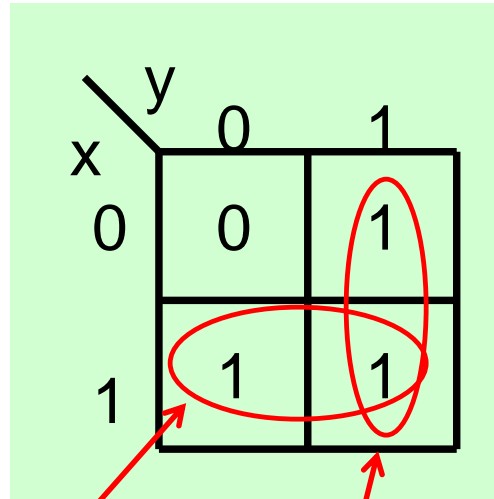

A Karnaugh map for two variables, x and y. The map is a 2x2 grid. The columns are labeled 0 and 1 for y, and the rows are labeled 0 and 1 for x. The cells contain the following values: (x=0, y=0) is 0; (x=0, y=1) is 1; (x=1, y=0) is 1; (x=1, y=1) is 1. A red circle is drawn around the cell (x=0, y=1). Another red circle is drawn around the cells (x=1, y=0) and (x=1, y=1). Two red arrows point from the algebraic terms in the block below to these circles: one from  $x \cdot \bar{y}$  to the circle around (x=0, y=1), and one from  $\bar{x} \cdot y$  to the circle around (x=1, y=0) and (x=1, y=1).

		y	0	1
x	0		0	1
	1		1	1

$$\begin{aligned}
 f &= x \cdot \bar{y} + x \cdot y + \bar{x} \cdot y \\
 &= x \cdot \bar{y} + x \cdot y + \bar{x} \cdot y + x \cdot y \\
 &= x \cdot (\bar{y} + y) + (\bar{x} + x) \cdot y \\
 &= x + y
 \end{aligned}$$

**The idea is to cover all the 1's with as few and as simple terms as possible**

### 3-variable minimization

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.z + x.y.z + x.\bar{y}.z$$

x \ yz	00	01	11	10
0	1	0	1	0
1	0	1	1	0

$$y.z$$

$$x.z$$

$$f = \bar{x}.\bar{y}.\bar{z} + y.z + x.z$$

## 3-variable minimization

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.\bar{z} + x.y.z + x.\bar{y}.z$$

x \ yz	00	01	11	10
0	1	0	0	1
1	0	1	1	0

$$\bar{x}.\bar{z}$$

$$x.z$$

$$f = \bar{x}.\bar{z} + x.z$$



# 3-variable minimization

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$x.\bar{y}$$

$$x.y$$

$$f = \bar{x}.\bar{y}.\bar{z} + \bar{x}.\bar{y}.z + x.y.z + x.y.\bar{z}$$

$$f = x.\bar{y} + x.y$$

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	1

$$f = x.(\bar{y} + y) = x$$

$$x$$

x \ yz	00	01	11	10
0	1	1	1	1
1	0	0	0	0

$\bar{x}$

x \ yz	00	01	11	10
0	1	0	0	1
1	1	0	0	1

$\bar{z}$

x \ yz	00	01	11	10
0	0	1	1	0
1	0	1	1	0

$z$

x \ yz	00	01	11	10
0	1	0	0	1
1	1	1	1	1

$\bar{z}$

$$f = x + \bar{z}$$

$x$

Can we do this ?

x \ yz	00	01	11	10
0	0	0	0	0
1	1	1	1	0

Note that each encirclement should represent a single product term. In this case it does not.

$$\begin{aligned} f &= x.\bar{y}.\bar{z} + x.\bar{y}.z + x.y.z \\ &= x.\bar{y} + x.z \end{aligned}$$

We do not get a single product term. In general we cannot make groups of 3 terms.

Can we use kmap with the following ordering of variables?

x \ yz	00	01	10	11
0	0	0	0	0
1	0	1	1	0

Can we combine these two terms into a single term ?

$$\begin{aligned} f &= x.\bar{y}.z + x.y.\bar{z} \\ &= x.(\bar{y}.z + y.\bar{z}) \end{aligned}$$

Note that no simplification is possible.

	$yz$	00	01	10	11
$x$	0	0	1	0	1
	1	0	0	0	0

These two terms can be combined into a single term but it is not easy to show that on the diagram.

$$\begin{aligned}
 f &= \bar{x}.\bar{y}.z + \bar{x}.y.z \\
 &= \bar{x}.(\bar{y} + y).z = \bar{x}.z
 \end{aligned}$$

Kmap requires information to be represented in such a way that it is easy to apply the principle  $x + \bar{x} = 1$