

ESC201A Assignment 3

Instructor Abhishek Gupta


2023-2024 Semester I

Topics


Transient analysis, Steady state, Sinusoidal sources, Phasors

Questions

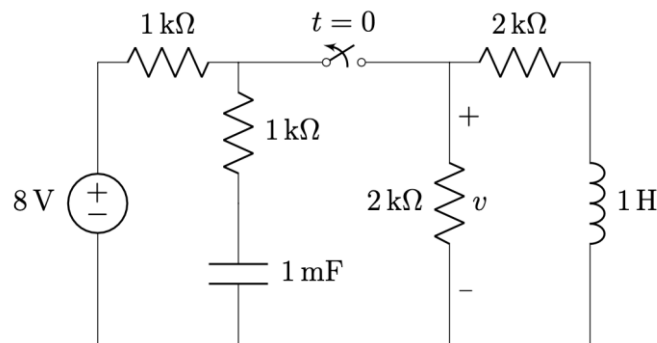1. For the circuit shown below, determine the voltage across the 2K resistor (vertical) as a function of time after the switch is opened at $t = 0$.



Solution:

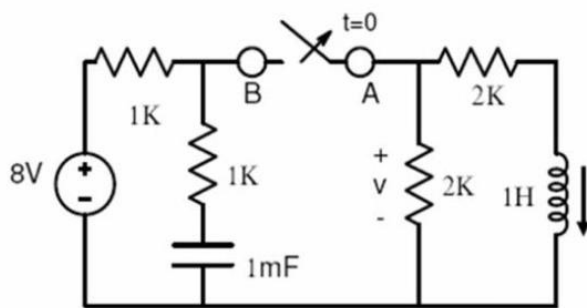


Circuit after opening the switch ($t > 0$)

First find the inductor current

$$i_L(t) = i_L(\infty) + \{i_L(0^+) - i_L(\infty)\} \times e^{-\frac{t}{\tau}}$$

$$R_{eq} = 2K + 2K = 4K$$


$$\tau = \frac{L}{R_{eq}} = 0.25ms$$

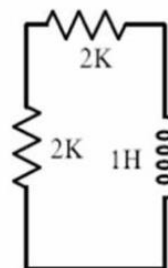

One can also see that : $i_L(\infty) = 0$


$$i_L(0^+) = i_L(0^-)$$

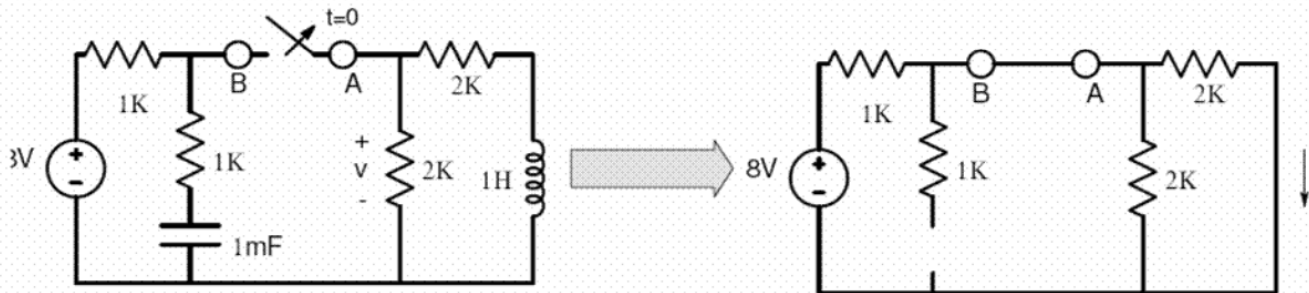Circuit before opening the switch ($t < 0$) and assuming steady state condition:




$$i_L(0^+) = i_L(0^-) = \frac{8}{(2K \parallel 2K) + 1K} \times 0.5 = 2mA \Rightarrow i_L(t) = 2 \times e^{-4000t} mA$$

Voltage across the 2K resistor:

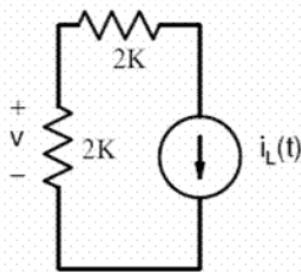


$$v(t) = -2 \times 10^3 \times i_L(t) = -4 \times e^{-4000t} V$$

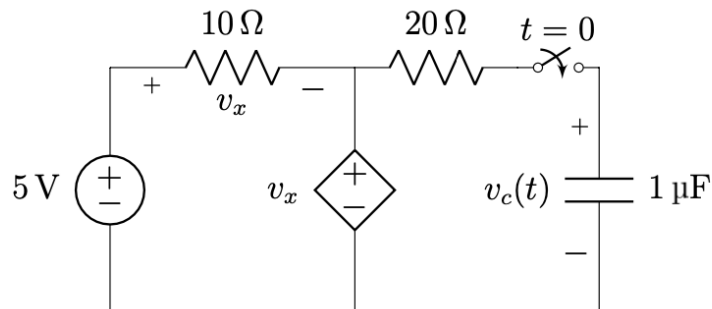2. Find $v_c(t)$ for $t > 0$ in the following circuit if the capacitor voltage is zero for $t < 0$.



Solution:

Before the circuit is closed:

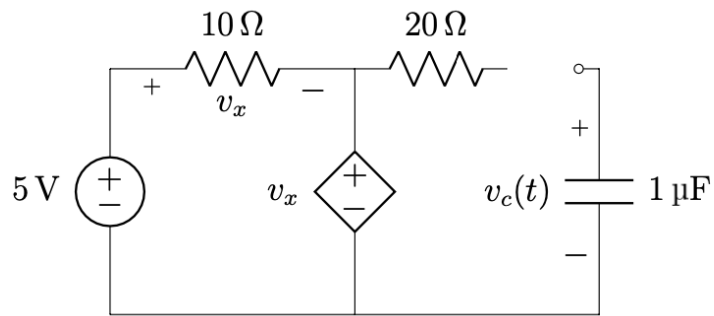


Applying KVL in the first loop

$$5 - V_x - V_x = 0$$

or

$$V_x = 2.5V$$

After the switch is closed

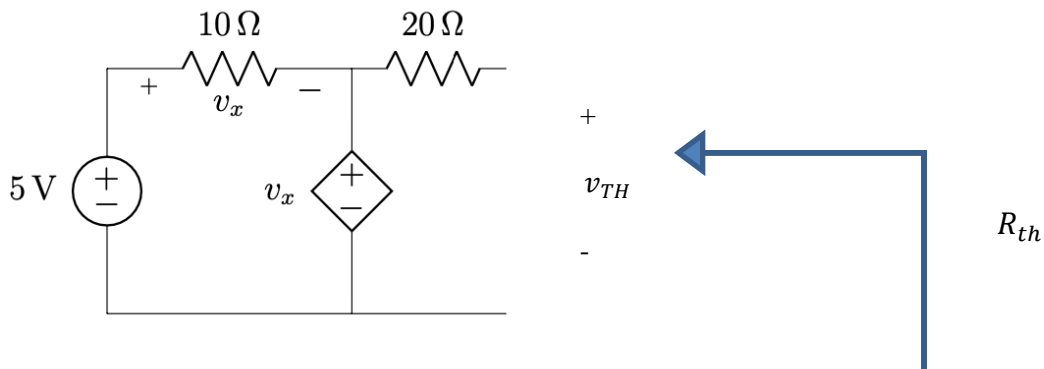

Thevenin voltage

$$V_{th} = 2.5V$$

Short circuit current=

$$I_{sc} = \frac{2.5V}{20} = 125mA$$

$$R_{th} = \frac{2.5V}{125mA} = 20\Omega$$


Hence, the time constant is

$$\tau = 20 \times 10^{-6} = 20\mu s$$

The voltage is given as

$$\begin{aligned} V_c(t) &= V_c(\infty) + [V_c(0) - V_c(\infty)]e^{-\frac{t}{\tau}} \\ &= 2.5 + (0 - 2.5)e^{-\frac{t}{2 \times 10^{-5}}} V \\ &= 2.5 \left(1 - e^{-\frac{t}{2 \times 10^{-5}}} \right) V \end{aligned}$$

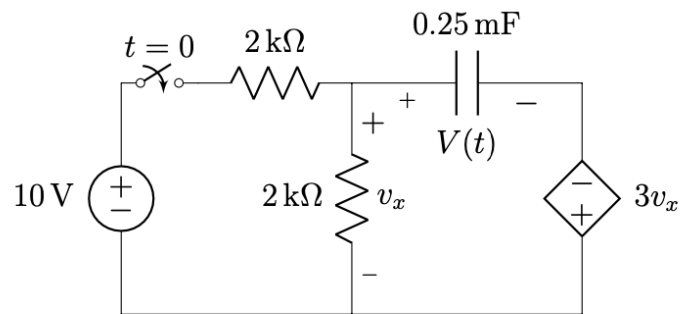3. Assuming that the capacitor does not have any initial charge, determine the voltage across the capacitor $V(t)$ as a function of time after the switch is closed at $t = 0$.



Solution:

$$v(t) = v(\infty) + \{v(0^+) - v(\infty)\}e^{-t/\tau}$$

$$v(0^+) = 0 \quad [1]$$


At $t \rightarrow \infty$, the capacitor is open circuit. Therefore,

$$v_X = \frac{2K}{2K + 2K} * 10 = 5V$$

$$v(\infty) = V_X - (-3V_X) = 4V_X = 20V \quad [1]$$

$$\tau = CR_{eq}$$

R_{eq} can be found from the circuit:

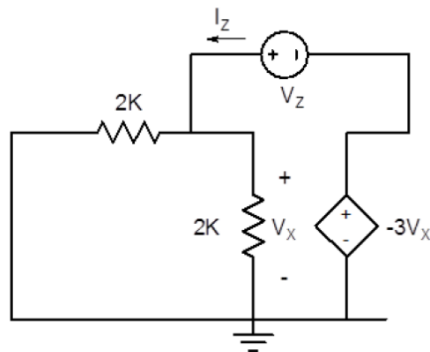

$$R_{eq} = \frac{v_z}{i_z}$$

$$v_z = v_x - -3v_x = 4v_x$$


$$i_z = \frac{v_x}{1K}$$

$$R_{eq} = \frac{v_z}{i_z} = 4K \quad [1]$$

$$\tau = CR_{eq} = 1s \quad [1]$$


$$v(t) = 20\{1 - e^{-t}\} \quad [1]$$

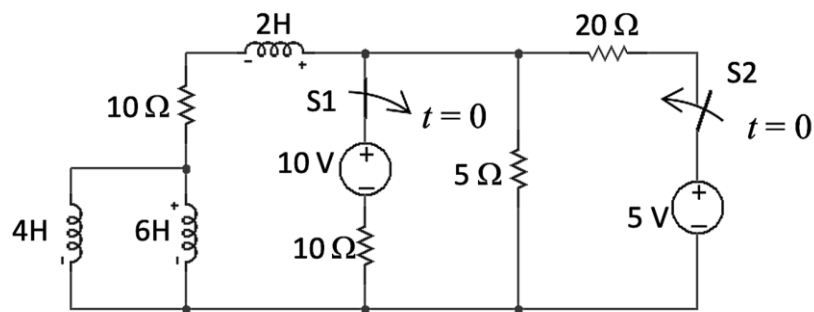4. In the following circuit the switch S1 is closed and S2 is left open for a long time. At $t=0$, S1 is opened and S2 is closed. Determine the current, i_5 , through the 5Ω resistor for all time



Solution:

For $t = 0^-$

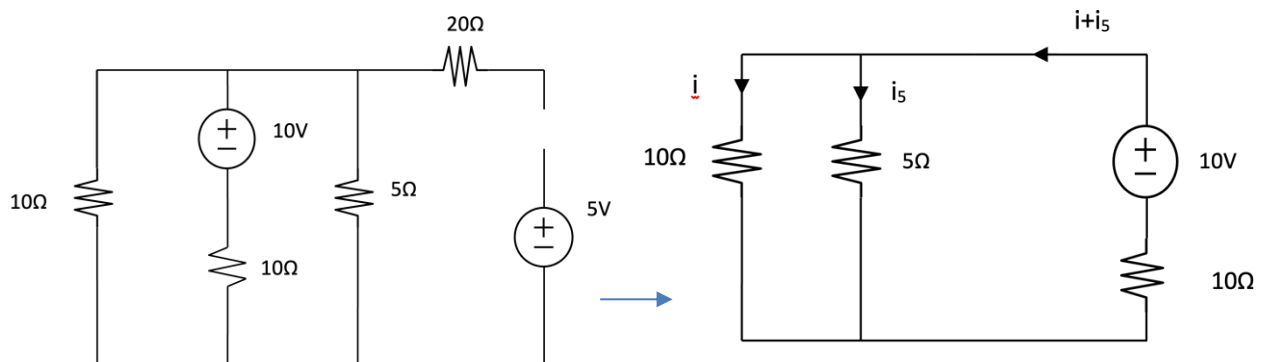

$$R_{eq} = 10 + \left(10 \times \frac{5}{15}\right) = \left(10 + \frac{50}{15}\right) \Omega = \left(10 + \frac{10}{3}\right) \Omega$$

$$i_{5\Omega} = \left(\frac{10}{10 + \frac{10}{3}}\right) \times \frac{10}{15} A = 0.5 A$$

$$10 - 10i - 10i - 10i_5 = 0$$


$$1 - i_5 = 2i$$

$$10 - 5i_5 - 10i - 10i_5 = 0$$


$$i = \left(\frac{1}{4}\right) A$$

$$i(0^-) = (1/4)A = i(0^+)$$

At $t > 0$

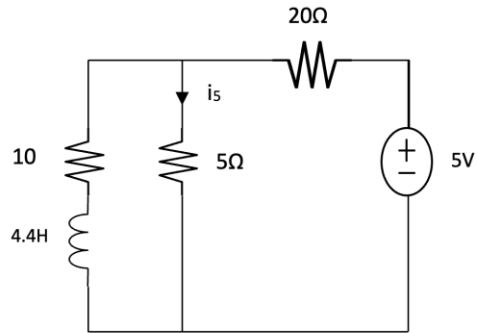

$t \rightarrow \infty$

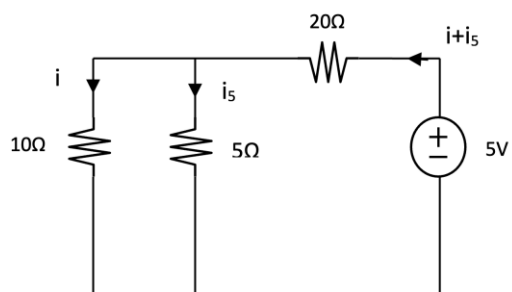

$$5 - 20i - 20v_5 - 5i_s = 0$$

$$5 - 20i - 20i_s - 10i = 0$$

$$i = 5/70 \text{ A}, i_s = 10/70 \text{ A}$$

$$R_{th} = (20 \parallel 5) + 10 = 14 \Omega$$

$$\text{Therefore, } \tau = 4.4/14 = 0.314 \text{ s}$$

$t > 0$

$$i(t) = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau}$$

$$\text{therefore, } i(t) = (1/14) + ((1/4) - (1/14))e^{-3.2t} \text{ A}$$

$$v_{5\Omega} = 10i + L \left(\frac{di}{dt} \right) = \frac{5}{7} + \left(\frac{5}{2} - \frac{5}{7} \right) e^{-3.2t} + (4.4) \left(\frac{1}{4} - \frac{1}{14} \right) e^{-3.2t} (-8.2) V$$

$$\text{therefore, } V_{5\Omega} = \left(\frac{10}{14} \right) (1 - e^{-3.2t}) V$$

therefore,

$$i_{5\Omega} = \left(\frac{1}{7} \right) (1 - e^{-3.2t}) A$$

5. Express the following sinusoidal signals in the canonical form $V_m \cos(\omega t + \theta)$:

(i) $v(t) = -110 \cos(\omega t + 30^\circ) \text{ V}$

(ii) $v(t) = 220 \sin(\omega t + 220^\circ) \text{ V}$

(iii) $v(t) = 10 \sin(\omega t + 110^\circ) + 4 \cos(\omega t + 110^\circ) \text{ V}$

(iv) $v(t) = 10 \cos(\omega t + 370^\circ) * 4 \sin(\omega t + 10^\circ) \text{ V}$

Wherever needed, you may use phasors to make your task easier.

Solution:

(a) $v(t) = -110 \cdot \cos(\omega t + 30^\circ) \text{ V} = 110 \cdot \cos(\omega t + 30^\circ - 180^\circ) \text{ V} = 110 \cdot \cos(\omega t - 150^\circ) \text{ V}$

(b) $v(t) = 220 \cdot \sin(\omega t + 220^\circ) \text{ V} = 220 \cdot \cos(\omega t + 220^\circ - 90^\circ) \text{ V} = 220 \cdot \cos(\omega t + 130^\circ) \text{ V}$

(c) $v(t) = 10 \cdot \sin(\omega t + 110^\circ) + 4 \cdot \cos(\omega t + 110^\circ) \text{ V}$

$$= 10 \cdot \cos(\omega t + 110^\circ - 90^\circ) + 4 \cdot \cos(\omega t + 110^\circ) \text{ V} = 10 \cdot \cos(\omega t + 20^\circ) + 4 \cdot \cos(\omega t + 110^\circ) \text{ V}$$

$$= 10 \angle 20^\circ + 4 \angle 110^\circ = 10 \cdot \cos(20^\circ) + j 10 \cdot \sin(20^\circ) + 4 \cdot \cos(110^\circ) + j 4 \cdot \sin(110^\circ)$$


$$= 8.029 + j 7.179 = 10.77 \angle 41.8^\circ = 10.77 \cdot \cos(\omega t + 41.8^\circ) \text{ V}$$

(d) $v(t) = 10 \cdot \cos(\omega t + 370^\circ) \cdot 4 \cdot \sin(\omega t + 10^\circ) \text{ V}$

$$= 10 \cdot \cos(\omega t + 10^\circ) \cdot 4 \cdot \cos(\omega t - 80^\circ) \text{ V} = 20 \cdot (\cos(2\omega t - 70^\circ) + \cos(90^\circ)) \text{ V}$$


$$= 20 \cdot \cos(2\omega t - 70^\circ) \text{ V. [You can't solve this by converting into phasors, because it's multiplying two voltages]}$$

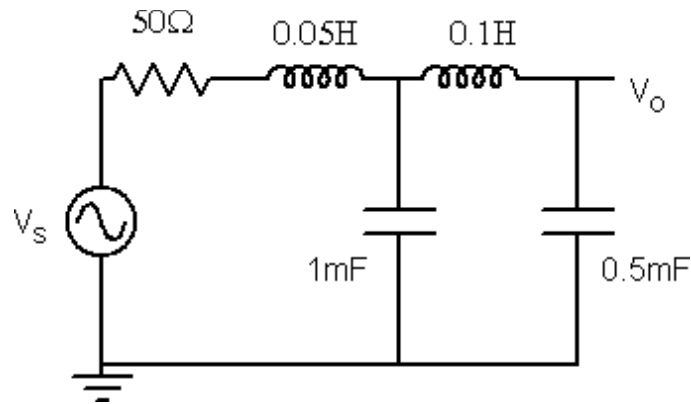6. Determine the output voltage as a function of time using the method of phasors for an input voltage of $V_s = 5\cos(100t) \text{ V}$.



Solution:
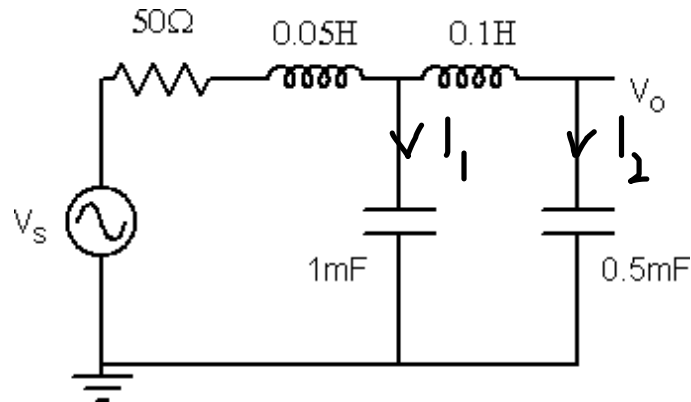
$$\begin{aligned} Z_{eq} &= 50 + j5 + [-j10 \parallel (j10 - j20)] \\ &= 50 + j5 + (-j10 \parallel -j10) \\ &= 50 + j5 - j5 \\ &= 50 \text{ ohm} \end{aligned}$$



$$I = \left(\frac{5}{50} \right) \cos(100t) \text{ A} = 0.1 \cos(100t) \text{ A}$$

$$\begin{aligned} I_2 &= \left(\frac{-j10}{-j10 + j10 - j20} \right) I = \left(-\frac{10}{-20} \right) \times 0.1 \cos(100t) \\ &= 0.05 \cos(100t) \text{ A} \end{aligned}$$

$$\begin{aligned} V_o &= I_2 (-j20) = \cos(100t - 90^\circ) \text{ V} \\ &= \sin(100t) \text{ V} \end{aligned}$$