

ESc201 : Introduction to Electronics



Transient Analysis of Capacitive and Inductive Circuits


Amit Verma
Dept. of Electrical Engineering
IIT Kanpur

Capacitance

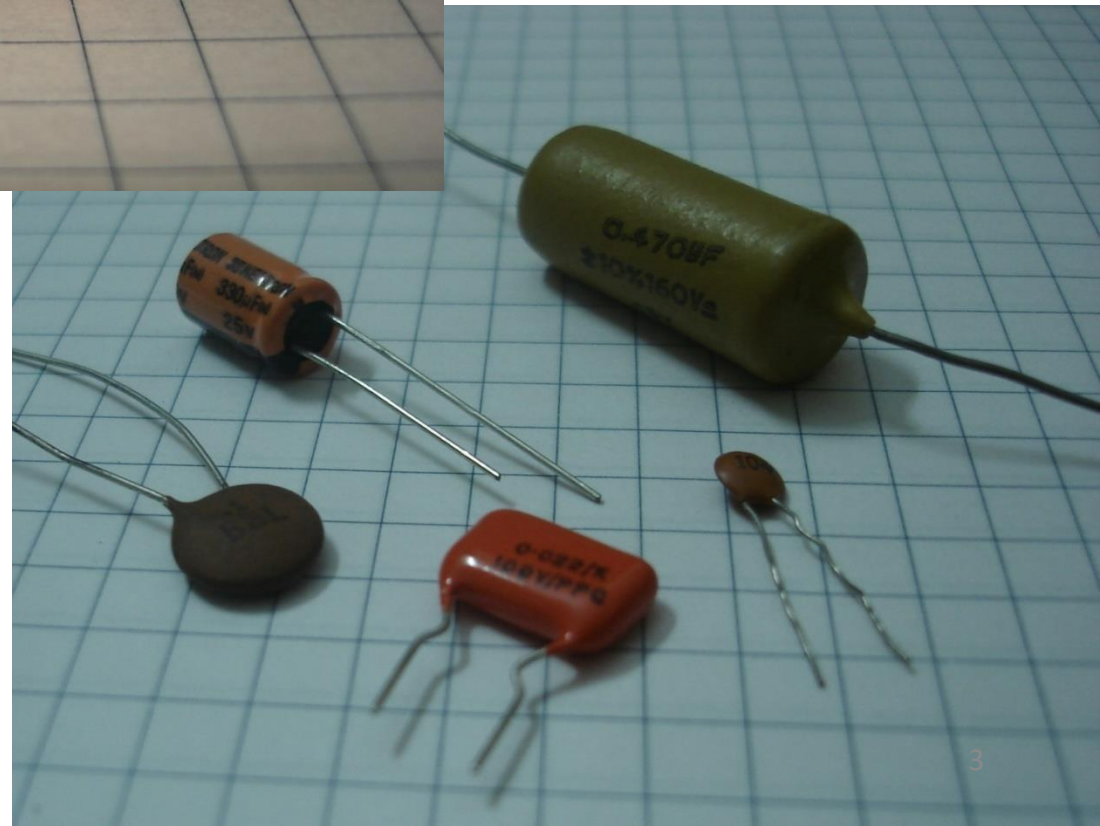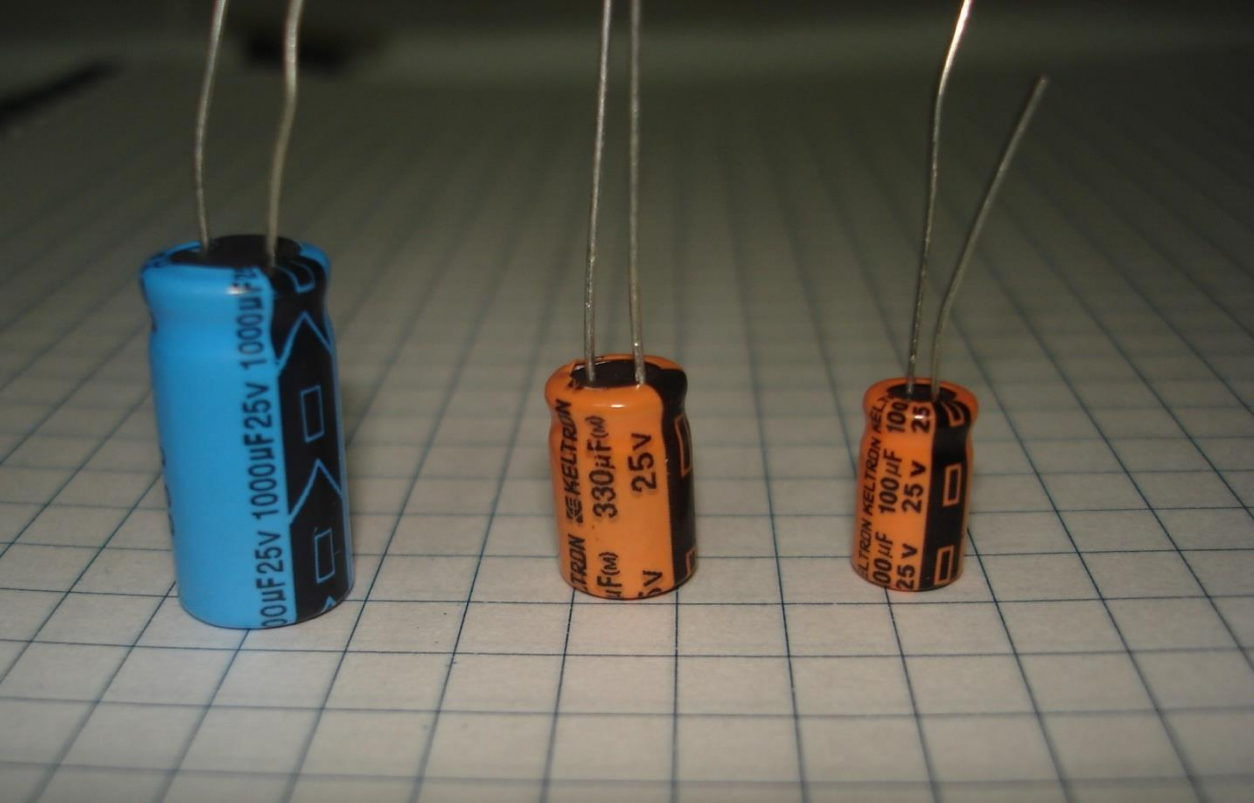- Two sheets of conductors separated by a layer of insulating material
- Insulating material is called dielectric - could be air, polyester, ...





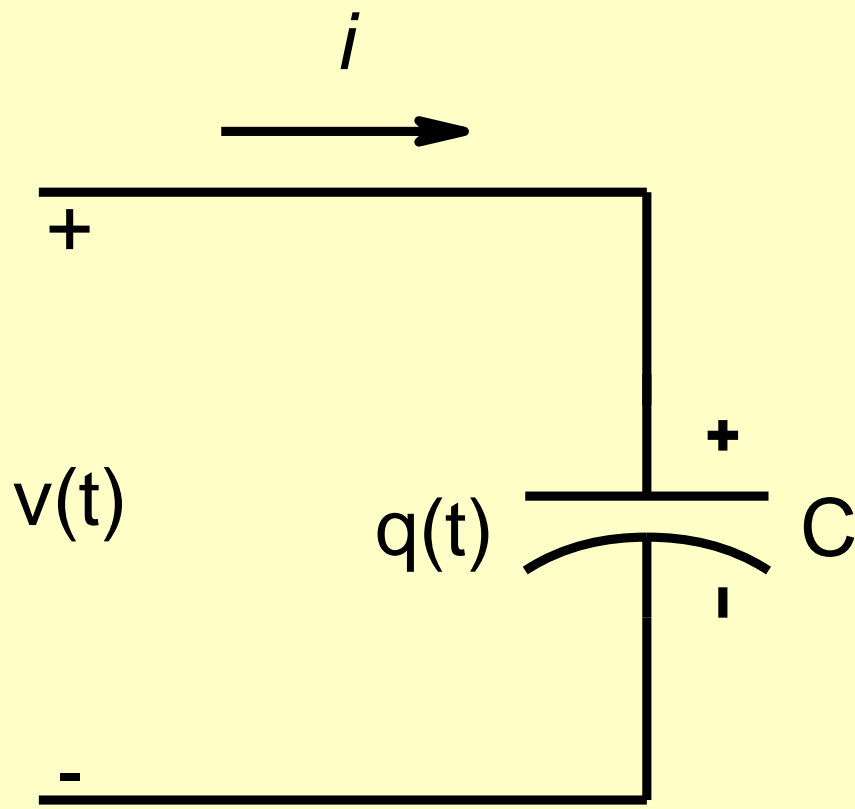

$$q = C \times v$$

Coulombs

Farad

Volt

$$i = \frac{dq}{dt}$$


$$i = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_o}^t i dt + v(t_o)$$

$$w_c(t) = \frac{1}{2} C \times v_c^2(t)$$

For dc or steady state when the voltage does not vary with time
 A capacitor under dc or steady state acts like an
 open circuit


$$i = 0$$

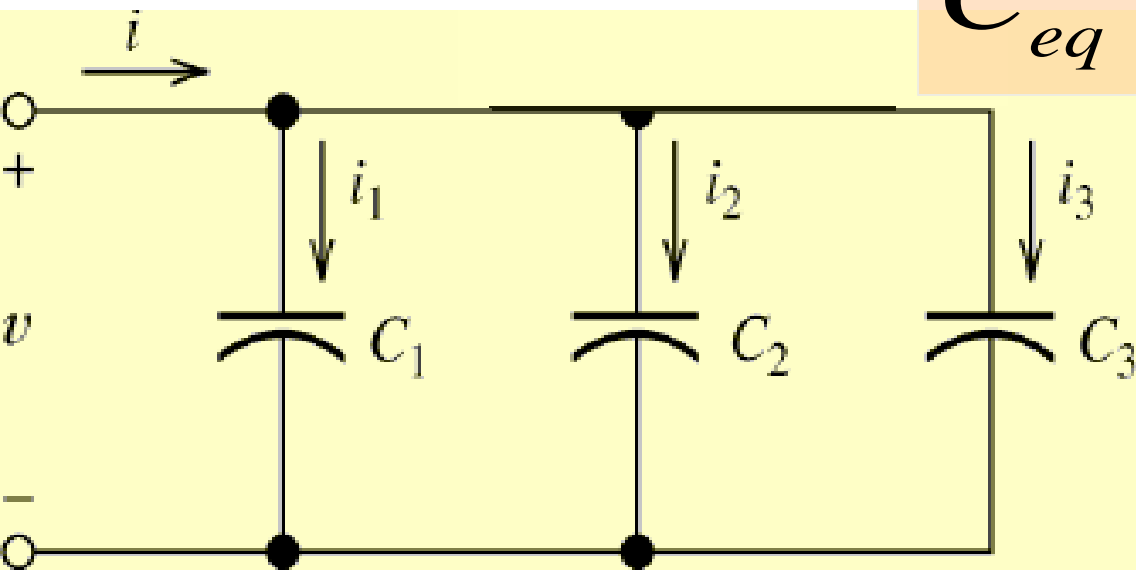



$$C_{eq} = C_1 + C_2 + C_3$$

$$i = C \frac{dv}{dt}$$
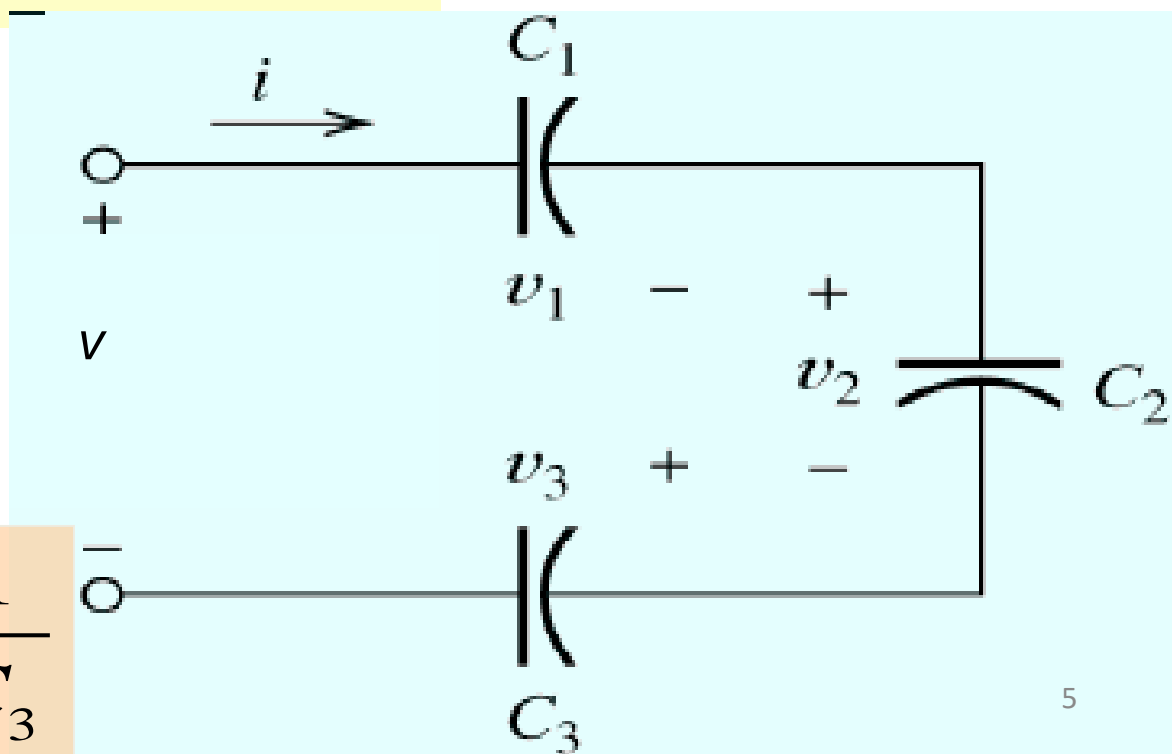
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$




Inductance

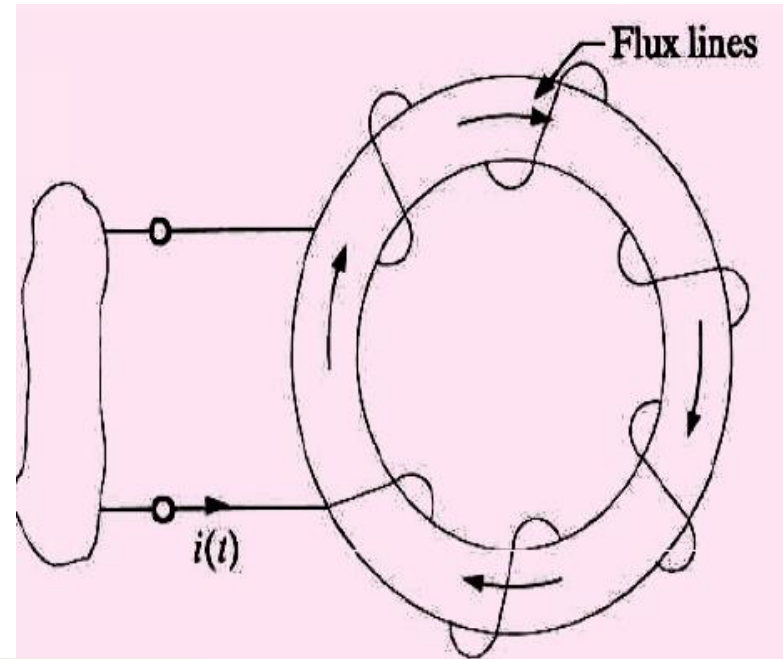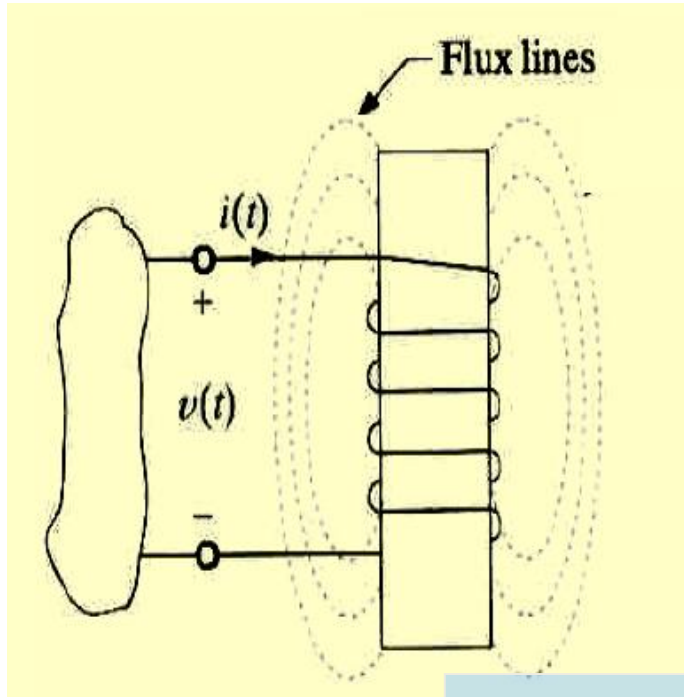

$$\phi = L \times i$$

A time varying flux causes voltage to appear across the device terminals
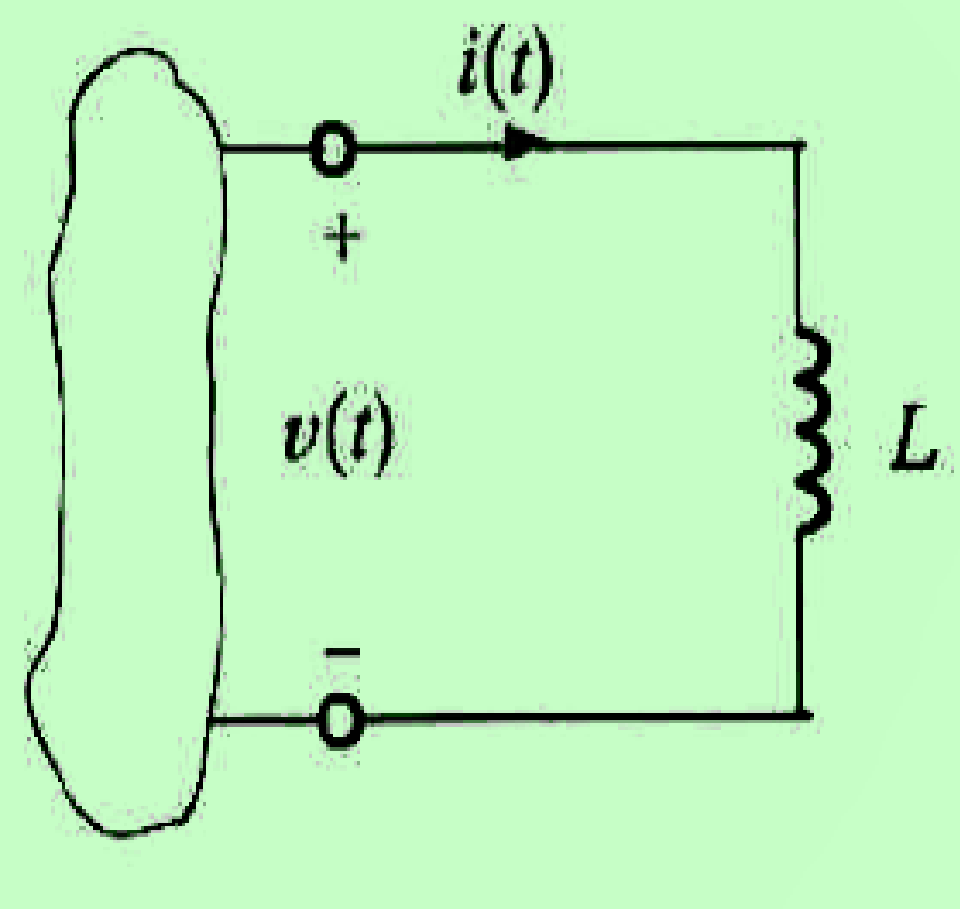
$$v = \frac{d\phi}{dt} = L \times \frac{di}{dt}$$



$$v = L \times \frac{di}{dt}$$



Henry


For dc or steady state when the current does not vary with time

$$v = 0$$


An inductor under dc or steady state acts like a **short circuit**

Typical Inductors




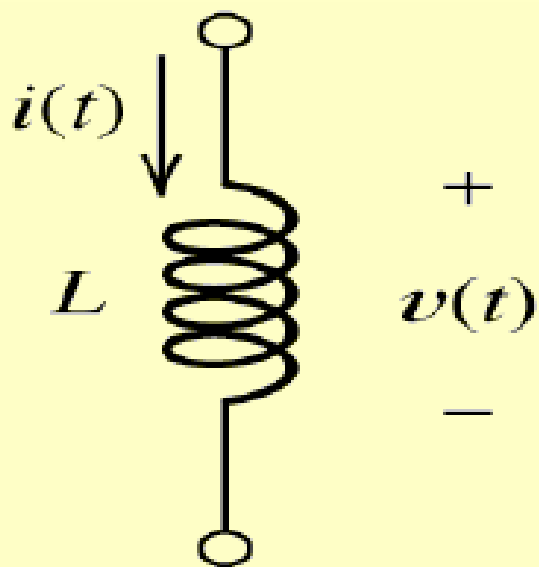

$$w_L(t) = \frac{1}{2} L \times i^2(t)$$

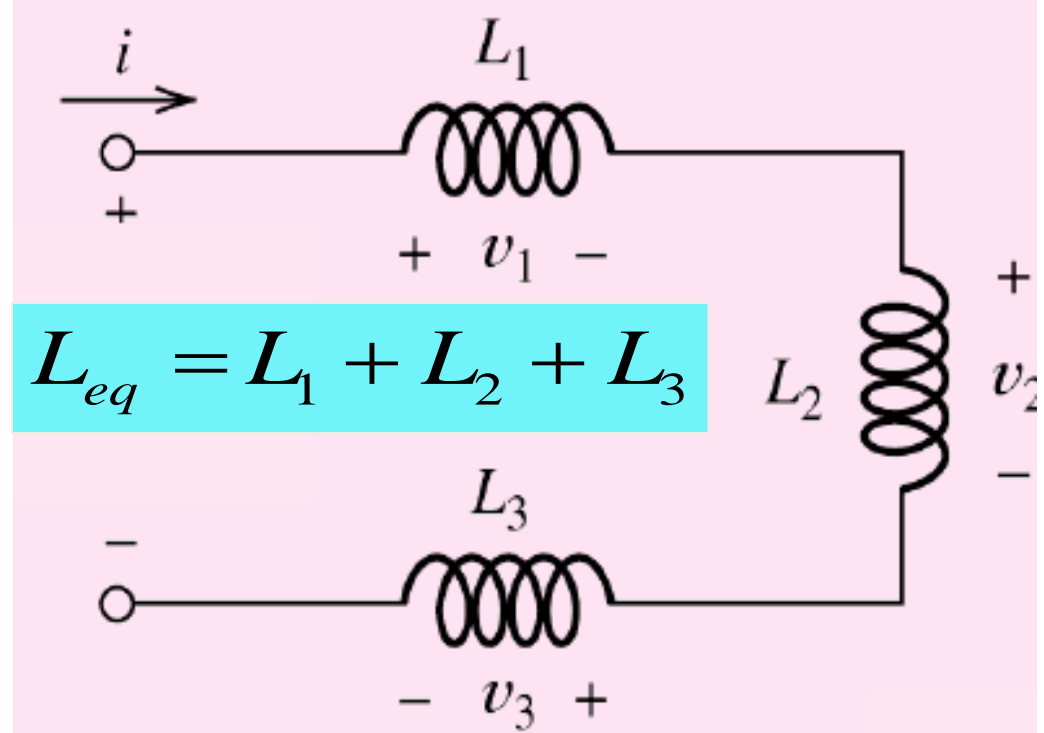

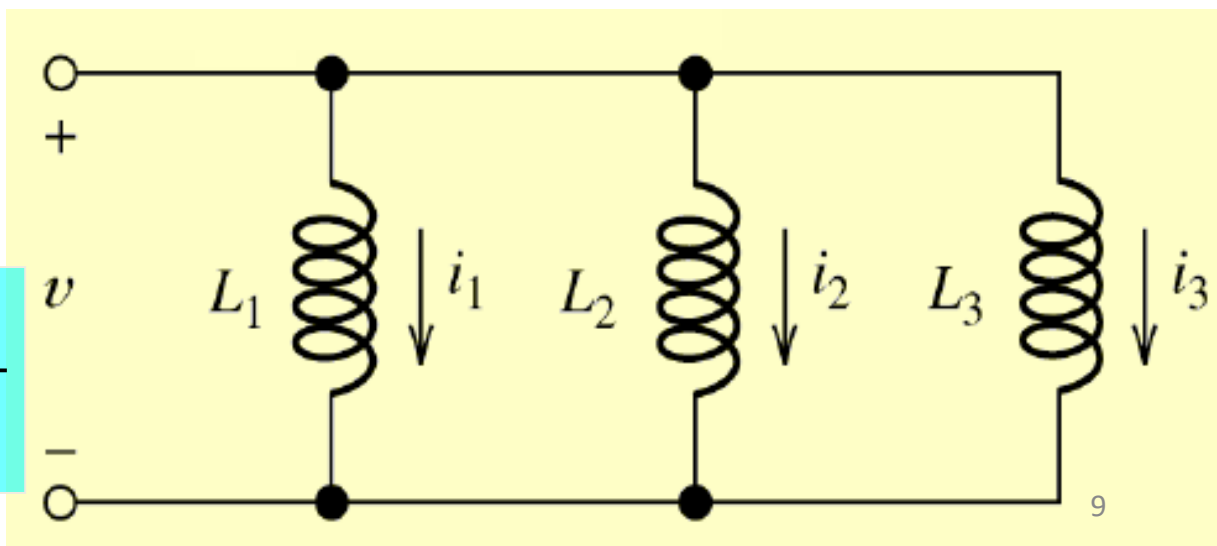
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$



Two important concepts

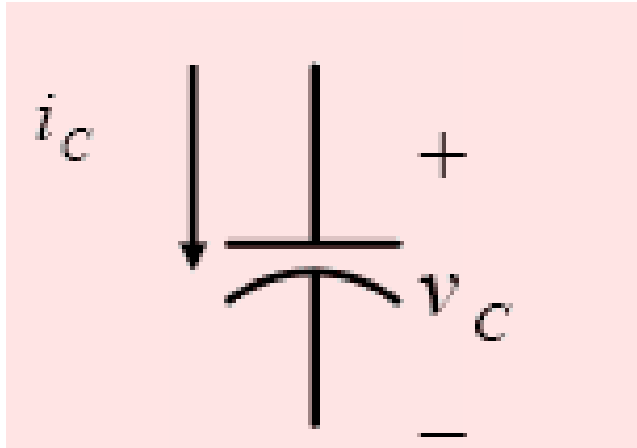
Voltage across a capacitor cannot change instantaneously



$$i_c = C \frac{dv_c}{dt}$$


Instantaneous change in voltage implies infinite current!

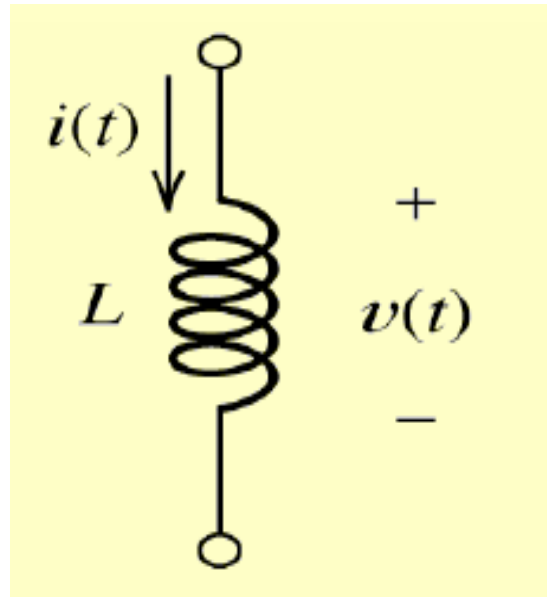Current through an inductor cannot change instantaneously



$$v = L \frac{di}{dt}$$

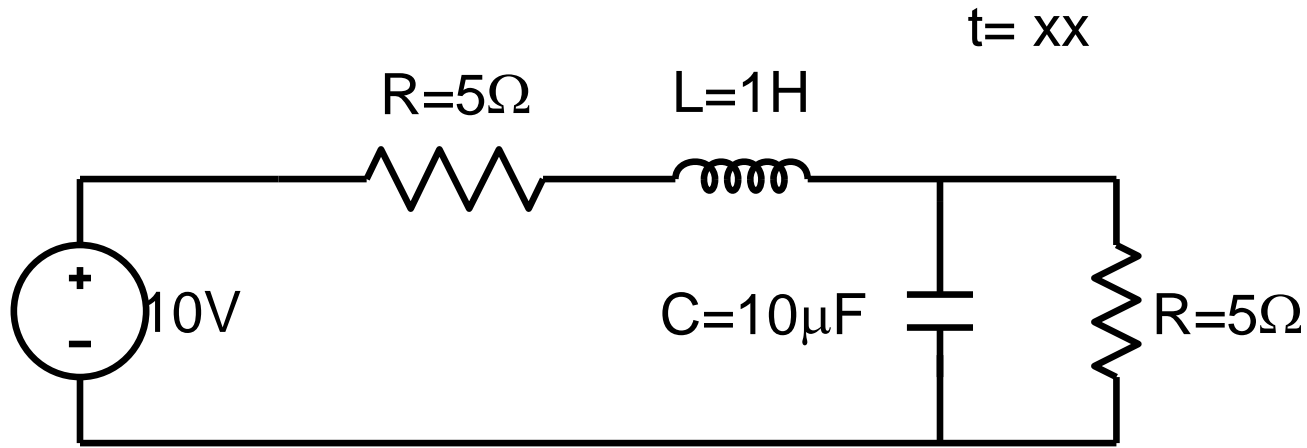
Instantaneous change in current implies infinite voltage!



What is current through the inductor or voltage across the capacitor ?

We can't give an answer unless we have some knowledge of the past state of the circuit


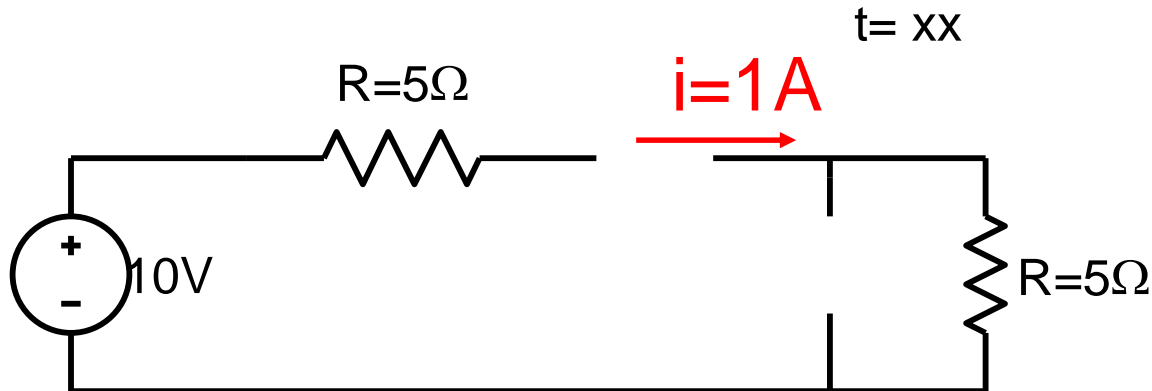
Suppose we are told that circuit has been in this state for a very very long time




$$i_c = C \frac{dv_c}{dt}$$

$$v = L \frac{di}{dt}$$

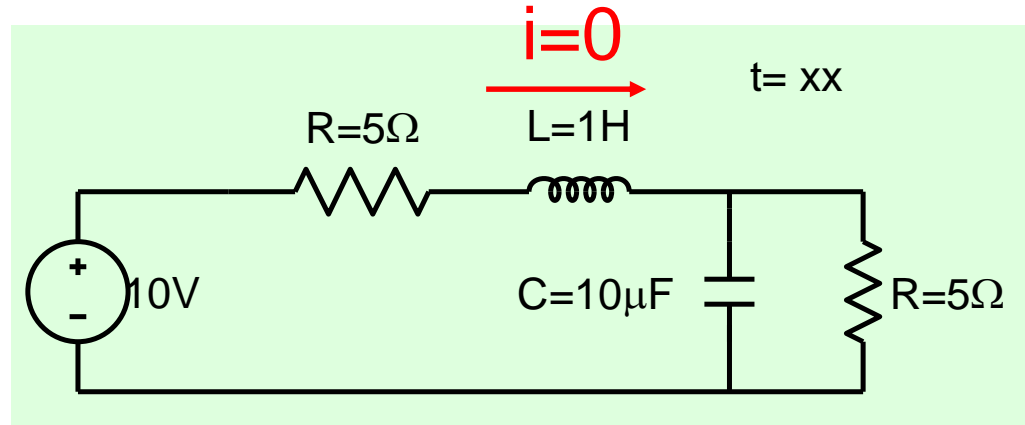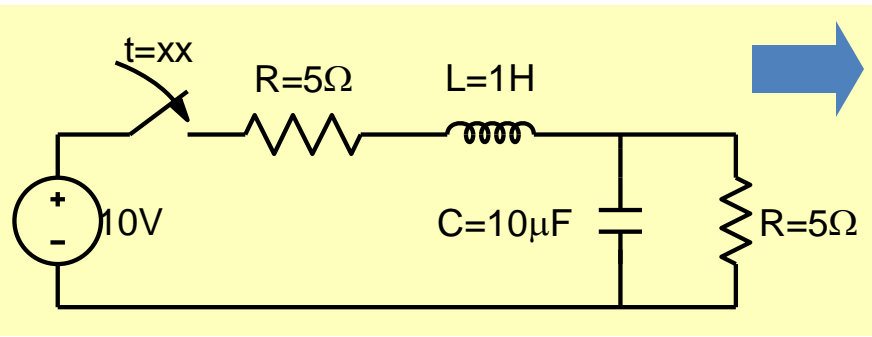Or suppose we are told that circuit was switched at $t = xx$




Circuit before switching

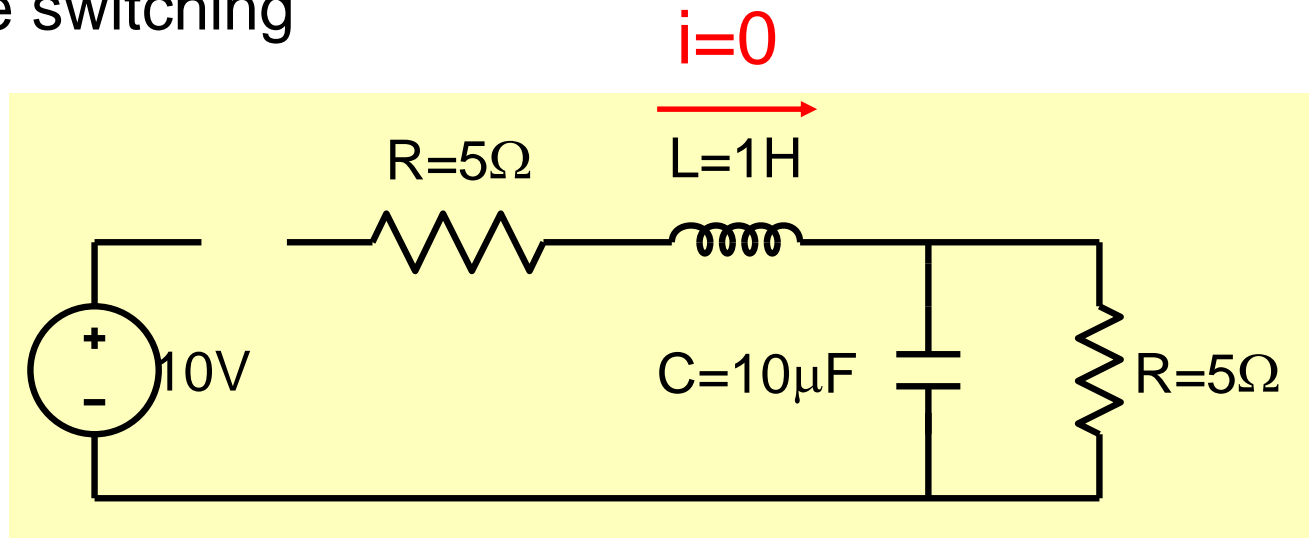


Circuits containing inductors or capacitors have a memory

Example

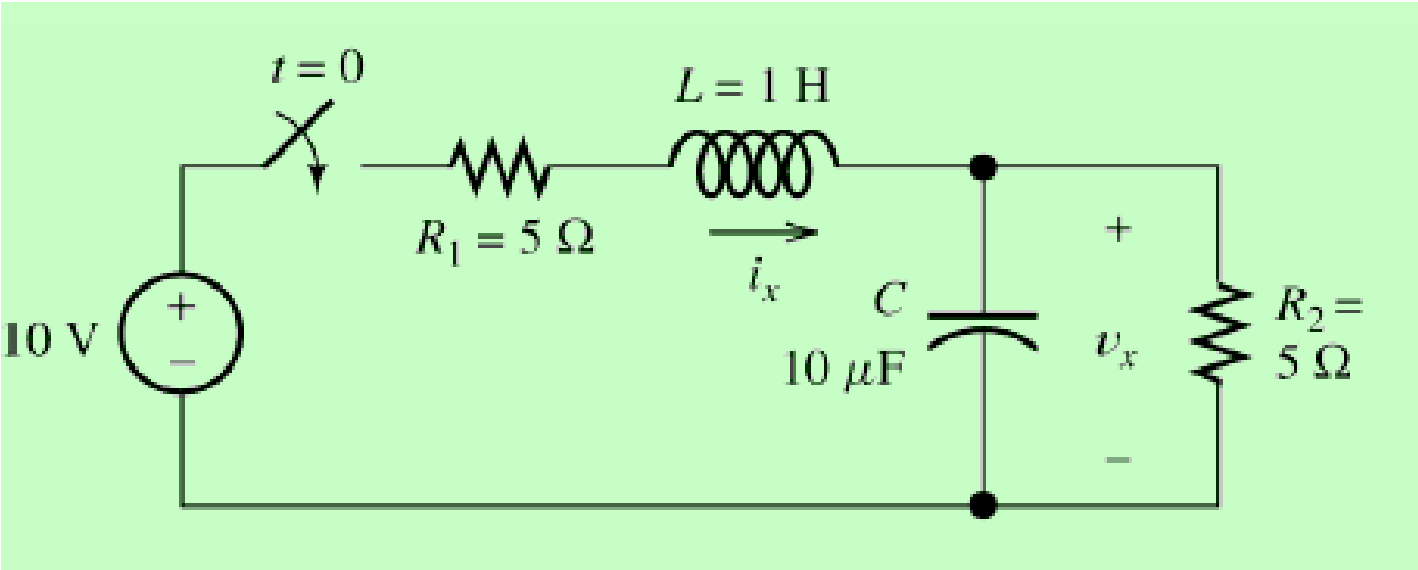


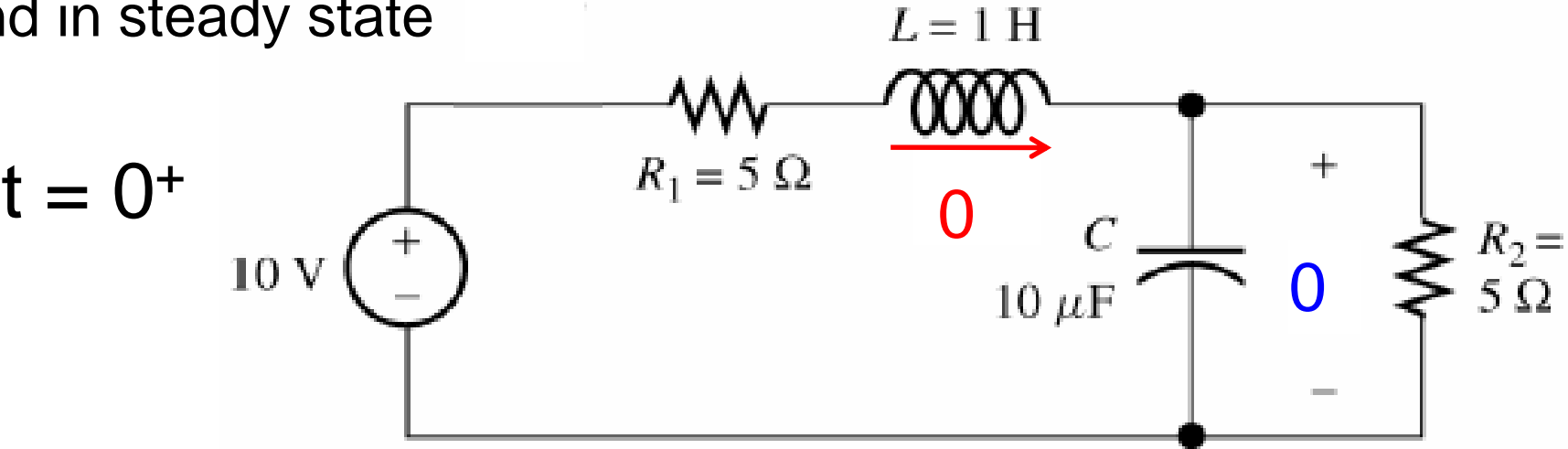Find voltage and current immediately after closing the switch and in steady state



Current through an inductor cannot change instantaneously

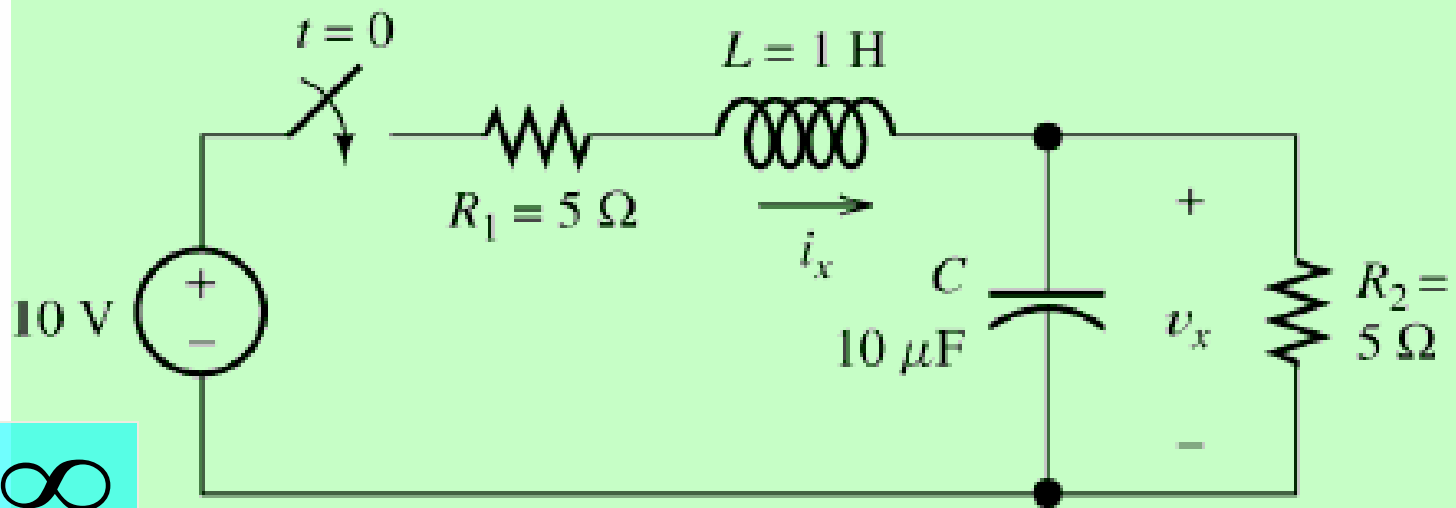
Voltage across a capacitor cannot change instantaneously



$t \rightarrow \infty$

An inductor under dc or steady state acts like a **short circuit**

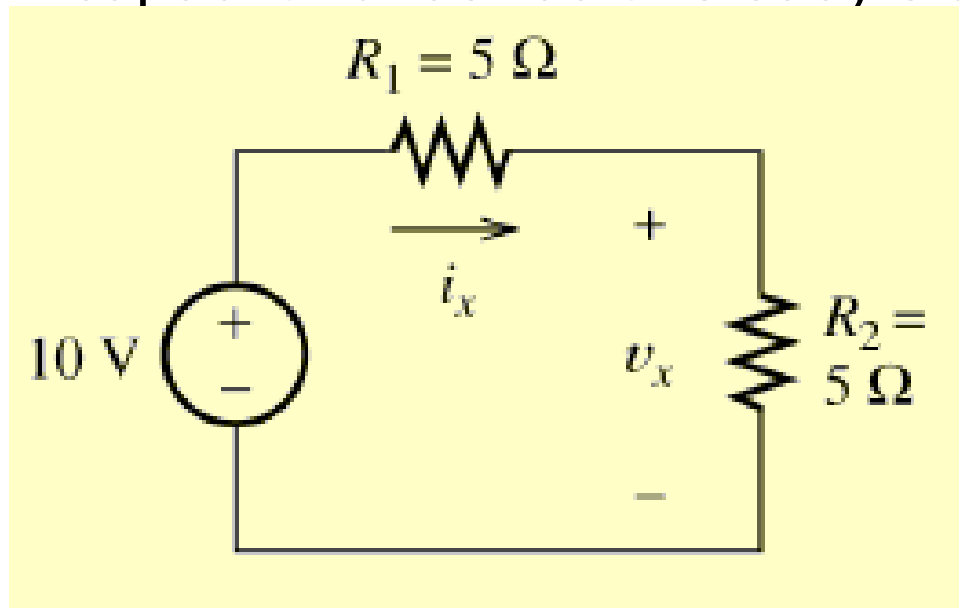A capacitor under dc or steady state acts like an **open circuit**



$$i_x = \frac{10}{R_1 + R_2} = 1\text{ A}$$



$$v_x = R_2 i_x = 5\text{ V}$$

$$i_L(t \rightarrow \infty) = 1\text{ A}$$

$$v_c(t \rightarrow \infty) = 5\text{ V}$$

Determine the current I_x immediately after switch is opened.

Circuit for $t > 0$

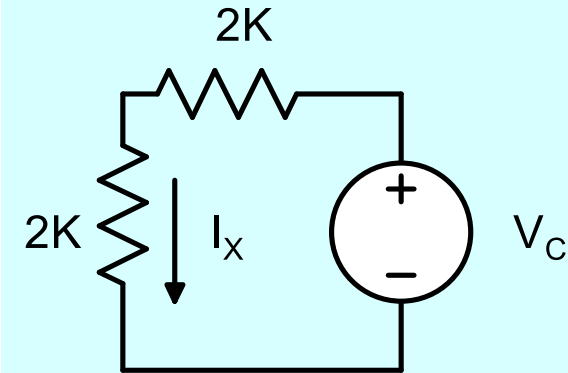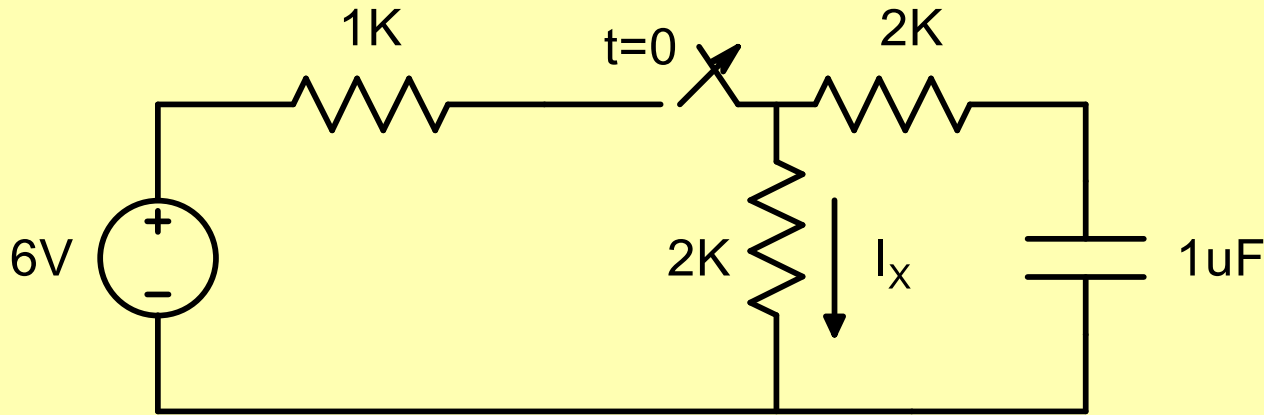


First find voltage $V_C(0^-)$

Circuit for $t < 0$


$$i_x(0^+) = \frac{v_C(0^+)}{4K} = 1mA$$

$$v_C(0^+) = v_C(0^-)$$

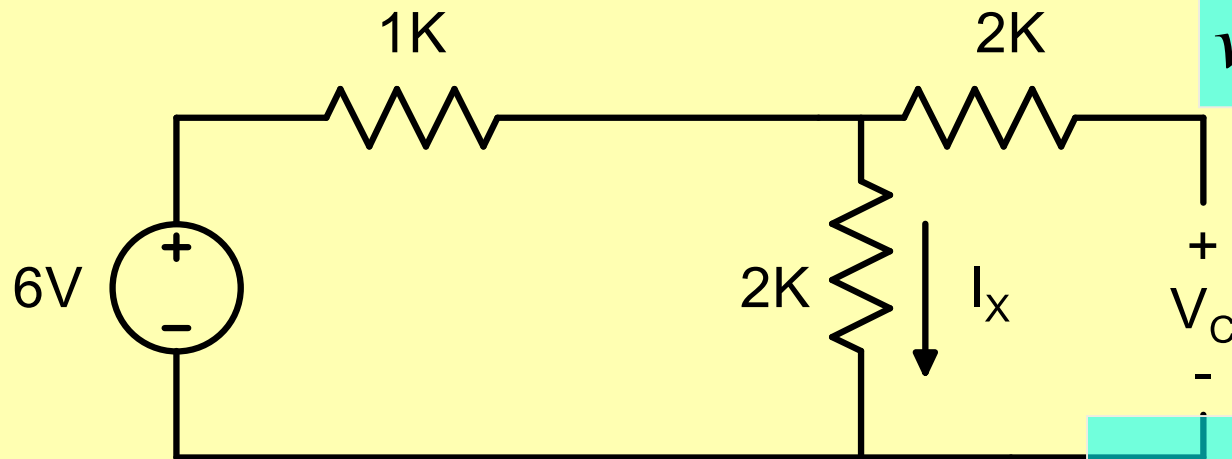


$$v_C(0^-) = \frac{2}{3} \times 6 = 4V$$

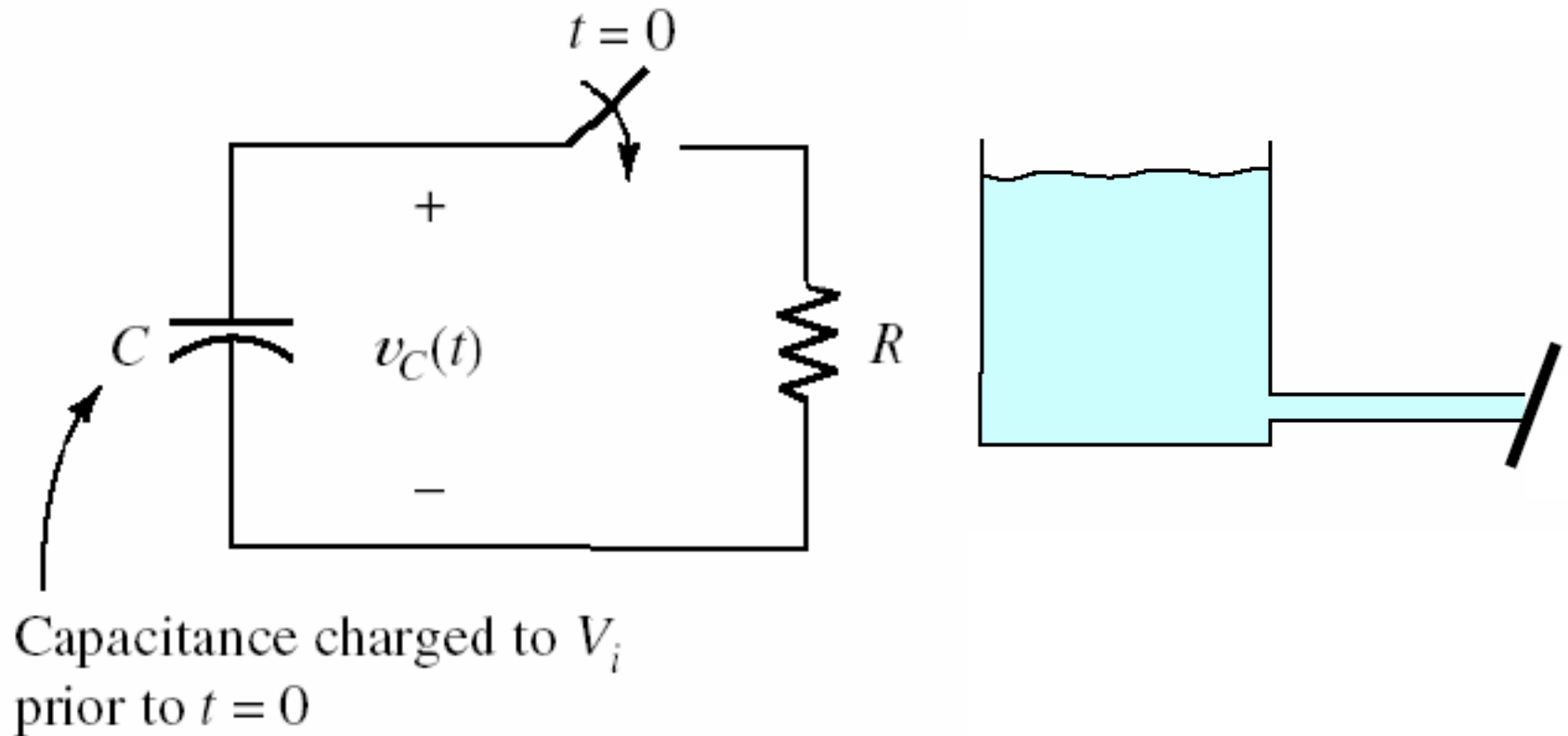
Discharge of a capacitor through a Resistor



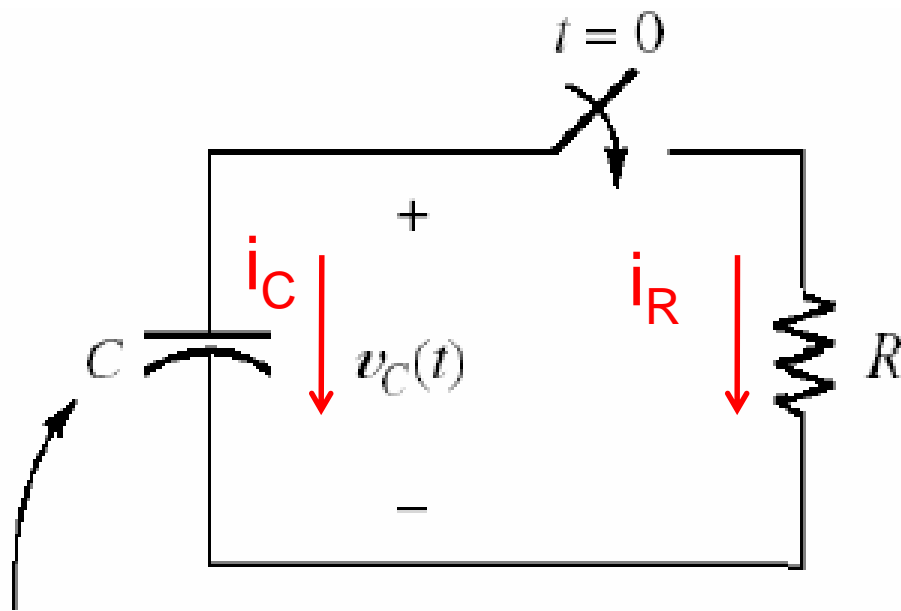How long will it take for capacitor voltage to fall to half its initial value?



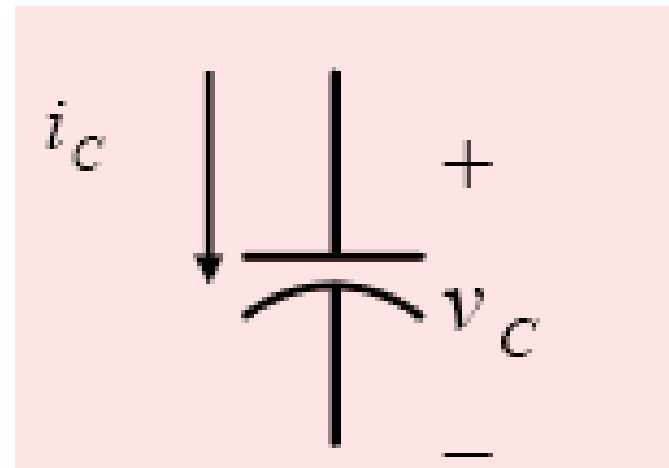Capacitance charged to V_i
prior to $t = 0$



$$i_c = C \frac{dv_c}{dt}$$

Write KCL at top node with
switch closed:

$$i_c(t) + i_R(t) = 0$$

$$C \frac{dv_c(t)}{dt} + \frac{v_c(t)}{R} = 0$$

$$\frac{dv_c(t)}{dt} = -\frac{1}{RC} v_c(t)$$

First Order Differential Equation

$$\frac{dy}{dt} = -a y$$


Solution:

$$y(t) = K e^{-at}$$

Constant K is often found from the initial condition

$$K = y(0)$$

$$y(t) = y(0) e^{-at}$$

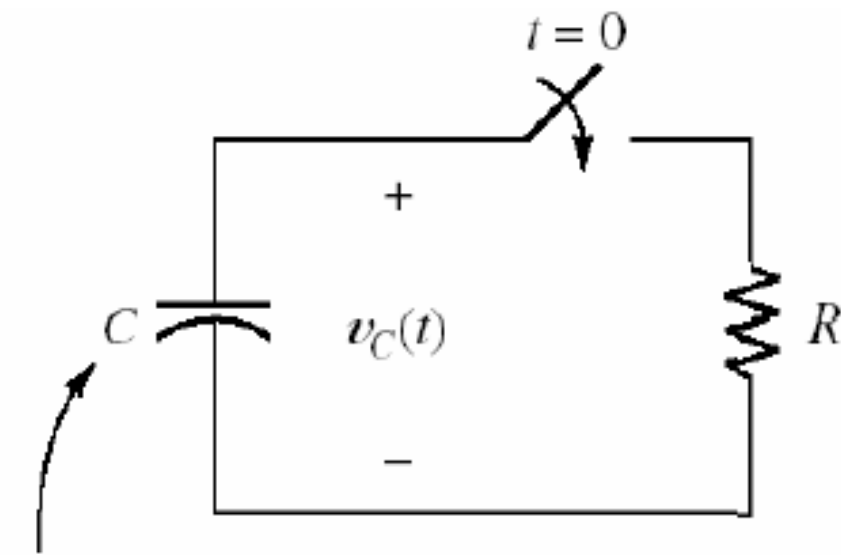

Capacitance charged to V_i
prior to $t = 0$

$$\frac{dy}{dt} = -a y$$

$$y(t) = y(0) e^{-at}$$

We know:

$$v_C(0^-) = V_i$$

$$\frac{dv_C(t)}{dt} = -\frac{1}{RC} v_C(t)$$


$$v_C(t) = v_C(0) e^{-\frac{t}{RC}}$$

$$v_C(t) = v_C(0^+) e^{-\frac{t}{RC}}$$


Voltage across a capacitor cannot change instantaneously

$$v_C(0^+) = v_C(0^-) = V_i$$

$$v_C(t) = V_i e^{-\frac{t}{RC}}$$

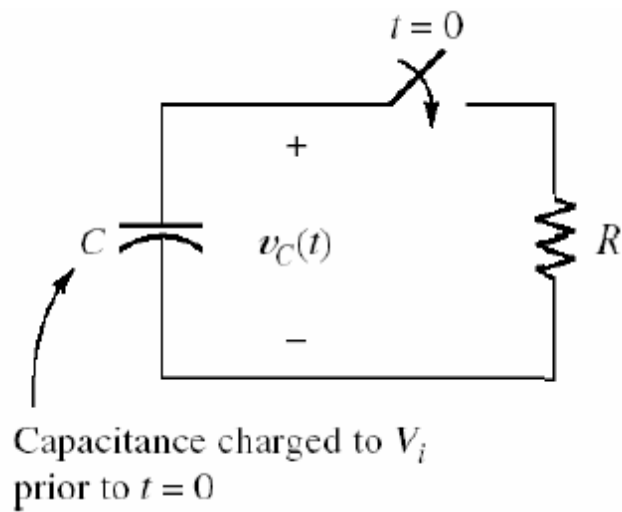


$$v_C(t) = V_i e^{-t/RC}$$

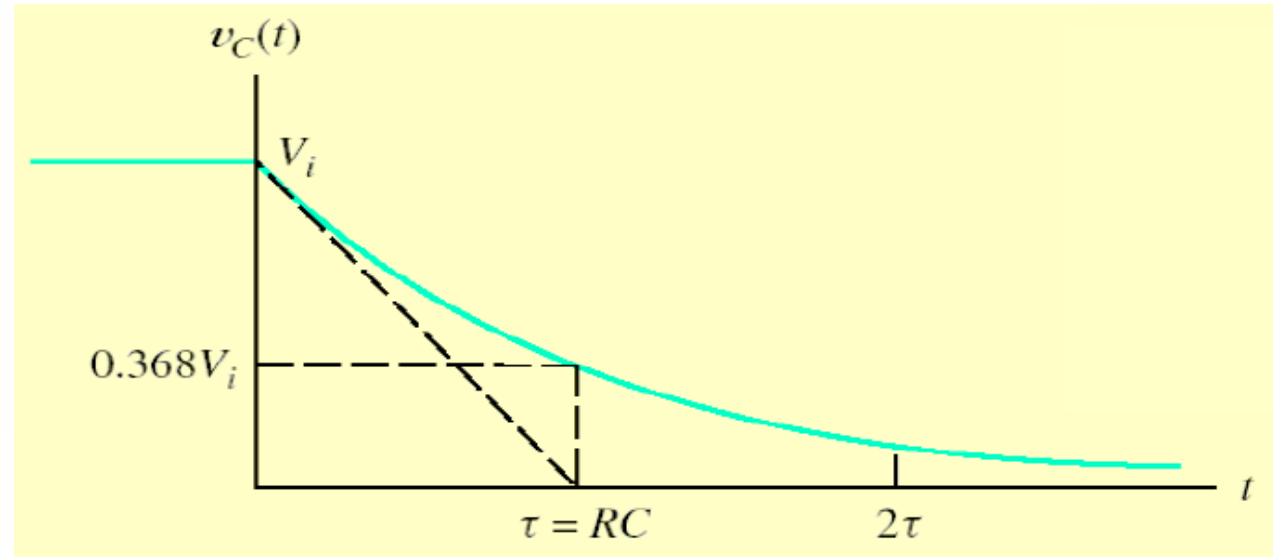

The time interval $\tau = RC$ is called the time constant of the circuit. After about **five time constants**, the voltage remaining on the capacitor will be negligible compared to the initial value

Time	τ	2τ	3τ	4τ	5τ
$V(t)/V_i$	0.368	0.135	.05	0.018	0.0067

Charging a capacitor

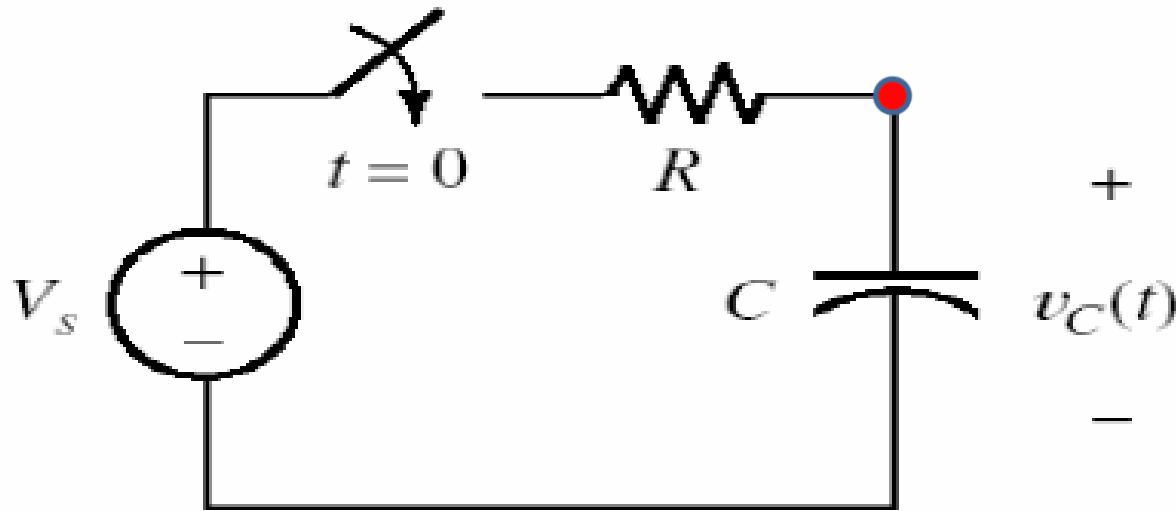

$$i_c = C \frac{dv_c}{dt}$$

Application of KCL at the indicated node gives

$$C \frac{dv_c(t)}{dt} + \frac{v_c(t) - V_s}{R} = 0$$

$$RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$

$$\frac{dx}{dt} = -a_1 x + a_2$$

Solution: $x(t) = K_1 + K_2 e^{-a_1 t}$

$$RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$

$$x(\infty) = K_1$$

$$x(t) = x(\infty) + K_2 e^{-a_1 t}$$

Use initial condition:

$$x(0) = x(\infty) + K_2$$

$$x(t) = x(\infty) + \{x(0) - x(\infty)\} e^{-a_1 t}$$

$$\frac{dx}{dt} = -a_1 x + a_2$$


$$x(t) = x(\infty) + \{x(0) - x(\infty)\} e^{-a_1 t}$$

$$RC \frac{dv_c(t)}{dt} + v_c(t) = V_s$$

$$a_1 = \frac{1}{RC}$$

$$v_c(t) = v_c(\infty) + \{v_c(0^+) - v_c(\infty)\} e^{-\frac{t}{RC}}$$

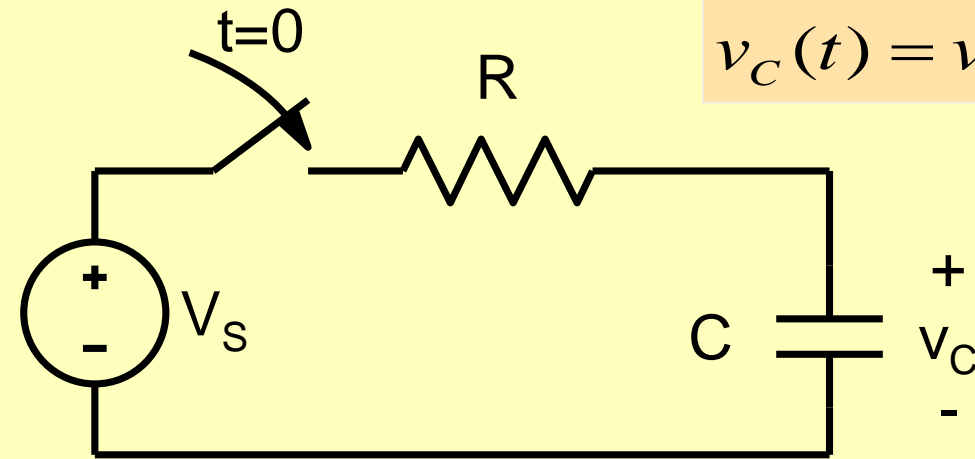
$$v_C(t) = v_C(\infty) + \{v_C(0^+) - v_C(\infty)\} e^{-\frac{t}{RC}}$$




What is $v_C(\infty)$? A capacitor under dc or steady state acts like an **open circuit**

$$v_C(\infty) = V_S$$

What is $v_C(0^+)$?

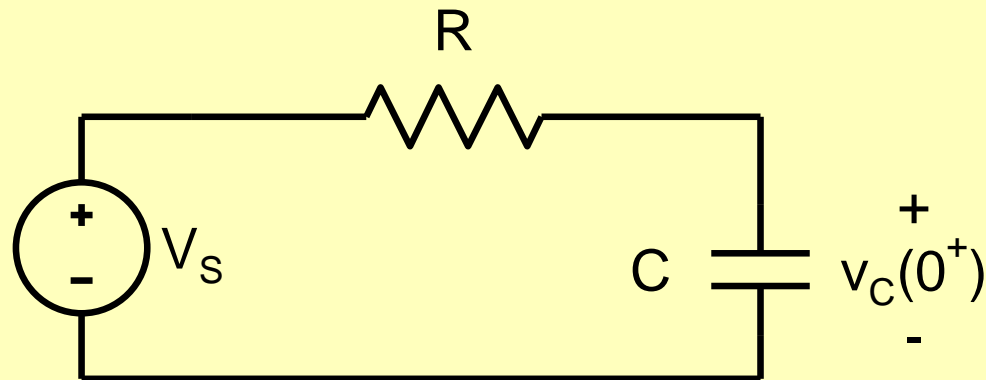

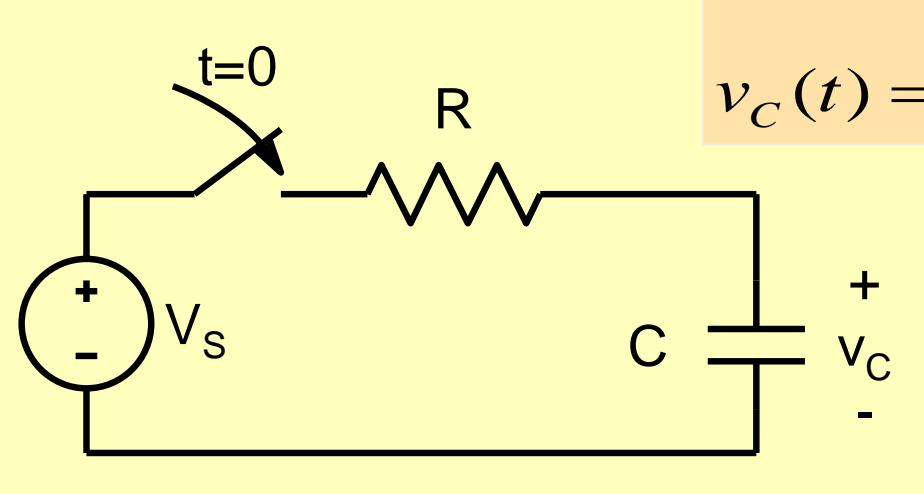

$$v_C(t) = v_C(\infty) + \{v_C(0^+) - v_C(\infty)\} e^{-\frac{t}{RC}}$$

$$v_C(0^+) = v_C(0^-)$$

We use the fact that voltage across a capacitor cannot change instantly

If the capacitor does not have any initial charge, then


$$v_C(0^+) = v_C(0^-) = 0$$

$$v_C(\infty) = V_s$$


$$v_C(t) = V_s (1 - e^{-\frac{t}{RC}})$$

$$\tau = RC$$

Charging a Capacitor

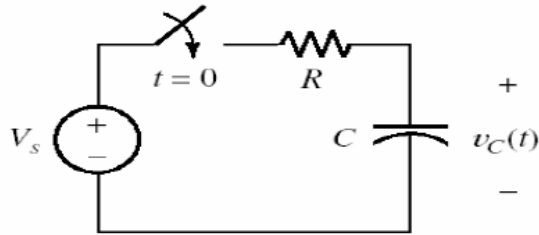


$$v_C(t) = V_s - V_s e^{-t/\tau}$$

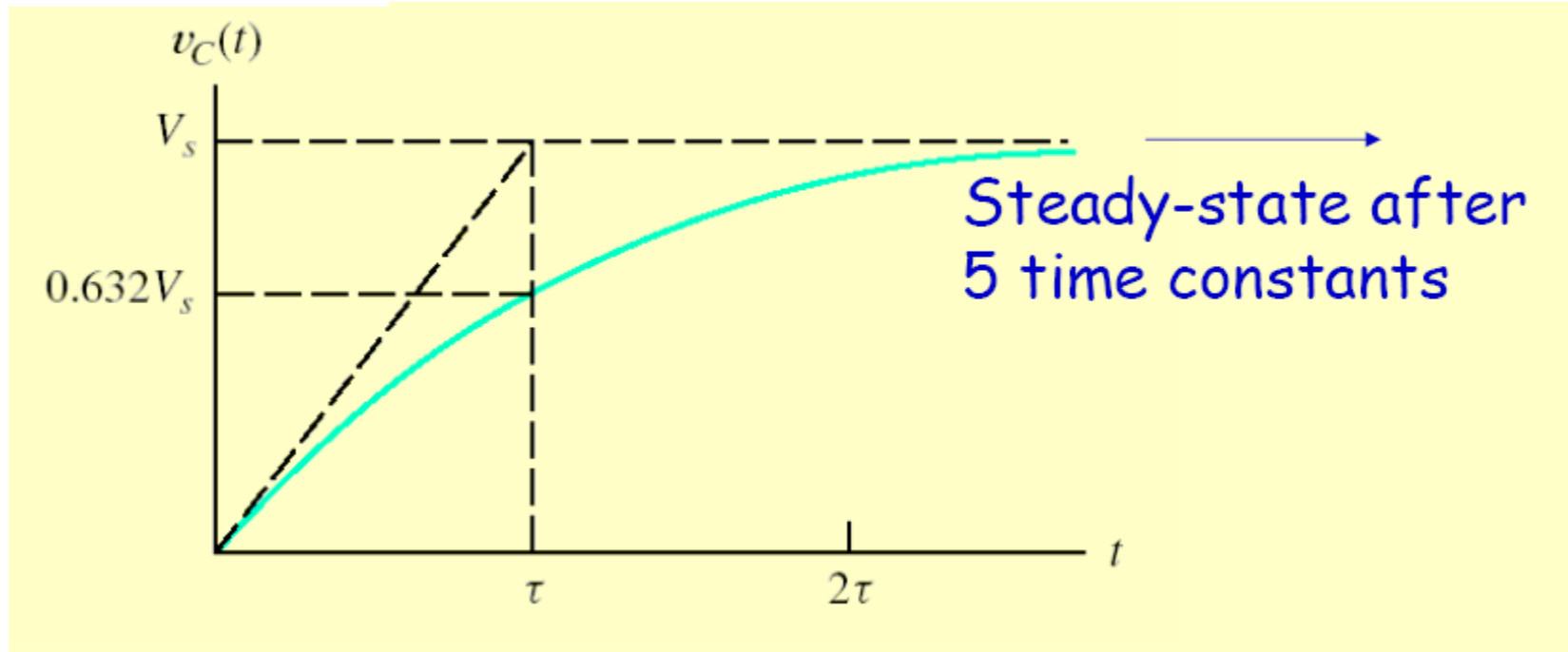

Time	τ	2τ	3τ	4τ	5τ
$V(t)/V_i$	0.632	0.865	.95	0.982	0.993

RL Transient Analysis

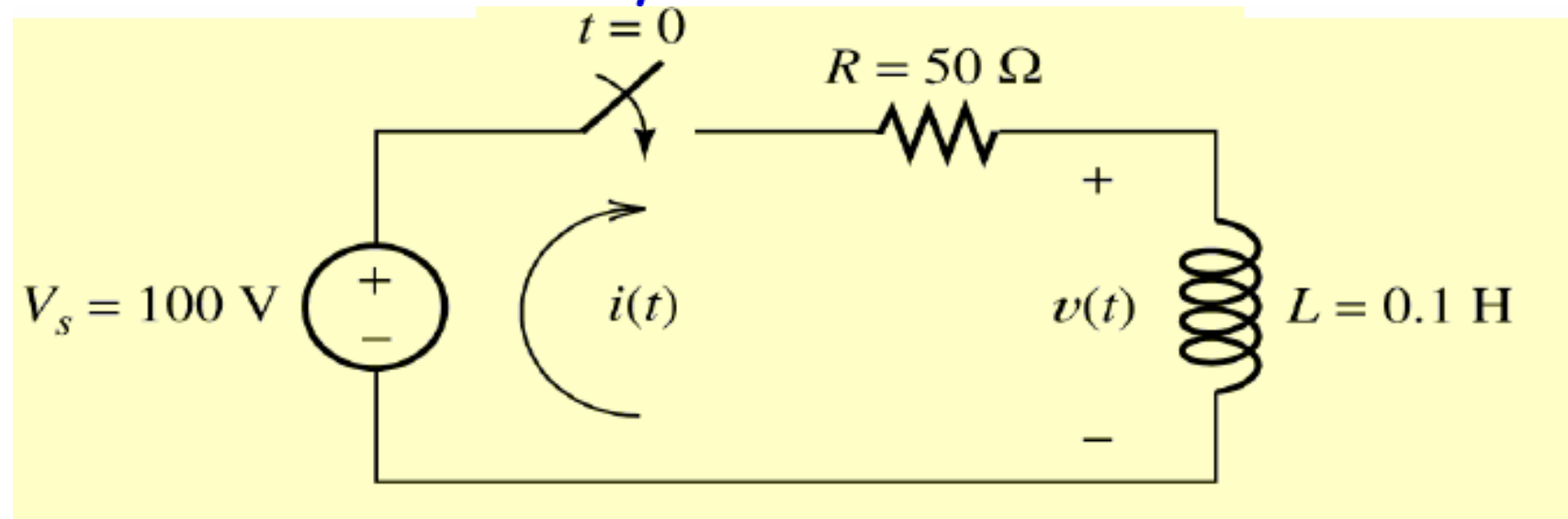

Write KVL equation:

$$\frac{dx}{dt} = -a_1 x + a_2$$

$$Ri(t) + L \frac{di}{dt} = V_s$$

$$v = L \frac{di}{dt}$$

$$x(t) = x(\infty) + \{x(0) - x(\infty)\} e^{-a_1 t}$$


$$i(t) = i(\infty) + \{i(0) - i(\infty)\} e^{-\frac{R}{L}t}$$

$$e^{-\frac{t}{\tau}}$$

$$\text{Time Constant : } \tau = \frac{L}{R}$$

What is $i(\infty)$?

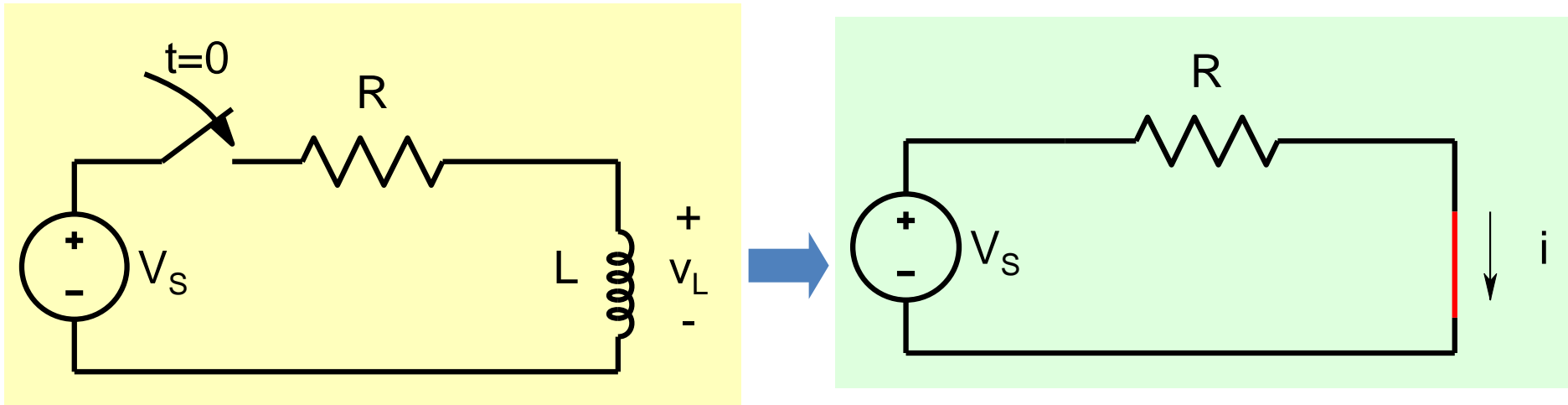Inductor in steady state is like a short circuit




$$i(\infty) = \frac{V_S}{R}$$

$$i(t) = \frac{V_S}{R} + \left\{ i(0) - \frac{V_S}{R} \right\} e^{-\frac{R}{L}t}$$

We also note that inductor current cannot change instantly

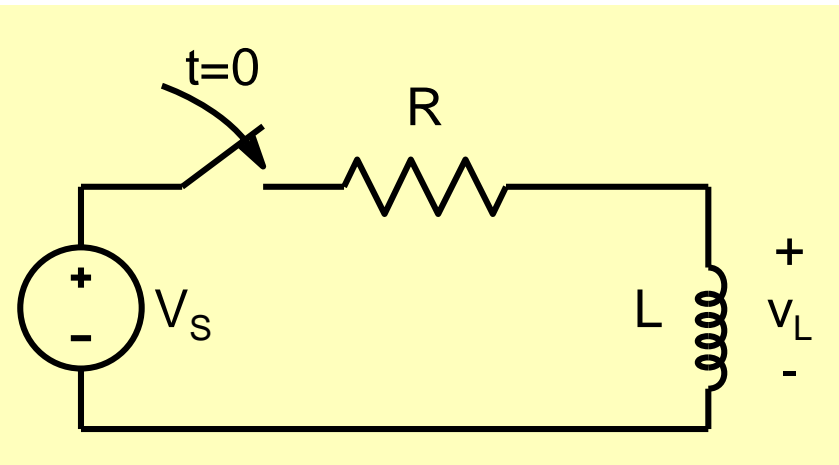
Current through an inductor cannot change instantaneously




$$i(0^+) = i(0^-)$$

If $i(0^+) = i(0^-) = 0$
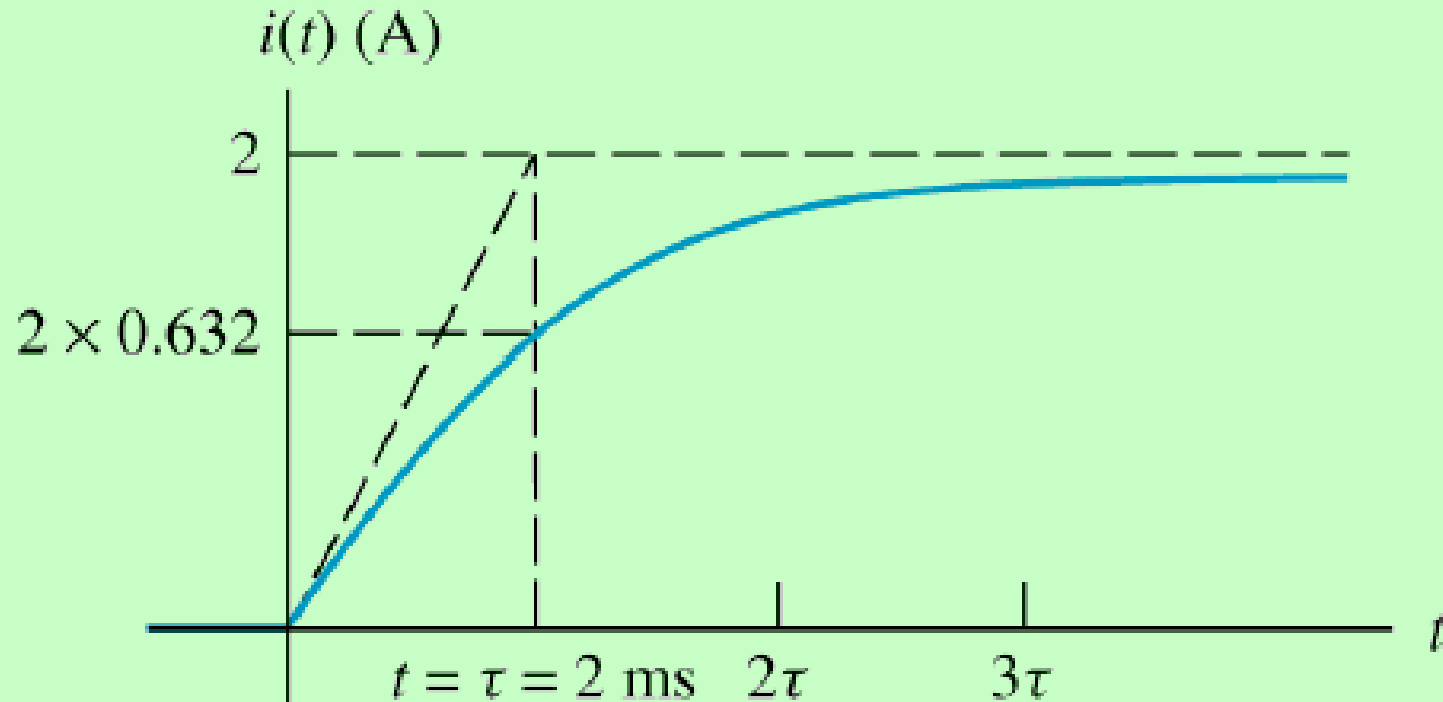
$$i(t) = \frac{V_S}{R} \times (1 - e^{-\frac{t}{\tau}})$$



What about voltage across the Inductor?

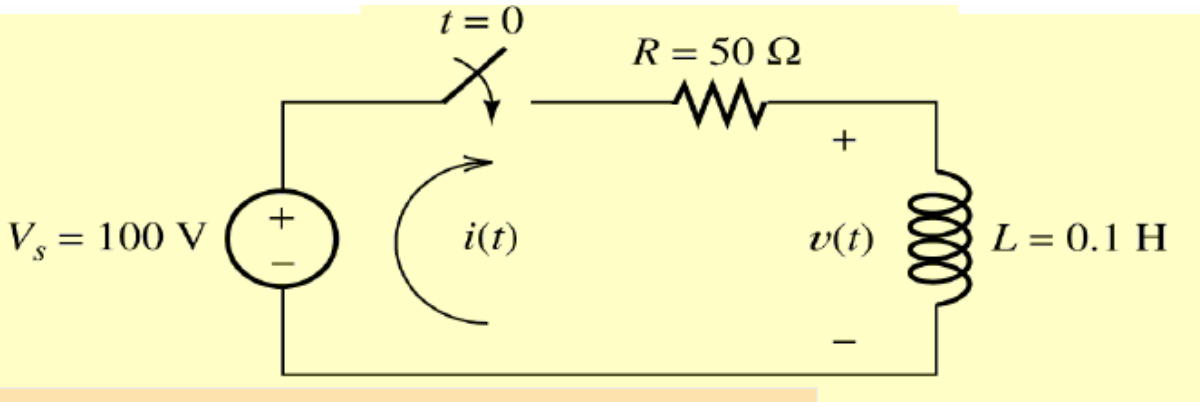

$$i(t) = \frac{V_s}{R} \times (1 - e^{-\frac{t}{\tau}})$$

$$v(t) = V_s e^{-\frac{t}{\tau}}$$

