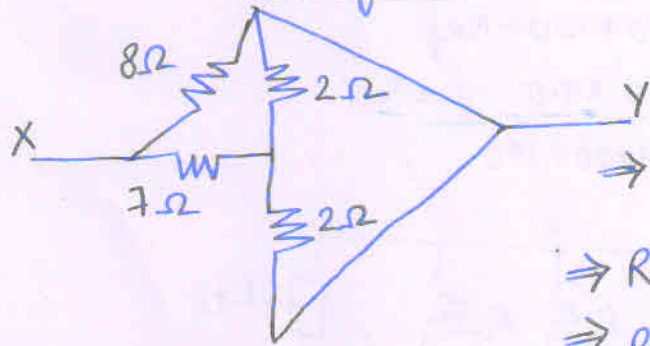


Assignment 1 SolutionsAns 1.



$$R_{eq} = R_1 \parallel [R_4 + (R_2 \parallel R_3)]$$

$$\Rightarrow R_{eq} = 8 \parallel [7 + (2 \parallel 2)] \Omega$$

$$\Rightarrow R_{eq} = 8 \parallel [7 + 1] \Omega$$


$$\Rightarrow R_{eq} = 8 \parallel 8 \Omega$$

$$\Rightarrow R_{eq} = 4 \Omega$$

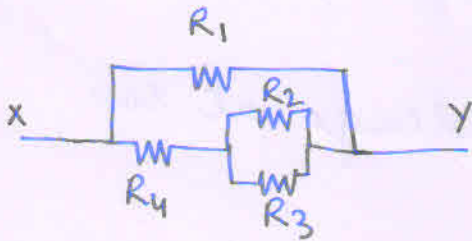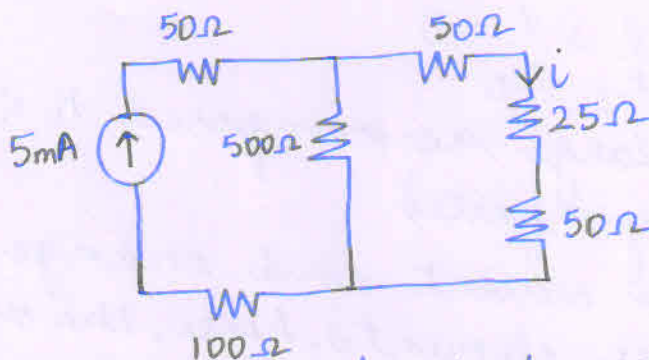Ans 2. (a)

Let current through 25Ω be i .

The circuit can be reduced as:

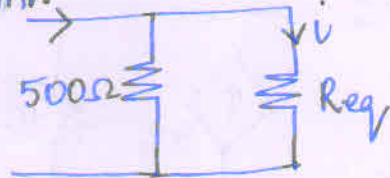


$$R_{eq} = 50 \Omega + 25 \Omega + 50 \Omega = 125 \Omega$$

\therefore By current division,


$$i = \frac{5 \text{mA} \times 500}{500 + 125} = 4 \text{mA}$$

(b)

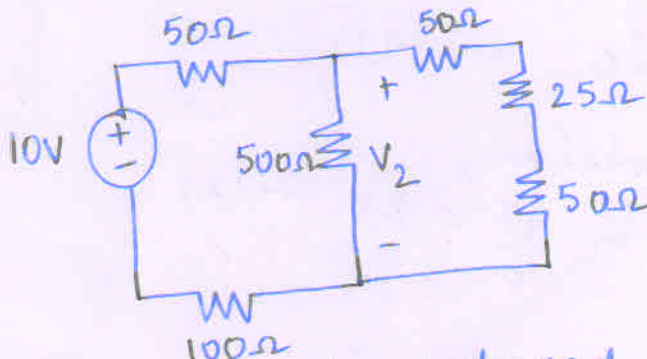

Let voltage across R_2 be V_2 .

The circuit can be reduced as:

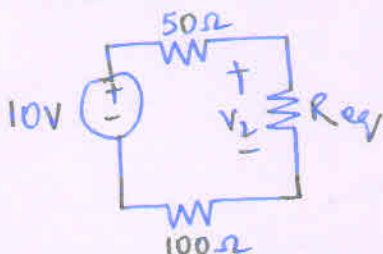

$$R_{eq} = 500 \parallel (50 + 25 + 50) \Omega = \frac{500 \times 125}{500 + 125} \Omega = 100 \Omega$$


By voltage division,

$$V_2 = \frac{10 \times R_{eq}}{50 + 100 + R_{eq}} \text{ V}$$

$$\Rightarrow V_2 = \frac{10 \times 100}{50 + 100 + 100} \text{ V} = 4 \text{ V}$$

(2)

Ans 3.

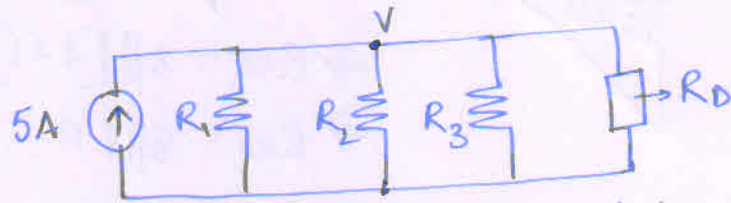


Let resistance of DMM be R_D . Let voltage at top node be V . Applying KCL,

$$-5 + \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \frac{V}{R_D} = 0$$

If R_D is not very large as compared to R_1, R_2, R_3 ,
(ideally infinite)

then, it will draw current and change the current through other elements, hence, the voltage.

Ans 4.

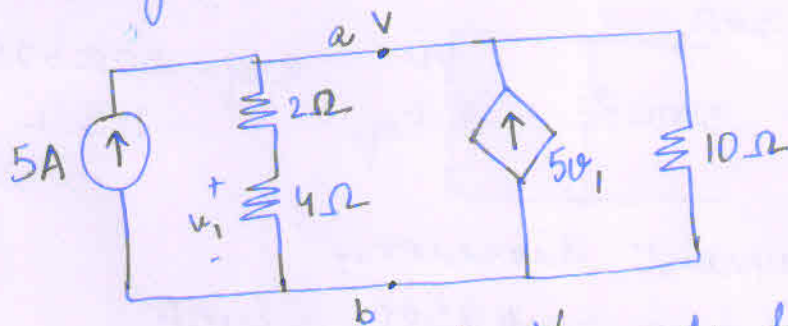

Let voltage at node a be V and let b be the reference node. Applying KCL at node a ,

$$-5 + \frac{V}{6} - 5V_1 + \frac{V}{10} = 0 \quad \text{--- (1)}$$

also, by voltage division,

$$V_1 = \frac{V \times 4}{2 + 4} = \frac{4V}{6} = \frac{2V}{3} \quad \text{--- (2)}$$

From (1) and (2),

$$-5 + \frac{V}{6} - 5\left(\frac{2V}{3}\right) + \frac{V}{10} = 0$$

$$\Rightarrow \frac{V}{6} - \frac{10V}{3} + \frac{V}{10} = 5$$

(3)

$$\Rightarrow \frac{5V - 100V + 3V}{30} = 5$$

$$\Rightarrow -92V = 5 \times 30$$

$$\Rightarrow V = -\frac{5 \times 30}{92} V$$

$$\therefore \text{Power across } 10\Omega = \left(\frac{5 \times 30}{92} \right)^2 \times \frac{1}{10} W$$

$$= \frac{25 \times 900}{920 \times 92} W = 265.83 mW$$

Ans 5. (a)



(b) A 15A circuit operating at 120V consumes
 $15 \times 120W = 1800W$ total power

Total power in a parallel circuit is the sum of power consumed in individual branches.

i) Coffee maker + microwave oven


$$: 850W + 1200W = 2050W > 1800W$$

ii) Microwave oven + toaster = $1200W + 900W = 2100W > 1800W$

iii) Toaster + coffee maker = $900W + 850W = 1750W < 1800W$

\therefore On this circuit, only coffee maker and toaster can be operated simultaneously. All other combinations will trigger the circuit breaker to open.

Ans 6.

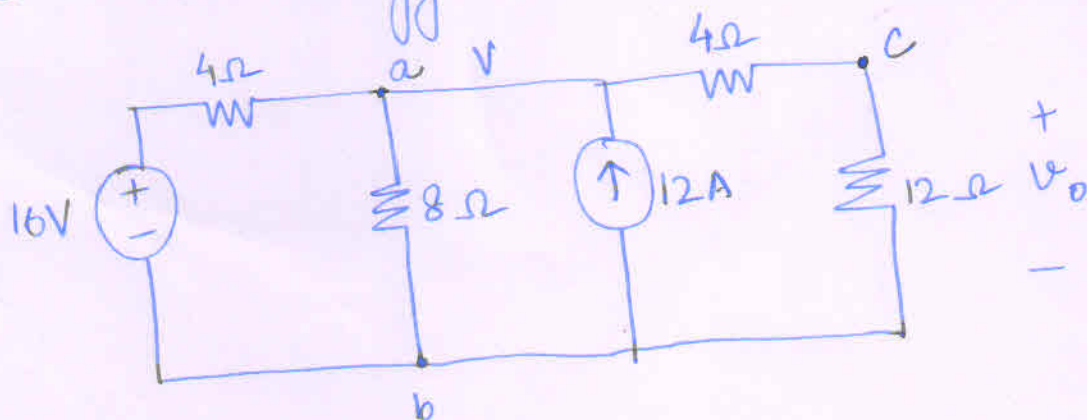

Let voltage at node a be V and let b be the reference node. Applying KCL at node a, (4)

$$\frac{V-16}{4} + \frac{V}{8} + \frac{V-V_0}{4} - 12 = 0$$

$$\Rightarrow 5V - 2V_0 = 128 \quad \text{--- (1)}$$

Applying KCL at node c,

$$\frac{V_0 - V}{4} + \frac{V_0}{12} = 0$$

$$\Rightarrow V = \frac{4V_0}{3} \quad \text{--- (2)}$$

From (1) and (2),

$$5\left(\frac{4V_0}{3}\right) - 2V_0 = 128$$

$$\Rightarrow V_0 = \frac{128 \times 3}{14} \text{ V} = 27.42 \text{ V}$$