 


ESc201 : Introduction to Electronics

Sequential Circuits


Amit Verma
Dept. of Electrical Engineering
IIT Kanpur

SR latch (recap)




S	R	Q	\overline{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\overline{Q}	HOLD
1	1	0	0	INVALID

NAND Latch (recap)

 


S	R	Q	\overline{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\overline{Q}	HOLD
0	0	1	1	INVALID

RS NAND Latch with Enable (recap)

 


Hold State

 


Enable	S	R	Q	\overline{Q}	State
0	x	x	Q	\overline{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\overline{Q}	Hold
1	1	1	0	0	Invalid

D latch (recap)


 


Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid

 



If $EN = 1$ then $Q = D$ otherwise the latch is in Hold state

  Edge Triggered Latch or Flip-flop (recap)




Positive edge triggered flipflop

  Negative Edge Triggered Latch or Flip-flop (recap)



Characteristic table (recap)

 
Given a input and the present state of the flip-flop, what is the next state of the flip-flop



Inputs (D)	Q(t+1)
0	0
1	1

Characteristic equation: $Q(t+1) = D$

JK Flip-flop

 

Inputs J K	Q(t+1)
0 0	Q(t)
0 1	0
1 0	1
1 1	$\overline{Q(t)}$

Characteristic equation: $Q(t+1) = J\overline{Q}(t) + \overline{K}Q(t)$

JK flip flop is refinement of RS flip flop where indeterminate state of RS flip flop is defined in JK Flip Flop


JK Flip-flop (characteristic equation)

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Q \ JK					
		00	01	11	10
0				1	1
1	1				1

$$Q(t+1) = J\bar{Q}(t) + \bar{K}Q(t)$$

Toggle or T Flip-flop (recap)

 


Inputs (T)	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

Characteristic equation: $Q(t+1) = T \oplus Q(t)$

T	$Q(t)$	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Toggle or T Flip-flop (recap)

 

Inputs (T)	$Q(t+1)$
0	$Q(t)$
1	$\overline{Q(t)}$

Characteristic equation:

$$Q(t+1) = T \oplus Q(t)$$

Excitation Table

What inputs are required to effect a particular state change


Q	T	$Q(t+1)$
0	0	0
0	1	1
1	0	1
1	1	0

Excitation Table

Inputs

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

JK Flip-flop excitation table (recap)

 

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	$\overline{Q(t)}$


Characteristic Table

		Inputs	
Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Excitation Table

Q	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

D Flip flop excitation table

 

D	Q(t+1)
0	0
1	1

Characteristic Table


Q	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

Inputs

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table

Convert a D FF to JK FF

 

J	K	Q	Q(t+1)	D
0	X	0	0	0
1	X	0	1	1
X	1	1	0	0
X	0	1	1	1

Inputs

Q(t)	Q(t+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0


Excitation Table

Inputs

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table


Convert a D FF to JK FF

 

J	K	Q	Q(t+1)	D
0	X	0	0	0
1	X	0	1	1
X	1	1	0	0
X	0	1	1	1


Q \ JK	JK			
	00	01	11	10
0			1	1
1	1			1

$$D = \overline{Q}.J + Q.\overline{K}$$

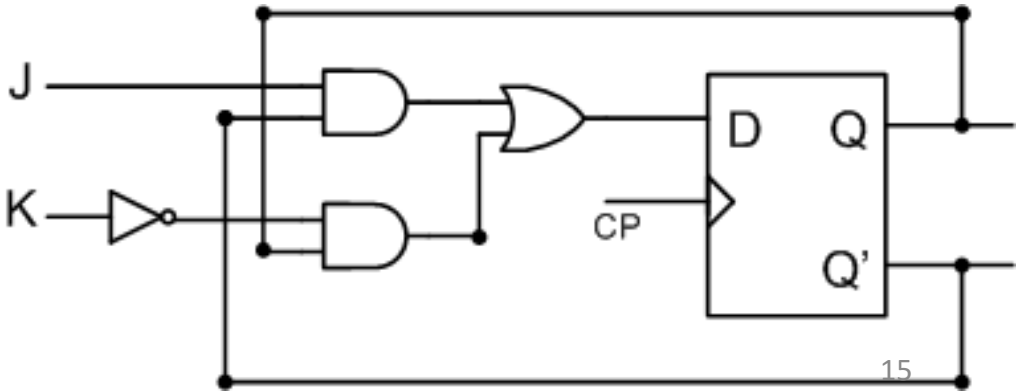

Convert a D FF to JK FF


$$D = \overline{Q}.J + Q.\overline{K}$$

 

Q	J	K	D	Q(t+1)
0	0	0	0	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	1
1	0	0	1	1
1	0	1	0	0
1	1	0	1	1
1	1	1	0	0

Inputs	J	K	Q(t+1)
	0	0	Q(t)
	0	1	0
	1	0	1
	1	1	<u>Q(t)</u>

Sequential Circuits

 


The binary information stored in the storage elements at any given time defines the **state** of the sequential circuit at that time

Output is a function of input as well as the present state of the storage elements.

Next state is also a function of the present state and the external inputs.

Synchronous Sequential Circuits

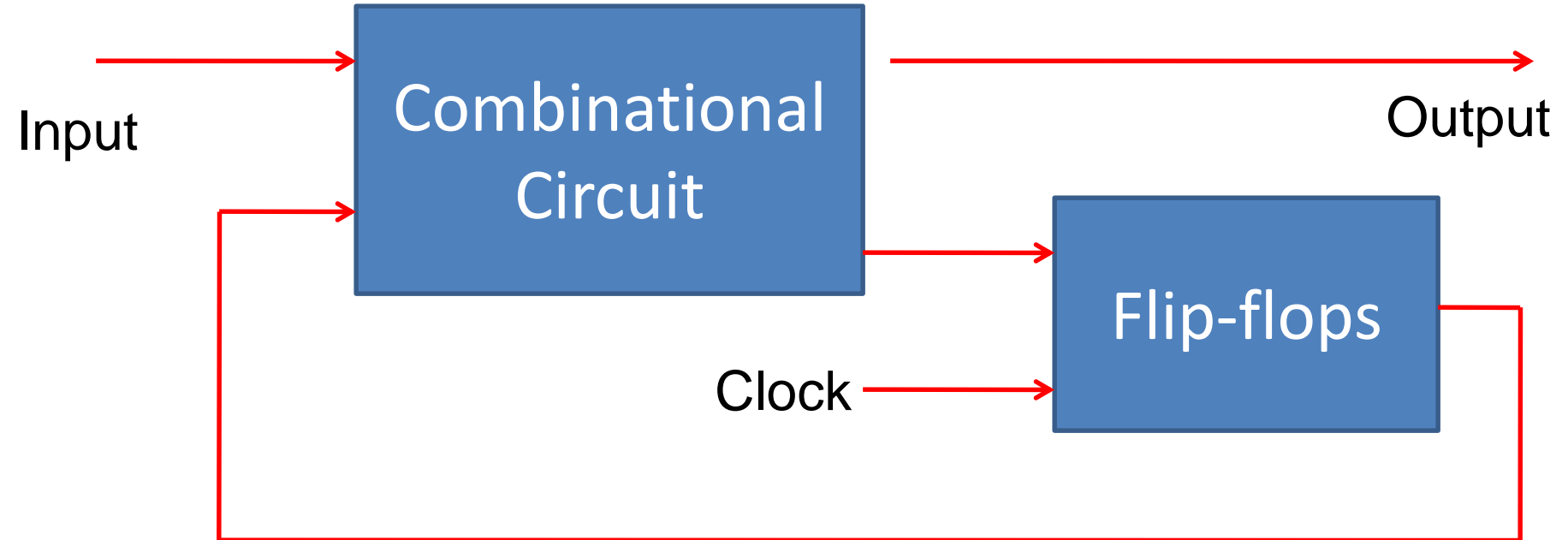


Employs signals that affect the storage elements only at discrete instants of time.

Synchronization is achieved via the ***clock pulses***.

Synchronous Clocked Sequential Circuits

Analysis

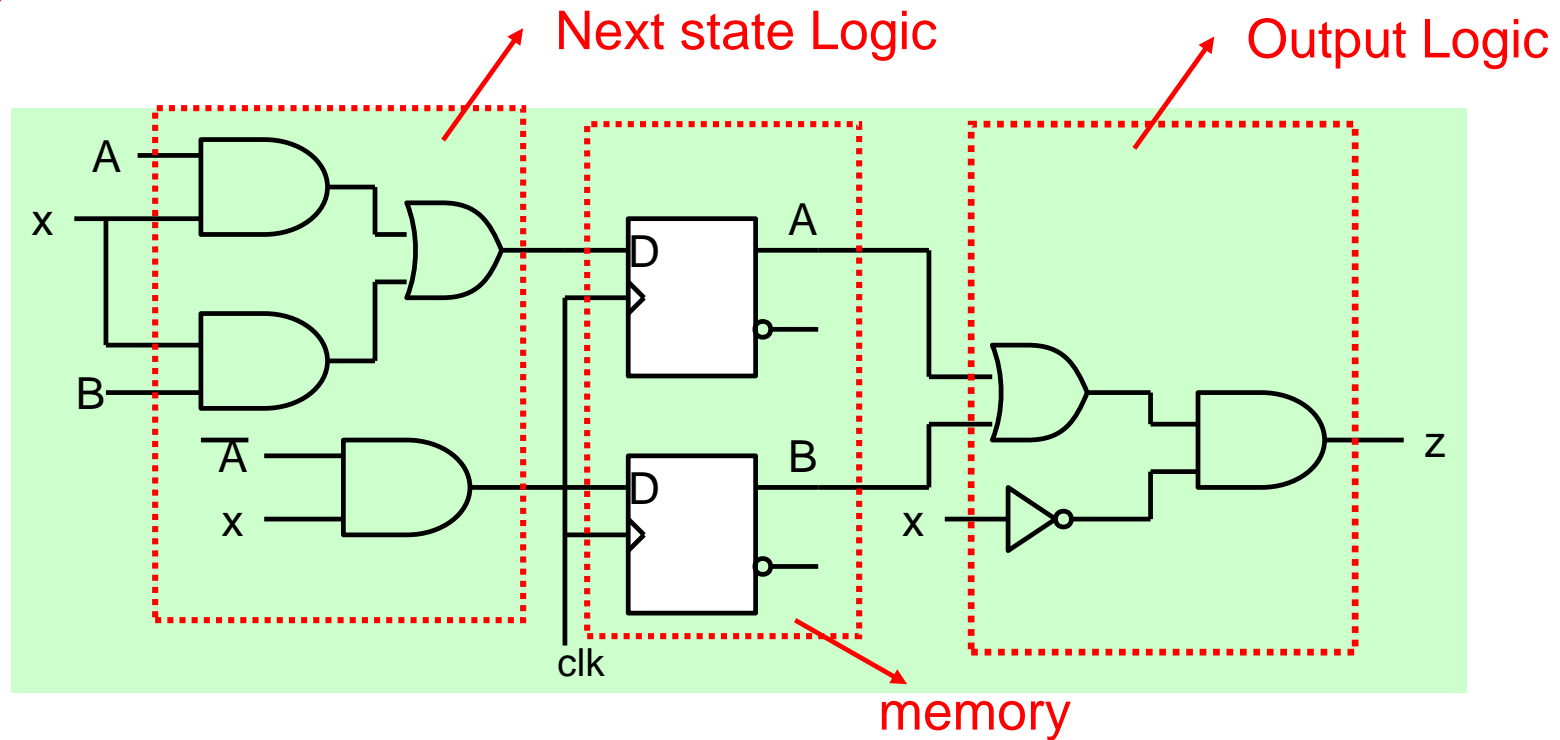


Output z depends on the input x and on the state of the memory (A, B)

The memory has 2 FFs and each FF can be in state 0 or 1. Thus there are four possible states: AB : 00, 01, 10, 11.

To describe the behavior of a sequential circuit, we need to show

1. How the system goes from one memory state to the next as the input changes
2. How the output responds to input in each state

Analysis of Sequential Circuits

 

Next state Logic

Output Logic

memory

clk

$$D_A = A.x + B.x \quad ; \quad D_B = \overline{A}.x ; z = (A + B).\overline{x}$$


State Transition Table

Present State		Input	Next State		Output
A	B	x	A	B	z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

$$A(t + 1) = A(t).x + B(t).x$$
$$B(t + 1) = \overline{A(t)}.x$$
$$z = (A + B).\overline{x}$$

State Transition Table

Present State		Input	Next State		Output
A	B	x	A	B	z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

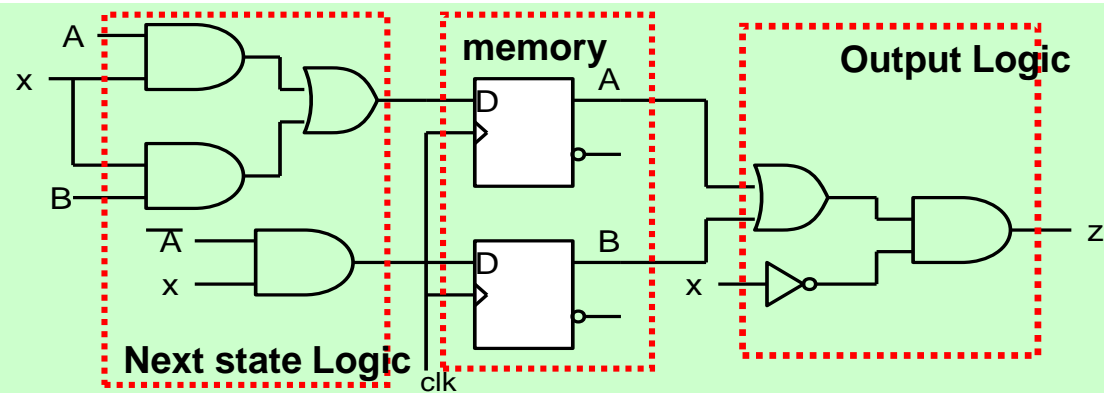

00

Memory state in which FF A& B have output values 00

x=0/z

?


00

x=1/z


?

If $x = 0$ then $z = 0$, When the clock edge comes the system would stay in 00 state.

 
If $x = 1$ then $z = 0$. When the clock edge comes the system would go to 01 state.



Analysis of Sequential Circuits

 

 
$$\begin{aligned} A(t+1) &= A(t).x + B(t).x \\ B(t+1) &= \overline{A(t)}.x \\ z &= (A + B). \overline{x} \end{aligned}$$




State transition Graph

State Transition Table

Present State		Input	Next State		Output
A	B	x	A	B	z
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 

State transition Graph

 

Quiz-2 Solution Discussion