


ESc201 : Introduction to Electronics

Counters

Amit Verma
Dept. of Electrical Engineering
IIT Kanpur


Recap

D Flip-flop

 

Inputs (D)	$Q(t+1)$
0	0
1	1


JK Flip-flop

 

Inputs J K	$Q(t+1)$
0 0	$Q(t)$
0 1	0
1 0	1
1 1	$\overline{Q(t)}$



Recap

Toggle or T Flip-flop

 

Inputs (T)	Q(t+1)
0	Q(t)
1	$\overline{Q(t)}$


Counters

  


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

In state S_0 , the output ABC is 000, in S_1 001 and so on

 There are 8 states so 3 FFs are at least required. Let us choose T FF.




PS			NS					
A	B	C	A	B	C	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

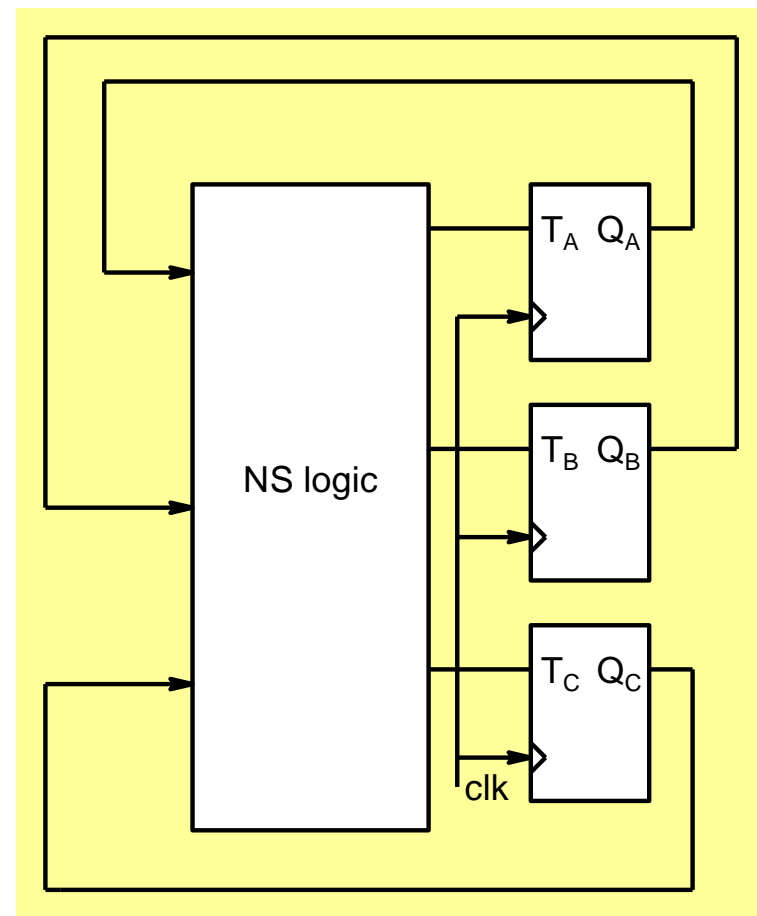


$$T_A = B.C ; T_B = C ; T_C = 1$$

Please prove this!

Binary UP counter

 


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

 


$$T_A = B.C ; T_B = C ; T_C = 1$$

Counter with Enable


 


Counter is in Hold state.

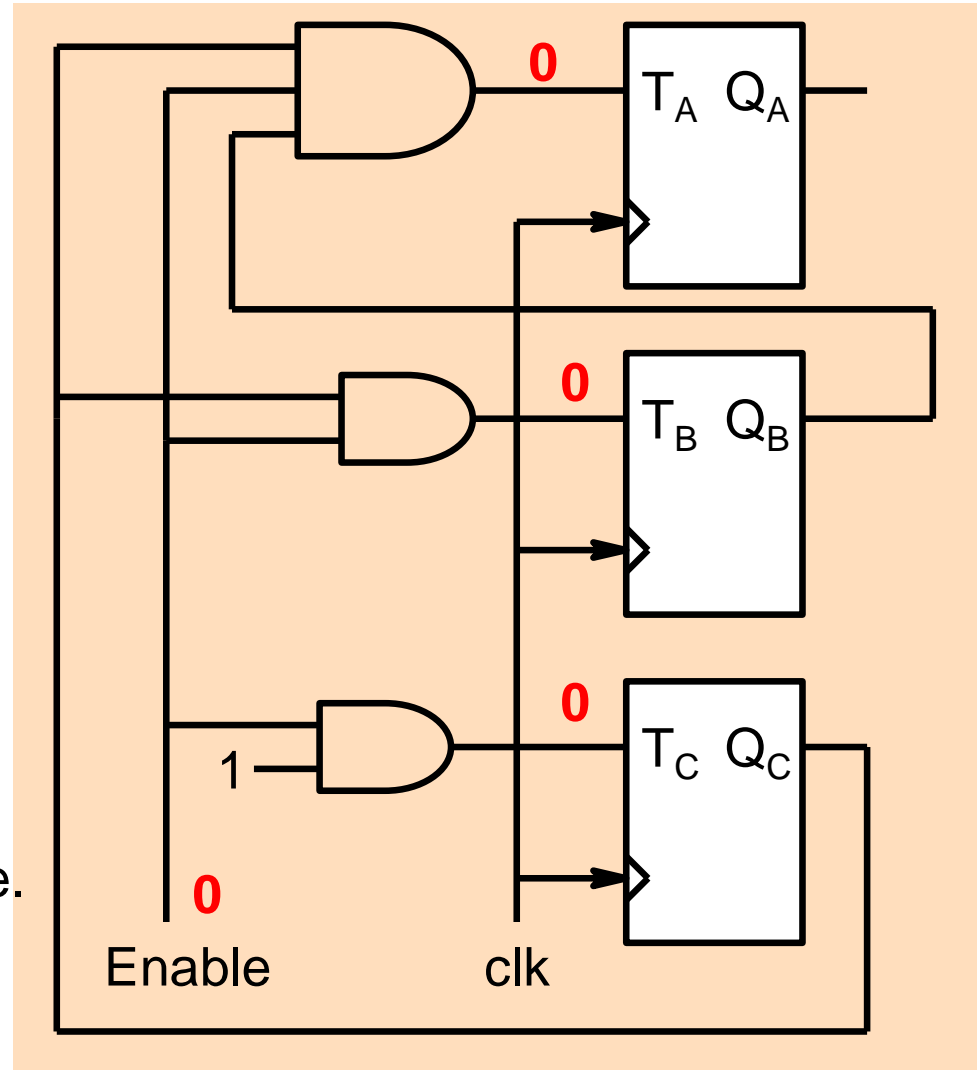

When Enable = 1, the counter begins the count.

Counter with Asynchronous Reset

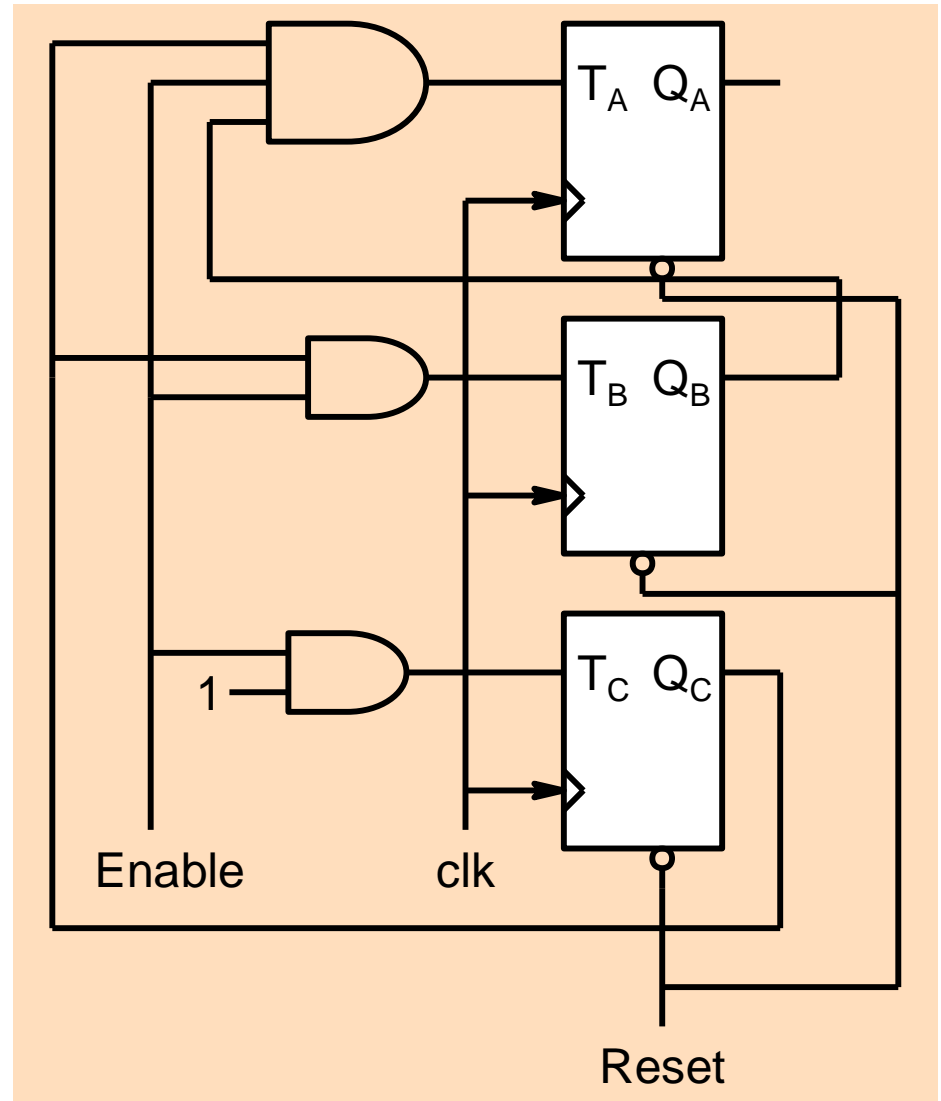 


When Reset = 1, counter gets initialized to a known state.

- D toggles every clock cycle
- C toggles only when D is 1
- B toggles only when both C and D are 1
- A toggles only when B C D are 1

T FF toggles when $T=1$

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
0	0	0	0

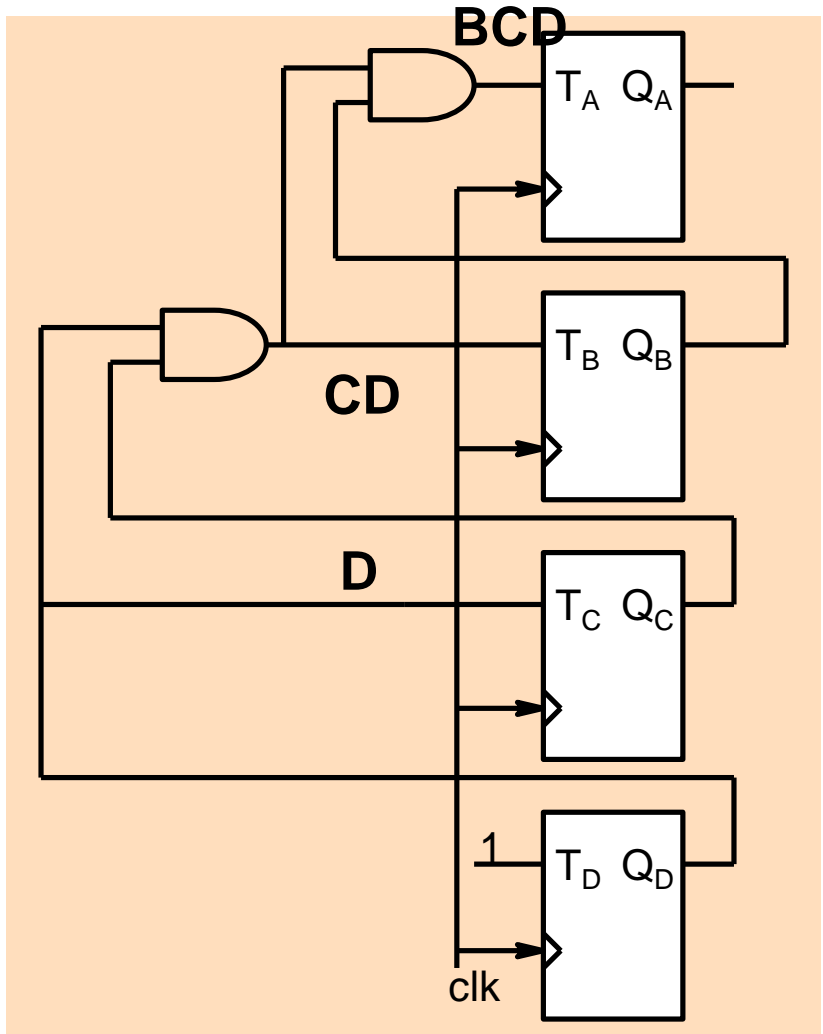


4-bit Down Counter

A B C D

1 1 1 1
1 1 1 0
1 1 0 1
1 1 0 0
1 0 1 1
1 0 1 0
1 0 0 1
1 0 0 0
0 1 1 1
0 1 1 0
0 1 0 1
0 1 0 0
0 0 1 1
0 0 1 0
0 0 0 1
0 0 0 0
1 1 1 1

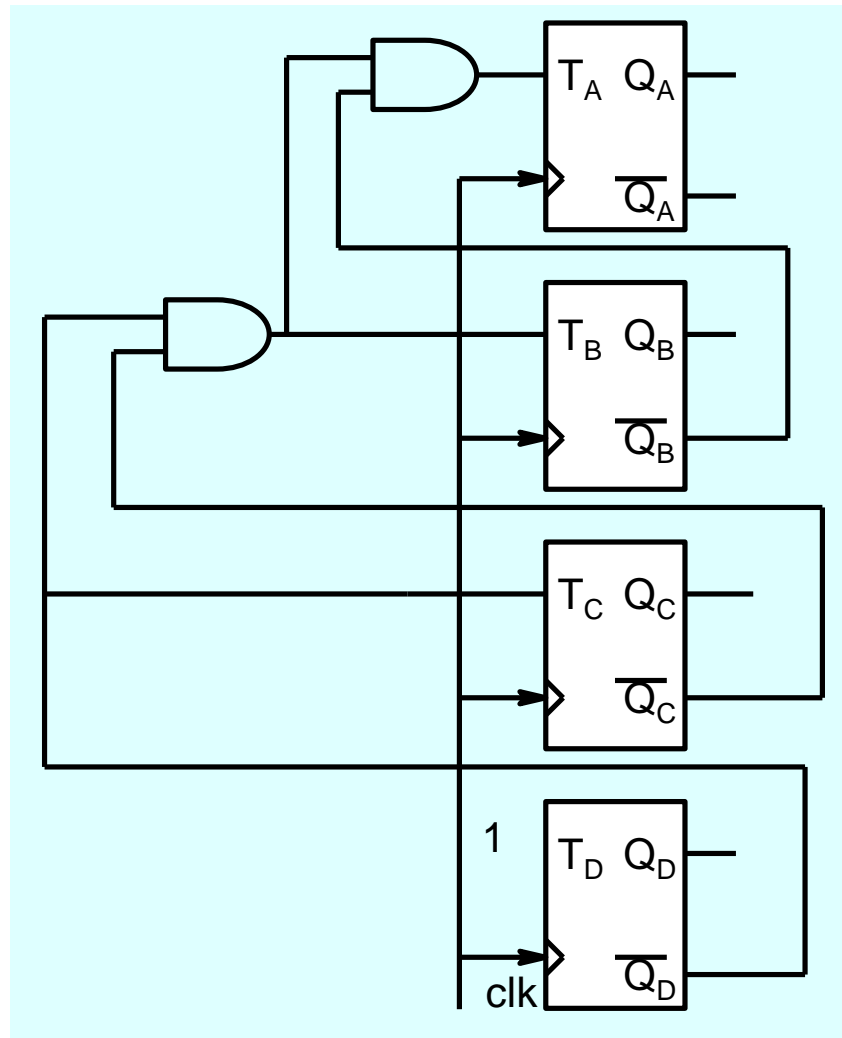- D toggles every clock cycle
- C toggles only when D is 0
- B toggles only when both C and D are 0
- A toggles only when D C B are 0



Counters

A	B	C
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0

Binary down counter

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

Decade counter

Modulo-10 Counter

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

Modulo-5 Counter

Counter with Unused States

PS			NS								
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

There are two unused states 011 and 111. one approach to handle this situation is that, while evaluating expressions for J K , we use don't care conditions corresponding to these unused states

Counter with Unused States

PS			NS								
A	B	C	A	B	C	J _A	K _A	J _B	K _B	J _C	K _C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

		BC			
		00	01	11	10
A	0	0	0	X	1
	1	X	X	X	X

$J_A = B$

Counter with Unused States



PS			NS			J_A K_A		J_B K_B		J_C K_C	
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

$$J_A = B \quad K_A = B$$

$$J_B = C \quad K_B = 1$$


$$J_C = \overline{B} \quad K_C = 1$$

  After synthesizing the circuit, one needs to check that if by chance the counter goes into one of the unused states, after one or more clock cycles, it enters a used state and then remains among the used states




We can see that if by chance the counter goes into unused states 111 or 011, then after a clock cycle it enters one of the used states.


Counter as frequency divider

 

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

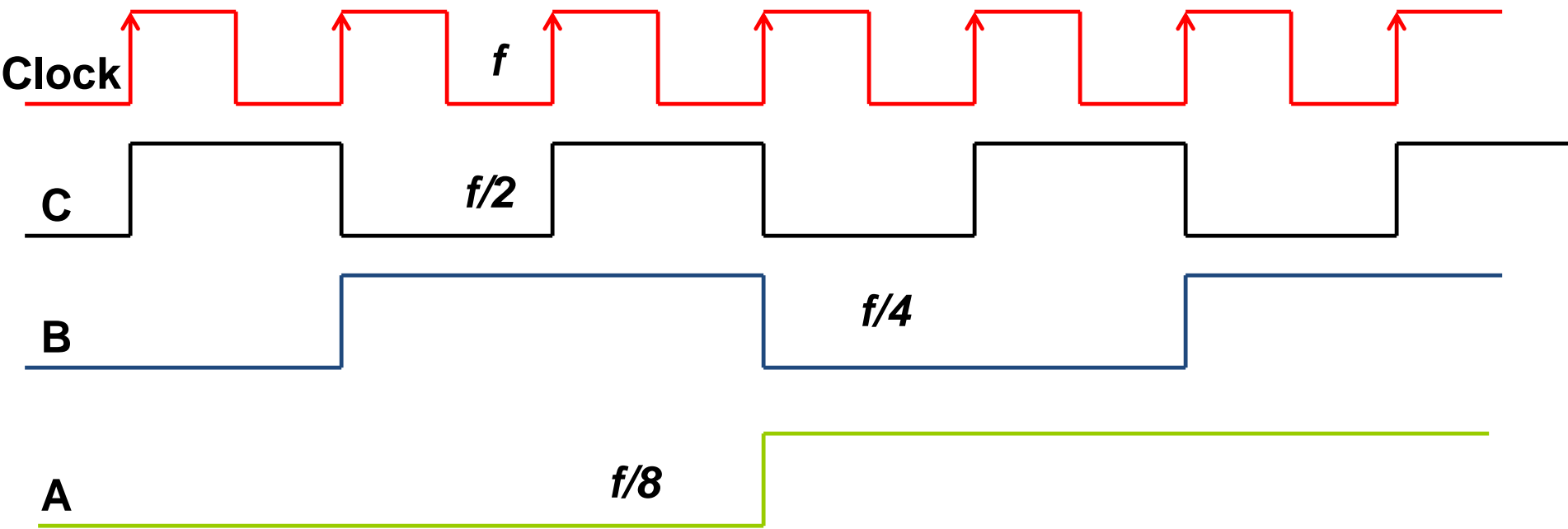

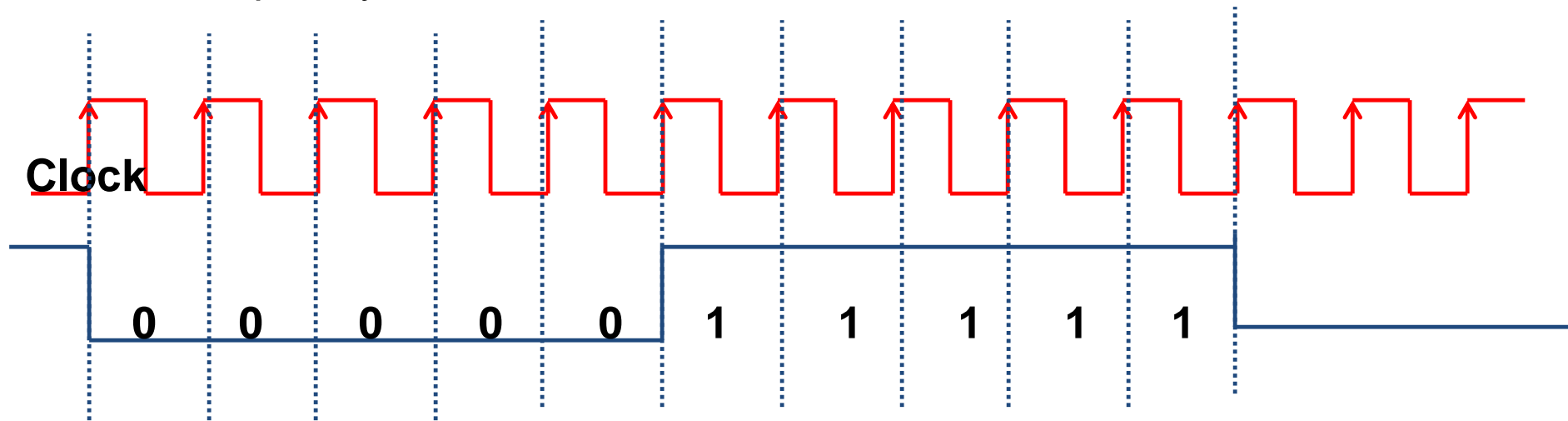
Example From a frequency of 10KHz, generate the following signal of frequency 1KHz



A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

This will have a frequency of 1KHz but it will not have the same waveform


Clock

 


Design a divide by 10 counter with the following states

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0

 Example From a frequency of 10KHz, generate the following signal of frequency 2KHz



 A divide by 5 counter is required that has 5 states.



A will give the required waveform.