

# ESC201A EndSem Part 2

SAMYAK SINGHANIA

TOTAL POINTS

**9 / 19**

QUESTION 1

**Q1** 9 pts

**1.1 1(a) 1 / 3**

+ 3 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

✓ + 1 pts *DC Equivalent circuit correctly found*

+ 1 pts Transistor currents correctly found

+ 1 pts Collector voltage correctly found

1 IB=0

2 IC=0

**1.2 1(b) 2 / 6**

+ 6 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 3 pts Transistor currents correctly found

+ 1.5 pts RE correctly calculated

+ 1.5 pts R2 correctly calculated

+ 2 Point adjustment

QUESTION 2

**Q2** 10 pts

**2.1 2(a) 6 / 6**

✓ + 6 pts *Completely Correct*

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 2 pts Desirable circuit schematic correctly

drawn

+ 1 pts Feedback resistance correctly found

+ 1.5 pts Resistors corresponding to source v1 correctly found

+ 1.5 pts Resistors corresponding to source v2 correctly found

**2.2 2(b) 0 / 4**

+ 4 pts Completely Correct

✓ + 0 pts *Completely Incorrect*

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1 pts Bias state of diodes correctly found

+ 1.5 pts Vo1 correctly found

+ 1.5 pts Vo2 correctly found

Name **SAMYAK SINGHANIA** Roll No. **210917** Seat/Room No. **128 / L-19**

1 (a). Carry out dc analysis to determine collector voltage for the circuit shown below. Assume that current gain  $\beta_F = 100$ . [3]

For DC analysis.

$$\frac{I_C}{I_B} = 100$$

$$\therefore I_E = I_C + I_B = 101 I_C$$

$$1 \text{ mA} + \frac{V_E}{1 \text{ k}\Omega} = 101 I_C$$

$$V_E = 101 I_C \times 1 \text{ k}\Omega$$

$$\text{Also, } 5 \text{ V} = 4 \text{ k}\Omega I_C + V_{CE} + V_E$$

$$\Rightarrow 5 \text{ V} = 4 \text{ k}\Omega I_C + V_C - V_E + V_E$$

$$\text{Also, } 1 + V_E = 101 I_C \times 10^3$$

$$\therefore 5 \text{ V} = \frac{4 \times (1 + V_E)}{101} + V_C$$

$$\text{Also, we can see that } V_{BE} + V_E = 0$$

$$\Rightarrow V_B = 0$$

$$\therefore V_{BE} = 0.7 \Rightarrow V_E = -0.7 \text{ V}$$

$$\therefore 5 \text{ V} = \frac{4}{101} \times 0.3 + V_C$$

$$\Rightarrow V_C = 4.988 \text{ V}$$

$$V_{CE} = 5.688 \text{ V}$$

$$V_{CE} > 0.2 \Rightarrow \text{It is in forward active.}$$



1 (b). Determine suitable values for resistances  $R_E$  and  $R_2$  so as to obtain a voltage gain of -1 for the amplifier shown. Assume that dc value of base voltage is 5.9 V, transistor is in forward active mode, thermal voltage  $V_T = 0.026 \text{ V}$  and  $\beta_F = 100$ . [6]

$$A_v = -50$$

$$\therefore V_T = 26 \text{ mV}$$

$$g_m = \frac{I_C}{V_T}$$

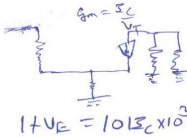
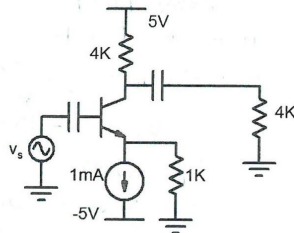
$$R_{E_{\text{eq}}} = \frac{\beta}{g_m}$$



$$V_{BE} = 0.7$$

$$V_B = 0.7 + V_E$$

$$V_{BE} + V_E = 0$$

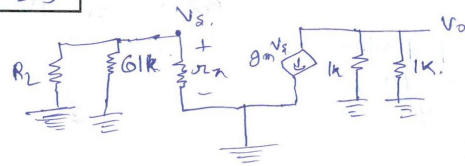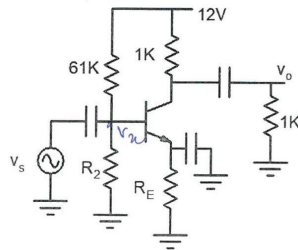

$$V_O = -g_m V_{be} \left( \frac{1}{2} \text{ k}\Omega \right)$$

$$\Rightarrow A_v = \frac{V_O}{V_{be}} = -g_m \times 500 = -50$$

$$g_m = \frac{I_C}{V_T} = \frac{1}{10}$$

$$\therefore \frac{I_C}{V_T} = \frac{1}{10} \Rightarrow I_C = \frac{V_T}{10} = 26 \times 10^{-4} \text{ A}$$

$$\text{Now, } R_{E_{\text{eq}}} = \frac{\beta}{g_m} = \frac{100}{1/10} = 1000 \Omega$$

$$\text{Now, } d_B = \frac{V_{be}}{V_{be}} = \frac{V_{be}}{\beta} g_m$$

DC analysis:

$$I_2 = 10^3 I_C + V_{CE} + R_E I_E$$

$$I_2 = 10^3 I_C + \frac{101 I_C R_E}{100} + V_{CE}$$

$$V_{ce} = \frac{R_2 (12) \text{ V}}{61 \text{ k}\Omega + R_2}$$


$$\therefore V_{ce} = 0.7 \text{ V} + I_E R_E$$

$$\frac{12 R_2}{61 \text{ k}\Omega + R_2} = 0.7 \text{ V} + I_E R_E$$

$$A_v = -g_m R_{E_{\text{eq}}}$$


2(a). Design an opamp circuit that would produce the output voltage  $V_o = -2 \times 10^3 I_1 - 2v_1 + v_2$ , where  $I_1$ ,  $v_1$  and  $v_2$  are input current and input voltages respectively as shown below. Assume ideal opamp characteristics and use only one opamp. [6]

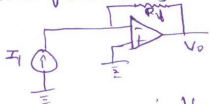using principle of superposition we can separate the output into following components




$$V_o = -R_f I_1$$

Take  $R_f = 2 \times 10^3 \Omega$

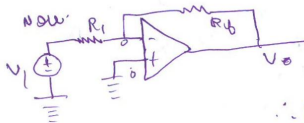
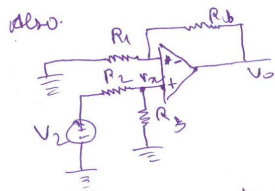
$$\begin{aligned} \frac{V_1 - 0}{R_1} &= \frac{0 - V_o}{R_f} \\ V_o &= -V_1 \frac{R_f}{R_1} \\ \therefore \frac{R_f}{R_1} &= 2 \Rightarrow R_1 = \frac{R_f}{2} \\ R_1 &= 10^3 \Omega \end{aligned}$$




$$\begin{aligned} V_x &= \frac{R_3}{R_2 + R_3} V_2 \\ \therefore \frac{V_x}{R_1} &= \frac{V_o - V_x}{R_f} \\ V_o &= V_x \left( 1 + \frac{R_f}{R_1} \right) \Rightarrow V_o = 3V_x \end{aligned}$$

$$V_o = 3 \times \frac{R_3}{R_2 + R_3} V_2 \Rightarrow \frac{3R_3}{R_2 + R_3} = 1 \Rightarrow R_3 = \frac{R_2}{2}$$

Choose  $R_2 = 2 \Omega$ ,  $R_3 = 1 \Omega$

Finally we get.

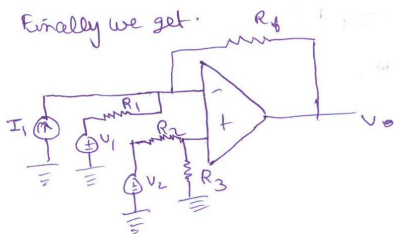

where  $R_f = 2 \times 10^3 \Omega$ ,  
 $R_1 = 10^3 \Omega$ ,  
 $R_2 = 2 \Omega$ ,  
 $R_3 = 1 \Omega$ .

2(b). Assuming ideal opamp and ideal diodes, determine output voltage  $V_{o1}$  and  $V_{o2}$ . Note that opamp supply voltages are  $\pm 12V$ . [4]

$$i = \frac{5 - 0}{1K} = 5mA$$

$\therefore$  Ideal opamp,  $V_- = V_+ = 0V$

Now,  $i = 5mA$

$$\therefore 5mA = \frac{0 - V_{o1}}{2K}$$

$$V_{o1} = -10V$$

$\therefore V_p = 0V$

$\Rightarrow V_{o2} < 0.7V$

$D_1$  is always off.

Clearly  $V_{o2} \rightarrow V_{o1}$

$\Rightarrow V_{o2} = V_{o1} + 0.7V$

$V_{o2} = -9.3V$

