

ESC201A Quiz3 Set A

SAMYAK SINGHANIA

TOTAL POINTS

8 / 10

QUESTION 1

Q1 5 pts

1.1 **Q1(a)** 2 / 3

+ 3 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

✓ + 1 pts 4-bit 2's complement representation
correct for both numbers

+ 0.5 pts 4-bit addition performed correctly

+ 0.5 pts Identified problem correctly

✓ + 1 pts 5-bit representation and addition correct

1.2 **Q1(b)** 2 / 2

✓ + 2 pts Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1 pts Solution correct but not minimal

QUESTION 2

2 **Q2** 4 / 5

+ 5 pts Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

✓ + 2.5 pts Excitation table for given flip flop

completely correct

✓ + 1.5 pts Assignment to input terminals of flip flop
correct

+ 1 pts Implementation of D flip correct with
minimal gates

Name: SAMYAK SINGHANIARoll. No. 210917Section: W3

Q.1(a) Carry out the operation $-5-6$ using 4-bit 2's complement representation. Do you get the right answer? If not, what is the problem? [3 Marks]

$$(5)_{10} = (0101)_2$$

signed bit representing positive.

$$\therefore -5 = 2's \text{ complement of } 5 = 1010 + 1 = \underline{1011}$$

$$(6)_{10} = (0110)_2$$

$$-6 = 1001 + 1 = \underline{1010}$$

$$\Rightarrow -5 - 6$$

$$= (-5) + (-6)$$

~~Magnitude of $10001 = 2's \text{ complement of } 10001$~~
 ~~$= 01110 + 1$~~

$$-5 - 6 = (-5) + (-6)$$

$$1011$$

$$+ 1010$$

$$\underline{10101}$$

\Rightarrow Negative Number since signed bit is 1.

~~$$\begin{array}{r} 1011 \\ + 0110 \\ \hline 10001 \end{array}$$~~

Negative No.

signed bit is 1

$$\text{Magnitude of } 10101 = 2's \text{ complement} = 01010 + 1 = (01011)_2 = 11$$

$$\therefore -5 - 6 = -11$$

The result is -11 & we got the right answer.

(b) Show how one can use a 4 to 1 multiplexer to implement the following 6-variable


Boolean expression: $F = \overline{x_1} \cdot \overline{x_2} \cdot x_3 + x_1 \cdot \overline{x_2} \cdot x_4 + \overline{x_1} \cdot x_2 \cdot x_5 + x_1 \cdot x_2 \cdot x_6$. Use minimum number

of external gates. [2 Marks]

Design the 4 to 1 multiplexer as follows.


x_1	x_2	x_3	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

 Hence, we can design the 4 to 1 multiplexer as follows



x_1	x_2	F
0	0	$F = x_3$
0	1	$F = x_5$
1	0	$F = x_4$
1	1	$F = x_6$

 Q.2 The characteristic table for a flip-flop X with two inputs A and B is given below. Show how one can implement a D flip-flop using flip-flop X and basic gates. Use as few gates as possible. [5 Marks]



A	B	$Q(t+1)$	State
0	0	$Q(t)$	Hold
0	1	1	Set
1	0	0	Reset
1	1	$Q(t)$	Hold


we get the following excitation table.

$Q(t)$	$Q(t+1)$	A	B	D
0	0	0	0	0
0	1	0	1	1
1	0	1	0	0
1	1	0	1	1

We know that the characteristic table for D-flip flop is

D	$Q(t+1)$
0	0
1	1

 ∴ If we choose $A = \bar{D}$ & $B = D$, we can implement D-flip flop using flipflop X.



when $D = 0$.

$A = 1, B = 0$

$\Rightarrow Q(t+1) = 0$

when $D = 1$

$A = 0, B = 1$

$\Rightarrow Q(t+1) = 1$