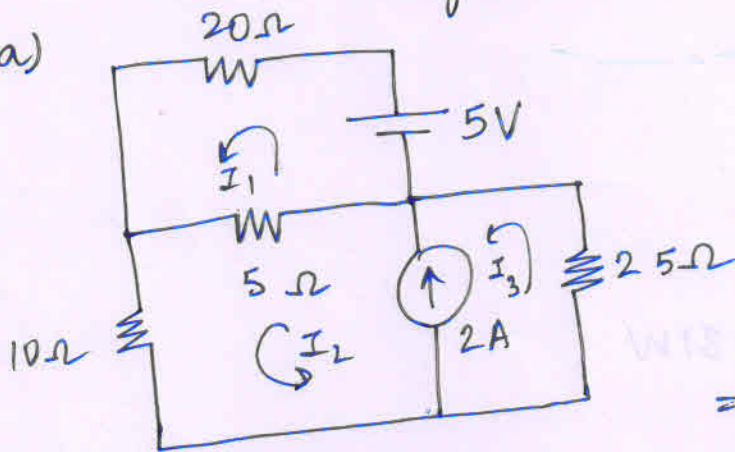


Assignment 2 SolutionsAns 1. (a)

$$20I_1 + 10I_2 + 25I_3 = 5$$

$$I_2 - I_3 = 2$$

$$\therefore 20I_1 + 10I_2 + 25I_2 = 55$$

$$\Rightarrow 20I_1 + 35I_2 = 55$$

$$\Rightarrow 4I_1 + 7I_2 = 11 \quad \text{--- (1)}$$

$$20I_1 + 5(I_1 - I_2) = 5$$

$$\Rightarrow 25I_1 - \frac{5}{7}(11 - 4I_1) = 5$$


$$\Rightarrow 25I_1 - \frac{55}{7} + \frac{20}{7}I_1 = 5$$

$$\Rightarrow I_1 = \frac{\left(5 + \frac{55}{7}\right)}{\left(25 + \frac{20}{7}\right)} = 0.46 \text{ A}$$

$$\therefore P_{5V} = -0.46 \times 5 \text{ W} = -2.31 \text{ W}$$

shows that power is supplied by the source.

(b)

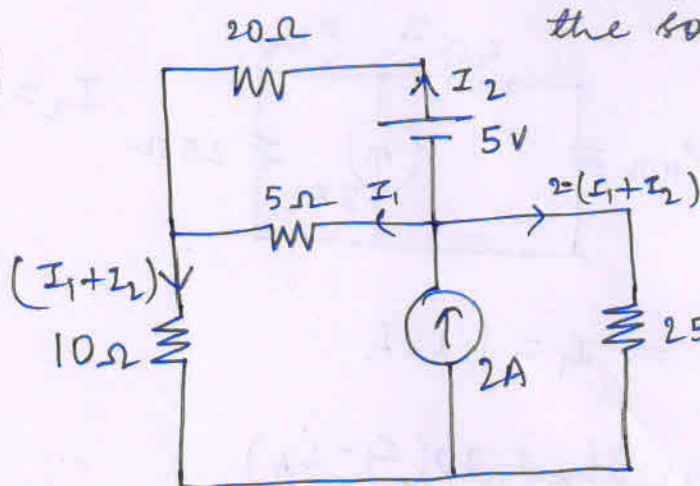

$$[10(I_1 + I_2) + 20I_2] -$$

$$[25(2 - I_1 - I_2)] = 5$$

$$\Rightarrow 10I_1 + 30I_2 - 50 + 25I_1 + 25I_2 = 5$$

$$\Rightarrow 11I_2 + 7I_1 = 11 \quad \text{--- (1)}$$

$$10(I_1 + I_2) + 5I_1 = (2 - I_1 - I_2)25$$

$$\Rightarrow 15I_1 + 10I_2 = 50 - 25I_1 - 25I_2$$

$$\Rightarrow 40I_1 + 35I_2 = 50$$

$$\Rightarrow 8I_1 + 7I_2 = 10 \quad \text{--- (2)}$$


From (1) and (2),

$$11I_2 + \frac{7}{8}(10 - 7I_2) = 11$$



$$\Rightarrow \left(11 - \frac{49}{8}\right) I_2 = 11 - \frac{70}{8}$$

$$\Rightarrow I_2 = 0.46 \text{ A}$$
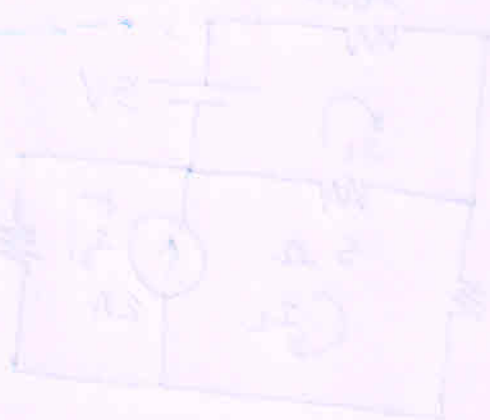
$$\therefore P_{5V} = -0.46 \times 5 \text{ W} = -2.31 \text{ W}$$





(c) Open circuit current source:

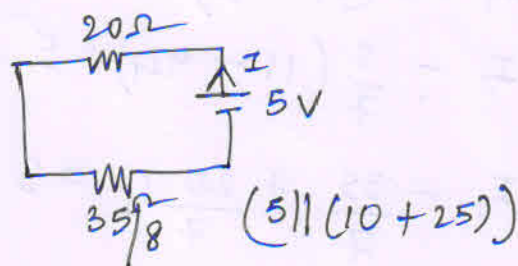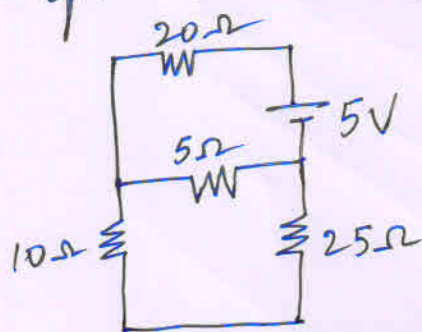


$$\therefore I = \frac{5}{20 + \frac{35}{8}} \text{ A} = 0.2 \text{ A}$$

Short circuit voltage source:

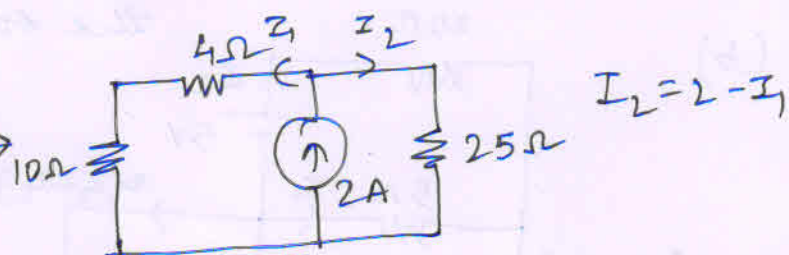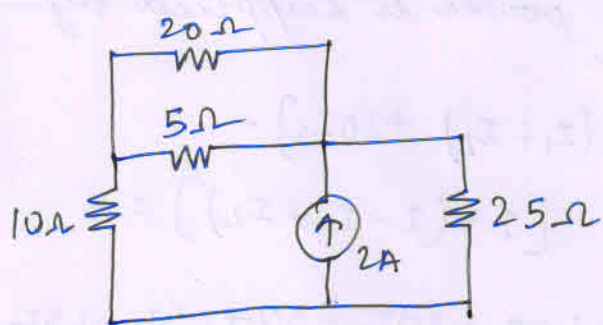
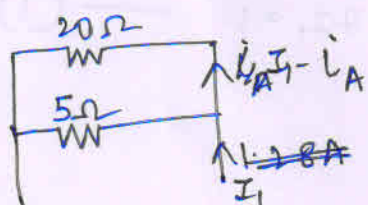
$$25(2 - I_1) = I_1(10 + 4) \Rightarrow I_1 = 1.28 \text{ A}$$



$$5(1.28) - 5i_A = 20(I_1 - i_A)$$

$$\Rightarrow i_A(5 + 20) = 20I_1$$


$$\Rightarrow i_A = \frac{4}{5} I_1$$

$$\Rightarrow I_1 - i_A = \frac{I_1}{5} = 0.26 \text{ A}$$


$$\therefore I = 0.2A + 0.26A = 0.46A$$

$$P_{5V} = -0.46A \times 5V = -2.31W$$

(d)

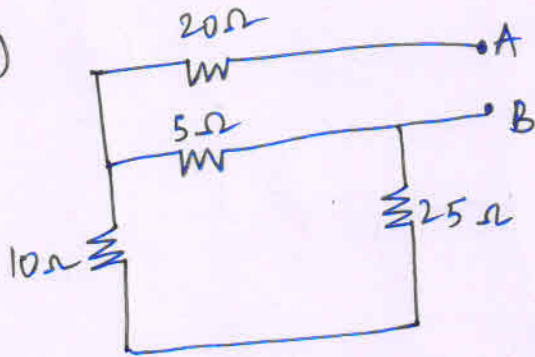

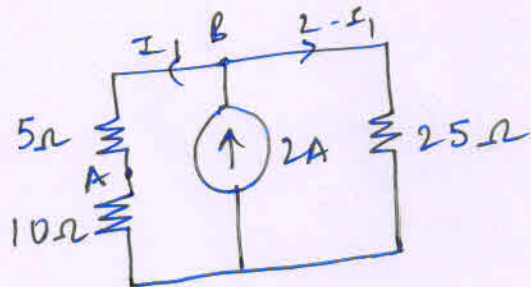
$$\rightarrow R_{TH} = 20 + (5 \parallel (10 + 25)) = \frac{195}{8} \Omega$$



$$I_1 = \frac{2 \times 25}{25 + 10 + 5} A = 1.25 A$$
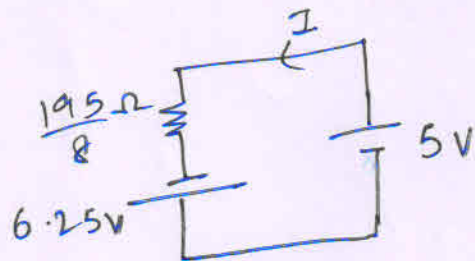
$$\therefore V_{AB} = -5I_1 = -6.25V = V_{TH}$$




$$(6.25 + 5) = I \left(\frac{195}{8} \right)$$

$$\Rightarrow I = 0.46A$$

$$\therefore P_{5V} = -0.46 \times 5W = -2.31W$$

Ans 2:

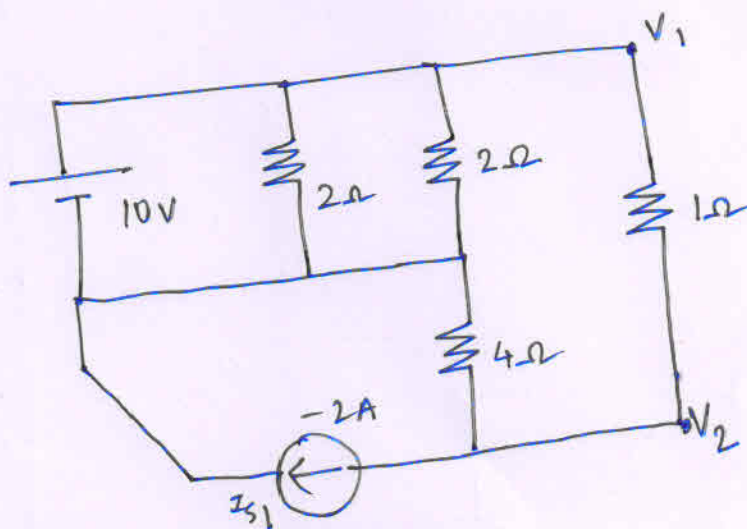

$$V_1 = V_{S1} = 10V$$

Apply KCL at node 2:


$$I_{S1} + \frac{V_2}{4} + \frac{V_2 - V_1}{1} = 0$$

$$\Rightarrow V_2 = 9.6V$$


$$\therefore P_{I_{S1}} = -2 \times 9.6W$$

$$= -19.2W$$

Ans 3.

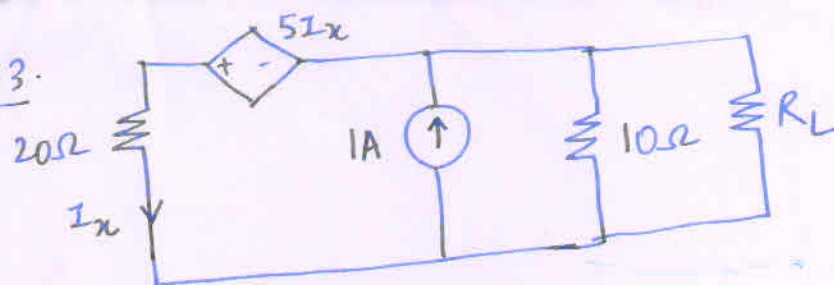

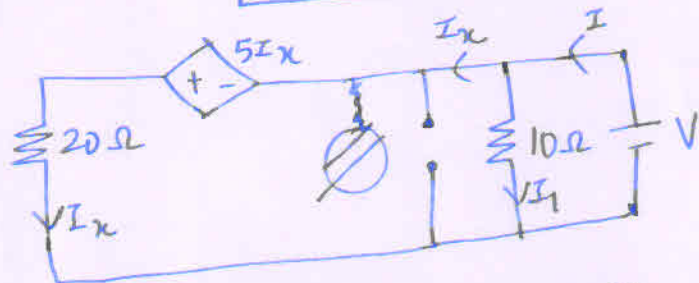
for maximum power transfer, $R_L = R_{TH}$.



$$\begin{aligned} V + 5I_x &= I_x \cdot 10 \\ \Rightarrow V &= 15I_x \quad \text{--- (1)} \end{aligned}$$


$$\frac{V}{10} = I_1 \Rightarrow I = I_1 + I_x = \frac{V}{10} + \frac{V}{15} = \frac{V}{6}$$
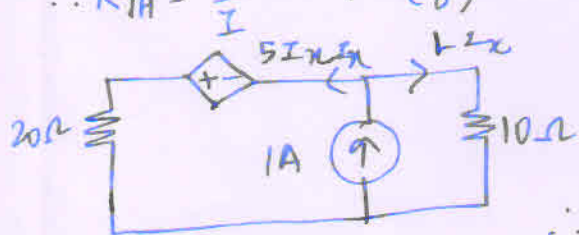
$$\therefore R_{TH} = \frac{V}{I} = V / V\left(\frac{1}{6}\right) = 6\Omega$$




$$\begin{aligned} \text{KVL: } 10(1 - I_x) + 5I_x &= 20I_x \\ \Rightarrow I_x &= \frac{2}{5} \text{ A} \end{aligned}$$
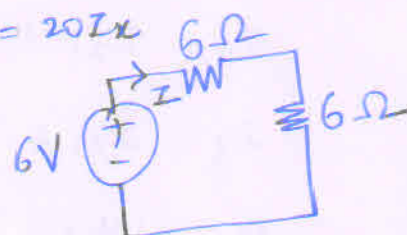
$$\therefore V_{OC} = \left(1 - \frac{2}{5}\right) \times 10 = 6V$$



$$I = \frac{6V}{12\Omega} = 0.5A \quad \therefore P_{max} = (0.5)^2 \times 6W = 1.5W$$

Ans 4. (i) Contribution of -2V source:

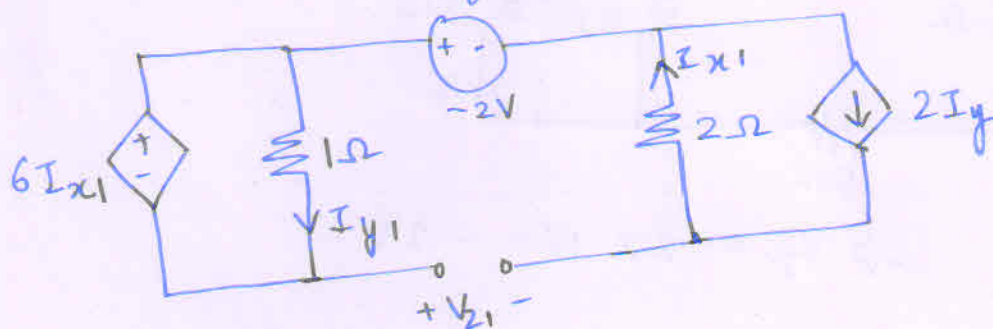

$$6I_{x1} = 1 \times I_{y1} \quad \text{--- (1)}$$


$$2I_{y1} = I_{x1} \quad \text{--- (2)}$$

$$\Rightarrow I_{x1} = I_{y1} = 0$$

$$\text{Also, } -V_{z1} - 1 \times I_{y1} + (-2V) - 2 \times I_{x1} = 0$$

$$\therefore V_{z1} = -2V$$

(ii) Contribution of 11A source:

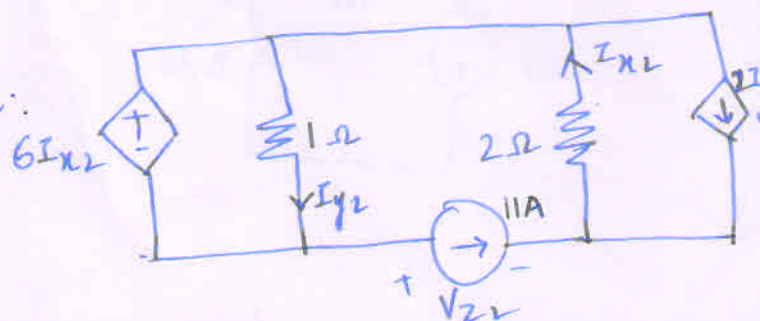

$$V_{12} = 6I_{x2}$$

$$V_{12} = 1 \times I_{y2}$$

$$\Rightarrow 6I_{x2} = I_{y2}$$

$$11 = I_{x2} - 2I_{y2}$$

$$\therefore I_{x2} = -1A, I_{y2} = -6A$$

$$\text{also, } 2I_{x2} + I_{y2} + V_{22} = 0$$


$$\Rightarrow V_{22} = 8V$$

$$\therefore I_x = I_{x1} + I_{x2} = -1A$$

$$I_y = I_{y1} + I_{y2} = -6A$$


$$V_2 = V_{21} + V_{22} = 6V$$

Ans 5.

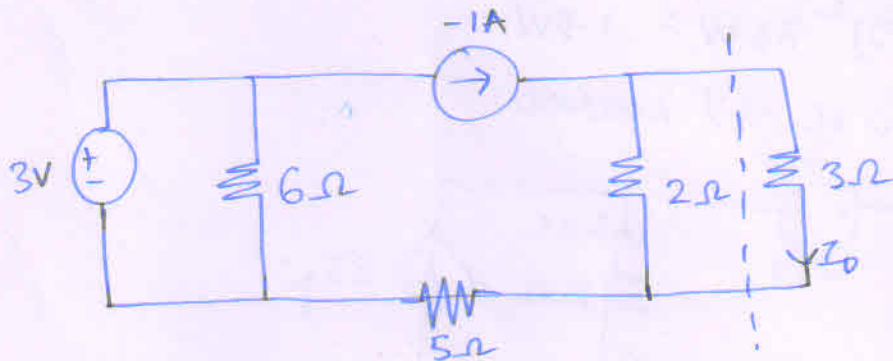


$$I_{2\Omega} = -1A \Rightarrow V_{TH} = 2 \times -1V = -2V$$

R_{TH} :

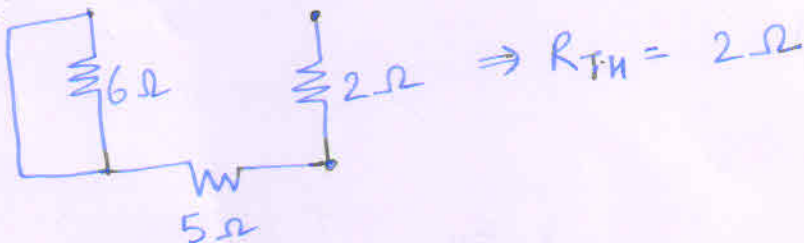


$$\Rightarrow R_{TH} = 2\Omega$$

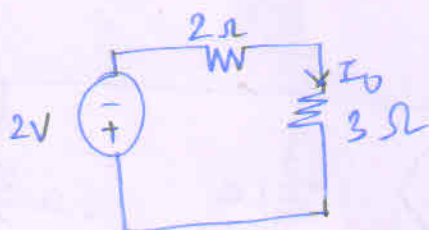

$$\therefore I_0 = \frac{-2}{2+3} A = -\frac{2}{5} A$$


Ans 6. (a) X is an inductor :

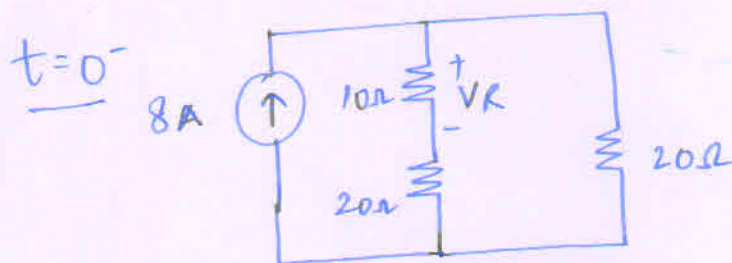When current has been flowing for a long time, it behaves like a short circuit.




$$\therefore I_{10\Omega} = \frac{20 \times 8}{50} \text{ A} = \frac{16}{5} \text{ A}$$
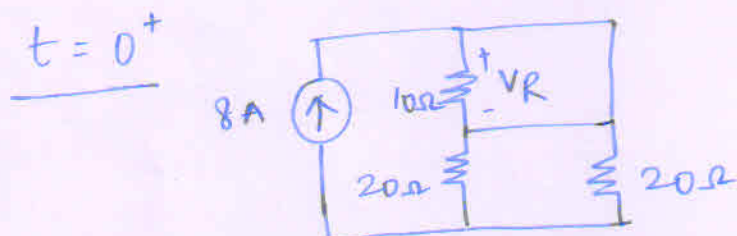
$$\therefore V_R = \frac{16}{5} \times 10 \text{ V} = 32 \text{ V}$$




The current through the inductor doesn't change instantaneously even after the switch is closed. Therefore, at $t = 0^+$, current through 10Ω is 3.2 A and $V_R|_{t=0^+} = 32 \text{ V}$

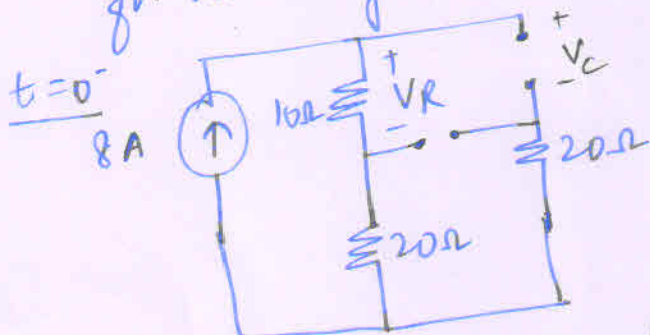(b) X is a capacitor: When current has been flowing for a long time, it behaves like an open circuit.



$$\therefore V_R = 10 \times 8 \text{ V} = 80 \text{ V}$$

$$\Rightarrow V_C = 240 \text{ V}$$

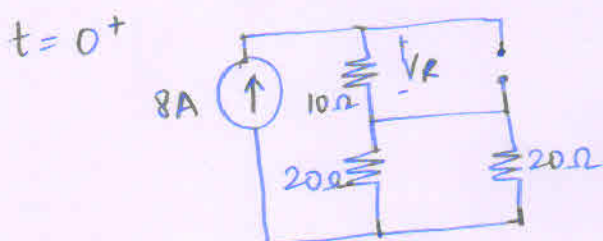

The voltage across the capacitor doesn't change instantaneously after the switch is closed. $V_C|_{t=0^+} = V_C|_{t=0^-} = V_R|_{t=0^-} = 80 \text{ V}$

$$V_R|_{t=0^+} = 80 \text{ V}$$