

# ESc201 : Introduction to Electronics


## Amplifiers

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur

# RECAP

Input resistance  $R_i = V_i / I_i$


(Ideally large)

 

Trans conductance

$$g_m = \left. \frac{I_o}{V_i} \right|_{V_o=0}$$


(Ideally large)

 

Output conductance:  $g_o = 1 / r_o = \left. \frac{I_o}{V_o} \right|_{V_i=0}$

(Ideally small)

# RECAP

 

$$A_V = \frac{V_o}{V_s} = -g_m r_o \times \frac{R_L}{r_o + R_L} \times \frac{R_i}{R_i + R_S}$$





In the ideal case  $r_o$  is infinite

$$A_V = \frac{V_o}{V_s} = -g_m R_L \times \frac{R_i}{R_i + R_S}$$

We would ideally like input resistance  $R_i$  to be infinite as well !



$$A_V = -g_m R_L$$

# RECAP

    



**Ideal Transistor Characteristics**

**Ideal transistor**

 
 


**RECAP**

**Device X**

  


**Device Y**

 
 


How do we use elements such as X, Y etc to make amplifiers?

 When only a part of device characteristics is suitable for amplification, then we need to push the device into that region by applying suitable bias voltages. This process is called **BIASING**






**RECAP**

 
 


How do we get rid of unwanted dc voltage at the output ?

**RECAP**

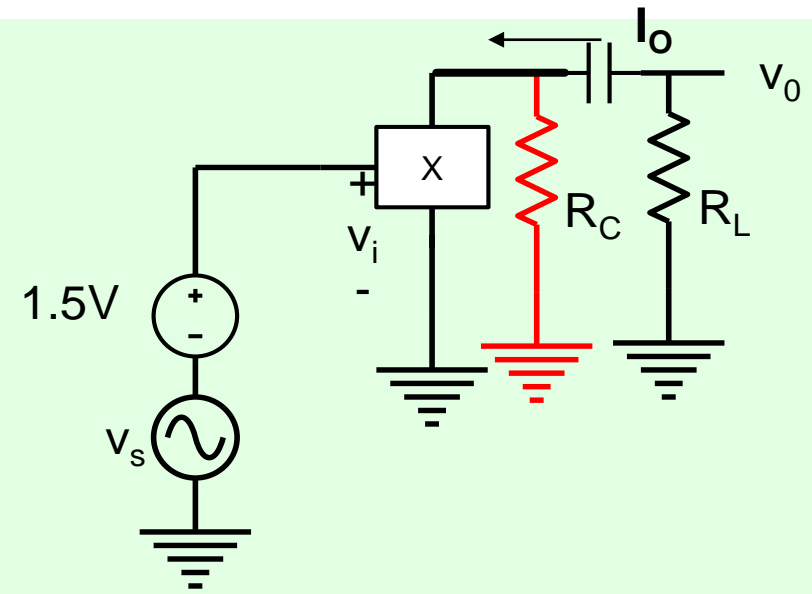 
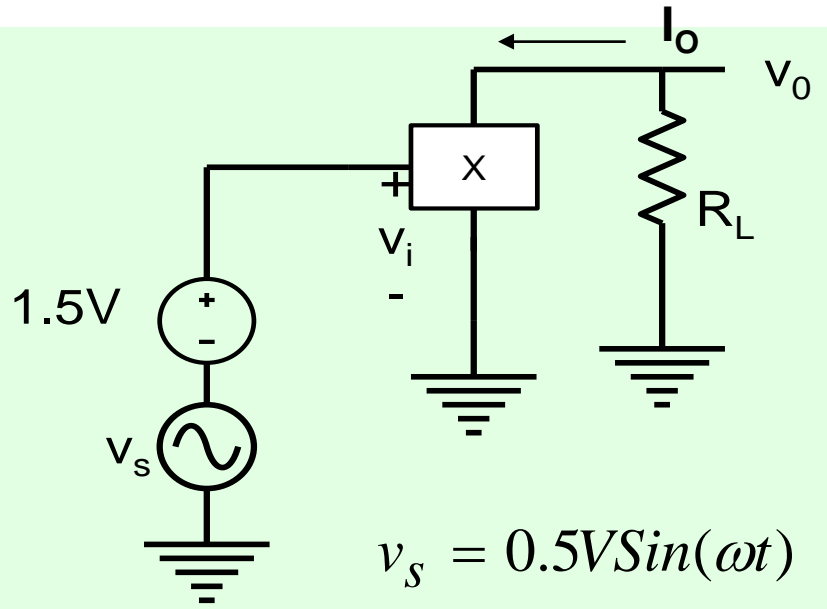


# RECAP

  

dc




ac (signal)

  



Capacitor is chosen large enough so that at the signal frequency  $1/j\omega C \sim 0$ .



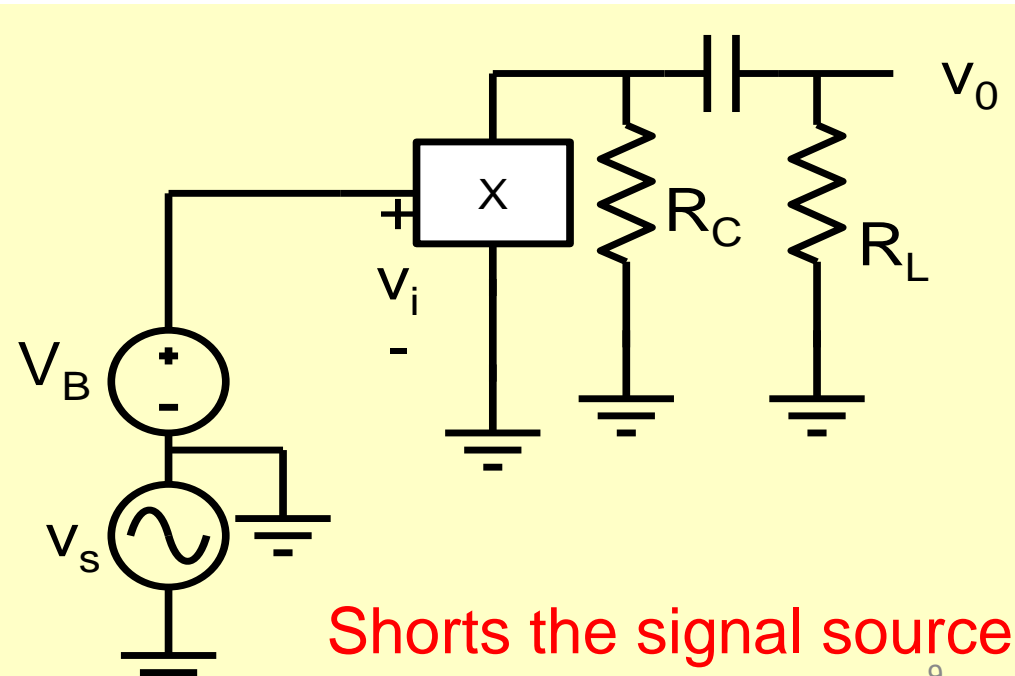 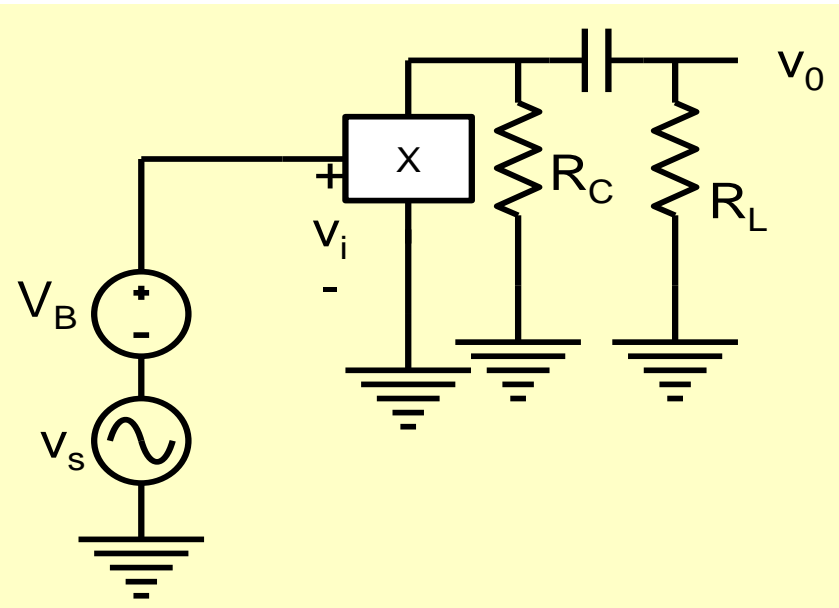
What happens if both dc voltage source and signal source have one terminal as ground?





Shorts the signal source

 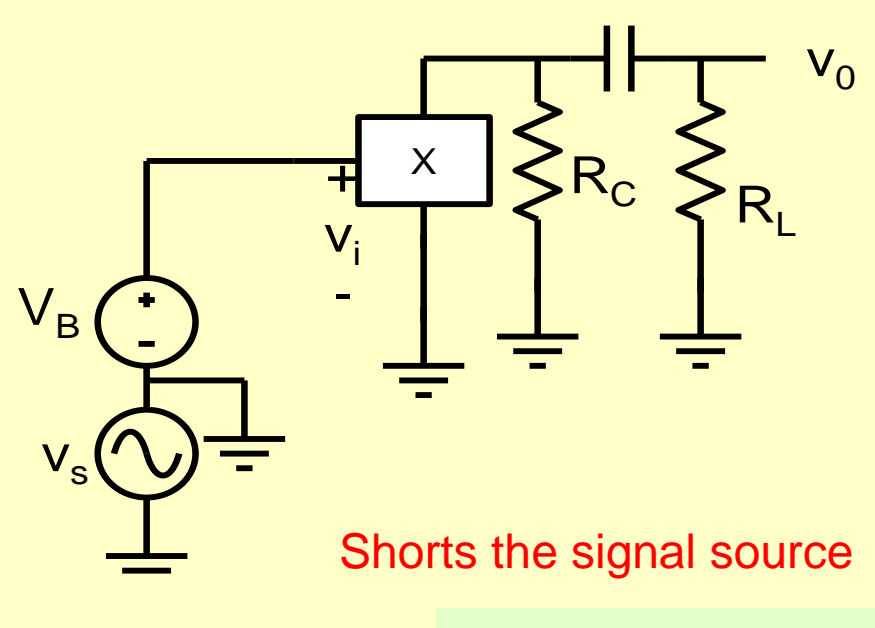



## Solution

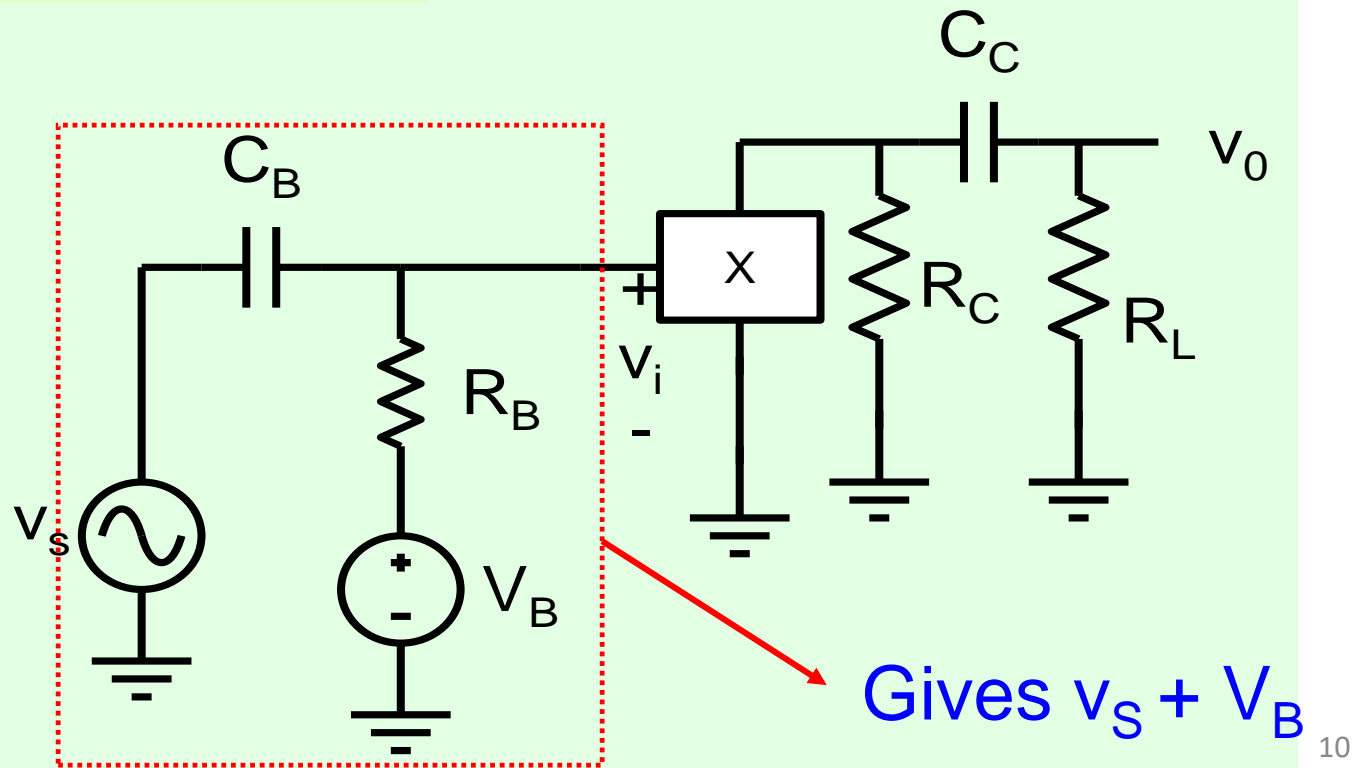

  

$$v_i = V_B$$

  Capacitor is chosen large enough so that at the signal frequency  $1/j\omega C \sim 0$ .







$$v_i = v_s$$



$$v_i(\text{total}) = v_s + V_B$$

Note the role of  $R_B$



# Amplifier Schematic using Device X

    



**Ideal transistor**

  

**Device X**


 
 


**Device Y**

  

How do we use element Y to make amplifiers?

# Device Y

   



$$I_o = 0 \quad \text{for } V_o < V_{\text{sat}}$$

$$I_o = 0 \quad \text{for } V_i \leq V_\alpha$$


$$= g_m \times (V_i - V_\alpha) \quad \text{for } V_i > V_\alpha$$

$$\text{for } V_o > V_{\text{sat}}$$

## Ideal Characteristics

  

 
# How do we use device Y to make an amplifier?





for  $V_O < V_{sat} : I_o = 0$   
for  $V_O \geq V_{sat} :$   
 $I_o = 0$  for  $V_i \leq V_\alpha$   
 $= g_m \times (V_i - V_\alpha)$  for  $V_i > V_\alpha$


## Will the earlier solution work?

 

  The purpose of biasing network is to operate the device in a region which resembles ideal transistor





 $V_o = -ve$  which is not possible for device Y






# Earlier Solution in terms of load line

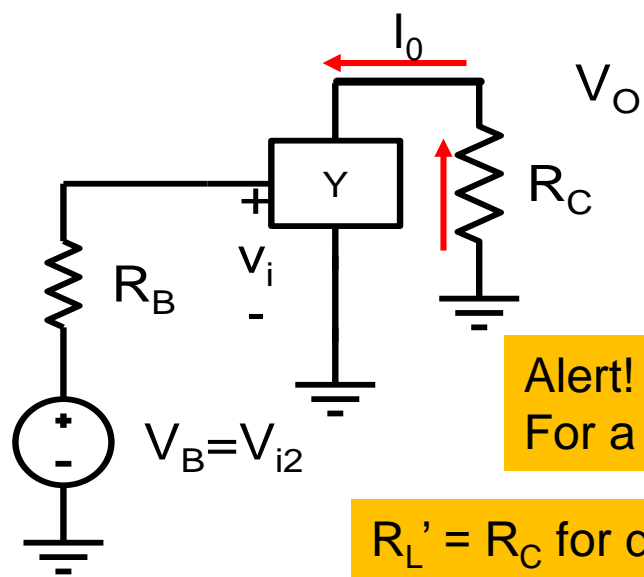 


Alert!  
For a positive  $I_o$ ,  $V_o = -ve$

$R_L' = R_C$  for dc and  $R_C || R_L$  for ac

 
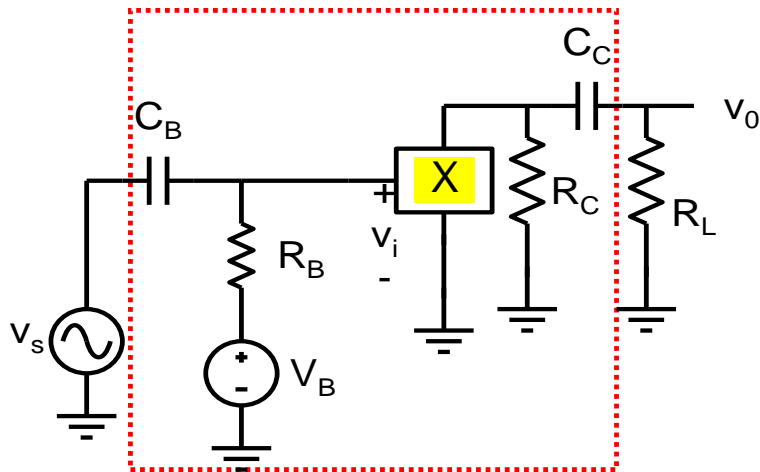
# Why is circuit working for Device X and not for Device Y?


**Device X** discussed in earlier lectures




Valid solution  
**possible**



**Output Characteristics**

 

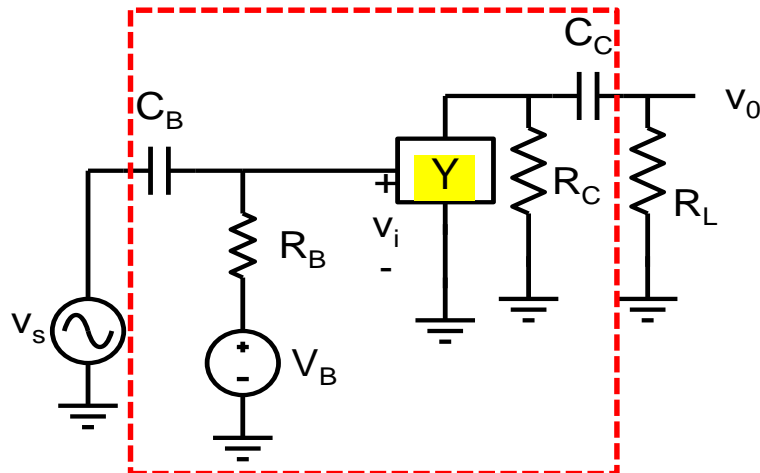
**Device Y** being discussed in current lecture




Valid solution  
**NOT possible**




$R_L' = R_C$  for dc and  $R_C || R_L$  for ac

 


# Solution to get meaningful Q point

 

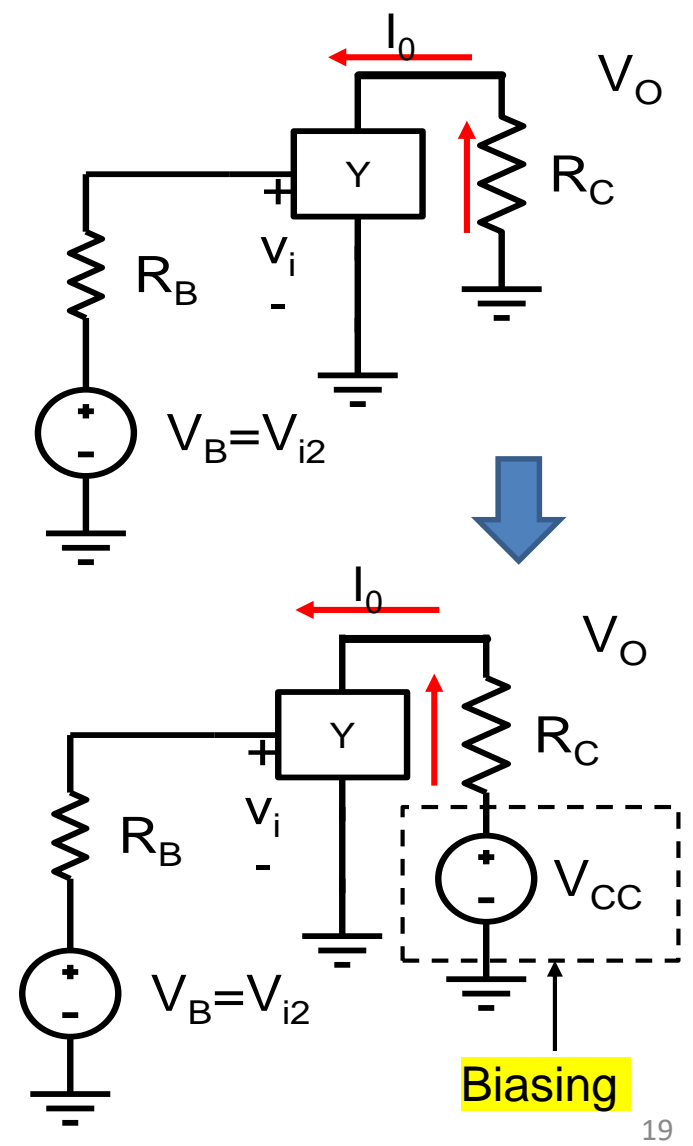
The purpose of biasing network is to operate the device in a region which resembles ideal transistor


 
# Revised Amplifier Schematic for Device Y




 Usually  $V_{CC}$  is fixed  
 $I_o$  and  $R_C$  are varied





Output biasing is included

# Better representation of biasing

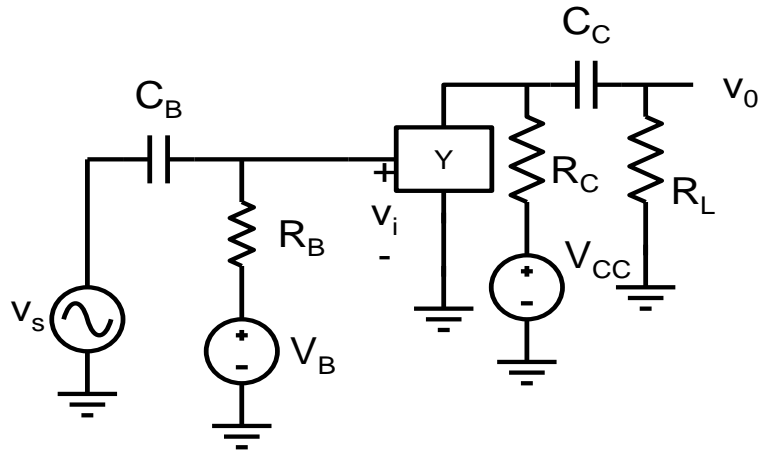


A more common representation

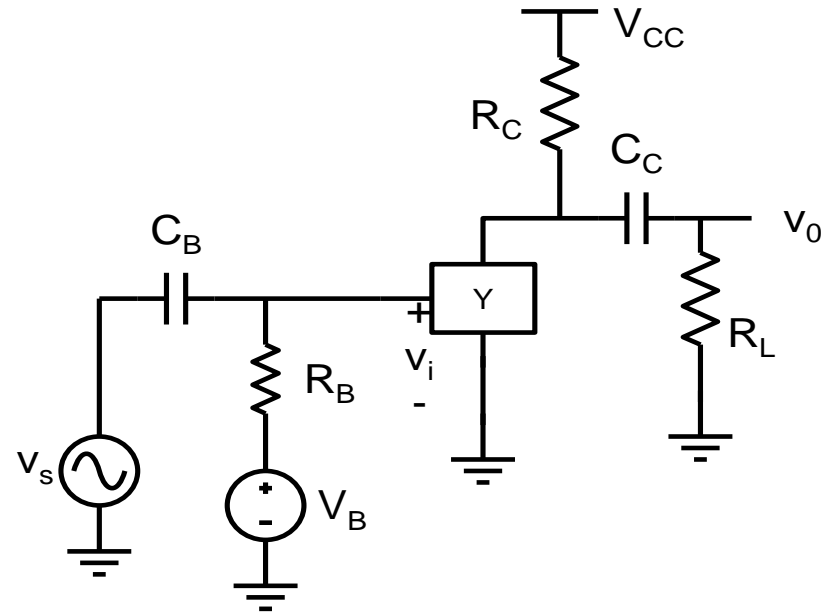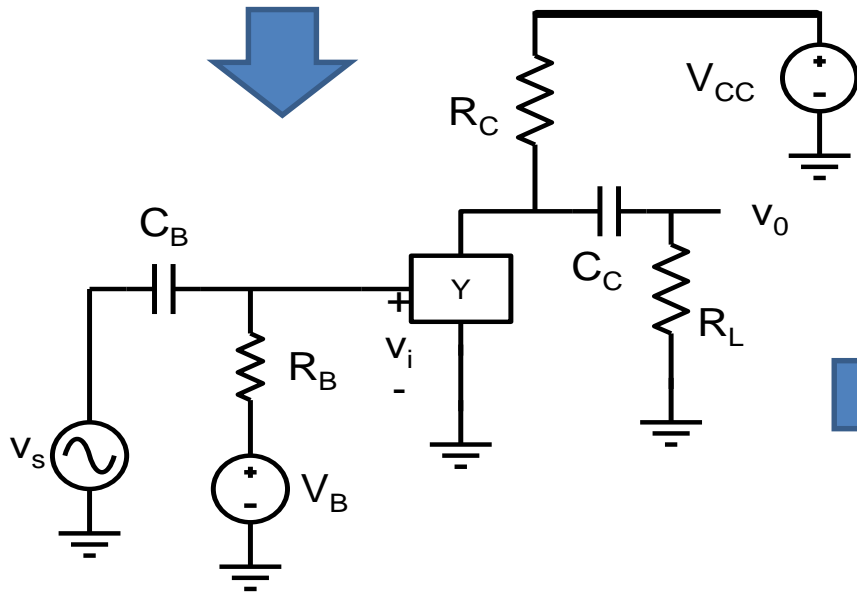
 
# Economising on power supplies

Can we implement an amplifying circuit using one dc voltage source only?




$$V_B = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

$$\text{and } R_B = R_1 || R_2$$

A single supply  $V_{CC}$  can be used to provide bias to both input and output

# High response device

## Device Z

 

For  $V_o < 0.2 \text{ V} \Rightarrow I_o = 0$       Output characteristics


For  $V_o \geq 0.2 \text{ V}$

$I_o = 0$  for  $V_i \leq 1 \text{ V}$


$I_o = 10^3 \cdot (V_i - 1 \text{ V}) \text{ mA}$  for  $V_i > 1 \text{ V}$

Transfer characteristics

Transfer characteristics

 

Output characteristics

 


- The voltage gain circuit we designed will be **very sensitive** to:
  - variations in resistor values, power supply, device parameters such as  $V_\alpha$ , etc.

# Highly sensitive to resistor value

Assume  $V_o \geq 0.2 \text{ V}$  by choosing proper bias

$I_o = 0$  for  $V_i \leq 1 \text{ V}$

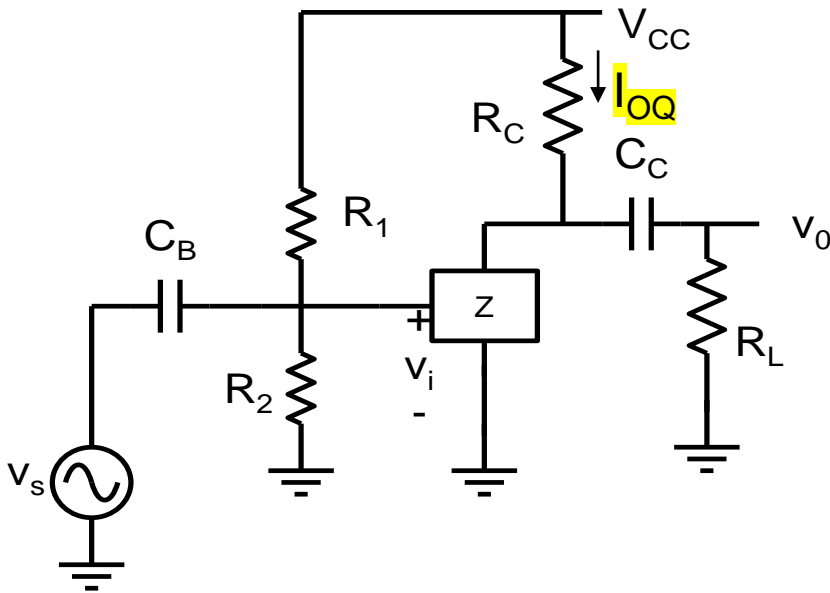$I_o = 10^3 \cdot (V_i - 1 \text{ V}) \text{ mA}$  for  $V_i > 1 \text{ V}$



Target Quiescent Current:

$V_{CC} = 5 \text{ V}; R_2 = 1 \text{ k}\Omega; R_1 = 3.95 \text{ k}\Omega$

$\Rightarrow V_i = 1.01 \text{ V} \Rightarrow I_{OQ} = 10 \text{ mA}$

What if  $R_2$  varies?

$V_{CC} = 5 \text{ V}; R_2 = 0.99 \text{ k}\Omega; R_1 = 3.95 \text{ k}\Omega$

$\Rightarrow V_i = 1.002 \text{ V} \Rightarrow I_{OQ} = 1.9 \text{ mA}$

$V_{CC} = 5 \text{ V}; R_2 = 0.98 \text{ k}\Omega; R_1 = 3.95 \text{ k}\Omega$


$\Rightarrow V_i = 0.994 \text{ V} \Rightarrow I_{OQ} = 0 \text{ mA}$

A 2% drop in  $R_2$  value causes the circuit to become non-operational!




# A solution


Original Circuit

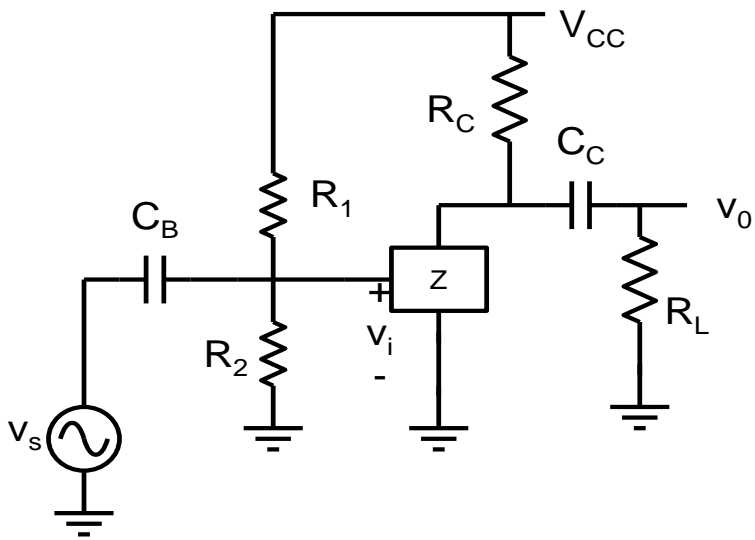


Modified Circuit

 

# DC analysis of modified circuit

 




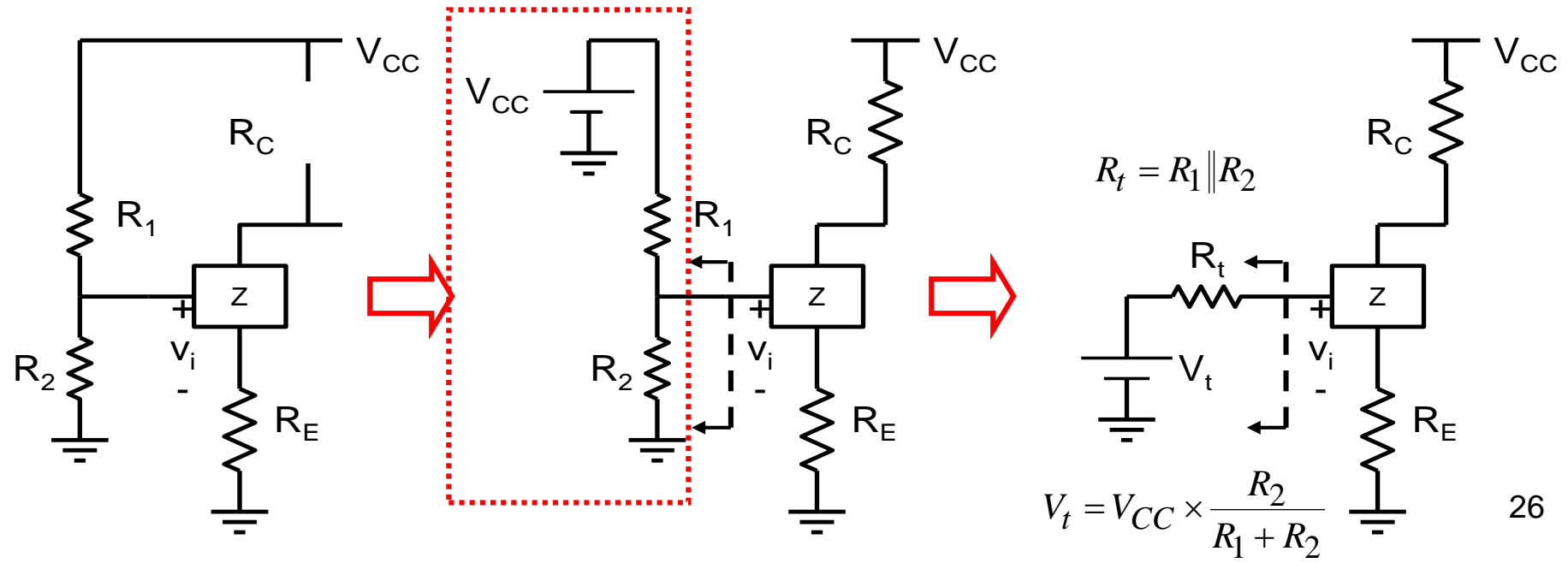
Represent the input bias as:  
Thévenin equivalent as seen from input



$$R_t = R_1 \parallel R_2$$

$$V_t = V_{CC} \times \frac{R_2}{R_1 + R_2}$$

# DC analysis of modified circuit

    

$$-V_t + 0 \times R_t + V_i + I_O R_E = 0$$

Since  $I_0$  vs.  $V_i$  characteristics is very sharp,  $V_i \sim V_\alpha = 1V$

$$I_O \cong \frac{V_t - V_\alpha}{R_E}$$

If  $V_t$  changes by 1% due to variation in resistor values then the change in output current is proportional.

Circuit much less sensitive to variations in circuit parameters