

# ESC201A Quiz1 Set B

SAMYAK SINGHANIA

TOTAL POINTS

**12 / 12**

QUESTION 1

**+ 1 pts** A simplified value of  $z_x$  is required.

1 Q1 8 / 8

✓ **+ 8 pts** Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not attempted

+ 0 pts Copied

+ 0.5 pts  $v(t)$  formula correct

+ 0.5 pts  $v(0+)$  calculation correct

+ 2.5 pts  $v_{\infty}$  calculation correct

+ 2 pts Req calculated correctly

+ 1 pts  $v(t)$  calculated correctly

+ 1.5 pts Energy Calculated Correctly

- 1 pts for minor mistakes

1 Great work!

QUESTION 2

2 Q2 4 / 4

✓ **+ 4 pts** Completely Correct

+ 0 pts Completely Incorrect

+ 0 pts Not Attempted

+ 0 pts Copied

+ 1.5 pts  $i_x$  calculated correctly

+ 1.5 pts  $Z_x$  calculated correctly

+ 1 pts Element Value Calculated Correctly


+ 0.5 pts Inductor Unit not written

+ 0.5 pts The element is not capacitor

+ 1 pts Simplified value of  $i_x$  is required.

Name: SAMYAK SINGHANIARoll. No. 210917Section: W3 C3

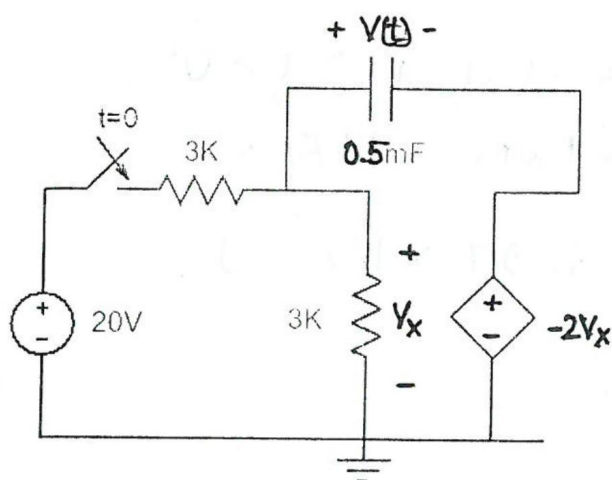Q.1 Assuming that the capacitor does not have any initial charge, determine the voltage across the capacitor  $V(t)$  as a function of time after the switch is closed at  $t = 0$ . Also find the energy stored in the capacitor at  $t = 1$  s. [8 Marks]




Solving the circuit by Thévenin across the capacitor.

$$V_{Th} = V_x - (-2V_x) = 3V_x$$

$$20 = 3K i_1 + 3K i_1$$

$$i_1 = \frac{20}{6000} A \Rightarrow V_x = \frac{3000}{6000} \times 20 = 10V$$
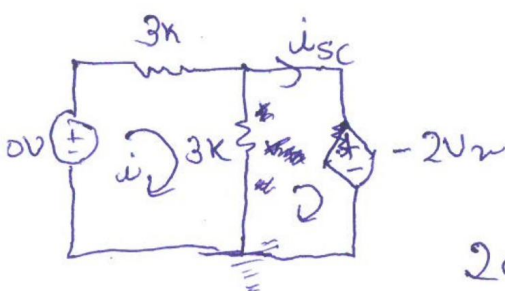
$$\Rightarrow V_{Th} = 3 \times 10 = 30V$$



To find  $i_{sc}$ , we use mesh analysis.

Let current  $i$  be flowing in mesh 1 &  $i_{sc}$  be flowing in mesh 2.

$$20 = 3K i + 3K i - 3K i_{sc} \quad \text{--- (1)}$$

$$-2V_x + 3K i_{sc} - 3K i = 0$$

$$\text{Also } V_x = 3K(i - i_{sc})$$

$$\Rightarrow 3K i_{sc} - 3K i = 6K i - 6K i_{sc}$$


$$\Rightarrow 9K i_{sc} = 9K i \Rightarrow i_{sc} = i$$

Putting this in eq (1), we get

$$20 = 3K i_{sc} + 3K i_{sc} - 3K i_{sc} \Rightarrow i_{sc} = \frac{20}{3000} A$$

$$\therefore R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{30}{\frac{20}{3000}} \Omega = 4500 \Omega = 4.5k\Omega$$

Thévenin

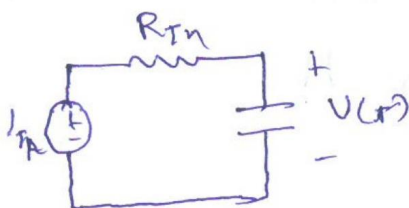

$\therefore$  Capacitor do not have any initial charge

$$\underline{V(0^-) = V(0^+) = V(0) = 0V}$$

$$V(\infty) = V_{Th} = 30V$$

$$\tau = R_{Th} C = 4500 \times \frac{1}{2} \times 10^{-3} = 2.25$$

$$\therefore V(t) = V(\infty) + (V(0) - V(\infty)) e^{-\frac{t}{\tau}}$$

$$V(t) = 30 + (0 - 30) e^{-\frac{t}{2.25}} = 30 (1 - e^{-\frac{t}{2.25}})$$

$$\Rightarrow V(t) = 30 (1 - e^{-\frac{t}{2.25}}) \text{ Volts.}$$

$$\text{At } t=1, V(1) = 30 (1 - e^{-\frac{1}{2.25}}) = 10.76 \text{ Volts.}$$

$$\therefore \text{Energy stored in capacitor at } t=1 \Rightarrow \frac{1}{2} C V^2$$

$$= \frac{1}{2} \times \frac{1}{2} \times 10^{-3} \times 115.87$$

$$= \underline{28.97 \times 10^{-3} \text{ J}}$$

1

**Q.2** Determine the impedance of element X for the given currents and voltages in the circuit shown below. If  $\omega = 5000 \text{ rad/s}$ , find the element X value? [4 Marks]

Let current  $i$  be flowing in X

By nodal analysis,

$$6j = i + 2j + 4\sqrt{2} \left( \frac{1}{\sqrt{2}} + \frac{j}{\sqrt{2}} \right)$$

$$i = -4 \text{ A}$$

Let Z be the impedance

$$\Rightarrow Z = \frac{8 \angle -90}{-4}$$

$$= \frac{-8j}{-4} = 2j = 2 \angle 90 \Omega$$

$\Rightarrow$  The impedance is  $2j \Omega$ .

Clearly the potential across X is ahead of the current in phase by  $90^\circ \Rightarrow$  X is inductor.

$$\therefore Z = j\omega L = 2j$$

$$\Rightarrow L = \frac{2}{\omega} = \frac{2}{5000}$$

$$L = 0.4 \times 10^{-3} \text{ H}$$

2/2

$\Rightarrow$  element X value is  $0.4 \times 10^{-3} \text{ H}$ .

