

ESc201 : Introduction to Electronics

Amplifiers


Amit Verma
Dept. of Electrical Engineering
IIT Kanpur

Objective


1. Learn ideal Transistor characteristics required for Voltage Amplification
2. Learn to build amplifiers using elements which have non-ideal characteristics.


Voltage Amplification

$$V_o = G \times V_i$$
$$G > 1$$

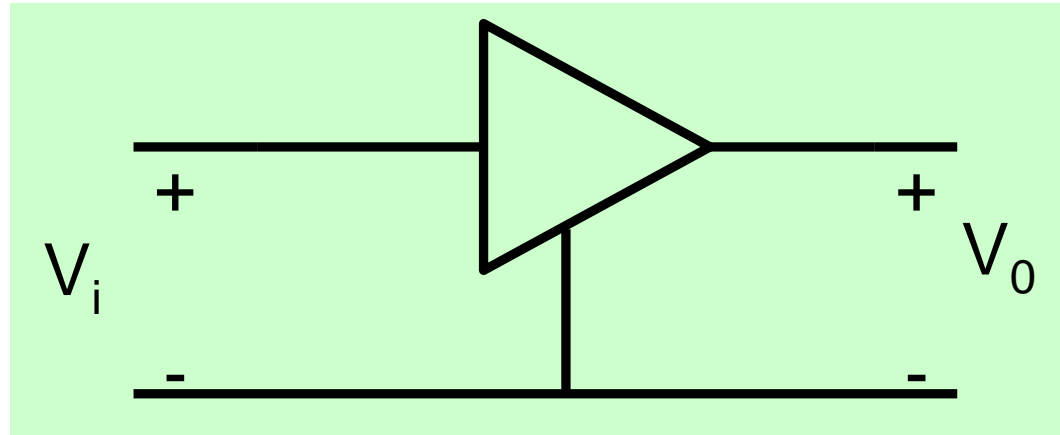

3-terminal unilateral linear device

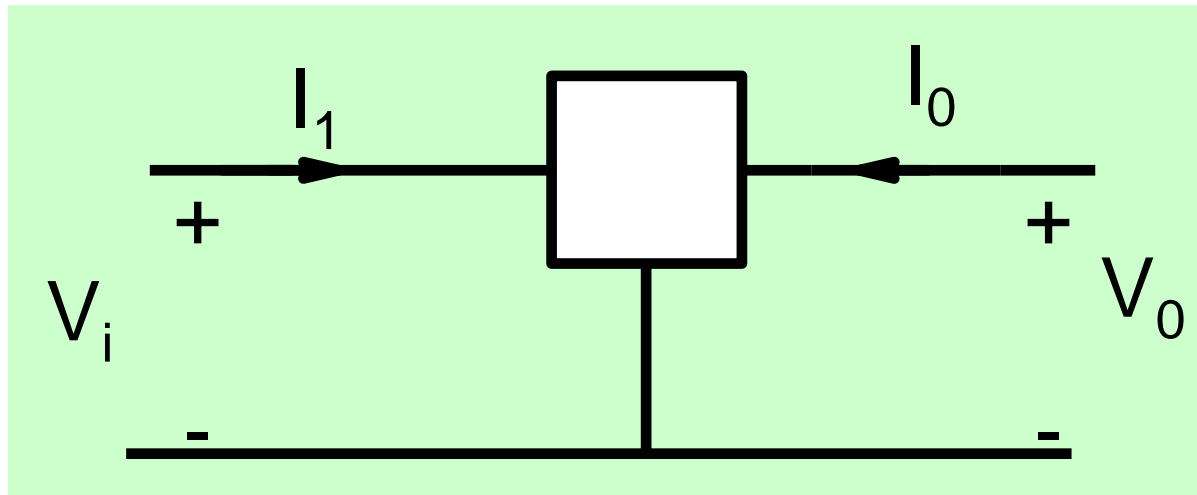

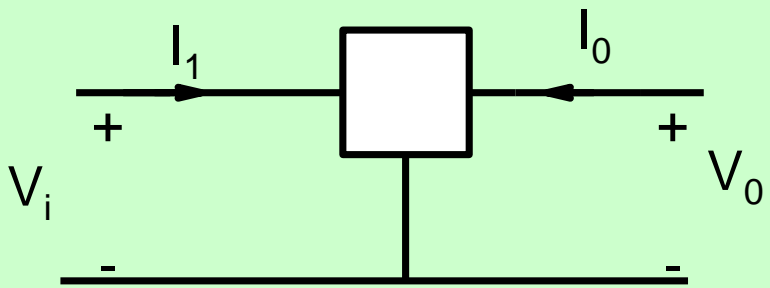


Input resistance $R_i = V_i / I_i$

(Ideally large)

Trans conductance

$$g_m = \left. \frac{I_o}{V_i} \right|_{V_o=0}$$




(Ideally large)

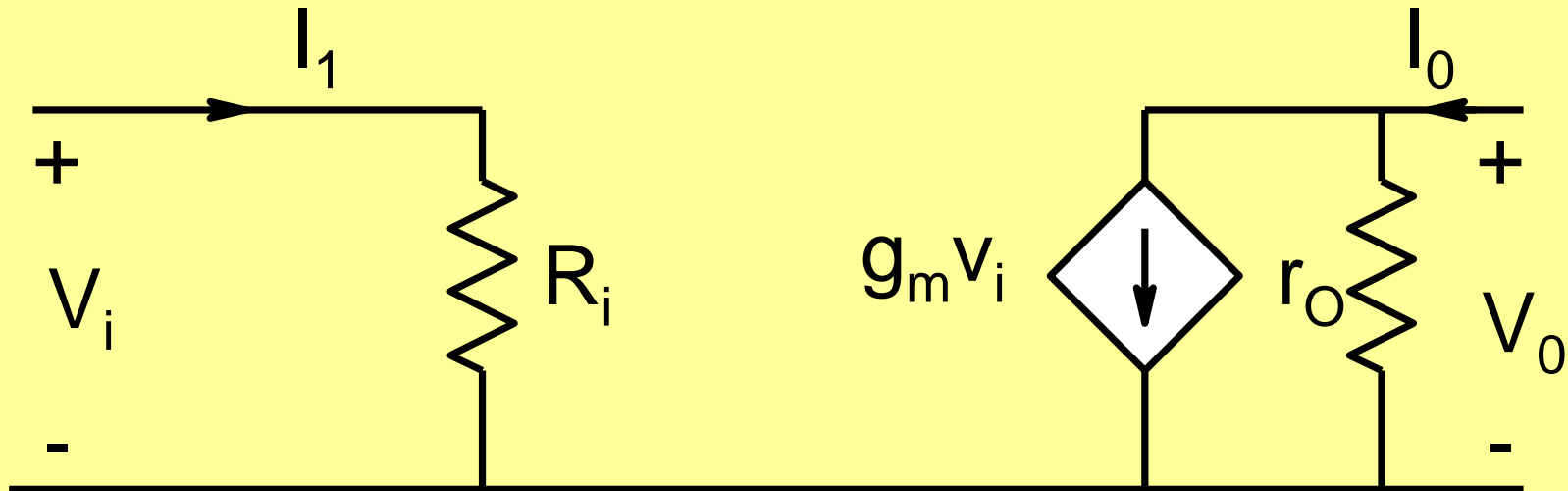


Output conductance: $g_o = 1 / r_o = \left. \frac{I_o}{V_o} \right|_{V_i=0}$

(Ideally small)

Voltage Amplifier

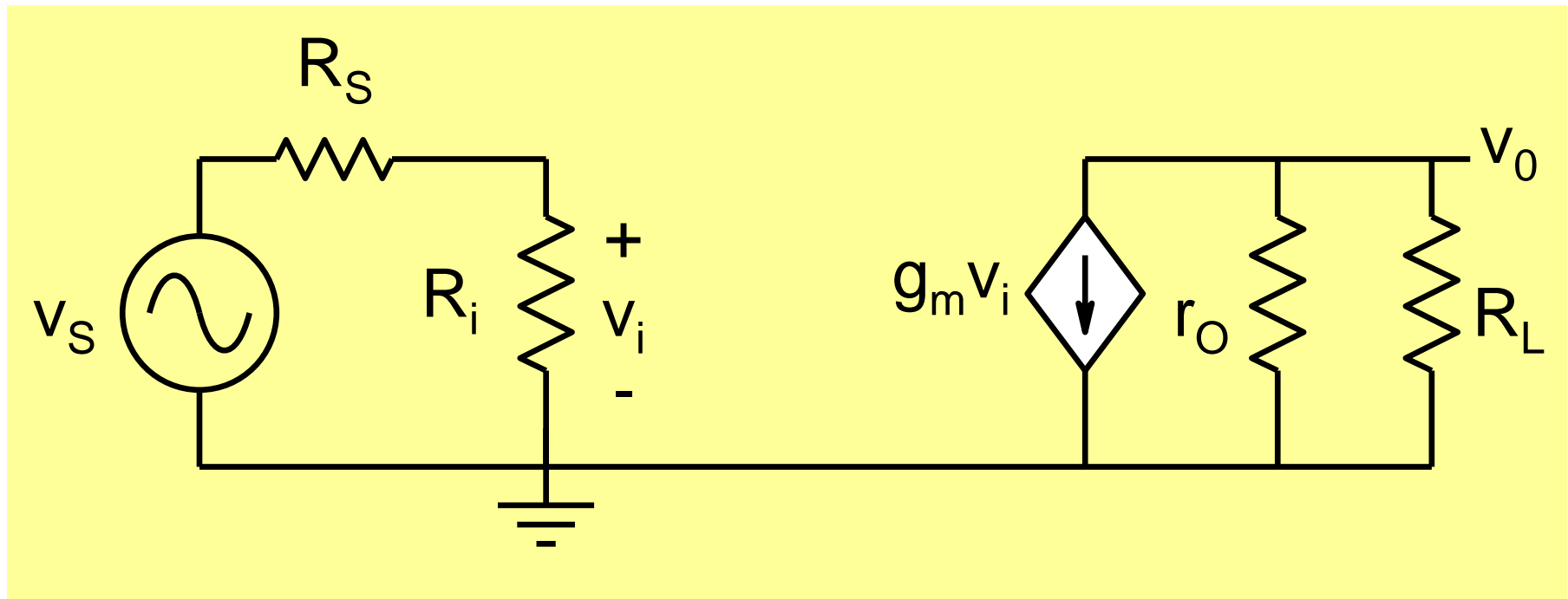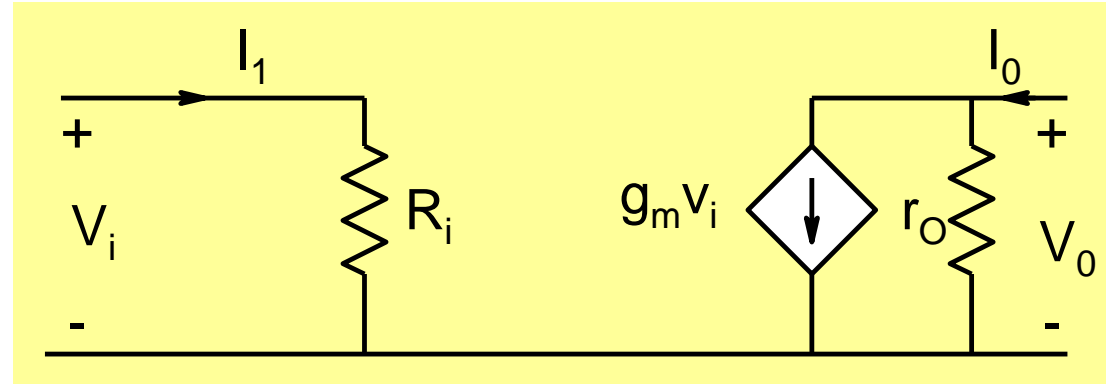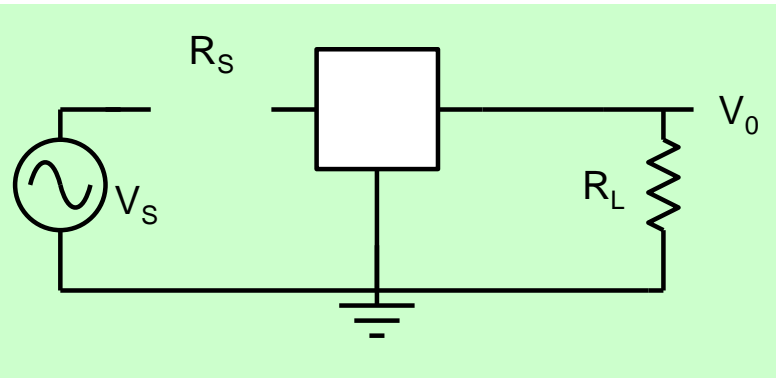

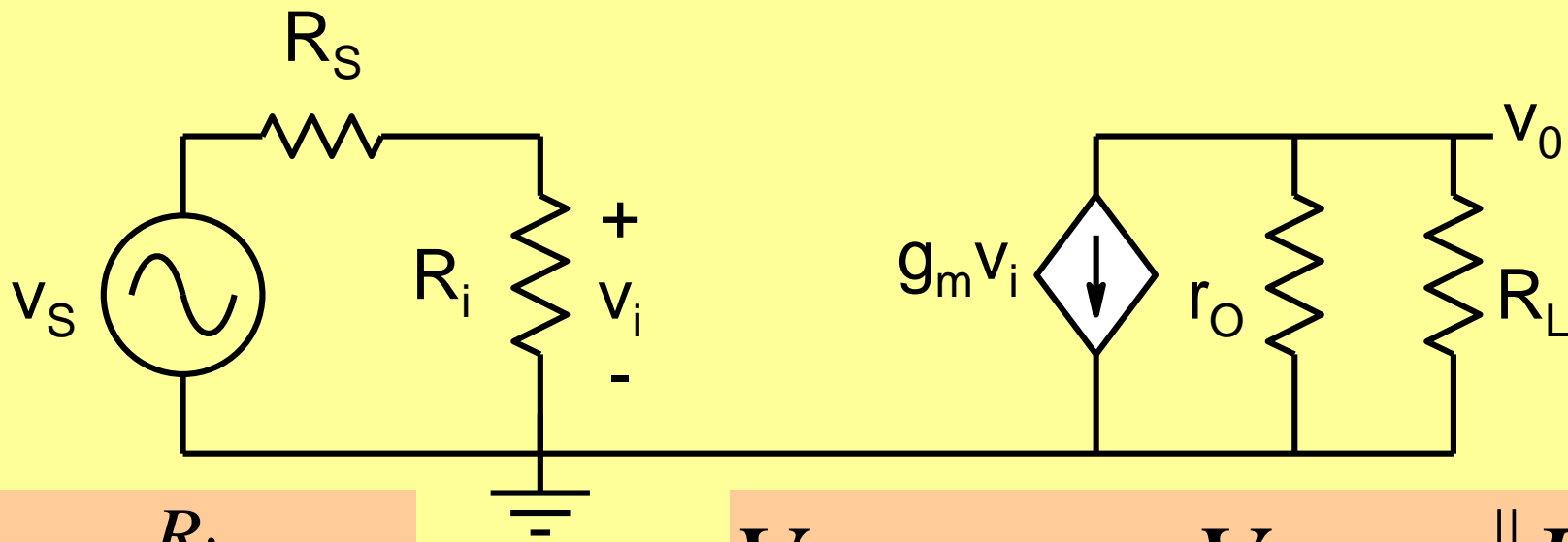

$$V_i = \frac{R_i}{R_i + R_S} V_S$$

$$V_o = -g_m V_i \times r_o \parallel R_L$$

$$A_V = \frac{V_o}{V_S} = -g_m r_o \times \frac{R_L}{r_o + R_L} \times \frac{R_i}{R_i + R_S}$$

$$|A_V| \leq g_m \times r_o$$

Necessary Condition for Voltage Amplification

$$g_m \times r_o > 1$$

Voltage Amplification



$$g_m r_o \gg 1$$

$$g_m \gg g_o$$

Trans-conductance \gg Output Conductance

$$g_m = \left. \frac{I_o}{V_i} \right|_{V_o=0}$$

$$g_o = \left. \frac{I_o}{V_o} \right|_{V_i=0}$$

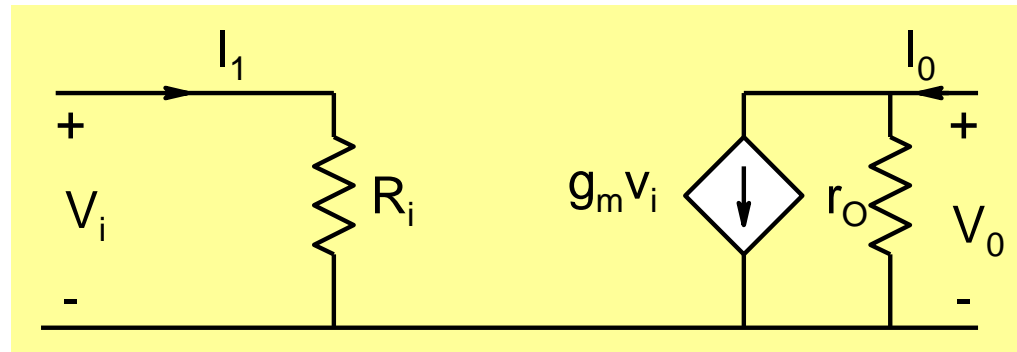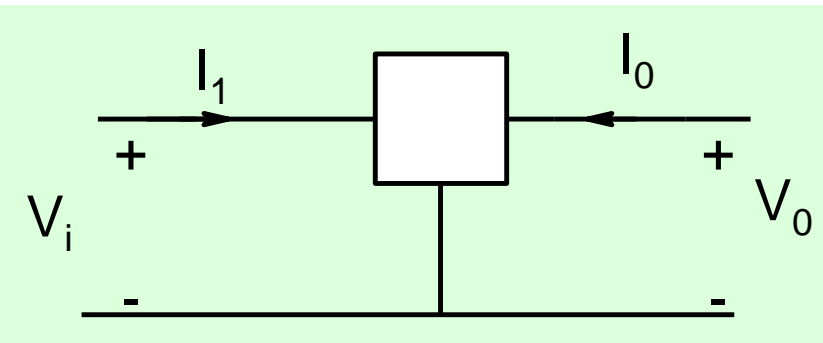

Transistor

Transistor





Trans-resistor



Current I_O is much more sensitive to V_{IN} than V_O

- Can be used for voltage amplification
- Can be used as a switch
- Implement logic
- ...

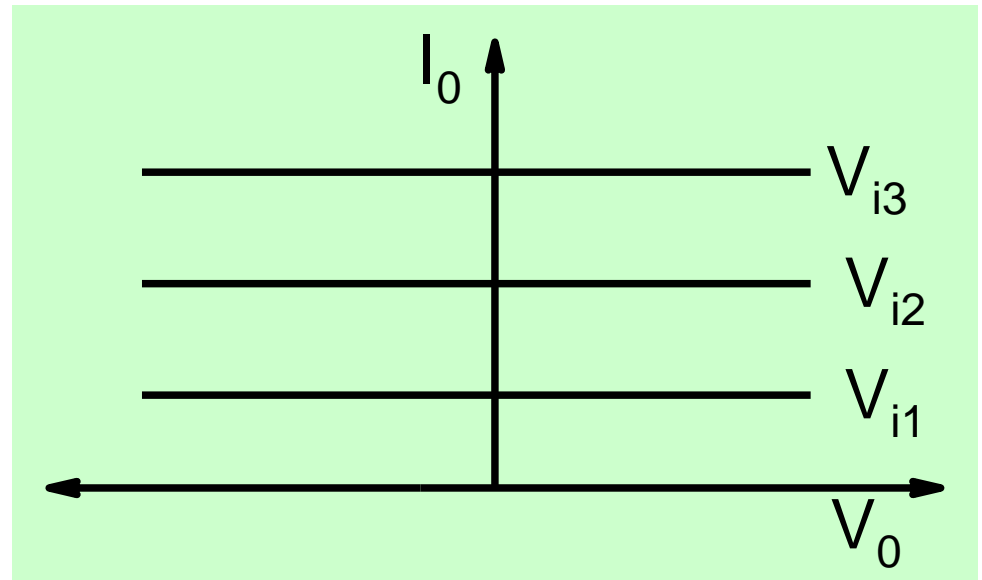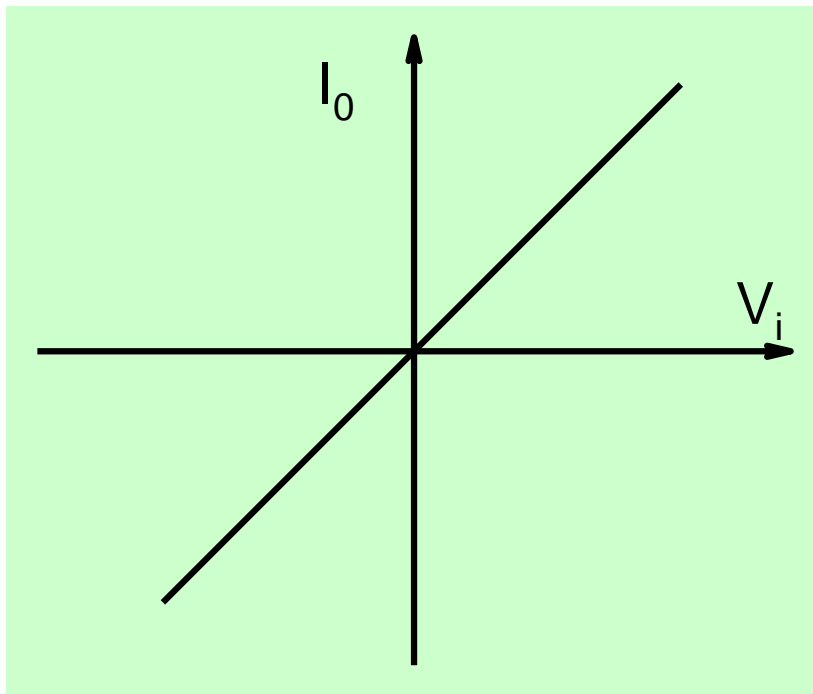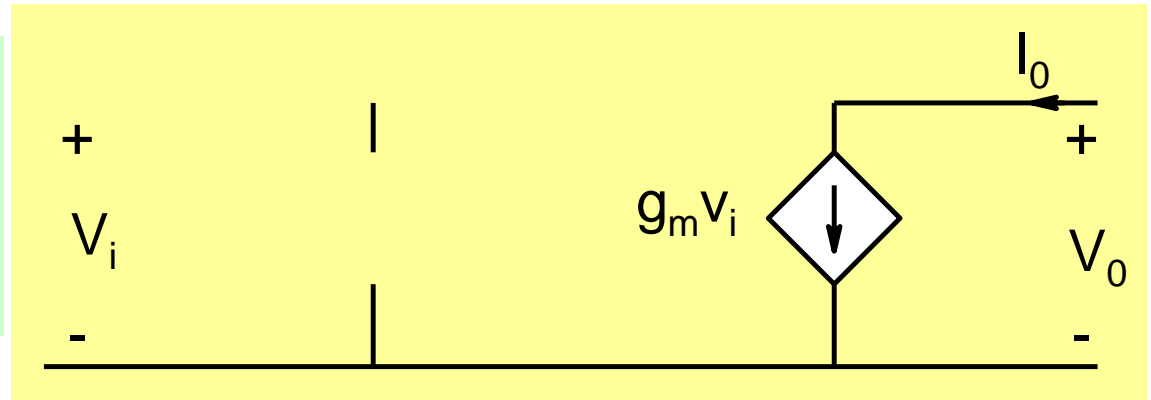
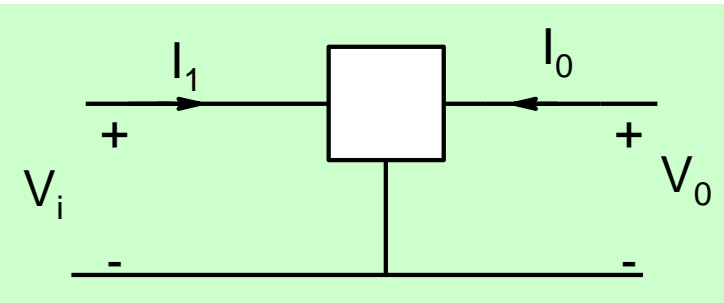
An ideal 3-terminal device for Voltage Amplification




Ideal Transistor Characteristics

Ideal Transistor (IT)

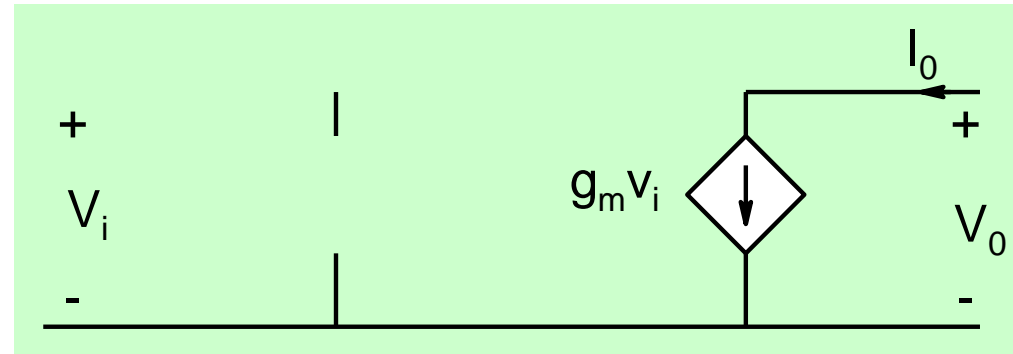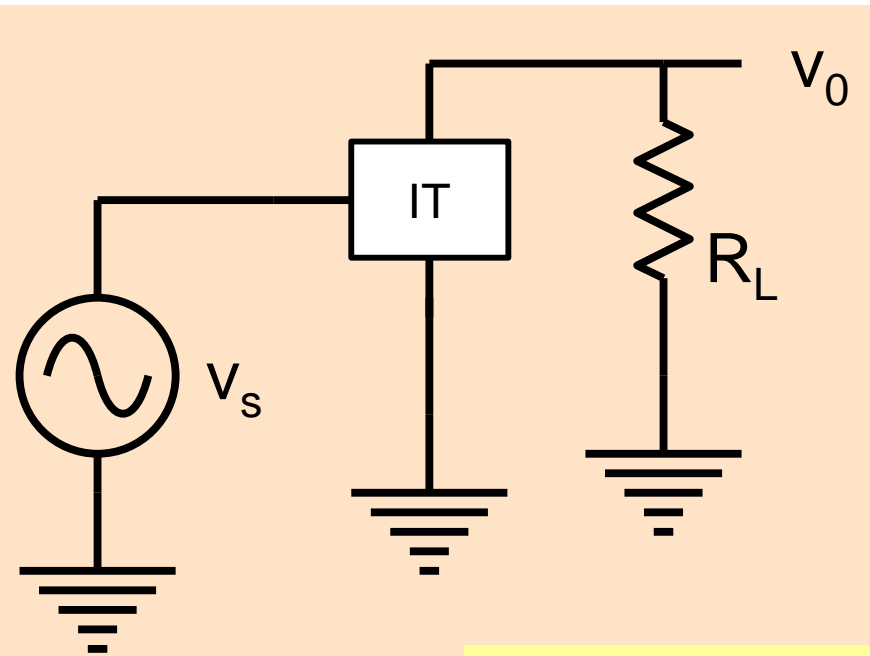Making a voltage amplifier with an ideal transistor is straightforward





$$A_V = \frac{v_o}{v_s} = -g_m R_L$$


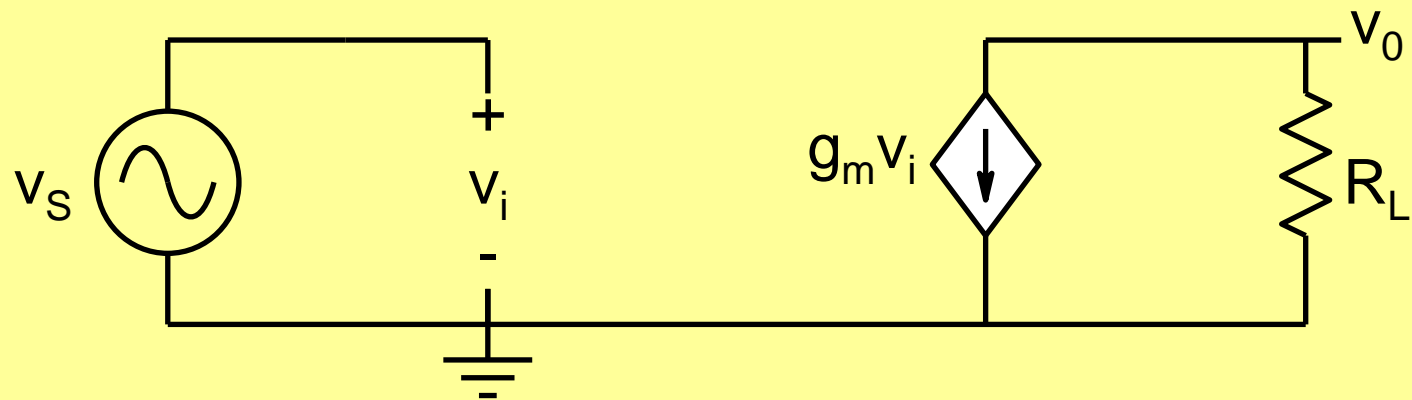


In practice there is no element which has the characteristics of ideal transistor !



Ideal transistor

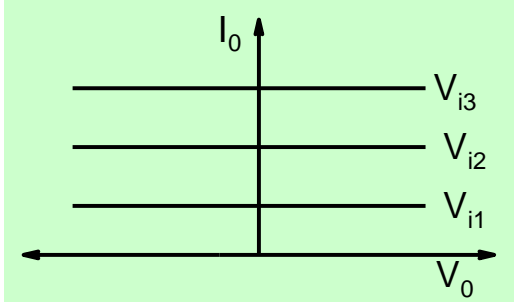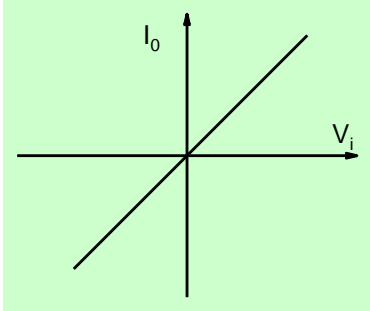

Device X

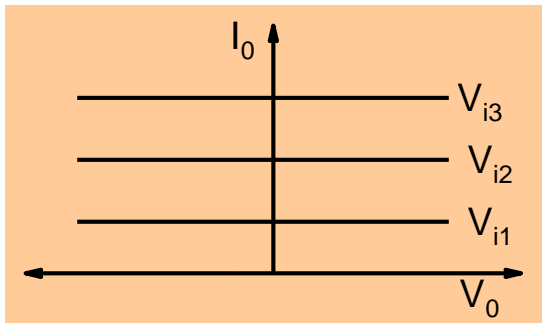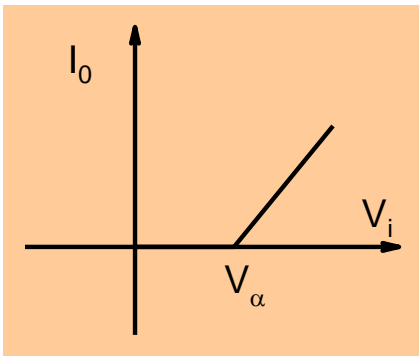


Device Y

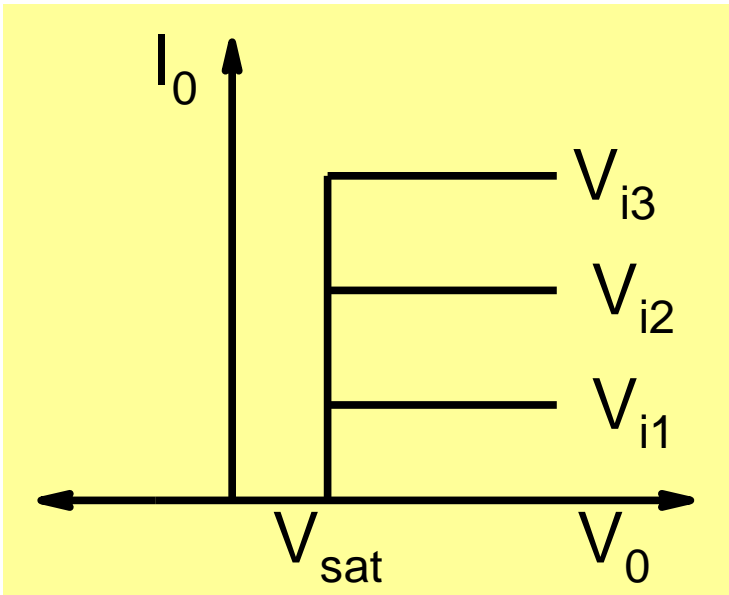
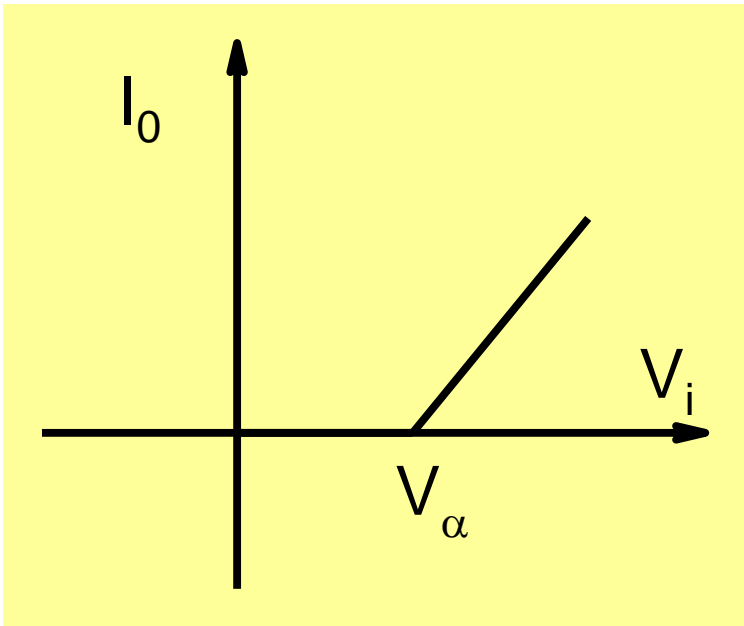


How do we use elements such as X, Y etc to make amplifiers?



Device X

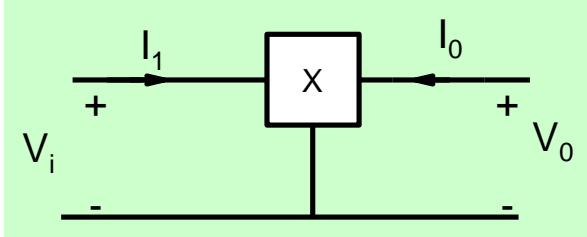



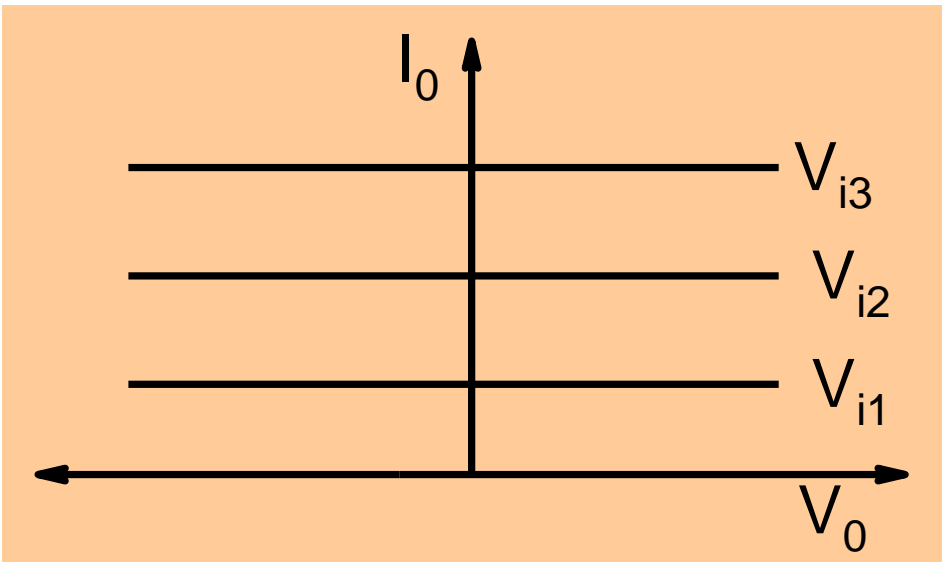
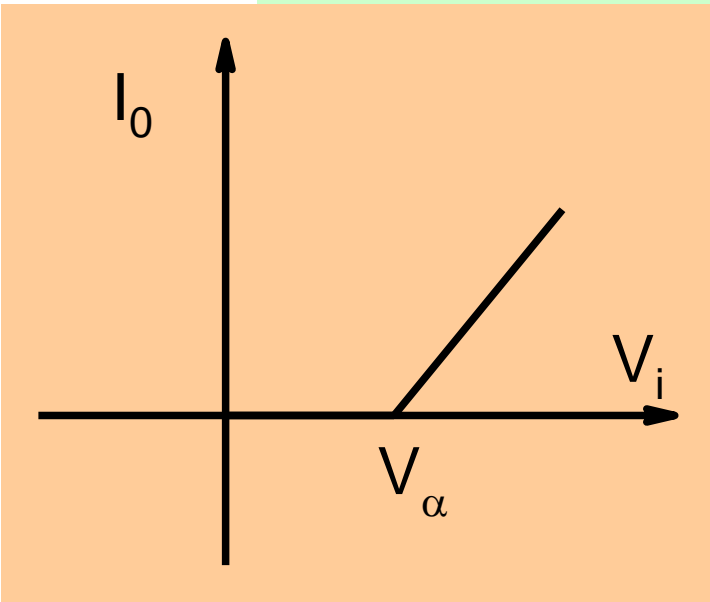
$I_o = 0$ for $V_i \leq V_\alpha$
 $= g_m \times (V_i - V_\alpha)$ for $V_i > V_\alpha$



Ideal Characteristics

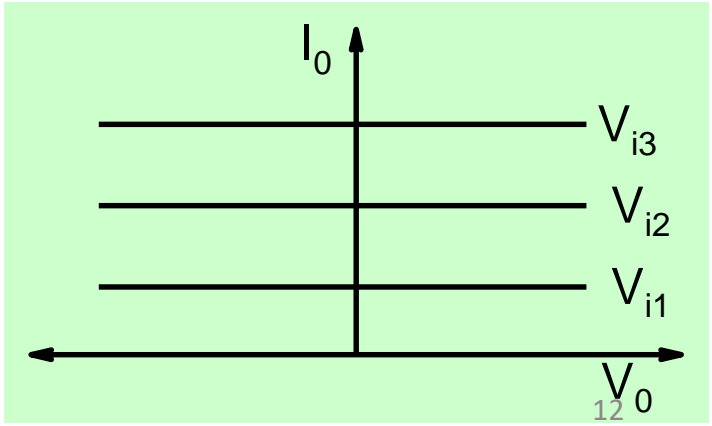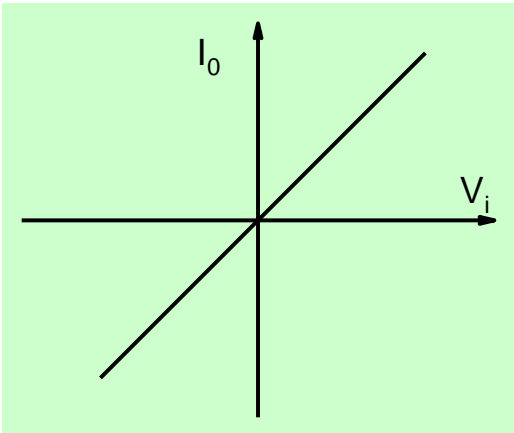

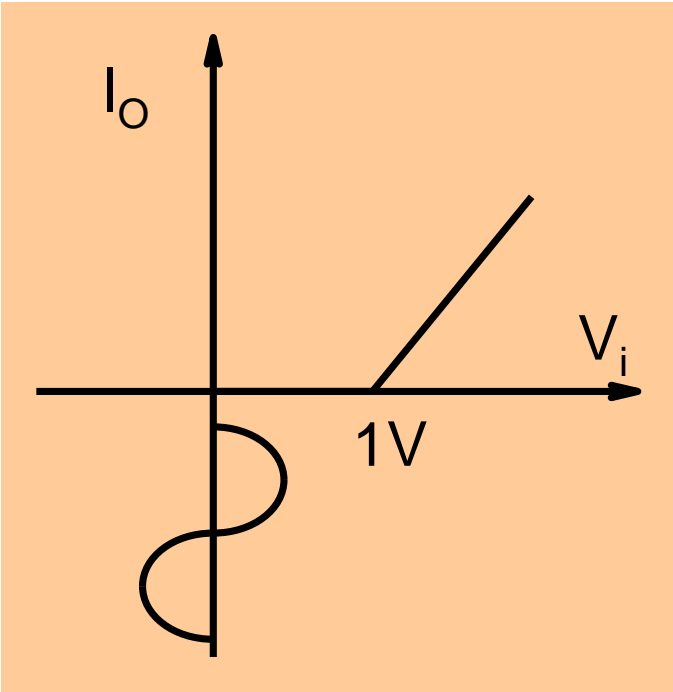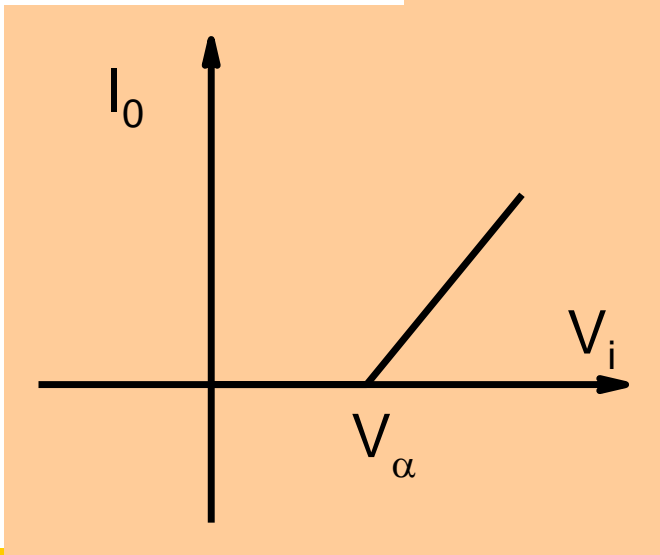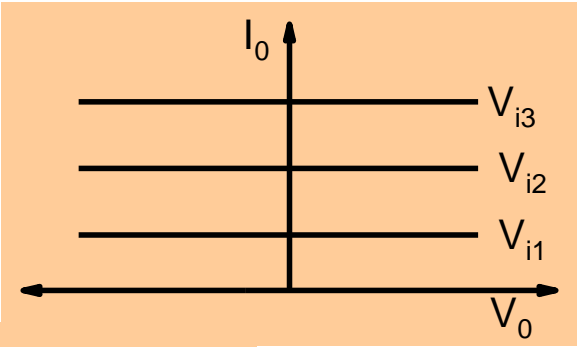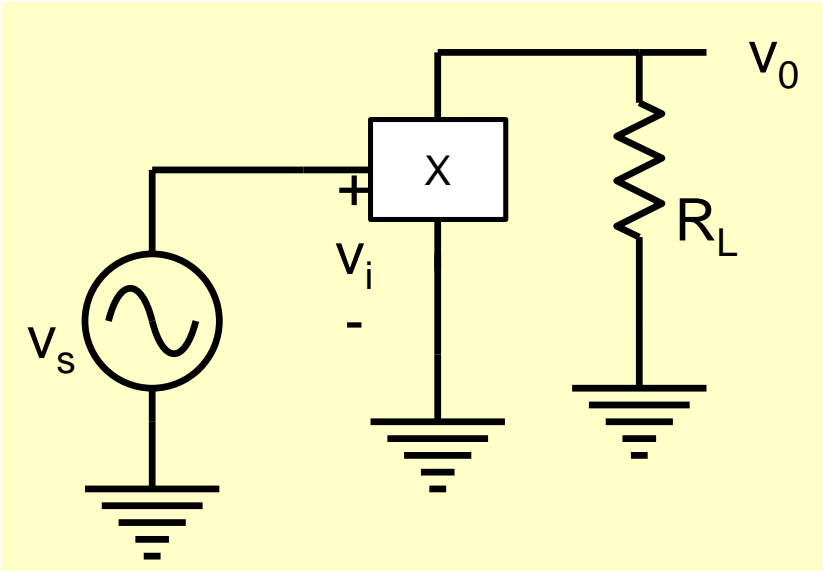How do we use device X to make an amplifier?




$V_\alpha = 1V; g_m = 0.01\Omega^{-1}$
 $R_L = 1K; v_s = 0.5V \sin \omega t$

$I_O = 0 \Rightarrow V_O = 0$

No Amplification




How do we use device X to make an amplifier?

$$V_o = -I_o R_L$$



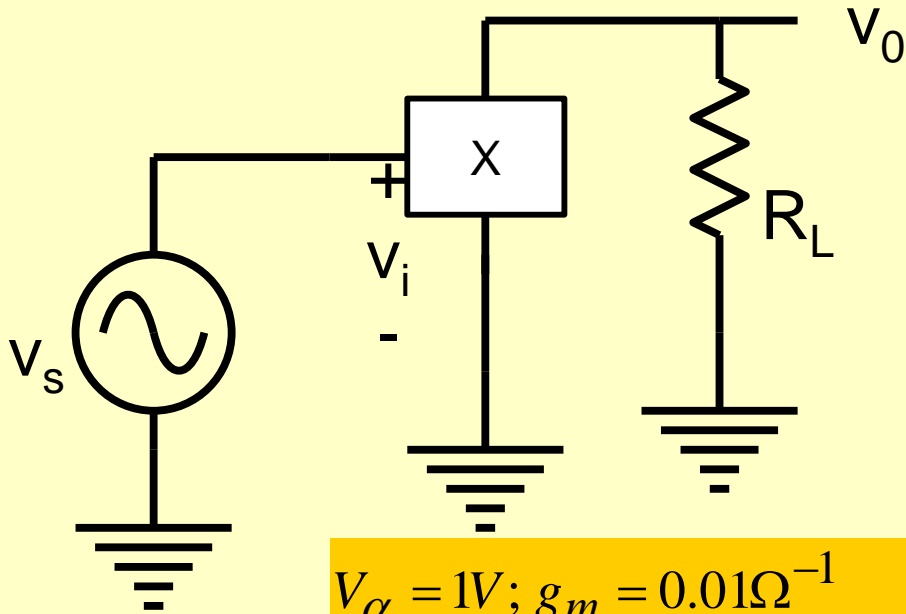


$$V_\alpha = 1V; g_m = 0.01\Omega^{-1}$$


$$R_L = 1K; v_s = 0.5V \sin \omega t$$

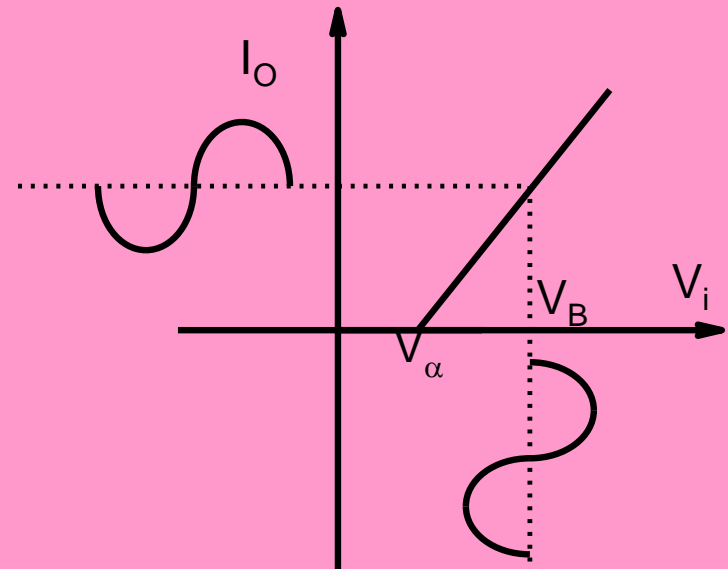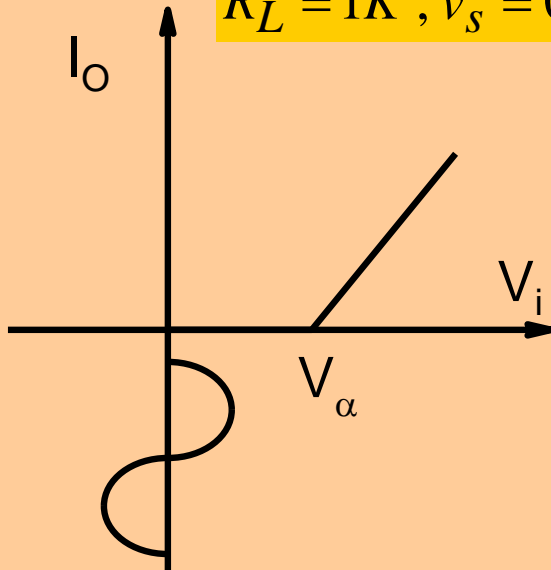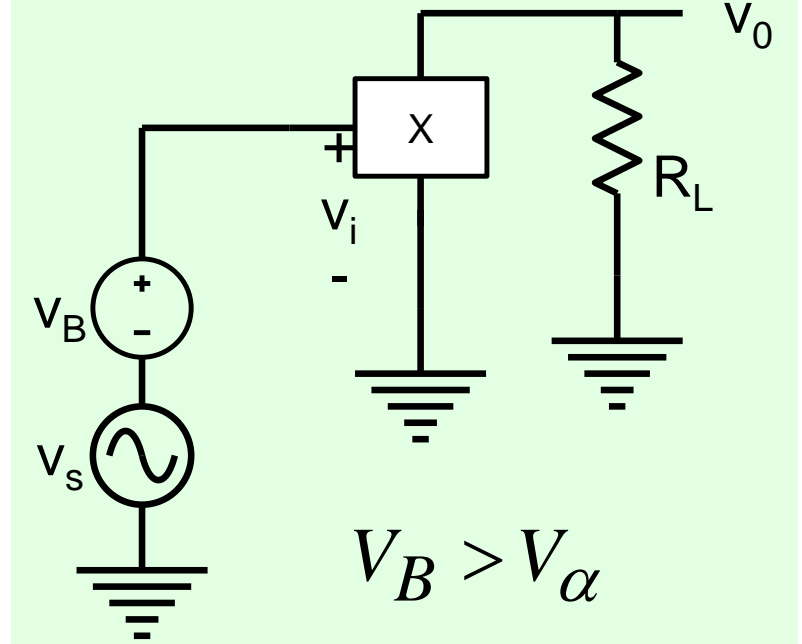

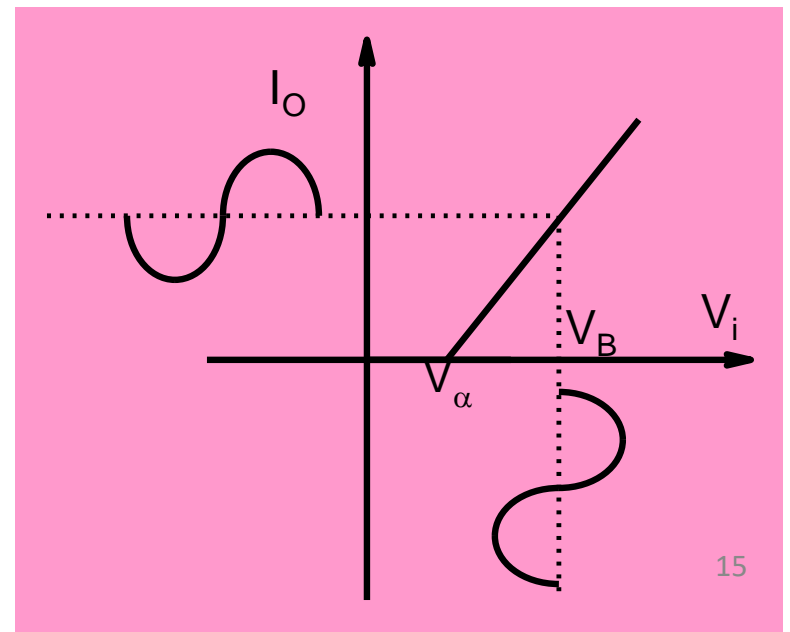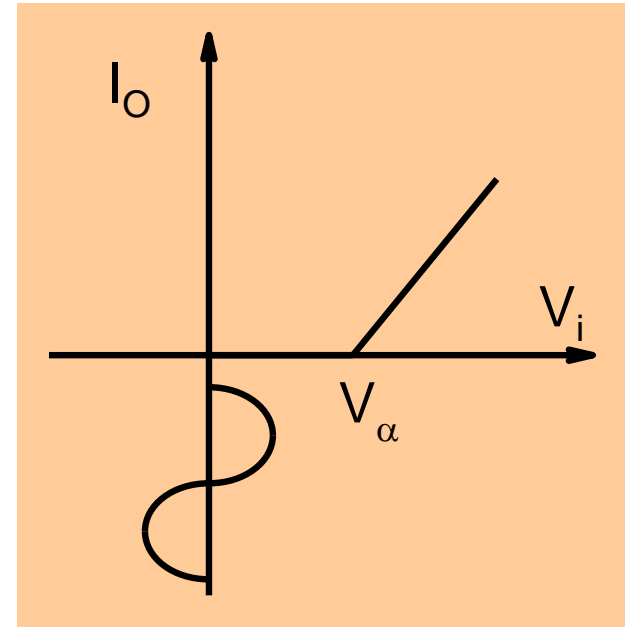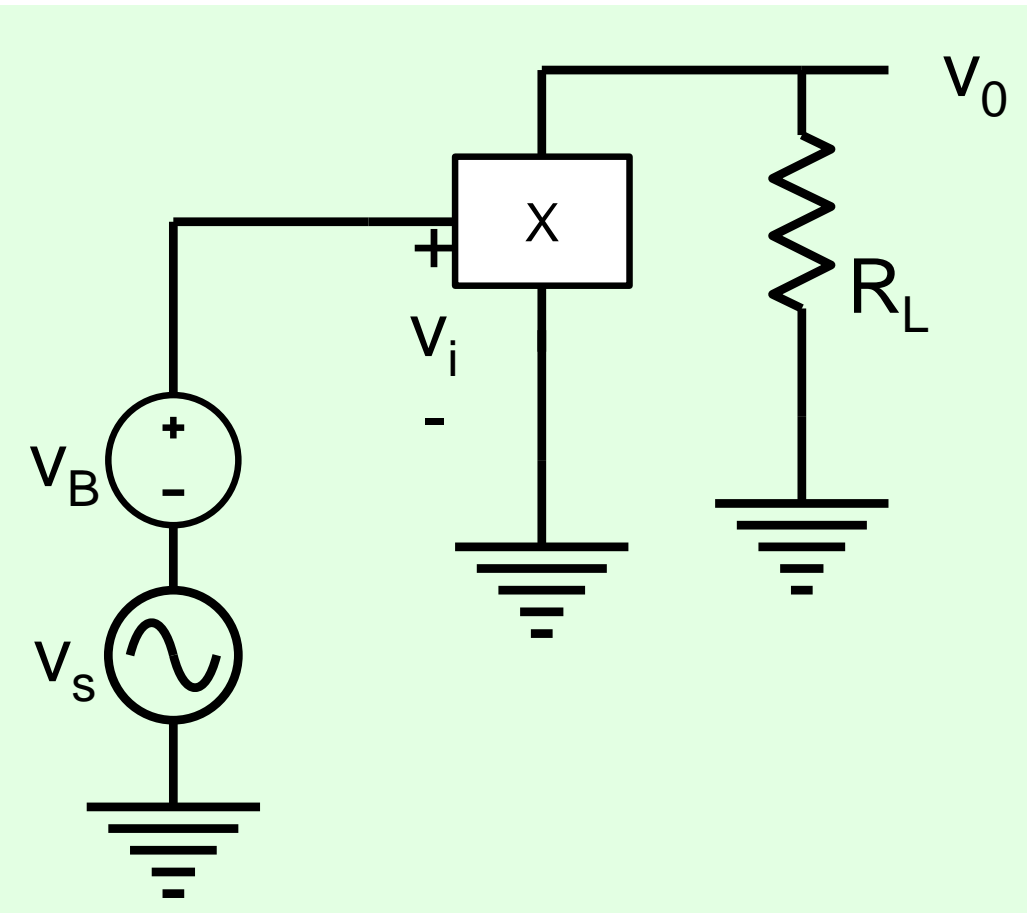When only a part of device characteristics is suitable for amplification, then we need to push the device into that region by applying suitable bias voltages. This process is called **BIASING**







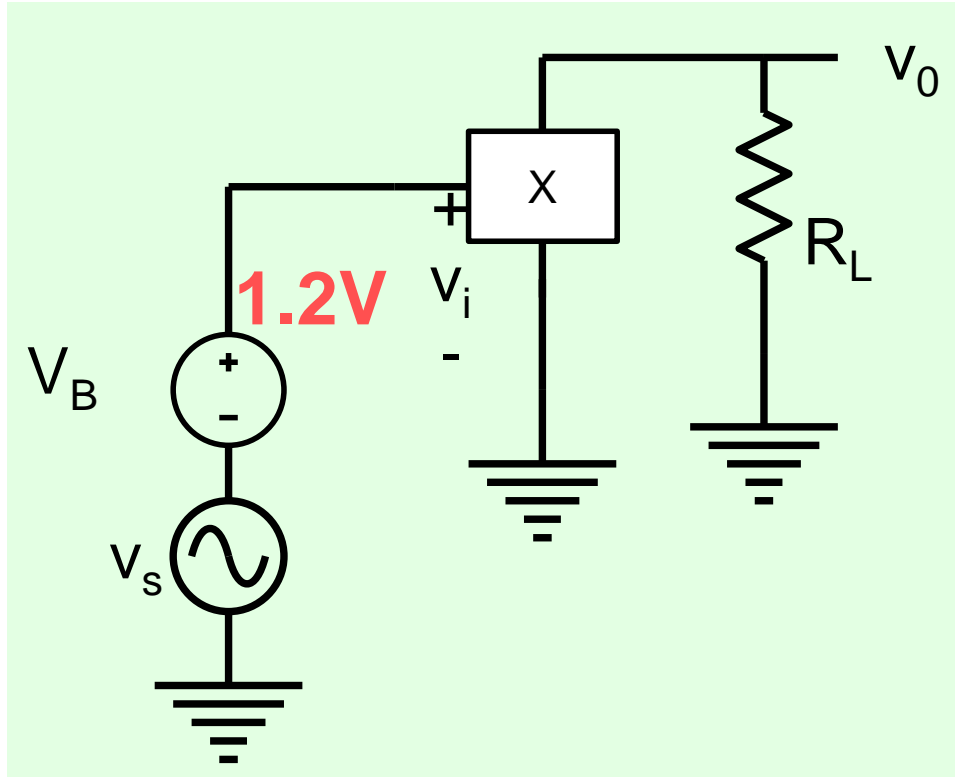
How should one choose the bias voltage V_B ?



$$v_s = 0.5V \sin \omega t$$

Quiescent point or Bias point

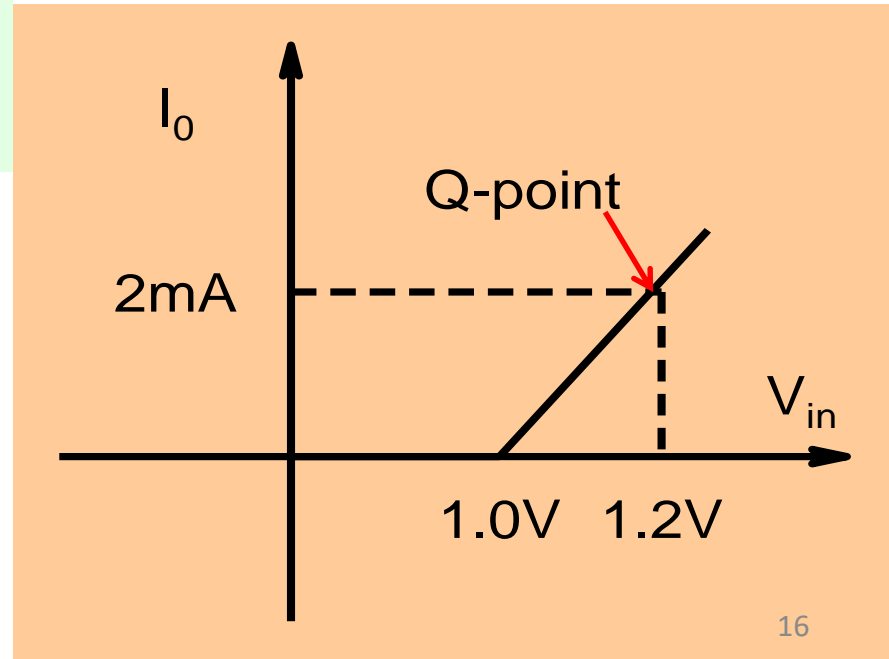

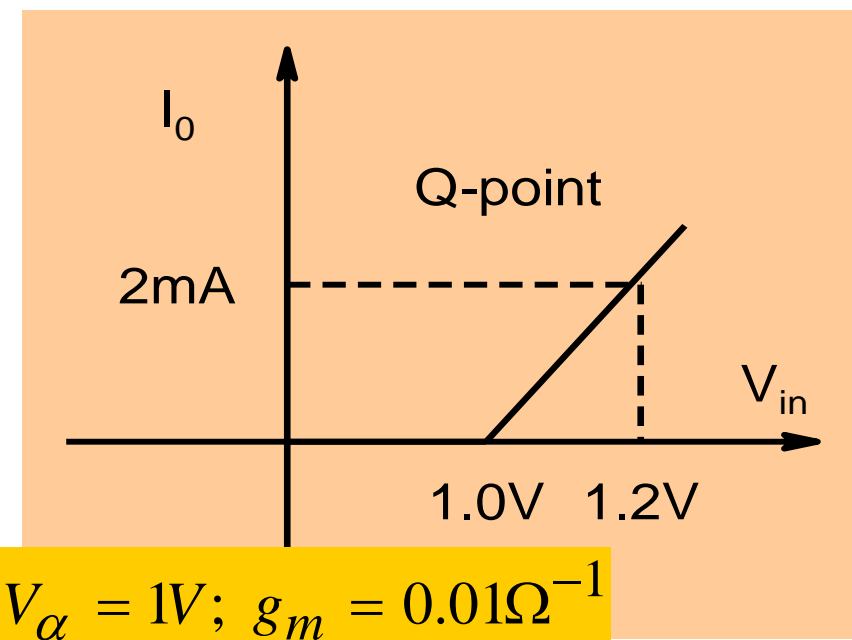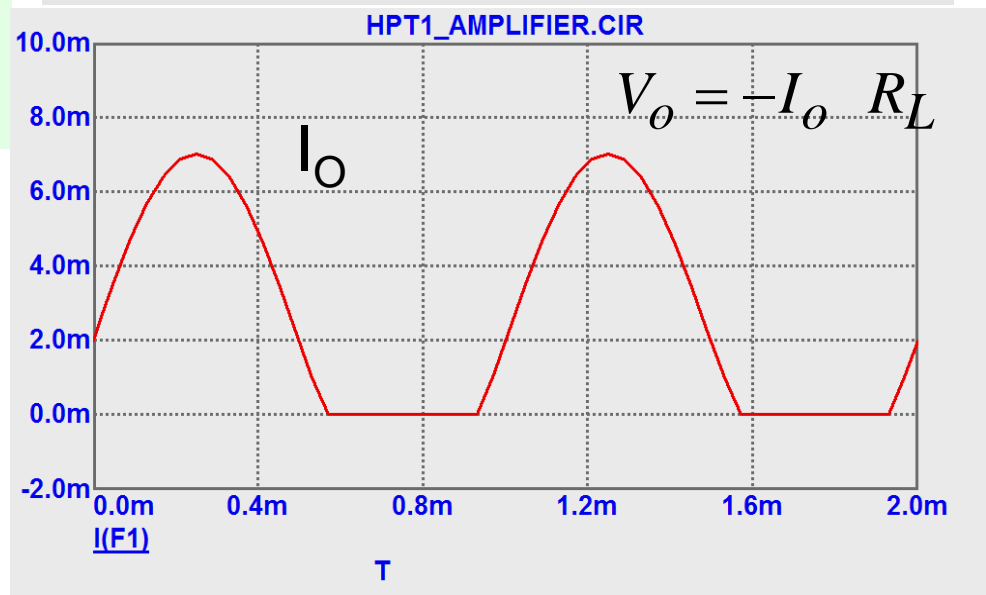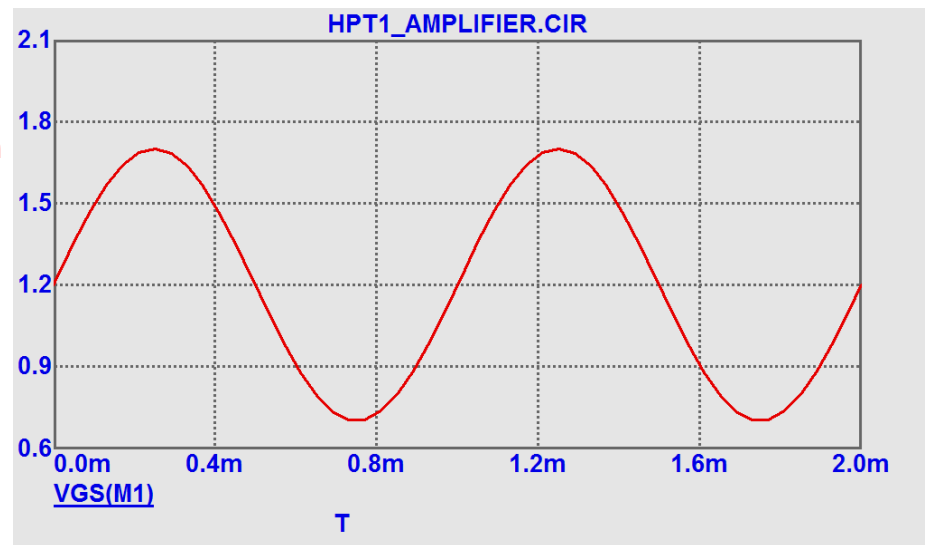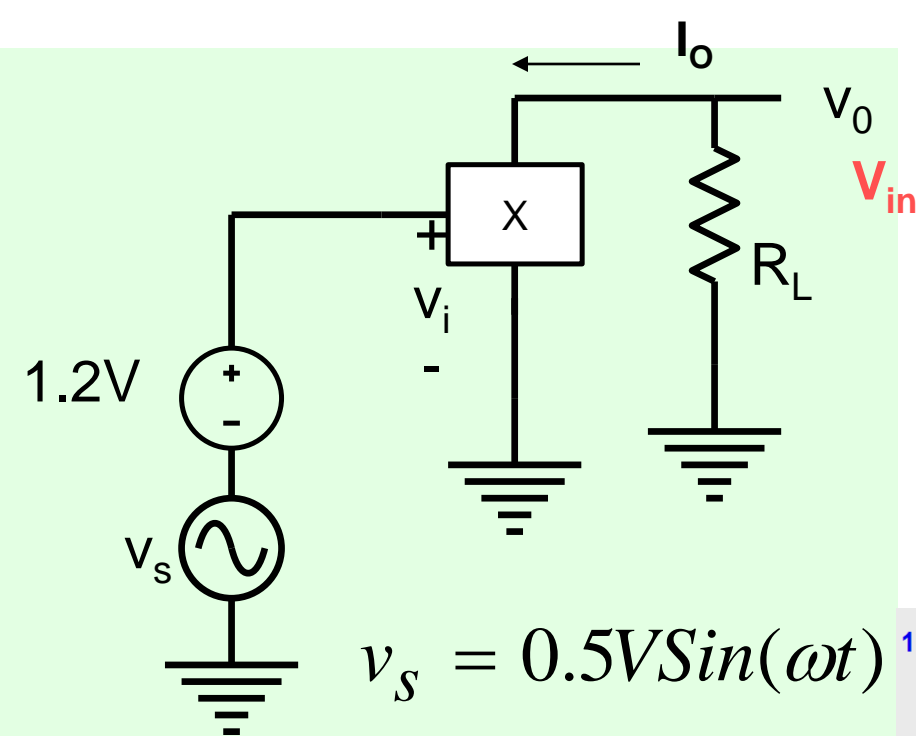



$$I_o = 0 \quad \text{for } V_i \leq V_{\alpha}$$

$$= g_m \times (V_i - V_{\alpha}) \quad \text{for } V_i > V_{\alpha}$$

Output voltage is distorted !






$$R_L = 1\text{k}\Omega$$

$$V_O = -I_O R_L$$




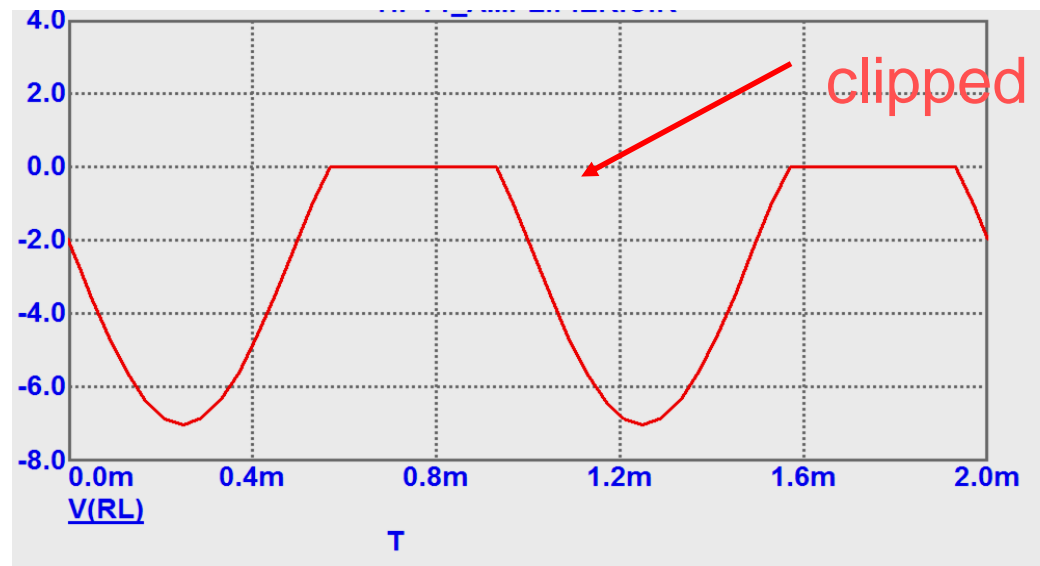
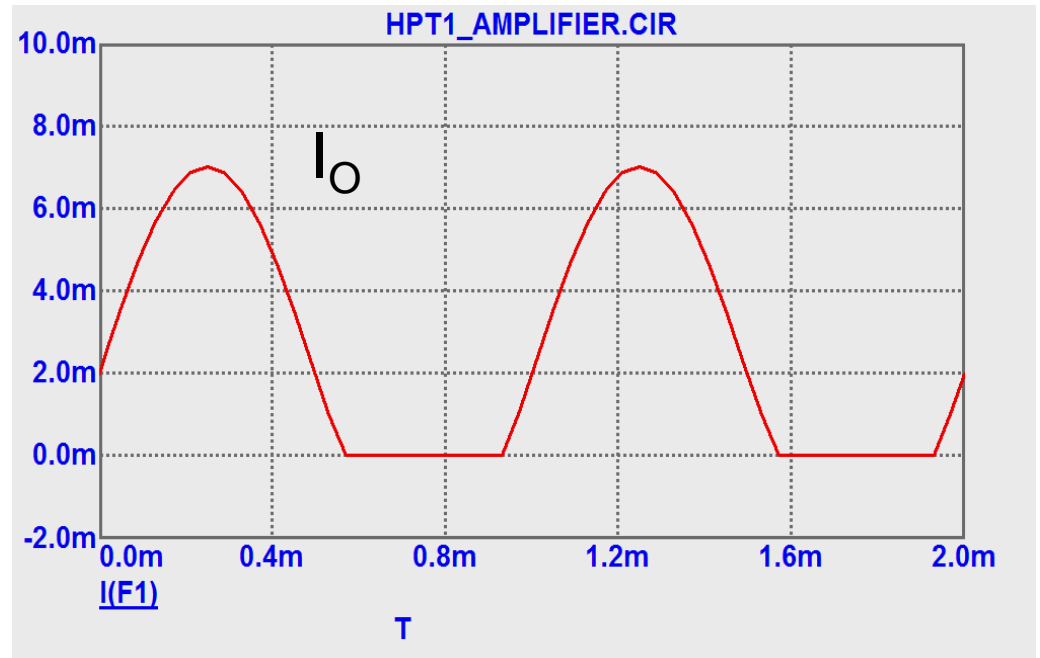


Need to choose a proper value of biasing Voltage





Unnecessary Power Dissipation

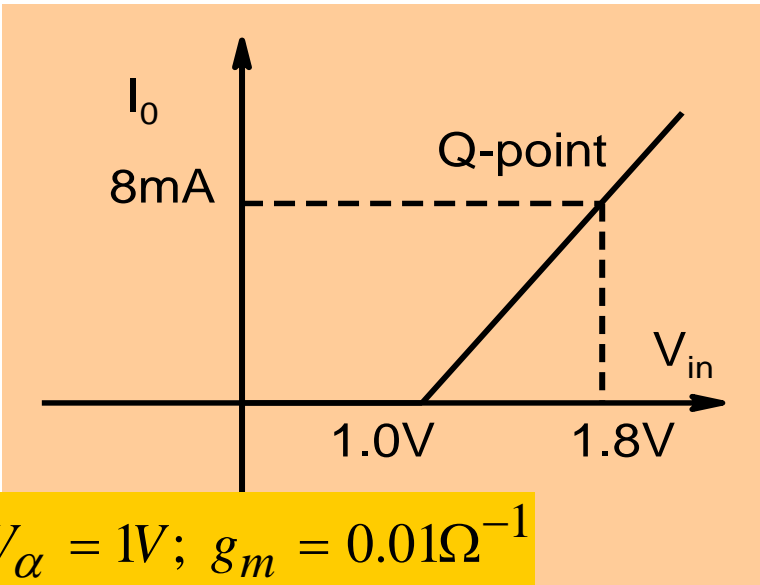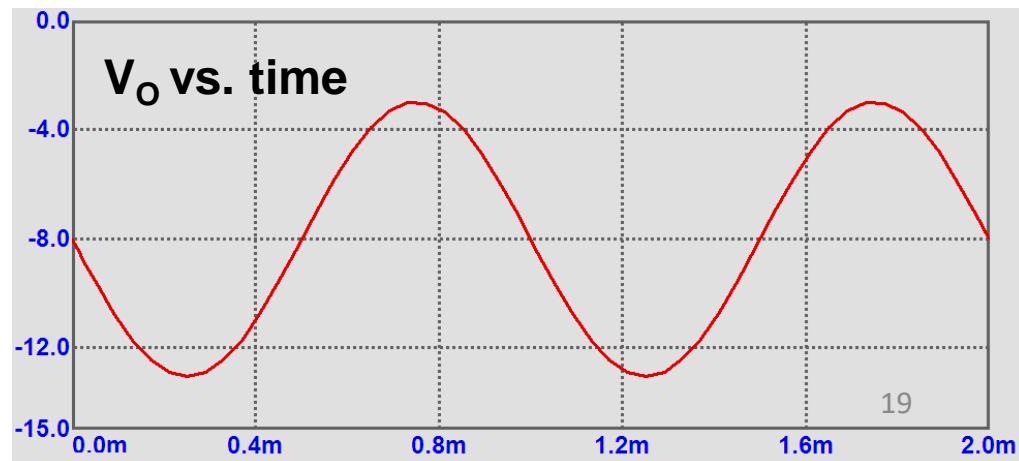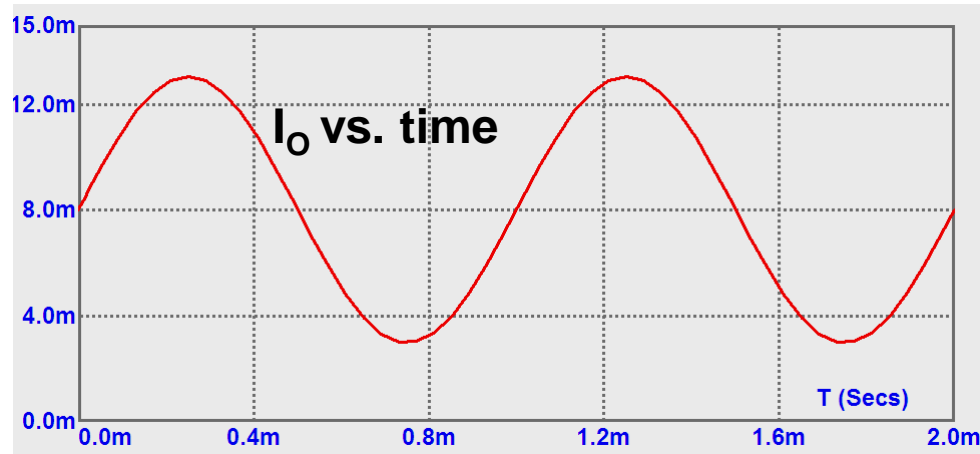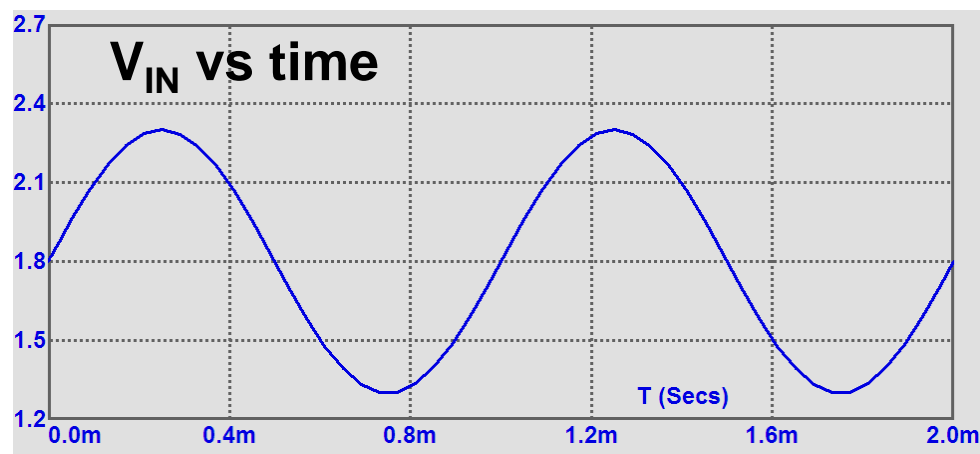
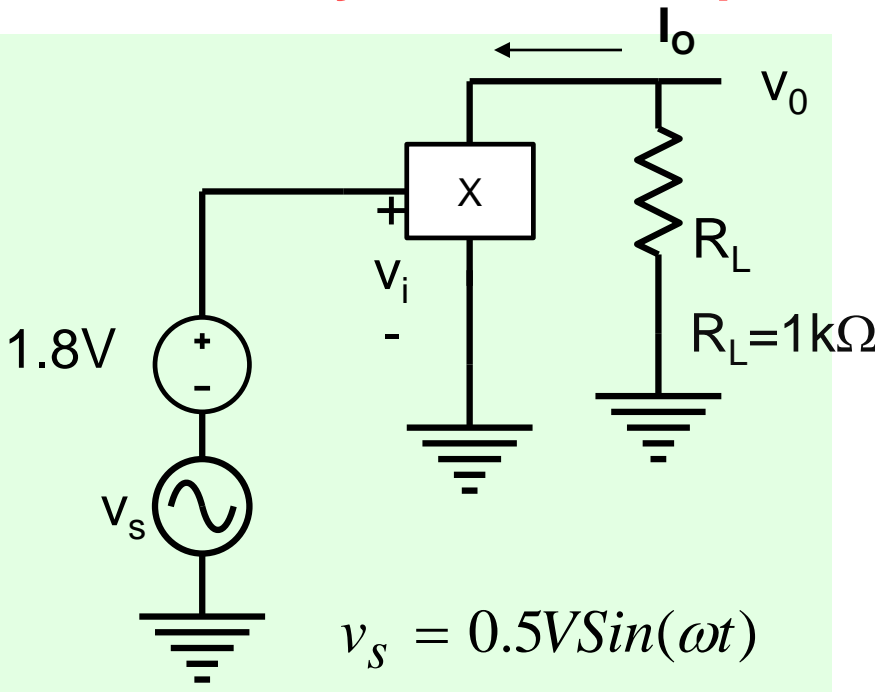


Optimum Biasing ?

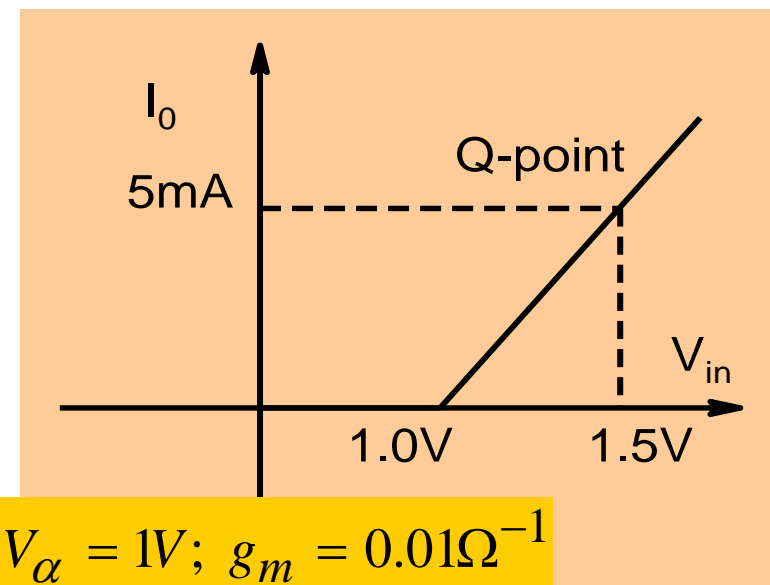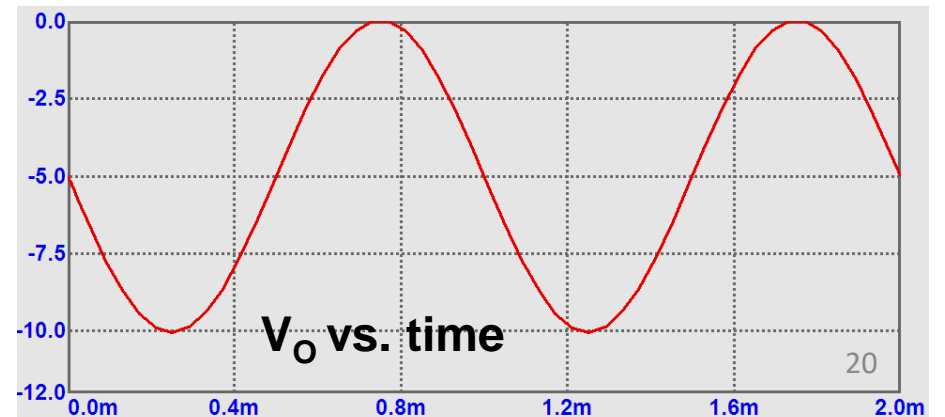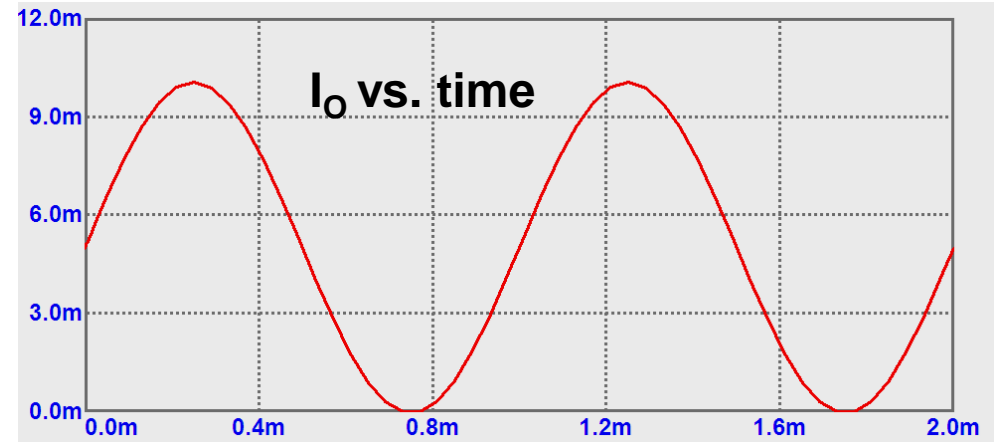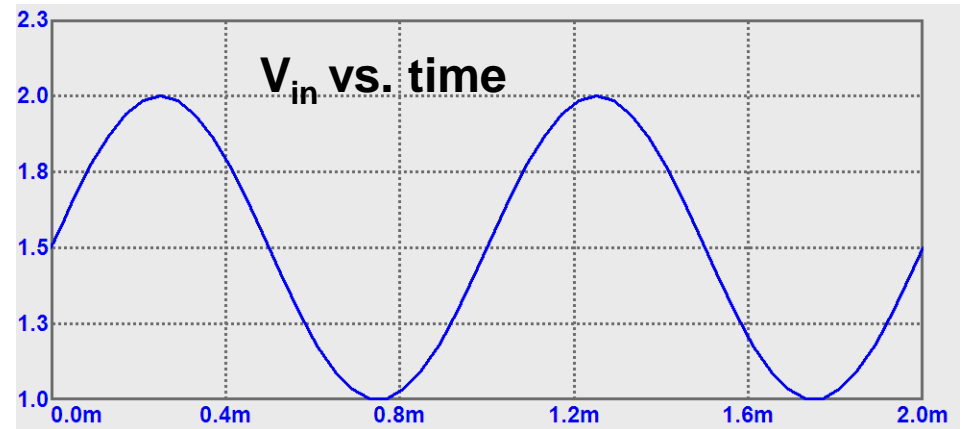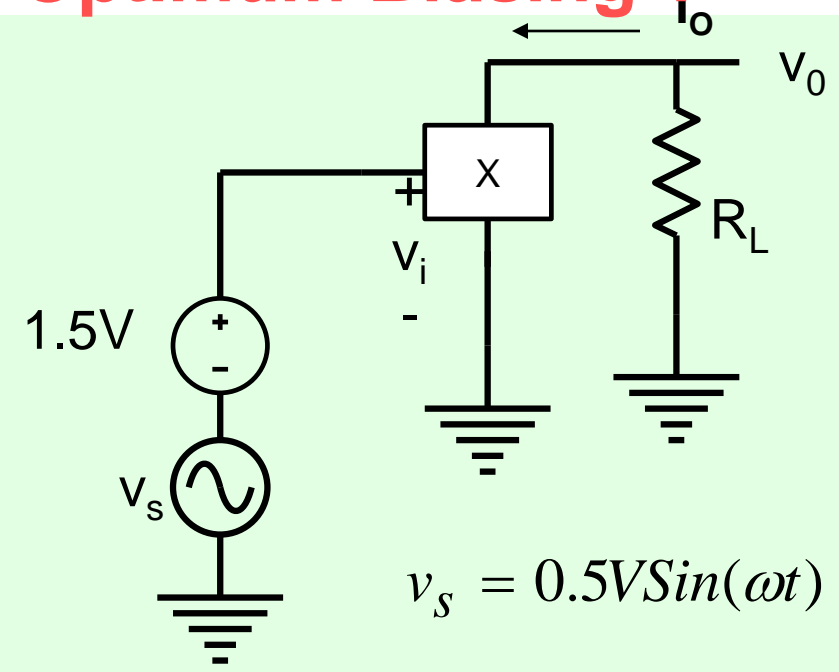

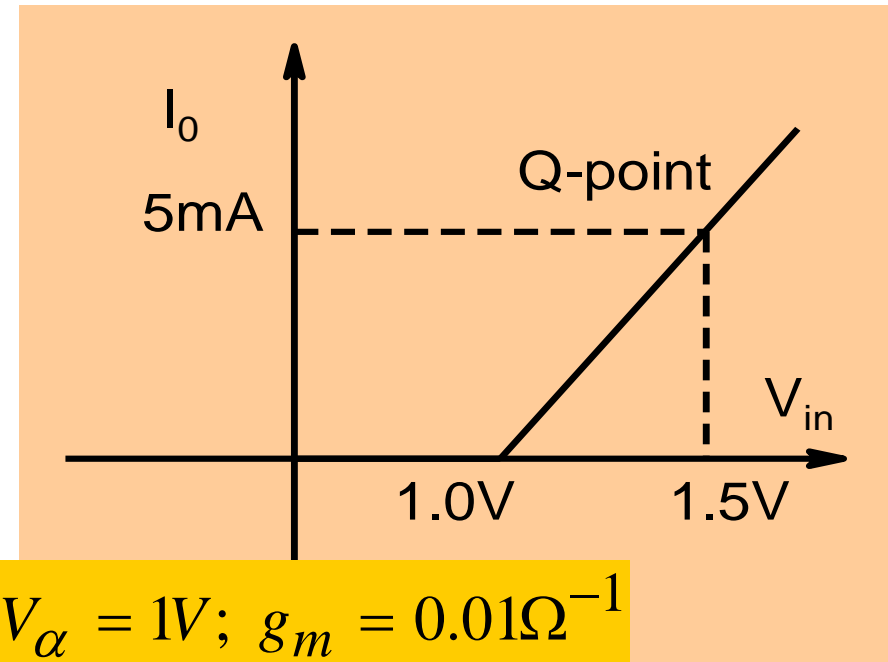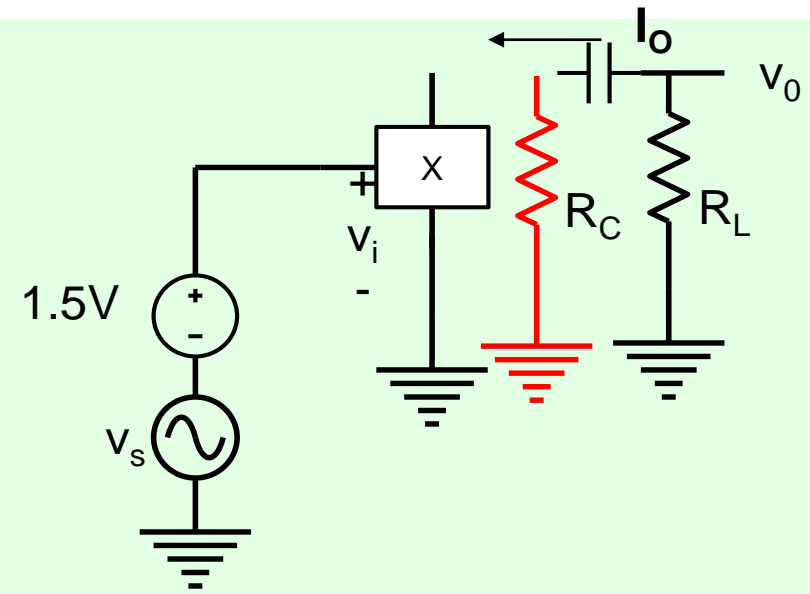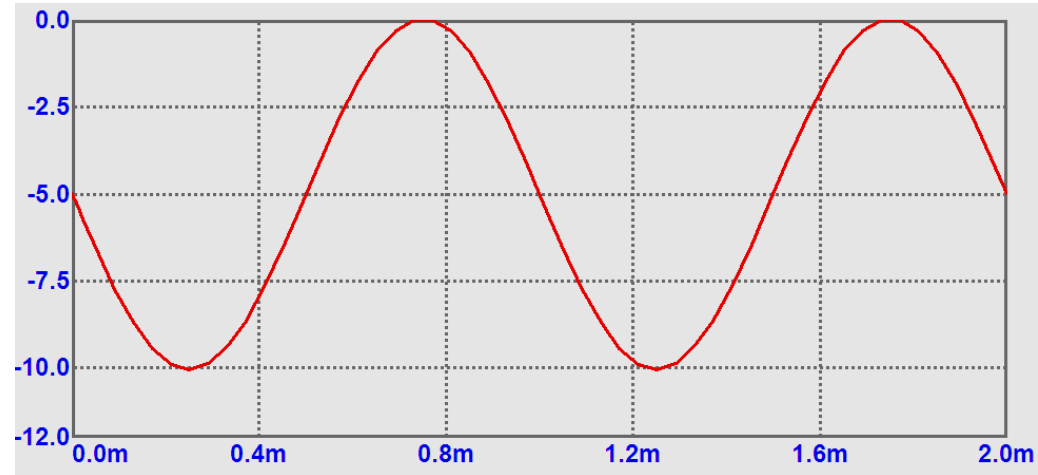
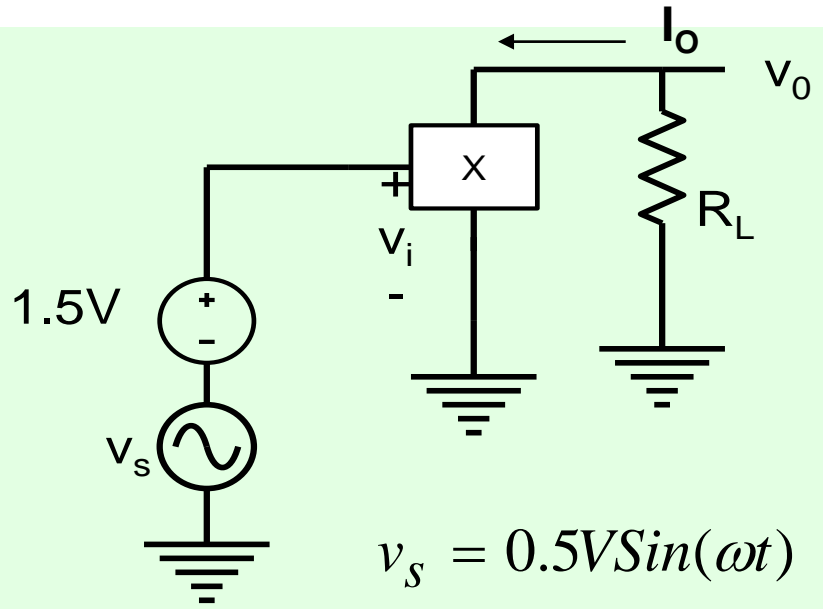
How do we get rid of unwanted dc voltage at the output ?



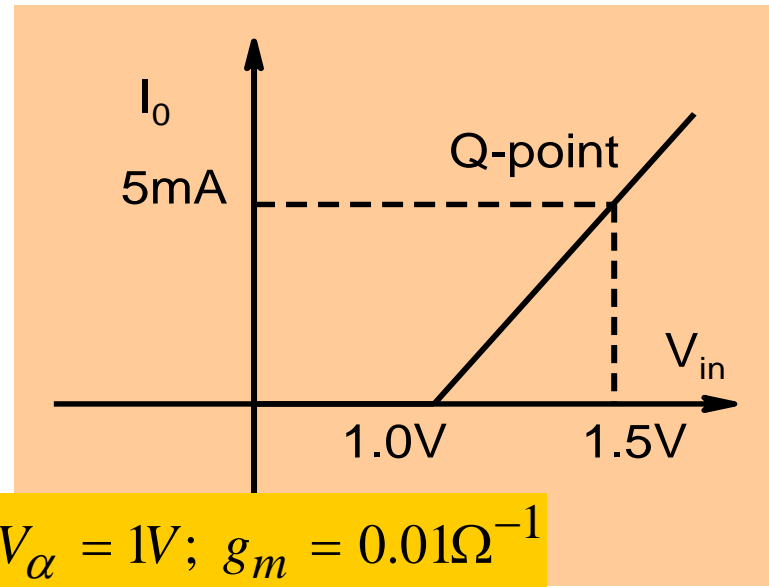
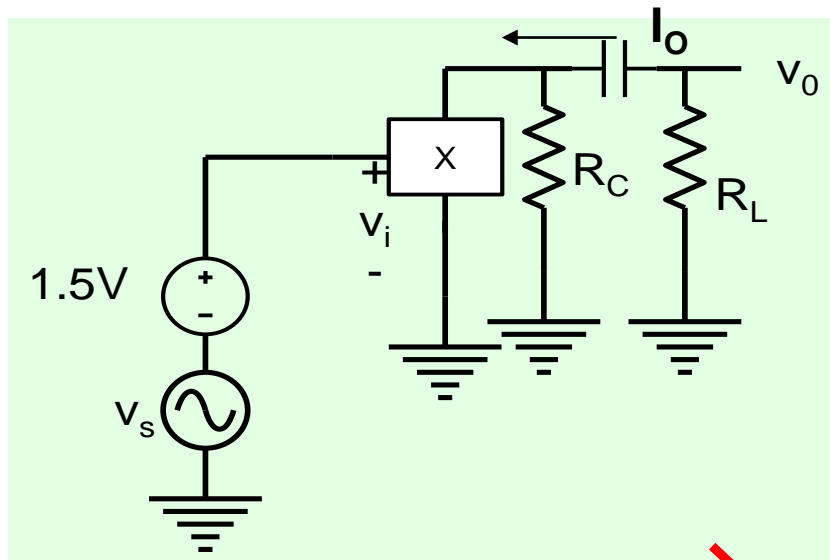


dc


ac (signal)

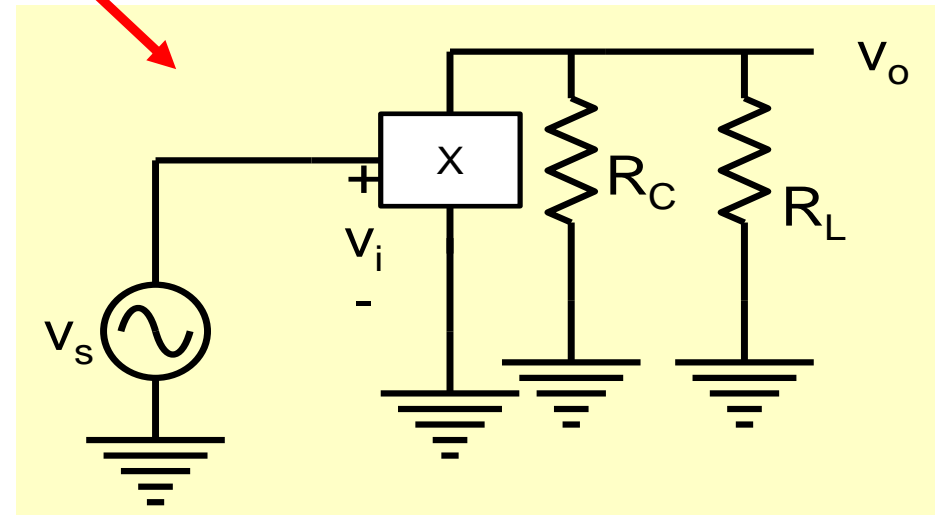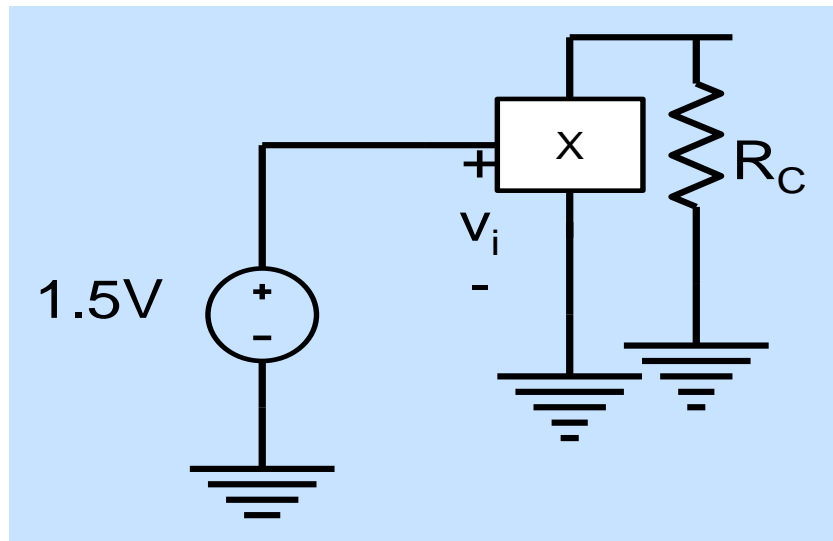




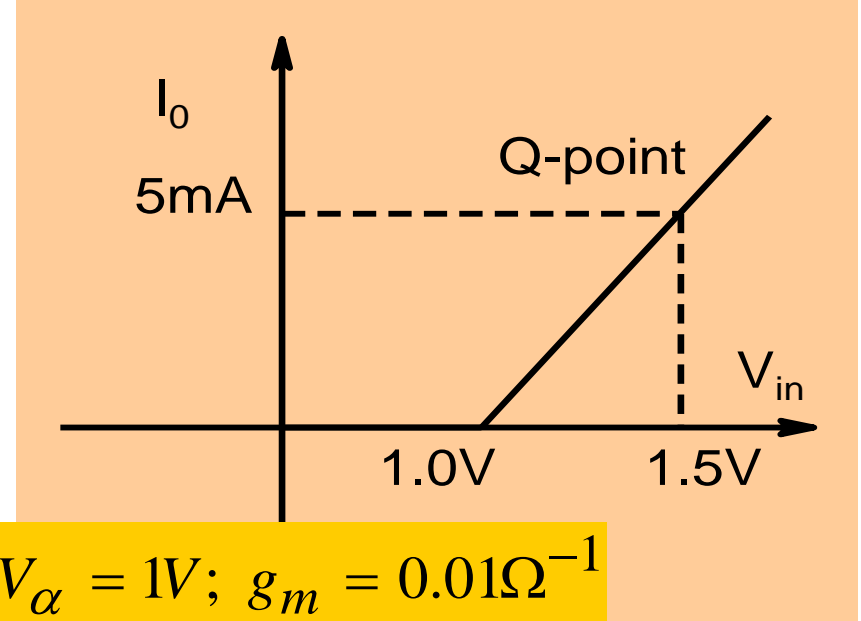
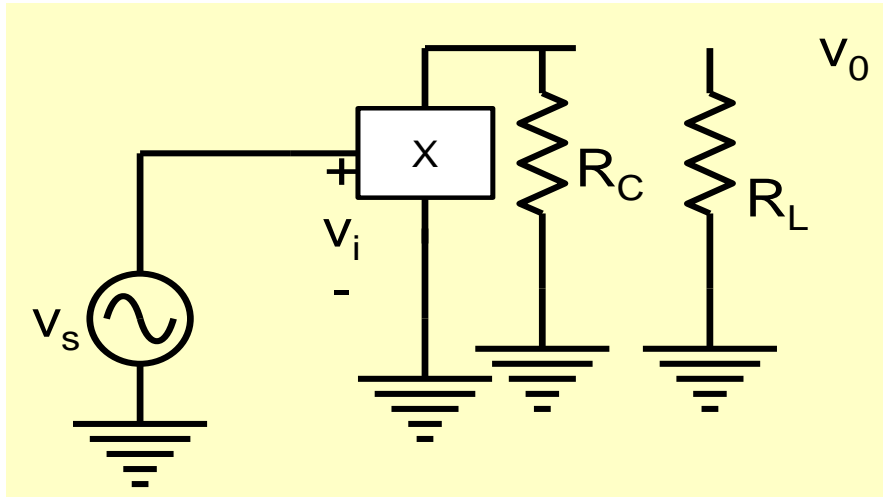
Capacitor is chosen large enough so that at the signal frequency $1/j\omega C \sim 0$.






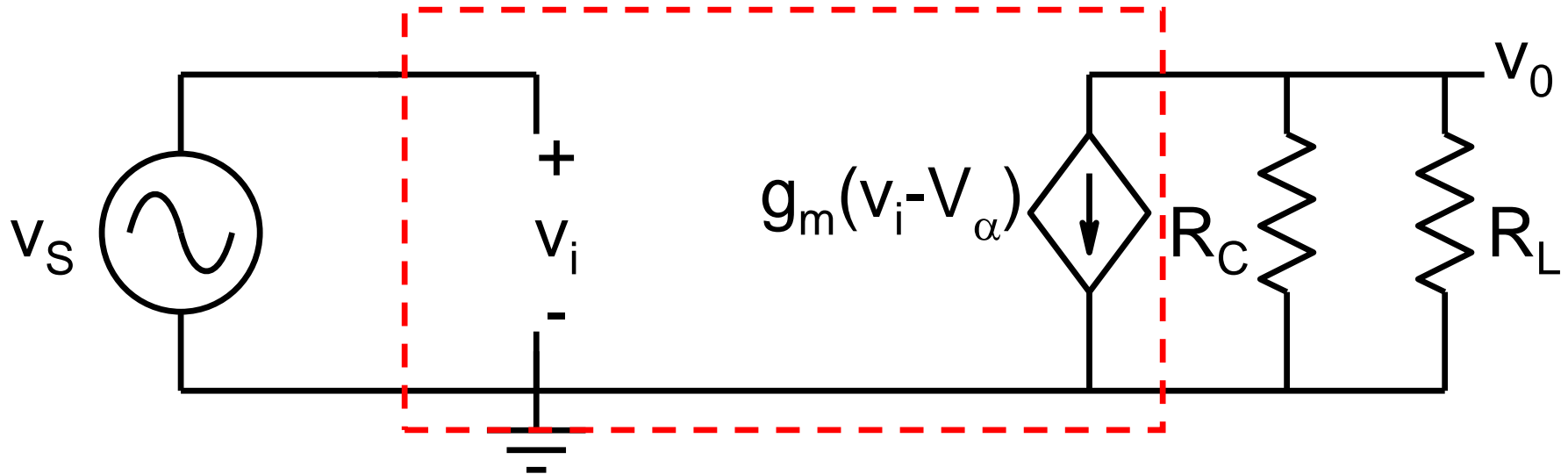
$$I_o = g_m \times (V_i - V_{\alpha}) \text{ for } V_i > V_{\alpha}$$



AC Analysis

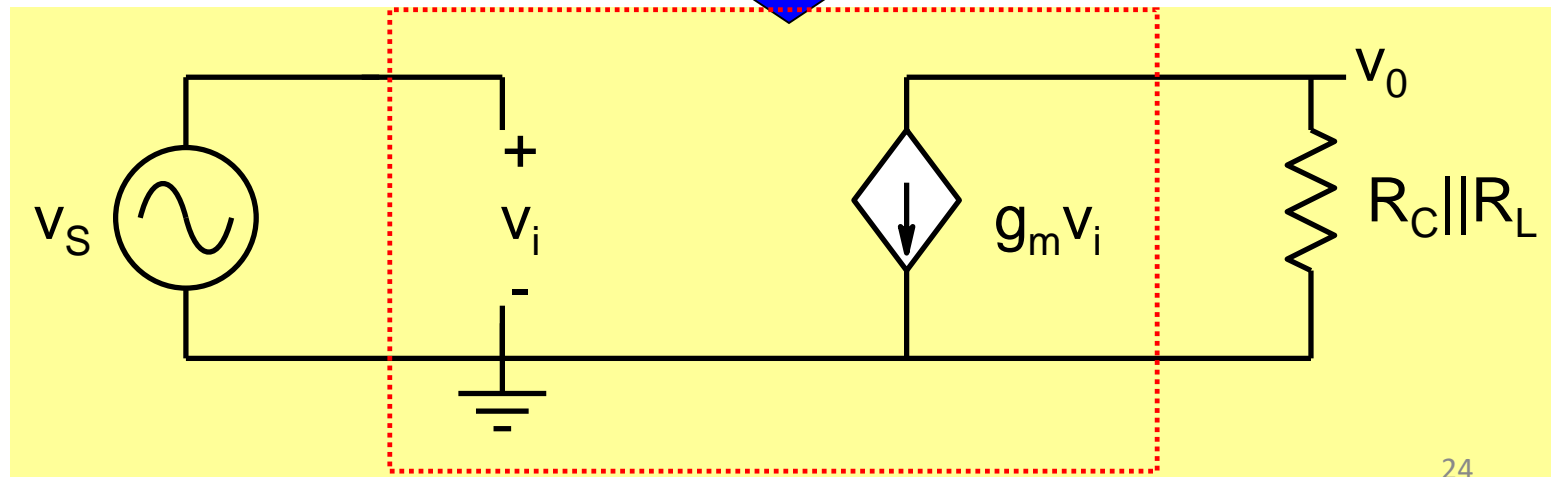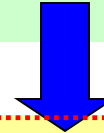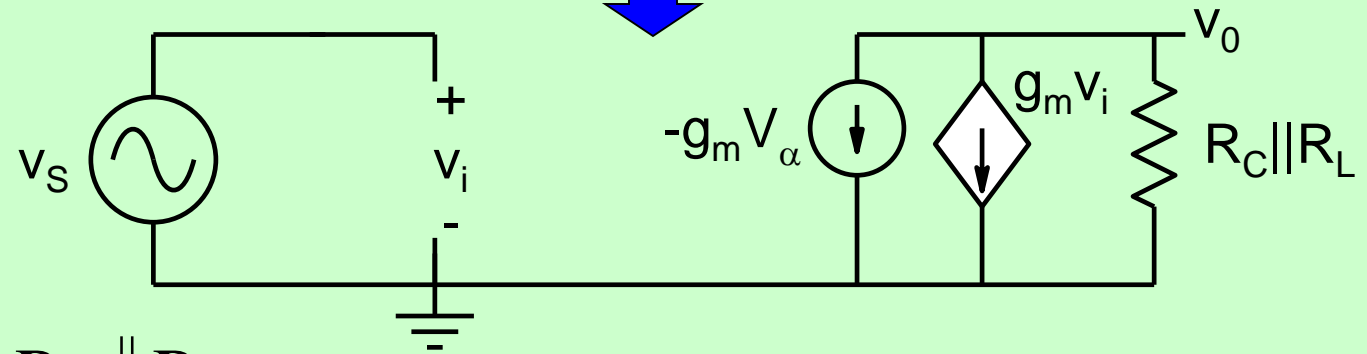
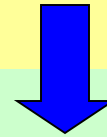
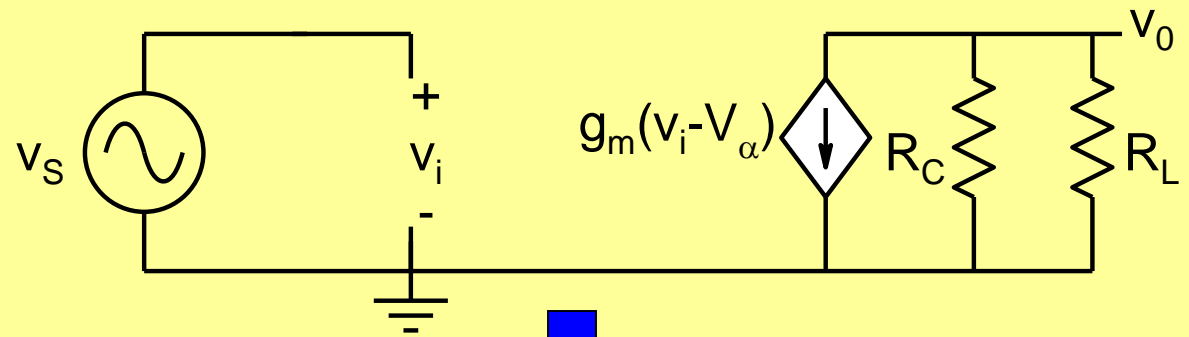


$$A_V = \frac{v_o}{v_s} = -g_m R_C || R_L$$

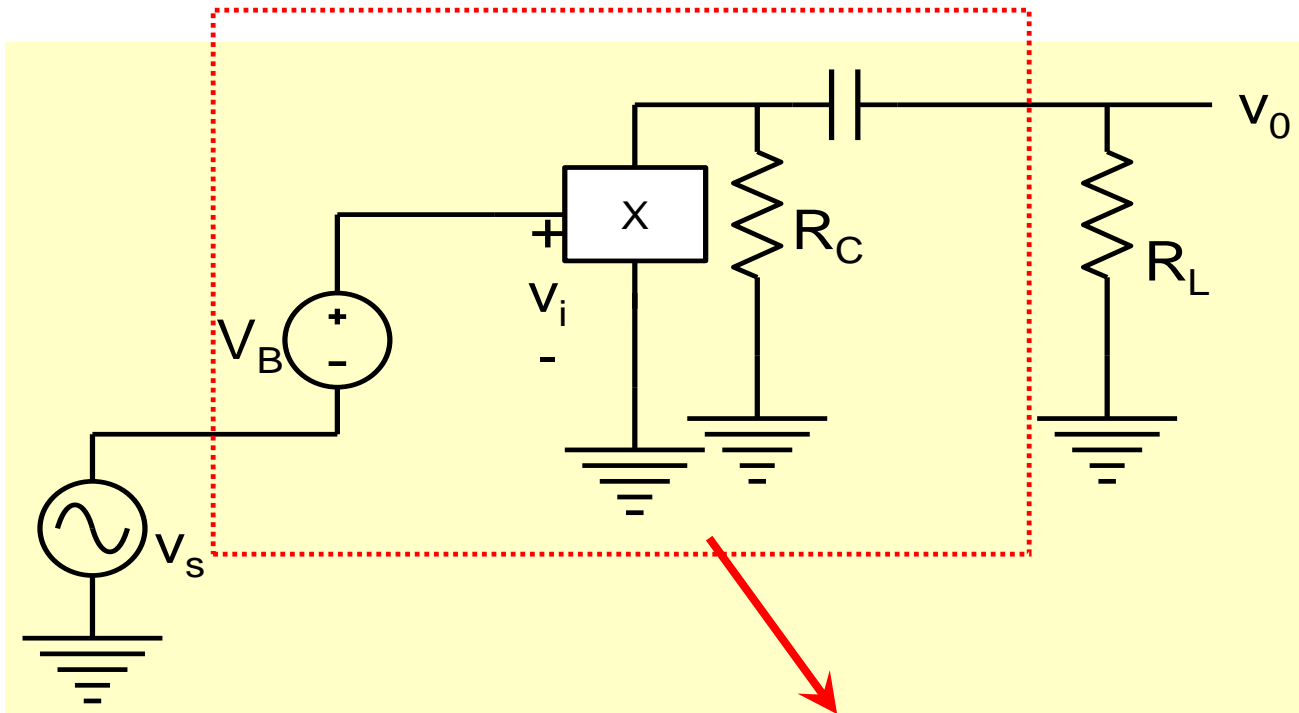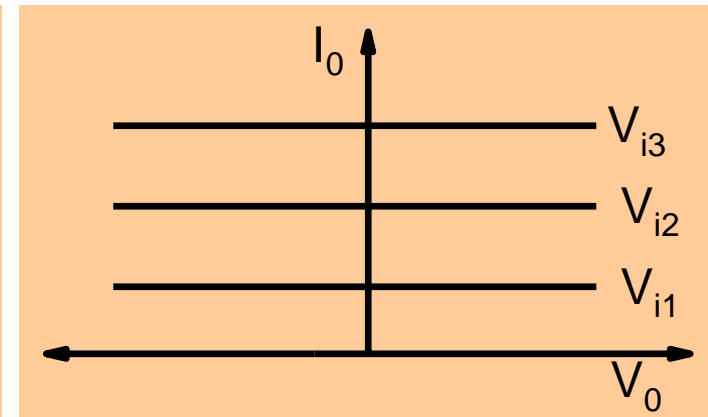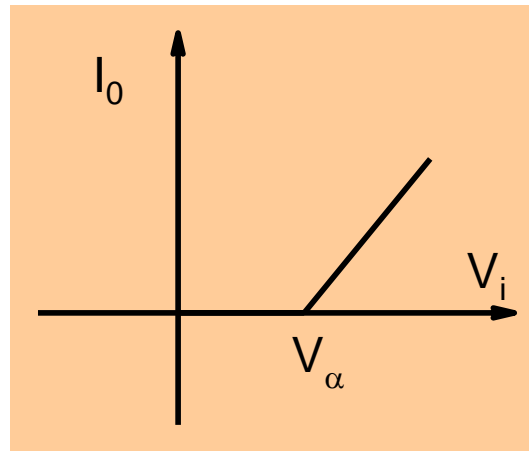
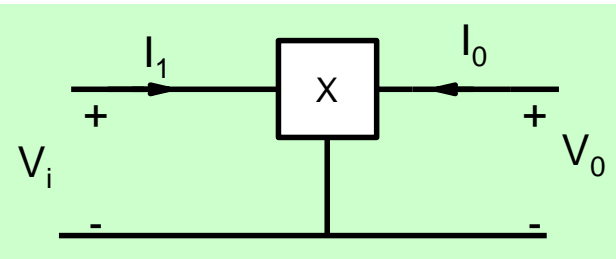


The addition of biasing network allows element X to appear as an ideal transistor to the signal source

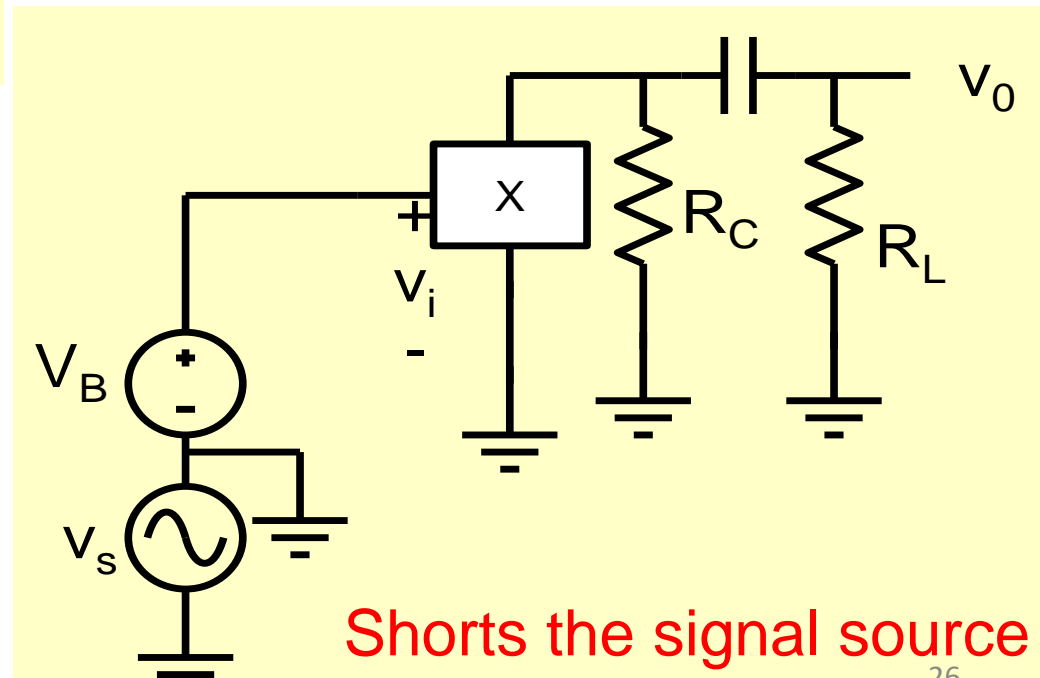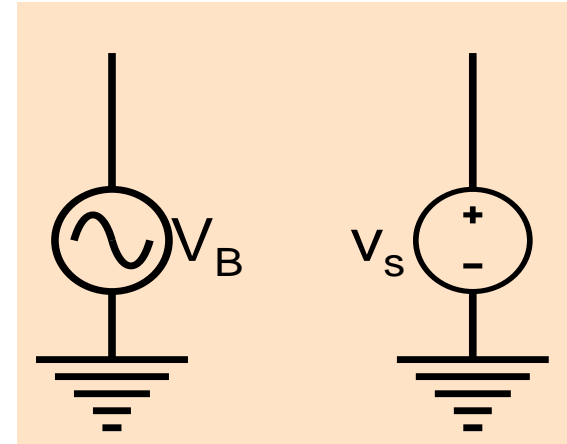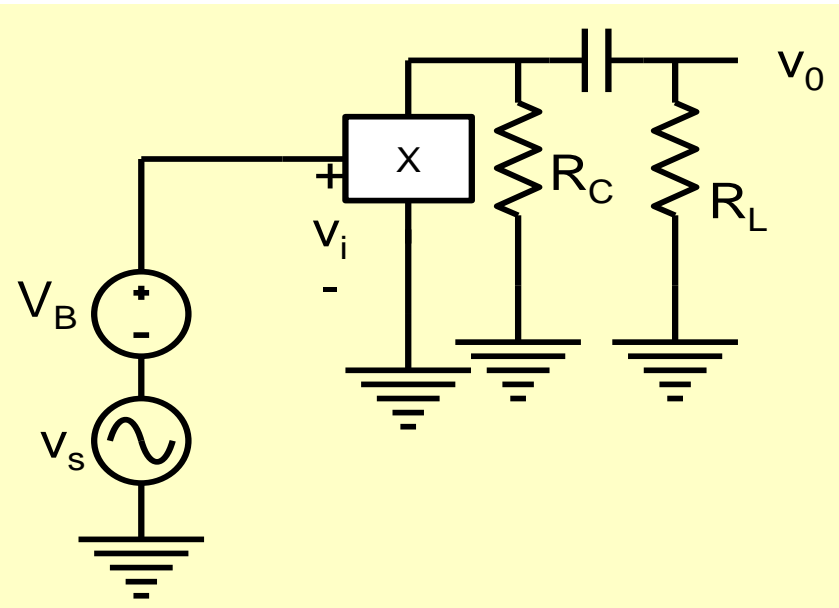
What happens if both dc voltage source and signal source have one terminal as ground?





Shorts the signal source

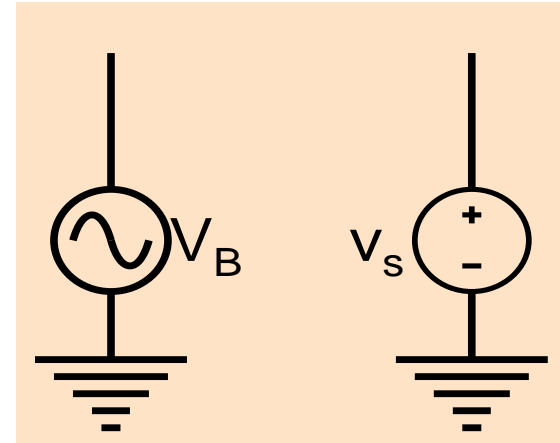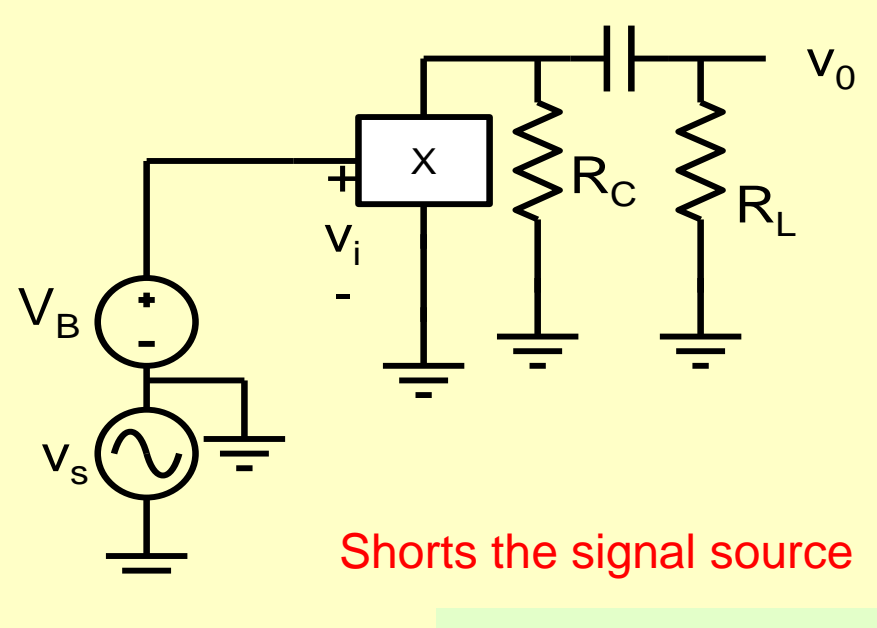



Solution

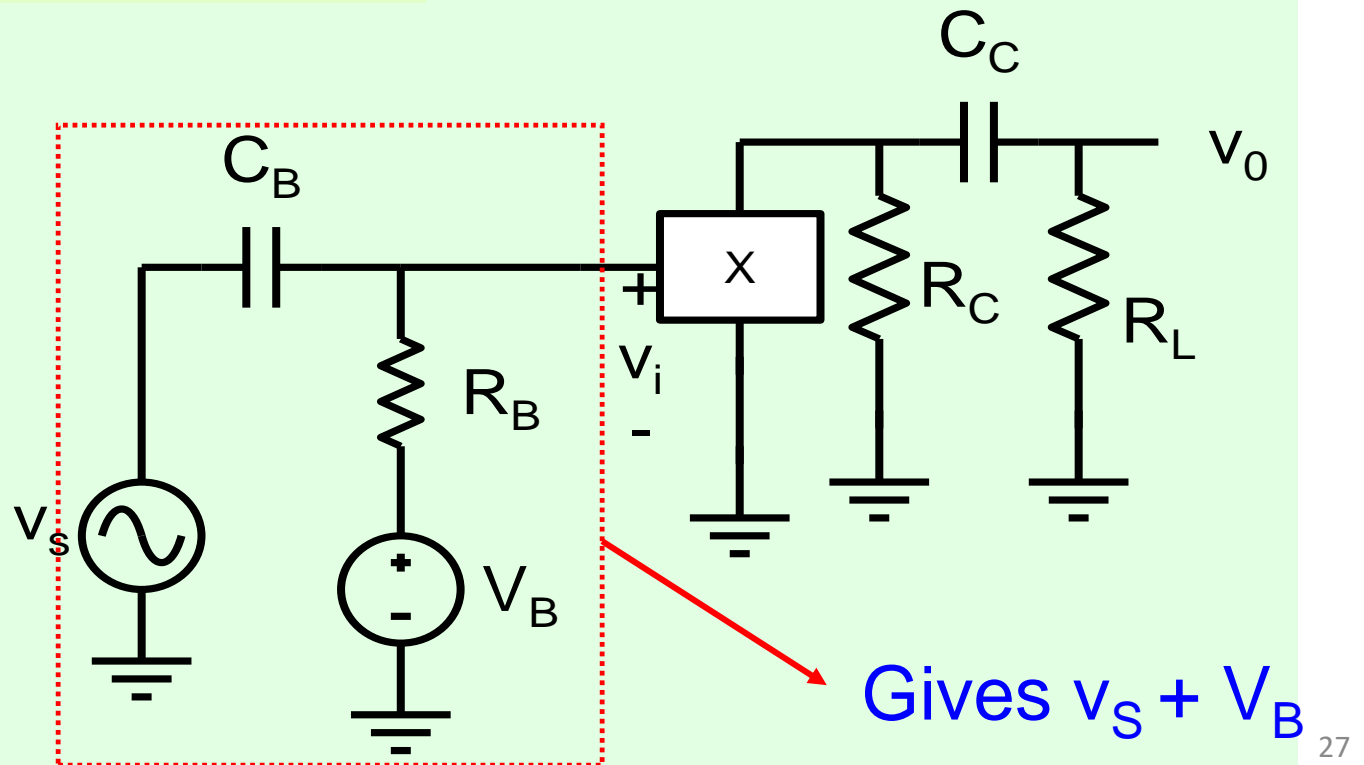

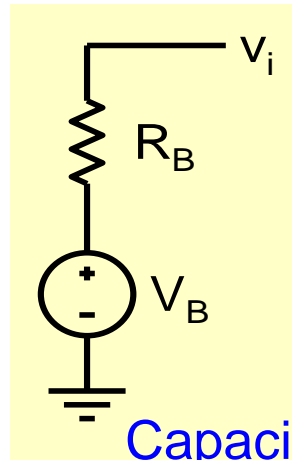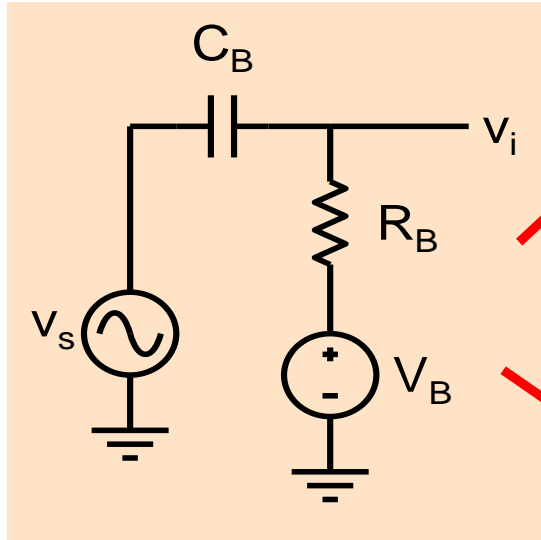

$$v_i = V_B$$

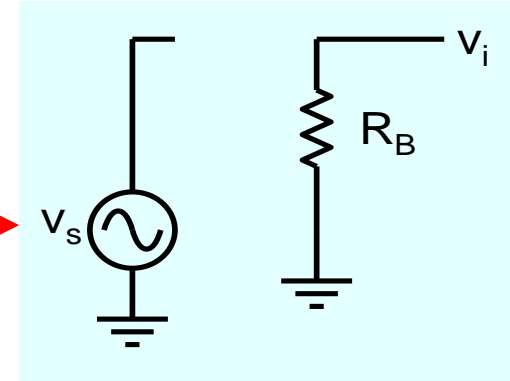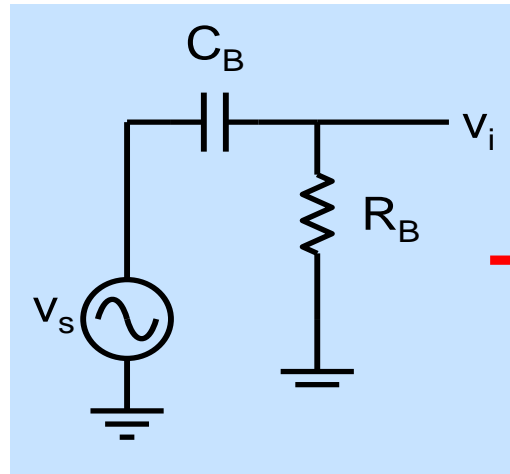Capacitor is chosen large enough so that at the signal frequency $1/j\omega C \sim 0$.



$$v_i = v_s$$

$$v_i(\text{total}) = v_s + V_B$$

Note the role of R_B

Amplifier Schematic

