

# ESc201 : Introduction to Electronics

Amit Verma  
Dept. of Electrical Engineering  
IIT Kanpur

# Recap

- Capacitors  $i = C \frac{dv}{dt}$

A capacitor under dc or steady state acts like an **open circuit**


- Inductors  $v = \frac{d\phi}{dt} = L \times \frac{di}{dt}$

An inductor under dc or steady state acts like a **short circuit**

**Circuits containing inductors or capacitors have a memory**

# Recap: Two important concepts

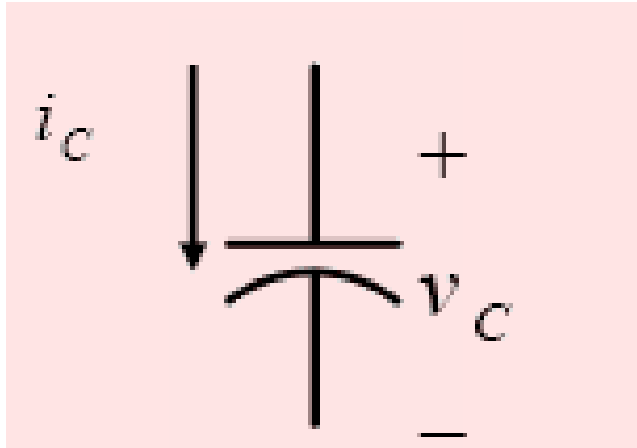
**Voltage across a capacitor cannot change instantaneously**



$$i_c = C \frac{dv_c}{dt}$$

Instantaneous change in voltage implies infinite current!

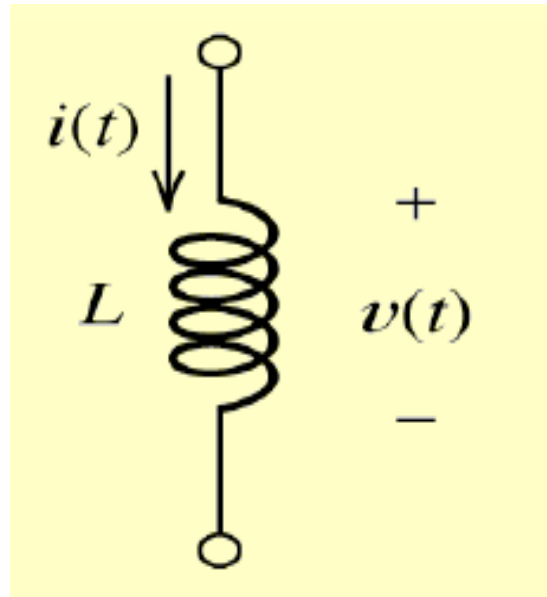**Current through an inductor cannot change instantaneously**




$$v = L \frac{di}{dt}$$

Instantaneous change in current implies infinite voltage!


# Recap

## Discharging of capacitor

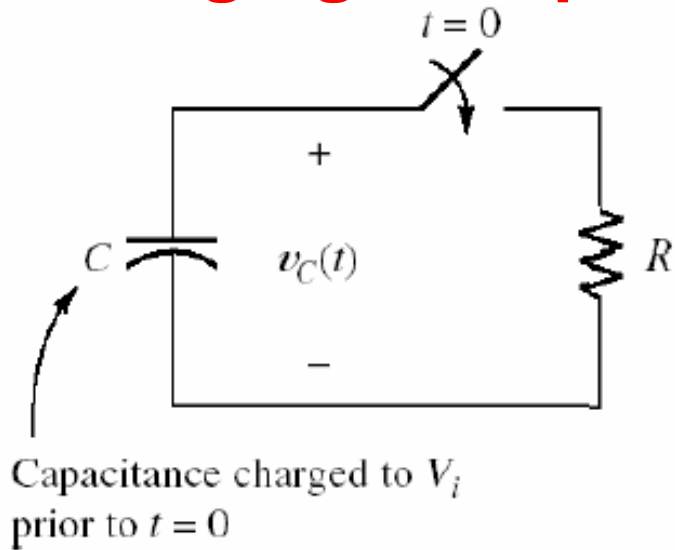


$$v_C(t) = V_i e^{-\frac{t}{RC}}$$

## Charging a capacitor

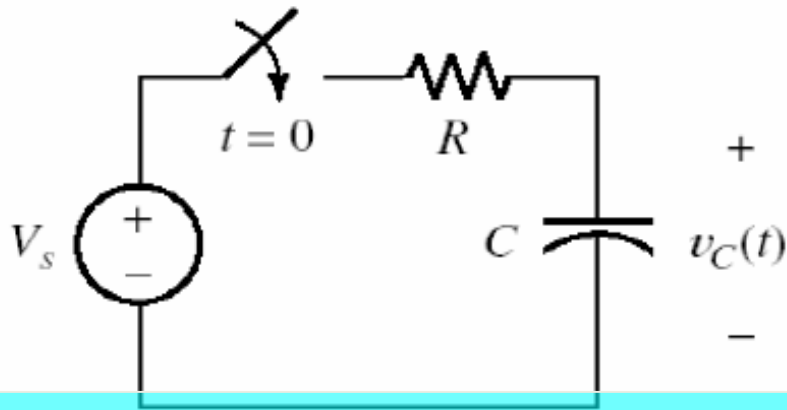

$$v_C(t) = v_C(\infty) + \{v_C(0^+) - v_C(\infty)\} e^{-\frac{t}{RC}}$$

# Recap: RL Transient Analysis

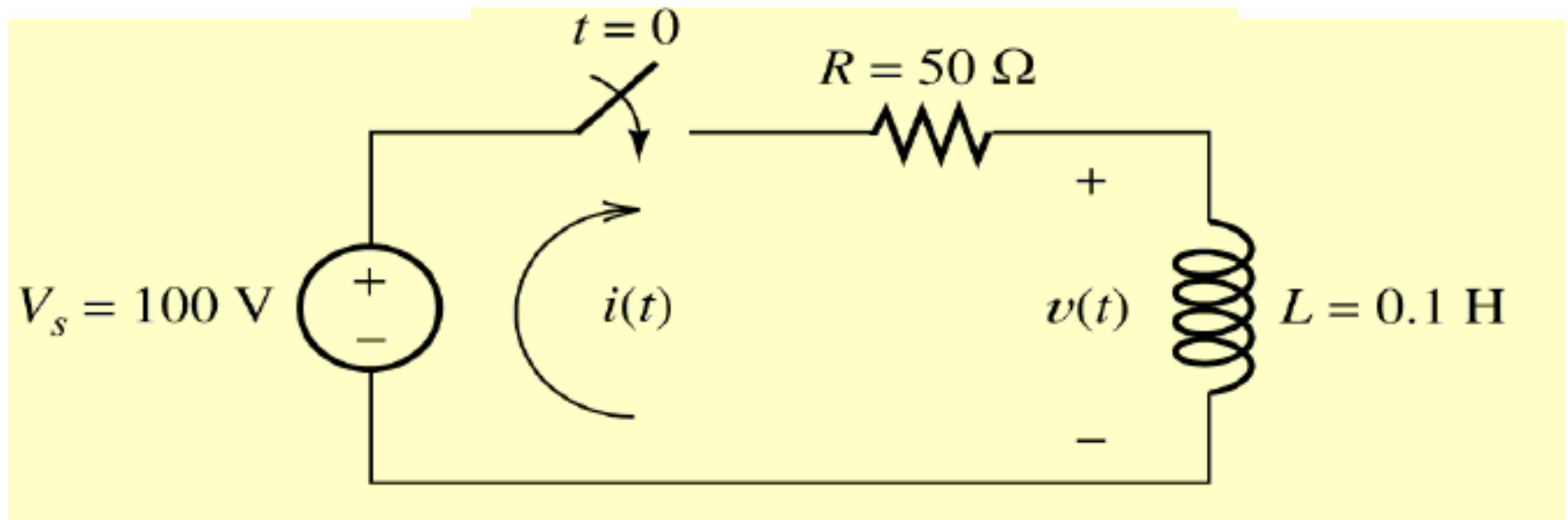


$$i(t) = i(\infty) + \{i(0) - i(\infty)\} e^{-\frac{R}{L}t}$$



$$e^{-\frac{t}{\tau}}$$


$$\text{Time Constant : } \tau = \frac{L}{R}$$

# RC Circuit

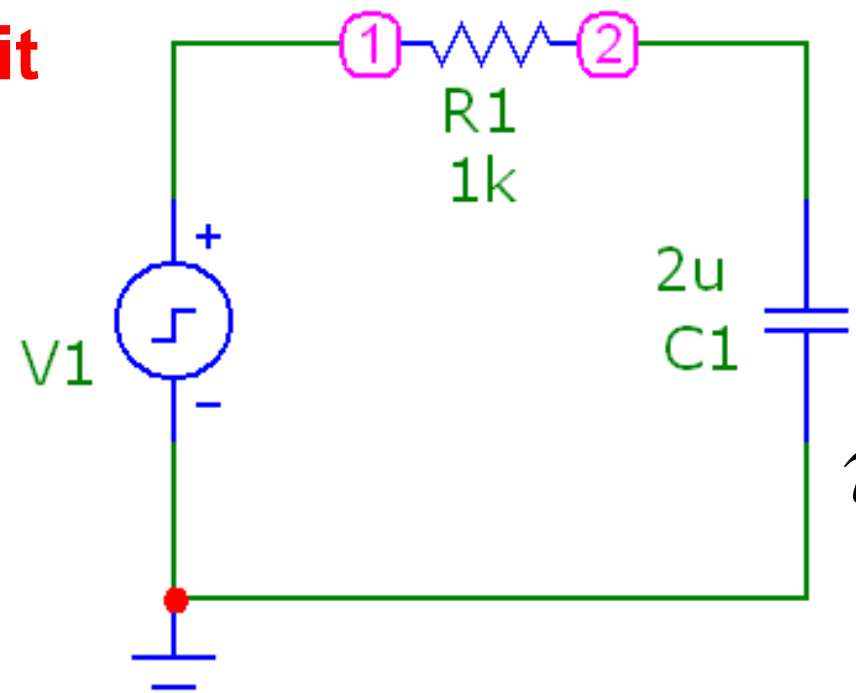

$$\tau = RC = 2 \text{ ms}$$

Input voltage

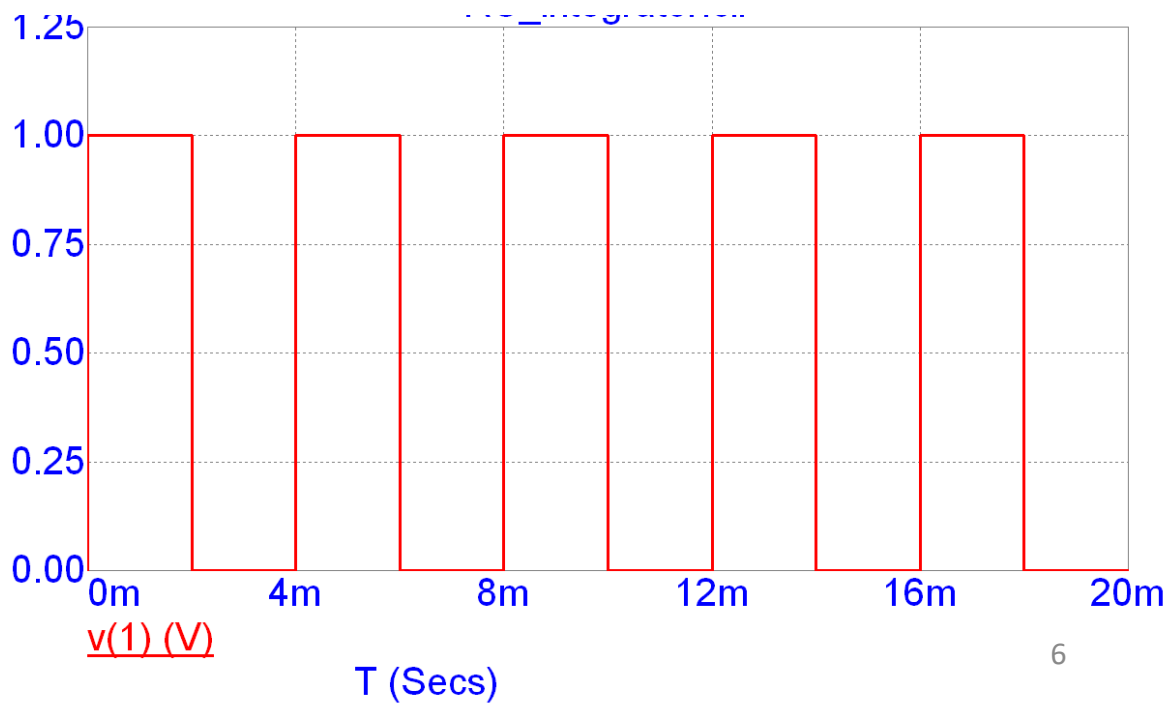

## RC Circuit


$$\tau = RC = 2 \text{ ms}$$

$$v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-\frac{t}{\tau}}$$


$$v_c(\infty) = 1V; \quad v_c(0^+) = 0;$$

$$v_c(t) = 1 - e^{-\frac{t}{2}}$$
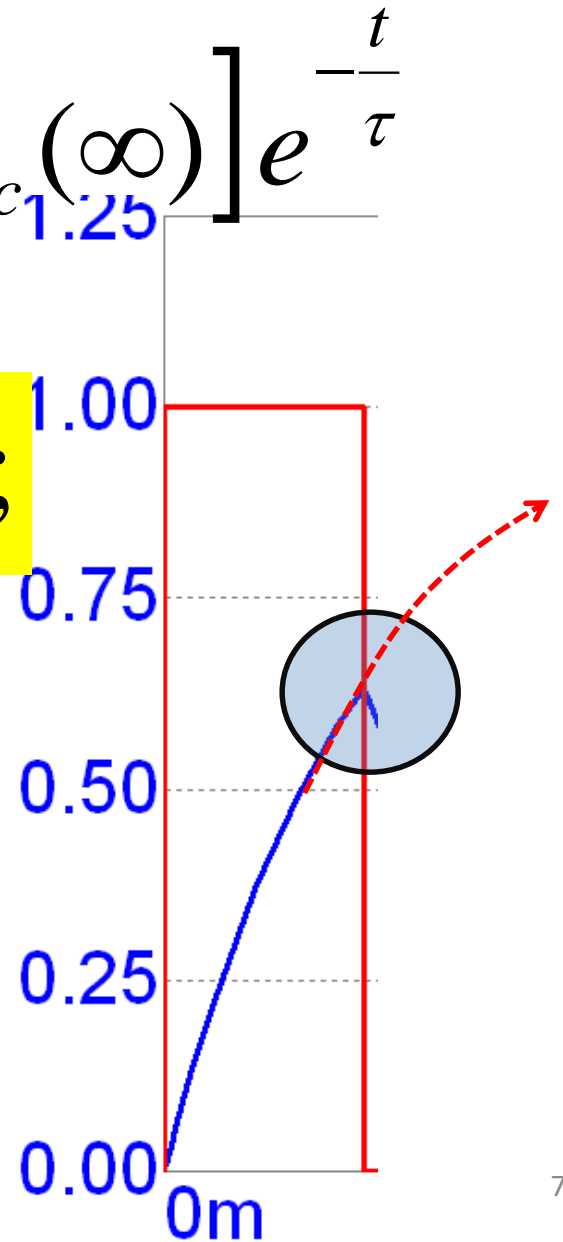
$$v_c(2) = 1 - e^{-\frac{2}{2}} = 0.63V$$



# RC Circuit

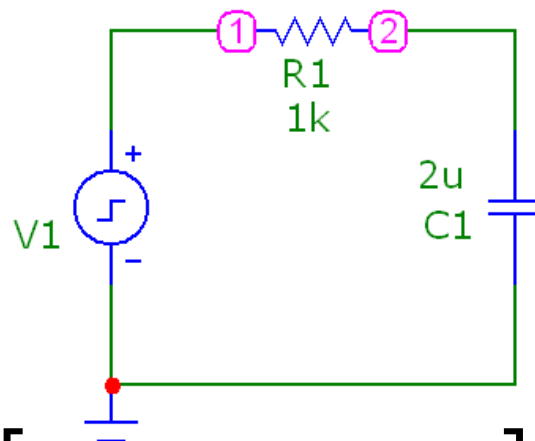

$$v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-\frac{t}{\tau}}$$


$$v_c(\infty) = 0; v_c(0^+) = 0.63V;$$

$$v_c(t) = 0.63e^{-\frac{(t-2)}{2}}; 2 \leq t \leq 4$$

$$v_c(4) = 0.63e^{-\frac{2}{2}} = 0.23V$$

time  $t$  is in ms

$$\tau = RC = 2 \text{ ms}$$

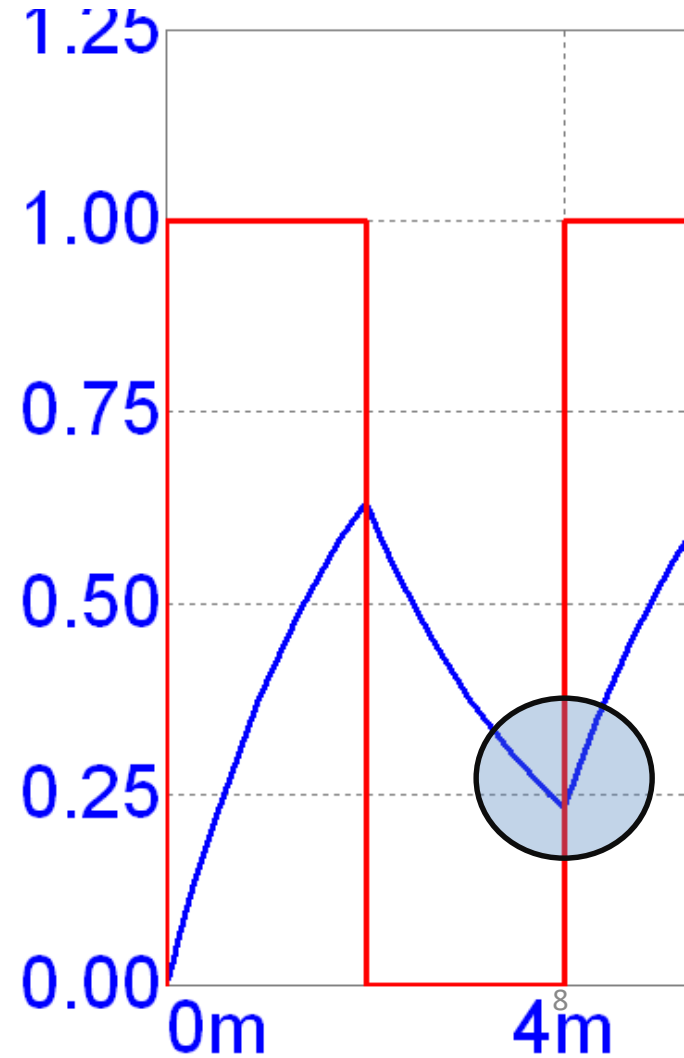





RC Circuit

$\tau = RC = 2\text{ ms}$

$t$ (ms)	$v_c(t)$ (V)
0	0
2	0.63
4	0.23
6	0.72
8	0.265
10	0.73
12	0.269
14	0.731
16	0.269

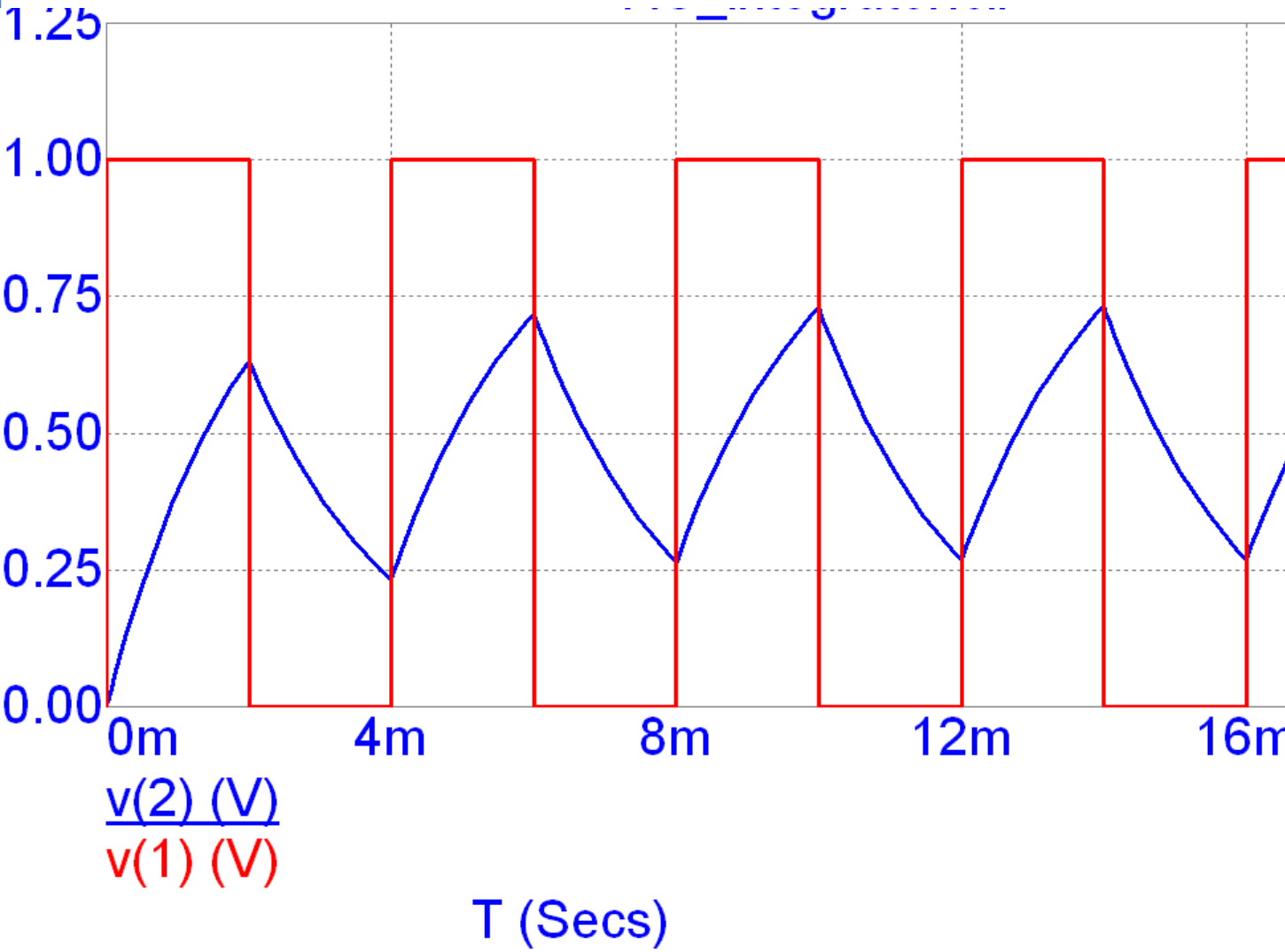


# RC Circuit – Steady State

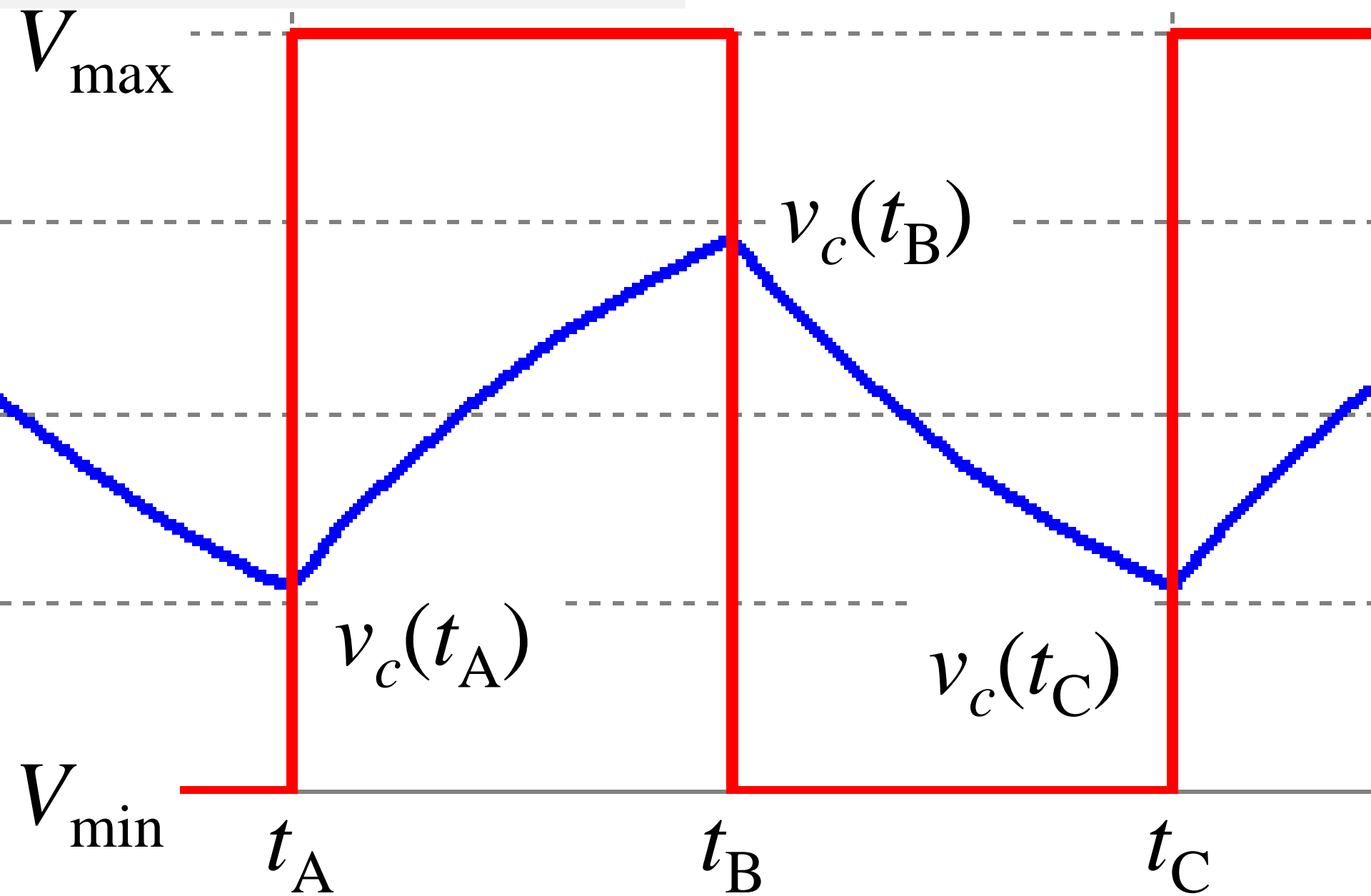

$$v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-\frac{t}{\tau}}$$


$$v_c(t) = V_{\max} + [v_c(t_A) - V_{\max}]e^{-\frac{(t-t_A)}{\tau}} \quad t_A \leq t \leq t_B$$
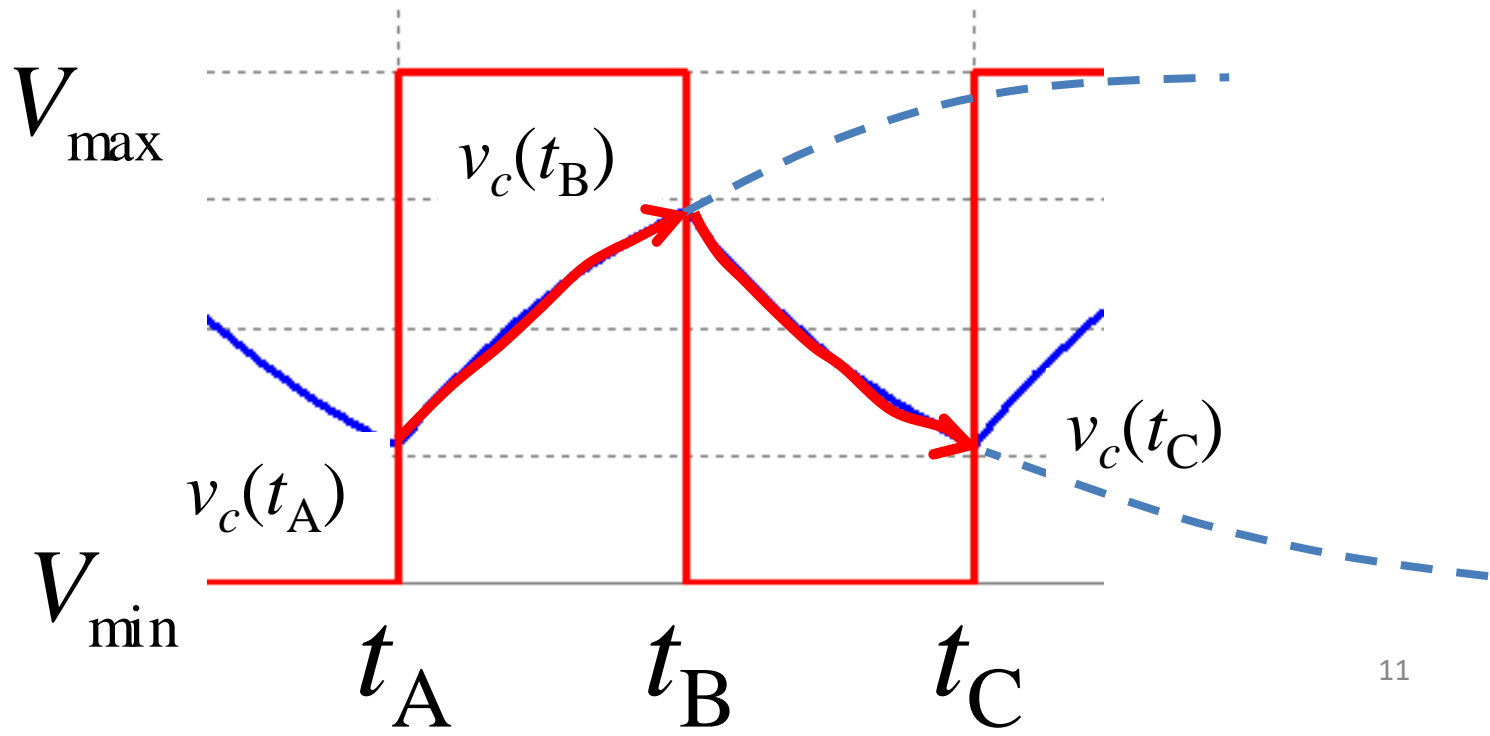
$$v_c(t) = V_{\min} + [v_c(t_B) - V_{\min}]e^{-\frac{(t-t_B)}{\tau}} \quad t_B \leq t \leq t_C$$




$$v_c(t_B) = V_{\max} + [v_c(t_A) - V_{\max}] e^{-\frac{(t_B - t_A)}{\tau}}$$
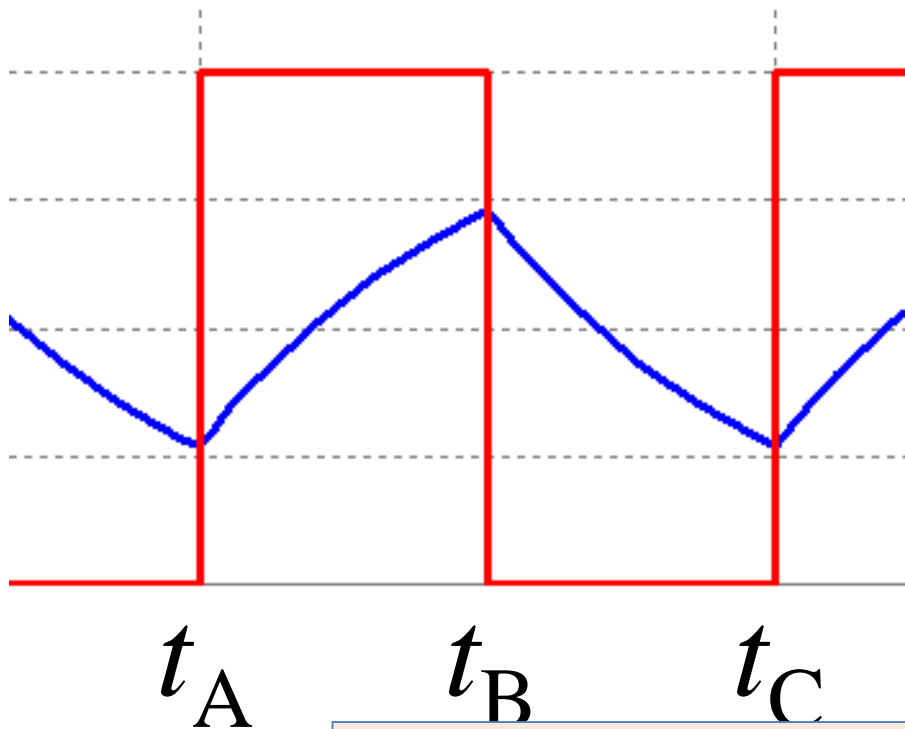
$$v_c(t_C) = V_{\min} + [v_c(t_B) - V_{\min}] e^{-\frac{(t_C - t_B)}{\tau}} = v_c(t_A)$$



$$(t_B - t_A) = (t_C - t_B) = \frac{T}{2}$$

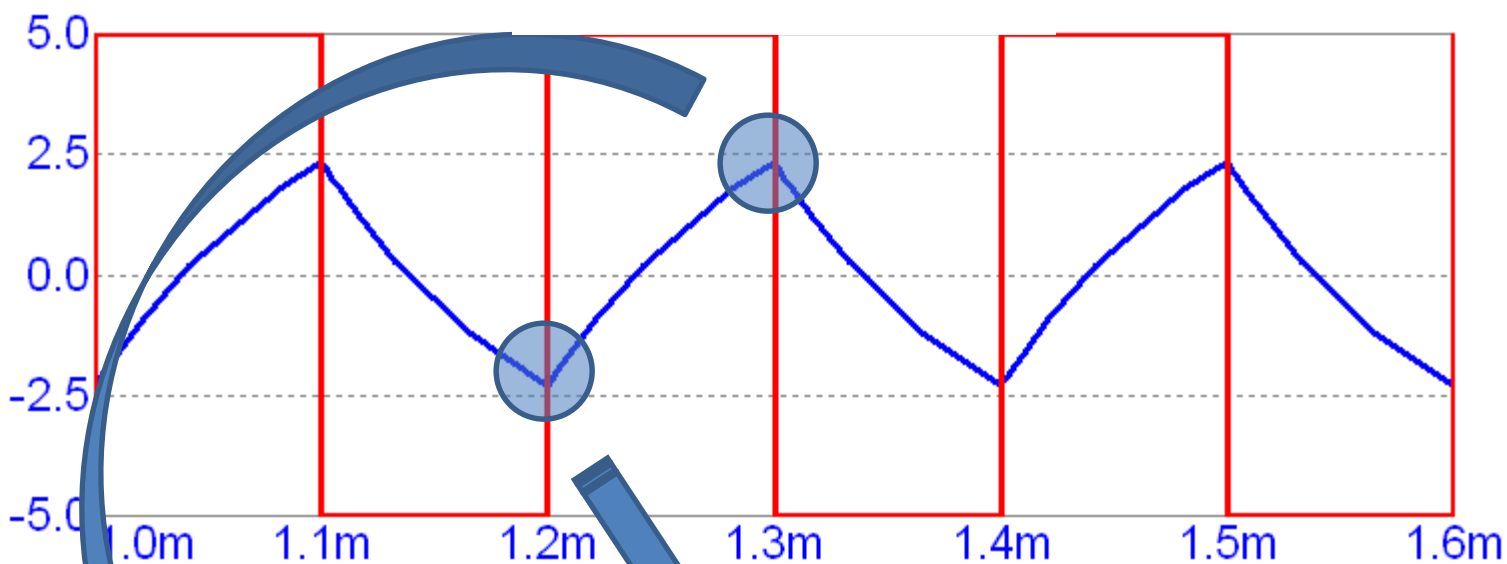Determine  $v_c(t_A)$  and  $v_c(t_B)$  in terms of  $V_{\max}$  and  $V_{\min}$







$$v_c(t_B) = V_{\max} + [v_c(t_A) - V_{\max}] e^{-\frac{(t_B - t_A)}{\tau}}$$

$$2.3 = 5 + [-2.3 - 5] e^{-\frac{0.1 \text{ ms}}{\tau}}$$





$$\tau = 0.1 \text{ ms}$$
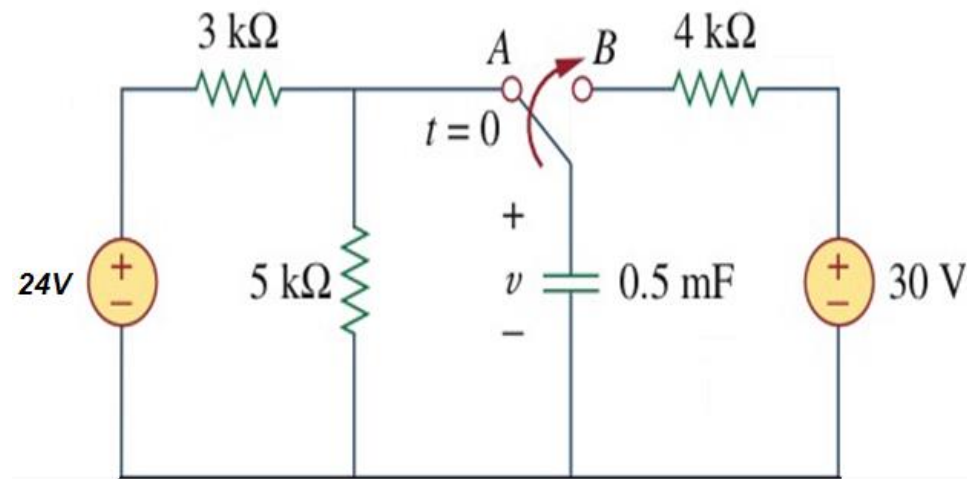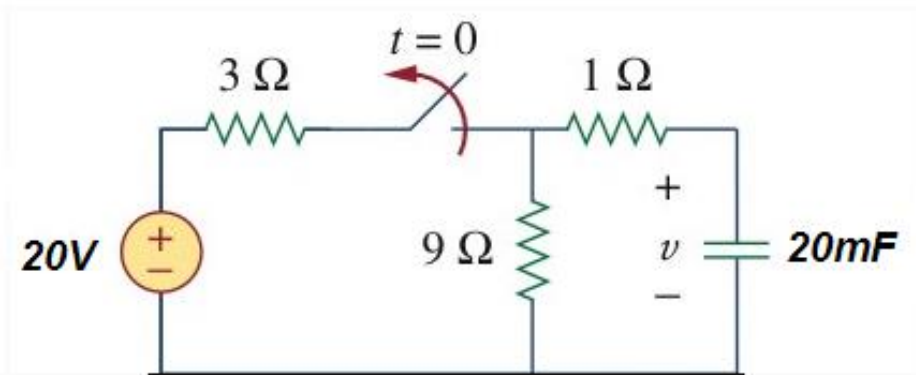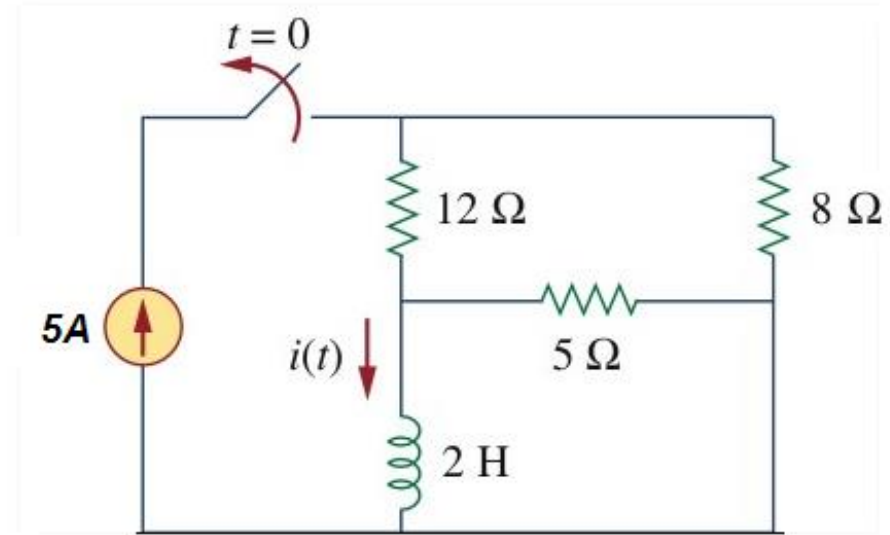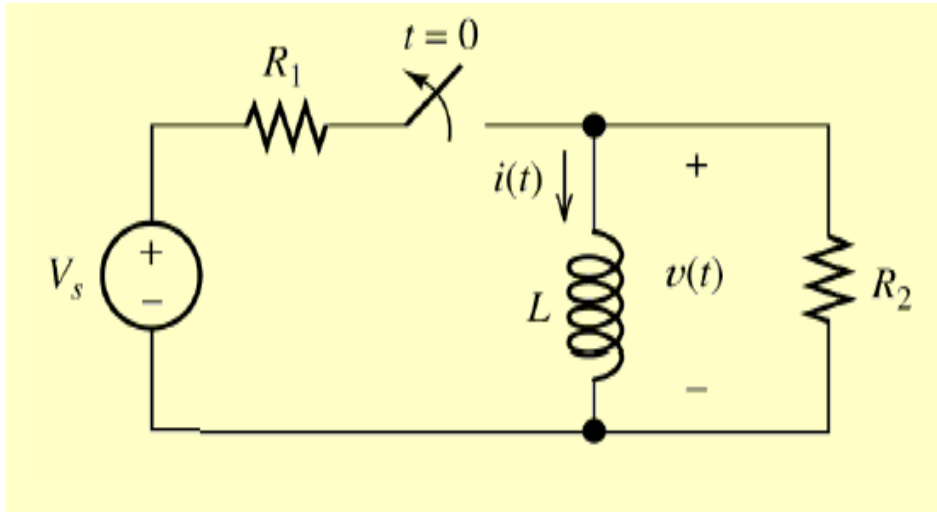
# How do we solve more complex circuits containing a single inductor or a capacitor?



# Method for circuits containing a single capacitor or inductor


Circuit for  $t > 0$

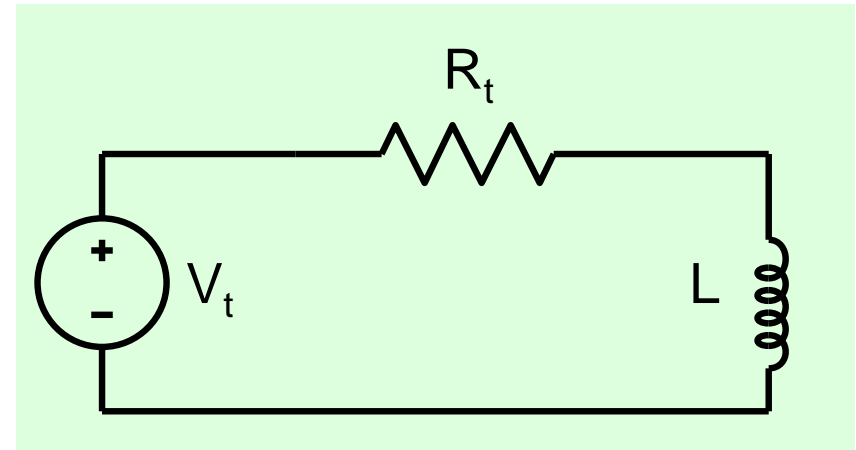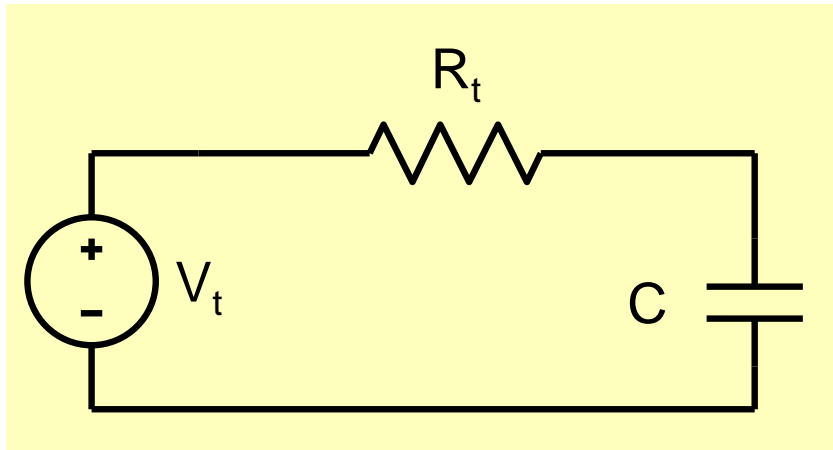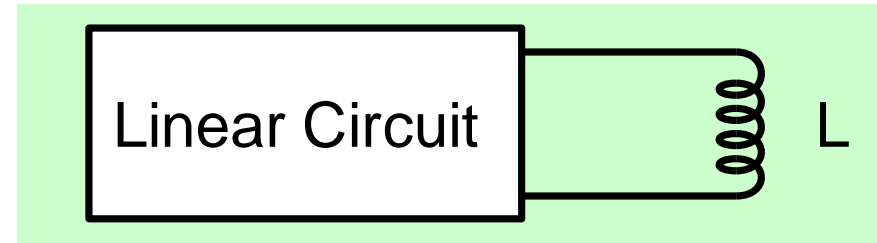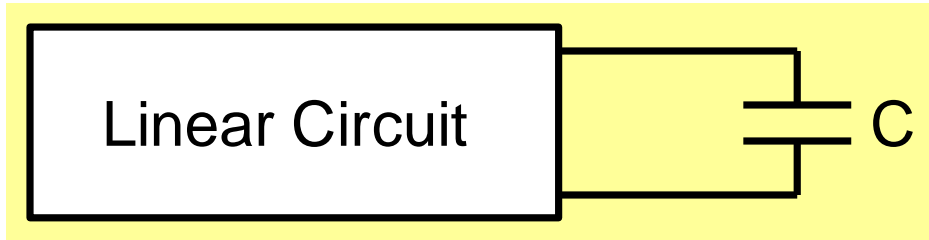


$$x(t) = x(\infty) + \{x(0^+) - x(\infty)\}e^{-\frac{t}{\tau}}$$

Where  $x$  is capacitor voltage or inductor current

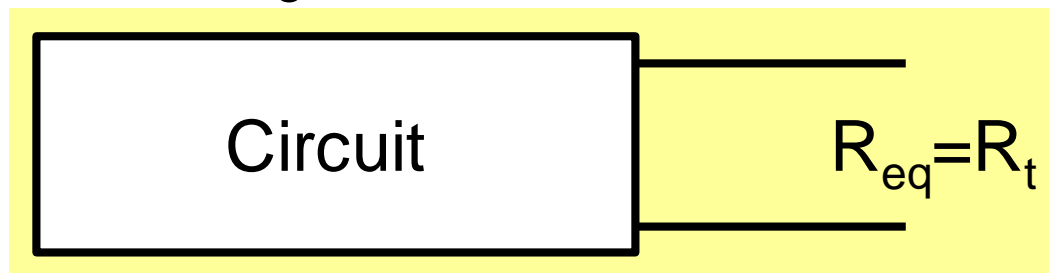
$$\tau = \frac{L}{R_{eq}} \text{ or } R_{eq}C$$



## Example-1

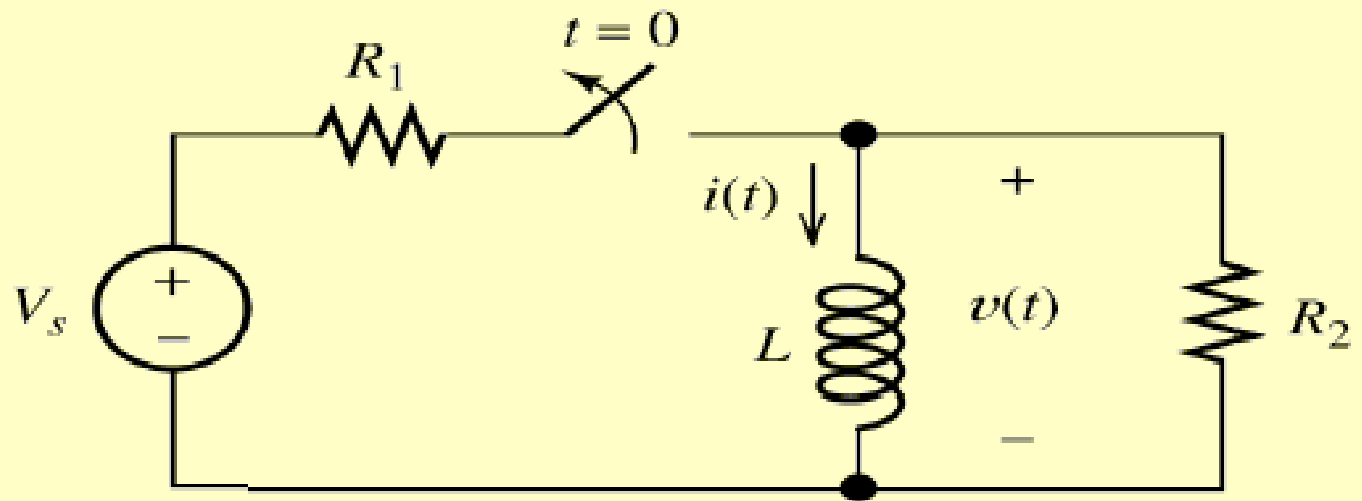

Circuit for  $t > 0$

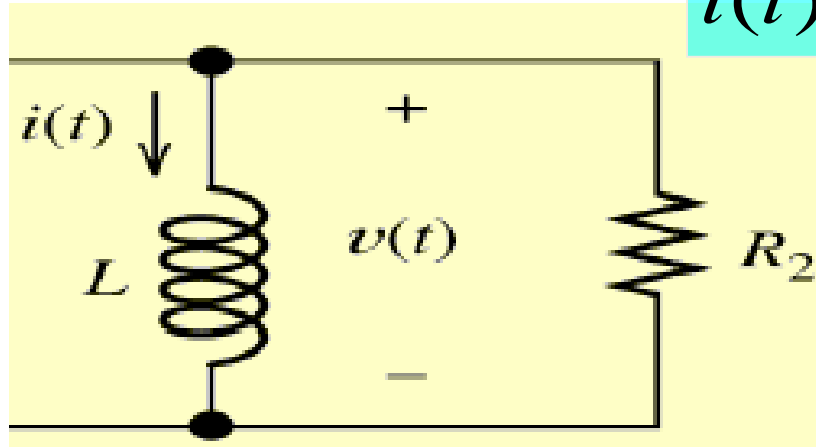

$$i(t) = i(\infty) + \{i(0^+) - i(\infty)\} \times e^{-\frac{t}{\tau}}$$

$$\tau = \frac{L}{R_2}$$


Steady state Solution:

$$i(t \rightarrow \infty) = 0$$



$$i(t) = i(0^+) \times e^{-\frac{t}{\tau}}$$



# Initial condition

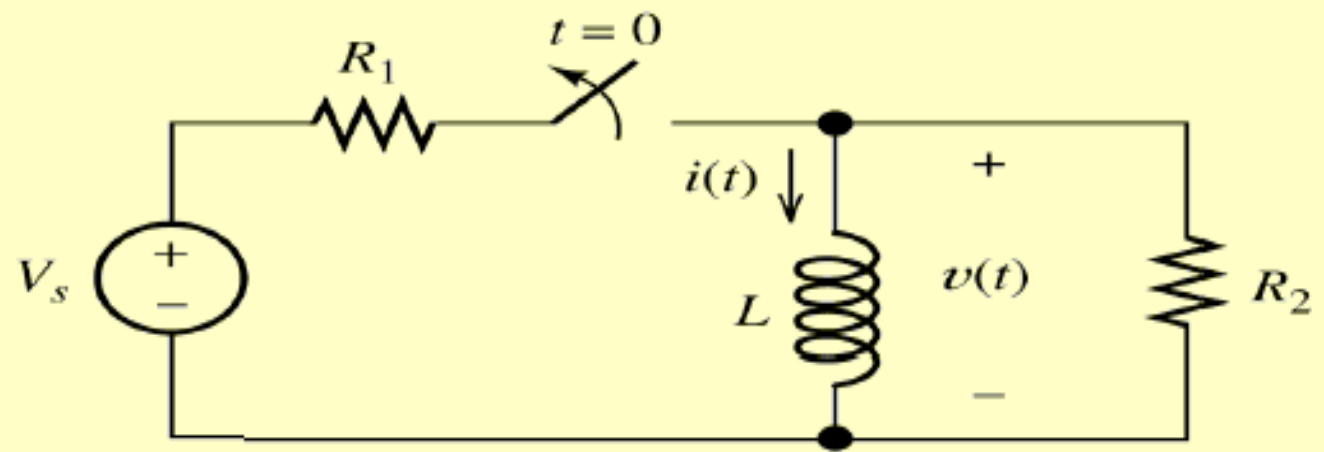


Circuit for  $t < 0$

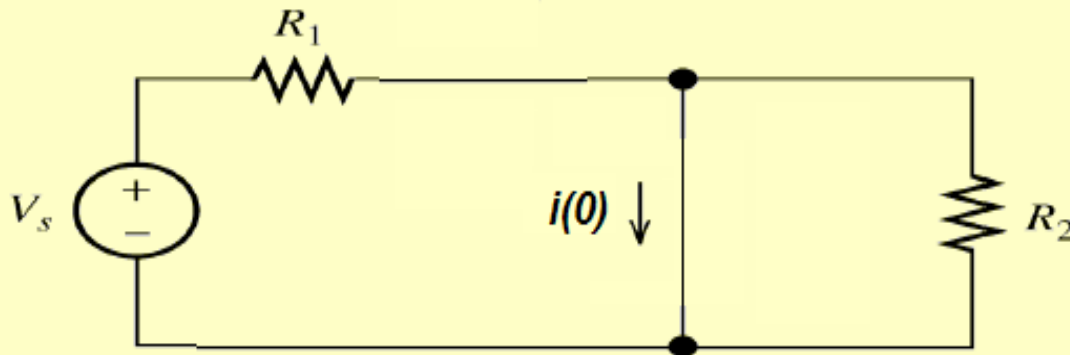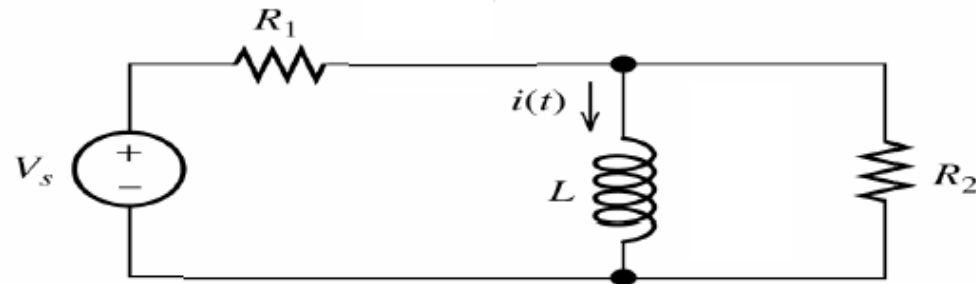



$$i(0^+) = i(0^-) = \frac{V_s}{R_1}$$

$$i(t) = \frac{V_s}{R_1} e^{-\frac{R_2}{L}t}$$

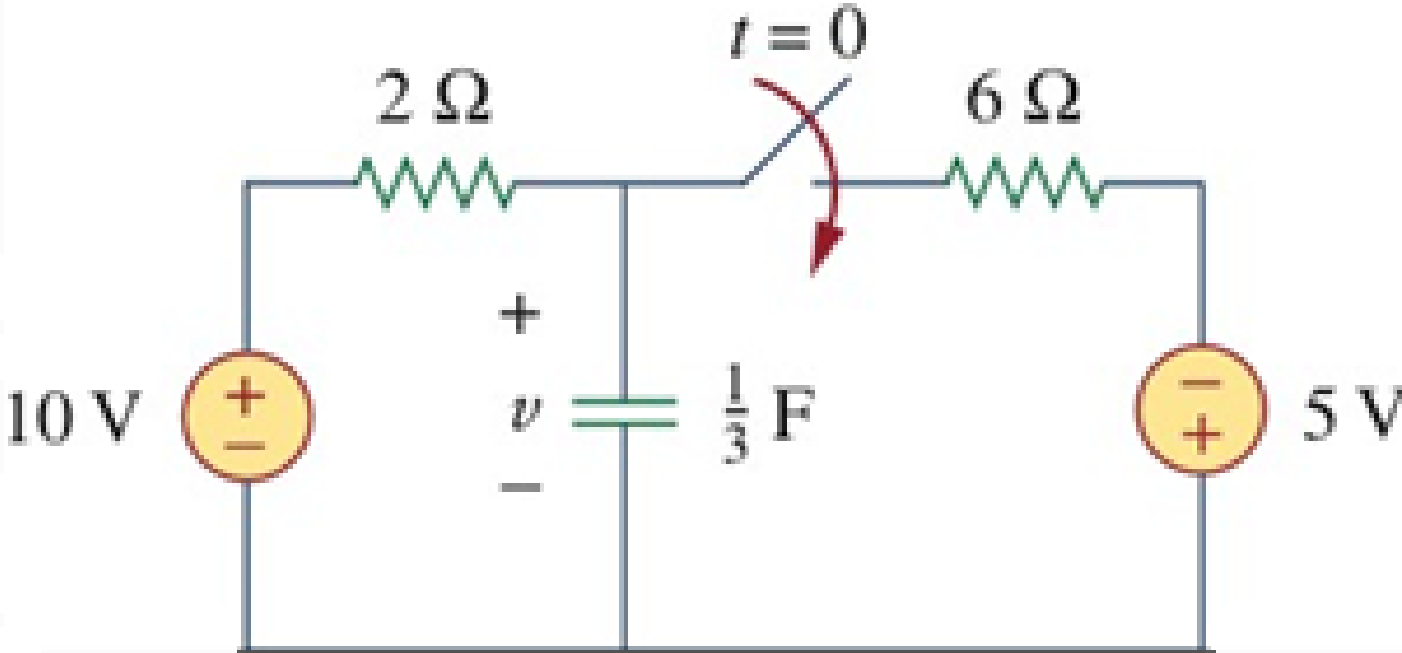Determine the capacitor voltage as a function of time.




Circuit for  $t < 0$

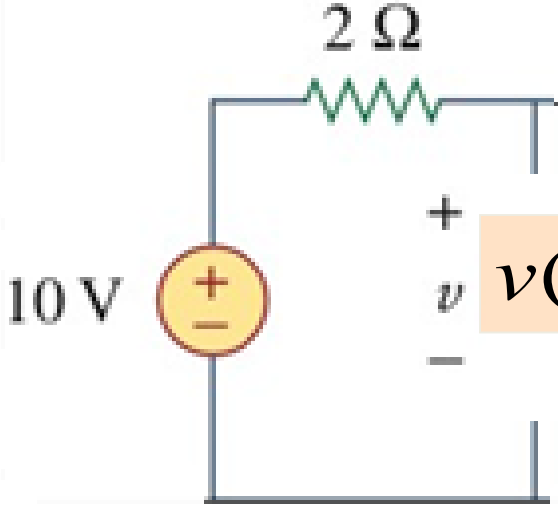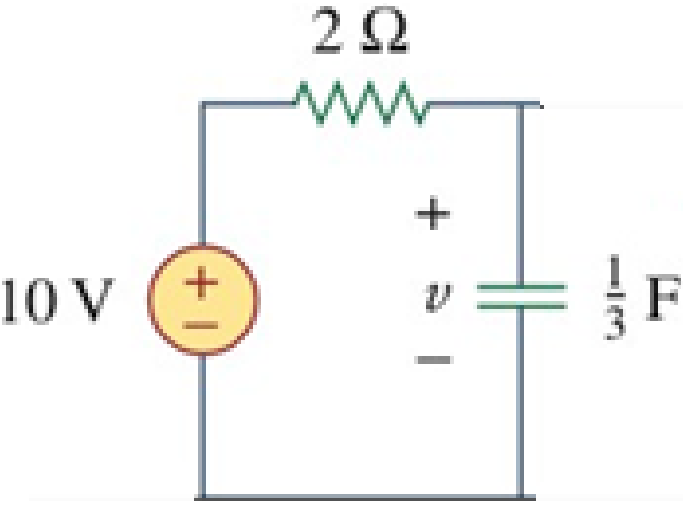


$v(0^+) = 10\text{ V}$

Circuit for  $t > 0$

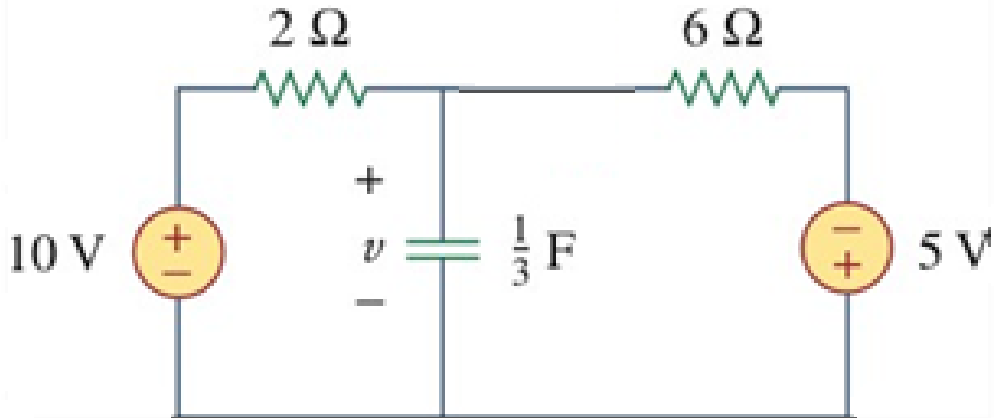


Determine the Thevenin equivalent, as seen by the capacitor:

Equivalent resistance

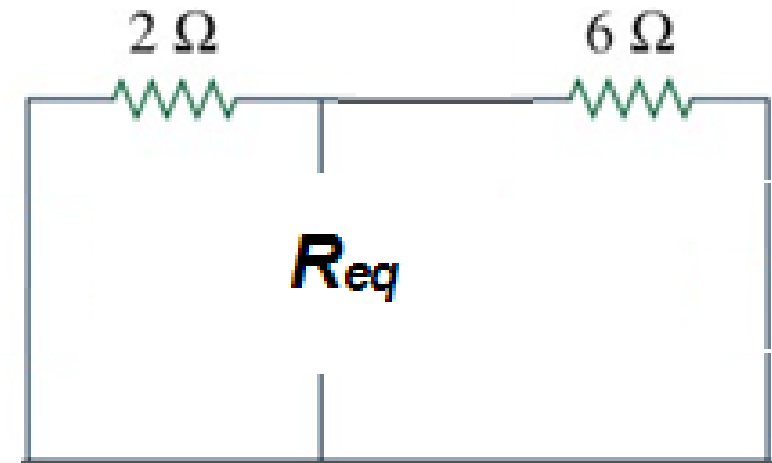

$$R_{eq} = 2 \parallel 6 = 1.5 \Omega$$

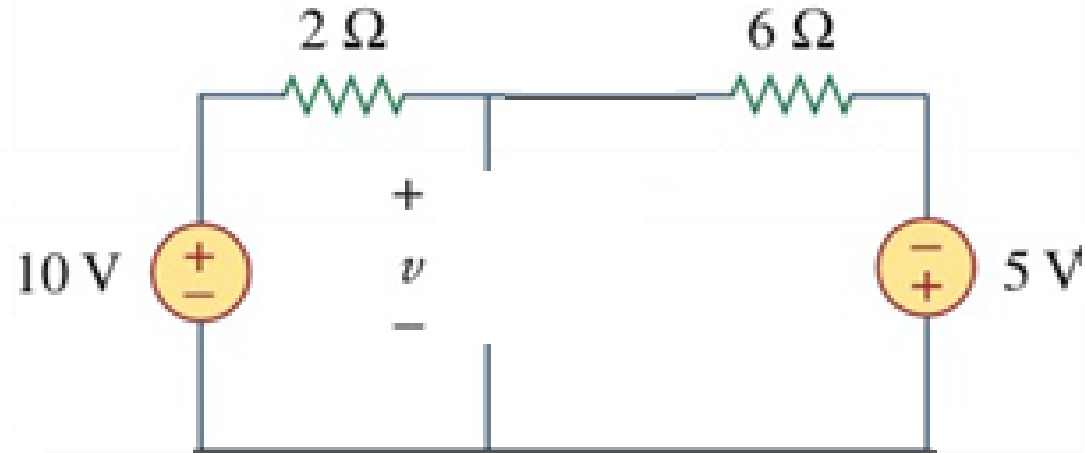We next find voltage long after closing the switch



$$v(\infty) = \frac{25}{4} \text{ V}$$

Final Solution:

$$v(t) = v(\infty) + \{v(0^+) - v(\infty)\}e^{-\frac{t}{\tau}}$$

$$v(0^+) = 10 \text{ V}$$


$$v(\infty) = \frac{25}{4} \text{ V}$$

$$\tau = C \times R_{eq} = \frac{1}{3} \times 1.5 = 0.5 \text{ s}$$


$$v(t) = \frac{25}{4} + \frac{15}{4}e^{-2t} \text{ V}$$

# How do we find voltages and currents elsewhere in the circuit?


Linear Circuit

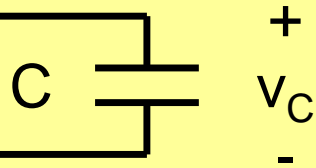


Linear Circuit

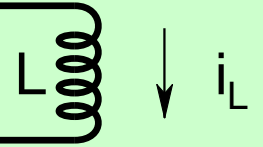


Linear Circuit

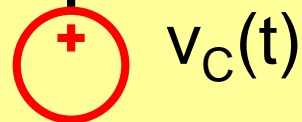

Linear Circuit

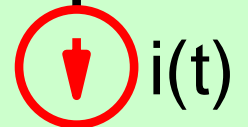

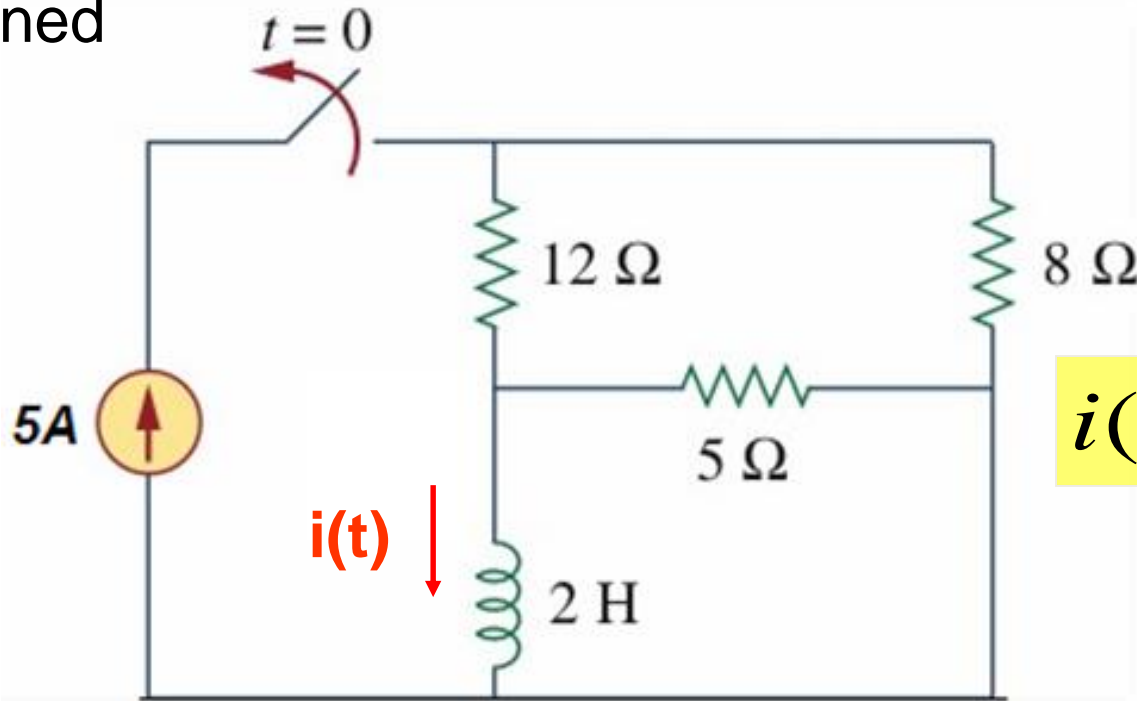Find current in  $8\Omega$  resistor as a function of time after the switch is opened



$$i(t) = 2 \times e^{-2t} \text{ A}$$


$$i(t = 0^-) = 5A \times \left( \frac{8}{12 + 8} \right) = 2A$$

No current will flow in  $5\Omega$  resistance for  $t < 0$


For  $t > 0$

$$R_{eq} = (12 + 8) \parallel 5 = 4 \quad \Omega$$
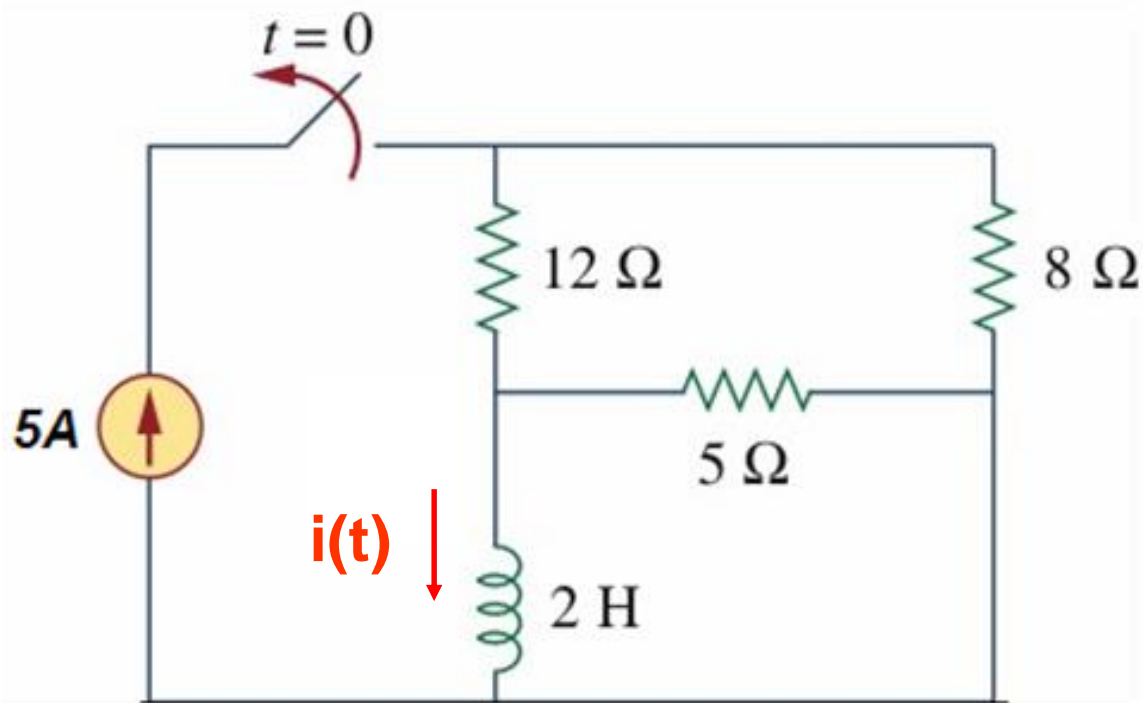
$$\tau = \frac{L}{R_{eq}} = 0.5 \text{ sec}$$





$$i(t) = 2 \times e^{-2t} \text{ A}$$

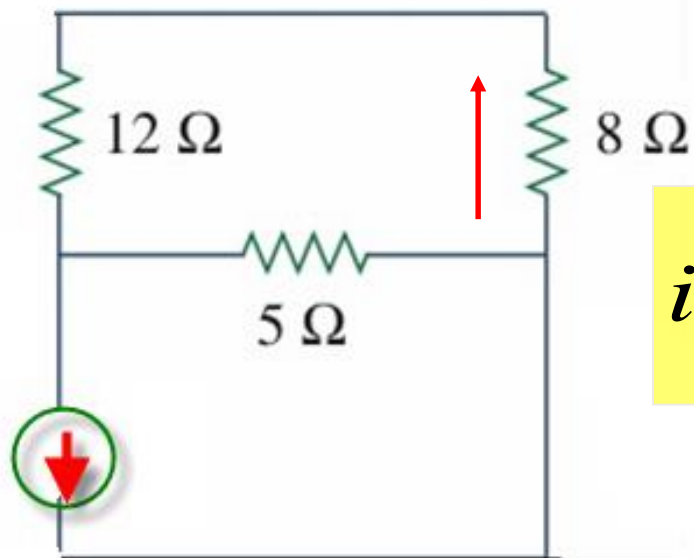

$$i_8 = i(t) \times \frac{5}{5 + 20} = 0.4 \times e^{-2t} \text{ A}$$

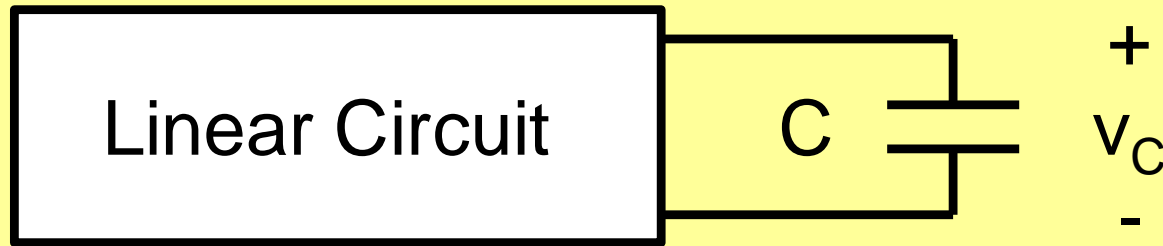
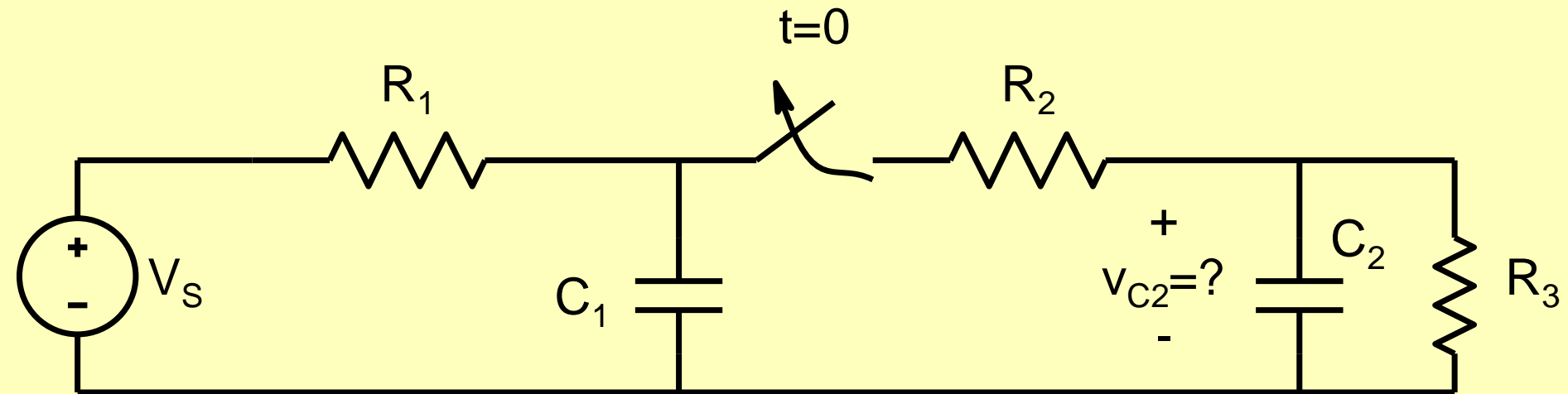
Can we solve this 2 capacitor problem using our present approach?



Circuit for  $t > 0$



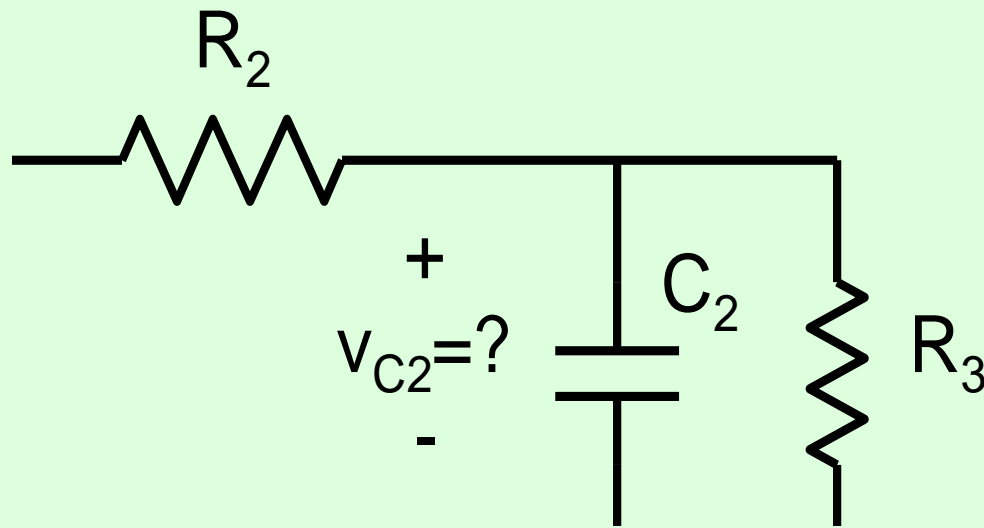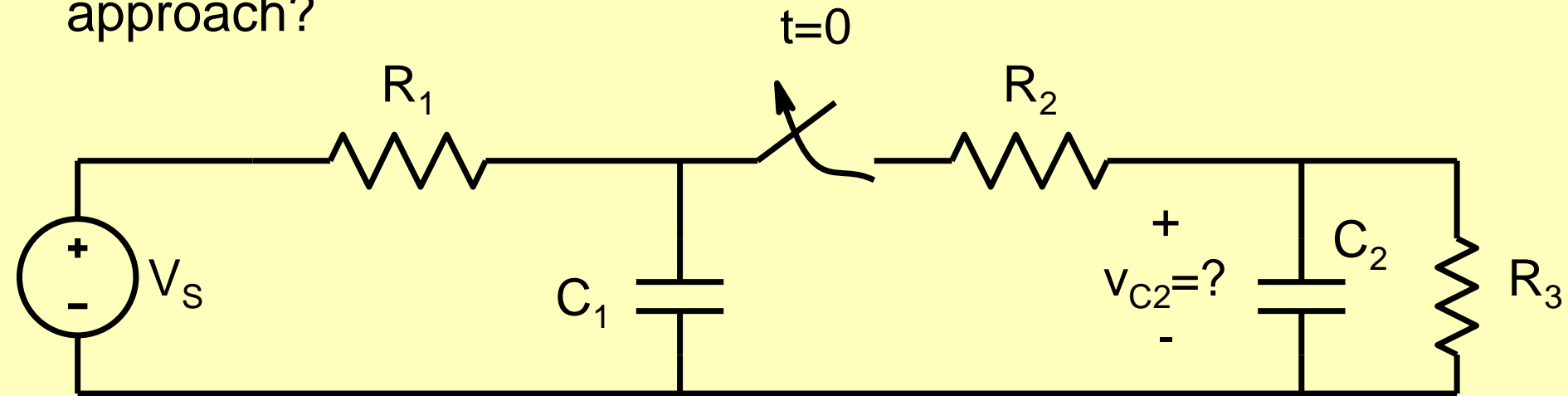Can we solve this 2 capacitor problem using our present approach?





Circuit for  $t > 0$


$$v_{c2}(0^+) = v_{c2}(0^-)$$

$$v_{c2}(t) = v_{c2}(\infty) + \{v_{c2}(0^+) - v_{c2}(\infty)\}e^{-\frac{t}{\tau}}$$

$$v_{c2}(0^+) = v_{c2}(0^-)$$

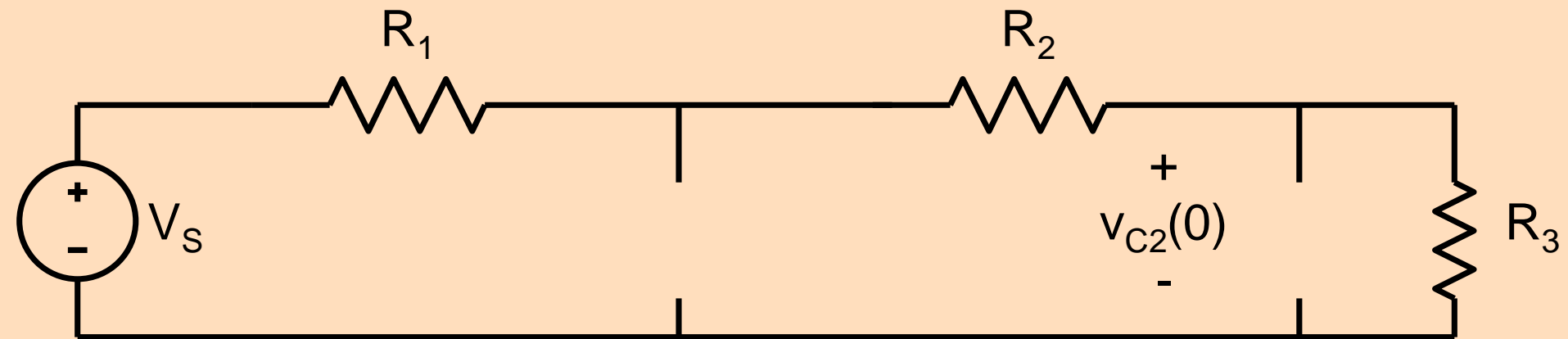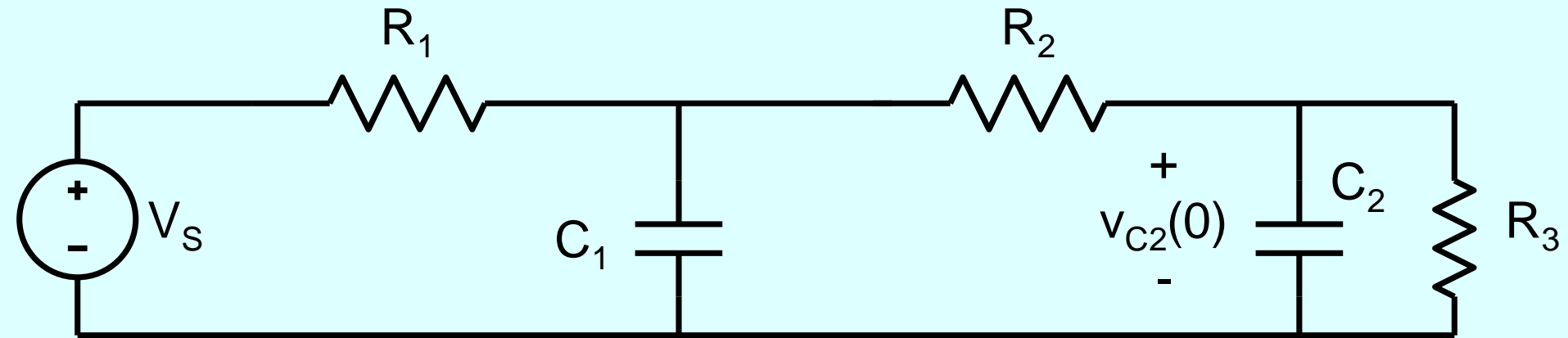


Will our approach work here?

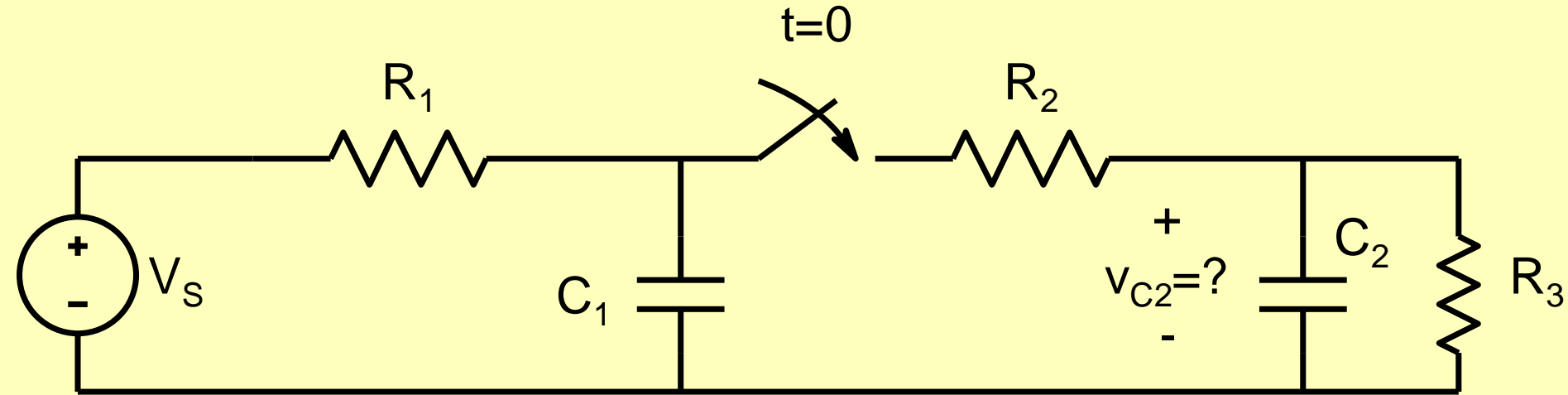

No, because circuit for  $t > 0$  has two capacitances

As long as the circuit has single capacitor or inductor for the time interval for which the analysis is being carried out, the stated approach will work fine.

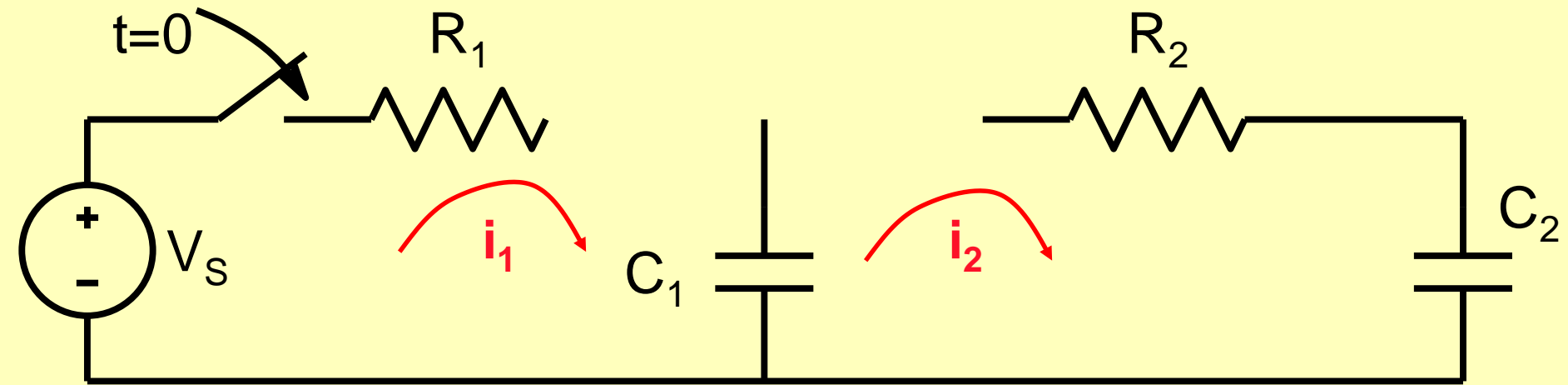What happens when there is more than one storage element?



$$V_S = i_1 R_1 + v_{C1} \quad (1)$$

$$v_{C1} = i_2 R_2 + v_{C2} \quad (2)$$

$$i_1 - i_2 = C_1 \frac{dv_1}{dt} \quad (3)$$

$$i_2 = C_2 \frac{dv_2}{dt} \quad (4)$$

$$R_1 R_2 C_1 C_2 \frac{d^2 v_{C2}}{dt^2} + (R_1 C_1 + R_1 C_2 + R_2 C_2) \frac{dv_{C2}}{dt} + v_{C2} \stackrel{28}{=} V_S$$