

ESC201A Assignment 9

Instructor Abhishek Gupta

2023-2024 Semester I

Topics

Truth Tables, Boolean Expressions, Minimization

Questions

1. Show that the Boolean expression $x + \bar{x} \cdot y$ is equivalent to $x + y$ using basic postulates and theorems of Boolean algebra.

$$\begin{aligned} & x + \bar{x} \cdot y \\ &= (x + \bar{x}) \cdot (x + y) \\ &= 1 \cdot (x + y) \\ &= x + y \end{aligned}$$

2. Reduce the following expressions to a minimum number of literals using basic postulates and theorems of Boolean algebra.

(a) $f = (x + y) \cdot (\bar{y} + \bar{x})$

(b) $f = ABCD + \bar{A}BD + AB\bar{C}D$


$$\begin{aligned} \therefore (a) \quad f &= (x + y) \cdot (\bar{y} + \bar{x}) \\ &\Rightarrow f = x\bar{y} + x\bar{x} + y\bar{y} + y\bar{x} \\ &\Rightarrow f = x\bar{y} + y\bar{x} \end{aligned}$$

$$\begin{aligned} (b) \quad f &= ABCD + \bar{A}BD + AB\bar{C}D \\ &\Rightarrow f = ABD(C + \bar{C}) + \bar{A}BD \\ &\Rightarrow f = ABD + \bar{A}BD \\ &\Rightarrow f = BD(A + \bar{A}) \\ &\Rightarrow f = BD \end{aligned}$$

3. Consider four-input function $F(A, B, C, D)$ that outputs 1 whenever an odd number of its inputs are 1, (a) construct the truth table (b) write down the Boolean expressions, present an implementation of

the function using two-input XOR gate

A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

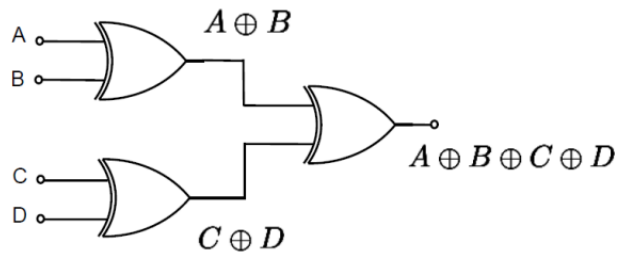

4. Four switches operate a lamp as follows: the lamp lights up if switches 1,3 and 4 are closed and switch 2 is open, or if 2, 4 are closed and 3 is open, or if all the switches are kept closed. Express this as a boolean function in a standard sum of product form and solve it using k- map. (Use bit '1' when switch is closed and bit '0' when switch is open).

let four switches are represented by w, x, y, z
 For closed switch variable will have value 1 and for open switch variable will have value 0.

1, 3, 4 closed ; 2 open $\rightarrow w \bar{x} y z$

2, 4 closed ; 3 open $\rightarrow x \bar{y} z$

All closed $\rightarrow wxyz$

$w \backslash x \ y \ z$	00	01	11	10
00	0	0	0	0
01	0	1	0	0
11	0	1	1	0
10	0	0	1	0

$$f = x \bar{y} z + w y z$$

5. Obtain the truth table for the following function: $(x \cdot y + z)(y + x \cdot z)$ and write it as sum of products (SOP) and product of sums (POS).

$$f = (x \cdot y + z) \cdot (y + x \cdot z)$$

x	y	z	$x \cdot y + z$	$y + x \cdot z$	f
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	0	1	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

SOP: $f = \bar{x}yz + x\bar{y}z + xy\bar{z} + xyz$

POS: $f = (x+y+z)(x+y+\bar{z})(x+\bar{y}+z)(\bar{x}+y+z)$

6. Simplify the following 4-variable functions into sum-of-products form using K-map.

a. $\Sigma(1,5,6,7,14)$

$\Sigma(1,5,6,7,14)$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	00 0	01 1	11 3	10 2
$\bar{A}B$	01 4	15 5	17 7	16 6
AB	11 12	13	15 15	14 14
$A\bar{B}$	10 8	9	11 11	10

$$\bar{A}\bar{C}D + BC\bar{D} + \bar{A}BD$$

$$\bar{A}\bar{C}D + BC\bar{D} + \bar{A}BC$$

there are two answers possible.

b. $\Sigma(0,4,6,8)$

$\Sigma(0,4,6,8)$

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	00 0	01 1	11 3	10 2
$\bar{A}B$	01 4	05 5	17 7	16 6
AB	11 12	13	15 15	14
$A\bar{B}$	10 8	09 9	11 11	10

$$\bar{B}\bar{C}\bar{D} + \bar{A}B\bar{D}$$

c. $\Sigma(0,1,4,6,8,9,14)$

$$\Sigma(0,1,4,6,8,9,14)$$

		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
		00	01	11	10
$\bar{A}\bar{B}$	00	1 ₀	1	3	2
$\bar{A}B$	01	1	5	7	1 ₆
AB	11	12	13	15	1 ₁₄
$A\bar{B}$	10	1 ₈	1 ₉	11	10

$$\bar{B}\bar{C} + \bar{A}B\bar{D} + BC\bar{D}$$

$$\bar{B}\bar{C} + \bar{A}\bar{C}\bar{D} + BC\bar{D}$$

d. $\Sigma(1,4,7,11,13,14)$

		$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
		00	01	11	10
$\bar{A}\bar{B}$	00	0	1 ₁	3	2
$\bar{A}B$	01	1 ₄	5	1 ₇	6
AB	11	12	1 ₁₃	15	1 ₁₄
$A\bar{B}$	10	8	9	1 ₁₁	10

$$\bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD$$

$$+ A\bar{B}CD + AB\bar{C}D + ABC\bar{D}$$

This cannot be minimized any further.

7. Simplify the following 4-variable functions into product-of-sums form using K-map

a. $\Pi(1,3,5,7,13,15)$

x_1x_2 \ x_3x_4	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	1	0	0	1
10	1	1	1	1

$$F = (x_1 + \bar{x}_4)(\bar{x}_2 + \bar{x}_4)$$

b. $\Pi(1,3,6,9,11,12,14)$

x_1x_2 \ x_3x_4	00	01	11	10
00	0	0		
01				0
11	0			0
10	0	0		

$$F = (x_2 + \bar{x}_4)(\bar{x}_1 + \bar{x}_2 + x_4)$$

$$(\bar{x}_2 + \bar{x}_3 + x_4)$$

c. $\Pi(1,3,5,7,9,11,12,13,14,15,)$

$x_1 x_2$ \ $x_3 x_4$	00	01	11	10
00		0	0	
01		0	0	
11	0	0	0	0
10		0	0	

$$F = (\bar{x}_1 + \bar{x}_2)(\bar{x}_4)$$

d. $\Pi(0,1,3,4,5,7,12,13,15)$

$x_1 x_2$ \ $x_3 x_4$	00	01	11	10
00	0	0	0	
01	0	0	0	
11	0	0	0	
10				

$$F = (x_1 + x_3)(x_1 + \bar{x}_4)(\bar{x}_2 + x_3)(\bar{x}_2 + \bar{x}_4)$$


8. Design a combinational circuit with 3 inputs and 1 output

(a) The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise

x	y	z	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

x \ $y z$	00	01	11	10
0	1	1		1
1				

$$F = \bar{x}\bar{y} + \bar{x}\bar{z}$$

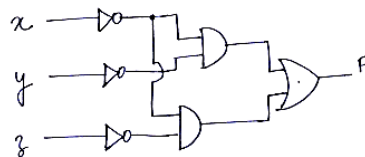

(b) The output is 1 when the binary value of inputs is an odd number.

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

x	yz			
	00	01	11	10
0		1	1	
1		1	1	

$$F = z$$