

ESC201A Assignment 2

Instructor Abhishek Gupta


2023-2024 Semester I

Topics


Superposition, Nodal/Mesh analysis, Thevenin/Nortan equivalent, Power

Questions

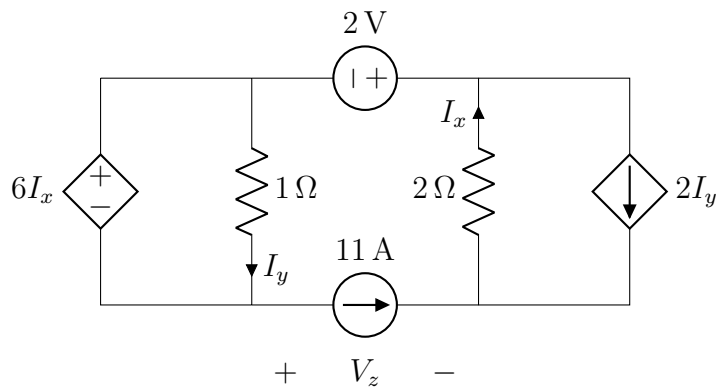
1. Determine I_x , I_y and V_z using superposition:



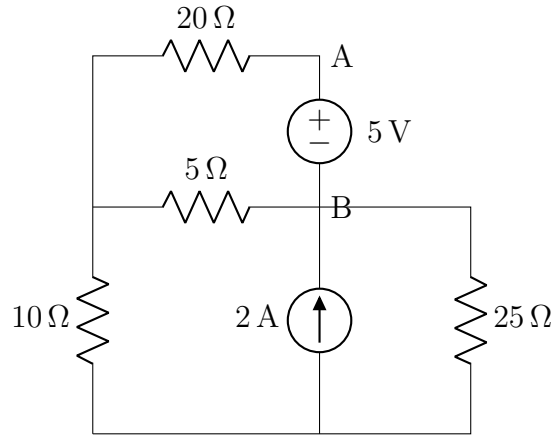
2. Determine the power supplied by the 5V source using
 - (a) Mesh analysis
 - (b) Nodal analysis
 - (c) Superposition principle
 - (d) Thevenin's equivalent circuit between terminals A and B.



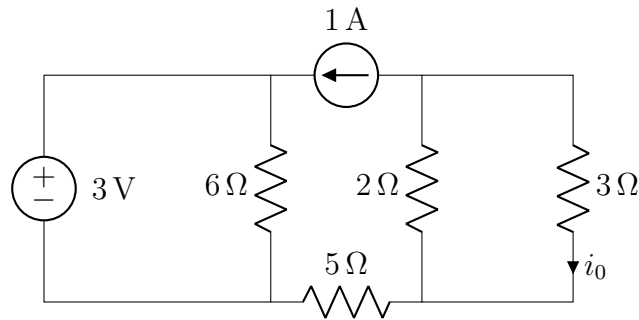
3. Use Thevenin's theorem to determine i_o .



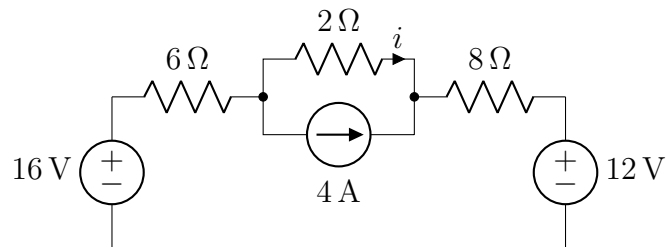
4. Determine current i through 2Ω resistor by building Thevenin's equivalent for the rest of the circuit.



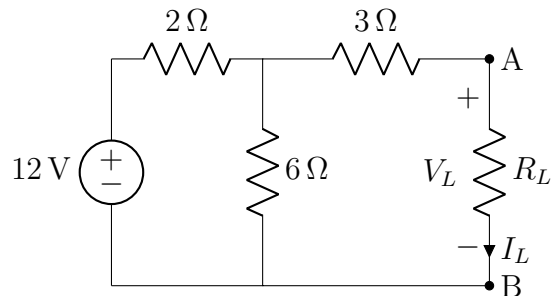
5. Find Voltage V_L across the load resistor R_L , and the current I_L flowing through the load resistor R_L , in the below circuit, by using Norton's Theorem. Where $R_L = 1.5\Omega$.



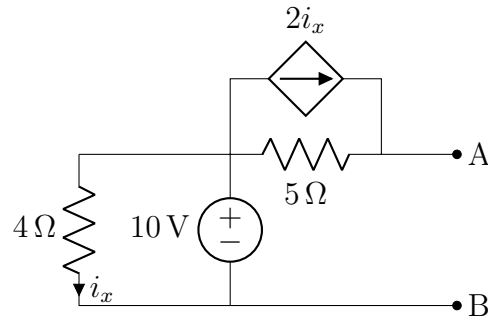6. Find the Norton resistance R_N , and the Norton current I_N , at the terminals $A - B$.



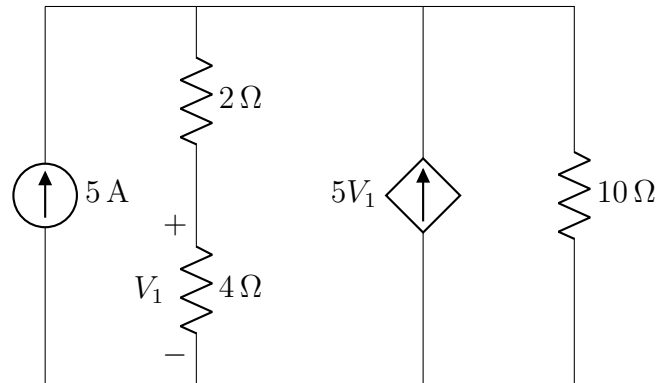7. Determine the power dissipated in the 10Ω resistor in the following circuit



8. A practical current source provides $10W$ to 250Ω load and, $20W$ to 80Ω load. A resistance R_L with voltage v_L across it, and with current i_L through it, is connected to the source. Find the values of R_L , v_L , and i_L if,
- $v_L \cdot i_L$ is maximum.
 - v_L is maximum.
 - i_L is maximum.
9. Determine the value of R_L in the below circuit, such that maximum power is delivered into R_L . Calculate the value of the maximum power.

