
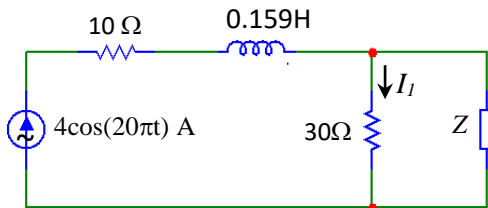


Assignment-4

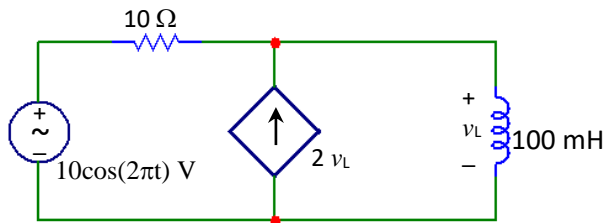
1. Determine the value of the impedance Z in the following circuit if the current $I_I = (2.56 + j1.92)\text{A}$.



2. Determine the voltage v_L across the inductor in the following circuit, and the average power supplied by the dependent current source.



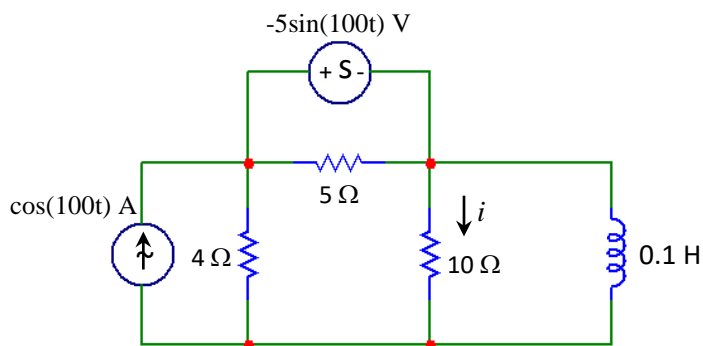3. Determine the current $i(t)$ through the 10Ω resistor.




4. Draw the Bode magnitude plot for the following transfer functions.

$$(a) \quad H(j\omega) = \frac{200 j\omega}{(j\omega + 2)(j\omega + 10)}$$

$$(b) \quad H(j\omega) = \frac{(j\omega)^2(j\omega + 100)}{(j\omega + 1)(j\omega + 10)(j\omega + 1000)}$$

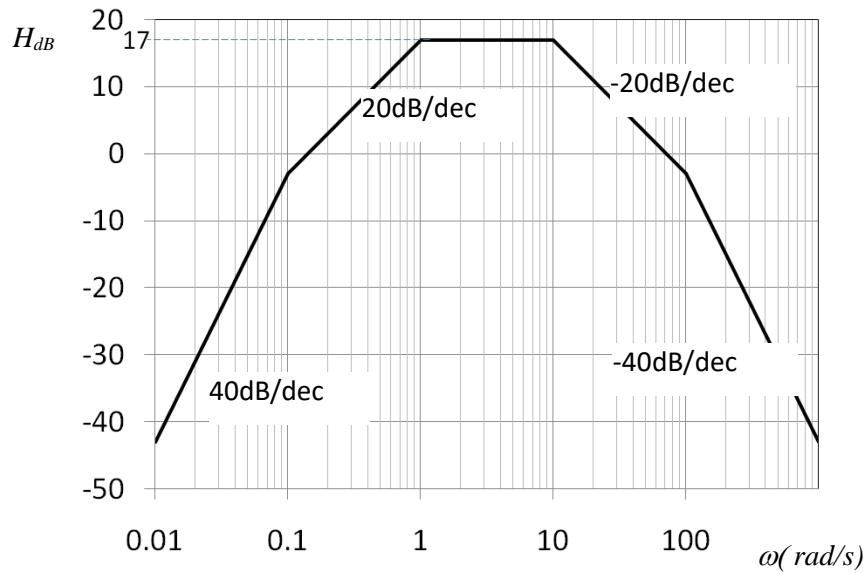5. Find the transfer function for the following Bode plot.



6. Determine the transfer function (V_o/V_s) for the following circuit.

